



Erasmus+

E(rasmus) M(undus) on I(nnovative) M(icrowave)  
Electronics and O(ptics) M(aster)



# **Semester S1**

## **Foundations of electromagnetic wave propagation**

### **TUTORIAL 2**


### **TRANSIENT STATE PROPAGATION COMPUTATION**

A lossless transmission line (propagation constant  $\beta$ , characteristic impedance  $Z_c$ , length  $l$ ) is loaded at its input by a generator (internal impedance  $Z_g$ , EMF  $E_g$ ) and at its output on the load  $Z_L$ .

We consider :

- $Z_g = Z_c = 50 \Omega$
- $Z_L$  is the impedance of an open circuit
- $E_g(p)$  is the Laplace transform of the Heaviside function

**Figure 1**

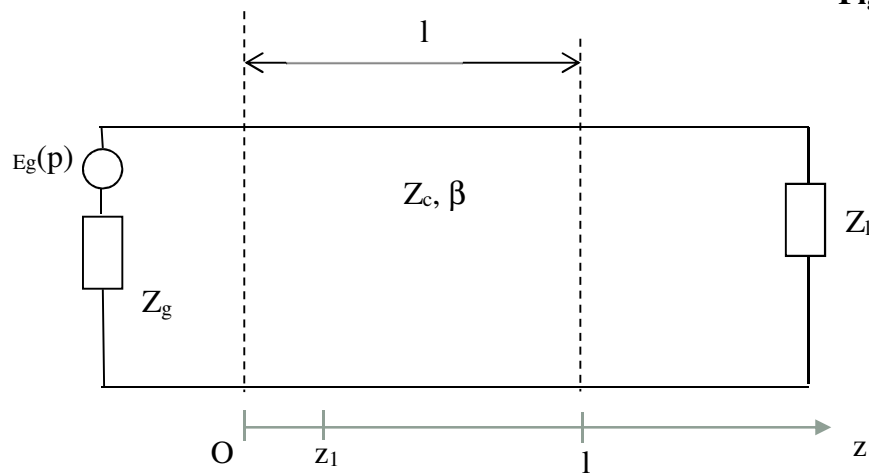

Applying the formula given in the lesson, compute the voltage  $v(z,t)$  and the current  $i(z,t)$ .

Draw these voltage and current at the  $z_1$  point.