

Lecture 1

1

What, When, Why measure

a) When

- During design phase
- During prototyping phase
- During production engineering
- While bringing new equipment/system into service
- Operating installations
- Maintaining installations

a) What


→ We measure all and only the parameters that are indispensable to reach the goal

Remember: it costs

a) In Telecommunications

- Large number of technologies SW/HW
Electrical, optical, mechanical, thermal quantities
- Complex systems
reliability important
self diagnosis of faults necessary
- Installations extend thousands of kilometers
- Very high speed signals
- Analog and digital signals

a) ISO/OSI model

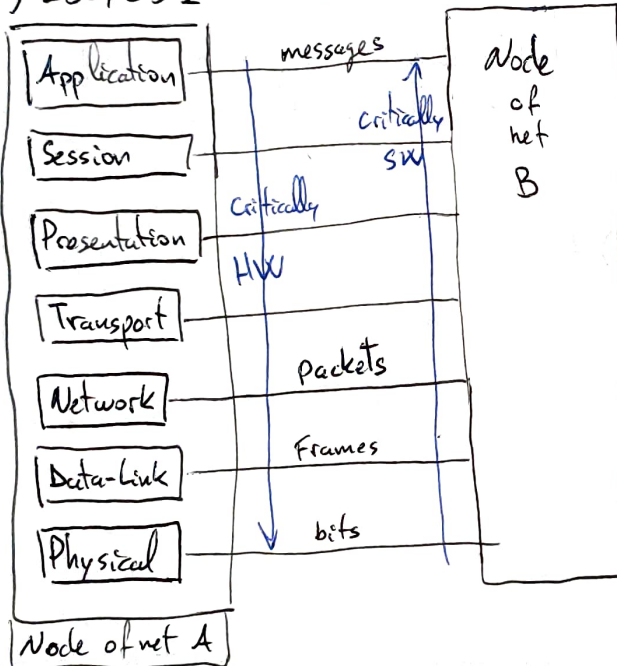

a) Layers

→ Physical (Layer 1)

- * cabling technology (copper, fiber)
- * wireless tech
- * network topology (bus, ring)
- * standards

→ Layers (2-6)

- * Test procedures to prove efficacy of network
- * Mainly (not exclusively) SW tech


→ Application (Layer 7)

- * application oriented test like specifications checking

a) Quality of service

- * User POV
response time, quality of image
- * operator POV
- finding measurable quantities correlated to the quality of
- monitoring quantities

Measuring Chain

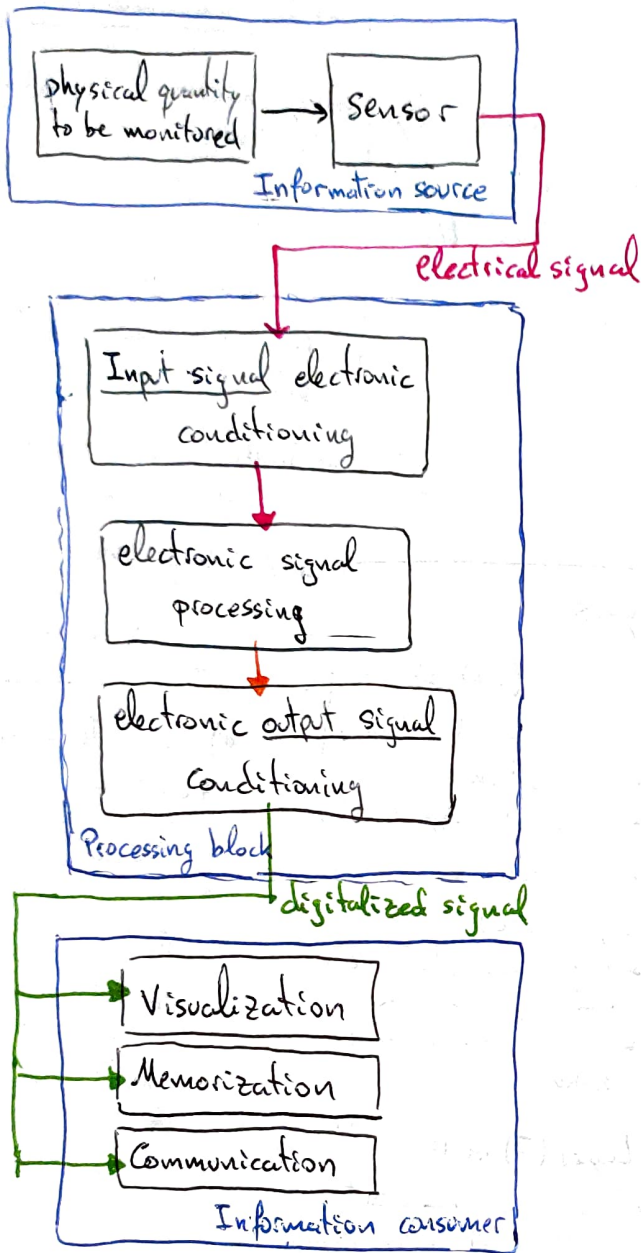

o) To measure a physical quantity we need a sensor that converts this phy. qu. to an electric signal (voltage or current)

o) Then we want to process this signal. The output of the sensor will be the input of the processing chain

For instance, the signal could be low, so we prepare the signal to make it visible for the user.

o) Finally make this signal available for the user

o) Signal Processing

→ Analog Processing

- linear amplif., addition, difference
- integration, derivation, linear filtering
- non-linear amplif., multiplication, division
- Scansion

→ Analog to dig. conversion

- sampling
- conversion


→ Digital processing

- Hardware
- Software

OPAMP

2

a) Model

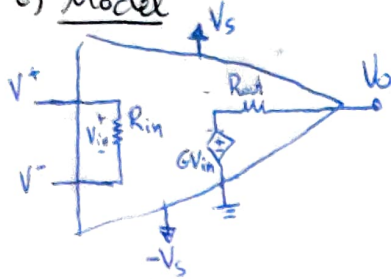


$$V_o = G(V^+ - V^-)$$

* Open loop: Gain is very large it reaches saturation
It acts as a **comparator**

- * Active device (needs voltage supply)
- * Non-linear

b) Ideal opamp

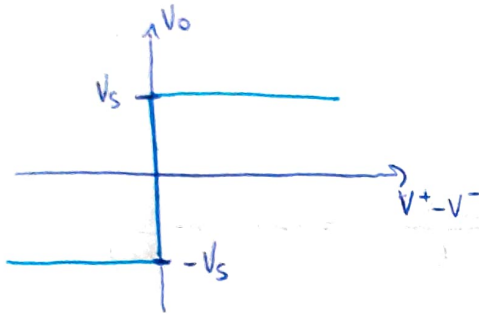


Input-output characteristics

$$\begin{aligned} G &= \infty \\ R_{in} &= \infty \Rightarrow i_{in} = 0 \\ R_{out} &= 0 \\ BW &= \infty \end{aligned}$$

c) Real Opamp

Input-output characteristics

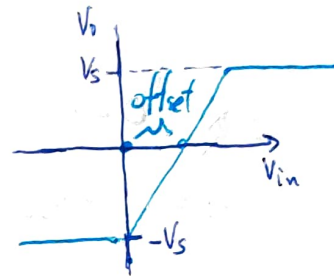

depends on freq

$G = \text{very high}$


$R_{in} = \text{very high}$

$R_{out} = \text{very small}$

→ Response time different from zero

→ There is an offset

d) Closed loop

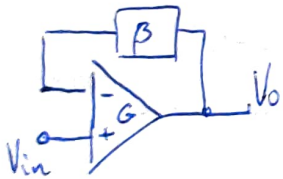

* Put a portion of the output in the inverted input

* Transfer function: Relation between input and output

$$T(s) = \frac{V_o(s)}{V_{in}(s)}$$

* Open loop: $G_{loop} = -G \cdot \beta$

* Closed loop

Transfer function

$$T(s) = \frac{G(s)}{1 - G_{loop}} = \frac{G(s)}{1 + G(s)\beta(s)}$$


* Ideal opamp \Rightarrow Independent from freq.

* $G \rightarrow \infty \Rightarrow T(s) \approx \frac{1}{\beta} \rightarrow V_o = \frac{1}{\beta} V_{in} \quad \beta \neq 0$ otherwise saturation at output

$\Rightarrow V^+ - V^- \approx 0 \rightarrow$ when there is feedback opamp the voltage difference at input is zero \Rightarrow **Voltage follower** (buffer)

$$\beta = 1$$


Non-Inverting Amplifier

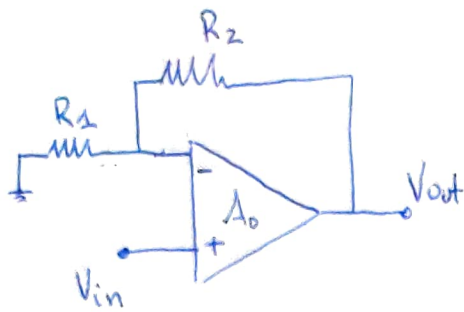

$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$

- * A_0 small
- * gain $< 10^2 - 10^3$
- * $R_2 \in [2, 100] k\Omega$
- * Z_{in} very high

* Solving

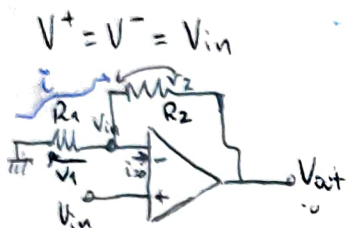

$$V_1 = 0 - V_{in}$$


$$V_2 = V_{in} - V_{out}$$

$$i = \frac{V_1}{R_1} = \frac{V_2}{R_2}$$

$$\frac{0 - V_{in}}{R_1} = \frac{V_{in} - V_{out}}{R_2} \Rightarrow -V_{in} \left(1 + \frac{R_2}{R_1}\right) = -V_{out}$$

$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$


Inverting Amplifier

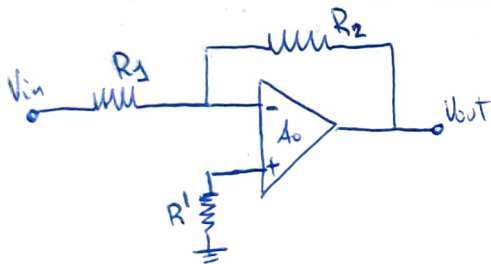

$$V_{out} = - \frac{R_2}{R_1} V_{in}$$

- * A_0 small
- * gain $\in [0, 1 - 10^3]$
- * Z_{in} relatively low

* Solving

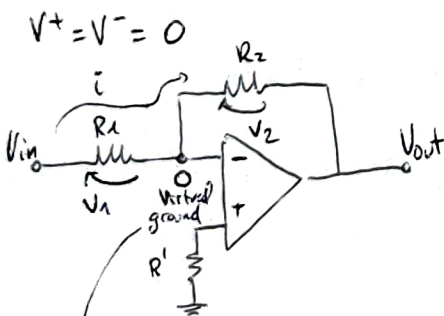

$$V_1 = \frac{V_{in} - 0}{R_1}$$

$$V_2 = \frac{0 - V_{out}}{R_2}$$


$$i = \frac{V_1}{R_1} = \frac{V_2}{R_2}$$

$$\frac{V_{in} - 0}{R_1} = \frac{0 - V_{out}}{R_2} \Rightarrow$$

$$V_{out} = - \frac{R_2}{R_1} V_{in}$$

We cannot put a ground!
it is the feedback loop
that maintains this voltage = 0V

Difference Amplifier

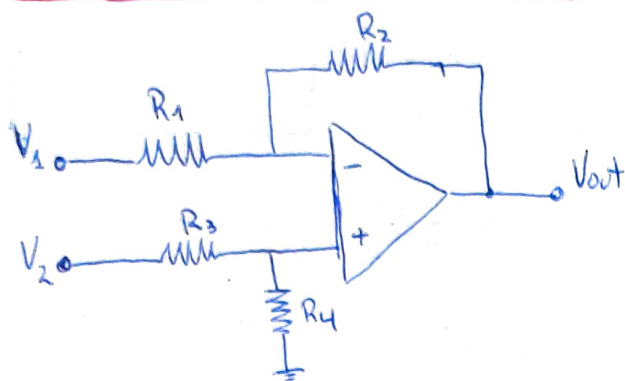


$$R_1 = R_3 \text{ \& } R_2 = R_4$$

$$V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$$

* Z_{in} from V_1
 $Z_{in} = R_1$

* Z_{in} from V_2

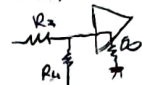


$$Z_{in} = R_3 + R_4$$

* Unbalanced difference amplified at inputs

* Solving


1) If I switch off V_2 : \Rightarrow I have the inverting amplifier: $V_{o1} = -\frac{R_2}{R_1} V_1$

2) If I switch off V_1 : \Rightarrow

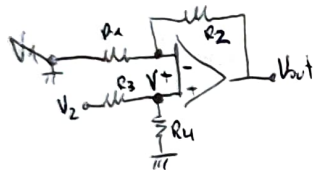

For V^+ I have
 non-inverted amplifier
 \Rightarrow I get V^+ as
 a voltage divider
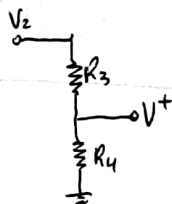
$$V_{o2} = \frac{R_4}{R_3 + R_4} \cdot V_2 \cdot \left(1 + \frac{R_2}{R_1}\right)$$



$$V_2 = I (R_3 + R_4)$$

$$I = \frac{V^+ - 0}{R_4}$$

$$V^+ = \frac{R_4}{R_3 + R_4} V_2$$

3) Add the solutions

$$V_{out} = V_{o1} + V_{o2} = -\frac{R_2}{R_1} V_1 + \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1}\right) V_2$$

$$V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$$


$$R_1 = R_3$$

$$\downarrow$$

$$R_2 = R_4$$

$$= -\frac{R_2}{R_1} V_1 + \frac{R_2}{R_1 + R_4} \left(\frac{R_1 + R_2}{R_1}\right) V_2$$

Common Mode Rejection Ratio (CMRR)

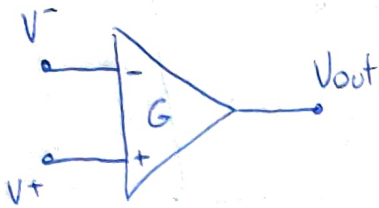

The gain could be not equal for V^+ and $V^- \Rightarrow$

$$V_{out} = G^+ V^+ - G^- V^-$$

Differential gain $\Rightarrow G_D = \frac{G^+ + G^-}{2}$

Common mode gain $\Rightarrow G_C = \frac{G^+ - G^-}{2}$

o) Common mode Rejection Ratio :

$$CMRR = \frac{G_D}{G_C}$$

* Ideal opamp: $CMRR \rightarrow \infty$


* In db: $CMRR = 20 \log \left(\frac{G_D}{G_C} \right)$

o) Output:

$$V_{out} = G_D (V^+ - V^-) + G_C \left(\frac{V^+ + V^-}{2} \right)$$

Common mode voltage

Instrumentation Amplifier

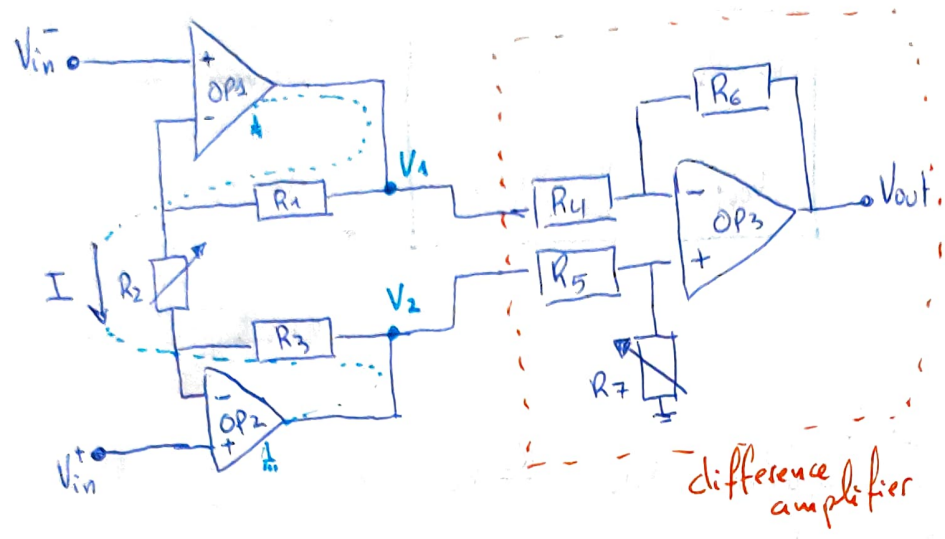

$R_1 = R_3, R_5 = R_4, R_6 = R_7$

$$V_{out} = \frac{R_6}{R_4} \left(1 + \frac{2R_1}{R_2} \right) (V_{in}^+ - V_{in}^-)$$

* Solving

$$I = \frac{V_{in}^- - V_{in}^+}{R_2}$$

Drop voltages

$V_1 = V_{in}^- + V_a = V_{in}^- + R_1 \cdot I$

$V_2 = V_{in}^+ - V_b = V_{in}^+ - R_3 \cdot I$

o) Using difference ampli results

$$V_{out} = V_2 \underbrace{\frac{R_7}{R_5 + R_7} \left(1 + \frac{R_6}{R_4} \right)}_{G^+} - V_1 \underbrace{\frac{R_6}{R_4}}_{G^-}$$

If we put all together (current, drop voltages) we get Vout


To get the best CMRR we just need to tune one of the resistance: R_4, R_5, R_6, R_7
 To adjust the total gain we just need to tune one resistance: R_2

Independently

* Equivalent impedance from $V_{in}^+ \rightarrow Z_{in} = \infty$
 $V_{in}^- \rightarrow Z_{in} = \infty$

* Usually the information is in voltage difference

Summing Amplifier

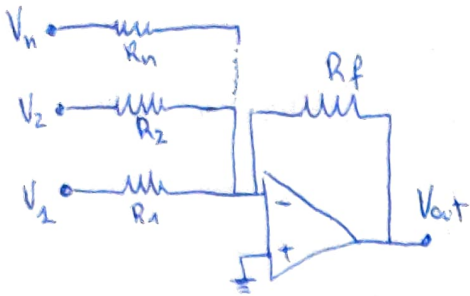

$$R_1 = R_2 = \dots = R_n = R$$

$$V_{out} = - \frac{R_f}{R_1} \sum_{i=1}^n V_i$$

* To get very accurate summer, means same voltage in, we have to tune resistance

* To avoid the minus we add another block




* Solving

We switch off all voltages except one. We do that with all of voltages

We get the inverting amplifier
 $V_1 \neq 0 \quad V_2 = \dots = V_n = 0$

$$V_{out1} = - \frac{R_f}{R_1} V_1 \Rightarrow V_{out} = - \frac{R_f}{R_1} V_1 - \frac{R_f}{R_2} V_2 \dots$$

Integrator

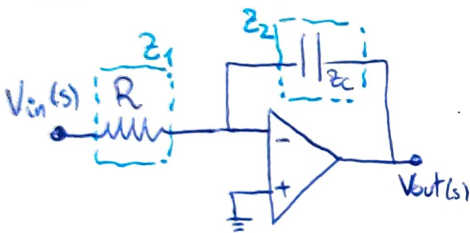

$$V_{out}(s) = - \frac{1}{sC} \cdot \frac{1}{R} V_{in}(s)$$


$\frac{1}{s} \rightarrow$ integration operator in time dom.

$$V_{out}(t) = - \frac{1}{RC} \int_0^t V_{in}(\tau) d\tau + V_0$$

Zero if we use switch to start the integration at $t=0$ $\left[\frac{1}{s} \right]_{\text{open}}$

* We use Laplace domain

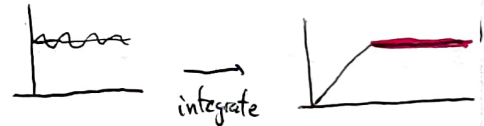
* Problem: If there is DC component the output will saturate



* Solving: Inverting amplif.

$$V_{out} = - \frac{Z_2}{Z_1} V_{in}, \quad Z_c = \frac{1}{sC}$$

\Rightarrow Approximate integrator

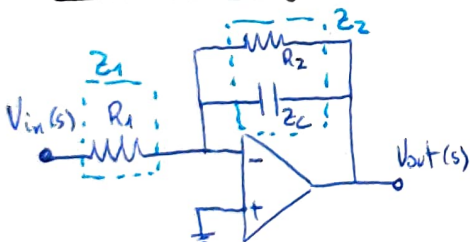

$$V_{out}(s) = - \frac{R_2}{R_1} \left(\frac{1}{1 + sCR_2} \right) V_{in}(s)$$


* Now it will behave like amplifier for $s=0$
 $(s=0 \Rightarrow Z_c = \infty \Rightarrow R_2 \parallel Z_c = R_2)$
 $(s=0 \text{ is DC component})$

* Solving

$$Z_2 = R_2 \parallel Z_c = \frac{R_2 \cdot \frac{1}{sC}}{R_2 + \frac{1}{sC}} = \frac{\frac{R_2}{sC}}{\frac{sCR_2 + 1}{sC}} = \frac{R_2}{sCR_2 + 1}$$


$$V_{out} = - \frac{Z_2}{Z_1} V_{in} = - \frac{R_2}{R_1} \cdot \frac{1}{(1 + sCR_2)} V_{in}$$

* Bode:

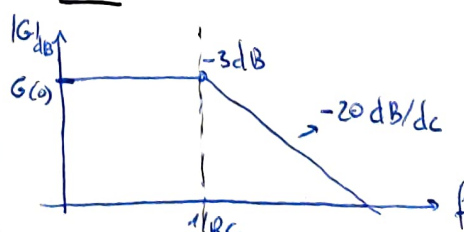

Very low freqs is an amplifier | For high freqs it is work as an integrator

Differentiator

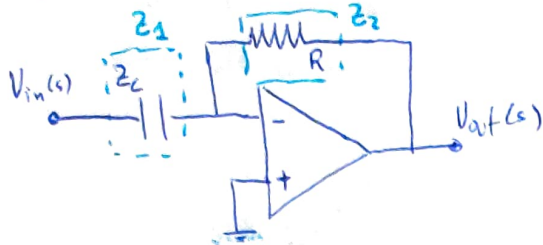

$$V_{out}(s) = -sCR V_{in}(s)$$

$s \rightarrow$ derivation operator in time dom.

$$V_{out}(t) = -RC \frac{dV_{in}(t)}{dt}$$

⊛ The good performance of the circuit depends on the BW


Some freqs. could lead to instability (oscillation)

⊛ Solving the problem

- Add small resistor in series with the capacitor

Opamp: Small signals behaviour

A better model for real opamp

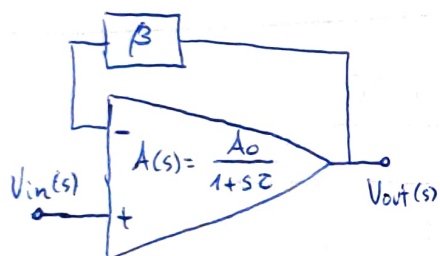

Same transfer function: $T(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{A(s)}{1 + \beta A(s)}$

Solving:


$$T(s) = \frac{A_0}{1 + sC} \cdot \frac{1}{1 + \frac{\beta A_0}{1 + sC}} = \frac{A_0}{1 + sC + \beta A_0} = \frac{A_0'}{1 + \beta A_0} \cdot \frac{1}{1 + s \frac{C}{1 + \beta A_0}}$$

* The gain is reduced

* The pole is shifted

$$A_0' \cdot \frac{1}{C'} = A_0 \cdot \frac{1}{C} = \text{constant}$$

* Bandwidth gain product is a specification of ampli.

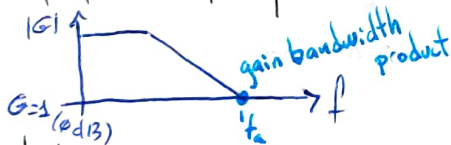

* Prob 1

We want $G=10$

We have gain BW prod = 1 MHz

$$\text{BW} ? \Rightarrow G \times \text{BW} = C \Rightarrow \text{BW} = \frac{C}{G} = \frac{1 \text{ MHz}}{10}$$

$$\Rightarrow \text{BW} = 100 \text{ kHz}$$

* Prob 2

We want $\text{BW} = 200 \text{ kHz}$

We want $G = 10$

G-BW prod = 1 MHz

We need at least two stages



$$\begin{aligned} \text{stage 1: } G_1 &= \sqrt{10} \\ \text{stage 2: } G_2 &= \sqrt{10} \end{aligned} \Rightarrow G_{\text{tot}} = G_1 \cdot G_2 = 10$$

stage 1



$$G \cdot \text{BW} = \sqrt{10} \cdot 200 \text{ kHz} < 1 \text{ MHz} \checkmark$$

* This product: Gain \times BW = constant is independent of the configuration of amplifier (β affects the amplification and band pass the same way)


Filters

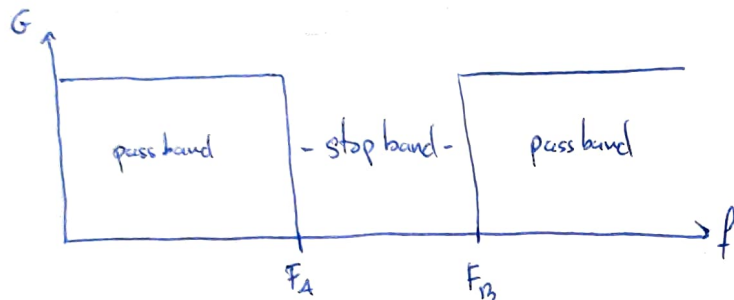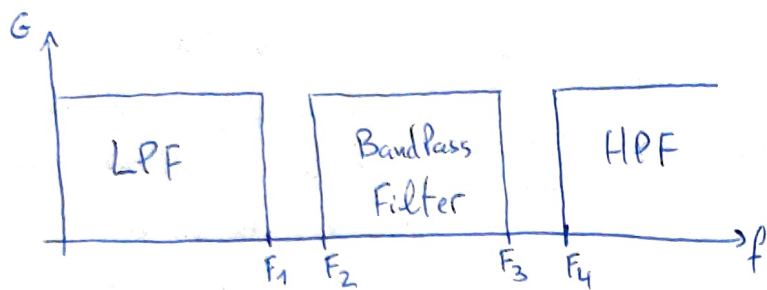

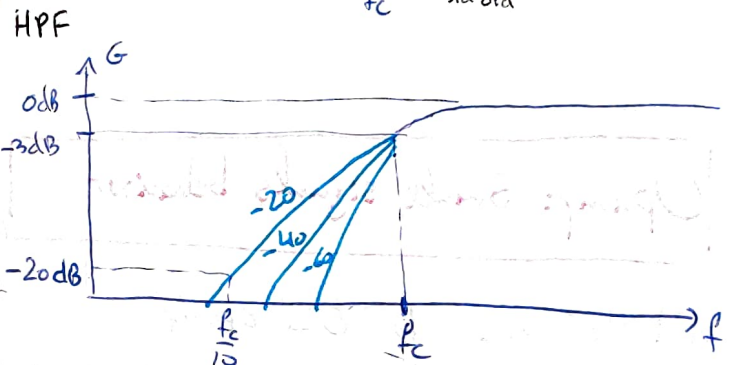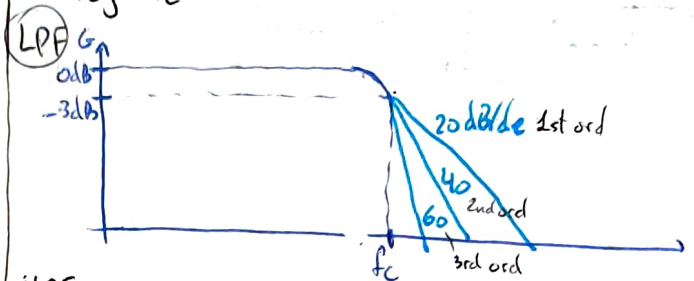HPF
* We characterise the LPF by the slope of transfer functions in the cut-off region



2nd order LPF

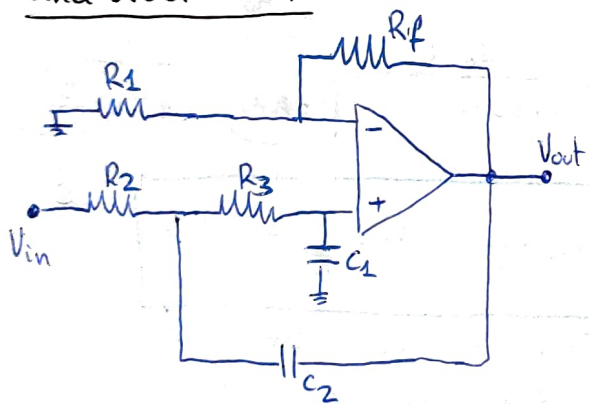

2nd order HPF

