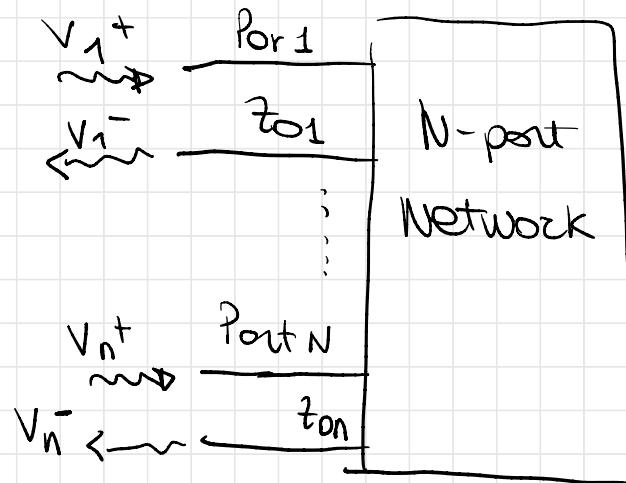


MICROWAVE ENGINEERING

lecture 20: Generalized
S parameters,
ABCD Matrix,
Discontinuities and
Modal Analysis

Generalized S parameters



At each port we will

define :

$$a_n = \frac{V_n^+}{\sqrt{z_{0n}}}$$

$$b_n = \frac{V_n^-}{\sqrt{z_{0n}}}$$

$$V_n = V_n^+ + V_n^- = \sqrt{z_{0n}} (a_n + b_n)$$

$$I_n = \frac{1}{z_{0n}} (V_n^+ - V_n^-) = \frac{1}{z_{0n}} (a_n - b_n)$$

The average power delivered at the n^{th} port : purely magnetic


$$P_n = \frac{1}{2} \operatorname{Re}\{V_n I_n^*\} = \frac{1}{2} \operatorname{Re} \left\{ |a_n|^2 - |b_n|^2 + (b_n a_n^* - b_n^* a_n) \right\}$$

$$= \frac{1}{2} |a_n|^2 - \frac{1}{2} |b_n|^2 \quad \leftarrow \text{Power delivered} = \text{incident power} - \text{reflected power}$$

The generalized $[S]$ matrix is :

$$[b] = [S][a] \quad \text{where } S_{ij} = \frac{b_i}{a_j} \begin{cases} = \frac{V_i - \sqrt{Z_0}j}{V_j + \sqrt{Z_0}i} & \text{for } k \neq j \\ 0 & \text{for } k = j \end{cases}$$

The ABCD (Transmission) matrix:

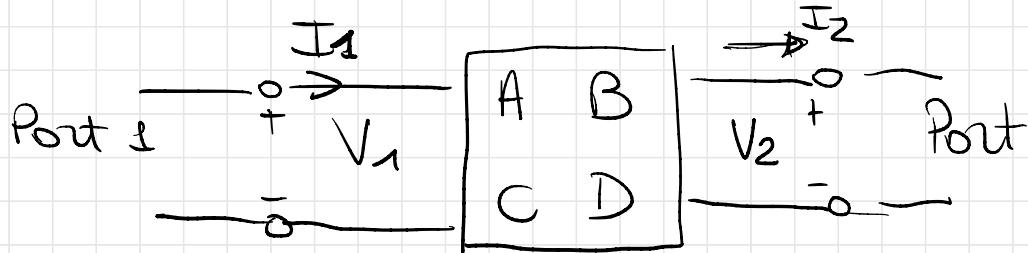

$$V_1 = A V_2 + B I_2$$

$$I_1 = C V_2 + D I_2$$




$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

If I have M networks

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \cdots \begin{bmatrix} A_n & B_n \\ C_n & D_n \end{bmatrix} \begin{bmatrix} V_m \\ I_m \end{bmatrix}$$

Useful Examples

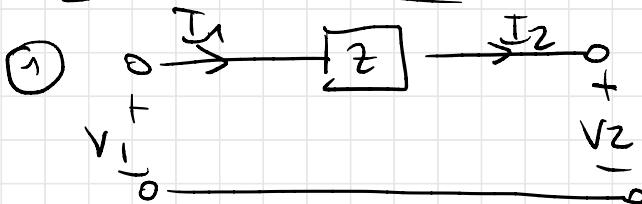

$$A = 1 \quad B = 2$$

$$C = 0 \quad D = 1$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = 1$$


$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = 0$$

$$B = \left. \frac{V_1}{I_2} \right|_{V_2=0} = \frac{V_1}{V_2} = 2$$

$$D = \left. \frac{I_1}{I_2} \right|_{V_2=0} = \frac{I_1}{I_2} = 1$$

$$\begin{bmatrix} 1 & 2 \\ 0 & 1 \end{bmatrix}$$


②

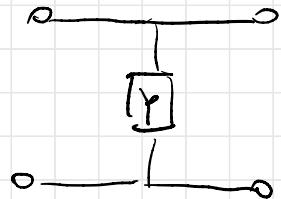

$$A = 1 \quad B = 0$$

$$C = Y \quad D = 1$$


③

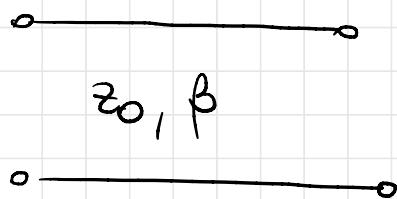

$$A = \cos \beta z_0 \quad B = j z_0 \sin \beta$$

$$C = j z_0 \sin \beta \quad D = \cos \beta z_0$$


④

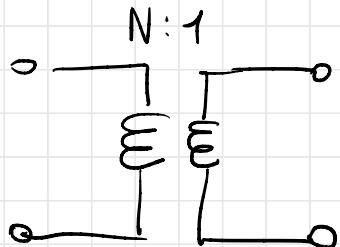

$$A = N \quad B = 0$$

$$C = 0 \quad D = \frac{L}{N}$$

⑤ Pi-Network

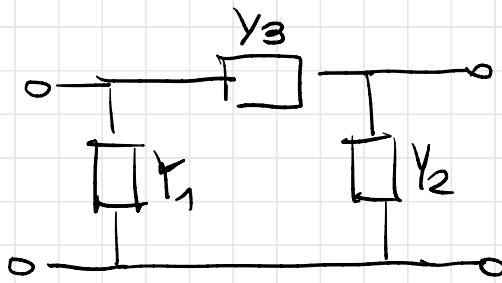


$$A = 1 + \frac{Y_2}{Y_3}$$

$$B = \frac{1}{Y_3}$$

$$C = Y_1 + Y_2 + \frac{Y_1 Y_2}{Y_3}$$

$$D = 1 + \frac{Y_1}{Y_3}$$

⑥ T-network

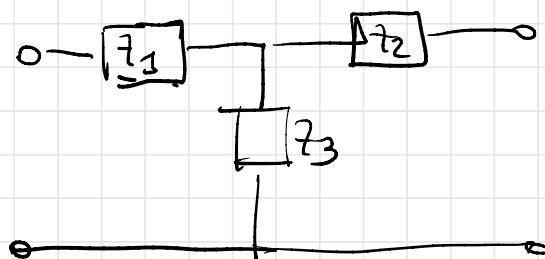

$$A = 1 + \frac{Z_1}{Z_3}$$

$$B = Z_1 + Z_2 + \frac{Z_1 Z_2}{Z_3}$$

$$C = \frac{1}{Z_3}$$

$$D = 1 + \frac{Z_2}{Z_3}$$

Relation between ABCD and Z matrix

For Zmatrix

$$\left\{ \begin{array}{l} V_1 = I_1 Z_{11} - I_2 Z_{12} \\ V_2 = I_1 Z_{21} - I_2 Z_{22} \end{array} \right.$$

$$A = \frac{V_1}{V_2} \Big|_{I_2=0} = \frac{Z_{11}}{Z_{21}}$$

$$B = \frac{V_1}{I_2} \Big|_{V_2=0} = \frac{I_1 Z_{11} - I_2 Z_{12}}{I_2} = Z_{11} \frac{I_1}{I_2} \Big|_{V_2=0} - Z_{12} =$$

$$= z_{11} \frac{\cancel{z_1 z_{22}}}{\cancel{z_1 z_{21}}} - z_{12} = \frac{z_{11} z_{22} - z_{12} z_{21}}{\cancel{z_{21}}}$$

$$C = \frac{I_1}{V_2} \Big|_{I_2=0} = \frac{1}{z_{21}}$$


$$D = \frac{I_1}{I_2} \Big|_{V_2=0} = \frac{z_{22}}{z_{21}}$$

If the network is reciprocal we know $z_{12} = z_{21}$ and it gives



$$\boxed{AD - BC = 1}$$

DISCONTINUITIES AND MODAL ANALYSIS


Rectangular waveguides



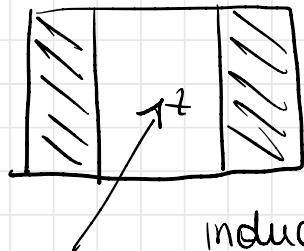


inductive shapheogen

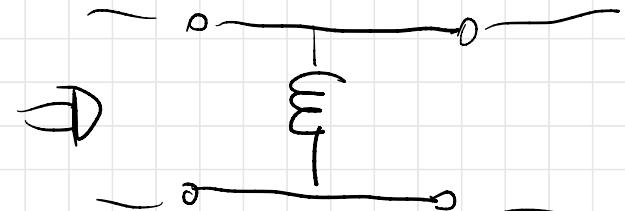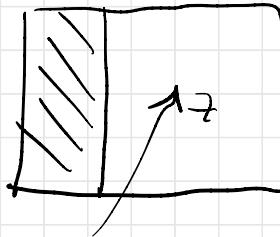


capactive shapheogen

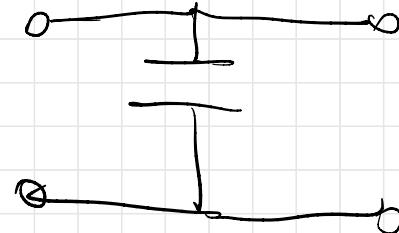


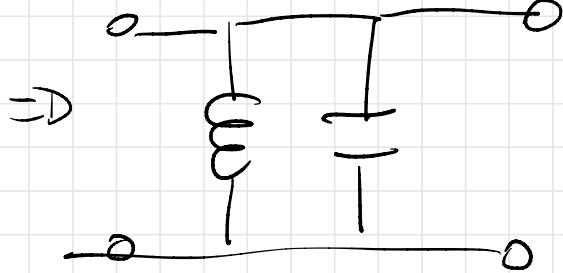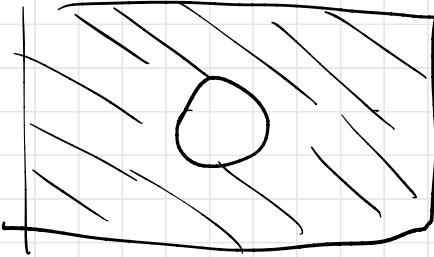
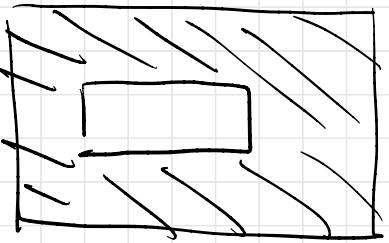


Resonant
in series

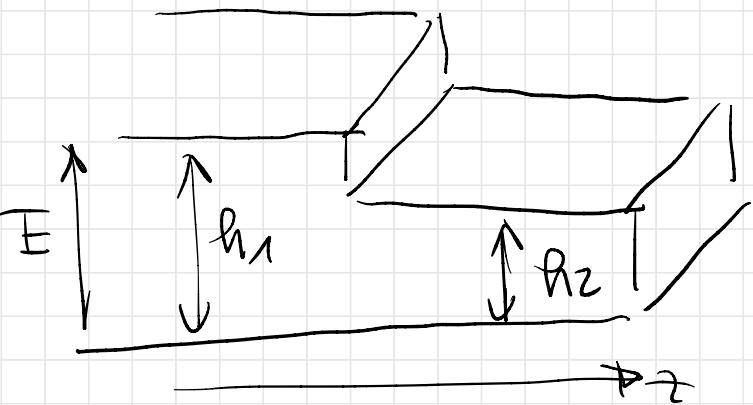


change in
height

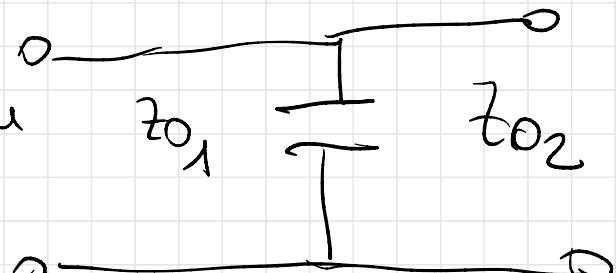

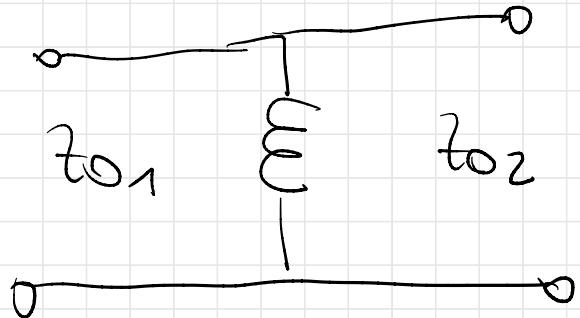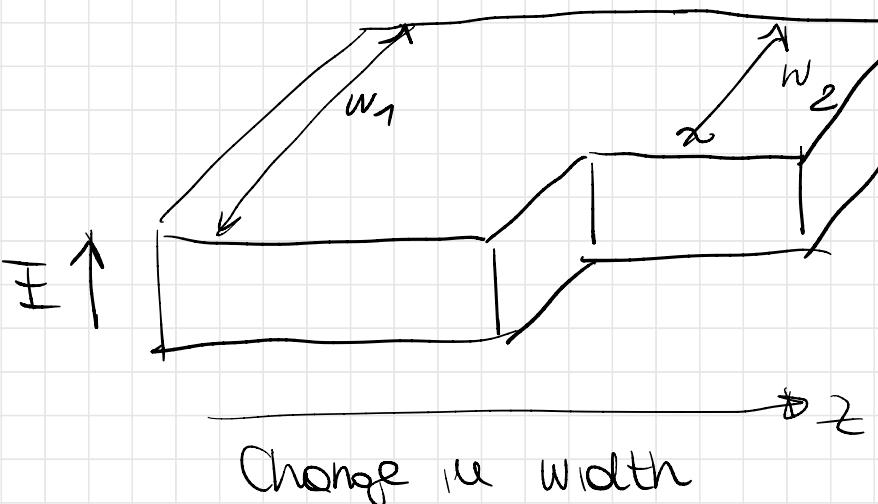


Change in width

Model analysis

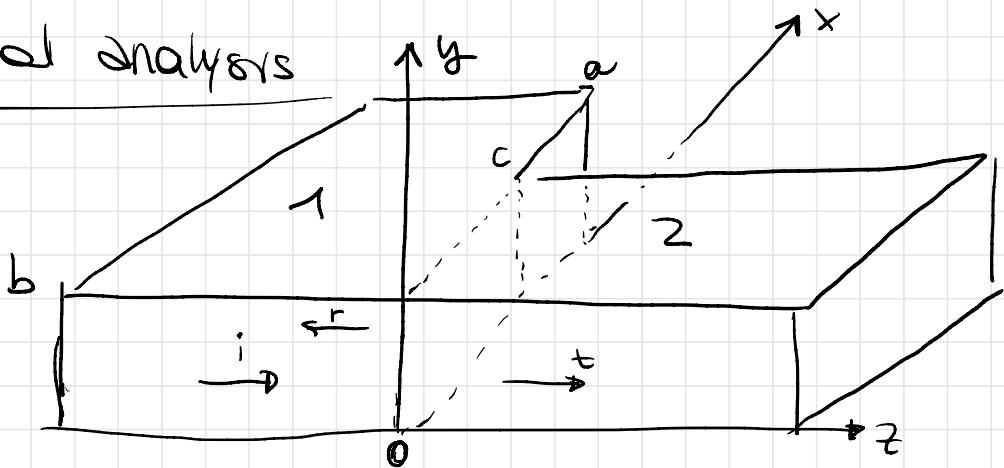

CHANGE IN
WIDTH

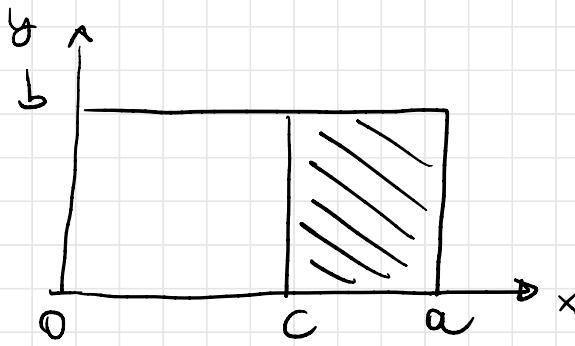

For $z < 0$ we assume only TE₁₀ mode propagating.

For $z > 0$ we assume NO modes are propagating

For $z < 0$ the incident modes are:

$$\left\{ \begin{array}{l} E_y^i = \sin \frac{\pi x}{a} e^{-j\beta_1^a z} \\ H_x^i = -\frac{1}{Z_1} \sin \frac{\pi x}{a} e^{-j\beta_1^a z} \end{array} \right.$$

$$\beta_1^a = \sqrt{k_0^2 - \left(\frac{m\pi}{a}\right)^2}$$

TE₀₀ mode in guide

$$Z_m^a = \frac{k_0 \eta_0}{\beta_m^a}$$

Wave impedance of TE₀₀ mode
in WG 1

The reflected modes ($z < 0$)

$$E_y^r = \sum_{n=1}^{\infty} A_n \sin \frac{n\pi x}{a} e^{j\beta_n^a z}$$

$$H_x^r = \sum_{n=1}^{\infty} \frac{A_n}{Z_m^a} \sin \frac{n\pi x}{a} e^{j\beta_m^a z}$$

The transmitted modes are ($z > 0$)

$$\bar{E}_y^t = \sum_{n=1}^{\infty} B_n \sin \frac{n\pi x}{c} e^{-j\beta_n^c z}$$

$$H_n^t = \sum_{n=1}^{\infty} \frac{B_n}{Z_n^c} \sin \frac{n\pi x}{c} e^{-j\beta_n^c z}$$

$$\beta_n^c = \sqrt{k_0^2 - \left(\frac{n\pi}{c}\right)^2}$$

$$Z_n^c = \frac{k_0 \mu_0}{\beta_n^c}$$


At $z=0$ the fields must be continuous and $\bar{E}_y = 0$ for $c < x < a$

$$\left\{ \begin{array}{l} E_y = \sin \frac{\pi x}{a} + \left(\sum_{n=1}^{\infty} A_n \sin \frac{n\pi x}{a} \right) \\ H_x = -\frac{1}{Z_1} \sin \frac{\pi x}{a} + \sum_{n=1}^{\infty} \frac{A_n}{Z_n} \sin \frac{n\pi x}{a} \end{array} \right. = \begin{cases} \sum_{n=1}^{\infty} B_n \sin \frac{n\pi x}{c} & 0 \leq x < c \\ 0 & c \leq x < a \end{cases}$$

$$H_x = -\frac{1}{Z_1} \sin \frac{\pi x}{a} + \sum_{n=1}^{\infty} \frac{A_n}{Z_n} \sin \frac{n\pi x}{a} = -\sum_{n=1}^{\infty} \frac{B_n}{Z_n c} \sin \frac{n\pi x}{c}$$

$0 \leq x < c$

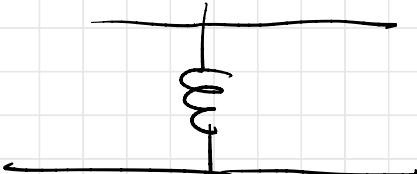
System can be solved numerically but if we assume
waveguide 2 does not support ANY MODE \rightarrow





$$X = -j Z_1 a \frac{1 + A_1}{1 - A_1}$$

A_1 is the reflection coeff. of the TE10 mode.


Microstrip discontinuities


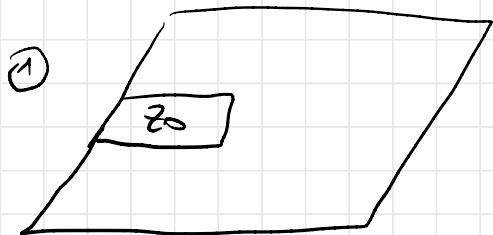


Open-ended
MS

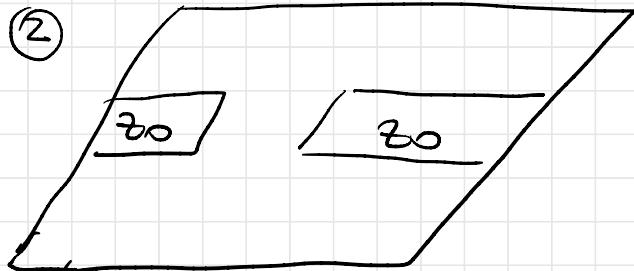
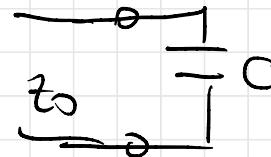


Gap in MS

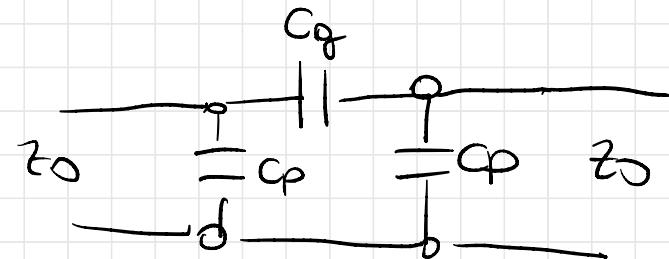

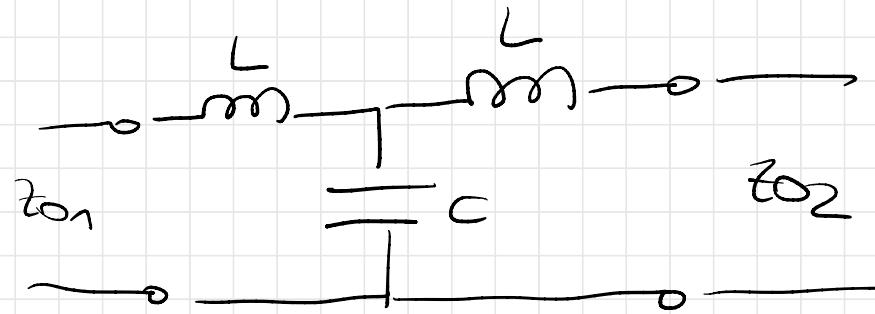
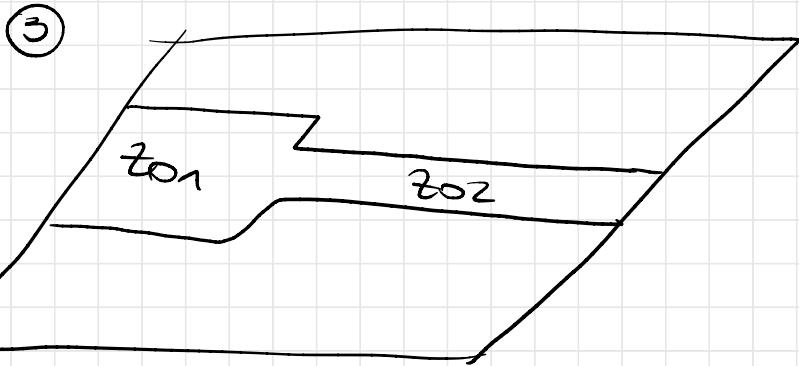


change in width

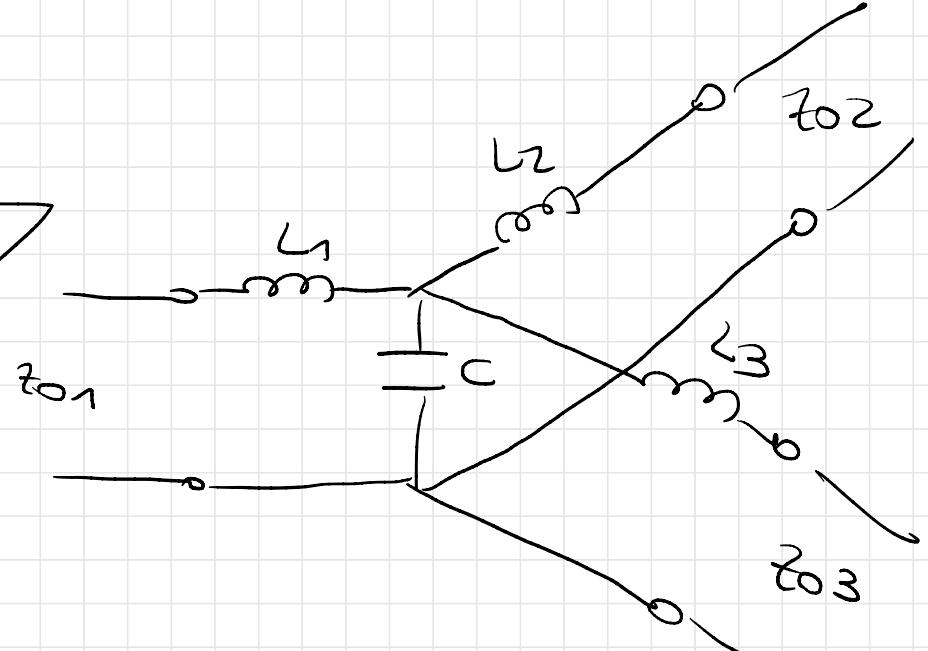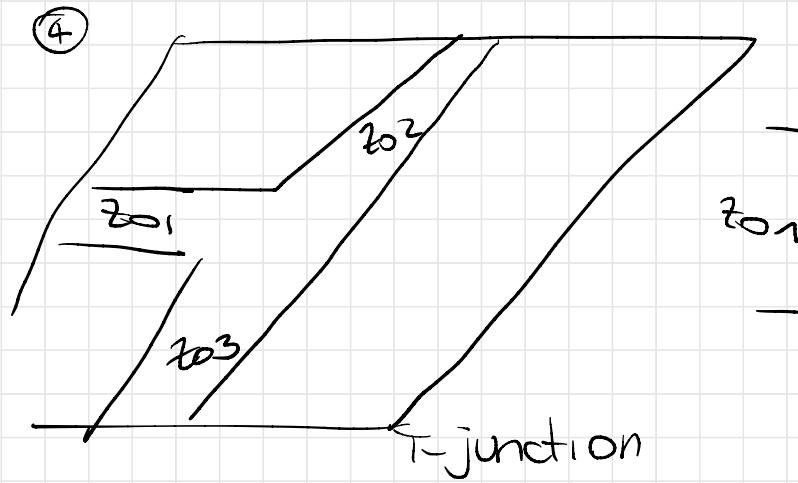

T-junction

⑤

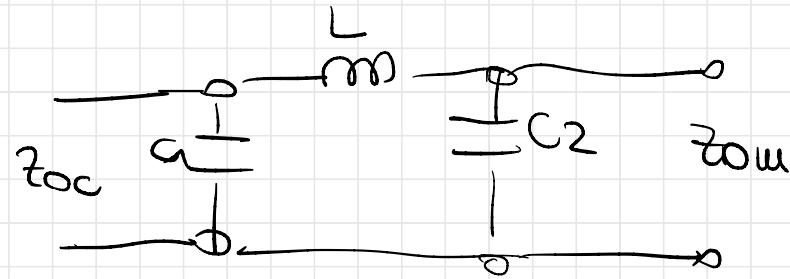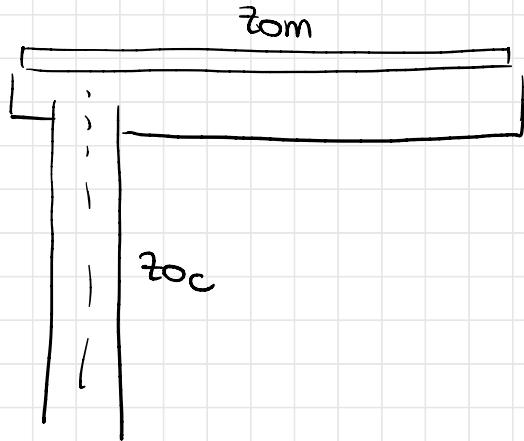

Coax - to - MS
junction