



Erasmus+

E(rasmus) M(undus) on I(nnovative) M(icrowave) E(lectronics)
and O(ptics) M(aster)



Semester S1

Basics of active and non linear electronics

RF Power amplifiers (JM Nebus)

COURSE N° 4

Module Name

Module's Author

-1-


Copyright notice : This material can be freely used within the E.M.I.M.E.O. Erasmus Mundus consortium. Explicit authorisation of the authors is required for its use outside this E.M.I.M.E.O. consortium. This learning Programme has been funded with support from the European Commission. This publication reflects the views only of the author, and the Commission cannot be held responsible for any use which may be made of the information contained therein.

Chapter IV

Power matching of microwave transistors using distributed components

I] Power matching conditions

For the simple following circuit

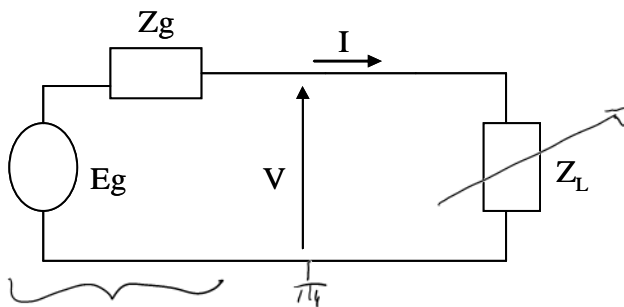

We have the following relationships

$$V = \frac{Z_L I}{Z_L + Z_G} \quad I = \frac{E_G}{Z_L + Z_G} \quad Z_L = \underbrace{R_L}_{\text{resistance}} + \underbrace{jX_L}_{\text{reactance}} \quad Z_G = R_G + jX_G$$

$$P_L = \frac{1}{2} \text{Re}(V.I^*) = \frac{1}{2} \frac{R_L E_G^2}{(R_L + R_G)^2 + (X_L + X_G)^2}$$

Max

→ If

$$\frac{\partial P_L}{\partial R_L} = 0 \quad \frac{\partial P_L}{\partial X_L} = 0$$


We have the maximum (available power) absorbed by Z_L

These derivatives are equal to 0 when $\underline{R_L = R_G}$ and $\underline{X_L = -X_G}$ so $\boxed{Z_L = Z_G^*}$


And

$$P_{L-\max} = P_{\text{available}} = \frac{1}{8} \cdot \frac{|E_G|^2}{R_G}$$

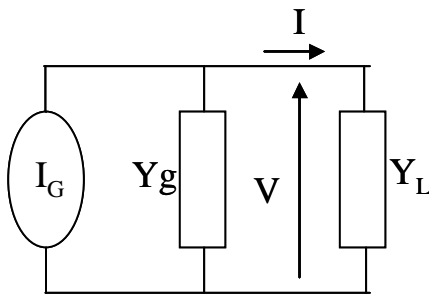
For a current generator we have the same property :




$$P_{L-\max} = P_{\text{available}} = \frac{1}{8} \cdot \frac{|I_G|^2}{G_G}$$

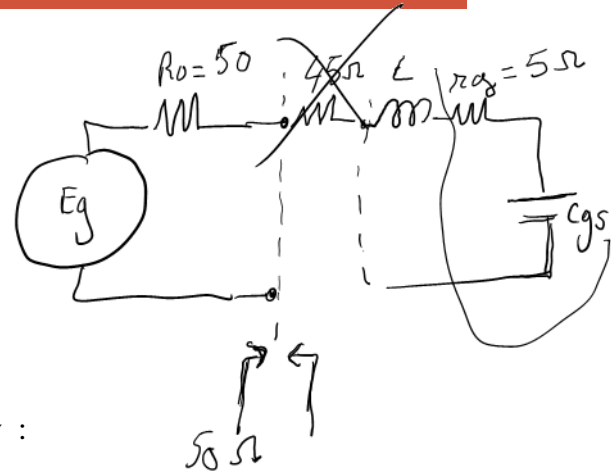

$$Y_L = G_L + jB_L$$

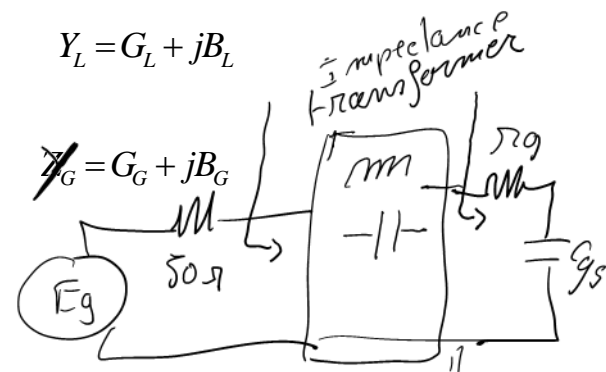

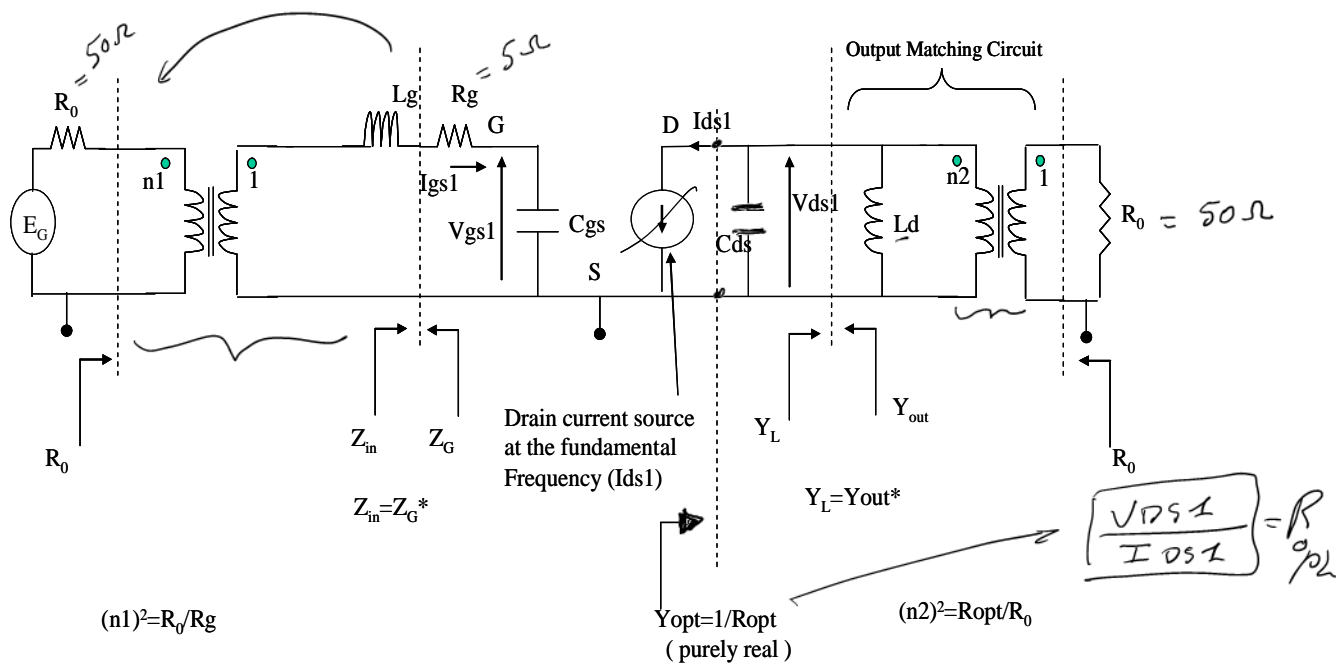II] Application to transistor's input and output matching (with ideal impedance transformers)




Module Name

Module's Author

-3-

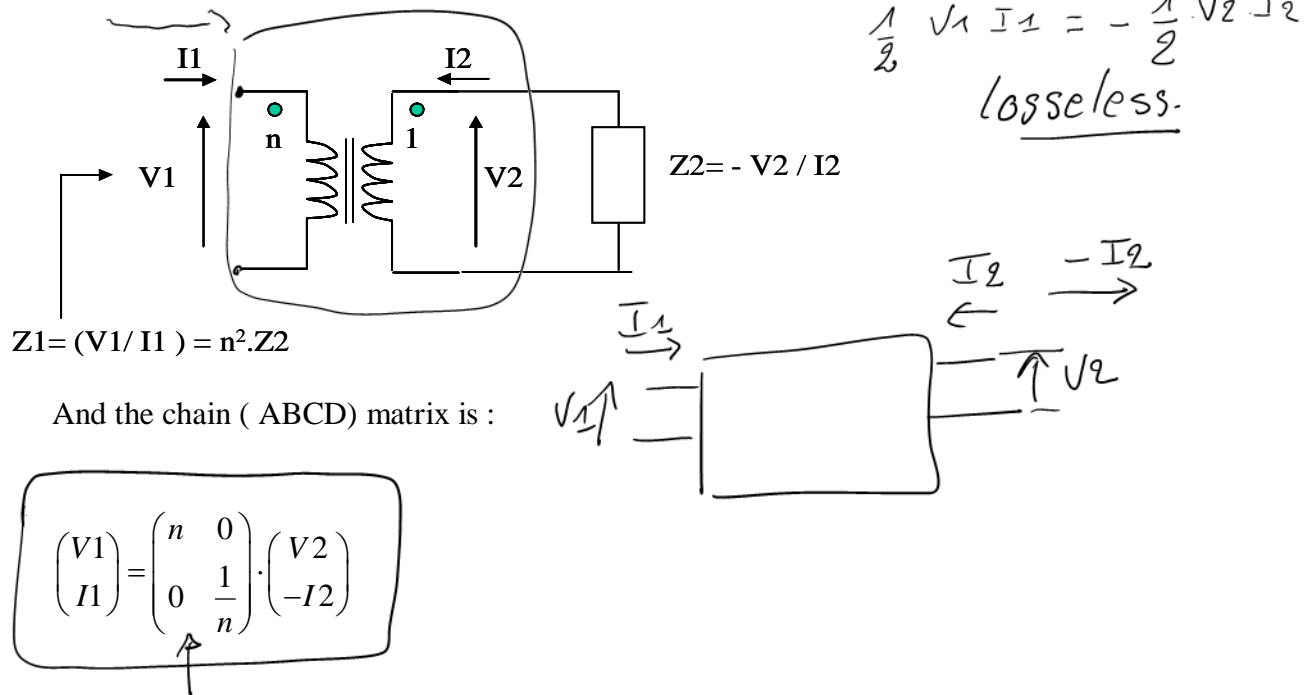
The ideal impedance transformer is represented as following



And the chain (ABCD) matrix is :

$$\begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \begin{pmatrix} n & 0 \\ 0 & \frac{1}{n} \end{pmatrix} \cdot \begin{pmatrix} V_2 \\ -I_2 \end{pmatrix}$$

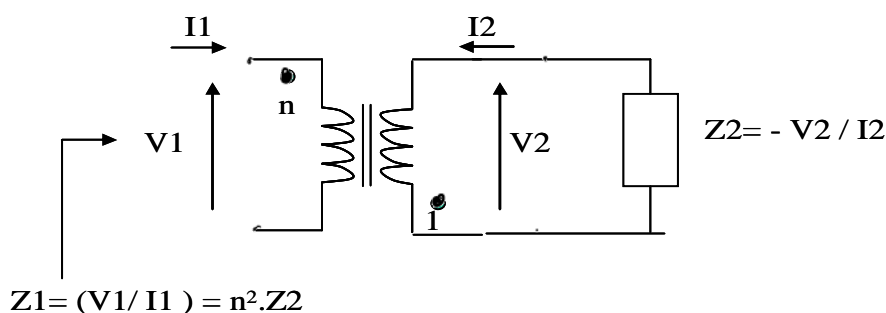We can have in a same manner an impedance transformer with 180° out of phase between input and output voltages . In this case we have the following symbolic representation and the associated chain matrix




$$\begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \begin{pmatrix} -n & 0 \\ 0 & -\frac{1}{n} \end{pmatrix} \cdot \begin{pmatrix} V_2 \\ -I_2 \end{pmatrix}$$

III] Impedance transformer with lumped capacitors and inductors

The chain matrix of a serie inductor is

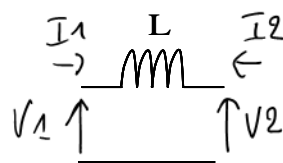
$$\begin{pmatrix} V1 \\ I1 \end{pmatrix} = \begin{pmatrix} 1 & jL\omega \\ 0 & 1 \end{pmatrix} \cdot \begin{pmatrix} V2 \\ -I2 \end{pmatrix}$$



$$\begin{aligned} V1 &= V2 + jL\omega I2 \\ V1 &= V2 - jL\omega I2 \\ I1 &= -I2 \end{aligned}$$

The chain matrix of a parallel capacitor is

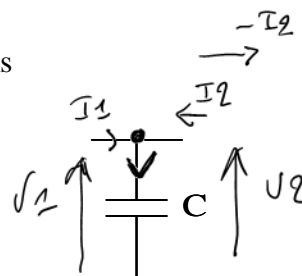
$$\begin{pmatrix} V1 \\ I1 \end{pmatrix} = \begin{pmatrix} 1 & 0 \\ jC\omega & 1 \end{pmatrix} \cdot \begin{pmatrix} V2 \\ -I2 \end{pmatrix}$$



$$\begin{aligned} V1 &= V2 \\ I1 &= -I2 + jC\omega V2 \end{aligned}$$

Doing the matrix product for cascaded components the chain matrix of the following circuit is :
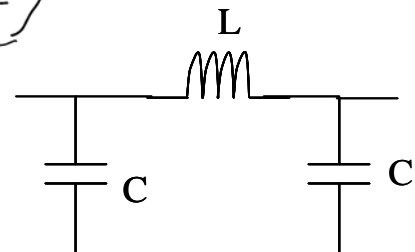
$$\begin{pmatrix} 1 & 0 \\ jC\omega & 1 \end{pmatrix} \cdot \begin{pmatrix} 1 & jL\omega \\ 0 & 1 \end{pmatrix} \cdot \begin{pmatrix} 1 & 0 \\ jC\omega & 1 \end{pmatrix}$$



$$\begin{pmatrix} V1 \\ I1 \end{pmatrix} = \begin{pmatrix} 1-LC\omega^2 & jL\omega \\ jC\omega(1-LC\omega^2) & 1-LC\omega^2 \end{pmatrix} \cdot \begin{pmatrix} V2 \\ -I2 \end{pmatrix}$$

If we have the relationship

$$LC\omega^2 = 1$$


$$\begin{pmatrix} 0 & jL\omega \\ jC\omega & 0 \end{pmatrix}$$

$$\begin{aligned} LC\omega^2 &= 1 \\ \omega &= \frac{1}{\sqrt{LC}} \end{aligned}$$

The matrix becomes

$$\begin{pmatrix} V1 \\ I1 \end{pmatrix} = \begin{pmatrix} 0 & jL\omega \\ jC\omega & 0 \end{pmatrix} \cdot \begin{pmatrix} V2 \\ -I2 \end{pmatrix} = \begin{pmatrix} 0 & j\sqrt{\frac{L}{C}} \\ j\sqrt{\frac{C}{L}} & 0 \end{pmatrix} \cdot \begin{pmatrix} V2 \\ -I2 \end{pmatrix}$$

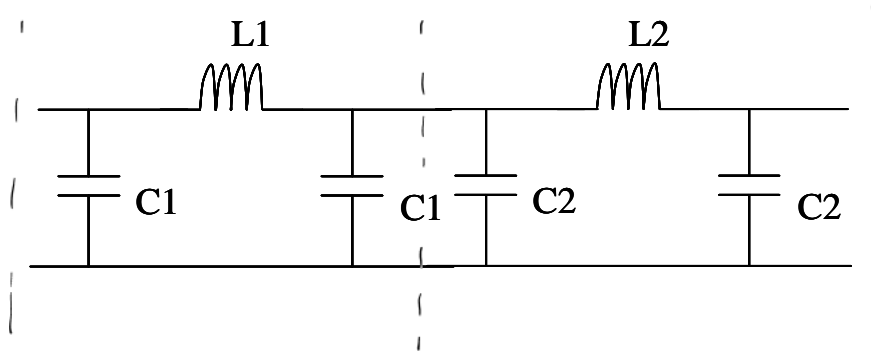And if we connect two different cells , we obtain an equivalent impedance transformer :



With $\underbrace{L_1 C_1 \omega^2 = 1}$ and $\underbrace{L_2 C_2 \omega^2 = 1}$ and $\underbrace{L_2 \neq L_1}$ $\underbrace{C_2 \neq C_1}$


And also $\sqrt{\frac{L_1}{C_1}} \neq \sqrt{\frac{L_2}{C_2}}$

$$\begin{pmatrix} 0 & j\sqrt{\frac{L_1}{C_1}} \\ j\sqrt{\frac{C_1}{L_1}} & 0 \end{pmatrix} \begin{pmatrix} 0 & j\sqrt{\frac{L_2}{C_2}} \\ j\sqrt{\frac{C_2}{L_2}} & 0 \end{pmatrix}$$

$$\begin{pmatrix} V1 \\ I1 \end{pmatrix} = \begin{pmatrix} -\sqrt{\frac{L_1 C_2}{L_2 C_1}} & 0 \\ 0 & -\sqrt{\frac{L_2 C_1}{L_1 C_2}} \end{pmatrix} \cdot \begin{pmatrix} V2 \\ -I2 \end{pmatrix} = \begin{pmatrix} -n & 0 \\ 0 & -\frac{1}{n} \end{pmatrix} \cdot \begin{pmatrix} V2 \\ -I2 \end{pmatrix}$$

III] Matching circuits with distributed components (microstrip line)

1) microstrip line

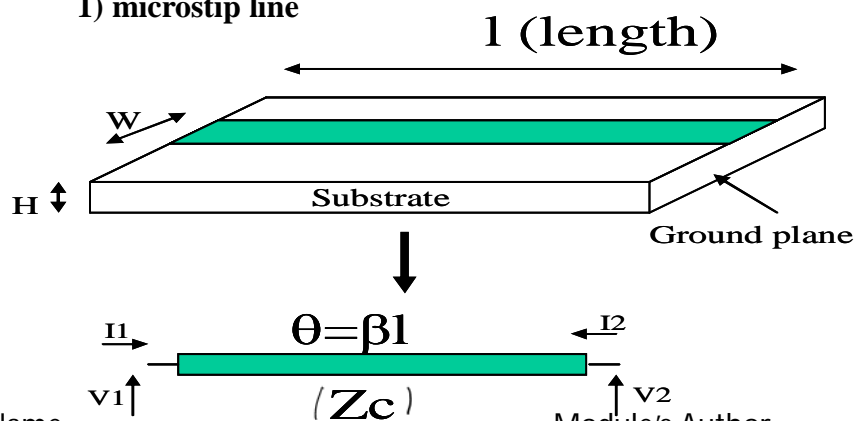


Module Name

Module's Author

-6-

The permittivity of the substrate is $\epsilon = \epsilon_0 \cdot \epsilon_r$

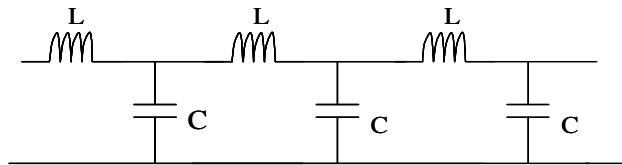The equivalent model of a lossless line is :



Here L is in henry/meter and C in farad /meter

The characteristic impedance of the line is defined as

$$Z_c = \sqrt{\frac{L}{C}}$$


The guided wavelength is

$$\lambda = \frac{\lambda_0}{\sqrt{\epsilon_r}}$$

$$\lambda_0 = \frac{c}{f} = \frac{3 \cdot 10^8}{f}$$

The input / output phase shift is
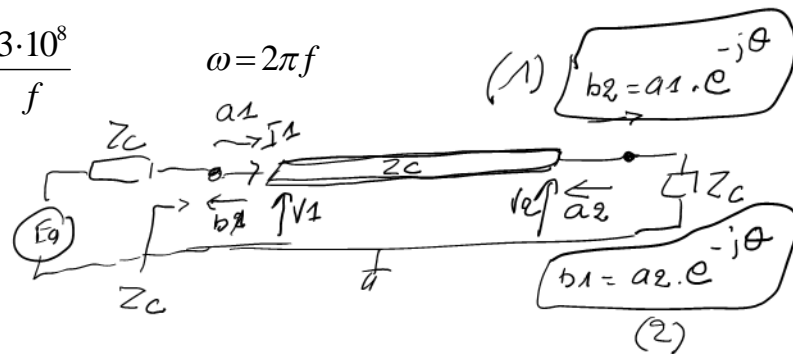
$$\theta = \beta l = \frac{2\pi \cdot l}{\lambda} = \omega \cdot \sqrt{LC}$$



As voltages and currents are not accurately measured directly , Kurokawa invented the power wave concept :

He defined a linear combination of voltage and current as following

$$a_1 = \frac{V_1 + \sqrt{R_0} \cdot I_1}{2\sqrt{R_0}} \quad b_1 = \frac{V_1 - \sqrt{R_0} \cdot I_1}{2\sqrt{R_0}} \quad b_2 = \frac{V_2 - \sqrt{R_0} \cdot I_2}{2\sqrt{R_0}} \quad a_2 = \frac{V_2 + \sqrt{R_0} \cdot I_2}{2\sqrt{R_0}}$$

Handwritten notes: $|a_1|^2 \rightarrow W$ (power), \sqrt{W} (voltage), \sqrt{W} (current)

Equation I

The unit of the magnitude of these power waves is


$$\sqrt{\text{Watt}}$$

So that their squares are expressed in Watt and are measurable which makes them very useful in microwave measurements .

We have the following relationships

$$P_1 = \frac{1}{2} \text{Re}_{\text{cal}}(V_1 \cdot I_1^*) = \frac{1}{2} (|a_1|^2 - |b_1|^2) \quad P_2 = -\frac{1}{2} \text{Re}_{\text{cal}}(V_2 \cdot I_2^*) = \frac{1}{2} (|b_2|^2 - |a_2|^2)$$

For a lossless line we have

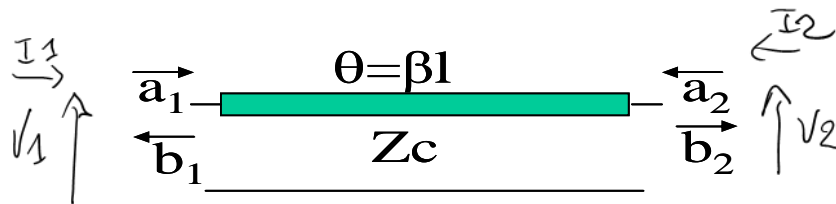


$$b_2 = a_1 \cdot e^{-j\theta} \quad b_1 = a_2 \cdot e^{-j\theta}$$

Equation II

Combining equations I and II we can obtain the chain matrix of the line :

$$\begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \begin{pmatrix} \cos(\theta) & jZ_c \sin(\theta) \\ \frac{j \sin(\theta)}{Z_c} & \cos(\theta) \end{pmatrix} \cdot \begin{pmatrix} V_2 \\ -I_2 \end{pmatrix}$$

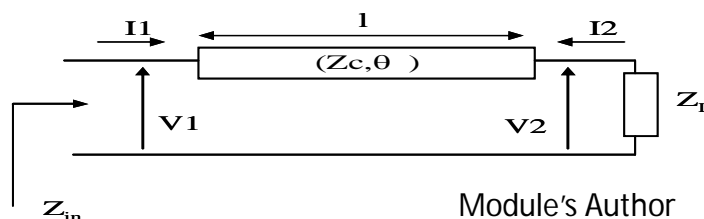And if we connect the line to a load impedance Z_L we have at the input of the line an impedance Z_1



Module Name

Module's Author

-8-

$$Z_{in} = \frac{V_1}{I_1} = Z_c \cdot \frac{Z_L + jZ_c \tan(\theta)}{Z_c + jZ_L \tan(\theta)}$$

2) Few specific examples


a) Impedance Inverter

$$l = \frac{\lambda}{4}$$

$$\theta = \frac{\pi}{2}$$


$$Z_{in} = \frac{Z_c^2}{Z_L}$$
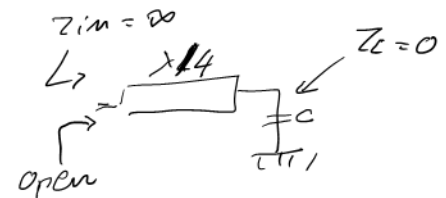
$$\begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \begin{pmatrix} 0 & jZ_c \\ \frac{j}{Z_c} & 0 \end{pmatrix} \cdot \begin{pmatrix} V_2 \\ -I_2 \end{pmatrix}$$




If $Z_L = 0$ (short circuit) $\rightarrow Z_{in} = \infty$ (open circuit) and vice versa

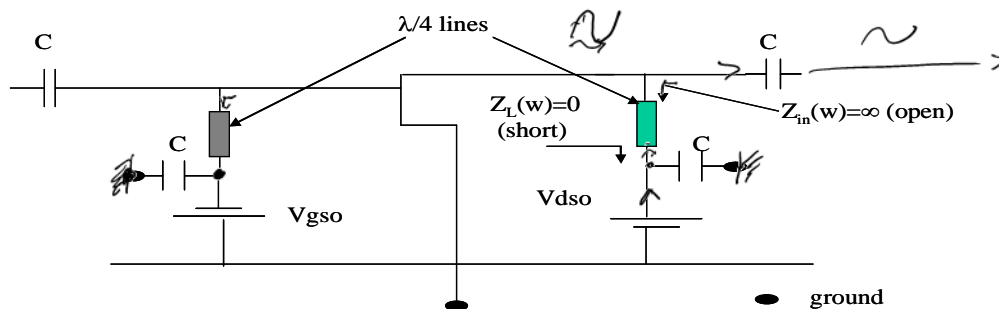This can be advantageously used for the design of transistor's bias circuits .



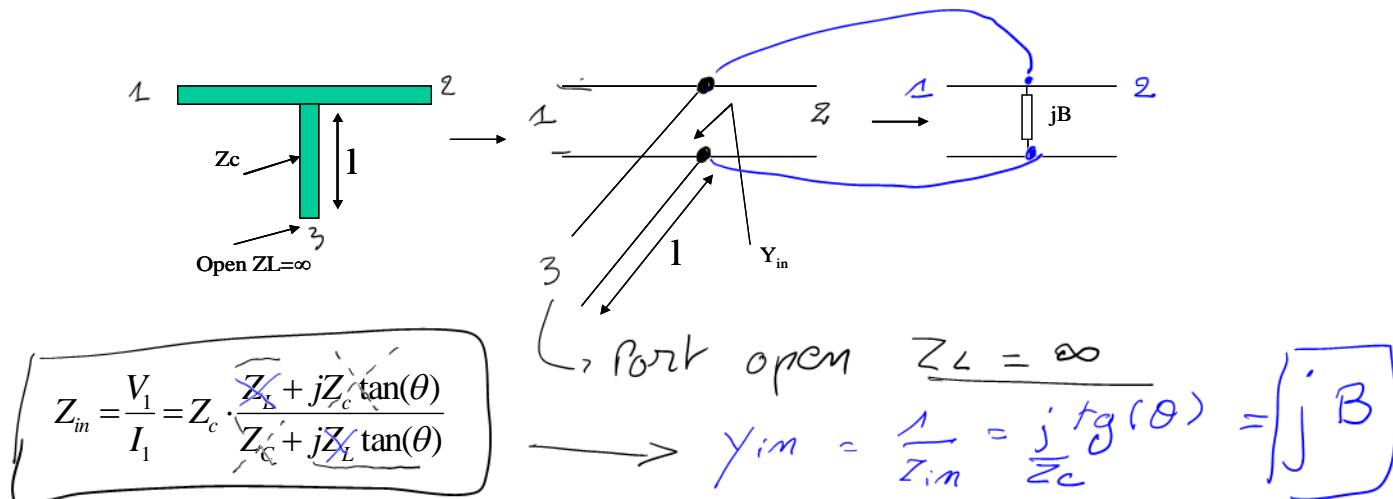b) Parallel line (open Stub $Z_L = \infty$)



If $Z_L = \infty$


$$Z_{in} = -jZ_c \cdot \tan^{-1}(\theta) \quad Y_{in} = \frac{1}{Z_{in}} = \frac{j}{Z_c} \cdot \tan(\theta) = \underline{jB}$$

Depending on the sign of $\tan(\theta)$, Y_{in} is corresponding to a parallel inductance or a parallel capacitance and can be used for narrowband transistor matching.

c) Small length lines

θ small means $\cos(\theta) \cong 1$ and $\sin(\theta) \cong \theta$

With high characteristic impedance Z_c

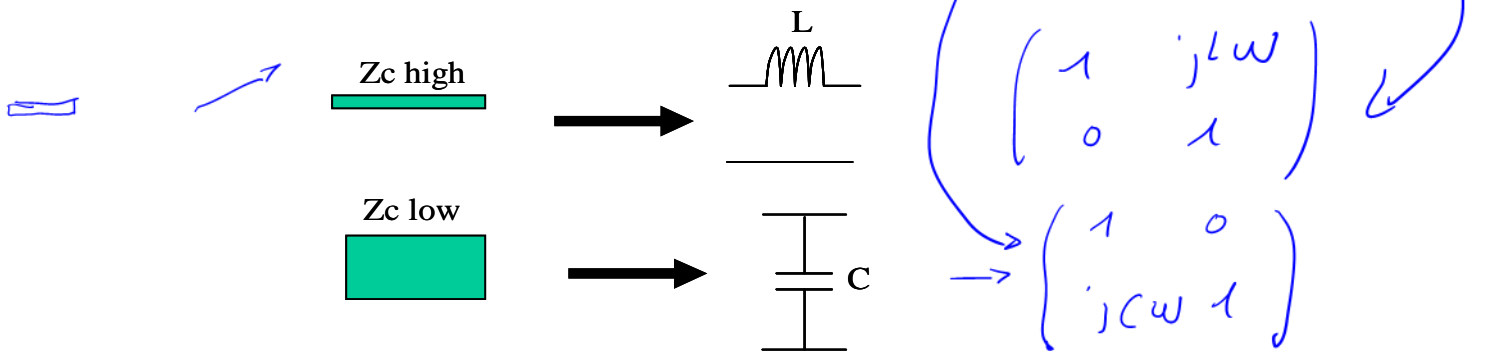

Module Name

Module's Author

-10-

For Z_c high

$$\begin{pmatrix} V1 \\ I1 \end{pmatrix} = \begin{pmatrix} \cos(\theta) & jZ_c \cdot \sin(\theta) \\ \frac{j \sin(\theta)}{Z_c} & \cos(\theta) \end{pmatrix} \cdot \begin{pmatrix} V2 \\ -I2 \end{pmatrix} = \begin{pmatrix} 1 & jZ_c \theta \\ 0 & 1 \end{pmatrix} \cdot \begin{pmatrix} V2 \\ -I2 \end{pmatrix} = \begin{pmatrix} 1 & jLw \\ 0 & 1 \end{pmatrix} \cdot \begin{pmatrix} V2 \\ -I2 \end{pmatrix}$$

With :

$$L = \frac{Z_c \cdot \beta l}{w}$$


For Z_c low

$$\begin{pmatrix} V1 \\ I1 \end{pmatrix} = \begin{pmatrix} \cos(\theta) & jZ_c \cdot \sin(\theta) \\ \frac{j \sin(\theta)}{Z_c} & \cos(\theta) \end{pmatrix} \cdot \begin{pmatrix} V2 \\ -I2 \end{pmatrix} = \begin{pmatrix} 1 & 0 \\ \frac{j\theta}{Z_c} & 1 \end{pmatrix} \cdot \begin{pmatrix} V2 \\ -I2 \end{pmatrix} = \begin{pmatrix} 1 & 0 \\ jCw & 1 \end{pmatrix} \cdot \begin{pmatrix} V2 \\ -I2 \end{pmatrix}$$

With

$$C = \frac{\beta l}{Z_c \cdot w}$$

d) Impedance transformer

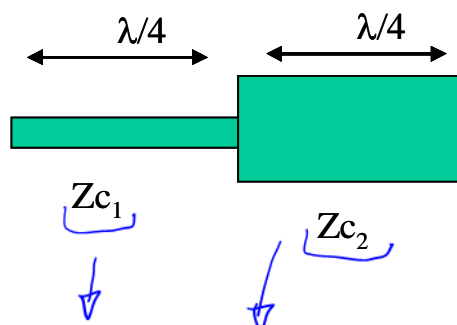

$$\begin{pmatrix} V1 \\ I1 \end{pmatrix} = \begin{pmatrix} 0 & jZ_{c1} \\ \frac{j}{Z_{c1}} & 0 \end{pmatrix} \cdot \begin{pmatrix} 0 & jZ_{c2} \\ \frac{j}{Z_{c2}} & 0 \end{pmatrix} \begin{pmatrix} V2 \\ -I2 \end{pmatrix} = \begin{pmatrix} -\frac{Z_{c1}}{Z_{c2}} & 0 \\ 0 & -\frac{Z_{c2}}{Z_{c1}} \end{pmatrix} \cdot \begin{pmatrix} V2 \\ -I2 \end{pmatrix} = \begin{pmatrix} -n & 0 \\ 0 & -\frac{1}{n} \end{pmatrix} \cdot \begin{pmatrix} V2 \\ -I2 \end{pmatrix}$$



IV] Basic Power amplifier Architecture

