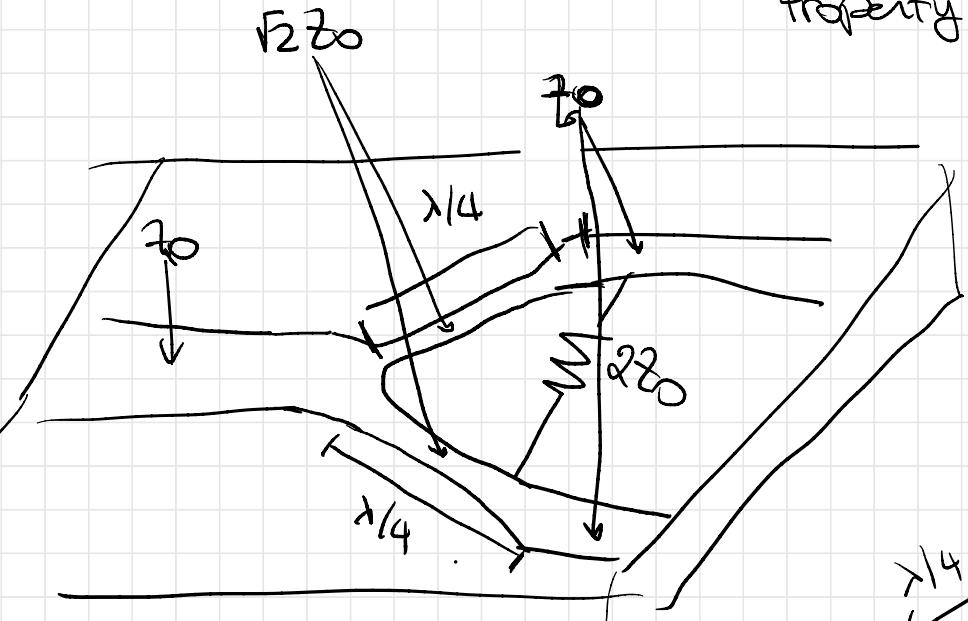


# MICROWAVE ENGINEERING

Lecture 25:  
Dividers and  
couplers –  
second part


# WILKINSON POWER DIVIDER



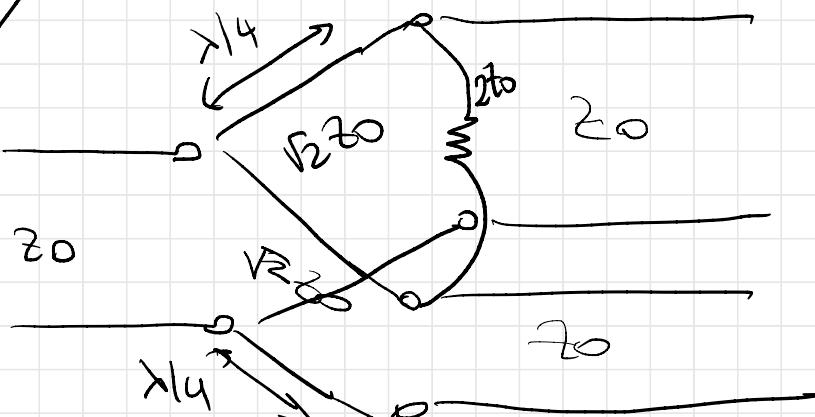
# 3 PORTS RESISTIVE POWER DIVIDERS

Property :- ISOLATION in between the output ports.

- LOSSLESS when the output ports are matched




## Even-odd mode analysis

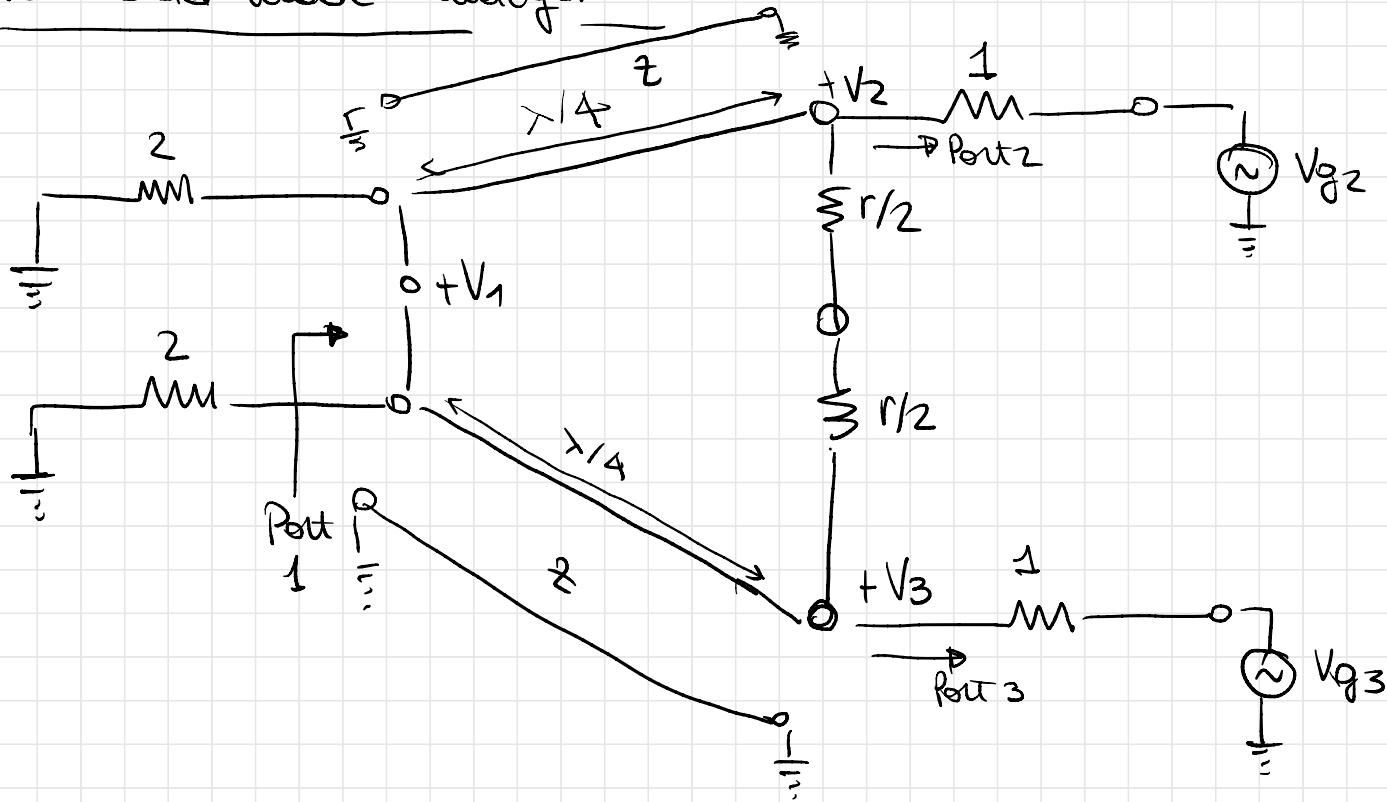
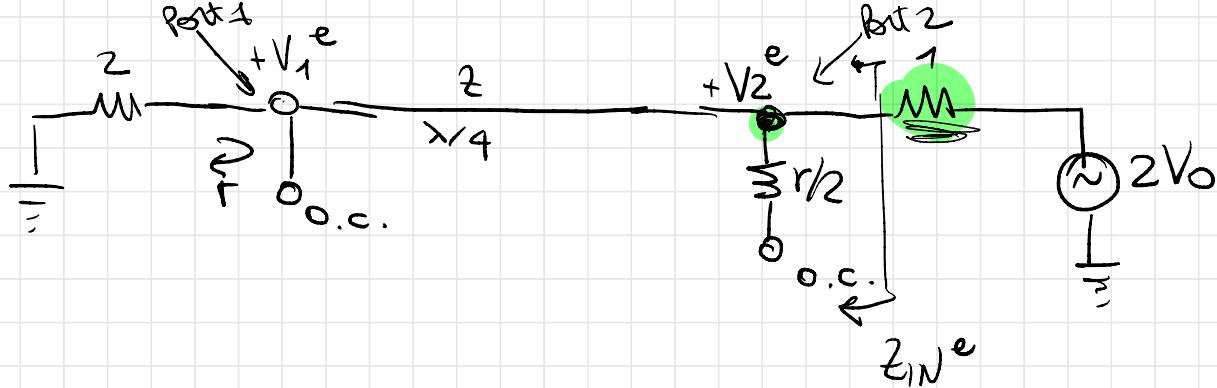
## EVEN MODE ANALYSIS

$$V_{02} = V_{03} = \frac{2V_0}{Z} \Rightarrow V_2^e = V_3^e$$



$$Z_{IN}^e = \frac{Z^2}{2}$$

If  $Z = \sqrt{2}$   $\rightarrow Z_{IN}^e = 1 \Rightarrow$  Port 2 will be matched for even mode

Then  $\boxed{V_2^e = V_0}$   $\rightarrow Z_{IN} \parallel 1 \Rightarrow Z_{eq} = 0.5$

$V_1^e$  can be found from TL equations with  $Z=0$  at port 1 and

$\lambda = -\frac{\lambda}{4}$  at port 2

$$V(x) = V^+ \left( e^{-j\frac{2\pi}{\lambda}x} + \Gamma e^{j\frac{2\pi}{\lambda}x} \right)$$



$$e^{-j\frac{2\pi}{\lambda} \left(-\frac{\lambda}{4}\right)} = e^{j\frac{\pi}{2}} = j$$

$$\textcircled{1} \quad V_2^e = V\left(-\frac{\lambda}{4}\right) = j V^+ (1 - \Gamma) = V_0 \quad e^{j\frac{2\pi}{\lambda} \left(-\frac{\lambda}{4}\right)} = e^{j\frac{\pi}{2}} = -j$$

$$\textcircled{2} \quad V_1^e = V(0) = V^+ (1 + \Gamma)$$

$V^+ = \frac{V_0}{j(1 - \Gamma)}$

$$V_1^e = \frac{V_0}{j} \frac{1 + \Gamma}{1 - \Gamma} = j V_0 \frac{1 + \Gamma}{\Gamma - 1}$$


$$\Gamma = \frac{2 - \sqrt{2}}{2 + \sqrt{2}}$$

(part i)

$$(V_1 e) = jV_0 \frac{1 + \Gamma}{\Gamma - 1} = jV_0 \left[ \frac{1 + \frac{2 - \sqrt{2}}{2 + \sqrt{2}}}{\frac{2 - \sqrt{2}}{2 + \sqrt{2}} - 1} \right] =$$

$$= jV_0 \left[ \frac{2 + \sqrt{2} + 2 - \sqrt{2}}{\sqrt{2} - \sqrt{2} - 2 - \sqrt{2}} \right] = jV_0 \left[ \frac{4}{-2\sqrt{2}} \right] = (-jV_0 \sqrt{2})$$

## ODD MODE ANALYSIS

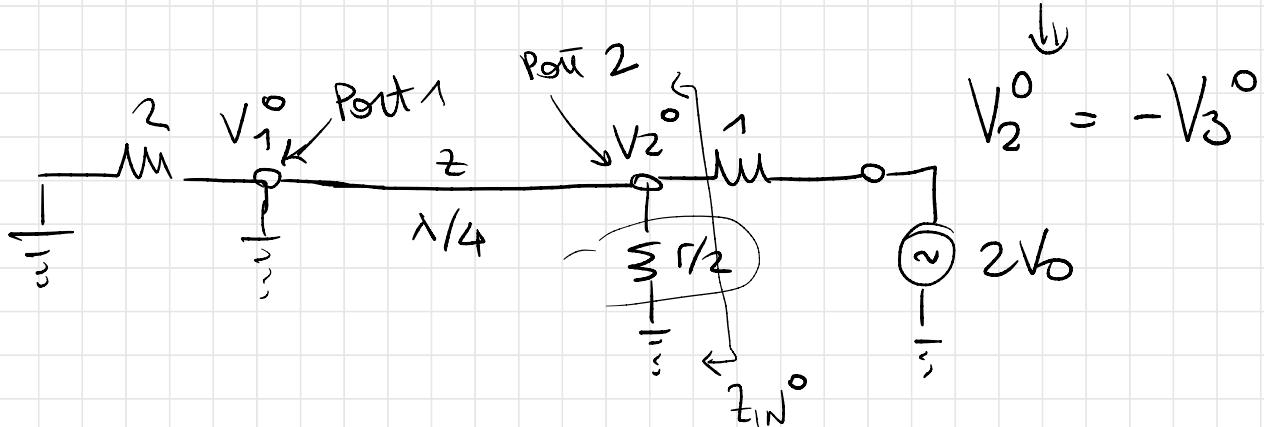

$$V_{g2} = -V_{g3} = 2V_0$$


$$\downarrow$$

$$V_2^0 = -V_3^0$$


In port 2 we see  $r/2$  and a  $\lambda/4$  TL connected in parallel and shortened at port 1. The  $\lambda/4$  line will look as an O.C. at port 2. Port 2 will be matched if  $r=2$ .

It follows  $V_2^0 = V_0$  and  $V_1^0 = 0 \rightarrow$  All power ends in the resistor

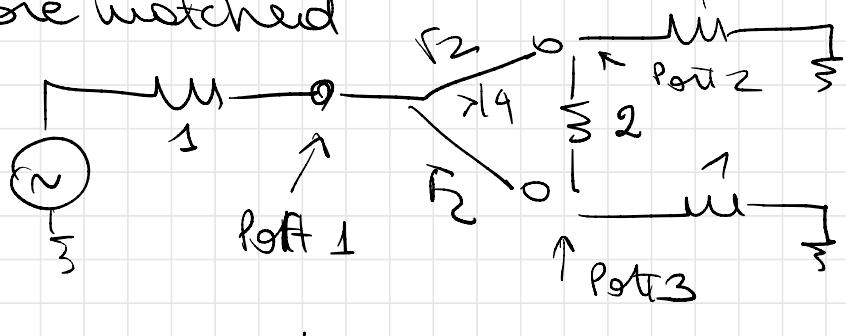
Finally we have to find the input impedance when ports 2 and 3 are matched



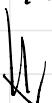$V_2 = V_3$  as  $\lambda/4$  is the even mode excitation



No current is flowing in the resistor

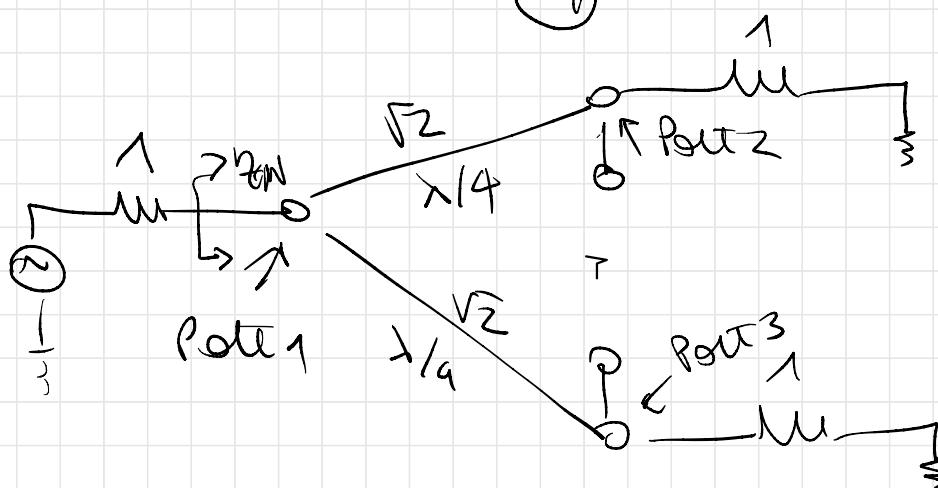

The input imp.

$$\underline{Z}_{IN} = \frac{1}{2} (\sqrt{2})^2 = 1$$

The S parameters for the Wilkinson power divider are

$$S_{11} = 0 \quad (Z_{IN} = 1 \text{ at port 1})$$

$$S_{22} = S_{33} = 0 \quad (\text{ports 2 and 3 are matched})$$

$$S_{12} = S_{21} = \frac{V_1^e + V_1^o}{V_2^e + V_2^o} = -j\sqrt{2}$$


$$S_{13} = S_{31} = -j\sqrt{2} \quad S_{23} = S_{32} = 0 \quad (\text{Port 2 and 3 are isolated})$$

NOTE: The divider is lossless only if ports 2 and 3 are matched

## DIRECTIONAL COUPLERS

Input  
→

①

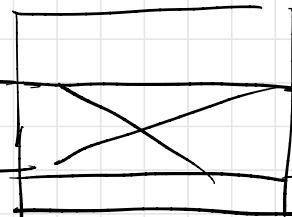

②

through

③

Coupled

Isolated  
←


④

Coupling  $\leq$   
Directive D


Isolation I

$$D = I - C$$

## - Bethe Hole Coupler

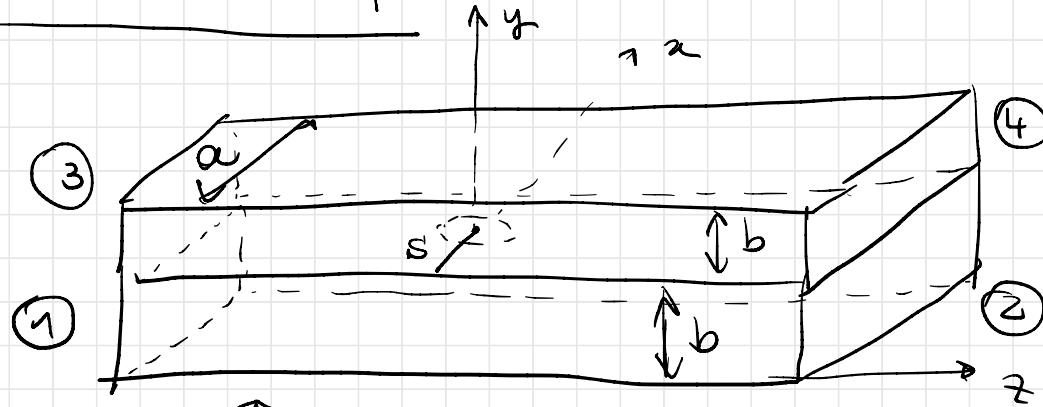


PARALLEL  
WAVEGUIDES

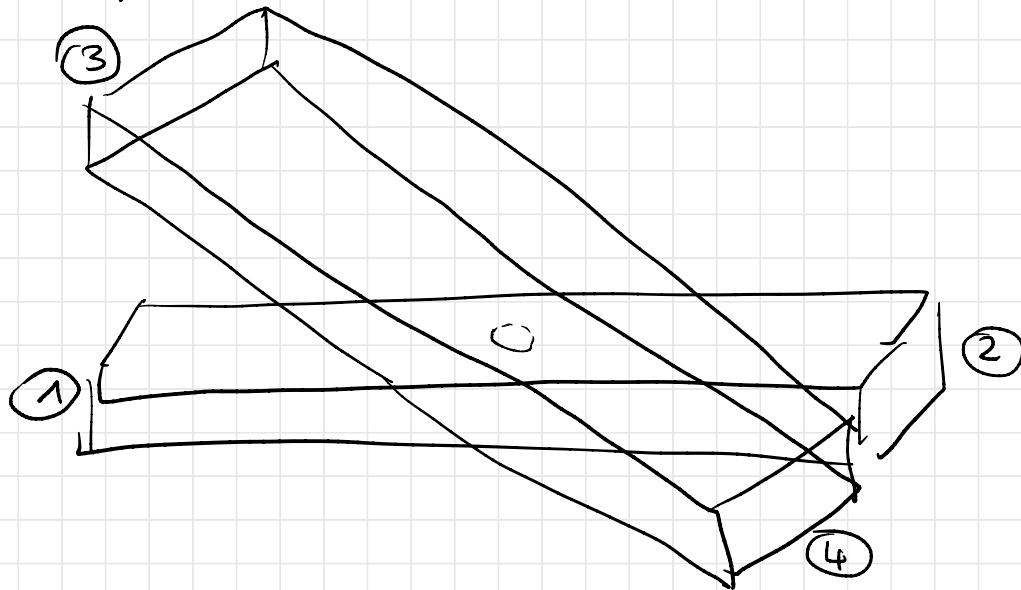

SKewed  
WAVEGUIDES


- Cous:
- Narrow bandwidth
  - Difficult fab in the skewed coupl.

### - Multihole coupler

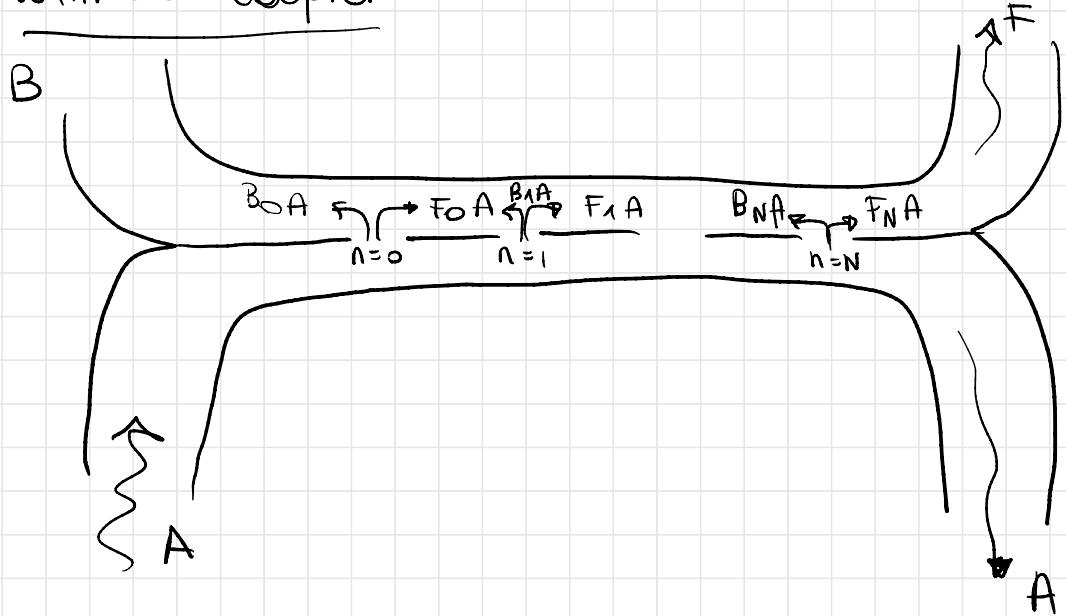



$N+1$  hole  
waveguide  
directional  
coupler

### - Coupled line directional coupler

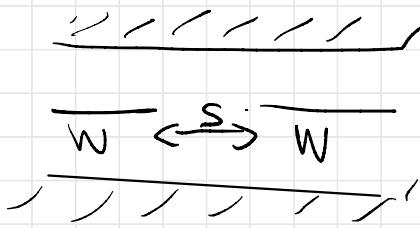

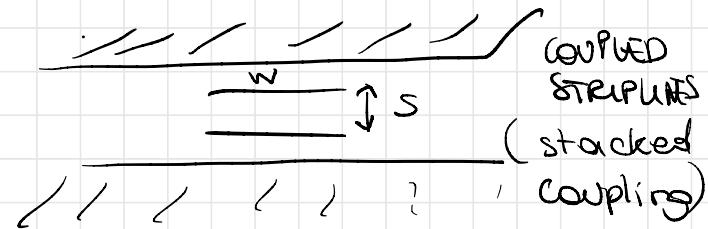
COPPIED  
STRIP LINE  
(planar or  
edge coupled)



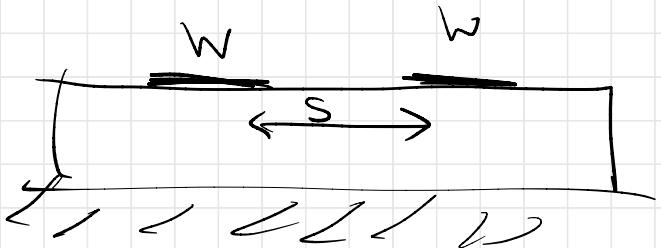


COUPL ED MICROSTRIPS


Coupled lines

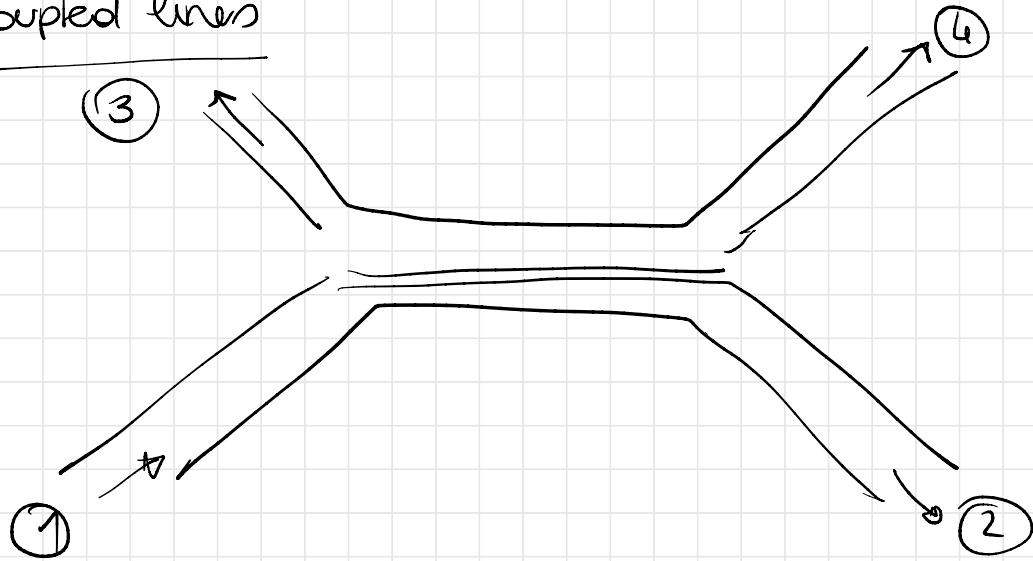

## Multisection coupled lines

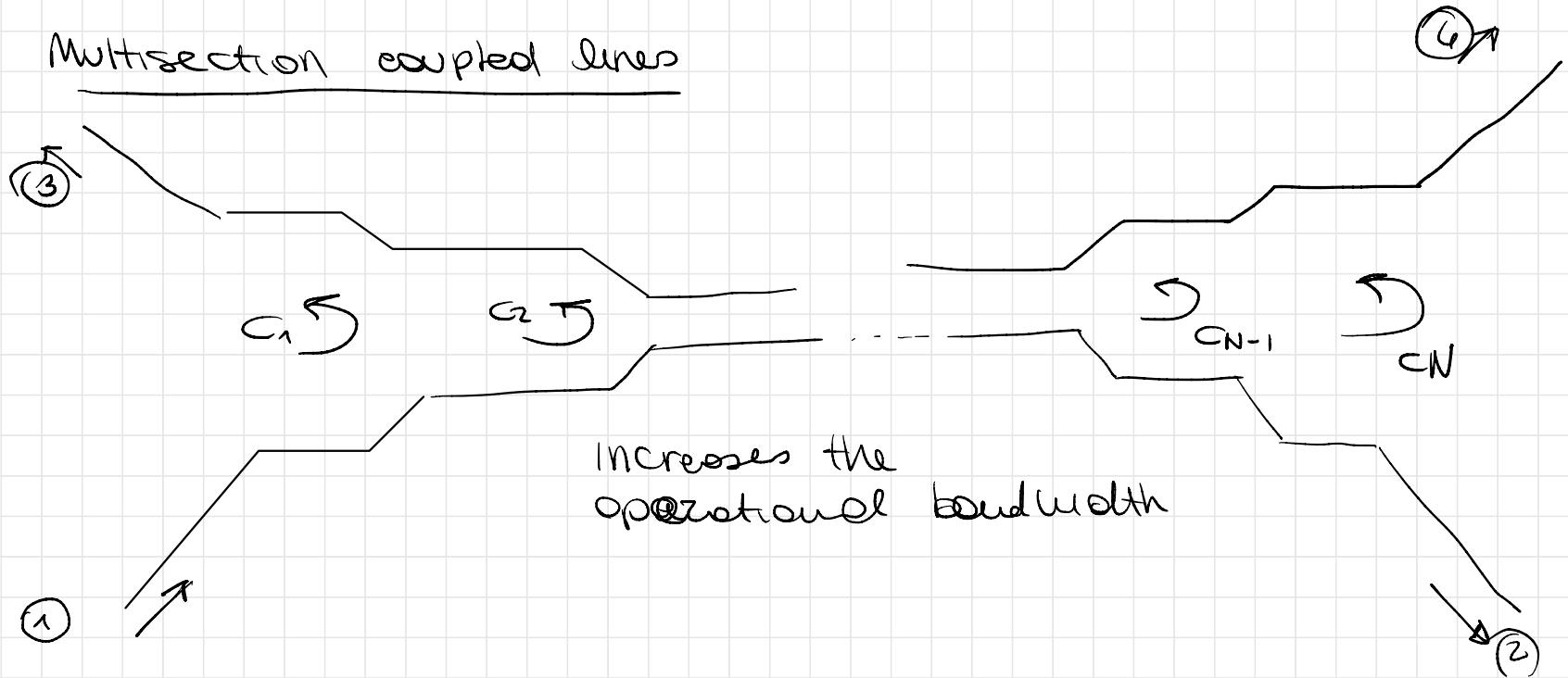

## The quadrature ( $90^\circ$ ) hybrid

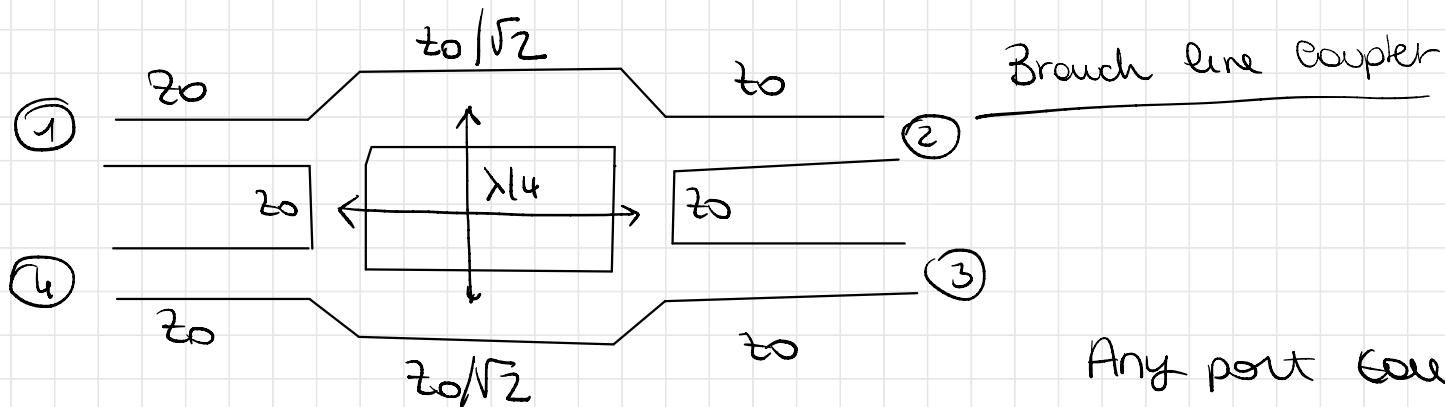


Any port can be the input port

$$[S] = -\frac{1}{\sqrt{2}} \begin{bmatrix} 0 & j & 1 & 0 \\ j & 0 & 0 & 1 \\ 1 & 0 & 0 & j \\ 0 & 1 & j & 0 \end{bmatrix}$$
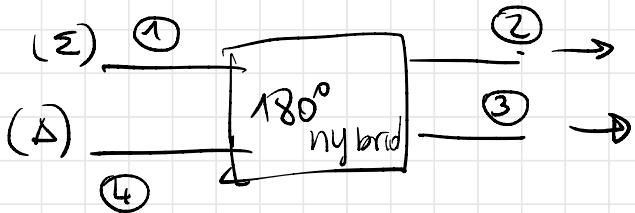
## The $180^\circ$ HYBRID

4 ports network  $\rightarrow$   $180^\circ$  between port 2 and (3)



Port 1 input  $\rightarrow$  in phase (2) and (3)

Port 4 input  $\rightarrow$   $180^\circ$  phase shift (2) and (3)

COMBINER : Inputs at ports 2 and 3  $\rightarrow$  Port 1  
 $\sum$  combine


$$[S] = -\frac{j}{R_2} \begin{bmatrix} 0 & 1 & 1 & 0 \\ 1 & 0 & 0 & -1 \\ 1 & 0 & 0 & 1 \\ 0 & -1 & 1 & 0 \end{bmatrix}$$

$\rightarrow$  Port 4  $\Delta$  difference

Realization:

RING HYBRID or RAT RACE

(microstrip/ stripline)

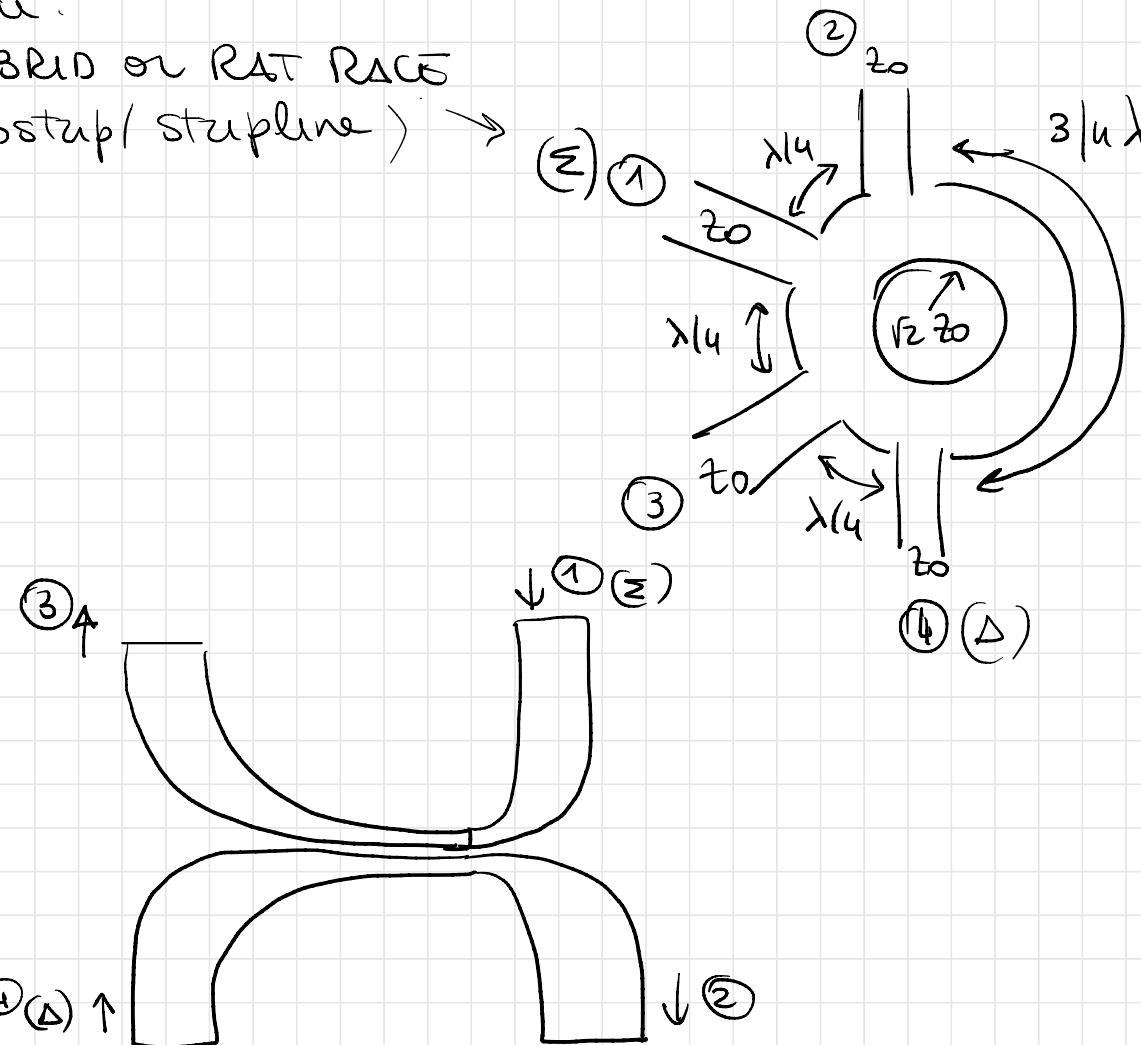

Waveguide  
hybrid junction  
(T-MAGIC)

