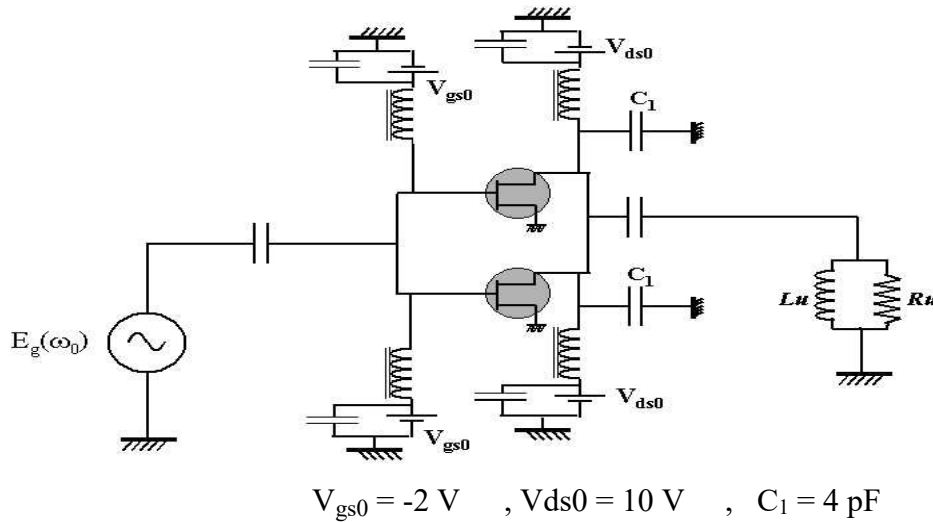


# **Semester S1 –Basics of active and non linear electronics**


## **RF Power amplifiers ( JM Nebus )**
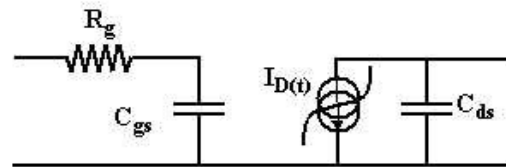
### **TUTORIAL N° 3**

Let us consider the following schematic of an amplifier . The operating frequency is 2 Ghz .



The non linear simplified model for each transistor is the following:



$$C_{gs} = 1 \text{ pF} ; \quad R_g = 5 \text{ } \Omega ; \quad C_{ds} = 0.5 \text{ pF}$$

$$I_D(t) = f_1(t) \cdot f_2(t)$$

$$\text{avec} \quad f_1(t) = I_{dss} \cdot \left( 1 - \frac{V_{gs}(t)}{V_p} \right)^2$$

$$f_2(t) = (1 + K \cdot V_{ds}(t))$$

$$\text{With} \quad I_{dss} = 100 \text{ mA} \quad V_p = -3 \text{ V} \quad K = 0.05$$

This model equation corresponds to the saturated region of the transistor

$$V_{ds\text{-min}} = 2 \text{ V} \text{ and } V_{ds\text{-max}} = 18 \text{ V} \quad \text{and} \quad -3 \text{ V} < V_{gs} < 0 \text{ V}$$

$$\text{For } V_{gs} < -3 \text{ V} \quad f_1(t) = 0 \quad \text{so} \quad I_D = 0$$

- 1) Plot the  $I_d(V_{ds})$  characteristic for three values of  $V_{gs}$  (  $V_{gs} = 0V$  ,  $V_{gs} = -1V$  ,  $V_{gs} = -2V$  )
- 2) Plot the  $I_d(V_{gs})$  characteristic for three values of  $V_{ds}$  (  $V_{ds} = 2V$  ,  $V_{ds} = 10V$  ,  $V_{ds} = 18V$  )
- 3) Determine the values of the small signal transconductance  $g_m$  and the output conductance  $g_d$  of the transistor at the operating bias point (  $V_{gs0} = -2V$  ,  $V_{ds0} = +10V$  )
- 4) What is the cut off frequency of the input ( $R_g C_{gs}$ ) circuit of the transistor
- 5) Now for large signal operation, we want to operate in class B and we want to obtain the maximum output RF power in the load  $R_u$ .

For this quadratic  $I_{ds} / V_{gs}$  characteristic, the terms of the Fourier serie of  $f_1(t)$  is given by the following relationships:

$$F_0 = \frac{I_p}{\pi} \frac{\varphi - \frac{3}{4} \sin(2\varphi) + \frac{1}{2} \varphi \cdot \cos(2\varphi)}{(1 - \cos(\varphi))^2}$$

$$F_1 = \frac{2 I_p}{\pi} \frac{\frac{3}{4} \sin(\varphi) + \frac{1}{12} \sin(3\varphi) - \varphi \cdot \cos(\varphi)}{(1 - \cos(\varphi))^2}$$

$$F_2 = \frac{2 I_p}{\pi} \frac{\frac{\varphi}{4} - \frac{1}{6} \sin(2\varphi) + \frac{1}{48} \sin(4\varphi)}{(1 - \cos(\varphi))^2}$$

$$V_{gs}(t) = V_{gs0} + V_{gs1} \cdot \cos(\omega t) \quad ; \quad V_{ds}(t) = V_{ds0} - V_{ds1} \cdot \cos(\omega t)$$

$$f_1(t) = F_0 + F_1 \cdot \cos(\omega t) + F_2 \cdot \cos(2\omega t) + \dots$$

$$I_D(t) = I_{D0} + I_{D1} \cdot \cos(\omega t) + I_{D2} \cdot \cos(2\omega t) + \dots$$

Determine the values of  $F_0$  ,  $F_1$  ,  $F_2$  and then the values of  $I_{D0}$  and  $I_{D1}$

- 6) What are the required values for  $R_u$  and  $L_u$  and what is the corresponding value of the load impedance (  $Z_u = R_u // L_u$  )
- 7) What are the values of the output power and the DC power of this two cell power amplifier
- 8) What are the values of the power gain and the power added efficiency