

MICROWAVE ENGINEERING

Lecture 28:

Microwave

filters - part 2



INSERTION LOSS METHOD

Perfect filter:

- zero insertion loss in the passband
- infinite attenuation in the stopband
- linear phase response in passband to avoid distortion

ORDER OF THE FILTER = NUMBER OF REACTIVE ELEMENTS

Power loss Ratio

$$P_{LR} = \frac{\text{Power at the source}}{\text{Power at the load}} = \frac{P_{INC}}{P_{LOAD}} = \frac{1}{1 - |\Gamma(\omega)|^2}$$

The INSERTION LOSS : $IL = 10 \log P_{LR}$

$$|\Gamma(\omega)|^2 = \frac{H(\omega^z)}{H(\omega^z) + N(\omega^z)} \Rightarrow P_{LR} = 1 + \frac{N(\omega^z)}{H(\omega^z)}$$

ALL FILTERS FALL INTO
THIS FORM

Typical Response is:

- MAXIMALLY FLAT (Binomial or Butterworth)

A low-pass filter of this type

$$P_{LR} = 1 + K^2 \left(\frac{\omega}{\omega_c} \right)^{2N}$$


N order of
the filter

ω_c is cut-off
frequency

EQUAL RIPPLE

(Chebyshev polynomial)
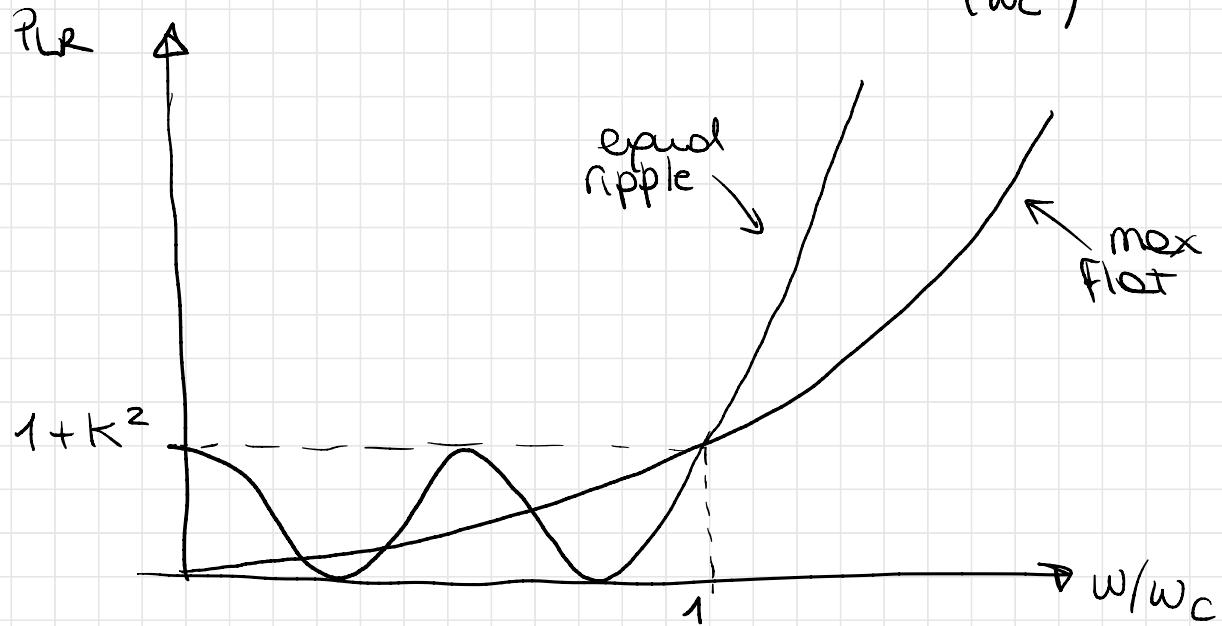
$$P_{LR} = 1 + k^2 T_N \left(\frac{\omega}{\omega_c} \right)$$



- ELLIPTIC FUNCTION



- LINEAR PHASE FILTERS → avoids distortion

cons: less sharp cut-off

DESIGN PROCESS

SPECIFICATION →

LOW-PASS
PROTOTYPE
DESIGN

→

SCALING
AND
CONVERSION

→


IMPLEMENTATION

PROTOTYPES


Designed with source impedance $R_S = 1 \Omega$
Cut-off freq. $\omega_C = 1$

- Maximally flat prototypes:

① SHUNT ELEMENT START

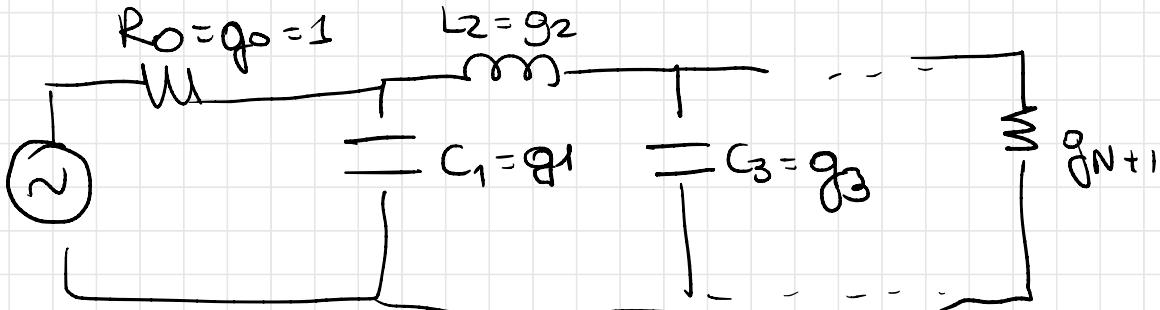

② SERIES ELEMENT START

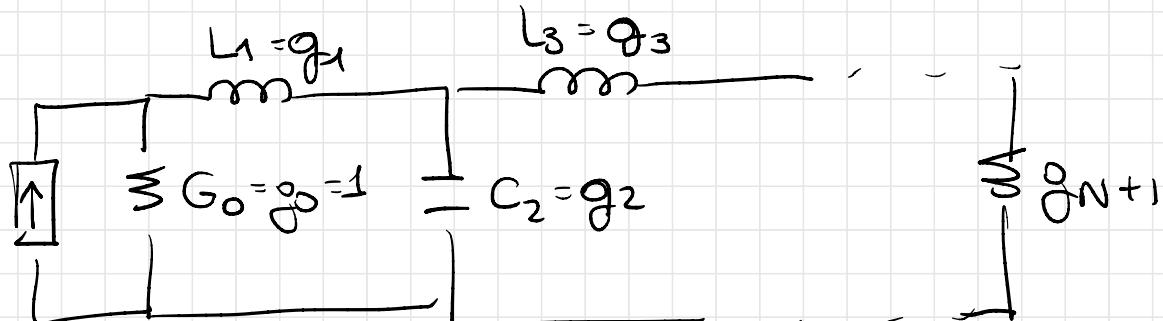

$$g_0 = \begin{cases} \text{generator resistance} & \rightarrow \text{shunt start} \\ \hookleftarrow \quad \text{conductance} & \rightarrow \text{series start} \end{cases}$$

$$\frac{g_K}{K=1:N} = \begin{cases} \text{inductance} & \rightarrow \text{series ind.} \\ \text{capacitance} & \rightarrow \text{shunt cap.} \end{cases}$$

$$g_{N+1} = \begin{cases} \text{load resistance} & \rightarrow \text{if } g_N \text{ is shunt cap.} \\ \text{conductance} & \rightarrow \text{if } g_N \text{ is series ind.} \end{cases}$$

Equal Ripple prototypes \rightarrow identical circuit as in
 max flat
 Values of g are taken
 from a different table.

FILTER TRANSFORMATIONS

Impedance scaling

A source resistance R_o can be obtained by scaling the filter component as follows:

$$L' = R_o L$$

$$C' = \frac{C}{R_o}$$

$$R_s' = R_o$$

$$R_L' = R_L R_o$$

Frequency scaling To move the cut-off freq. from 1 to ω_c

$$P_{LR}'(\omega) = P_{LR}\left(\frac{\omega}{\omega_c}\right) \leftarrow \text{stretching the passband}$$

$$L_k' = \frac{L_k}{\omega_c}$$

$$C_k' = \frac{C_k}{\omega_c}$$

Scaling both impedance and freq.:

$$L_k' = \frac{R_o L_k}{\omega_c} \quad C_k' = \frac{C_k}{R_o \omega_c}$$

low-pass to high-pass transformation: Replace ω with $\frac{\omega_b}{\omega}$

$$C_k' = \frac{1}{\omega_c L_k}$$

$$L_k' = \frac{1}{\omega_c C_k}$$

With impedance scaling

$$C_k' = \frac{1}{R_0 w_0 L_k} \quad L_k' = \frac{R_0}{w_0 C_k}$$

Band-pass and band-stop transformations

If we want a band pass response between ω_1 and ω_2

fractional bandwidth $\Delta = \frac{\omega_2 - \omega_1}{\omega_0}$ $\omega_0 = \sqrt{\omega_1 \omega_2}$ center freq.

The new elements:

The single element L_k gets transformed into series LC circuit

$$\begin{cases} L_k' = \frac{L_k}{\Delta \omega_0} \\ C_k' = \frac{\Delta}{\omega_0 L_k} \end{cases}$$

The shunt capacitors at one transformed
in shunt LC circuit
with elements

$$\left. \begin{array}{l} L_k' = \frac{\Delta}{\omega_0 C_k} \\ C_k' = \frac{C_k}{\Delta \omega_0} \end{array} \right\}$$

If we want a stopband response between ω_1 and ω_2

series inductor
will be replaced
with shunt
LC

$$\left. \begin{array}{l} L_k' = \frac{\Delta L_k}{\omega_0} \\ C_k' = \frac{1}{\omega_0 \Delta L_k} \end{array} \right\}$$

shunt capacitor
becomes a series
LC circuit

$$\left. \begin{array}{l} L_k' = \frac{1}{\omega_0 \Delta C_k} \\ C_k' = \frac{\Delta C_k}{\omega_0} \end{array} \right\}$$

SUMMARY TRANSFORMATIONS

LOW-PASS

$$\frac{1}{L}$$

$$\frac{1}{C}$$


HIGH-PASS

$$\frac{1}{T} \frac{1}{\omega_c L}$$

$$\frac{1}{T} \frac{1}{\omega_c C}$$

BANDPASS
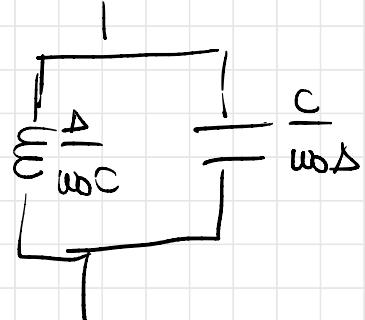
$$\frac{1}{T} \frac{\Delta}{\omega_0 L}$$



STOP BAND

$$\frac{1}{T} \frac{\Delta}{\omega_0} \frac{1}{T} \frac{1}{\omega_0 \Delta}$$

$$\frac{1}{T} \frac{1}{\omega_0 C \Delta} \frac{C \Delta}{\omega_0}$$

FILTER IMPLEMENTATION

Richard's Transformations



$$jX_L \Rightarrow \begin{array}{c} \circ \\ \diagdown \\ \text{---} \\ \diagup \\ \circ \end{array} \in L$$

equivalent to

$$jB_C \Rightarrow \begin{array}{c} \circ \\ \diagup \\ \text{---} \\ \diagdown \\ \circ \end{array} \in C$$

equivalent to

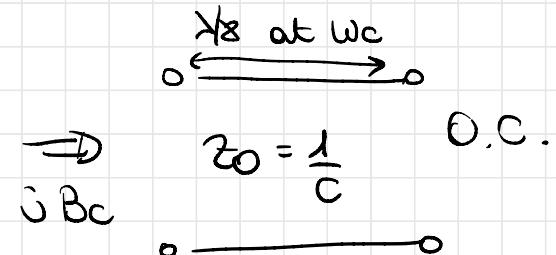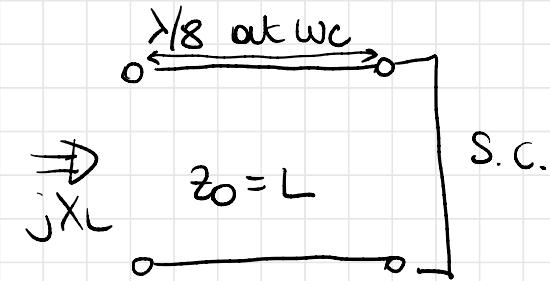Replace lumped elements with
concentrated lines:



KURODA IDENTITIES

- Physically separate TL stubs
- Transform series stubs into shunt stubs and V.V.
- Change impractical charact. (impedance) into more practical ones

All T.L. are intended to be $\gg 0$ at ω_c . Inductors and capacitors represent SC. and OC stubs

L IDENTITIES


①





②



③

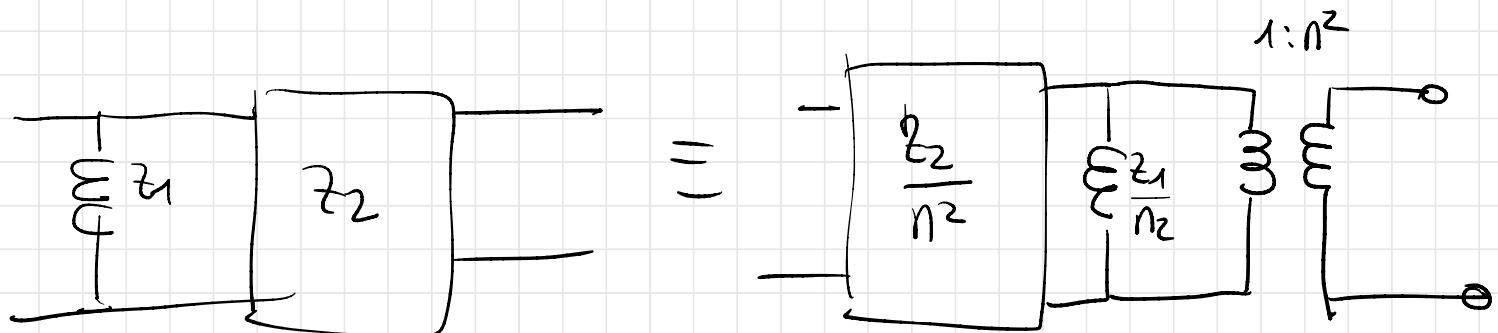

④

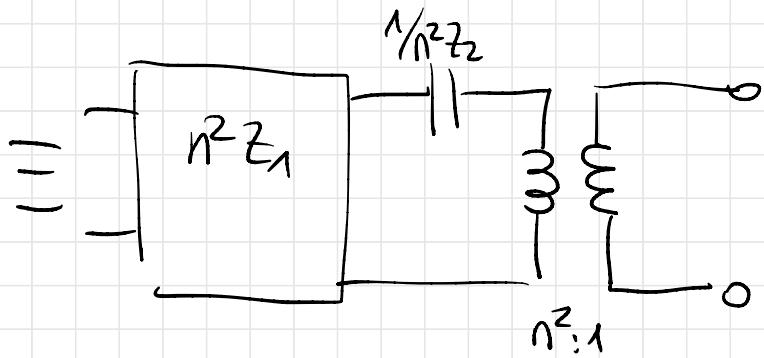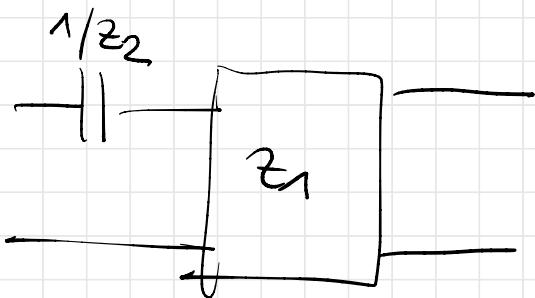

$$\boxed{n^2 = 1 + \frac{z_2}{z_1}}$$