

PRACTICAL WORK PW4:

SIMULATION OF A LINEAR AMPLIFIER @ 2GHZ USING KEYSIGHT ADS AND BASED ON LUMPED COMPONENTS


- Student Help Manual for PW 3, 4

Copy to be left
on site




UNIVERSITÀ
DEGLI STUDI
DI BRESCIA



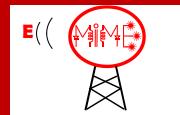



This booklet presents the architecture of the ADS project you will use.

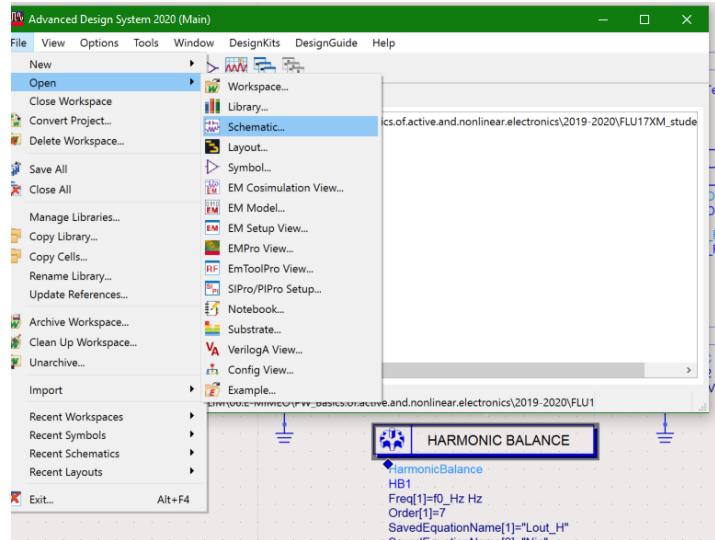After launching ADS, click on *file/open Schematic* to obtain the following list of schematics :




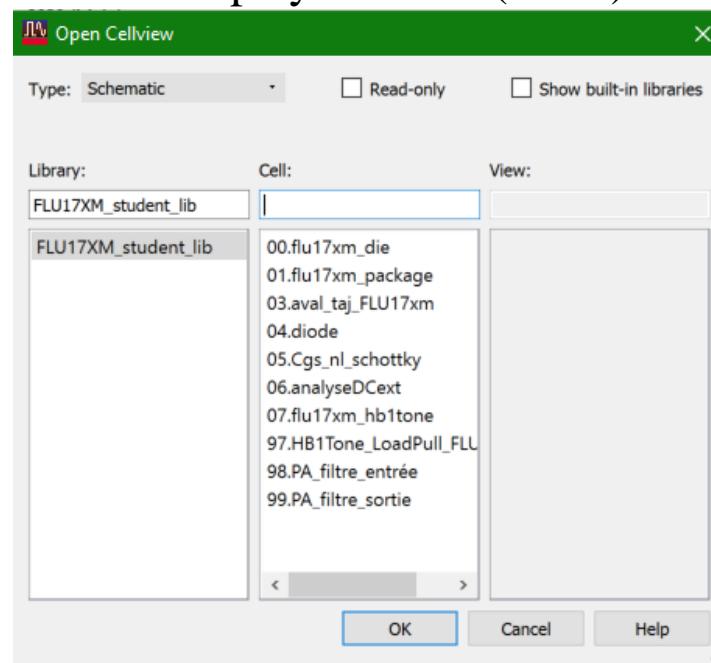Each schematic file (*.dsn) is detailed hereafter as well as the corresponding data display window (*.dds).





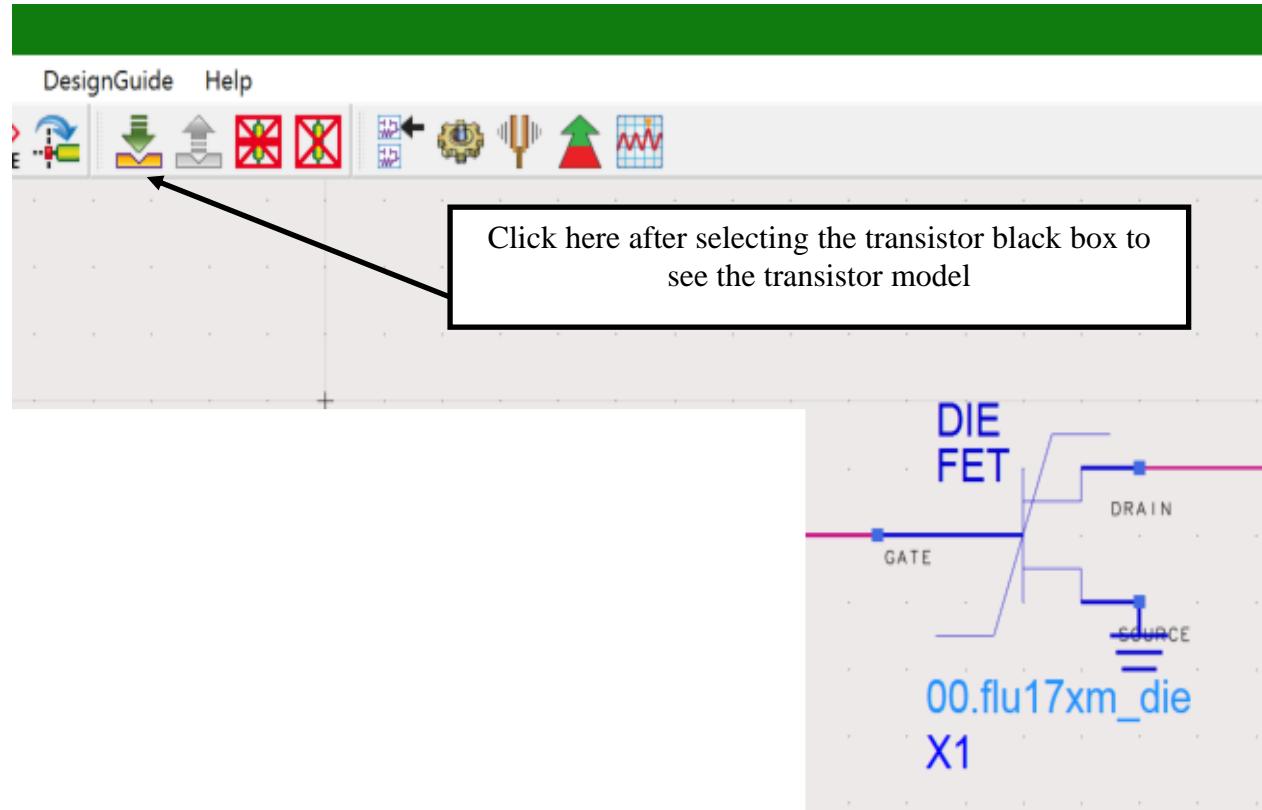


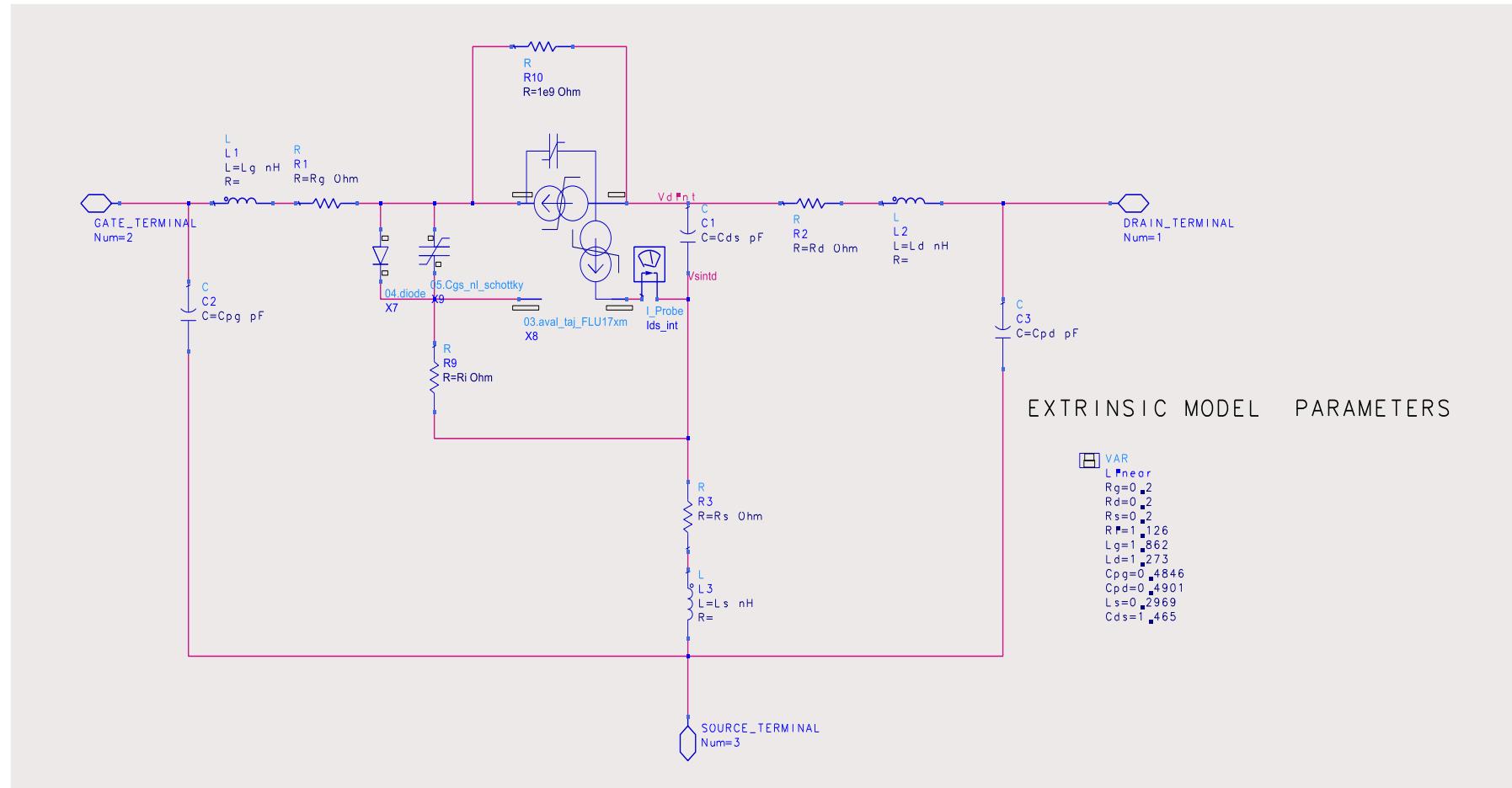
The *01.flu17xm_package.dsn* file defines the non-linear packaged model of the FET. The figure below represents the symbol associated to this model (and to this file). You can click on *Window/symbol* in the *Window* menu.



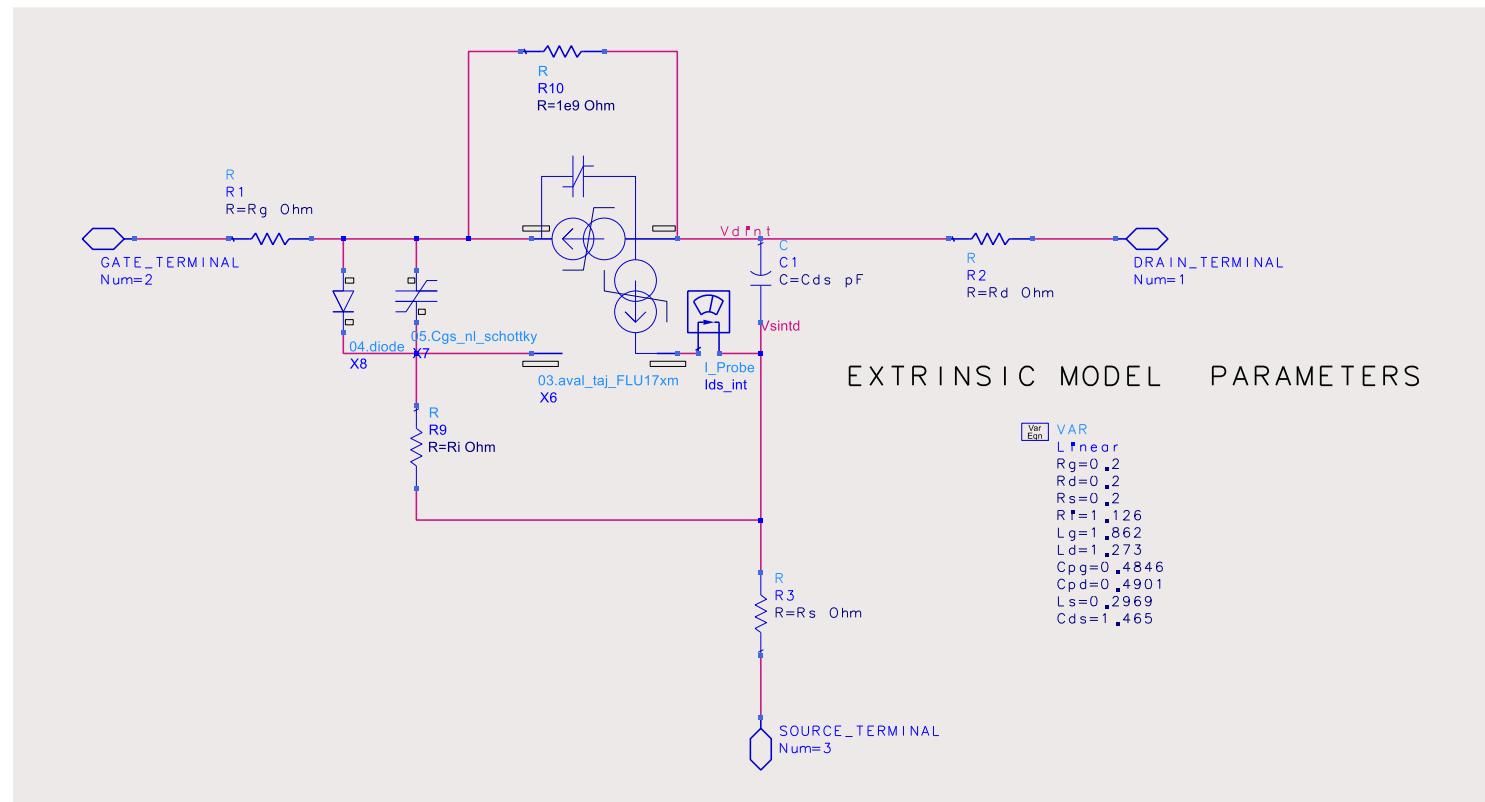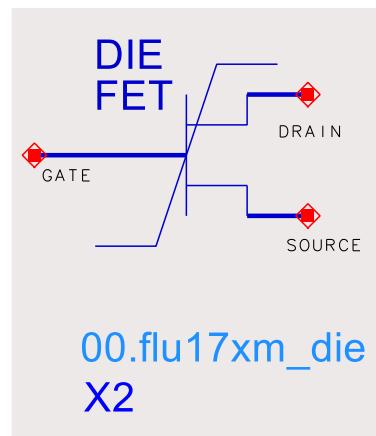
The *00.flu17xm_package.dsn* file defines the non-linear packaged model of the FET. The figure below represents the symbol associated to this model (and to this file). You can click on *Window/symbol* in the *Window* menu.



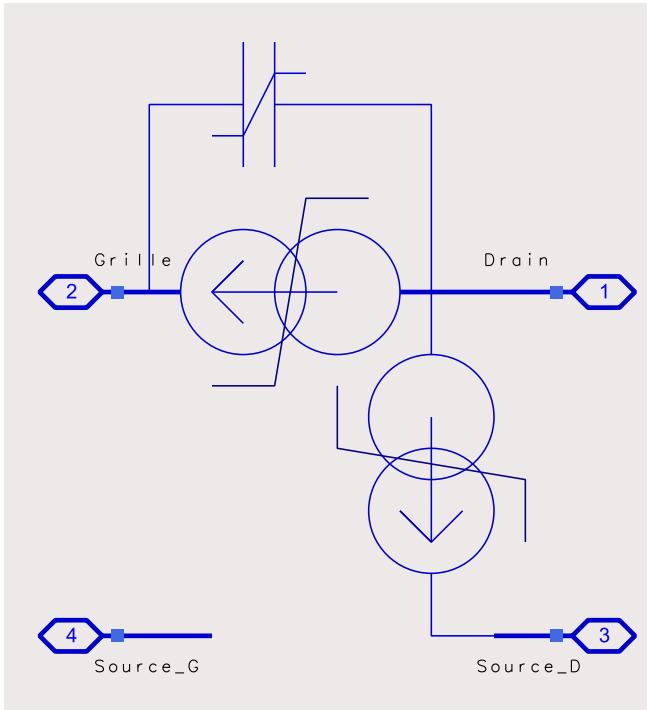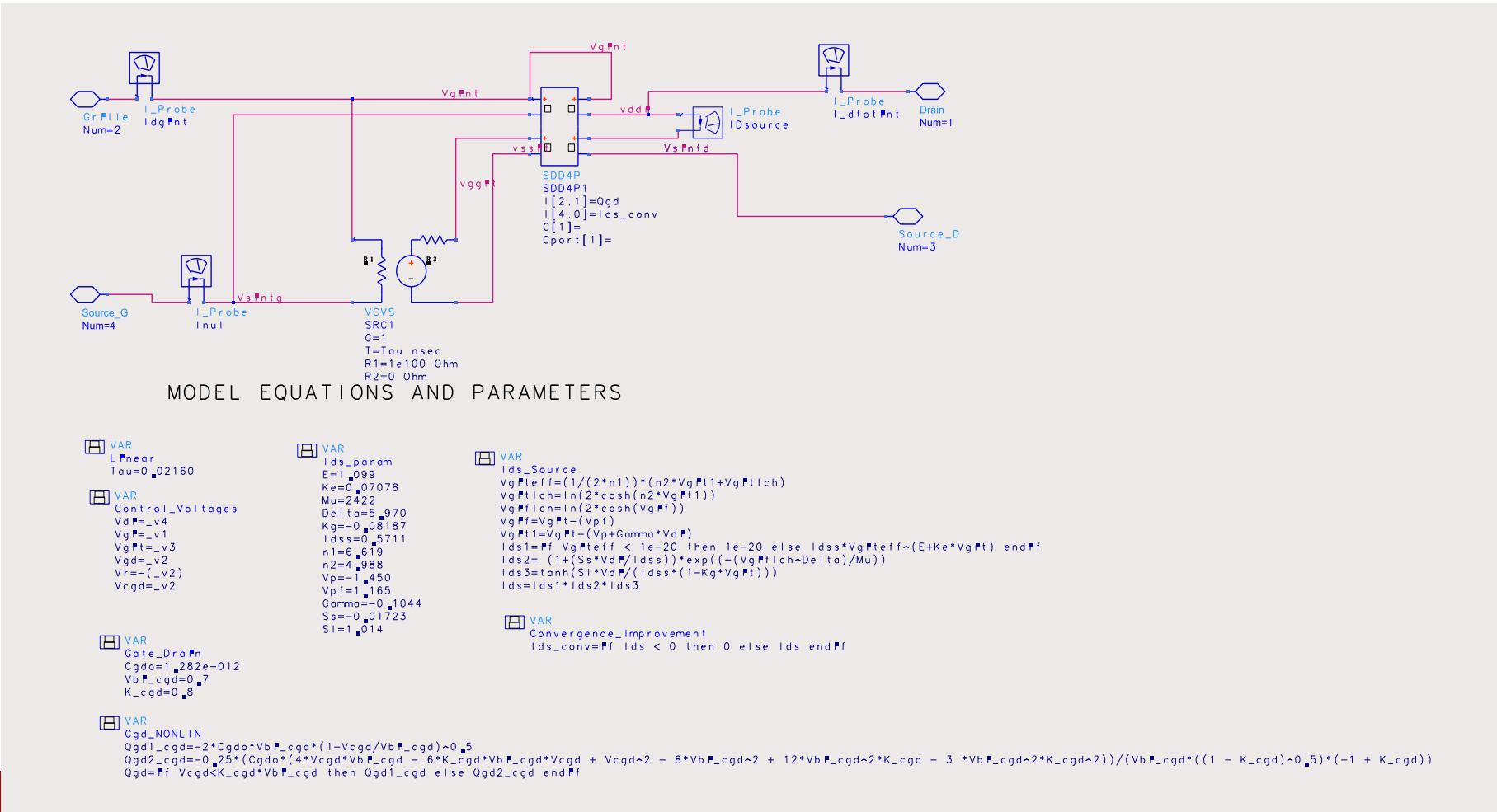The *aval_taj.dsn* file defines the non-linear intrinsic model of the FET. The figure below represents the symbol associated to this model (and to this file). You can click on *Window/symbol* in the *Window* menu.



Cgs Non linear EQUATIONS AND PARAMETERS

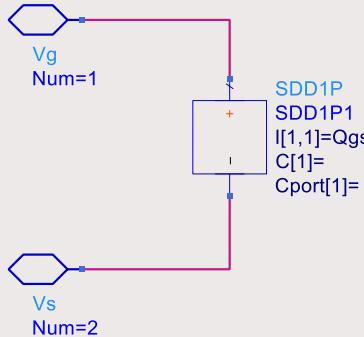


Var Eqn VAR
Control_Voltages
Vcgs=_v1

Var Eqn VAR
Gate_Source
Cgso=9.592e-012
Vbi_cgs=0.8
K_cgs=0.8


Var Eqn VAR
Cgs_NONLIN
Qgs1_cgs=-2*Cgso*Vbi_cgs*(1-Vcgs/Vbi_cgs)^0.5
Qgs2_cgs=-0.25*(Cgso*(4*Vcgs*Vbi_cgs - 6*K_cgs*Vbi_cgs*Vcgs + Vcgs^2 - 8*Vbi_cgs^2 + 12*Vbi_cgs^2*K_cgs - 3 *Vbi_cgs^2*K_cgs^2))/((Vbi_cgs*((1 - K_cgs)^0.5)*(-1 + K_cgs)))
Qgs;if Vcgs<K_cgs*Vbi_cgs then Qgs1_cgs else Qgs2_cgs endif

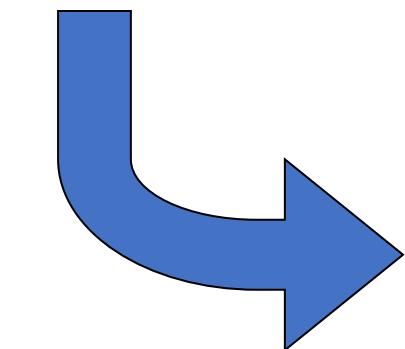The
Cgs_nl_schottky.dsn
file defines the non-
linear model of the
C_{GS} capacitance of the
FET.



Associated symbol



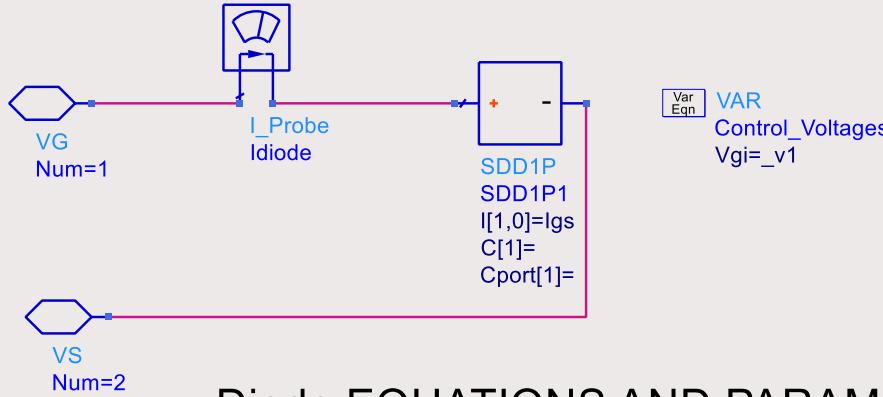


Diode EQUATIONS AND PARAMETERS


Var Eqn VAR
lgS_NONLIN
as_igs=Alphas_igs*Vgi
bs_igs=Alphas_igs*Vgi-Ms_igs
I1_igs=Ins_igs*(exp(Ms_igs)*(1+bs_igs+bs_igs^2/2)-1)
I2_igs;if as_igs<-20 then -Ins_igs else Ins_igs*(exp(as_igs)-1) endif
Igs;if bs_igs>0 then I1_igs else I2_igs endif

Var Eqn VAR
Gate_Source
Ins_igs=4.822e-011
Ms_igs=40
Alphas_igs=29.1
Cgso=9.592e-012
Vbi_cgs=0.8
K_cgs=0.8


Associated symbol

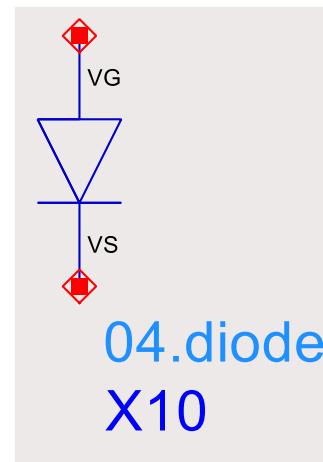

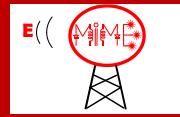The *Diode.dsn* file defines the non-linear model of the input Diode of the FET.



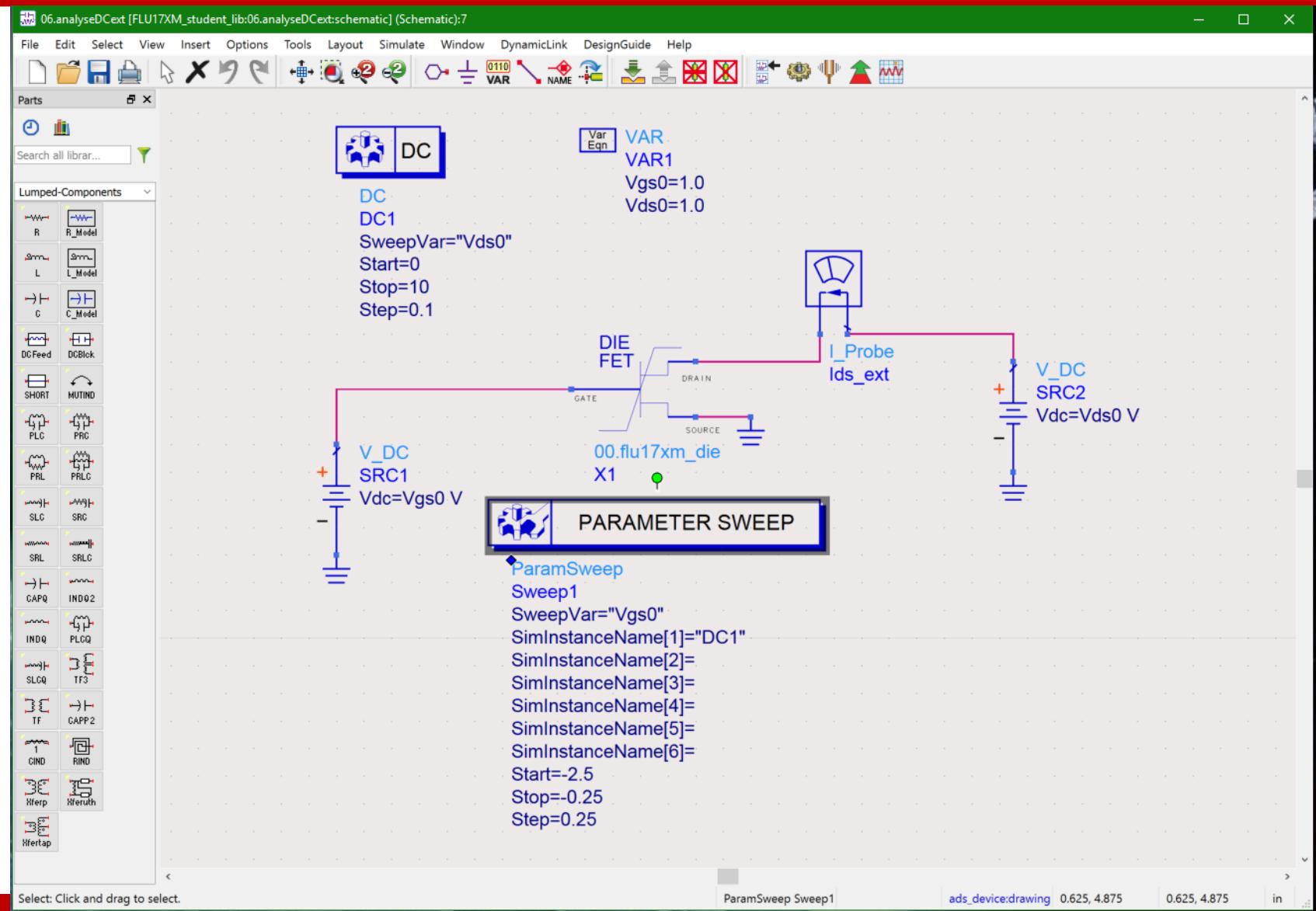
Schematic to plot the extrinsic I/V curves of the Die transistor




Basics of Active and Non-Linear Electronics : PW

Date

- 9 -

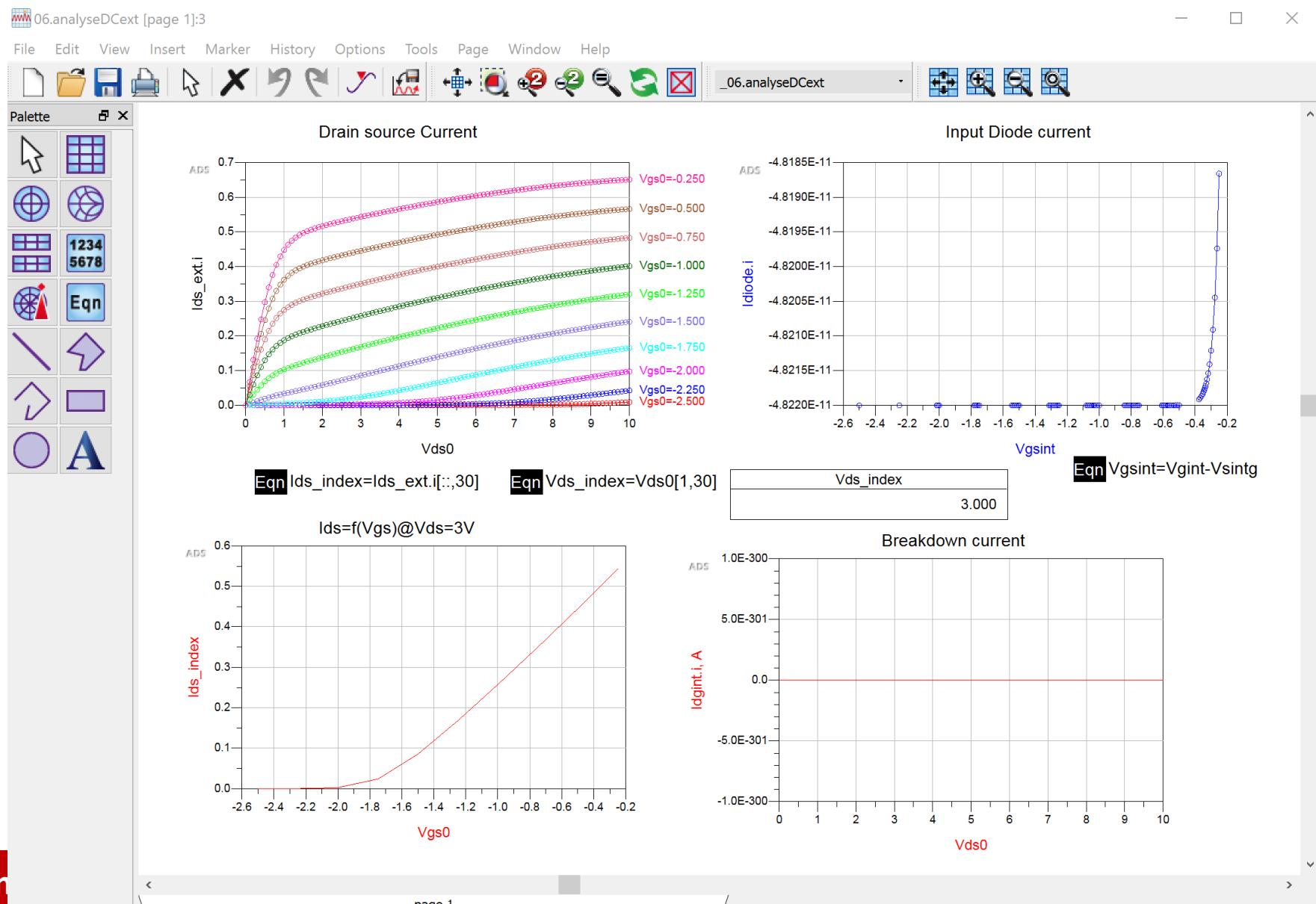

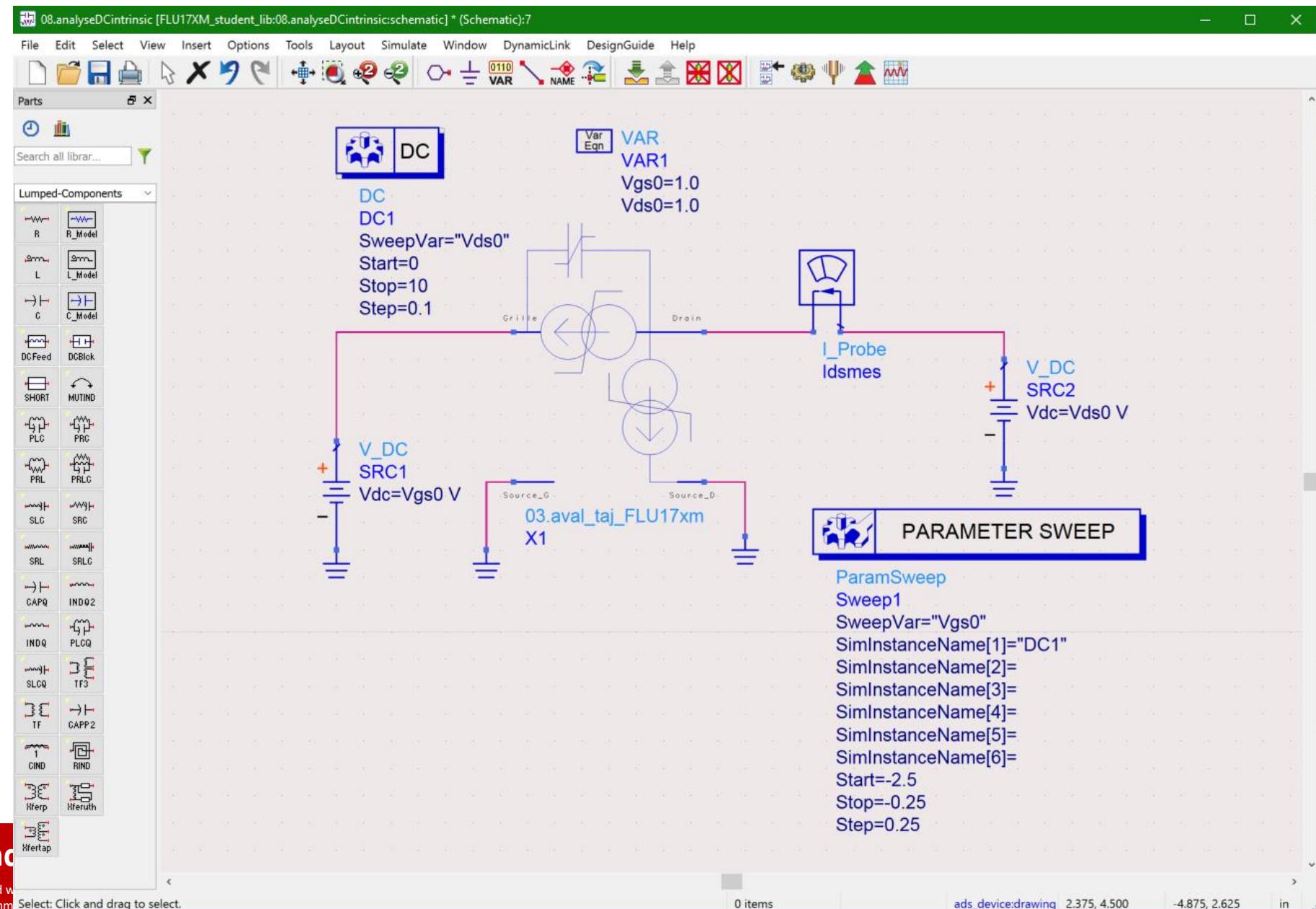Schematic to plot the
intrinsic I/V curves of the
Die transistor



Basics of Active and

Copyright notice : This material can be freely used
reflects the views only of the author, and the Comm


Select: Click and drag to select.

0 items


ads_device:drawing 2.375, 4.500

-4.875, 2.625

This publication







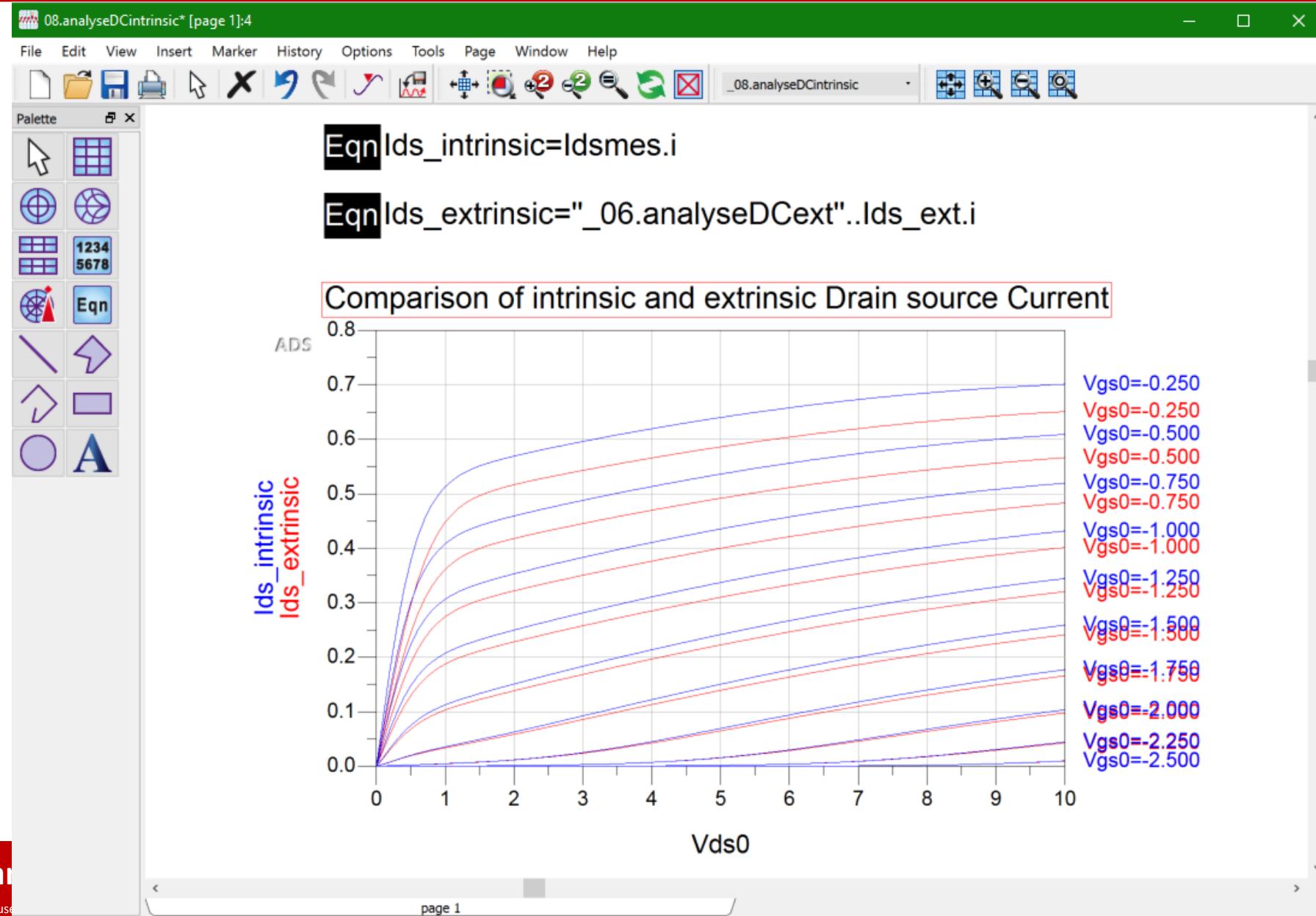





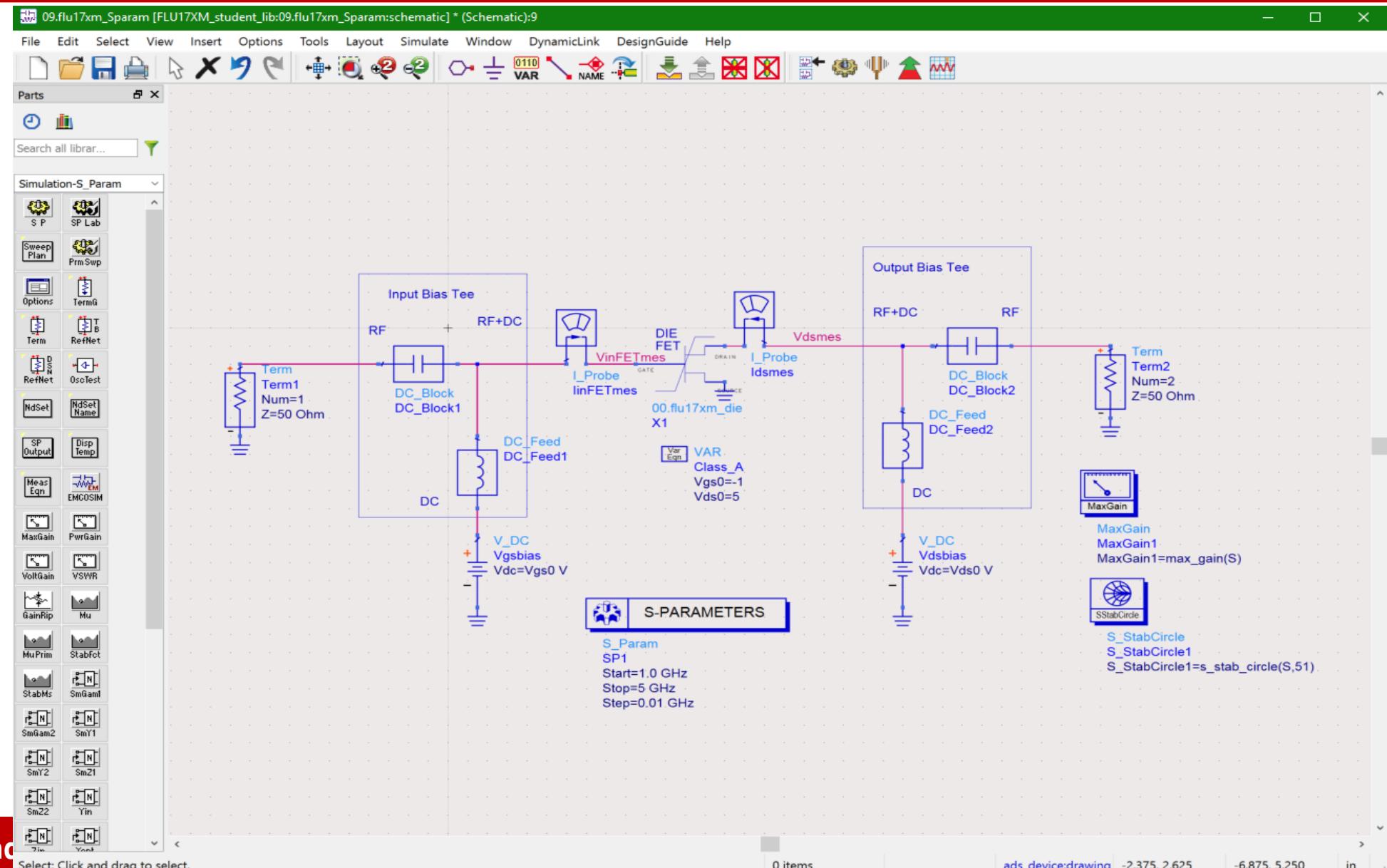
Schematic to plot the S parameter curves of the Die transistor



Work Frequency Selection :
Choose the value of index_freq to choose the desired frequency
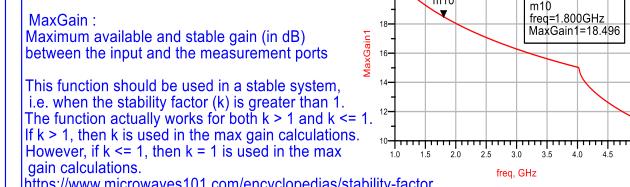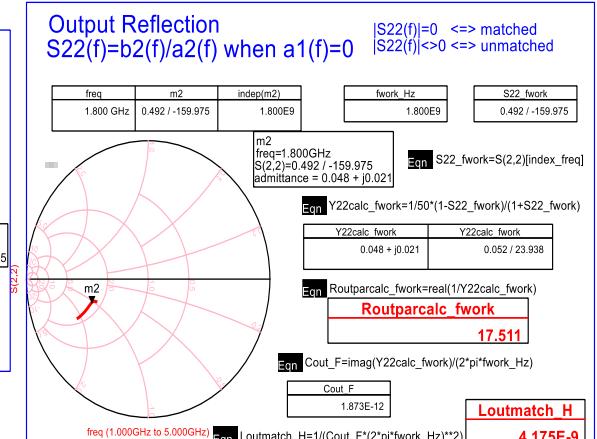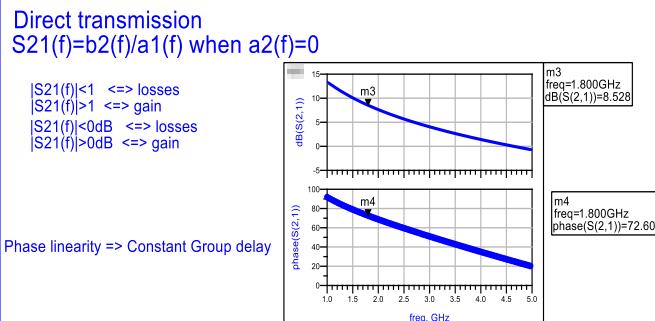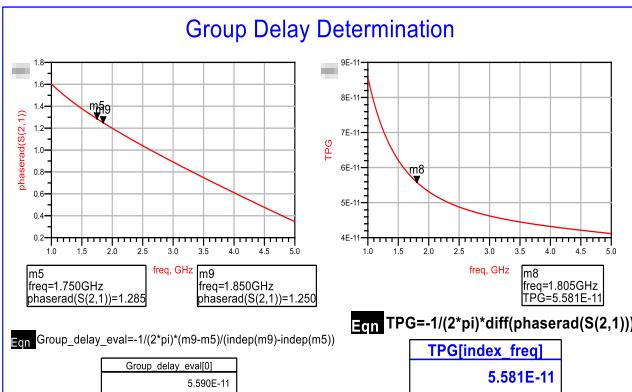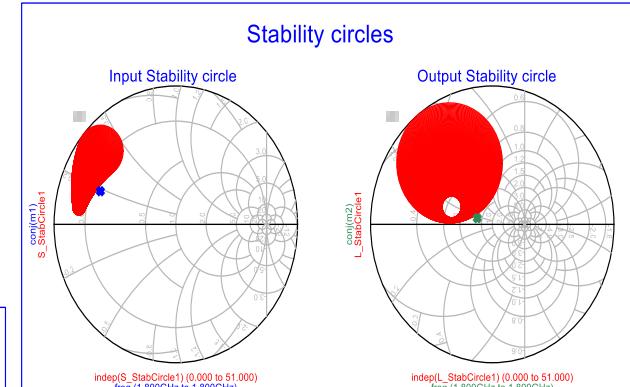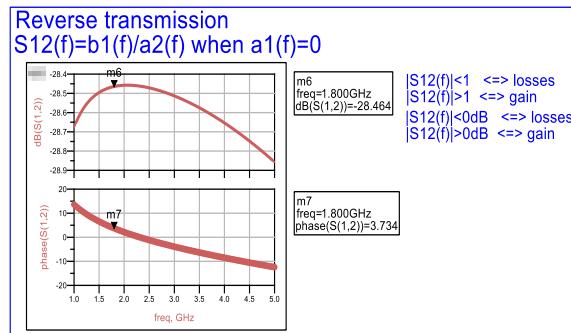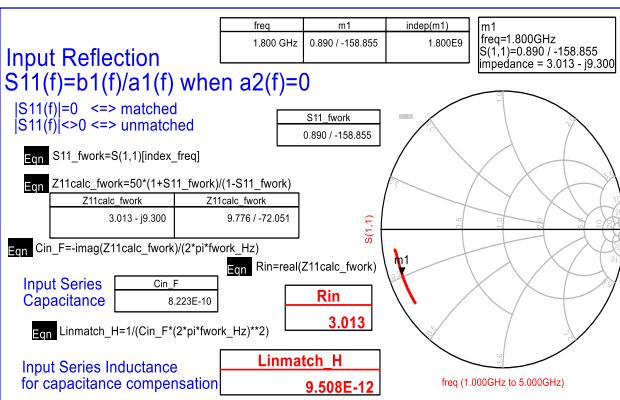
```
Eqn index_freq=80
Eqn fwork_Hz=freq[index_freq]
```



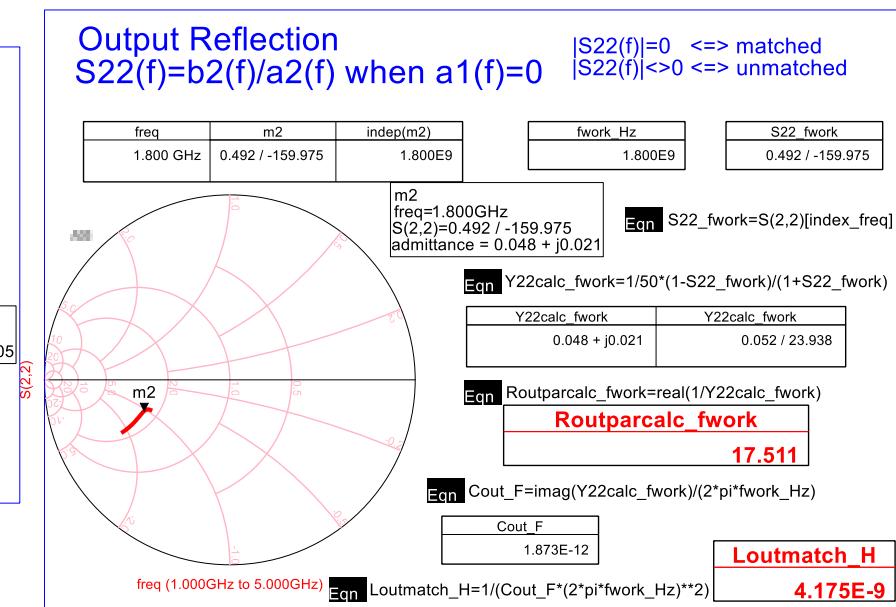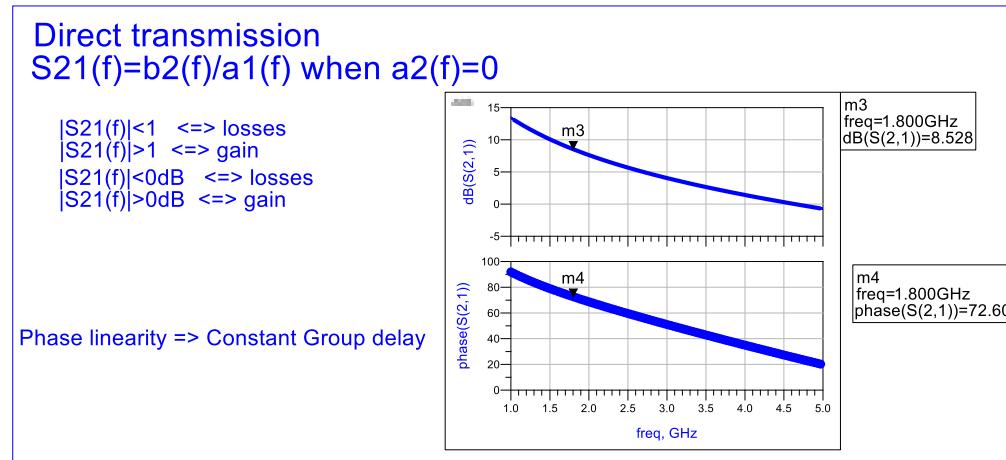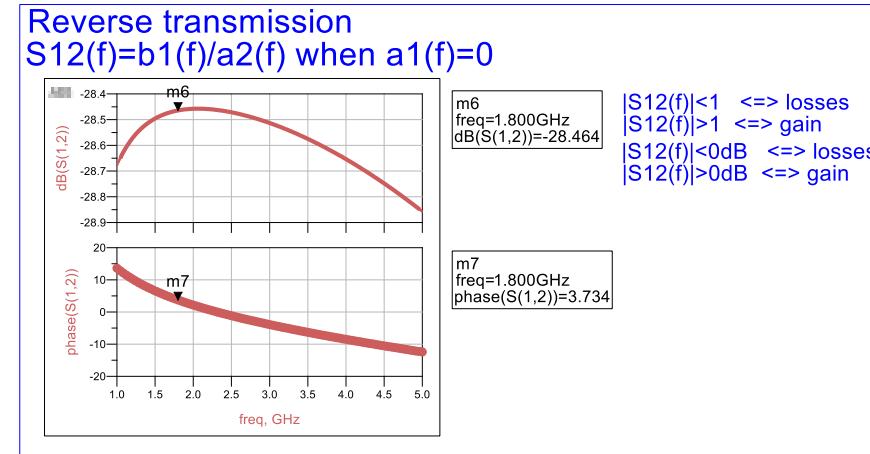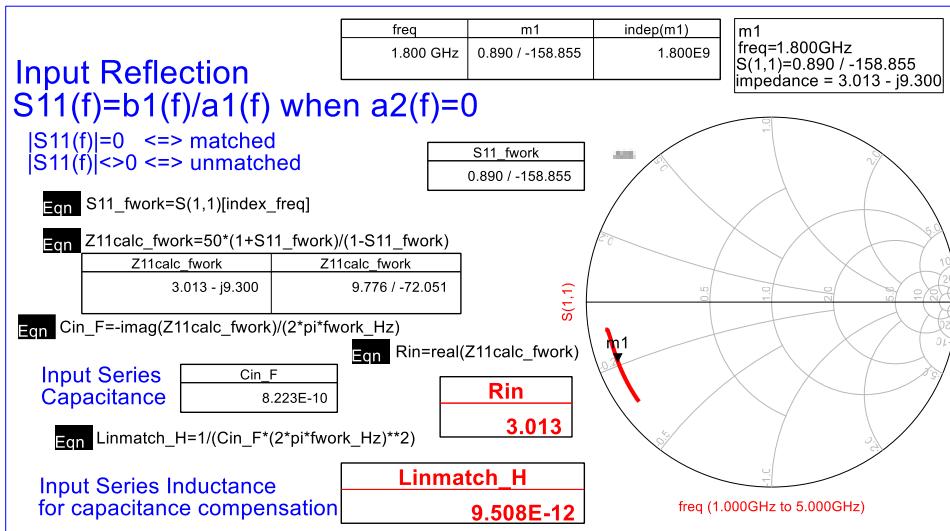

Input Reflection

$S_{11}(f)=b_1(f)/a_1(f)$ when $a_2(f)=0$

$|S_{11}(f)|=0 \Leftrightarrow$ matched
 $|S_{11}(f)|>0 \Leftrightarrow$ unmatched

| freq | m1 | indep(m1) |
|-----------|------------------|-----------|
| 1.800 GHz | 0.890 / -158.855 | 1.800E9 |

m1
freq=1.800GHz
 $S(1,1)=0.890 / -158.855$
impedance = $3.013 - j9.300$

Eqn $S_{11_fwork}=S(1,1)[\text{index_freq}]$

| S_{11_fwork} |
|------------------|
| 0.890 / -158.855 |

Eqn $Z_{11\text{calc_fwork}}=50*(1+S_{11_fwork})/(1-S_{11_fwork})$

| $Z_{11\text{calc_fwork}}$ | $Z_{11\text{calc_fwork}}$ |
|----------------------------|----------------------------|
| $3.013 - j9.300$ | $9.776 / -72.051$ |

Eqn $C_{in_F}=-\text{imag}(Z_{11\text{calc_fwork}})/(2*\pi*f_{work_Hz})$

Eqn $R_{in}=\text{real}(Z_{11\text{calc_fwork}})$

Input Series
Capacitance


| C_{in_F} |
|-------------|
| $8.223E-10$ |

Eqn $L_{inmatch_H}=1/(C_{in_F}*(2*\pi*f_{work_Hz})^2)$


R_{in}
3.013

Input Series Inductance
for capacitance compensation

Linmatch_H
9.508E-12

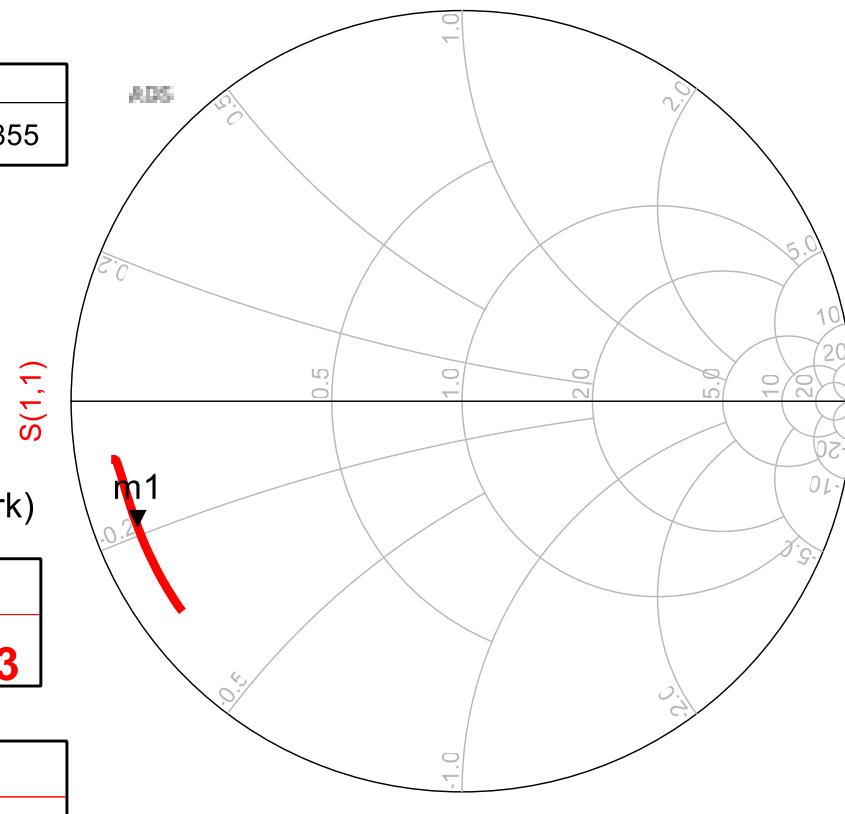

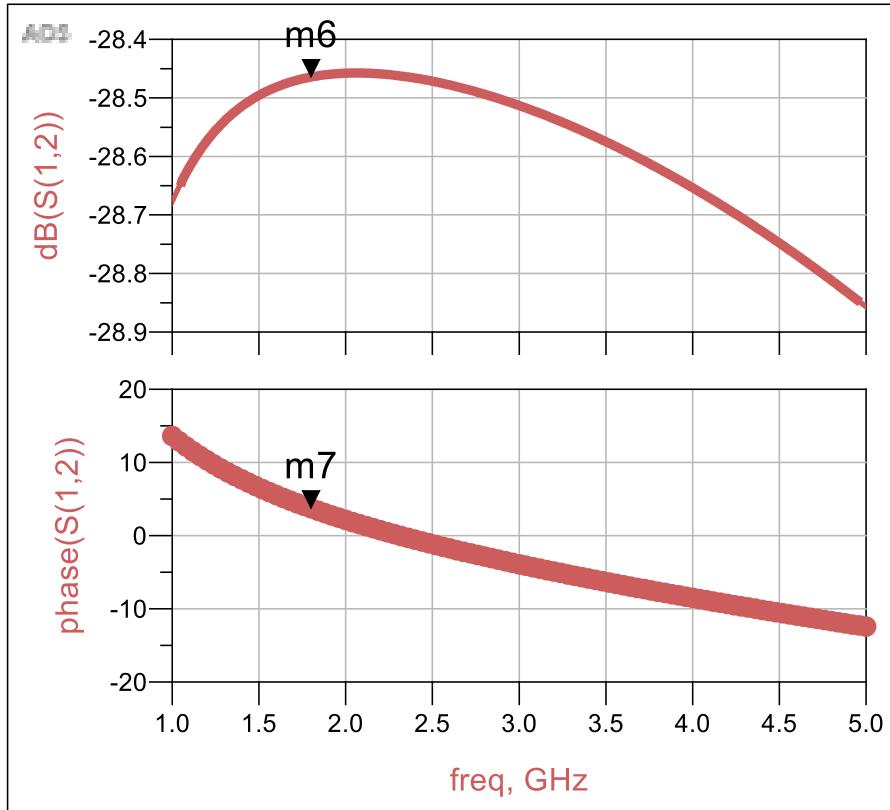Reverse transmission $S_{12}(f)=b_1(f)/a_2(f)$ when $a_1(f)=0$



m6
freq=1.800GHz
dB(S(1,2))=-28.464

$|S_{12}(f)|<1 \Leftrightarrow$ losses
 $|S_{12}(f)|>1 \Leftrightarrow$ gain
 $|S_{12}(f)|<0\text{dB} \Leftrightarrow$ losses
 $|S_{12}(f)|>0\text{dB} \Leftrightarrow$ gain


m7
freq=1.800GHz
phase(S(1,2))=3.734

Direct transmission $S_{21}(f)=b_2(f)/a_1(f)$ when $a_2(f)=0$

$|S_{21}(f)| < 1 \Leftrightarrow$ losses
 $|S_{21}(f)| > 1 \Leftrightarrow$ gain

$|S_{21}(f)| < 0\text{dB} \Leftrightarrow$ losses
 $|S_{21}(f)| > 0\text{dB} \Leftrightarrow$ gain

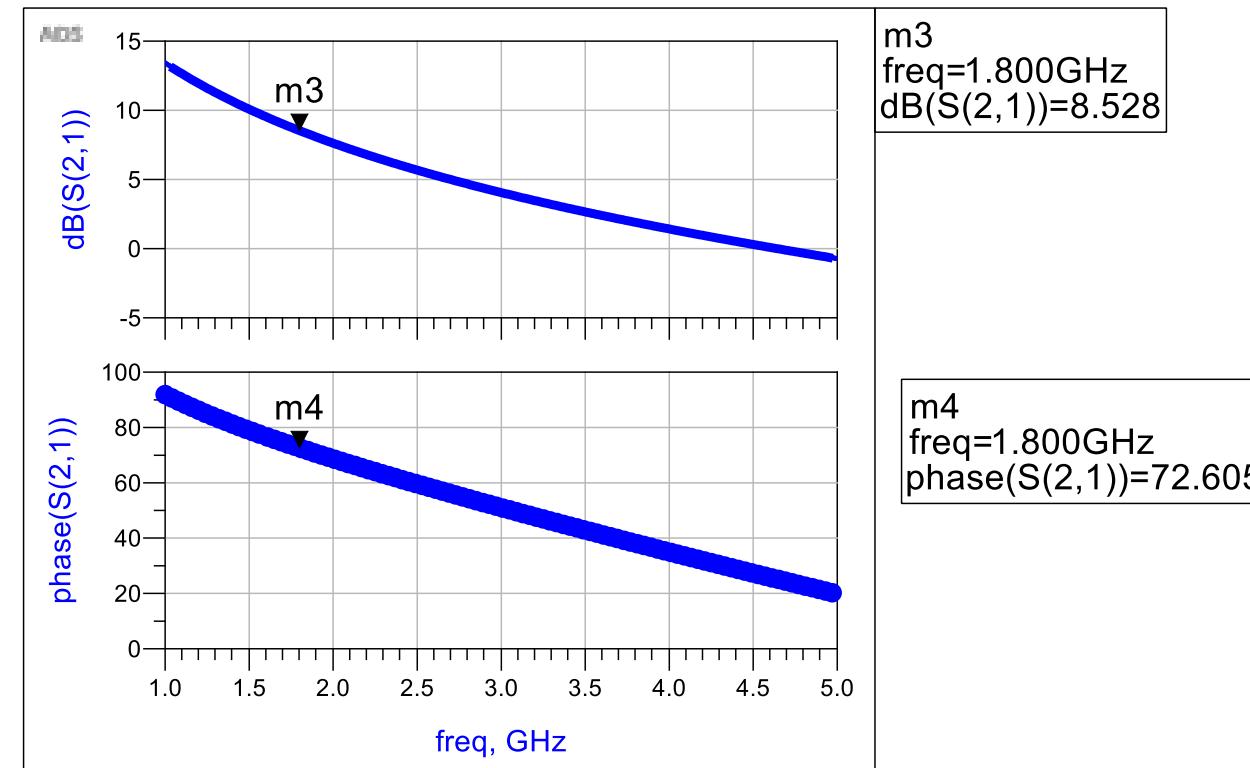Phase linearity \Rightarrow Constant Group delay




Output Reflection $S_{22}(f)=b_2(f)/a_2(f)$ when $a_1(f)=0$

$|S_{22}(f)|=0 \Leftrightarrow$ matched
 $|S_{22}(f)|>0 \Leftrightarrow$ unmatched

| freq | m2 | indep(m2) |
|-----------|------------------|-----------|
| 1.800 GHz | 0.492 / -159.975 | 1.800E9 |

| fwork_Hz |
|----------|
| 1.800E9 |

| S22_fwork |
|------------------|
| 0.492 / -159.975 |

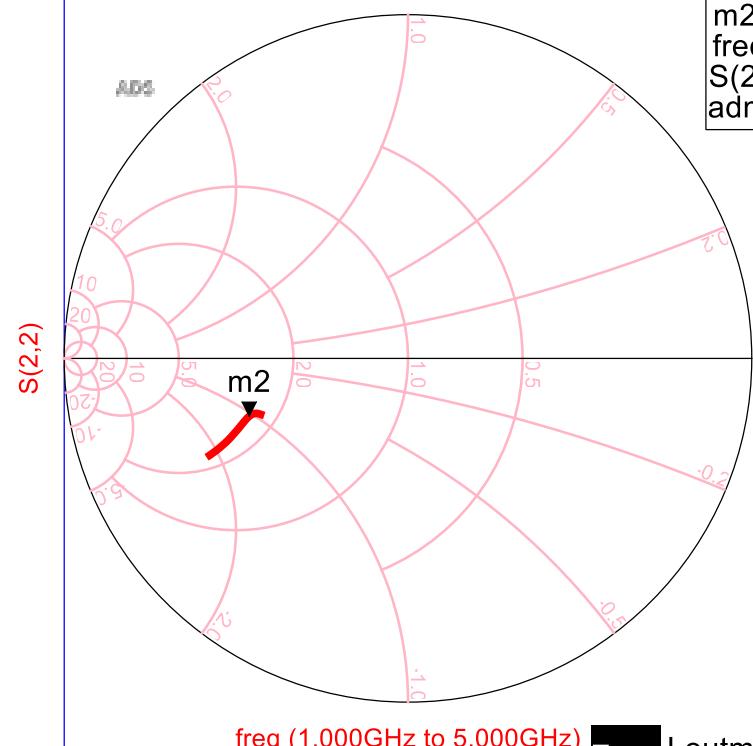

Eqn $S_{22_fwork}=S(2,2)[\text{index_freq}]$

Eqn $Y_{22\text{calc}_fwork}=1/50*(1-S_{22_fwork})/(1+S_{22_fwork})$

| Y22calc_fwork | Y22calc_fwork |
|------------------|------------------|
| $0.048 + j0.021$ | $0.052 / 23.938$ |

Eqn $R_{\text{outparcalc}_fwork}=\text{real}(1/Y_{22\text{calc}_fwork})$

Routparcalc_fwork

17.511


Eqn $C_{\text{out_F}}=\text{imag}(Y_{22\text{calc}_fwork})/(2*\pi*fwork_Hz)$

| Cout_F |
|-----------|
| 1.873E-12 |

Loutmatch_H


4.175E-9

Group Delay Determination

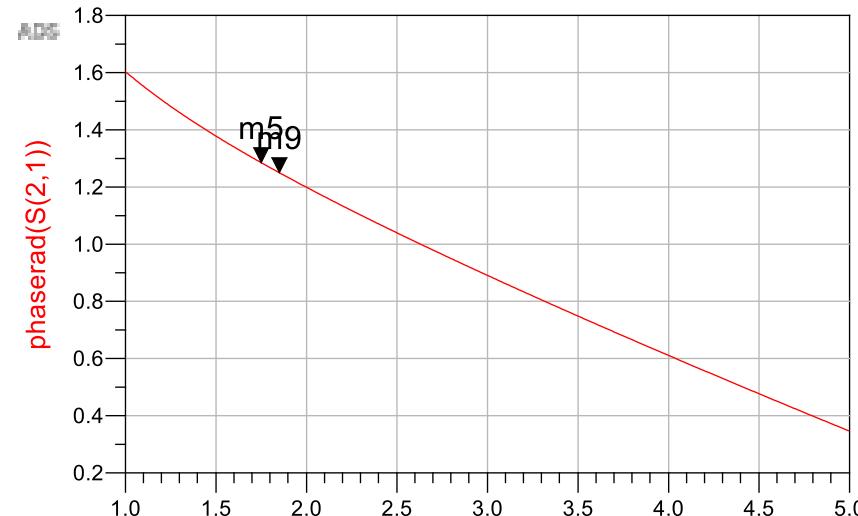


Eqn Group_delay_eval=-1/(2*pi)*(m9-m5)/(indep(m9)-indep(m5))

| |
|---------------------|
| Group_delay_eval[0] |
| 5.590E-11 |

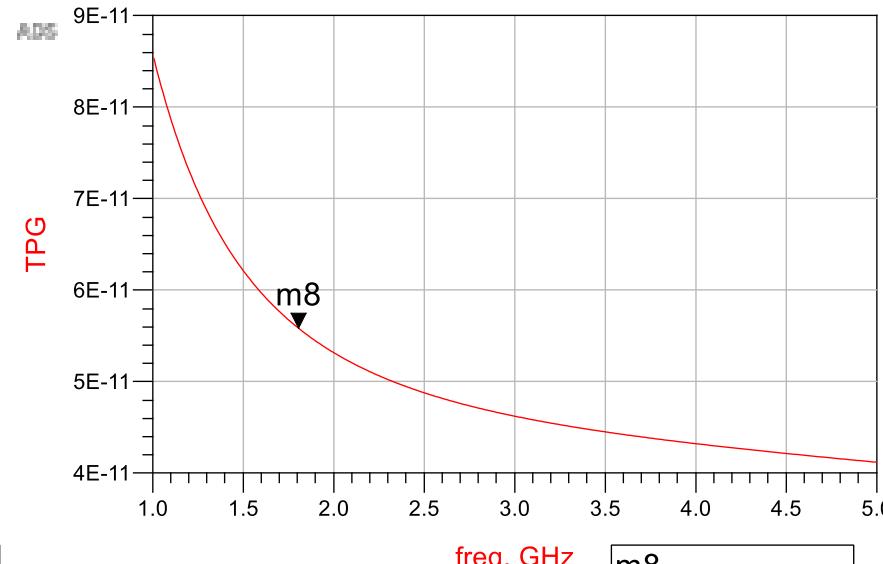


Eqn $TPG = -1/(2\pi) \cdot \text{diff}(\text{phaserad}(S(2,1)))$

| |
|-----------------|
| TPG[index_freq] |
| 5.581E-11 |

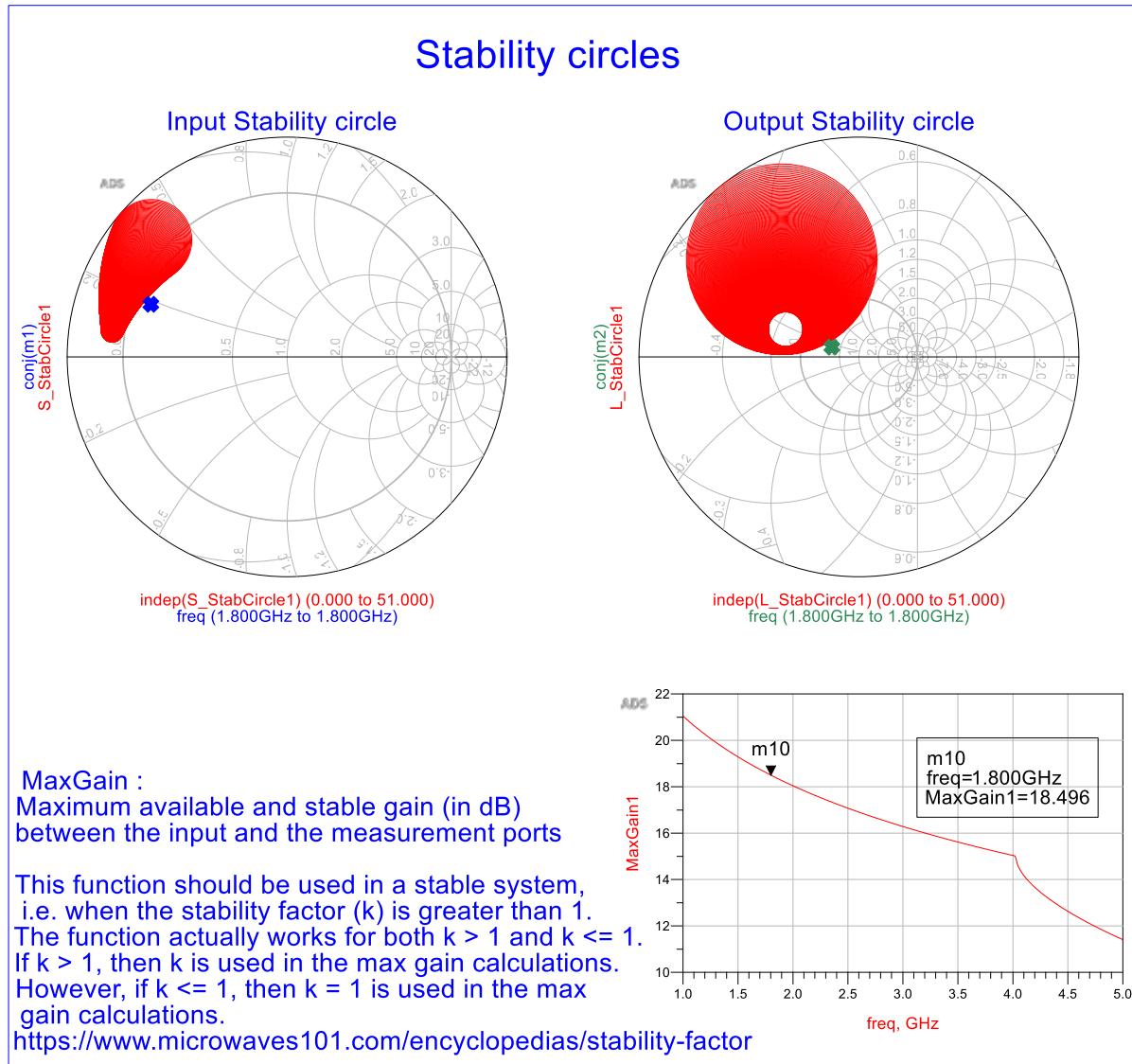

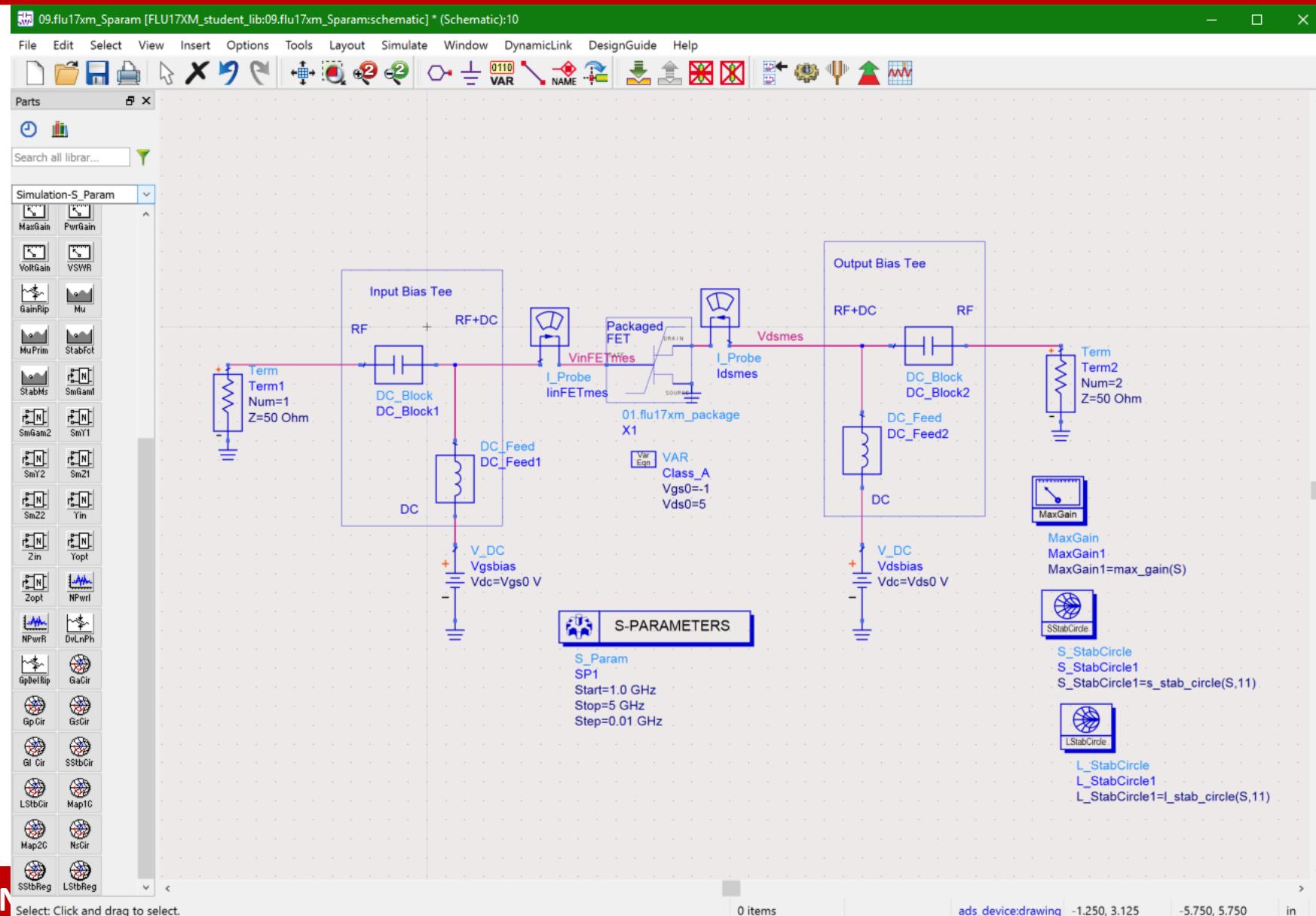Schematic to plot the S parameter curves of the Packaged transistor




Basics of Active and N


Select: Click and drag to select.


0 items



ads_device:drawing -1.250, 3.125 -5.750, 5.750


e

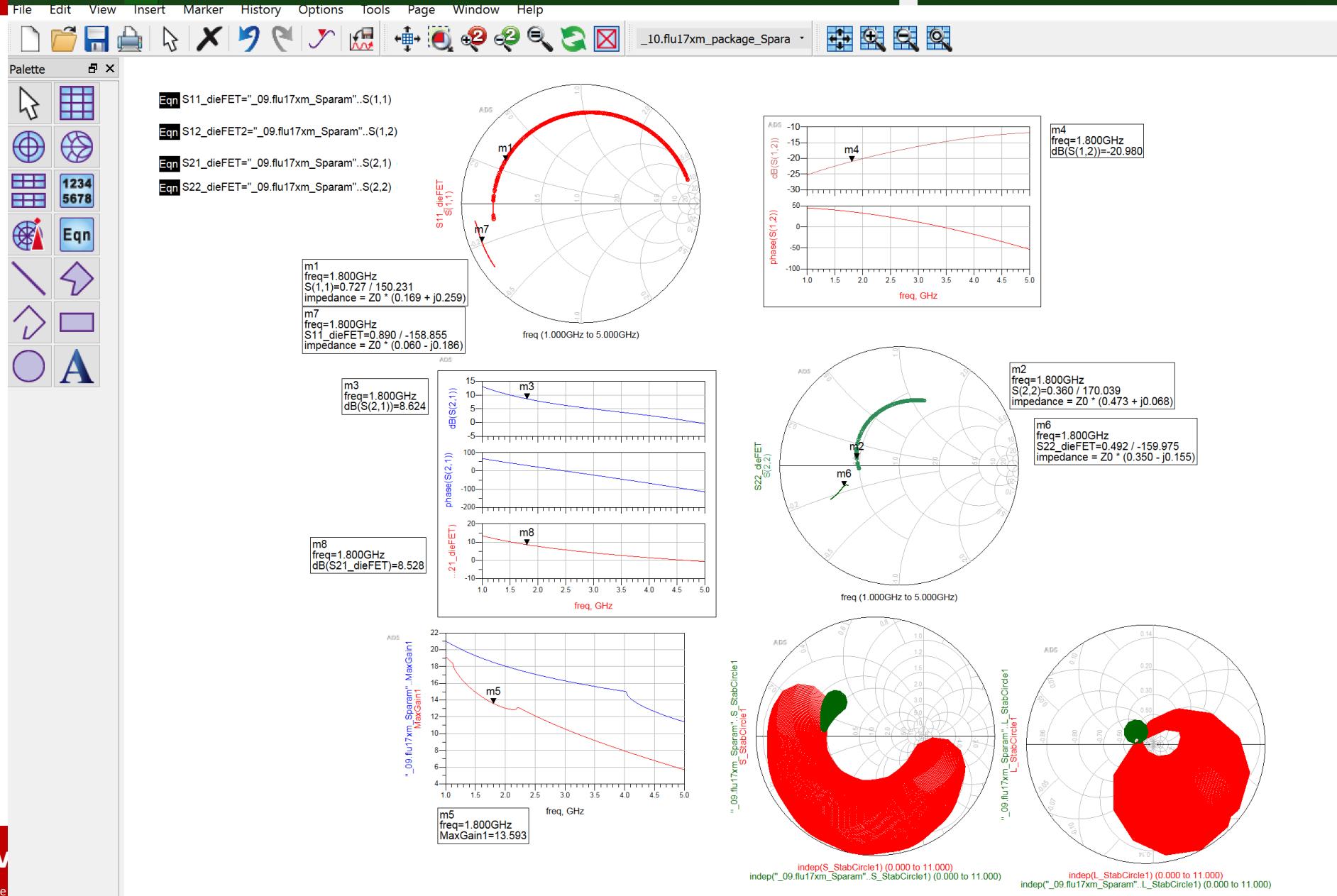


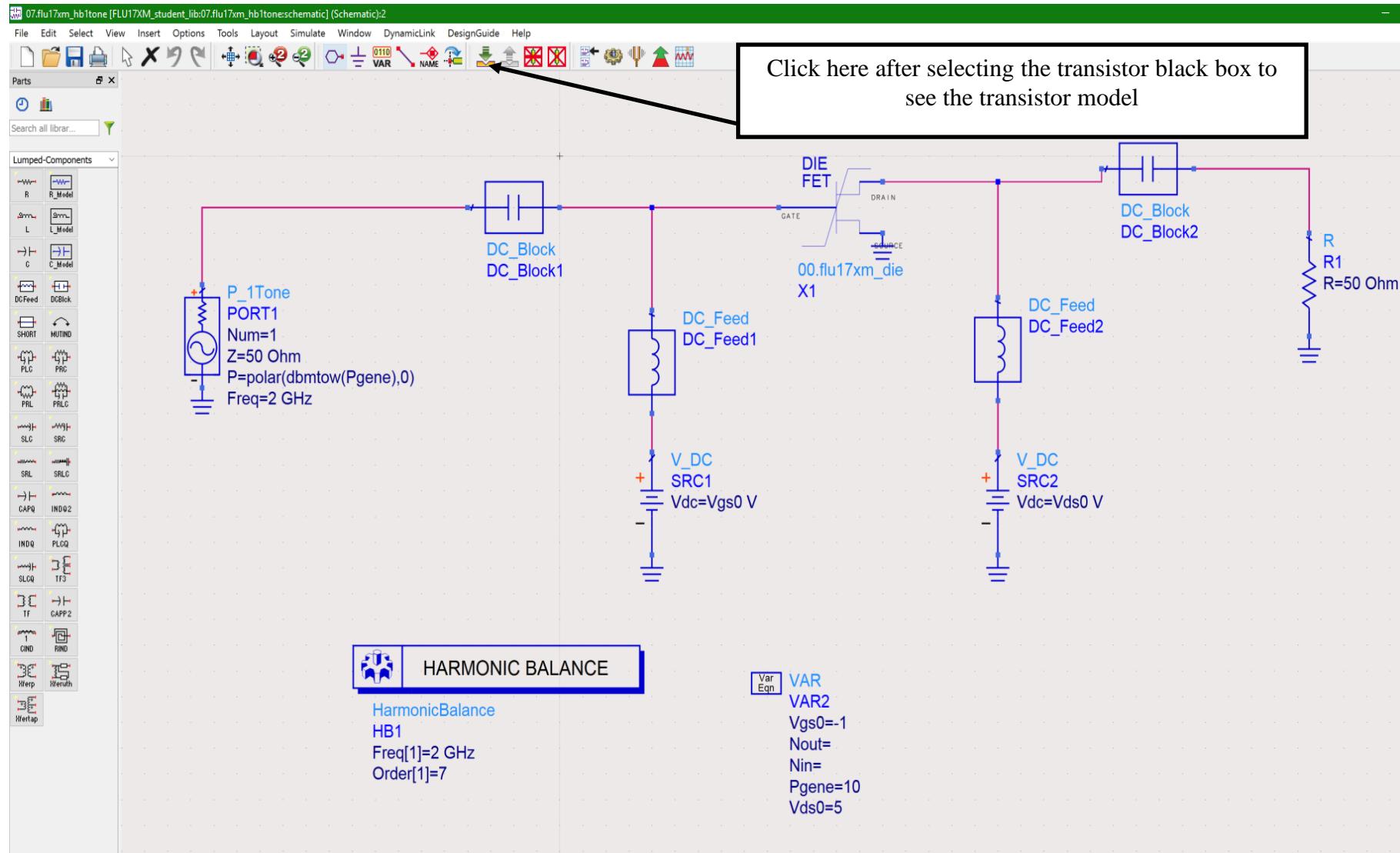


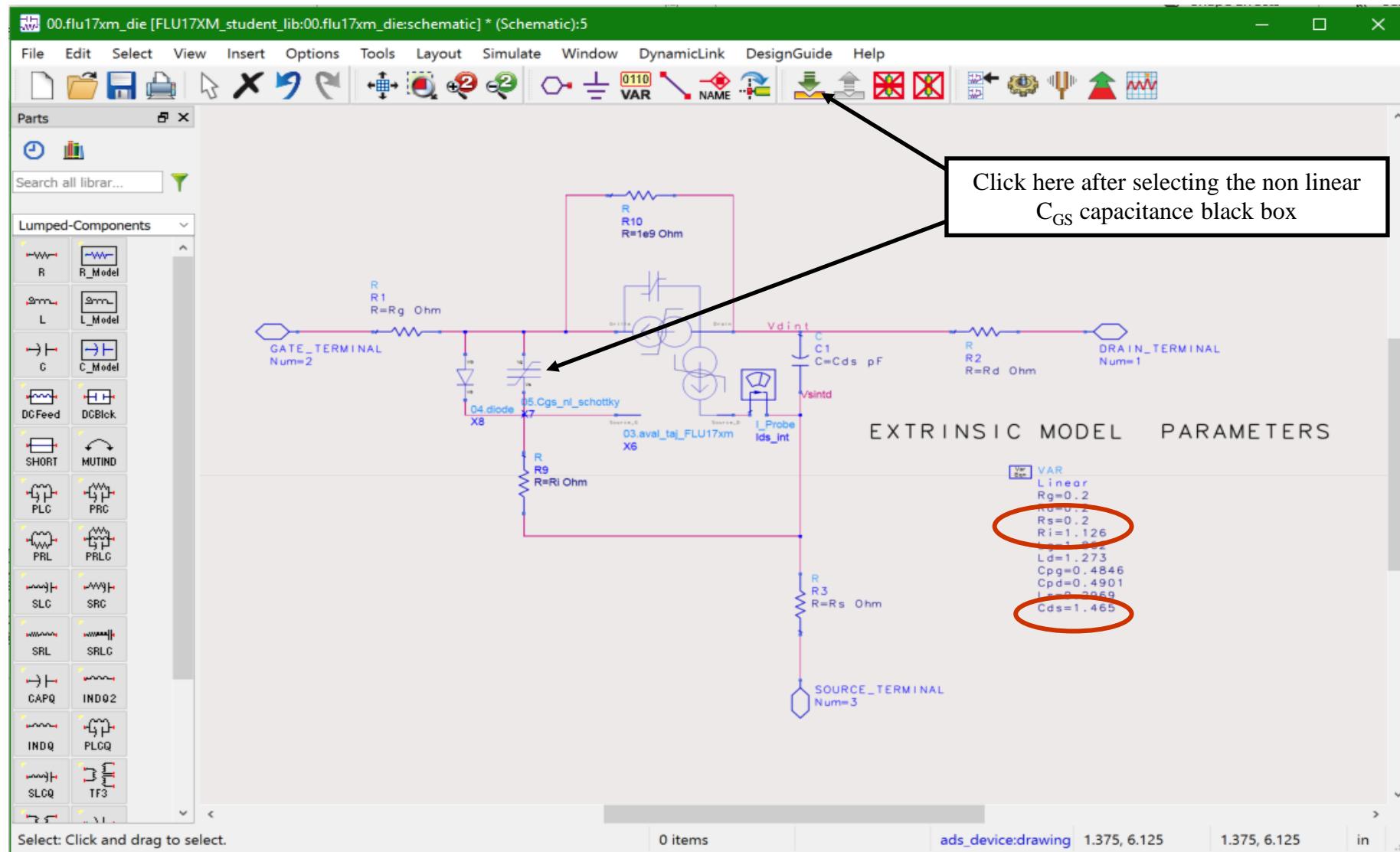


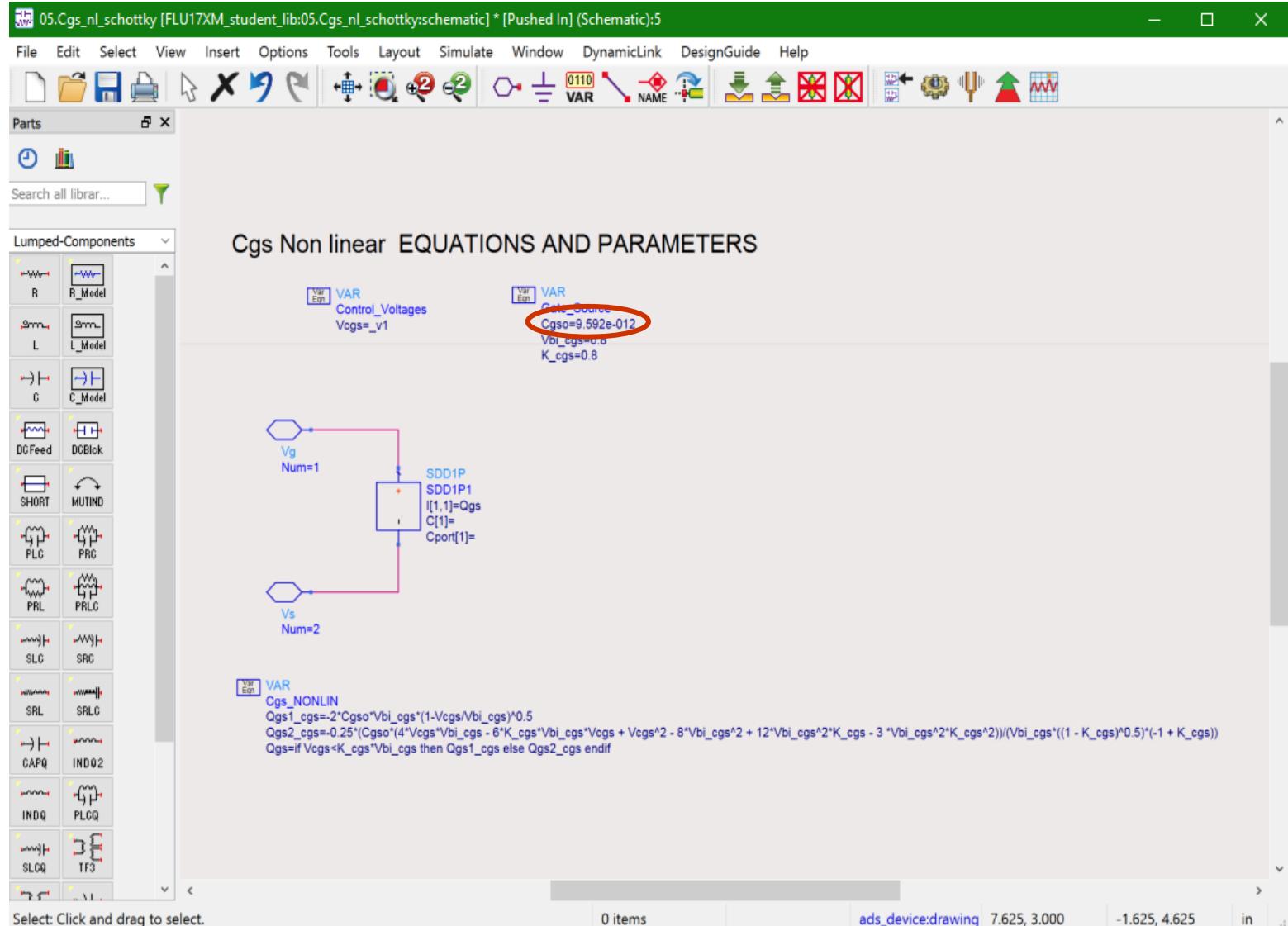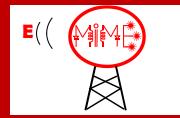


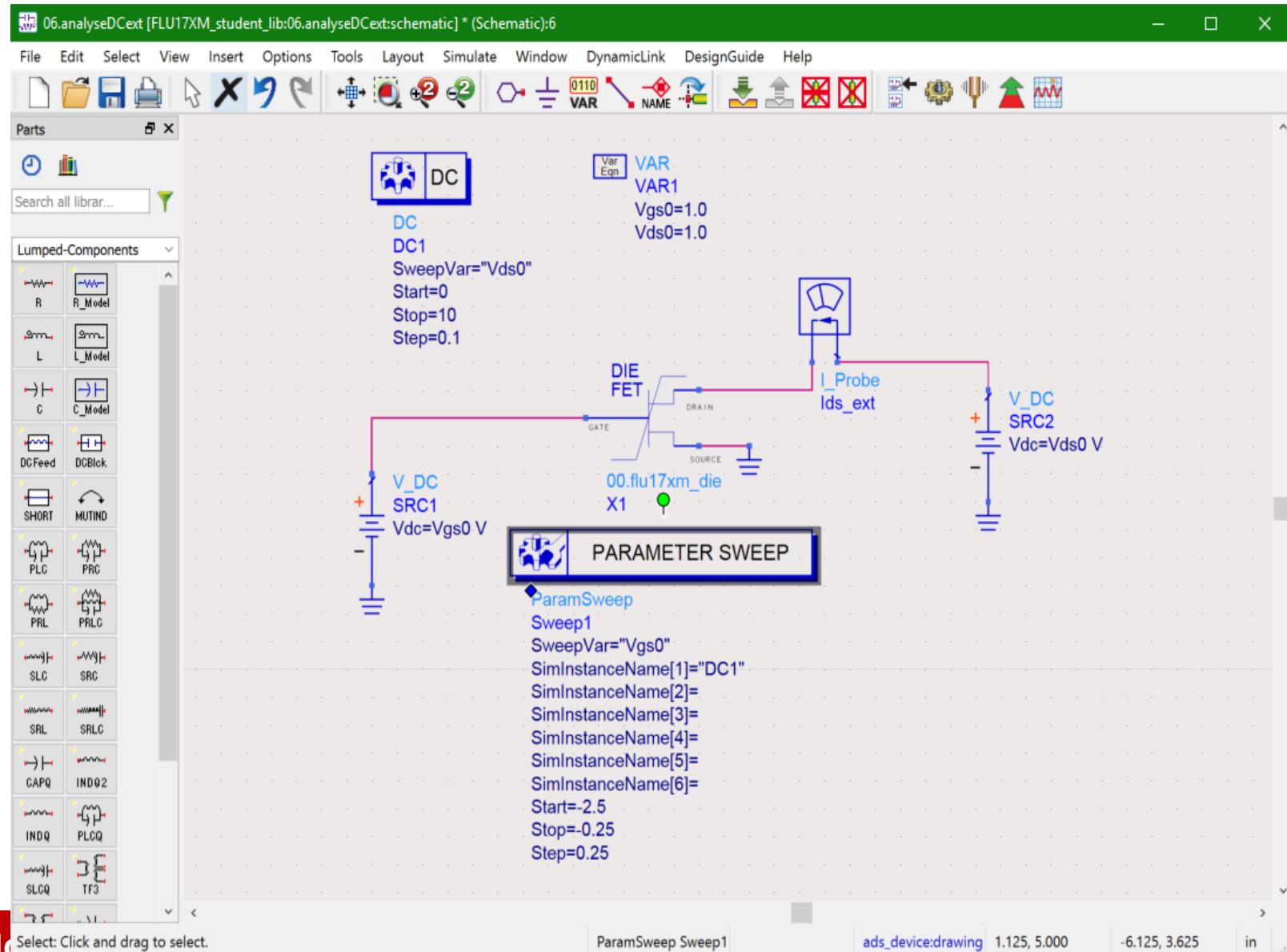


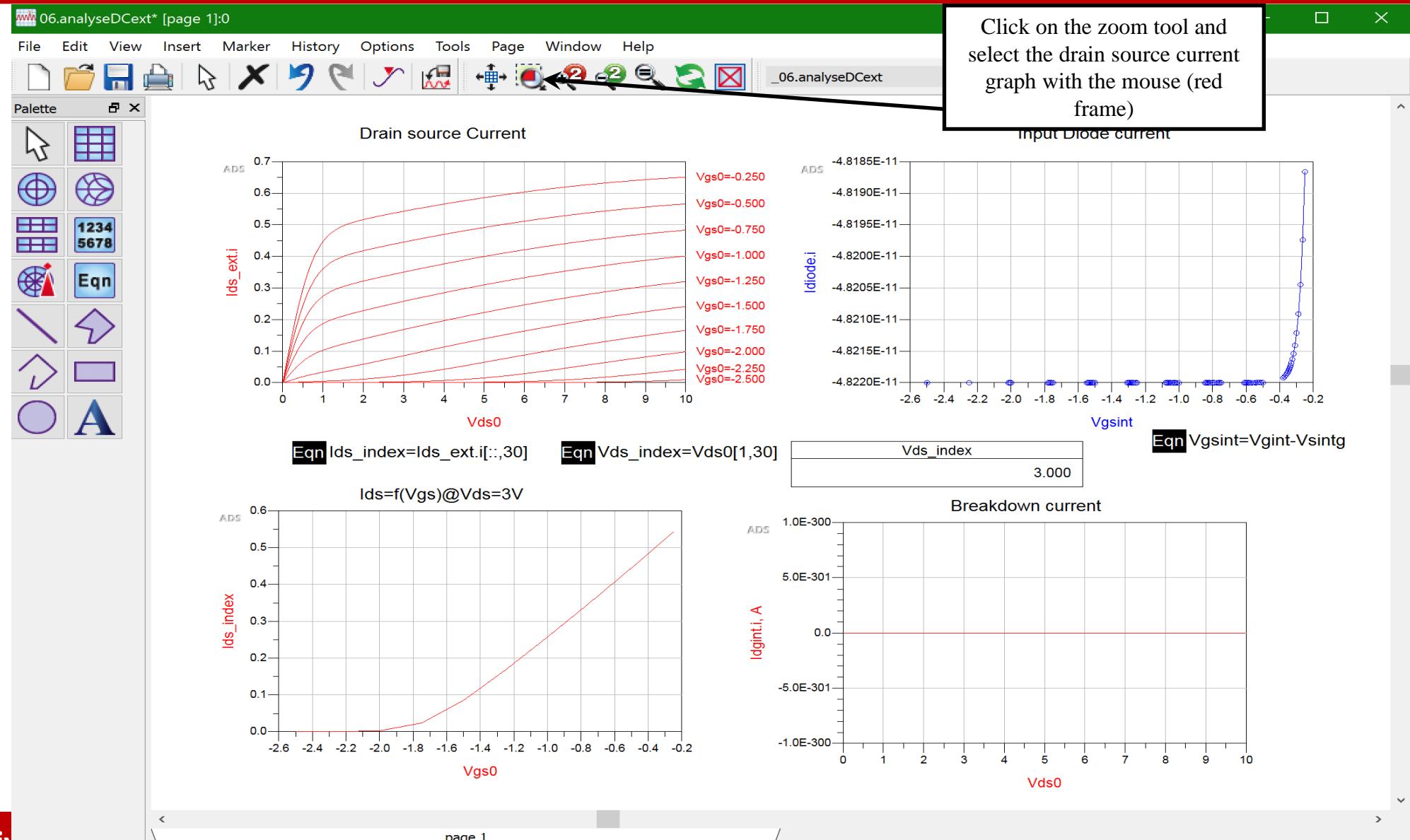

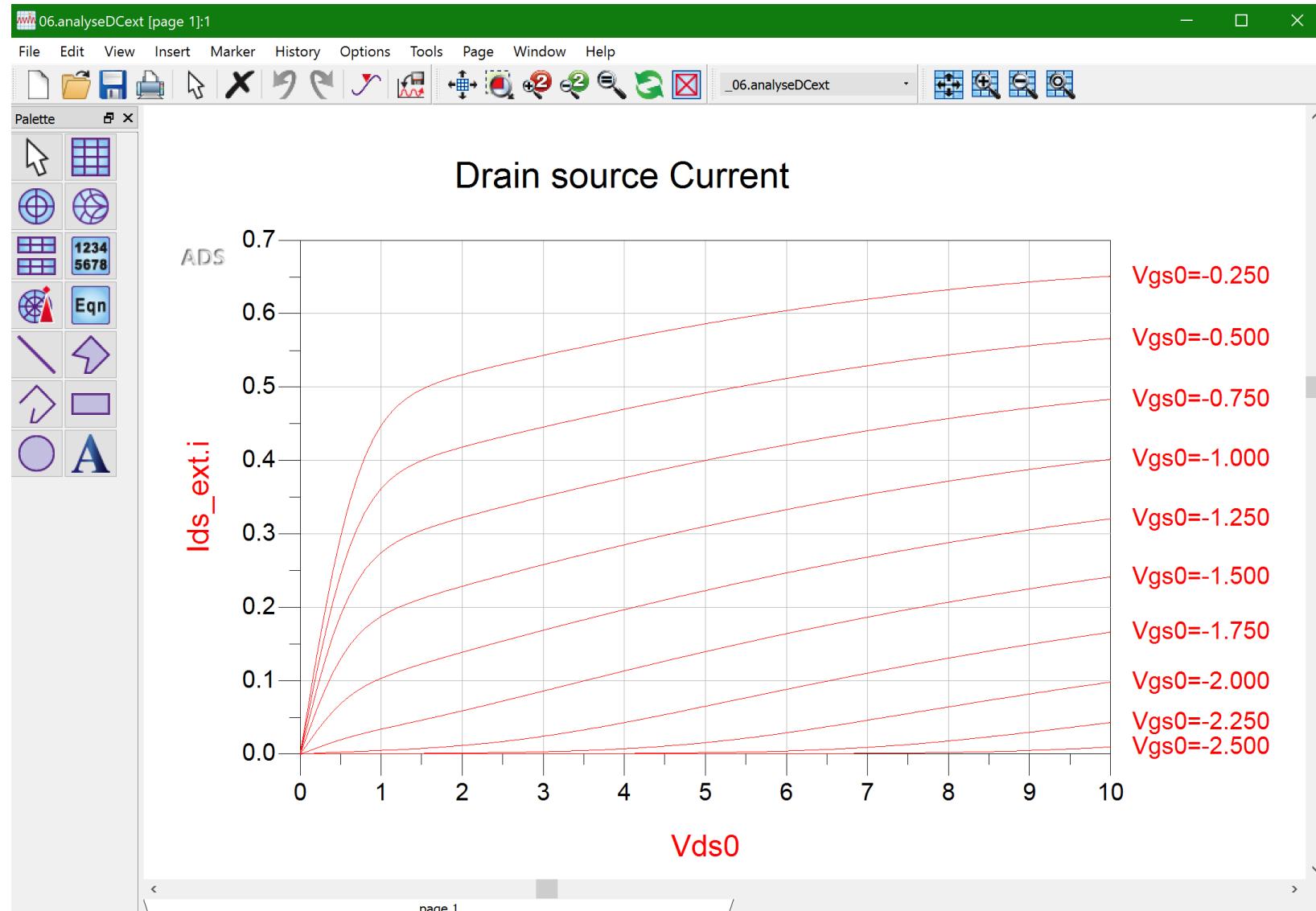


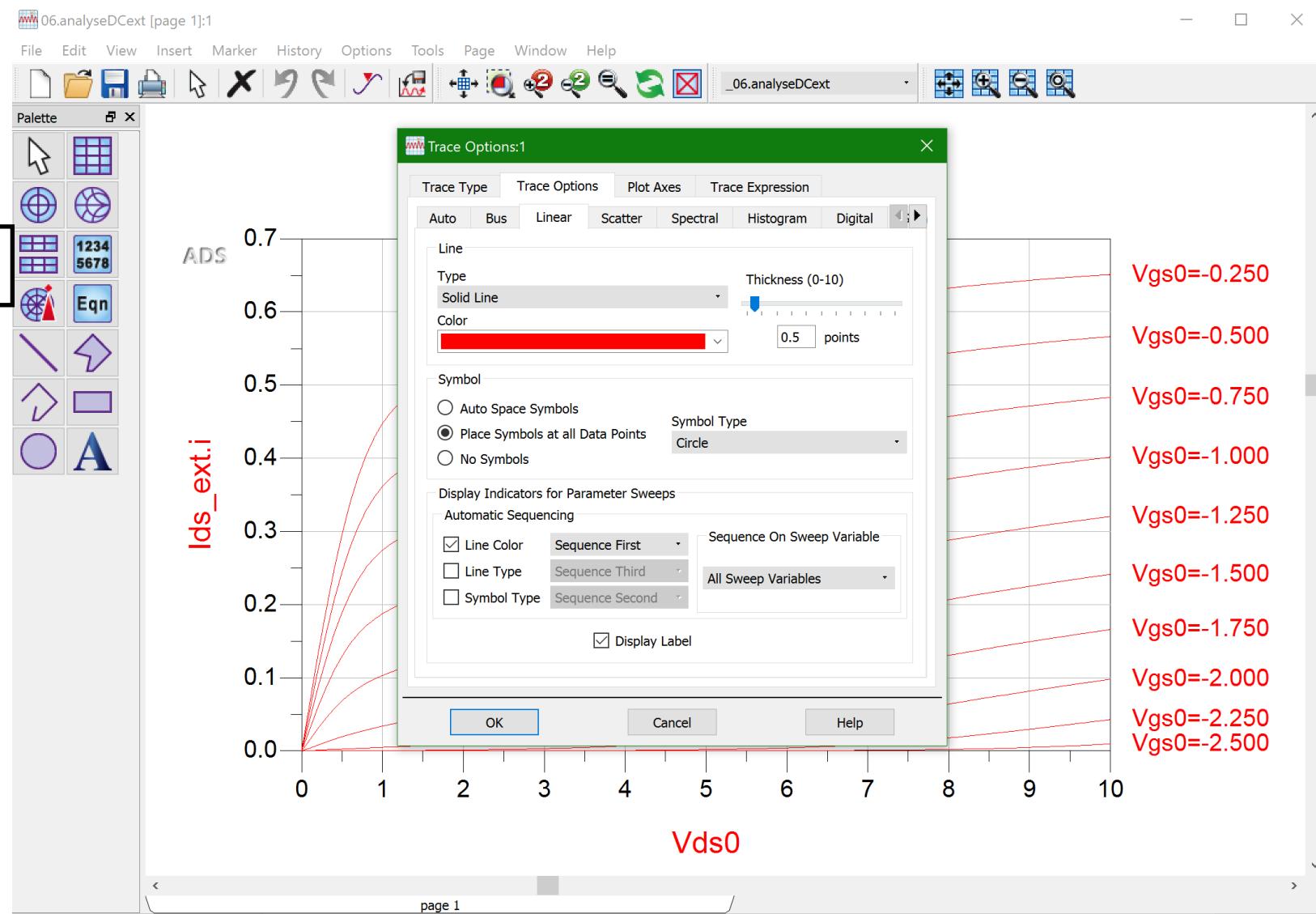

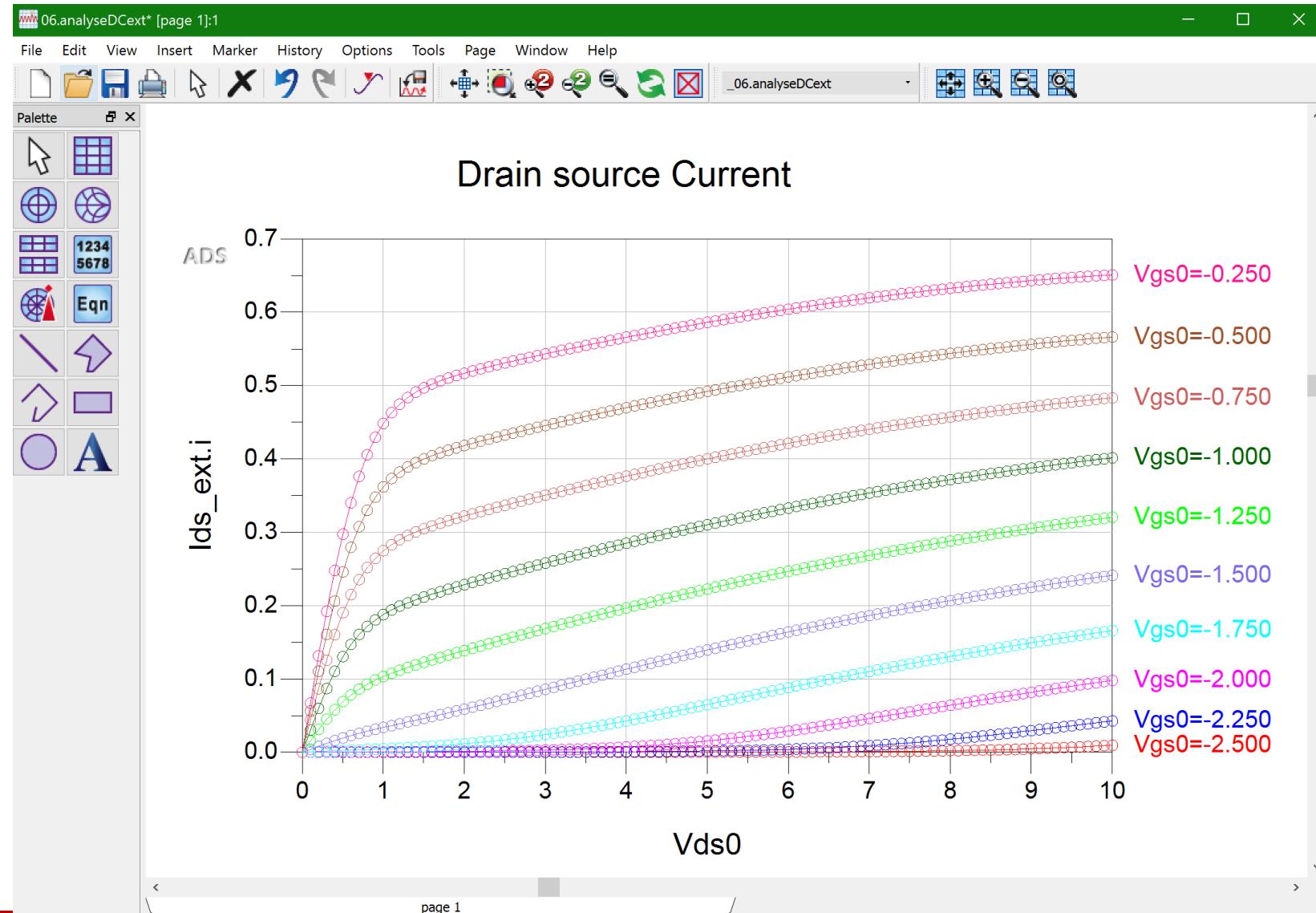

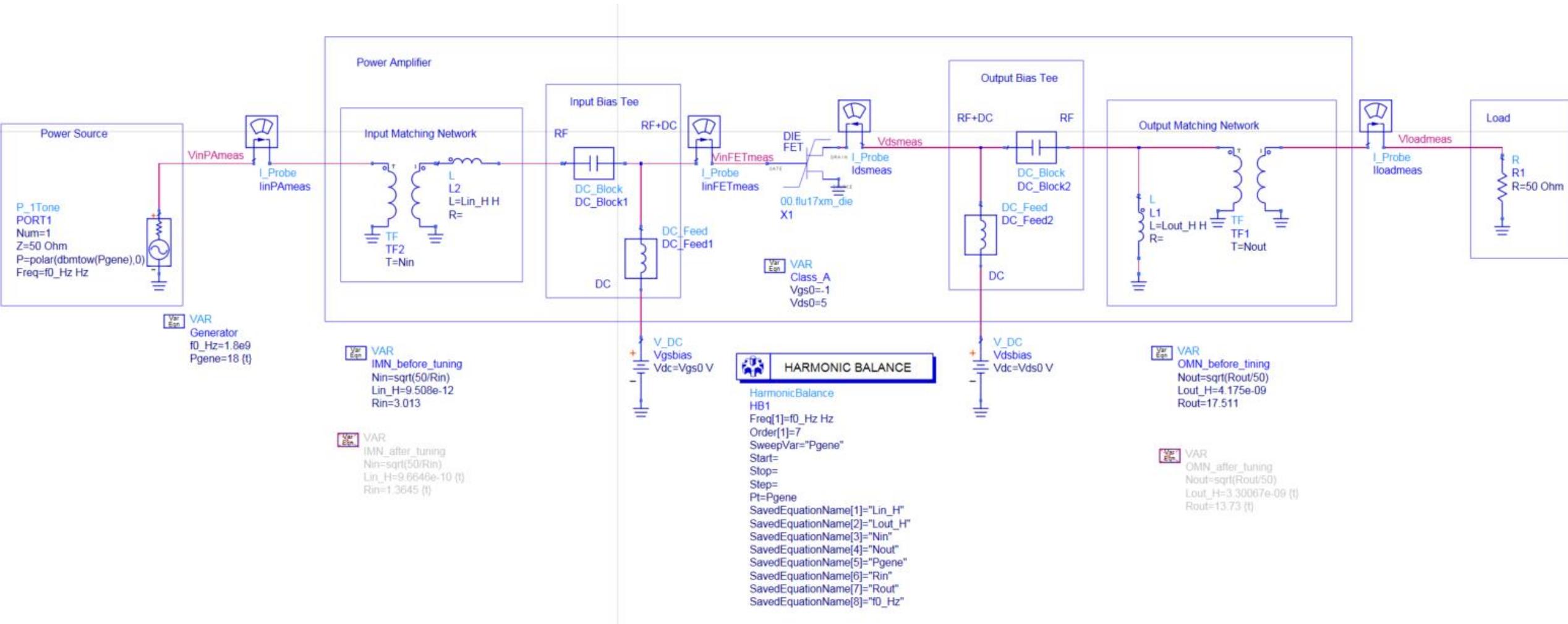




$$\begin{aligned} \text{Eqn } & \text{VinPA_f0=VinPAmeas[1]} & \text{Eqn } & \text{linPA_f0=linPAmeas.i[1]} \\ \text{Eqn } & \text{VoutPA_f0=Vloadmeas[1]} & \text{Eqn } & \text{loutPA_f0=lloadmeas.i[1]} \\ \\ \text{Eqn } & \text{VinPA_DC=mag(VinFETmeas[0])} & \text{Eqn } & \text{PinPA_f0_mW=0.5*1000*real(VinPA_f0*conj(linPA_f0))} \\ \text{Eqn } & \text{loutPA_DC=mag(linFETmeas.i[0])} & \text{Eqn } & \text{PinPA_f0_dBm=10*log10(PinPA_f0_mW)} \\ \\ \text{Eqn } & \text{VoutPA_DC=mag(Vdsmeas[0])} & \text{Eqn } & \text{PoutPA_f0_mW=0.5*1000*real(VoutPA_f0*conj(loutPA_f0))} \\ \text{Eqn } & \text{loutPA_DC=mag(ldsmeas.i[0])} & \text{Eqn } & \text{PoutPA_f0_dBm=10*log10(PoutPA_f0_mW)} \\ \\ \text{Eqn } & \text{ZinFET_f0=VinFETmeas[1]/linFETmeas.i[1]} & \text{Eqn } & \text{PDC_mW=1000*(VinPA_DC*linPA_DC+VoutPA_DC*loutPA_DC)} \\ \text{Eqn } & \text{ZinPA_f0=VinPAmeas[1]/linPAmeas.i[1]} & \text{Eqn } & \text{GPA_f0=PoutPA_f0_mW/PinPA_f0_mW} \\ \text{Eqn } & \text{GamainFET_f0=(ZinFET_f0-50)/(ZinFET_f0+50)} & \text{Eqn } & \text{GPA_f0_dB=10*log10(GPA_f0)} \\ \text{Eqn } & \text{GamainPA_f0=(ZinPA_f0-50)/(ZinPA_f0+50)} & \text{Eqn } & \text{PaddPA_f0_mW=PoutPA_f0_mW-PinPA_f0_mW} \\ \\ \text{Eqn } & \text{PaddPA_f0_dBm=10*log10(PaddPA_f0_mW)} & \text{Eqn } & \text{PaddPA_f0_dBm=10*log10(PaddPA_f0_mW)} \\ \text{Eqn } & \text{Drain_Efficiency=PoutPA_f0_mW/PDC_mW*100} & \text{Eqn } & \text{PAE=PaddPA_f0_mW/PDC_mW*100} \end{aligned}$$

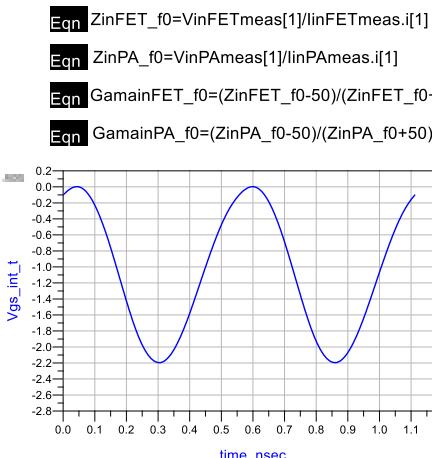


$$\begin{aligned} \text{Eqn } & \text{lds_static="06.analyseDCext".lds_int.i} \\ \text{Eqn } & \text{time_s=indep(Vds_int_t[0,:])} \\ \text{Eqn } & \text{Vds_int=Vdint-Vsintd} \\ \text{Eqn } & \text{Vds_int_t=ts(Vds_int)} \\ \text{Eqn } & \text{Vgs_int_t=ts(Vgint-Vsingt)} \\ \text{Eqn } & \text{lds_int_t=ts(lds_int.i)} \end{aligned}$$

| Pgene | PinPA_f0_mW | ...lPA_f0_mW | GPA_f0 | PDC_mW | ...in_Efficiency | PAE |
|--------|-------------|--------------|--------|----------|------------------|--------|
| 18.000 | 9.413 | 614.277 | 65.261 | 1565.602 | 39.236 | 38.635 |

| Pgene | ...PA_f0_dBm | ...lPA_f0_dBm | GPA_f0_dB | PDC_mW | ...in_Efficiency | PAE |
|--------|--------------|---------------|-----------|----------|------------------|--------|
| 18.000 | 9.737 | 27.884 | 18.147 | 1565.602 | 39.236 | 38.635 |

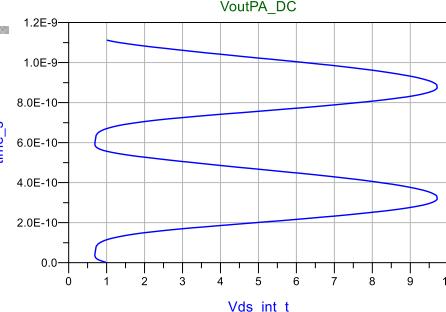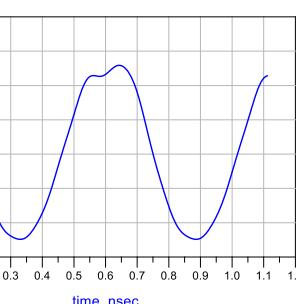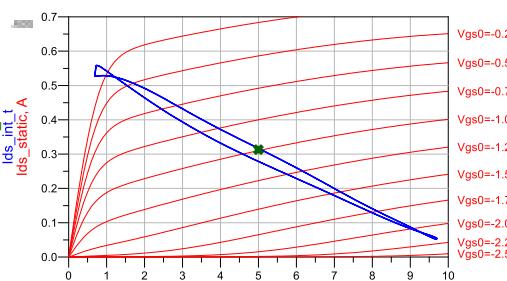



| | |
|----|--------------------------------------|
| m1 | Pgene=18.000 |
| | GmainFET_f0=0.941 / -156.472 |
| | impedance = $Z_0 * (0.031 - j0.208)$ |
| m2 | Pgene=18.000 |
| | GmainPA_f0=0.922 / -31.974 |
| | impedance = $Z_0 * (0.522 - j3.417)$ |

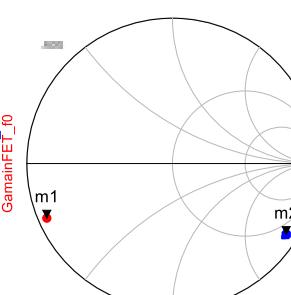

| freq | PinPA_spectrum_mW |
|-----------|-------------------|
| 0.0000 Hz | 0.000 |
| 1.800 GHz | 9.413 |
| 3.600 GHz | -0.316 |
| 5.400 GHz | -0.001 |
| 7.200 GHz | -0.001 |
| 9.000 GHz | -0.001 |
| 10.80 GHz | -8.805E-5 |
| 12.60 GHz | -1.122E-4 |



$$\text{Eqn } \text{PinPA_spectrum_mW} = 0.5 * 1000 * \text{real}(\text{VinPAmeas} * \text{conj}(\text{linPAmeas}.i))$$
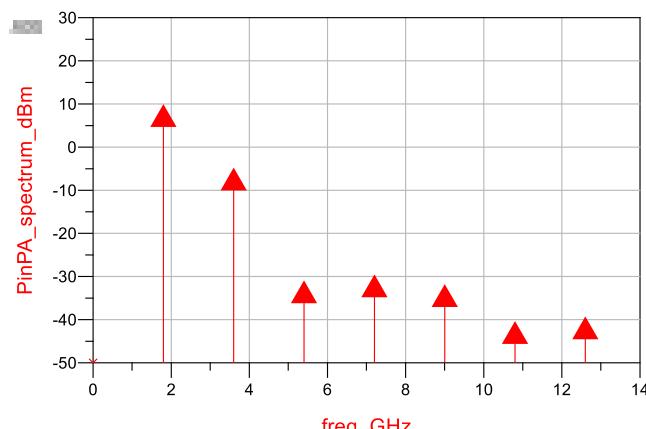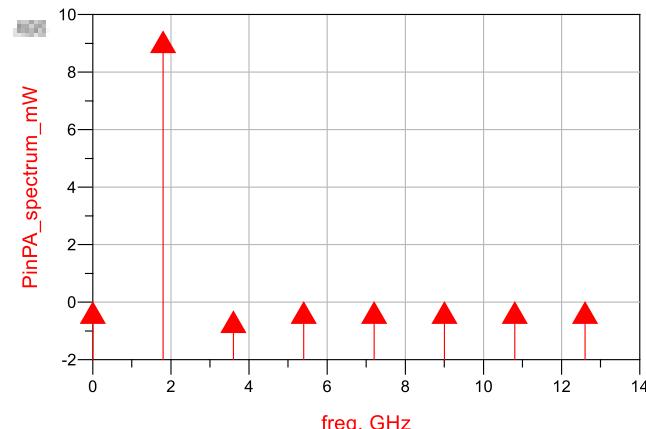
$$\text{Eqn } \text{PinPA_spectrum_dBm} = 10 * \log_{10}(\text{mag}(\text{PinPA_spectrum_mW}))$$



$$\text{Eqn } \text{PoutPA_spectrum_mW} = 0.5 * 1000 * \text{real}(\text{Vloadmeas} * \text{conj}(\text{lloadmeas}.i))$$
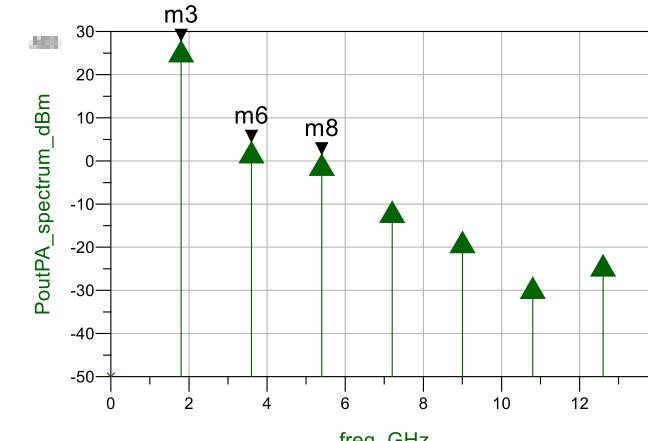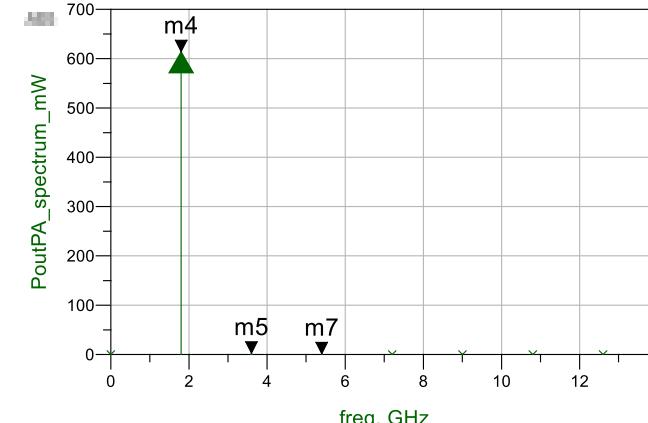
$$\text{Eqn } \text{PoutPA_spectrum_dBm} = 10 * \log_{10}(\text{PoutPA_spectrum_mW})$$



m4
freq=1.800GHz
PoutPA_spectrum_mW=614.277
Pgene=18.000


m5
freq=3.600GHz
PoutPA_spectrum_mW=2.789
Pgene=18.000

m7
freq=5.400GHz
PoutPA_spectrum_mW=1.437
Pgene=18.000

m3
freq=1.800GHz
PoutPA_spectrum_dBm=27.884
Pgene=18.000

m6
freq=3.600GHz
PoutPA_spectrum_dBm=4.454
Pgene=18.000

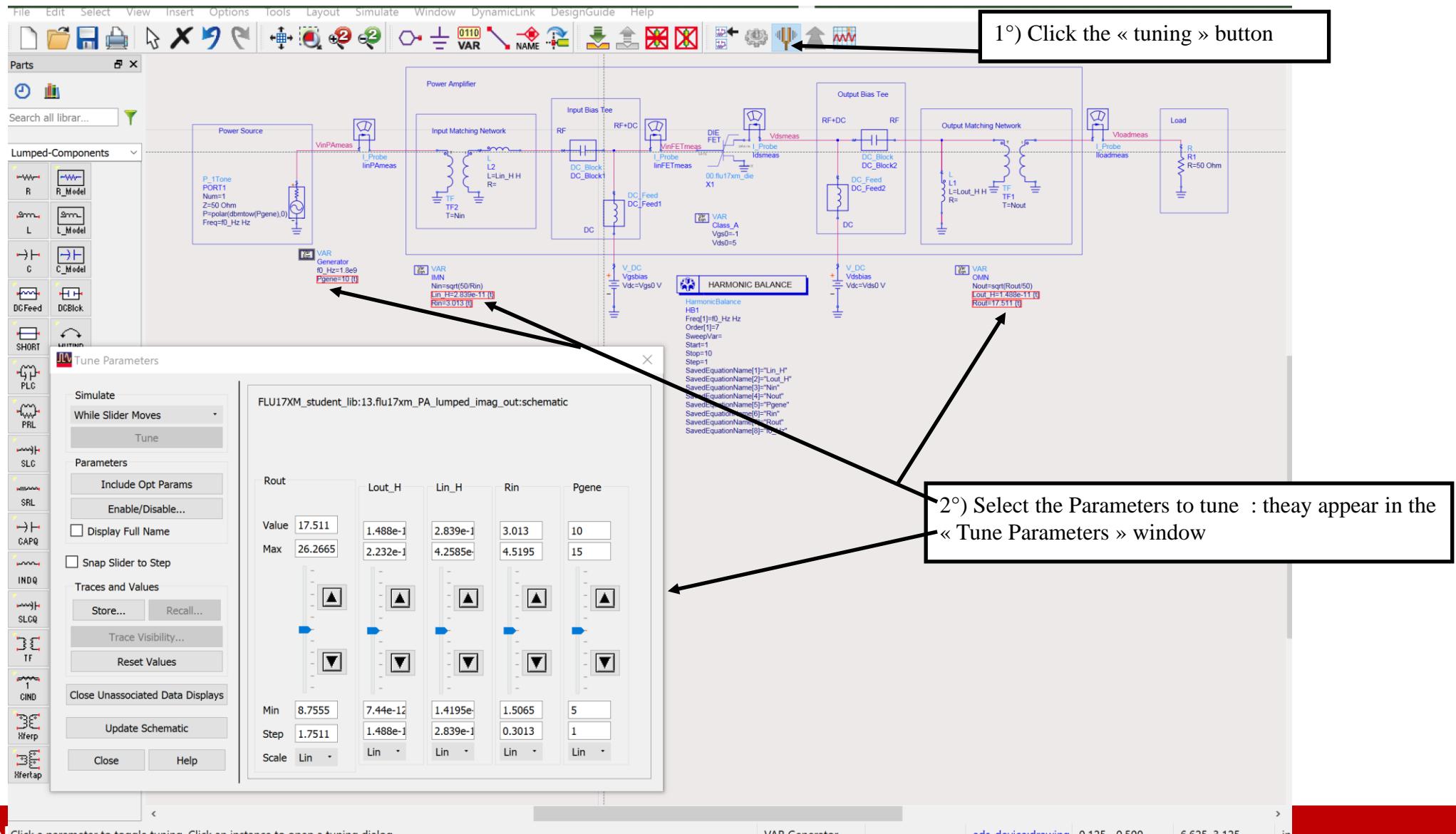m8
freq=5.400GHz
PoutPA_spectrum_dBm=1.574
Pgene=18.000



Basics of Active and Non-Active Tuning

Click a parameter to toggle tuning. Click an instance to open a tuning dialog.


VAR Generator

ads device:drawing 0.125--0.500

in

- 35 -

After the tuning of the 5 parameters

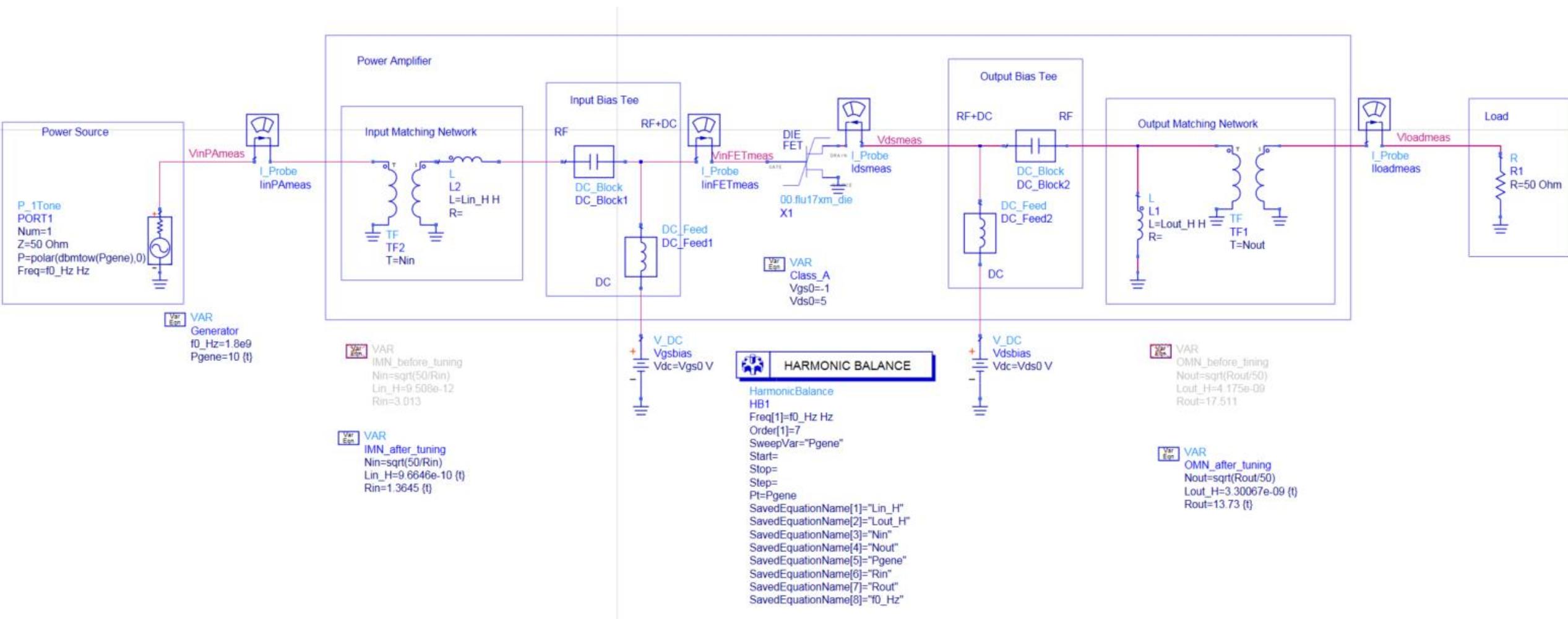

E(rasmus) Mundus on Innovative Microwave Electronics and Optics


Results after the tuning of the 5 parameters to maximise the output power of the PA.

Method to tune the parameters

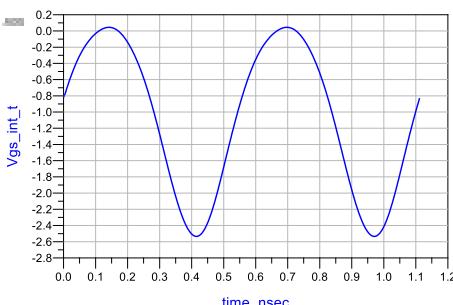- 1) Tune first Lout_H
- 2) Tune Secondly Rout
- 3) Modify Pgene if required
- 4) Tune again Lout_H
- 5) Tune again Rout
- 6) Tune then Lin_H to cancel Imag(Zin)
- 7) Tune Secondly Rin (To match Zin=50Ω)
- 8) Modify Pgene if required
- 9) Tune again Lout_H if required
- 10) Tune again Rout if required
- 11) Tune again Lin_H to cancel Imag(Zin)
- 12) Tune again Rin (To match Zin=50Ω)
- 13) Repeat again step 8 to 12 to maximise the Gain or the output power or the PAE

$$\begin{aligned}
 & \text{Eqn } \text{VinPA_f0} = \text{VinPAmeas}[1] \quad \text{Eqn } \text{linPA_f0} = \text{linPAmeas.i}[1] \quad \text{Eqn } \text{PinPA_f0_mW} = 0.5 * 1000 * \text{real}(\text{VinPA_f0} * \text{conj}(\text{linPA_f0})) \quad \text{Eqn } \text{GPA_f0} = \text{PoutPA_f0_mW} / \text{PinPA_f0_mW} \\
 & \text{Eqn } \text{VoutPA_f0} = \text{Vloadmeas}[1] \quad \text{Eqn } \text{loutPA_f0} = \text{lloadmeas.i}[1] \quad \text{Eqn } \text{PinPA_f0_dBm} = 10 * \log_{10}(\text{PinPA_f0_mW}) \quad \text{Eqn } \text{GPA_f0_dBm} = 10 * \log_{10}(\text{GPA_f0}) \\
 & \text{Eqn } \text{VinPA_DC} = \text{mag}(\text{VinFETmeas}[0]) \quad \text{Eqn } \text{linPA_DC} = \text{mag}(\text{linFETmeas.i}[0]) \quad \text{Eqn } \text{PoutPA_f0_mW} = 0.5 * 1000 * \text{real}(\text{VoutPA_f0} * \text{conj}(\text{loutPA_f0})) \quad \text{Eqn } \text{PaddPA_f0_mW} = \text{PoutPA_f0_mW} - \text{PinPA_f0_mW} \\
 & \text{Eqn } \text{VoutPA_DC} = \text{mag}(\text{Vdsmeas}[0]) \quad \text{Eqn } \text{loutPA_DC} = \text{mag}(\text{ldsmeas.i}[0]) \quad \text{Eqn } \text{PoutPA_f0_dBm} = 10 * \log_{10}(\text{PoutPA_f0_mW}) \quad \text{Eqn } \text{PaddPA_f0_dBm} = 10 * \log_{10}(\text{PaddPA_f0_mW}) \\
 & \text{Eqn } \text{PDC_mW} = 1000 * (\text{VinPA_DC} * \text{linPA_DC} + \text{VoutPA_DC} * \text{loutPA_DC}) \quad \text{Eqn } \text{Drain_Efficiency} = \text{PoutPA_f0_mW} / \text{PDC_mW} * 100 \quad \text{Eqn } \text{PAE} = \text{PaddPA_f0_mW} / \text{PDC_mW} * 100
 \end{aligned}$$





$$\begin{aligned}
 & \text{Eqn } \text{ZinFET_f0} = \text{VinFETmeas}[1] / \text{linFETmeas.i}[1] \\
 & \text{Eqn } \text{ZinPA_f0} = \text{VinPAmeas}[1] / \text{linPAmeas.i}[1] \\
 & \text{Eqn } \text{GamainFET_f0} = (\text{ZinFET_f0} - 50) / (\text{ZinFET_f0} + 50) \\
 & \text{Eqn } \text{GamainPA_f0} = (\text{ZinPA_f0} - 50) / (\text{ZinPA_f0} + 50)
 \end{aligned}$$



$$\begin{aligned}
 & \text{Eqn } \text{Ids_static} = \text{"_06.analyseDCext"}..ids_int.i \\
 & \text{Eqn } \text{time_s} = \text{indep}(\text{Vds_int}_t[0, :]) \\
 & \text{Eqn } \text{Vds_int} = \text{Vdint-Vsintd} \\
 & \text{Eqn } \text{Vds_int}_t = \text{ts}(\text{Vds_int}) \\
 & \text{Eqn } \text{Vgs_int}_t = \text{ts}(\text{Vgint-Vsintg}) \\
 & \text{Eqn } \text{Ids_int}_t = \text{ts}(\text{Ids_int}.i)
 \end{aligned}$$

| Pgene | PinPA_f0_mW | ...tPA_f0_mW | GPA_f0 | PDC_mW | ...in_Efficiency | PAE |
|--------|-------------|--------------|--------|----------|------------------|--------|
| 10.000 | 10.000 | 733.199 | 73.320 | 1675.090 | 43.771 | 43.174 |

| Pgene | ...PA_f0_dBm | ...tPA_f0_dBm | GPA_f0_dB | PDC_mW | ...in_Efficiency | PAE |
|--------|--------------|---------------|-----------|----------|------------------|--------|
| 10.000 | 10.000 | 28.652 | 18.652 | 1675.090 | 43.771 | 43.174 |

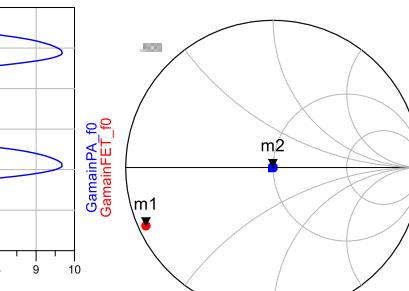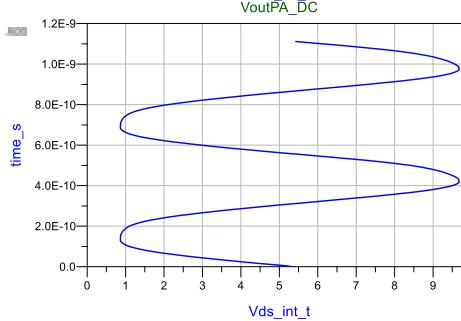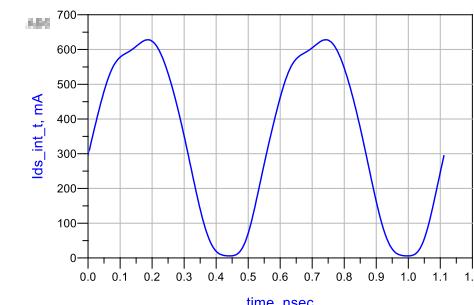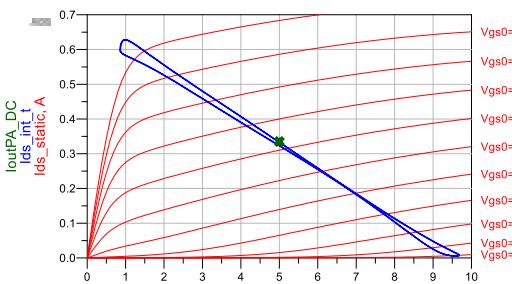

$$\begin{aligned}
 & \text{m1} \quad \text{Pgine} = 10.000 \quad \text{GammaInFET_f0} = 0.949 / -155.321 \quad \text{impedance} = Z_0 * (0.027 - j0.219) \\
 & \text{m2} \quad \text{Pgine} = 10.000 \quad \text{GammaMainPA_f0} = 0.002 / 177.310 \quad \text{impedance} = Z_0 * (0.996 + j1.780E-4)
 \end{aligned}$$



| Pgene | ZinFET_f0 | ...ainFET_f0 |
|--------|-----------------|------------------|
| 10.000 | 1.359 - j10.... | 0.949 / -155.... |

| Pgene | ZinPA_f0 | ...mainPA_f0 |
|--------|-----------------|-----------------|
| 10.000 | 49.810 + j0.... | 0.002 / 177.... |

| freq | PinPA_spectrum_mW |
|------------|-------------------|
| 0.0000 Hz | 0.000 |
| 1.800 GHz | 10.000 |
| 3.600 GHz | -0.048 |
| 5.400 GHz | -2.714E-4 |
| 7.200 GHz | -9.894E-7 |
| 9.000 GHz | -1.955E-6 |
| 10.800 GHz | -1.466E-7 |
| 12.60 GHz | -8.569E-12 |



$$\text{Eqn} \quad \text{PinPA_spectrum_mW} = 0.5 * 1000 * \text{real}(\text{VinPAmeas} * \text{conj}(\text{linPAmeas}.i))$$
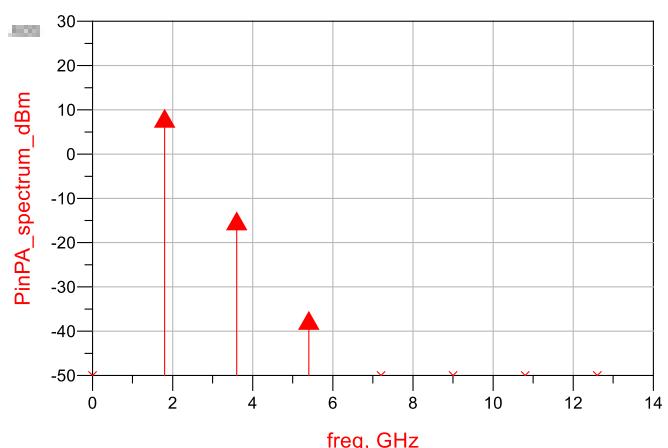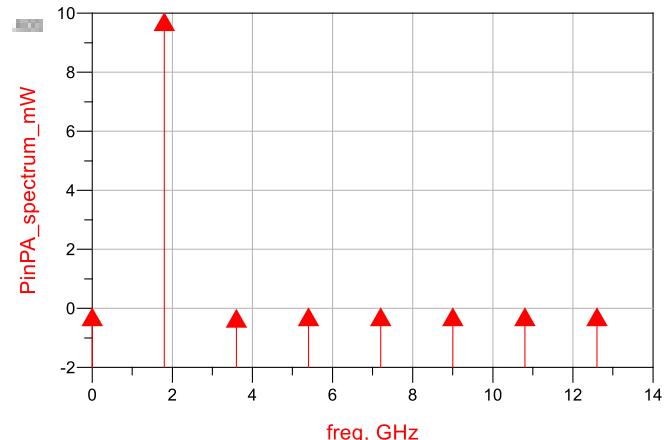
$$\text{Eqn} \quad \text{PinPA_spectrum_dBm} = 10 * \log_{10}(\text{mag}(\text{PinPA_spectrum_mW}))$$




$$\text{Eqn} \quad \text{PoutPA_spectrum_mW} = 0.5 * 1000 * \text{real}(\text{Vloadmeas} * \text{conj}(\text{lloadmeas}.i))$$
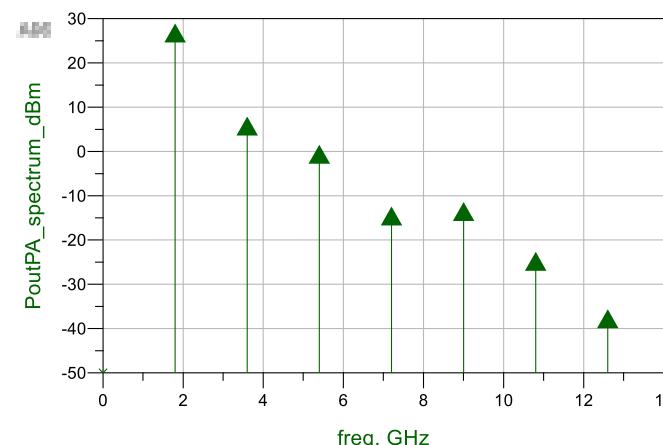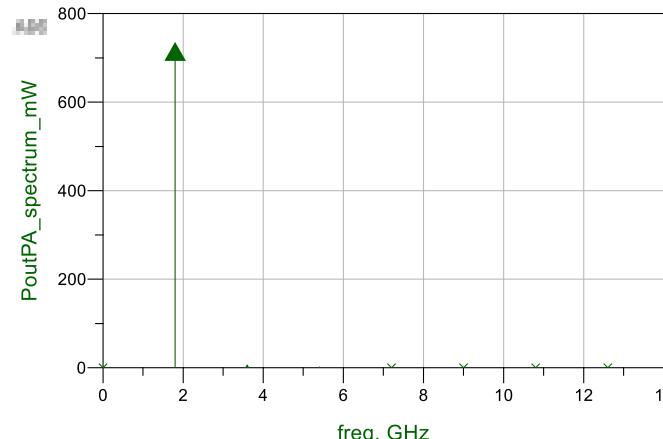
$$\text{Eqn} \quad \text{PoutPA_spectrum_dBm} = 10 * \log_{10}(\text{PoutPA_spectrum_mW})$$




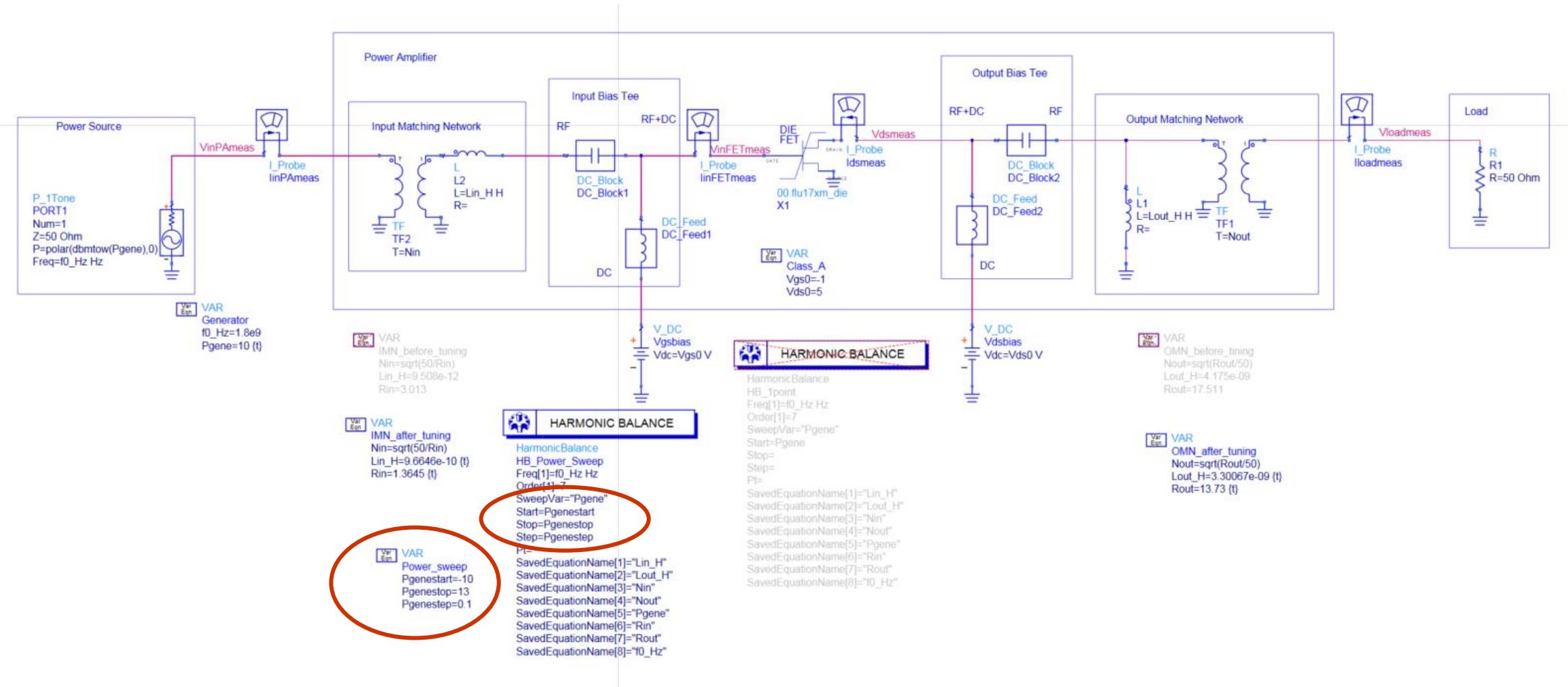With a power sweep of the generator Power





| | | | |
|---------------------------------------|--|--|---|
| Eqn VinPA_f0=VinPAmeas[1] | Eqn linPA_f0=linPAmeas.i[1] | Eqn PinPA_f0_mW=0.5*1000*real(VinPA_f0*conj(linPA_f0)) | Eqn GPA_f0=PoutPA_f0_mW/PinPA_f0_mW |
| Eqn VoutPA_f0=Vloadmeas[1] | Eqn loutPA_f0=lloadmeas.i[1] | Eqn PinPA_f0_dBm=10*log10(PinPA_f0_mW) | Eqn GPA_f0_dB=10*log10(GPA_f0) |
| Eqn VinPA_DC=mag(VinFETmeas[0] | Eqn linPA_DC=mag(linFETmeas.i[0]) | Eqn PoutPA_f0_mW=0.5*1000*real(VoutPA_f0*conj(loutPA_f0)) | Eqn PaddPA_f0_mW=PoutPA_f0_mW-PinPA_f0_mW |
| Eqn VoutPA_DC=mag(Vdsmeas[0]) | Eqn loutPA_DC=mag(ldsmeas.i[0]) | Eqn PoutPA_f0_dBm=10*log10(PoutPA_f0_mW) | Eqn PaddPA_f0_dBm=10*log10(PaddPA_f0_mW) |
| | | Eqn PDC_mW=1000*(VinPA_DC*linPA_DC+VoutPA_DC*loutPA_DC) | Eqn Drain_Efficiency=PoutPA_f0_mW/PDC_mW*100 |
| | | | Eqn PAE=PaddPA_f0_mW/PDC_mW*100 |

| |
|---|
| Eqn ZinFET_f0=VinFETmeas[1]/linFETmeas.i[1] |
| Eqn ZinPA_f0=VinPAmeas[1]/linPAmeas.i[1] |
| Eqn GamainFET_f0=(ZinFET_f0-50)/(ZinFET_f0+50) |
| Eqn GamainPA_f0=(ZinPA_f0-50)/(ZinPA_f0+50) |


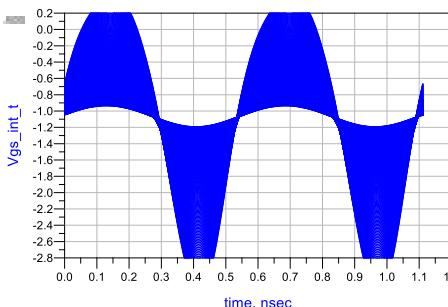


| Pgene | PinPA_f0_mW | ...lPA_f0_mW | GPA_f0 | PDC_mW | ...in Efficiency | PAE |
|---------|-------------|--------------|--------|----------|------------------|-------|
| -10.000 | 0.099 | 9.234 | 92.811 | 1551.479 | 0.595 | 0.589 |

| Pgene | ...PA_f0_dBm | ...lPA_f0_dBm | GPA_f0_dB | PDC_mW | ...in Efficiency | PAE |
|---------|--------------|---------------|-----------|----------|------------------|-------|
| -10.000 | -10.022 | 9.654 | 19.676 | 1551.479 | 0.595 | 0.589 |

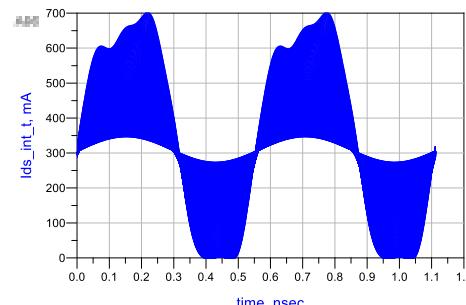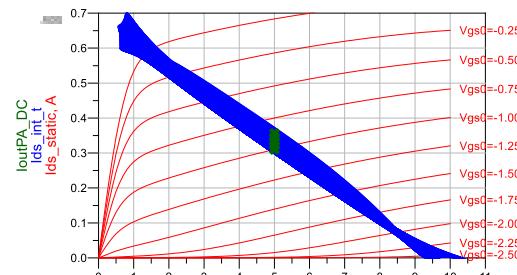








| |
|---|
| Eqn Ids_static=_06.analyseDCext..Ids_int.i |
| Eqn time_s=indep(Vds_int_t[0,:,:]) |
| Eqn Vds_int=Vdint-Vsintd |
| Eqn Vds_int_t=ts(Vds_int) |
| Eqn Vgs_int_t=ts(Vgint-Vsintg) |
| Eqn Ids_int_t=ts(Ids_int.i) |

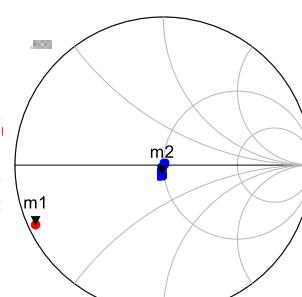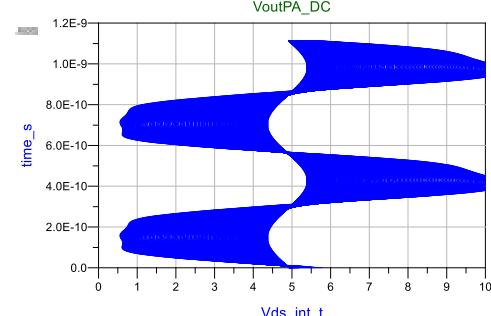

| Pgene | ZinFET_f0 | ...ainFET_f0 |
|---------|----------------|------------------|
| -10.000 | 1.332 -j11.... | 0.951 / -154.... |
| -9.900 | 1.332 -j11.... | 0.951 / -154.... |

| Pgene | ZinPA_f0 | ...mainPA_f0 |
|---------|----------------|-----------------|
| -10.000 | 48.798 -j6.... | 0.071 / -95.... |
| -9.900 | 48.798 -j6.... | 0.071 / -95.... |



| | |
|---|--|
| m1 Pgene=(-10.000 to 13.000) Gamma10=1.879E-14 Gamma20=0.950 / -154.969 impedance = Z0 * (0.027 - j0.222) | m2 Pgene=1.879E-14 Gamma10=1.879E-14 Gamma20=0.061 / -97.558 impedance = Z0 * (0.977 - j0.118) |
|---|--|

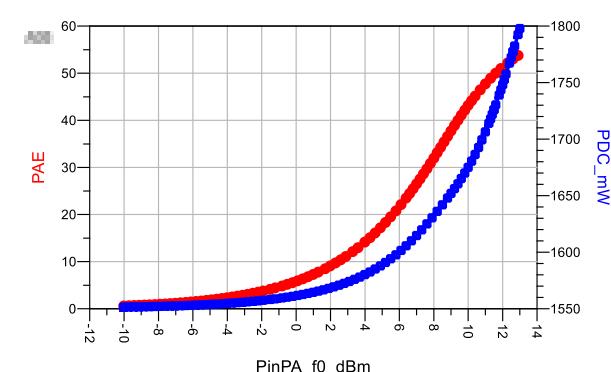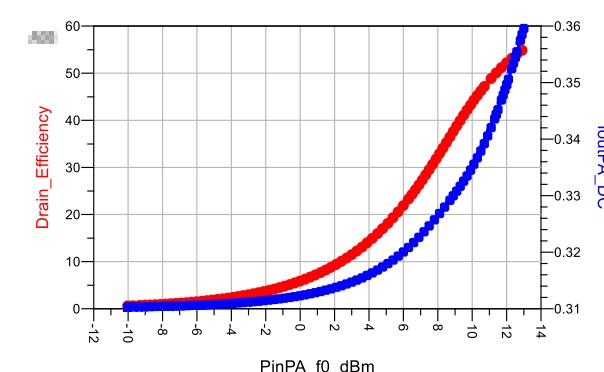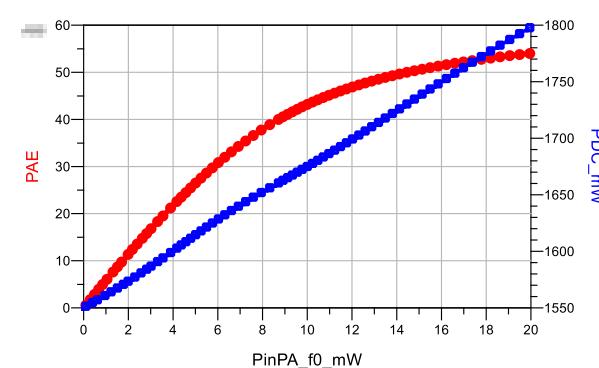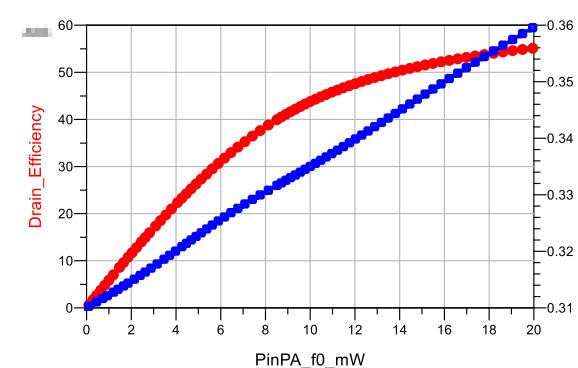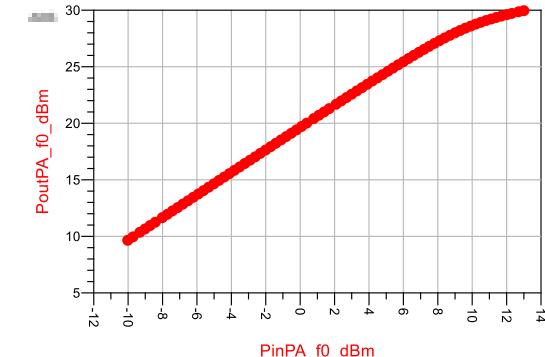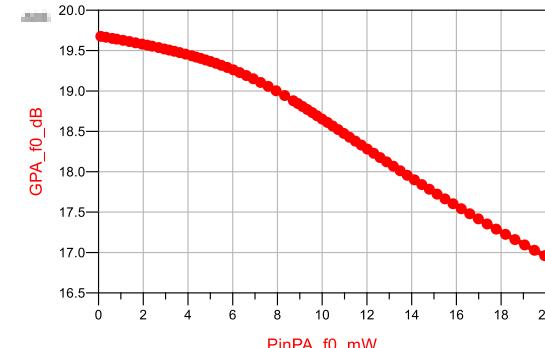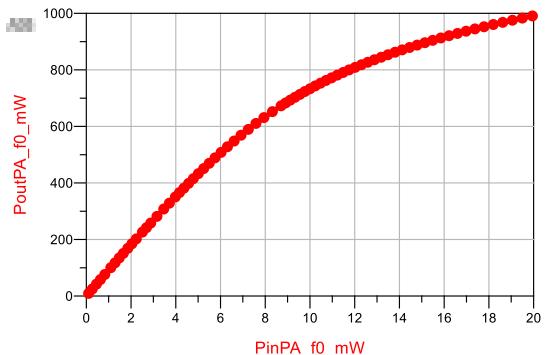

| freq | PinPA_spectrum_mW |
|----------------------------|-------------------|
| Pgene=-10.000 0.0000 Hz | 0.000 |
| 1.800 GHz | 0.099 |
| 3.600 GHz | -4.957E-6 |
| 5.400 GHz | -8.445E-11 |
| 7.200 GHz | -2.161E-14 |
| 9.000 GHz | -3.669E-17 |
| 10.80 GHz | -3.145E-20 |
| 12.60 GHz | -1.887E-23 |
| Pgene=-9.900 0.0000 Hz | 0.000 |
| 1.800 GHz | 0.102 |
| 3.600 GHz | -5.190E-6 |
| 5.400 GHz | -9.050E-11 |
| 7.200 GHz | -2.370E-14 |
| 9.000 GHz | -4.117E-17 |
| 10.80 GHz | -3.611E-20 |
| 12.60 GHz | -2.220E-23 |
| Pgene=-9.800 0.0000 Hz | 0.000 |
| 1.800 GHz | 0.104 |
| 3.600 GHz | -5.435E-6 |
| 5.400 GHz | -9.698E-11 |
| 7.200 GHz | -2.600E-14 |
| 9.000 GHz | -4.620E-17 |
| 10.80 GHz | -4.145E-20 |
| 12.60 GHz | -2.610E-23 |

$$\text{Eqn} \quad \text{PinPA_spectrum_mW} = 0.5 * 1000 * \text{real}(\text{VinPAmeas} * \text{conj}(\text{linPAmeas}.i))$$
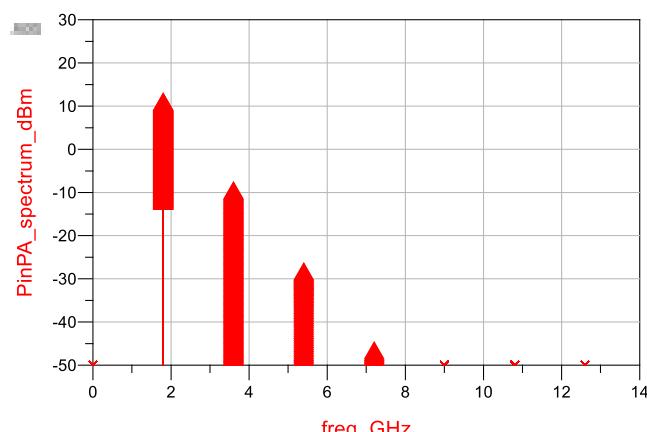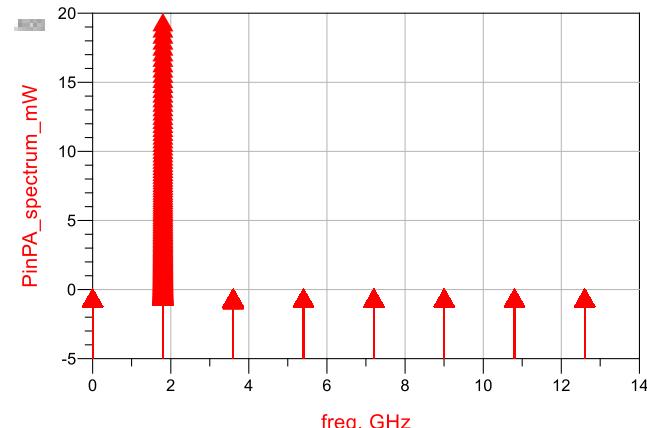
$$\text{Eqn} \quad \text{PinPA_spectrum_dBm} = 10 * \log10(\text{mag}(\text{PinPA_spectrum_mW}))$$



$$\text{Eqn} \quad \text{PoutPA_spectrum_mW} = 0.5 * 1000 * \text{real}(\text{Vloadmeas} * \text{conj}(\text{lloadmeas}.i))$$

$$\text{Eqn} \quad \text{PoutPA_spectrum_dBm} = 10 * \log10(\text{PoutPA_spectrum_mW})$$

