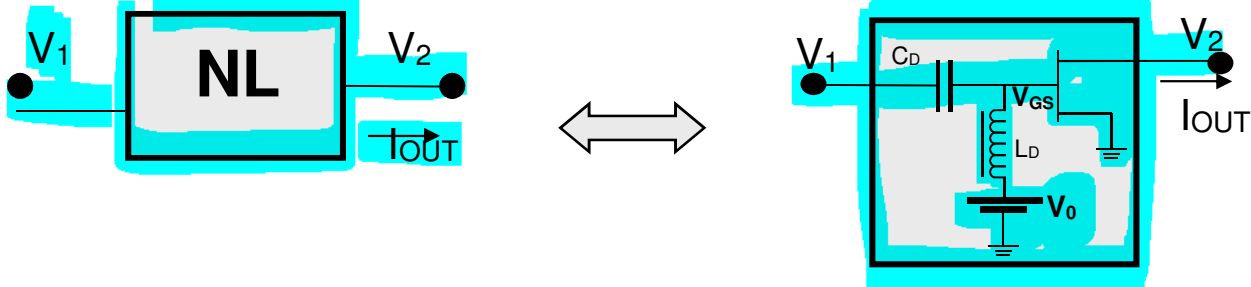


Tutorial (SEM cold-FET Mixer)

The following cold-FET mixer (biased @ $V_{DS0}=0$ V) is used to design a SEM up-converter where the LO signal V_1 is applied to the gate, which is biased @ ($V_{GS0}=V_0$) while the IF input signal is applied to the drain using a low-pass filter and the output signal is extracted at the drain port using a high-pass filter.



The nonlinear operation of the cold-FET (NL) is expressed by the 2 following equations that give the output current I_{OUT} as a function of input and output control voltages V_1 and V_2 :

$$V_{GS} = V_0 + V_1 \quad (\text{eq1})$$

where V_0 is a constant (gate bias voltage)

$$I_{OUT} = p V_2 - q V_2 V_{GS}^2 + r V_1 \quad (\text{eq2})$$

where p, q and r are constants



The SEM cold-FET mixer is shown below and the main frequencies are :

$$f_{LO} = 9 \text{ GHz}, f_{IF} = 0.5 \text{ GHz et } f_{RF} = f_{LO} + f_{IF} = 9.5 \text{ GHz } (\omega_{RF} = \omega_{LO} + \omega_{IF}).$$


The two control voltages V_1 and V_2 of the FET mixer are :


$$\text{LO voltage at gate port : } V_1 = V_{LO} \cos(\omega_{LO} t) \quad (\text{eq3})$$
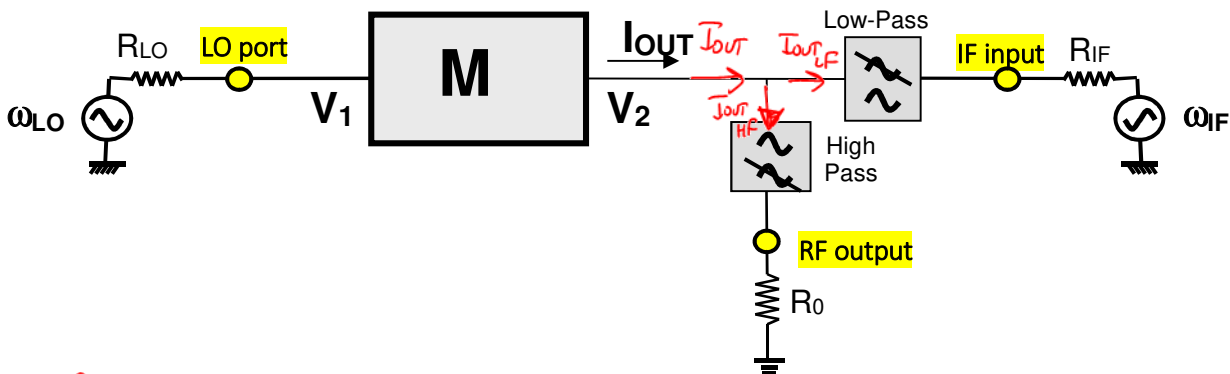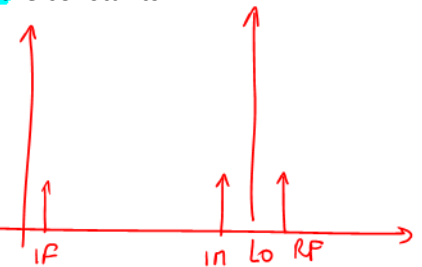
$$\text{IF voltage at drain port : } V_2 = V_{IF} \cos(\omega_{IF} t) \quad (\text{eq4})$$



- Using equations 1 to 4, express the output current I_{OUT} as a function of signal magnitudes (V_{LO} , V_{IF}), nonlinearity constants (p , q , r), gate bias V_0 and the mixing frequencies. The following notations can be used for mixing frequencies: $\omega_{IM} = (\omega_{LO} - \omega_{IF})$; $\omega_1 = (2\omega_{LO} - \omega_{IF})$; $\omega_2 = (2\omega_{LO} + \omega_{IF})$
- The high-pass filter is designed to reject frequencies lower than 5GHz while the low-pass frequency is designed to cut frequencies greater than 5GHz. Therefore, what are the mixing frequencies at the RF output port?
- Determine the expression of the voltage conversion gain G_{CV} .
- If the LO port is assumed to be matched to R_{LO} ,
 - express the LO power applied at the LO port *
 - express the LO power at the RF output port *
 - express in dB the LO-to-RF isolation *
 - what is the LO-to-IF isolation ? *
 - express the equivalent impedance Z_{IN} seen by the IF generator @ ω_{IF} at the IF input port

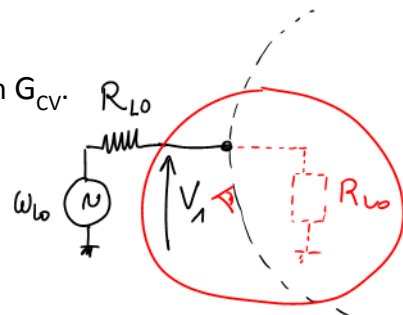

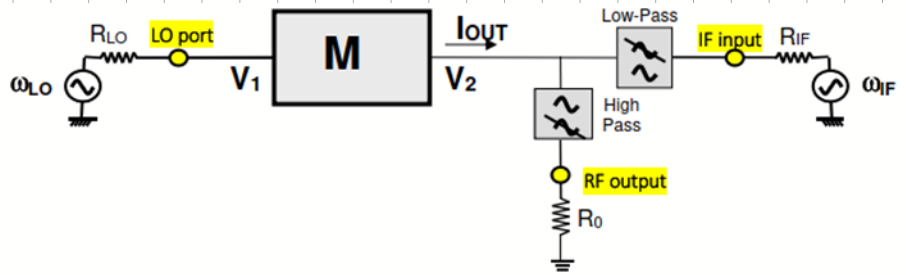

- 1) Using equations 1 to 4, express the output current I_{OUT} as a function of signal magnitudes (V_{LO} , V_{IF}), nonlinearity constants (p , q , r), gate bias V_0 and the mixing frequencies. The following notations can be used for mixing frequencies: $\omega_{IM} = (\omega_{LO} - \omega_{IF})$; $\omega_1 = (2\omega_{LO} - \omega_{IF})$; $\omega_2 = (2\omega_{LO} + \omega_{IF})$

$$V_1 = V_{LO} \cos(\omega_{LO} t) \quad (eq3)$$

$$V_2 = V_{IF} \cos(\omega_{IF} t) \quad (eq4)$$

$$\cos^2(x) = \frac{1}{2} + \frac{1}{2} \cos(2x)$$

$$V_{GS} = V_0 + V_1 \quad (eq1)$$

$$I_{OUT} = p V_2 - q V_2 V_{GS}^2 + r V_1 \quad (eq2)$$

$$V_2 \times V_{GS}^2 = V_2 (V_0 + V_1)^2 = V_2 (V_0^2 + V_1^2 + 2V_0 V_1)$$

$$= V_{IF} \cos(\omega_{IF} t) \left[\underbrace{V_0^2}_{\text{X}} + \underbrace{\frac{1}{2} V_{LO}^2}_{\text{X}} + \underbrace{\frac{1}{2} V_{LO}^2 \cos(2\omega_{LO} t)}_{\text{X}} + 2V_0 V_{LO} \cos(\omega_{LO} t) \right]$$



$$= \left(V_0^2 + \frac{V_{LO}^2}{2} \right) V_{IF} \cos(\omega_{IF} t) + \underbrace{V_0 V_{LO} V_{IF} [\cos(\omega_{RF} t) + \cos(\omega_{IM} t)]}_{\text{X}} + \underbrace{\frac{1}{4} V_{LO}^2 V_{IF} [\cos(\omega_1 t) + \cos(\omega_2 t)]}_{\text{X}}$$

$$I_{OUT} = \underbrace{\left[p - q \left(V_0^2 + \frac{V_{LO}^2}{2} \right) \right] V_{IF} \cos(\omega_{IF} t)}_{I_{OUT, LF}} - \underbrace{q V_0 V_{LO} V_{IF} [\cos(\omega_{RF} t) + \cos(\omega_{IM} t)] - \frac{q}{4} V_{LO}^2 V_{IF} [\cos(\omega_1 t) + \cos(\omega_2 t)] + r V_{LO} \cos(\omega_{LO} t)}_{I_{OUT, HF}}$$

$$I_{out} = \left[p - q \left(V_o^2 + \frac{V_{lo}^2}{2} \right) \right] V_{IF} \cos(\omega_{IF} t) - q V_o V_{lo} V_{IF} \left[\cos(\omega_{RF} t) + \cos(\omega_{in} t) \right] - \frac{q}{4} V_{lo}^2 V_{IF} \left[\cos(\omega_1 t) + \cos(\omega_2 t) \right] + r V_{lo} \cos(\omega_{lo} t)$$

$I_{out}(t) \rightarrow$ phasors

$$P = \frac{1}{2} \operatorname{Re} (V I^*) = \frac{1}{2} \frac{|V|^2}{R} = \frac{1}{2} R |I|^2$$

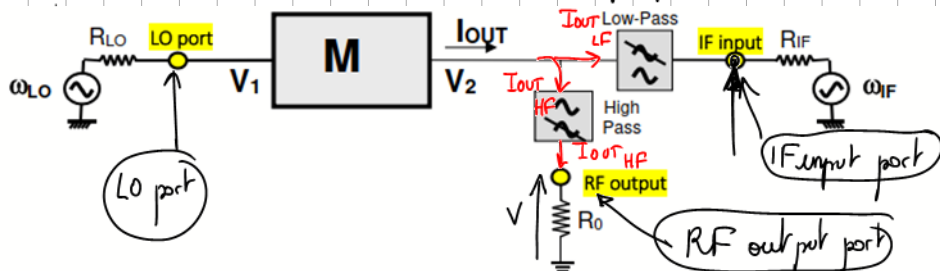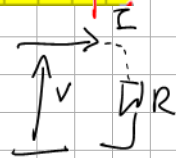


- 1) Using equations 1 to 4, express the output current I_{out} as a function of signal magnitudes (V_{LO} , V_{IF}), nonlinearity constants (p , q , r), gate bias V_o and the mixing frequencies. The following notations can be used for mixing frequencies: $\omega_m = (\omega_{LO} - \omega_{IF})$; $\omega_1 = (2\omega_{LO} - \omega_{IF})$; $\omega_2 = (2\omega_{LO} + \omega_{IF})$

$$2) G_{cv} = \frac{V_{out}(\omega_{out})}{V_{in}(\omega_{in})} = \frac{V_{RF \text{ port}}(\omega_{RF})}{V_{IF \text{ port}}(\omega_{IF})} = \frac{R_0 I_{out \text{ RF}}(\omega_{RF})}{V_{IF}} = \frac{R_0 (-q V_o V_{lo} V_{IF})}{V_{IF}}$$

$$G_{cv} = -q R_0 V_o V_{lo}$$

2) Output frequencies @ RF port are: (f_{LO}, f_m, f_1, f_2) spurs and f_{RF}


$$4) a) P_{Lo \text{ port}}(\omega_{lo}) = \frac{1}{2} \frac{|V_{lo}|^2}{R_{lo}}$$

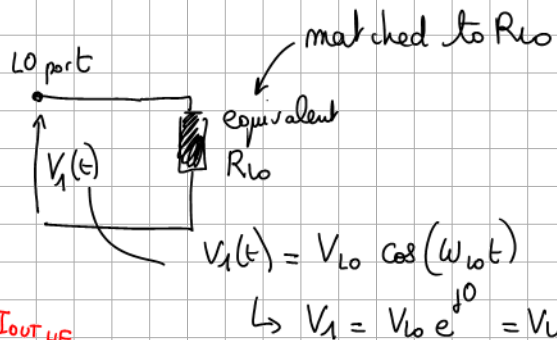

$$b) P_{RF \text{ port}}(\omega_{lo}) = \frac{1}{2} R_0 \left| I_{out}(\omega_{lo}) \right|^2 = \frac{1}{2} R_0 \pi^2 V_{lo}^2$$

$$c) ISO_{LO \rightarrow RF} (dB) = 10 \log \left(\frac{P_{Lo \text{ port}}(\omega_{lo})}{P_{RF \text{ port}}(\omega_{lo})} \right) = 10 \log \left(\frac{\frac{1}{2} \frac{V_{lo}^2}{R_{lo}}}{\frac{1}{2} R_0 \pi^2 V_{lo}^2} \right) = 10 \log \left(\frac{1}{R_0 R_{lo} \pi^2} \right)$$
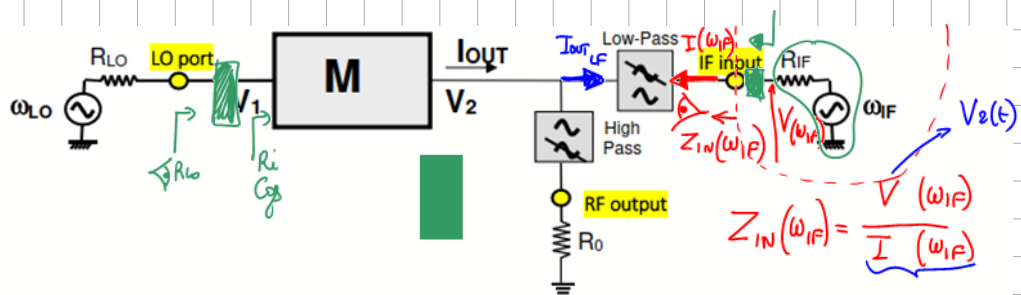
$$d) ISO_{lo \rightarrow IF} (dB) = 10 \log \left(\frac{P_{Lo \text{ port}}(\omega_{lo})}{P_{IF \text{ port}}(\omega_{lo})} \right) = \infty \text{ because of the ideal low-pass filter}$$



- 1) Using equations 1 to 4, express the output current I_{OUT} as a function of signal magnitudes (V_{LO} , V_{IF}), nonlinearity constants (p , q , r), gate bias V_0 and the mixing frequencies. The following notations can be used for mixing frequencies: $\omega_M = (\omega_{LO} - \omega_{IF})$; $\omega_1 = (2\omega_{LO} - \omega_{IF})$; $\omega_2 = (2\omega_{LO} + \omega_{IF})$

$$Z_{IN}(\omega_{IF}) = \frac{V_{IF}}{\left(\frac{1}{q} I_{OUT}(\omega_{IF}) \right)} = \frac{V_{IF}}{-\left(p - q \left(V_0^2 + \frac{V_{LO}^2}{2} \right) \right) V_{IF}} =$$

$$v(t) = V_1 \cos(\omega_1 t + \theta_1) \rightarrow \underline{\underline{V}} = V_1 e^{j\theta_1} = V_1 \cos(\theta_1) + j V_1 \sin(\theta_1)$$

$$\boxed{Z_{IN}(\omega_{IF}) = \frac{1}{q \left(V_0^2 + \frac{V_{LO}^2}{2} \right) - p} = R_{IF}}$$

To match the IF generator, $Z_{IN}(\omega_{IF}) = R_{IF}$