

MICROWAVE ENGINEERING

Lecture 18:
Impedance
Matching and
Tuning Problems

Problem 1 : Design two lossless L-section (Lumped Elements) matching circuits to match each of the following loads to a 100Ω generator at 3 GHz:


a) $Z_L = 150 - j200 \Omega$

b) $Z_L = 20 - j90 \Omega$

For load (a) we start by normalizing the load impedance to the line impedance.

$$Z_{\text{N}} = \frac{Z_L}{Z_0} = \frac{150 - j200}{100} = 1.5 - j2$$

If $Z_L > Z_0$

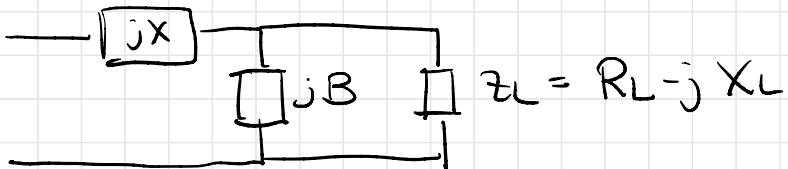

$$Z_L = R_L - j X_L$$

The values of our components:

$$B = \frac{X_L \pm \sqrt{\frac{R_L}{Z_0} \sqrt{R_L^2 + X_L^2} - Z_0 R_L}}{R_L^2 + X_L^2} =$$

$$= \frac{-200 \pm \sqrt{1.5 \sqrt{150^2 + 200^2} - 100 \cdot 150}}{150^2 + 200^2} =$$


$$= \frac{-200 \pm 217.94 \cdot 122}{62500} = \begin{cases} 1.06 \cdot 10^{-3} \\ -7.5 \cdot 10^{-3} \end{cases}$$

$$X = \frac{1}{B} + \frac{X_L Z_0}{R_L} - \frac{Z_0}{B R_L} = \begin{cases} \frac{1}{1.06 \cdot 10^{-3}} + \frac{-200 \cdot 100}{150} - \frac{100}{1.06 \cdot 10^{-3} \cdot 150} = 181.13 \\ \dots = -178.07 \end{cases}$$

$$\left. \begin{array}{l} \text{Sol 1: } B = 1.06 \cdot 10^{-3} \text{ and } X = 181.13 \\ \text{Sol 2: } B = -7.5 \cdot 10^{-3} \text{ and } X = -178.07 \end{array} \right|$$

for load
(a)

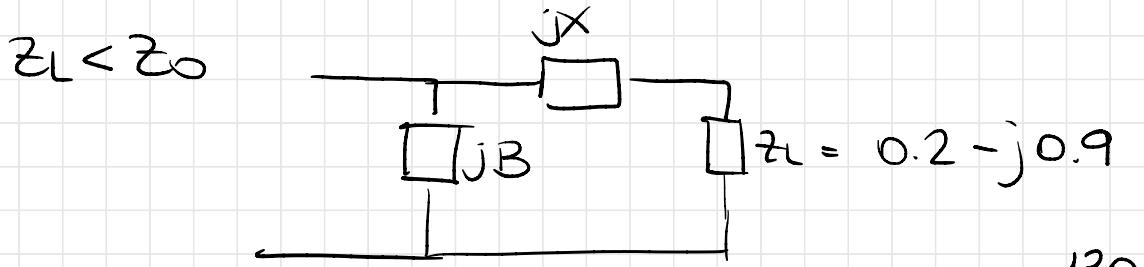
$$\text{For load (b): } Z_L = 20 - j90 \rightarrow Z_0 = \frac{Z_L}{Z_0} = 0.2 - j0.9$$



$$X = \pm \sqrt{R_L (Z_0 - R_L)} - X_L = \begin{cases} 130 \\ 50 \end{cases}$$

$$B = \frac{\pm \sqrt{(Z_0 - R_L)/R_L}}{Z_0} = \begin{cases} 0.02 \\ -0.02 \end{cases}$$

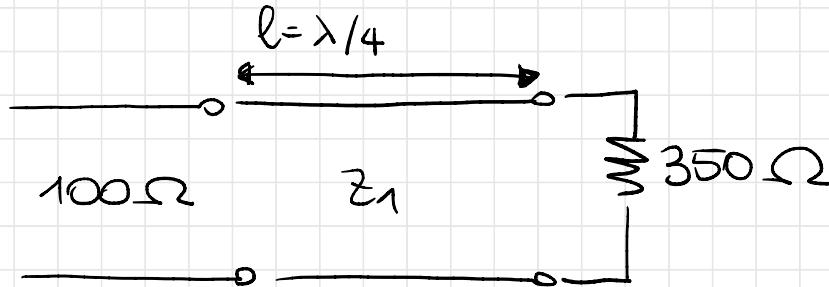Problem 2 : Design a single section quarter-wave matching transformer to match a 350Ω load to a 100Ω line. What is the fractional bandwidth (in percent) of this transformer if $\text{SWR} \leq 2$?



$$Z_1 = \sqrt{100 \cdot 350} = 187,1 \Omega$$

From the value of the SWR:

$$\underline{\Gamma_m} = \frac{\text{SWR} - 1}{\text{SWR} + 1} = \frac{1}{3}$$


The fractional bandwidth is:

$$\frac{\Delta f}{f_0} = 2 - \frac{4}{\pi} \cos^{-1} \left[\frac{\Gamma_m}{\sqrt{1-\Gamma_m^2}} \frac{2\sqrt{Z_L Z_0}}{|Z_L - Z_0|} \right] =$$

$$= 2 - \frac{4}{\pi} \cos^{-1} \left[\frac{\frac{1}{3}}{\sqrt{1-\frac{1}{9}}} \frac{2 \cdot 187.1}{1350 - 100} \right] = 0.071$$

$$\rightarrow \frac{\Delta f}{f_0} \text{ percentage} = 71\%$$

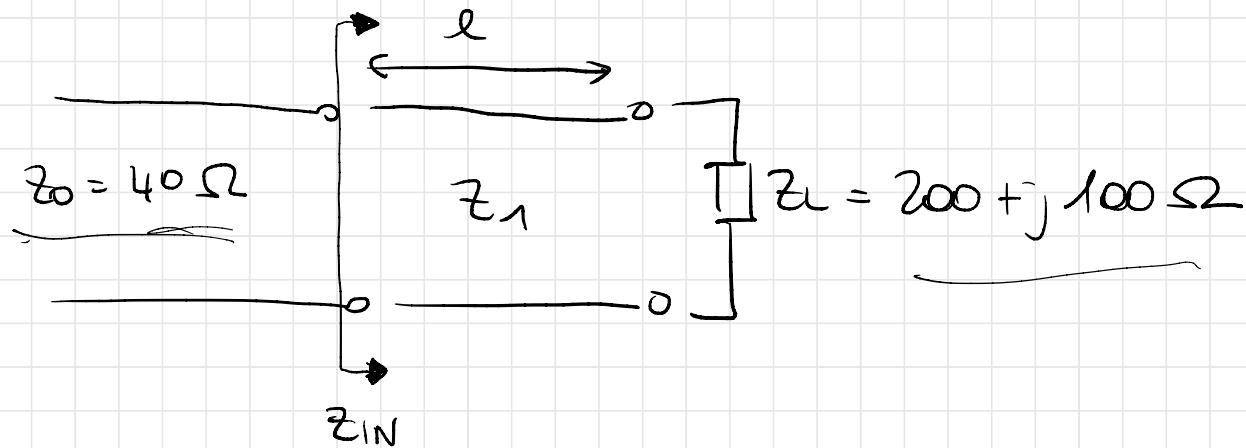Problem 3 : In the circuit shown below a $Z_L = 200 + j100 \Omega$ load is to be matched to a 40Ω line using a length l of a lossless transmission line of impedance Z_1 . Find l and Z_1 .



$$Z_{IN} = Z_1 \frac{(Z_0 + jZ_1 t) + jZ_1 t}{Z_1 + j(Z_0 + jZ_1 t)} = 40 = Z_0$$

$t = \text{time}$

$$Z_1 (200 + j100) + j Z_1^2 t = 40 Z_1 + j 40 (200 + j100)t$$

$$200 Z_1 + j (100 + Z_1 t) Z_1 = (40 Z_1 - 4000t) + j 8000t$$

By equating real and imaginary parts:

$$\begin{cases} 200 Z_1 = 40 Z_1 - 4000t \\ (100 + Z_1 t) Z_1 = 8000t \end{cases}$$

$$\begin{cases} 160 z_1 = -4000 t \Rightarrow z_1 = -25t \\ (100 - 25t^2)(-25t) = 8000t \end{cases}$$

$$\begin{cases} z_1 = -25t \\ -25(100 - 25t^2) = 8000 \end{cases}$$

$$\begin{cases} z_1 = -25t \\ 8000 + 2500 = 655t^2 \Rightarrow t^2 = 16.8 \end{cases}$$

↓

$$t = \pm \sqrt{16.8} = \pm 4.0$$

If $z_1 > 0$ then $t < 0 \Rightarrow t = -4.10$

$$t = \tan \beta e$$

$$\beta e = \tan^{-1} (-4.10) = -76.3^\circ \approx 104^\circ$$


$$\Rightarrow l = \frac{104}{\beta} = \frac{104^\circ \lambda}{2\pi} = \underline{\underline{0.288 \lambda}}$$

$\nwarrow 360^\circ$

$$z_1 = \underline{-25 \tan \beta e} = -25 (-4.1) = 102.5 \Omega$$

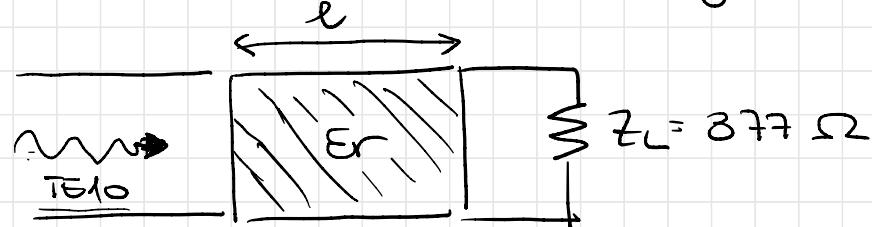Problem 4 : A waveguide load with an equivalent TE_{10} wave impedance of 377Ω must be matched to an air-filled X-band rectangular waveguide at 10 GHz.

A quarter wave matching transformer has to be used and consists of a section of a guide filled with dielectric. Find the required dielectric constant and physical length of the matching section. NOTE: All waveguides have the same geometrical dimensions.



X-band rectangular waveguide $\rightarrow a = 2.286 \text{ cm}$

$$k_0 = \frac{2\pi f}{c} = \frac{2\pi \cdot 10 \cdot 10^9}{3 \cdot 10^8} = 209.4 \text{ m}^{-1}$$

NO NEED for b since
we are propagating
a TE₁₀ mode!

In the air-filled waveguide

$$\beta_a = \sqrt{k_0^2 - \left(\frac{\pi}{a}\right)^2} = 158 \text{ m}^{-1}$$

$$Z_a = \frac{k_0 \mu_0}{\beta_a} = \frac{(209.4)(377)}{158} = 499.6 \Omega$$

The matching section will have

$$Z_m = \sqrt{Z_a Z_u} = \sqrt{499.6 \cdot 377} = 434 \Omega$$

$$l = \frac{\lambda_g}{4} = \frac{2\pi}{4\beta_m}$$

$$z_m = \frac{k_m \eta_m}{\beta_m} \Rightarrow \frac{k_0 \sqrt{\epsilon_r} \frac{\eta_0}{\sqrt{\epsilon_r}}}{\beta_m} \Rightarrow \beta_m = \frac{k_0 \eta_0}{z_m} = \frac{(209.4)(377)}{434} = 181.9 \text{ m}^{-1}$$

$$l = \frac{2\pi}{4\beta_m} = \frac{\pi}{2\beta_m} = 0.86 \text{ cm}$$

$$\beta_m = \sqrt{\epsilon_r k_0^2 - \left(\frac{\pi}{a}\right)^2} \Rightarrow \beta_m^2 = \epsilon_r k_0^2 - \left(\frac{\pi}{a}\right)^2$$

$$\epsilon_r = \frac{\beta_m^2 + \left(\frac{\pi}{a}\right)^2}{k_0^2} = \frac{(181.9)^2 + \left(\frac{\pi}{0.02285}\right)^2}{(209.4)^2} = 1.18$$

Problem 5: Design a three section binomial transformer


To match a $Z_L = 100 \Omega$ load to a $Z_0 = 50 \Omega$ line and calculate the bandwidth for $\Gamma_m = 0.05$.

$$N=3$$

$$Z_L = 100 \Omega$$

$$Z_0 = 50 \Omega$$

$$\Gamma_m = 0.05$$

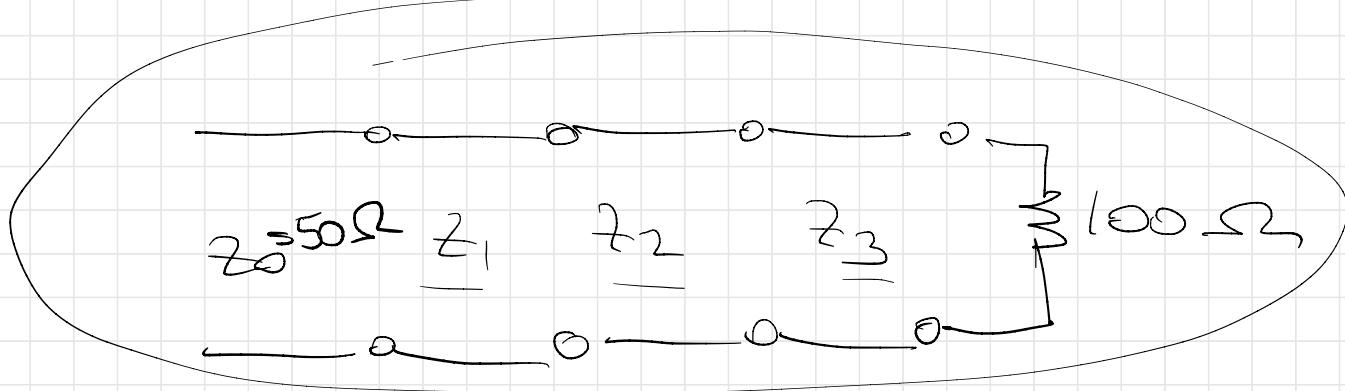

$$\frac{\Delta f}{f_0} = 2 - \frac{4}{\pi} \cos^{-1} \left[\frac{1}{2} \left(\frac{\Gamma_m}{|\Gamma|} \right)^{\frac{1}{N}} \right]$$

$$A = 2^{-N} \frac{z_L - z_0}{z_L + z_0} \underset{\underline{\hspace{10em}}}{\simeq} \frac{1}{2^{N+1}} \ln \frac{z_L}{z_0} \simeq 0.0433$$

$$\frac{\Delta f}{f_0} = 2 - \frac{4}{\pi} \cos^{-1} \left[\frac{1}{2} \left(\frac{0.05}{0.0433} \right)^{1/3} \right] = 0.7$$

70%

From Table:

$$z_1 = 1.0907 \cdot z_0 = 1.0907 \cdot 50 = 54.5 \Omega$$

$$z_2 = 1.4142 \cdot z_0 = 70.7 \Omega$$

$$z_3 = 1.8337 \cdot z_0 = 91.7 \Omega$$

Problem 6

Design a three-section Chebyshev transformer to match a 100Ω load to a 50Ω line with $\Gamma_m = 0.05$.

$$N = 3$$

$$Z_L = 100\Omega$$

$$Z_0 = 50\Omega$$


$$\Gamma_m = 0.05$$

$$\frac{\Delta f}{f_0} = 2 - \frac{4\Gamma_m}{\pi}$$

$$\begin{aligned} \sec \Theta_m &= \cosh \left[\frac{1}{N} \cosh^{-1} \left(\frac{\ln(Z_L/Z_0)}{2\Gamma_m} \right) \right] = \\ &= \cosh \left[\frac{1}{3} \cosh^{-1} \left(\frac{\ln(100/50)}{2(0.05)} \right) \right] = \\ &= 1.408 \end{aligned}$$

$$\Theta_m = 44.7^\circ$$
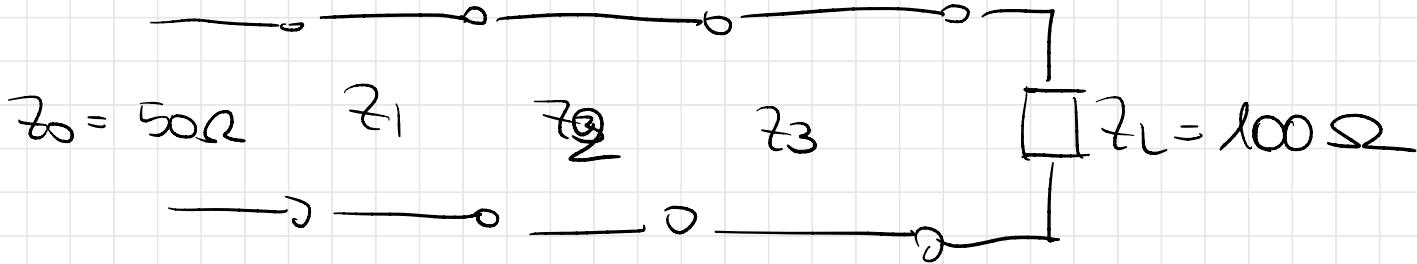
$$\frac{df}{f_0} = 2 - 4 \left(\frac{44.7^\circ}{180^\circ} \right) = 1.01$$



From Table:

$$z_1 = 1.1475 z_0 = 57.5 \Omega$$

$$z_2 = 1.4142 z_0 = 70.7 \Omega$$

$$z_3 = 1.7429 z_0 = 87 \Omega$$

