



SBM and DBM diode-based mixers

SBM: Single Balanced Mixer = 2 SEM with couplers or baluns

DBM: Double Balanced Mixer = 2 SBM with couplers or baluns



Advantages

- Suppression of some spurs by out of phase recombination
- Good LO-RF Isolation and sometimes LO-IF isolation without filtering issues


Disadvantages

- Requirement of higher levels of LO power



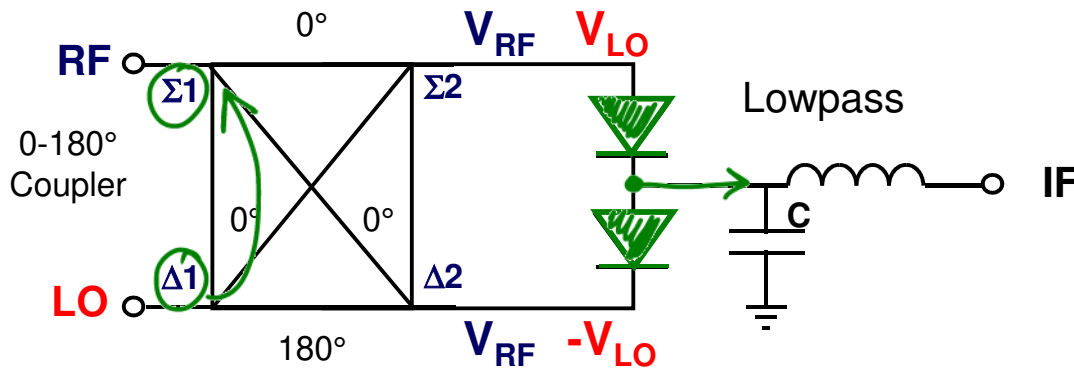Example of a diode-based SBM (LO at Δ port)

• Architecture with 180° coupler (LO @ Δ)



180° Coupler


Input Matching @LO/RF \approx Input Matching@LO/RF of coupler

Isolation LO-RF \approx Isolation LO-RF of coupler

LO @ $\Sigma \rightarrow \text{mix}[\text{EH}(\text{LO}), *]$ rejected

LO @ $\Delta \rightarrow \text{mix}[*, \text{EH}(\text{RF})]$ rejected

• Operation mode (LO @ Δ)

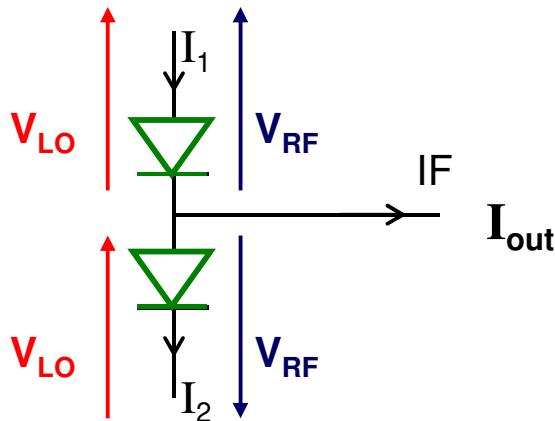

Diode current law

$$I(V) = \mathbf{F}(V) = a.V + b.V^2 + c.V^3 + \dots$$

$$I_1 = \mathbf{F}(V_{\text{LO}} + V_{\text{RF}})$$

$$I_2 = \mathbf{F}(V_{\text{LO}} - V_{\text{RF}})$$


$$V_{\text{LO}}^p \cdot V_{\text{RF}}^q \rightarrow \pm p.\omega_{\text{LO}} \pm q.\omega_{\text{RF}}$$

$$I_{\text{OUT}} = I_1 - I_2 = 0 \Leftrightarrow \omega = \pm m.\omega_{\text{LO}} \pm n.\omega_{\text{RF}}$$

If **n is even** because $(V_{\text{RF}})^n = (-V_{\text{RF}})^n$

$\omega_{\text{LO}}, 2(\omega_{\text{LO}} - \omega_{\text{RF}}), \dots$ suppressed @ IF port \rightarrow (LO-IF Isolation) ...

n=0 n=2

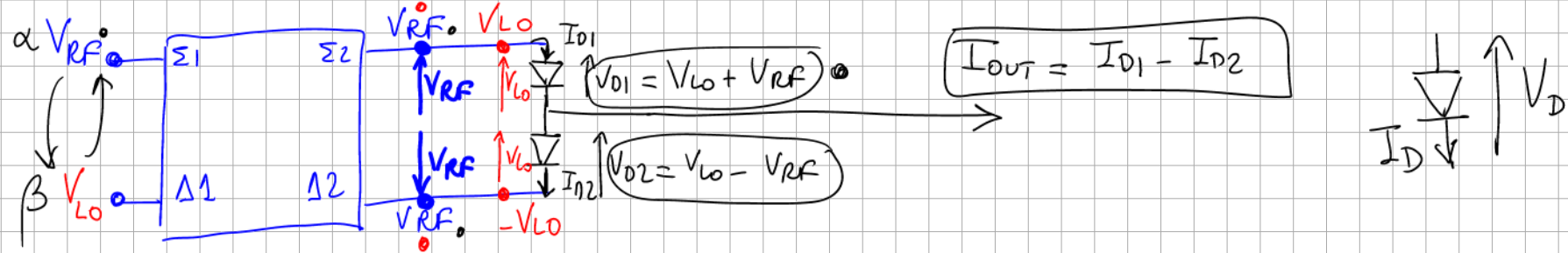

~~$$I_D = \exp(V_D)$$~~

$$I_D = f_{NL}(V_D) = a V_D + b V_D^2 + c V_D^3 + \dots$$

$$\begin{cases} I_{D1} = a(V_{LO} + V_{RF}) + b(V_{LO} + V_{RF})^2 + c(V_{LO} + V_{RF})^3 \\ I_{D2} = a(\text{---}) + b(\text{---}) + c(\text{---}) \end{cases}$$

$$I_{OUT} = I_{D1} - I_{D2}$$

$$= 2aV_{RF} + 4bV_{LO}V_{RF} + 2cV_{RF}^3 + 6cV_{LO}^2V_{RF}$$

$$\omega_{RF}$$

spurs

$$\omega_{IF}$$

$$\omega_{\Sigma}$$

$$\omega_{RF}$$

$$3\omega_{RF}$$

$$\omega_{RF}$$

$$2\omega_{LO} + \omega_{RF}$$

$$2\omega_{LO} - \omega_{RF}$$

$$(a+b)^3 = a^3 + b^3 + 3a^2b + 3ab^2$$


$$(a-b)^3 = a^3 - b^3 - 3a^2b + 3ab^2$$

$$ISO_{LO-RF} =$$


$$ISO_{LO-IF} = \infty$$

Diode-based SBM : LO and RF ports are reversed (LO at Σ port)

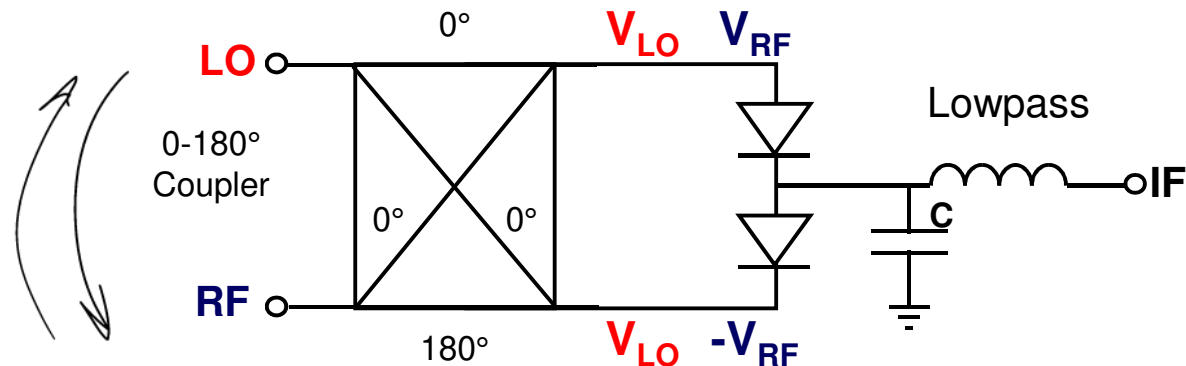• Architecture with 180° coupler (LO @ Σ)



• If LO and RF are reversed

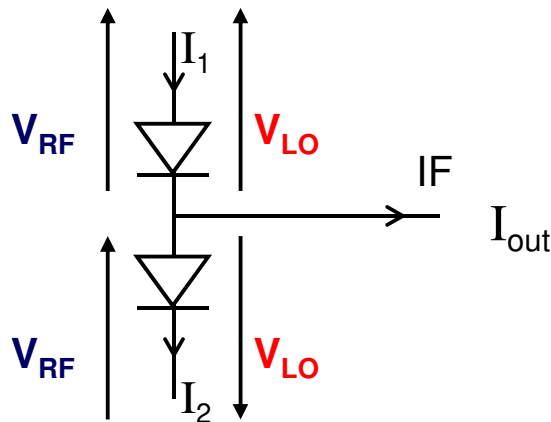

$$I(V) = F(V) = a.V + b.V^2 + c.V^3 + \dots$$

$$I_1 = F(V_{RF} + V_{LO})$$

$$I_2 = F(V_{RF} - V_{LO})$$

$$V_{LO}^p \cdot V_{RF}^q \rightarrow p\omega_{LO} \pm q\omega_{RF}$$

$$I_{OUT} = I_1 - I_2 = 0 \Leftrightarrow \omega = \pm m.\omega_{LO} \pm n.\omega_{RF}$$

$$\text{If } m \text{ is even because } (V_{LO})^m = (-V_{LO})^m$$

➡ $\omega_{RF}, 2(\omega_{LO} - \omega_{RF}), \dots$ suppressed @IF port \rightarrow (RF-IF Isolation) ...
 $m=0 \quad m=2$ Less critical ✖

Diode-based SEM

- Properties are linked to the architecture (Baluns, Couplers, ...)
- Conversion losses of SBM are higher than conversion losses of SEM
(Coupler losses, Non ideal phase shift and amplitude balance ...)
- SBM enable to suppress critical spurs and enhance isolations



Diode-based SBM are more efficient than diode-based SEM


Diode-based DBM

A diode-based DBM \times
integrates 2 pairs of diodes

Diode-based DBM are preferred to SBM
if the isolation requirements are more critical than the conversion loss specifications

Example of diode-based DBM : Ring oscillator


•Architecture

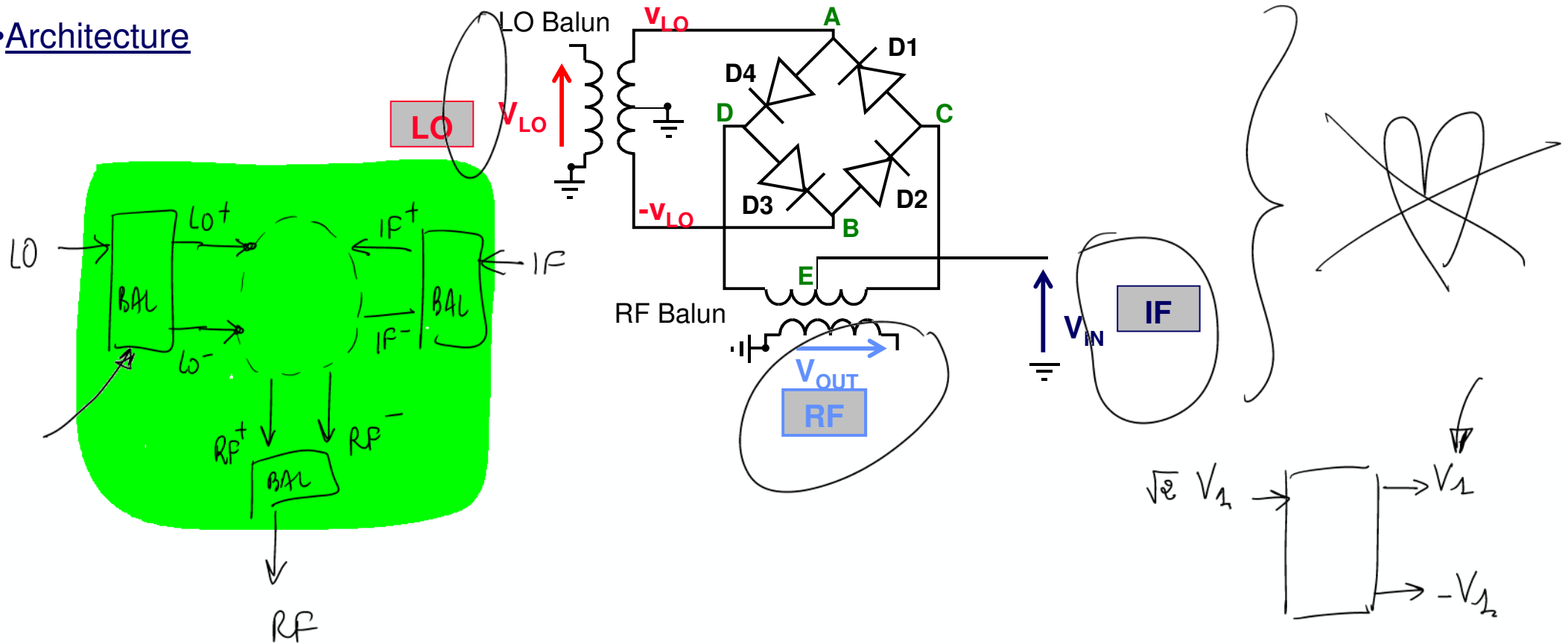

Cold-FET mixers : Principle

Main advantages : High linearity and No Consumption

Principle of cold-FET resistive mixers

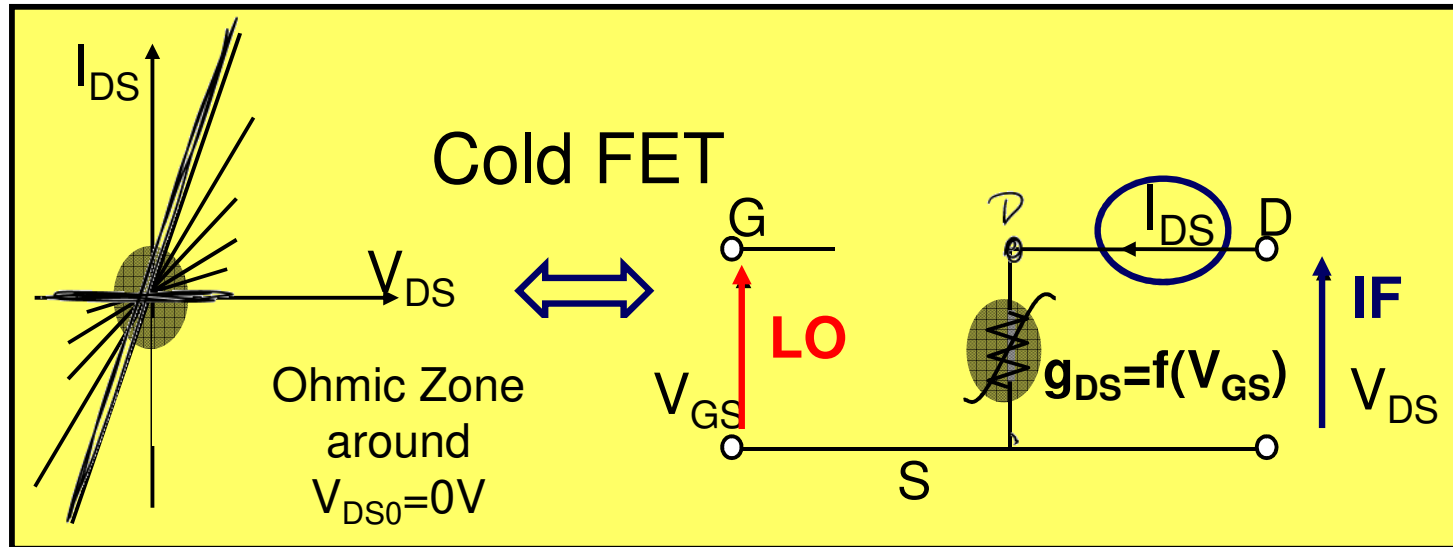

$$V = RI$$

Not biased Drain


→ Transconductance g_m is zero @ $V_{DS0}=0$

→ Resistive Nonlinearity $R_{DS}(V_{GS})$ between drain and source

$$\text{Cold} \rightarrow V_{DS0} = 0 \rightarrow P_{DC} \neq V_{DS0} \cdot I_{DS0} = 0 \rightarrow P_{DIS} = 0 \rightarrow T = T_{amb}$$

$$\rightarrow \text{Ohmic zone} \begin{cases} g_m = 0 \text{ (no gain)} \\ R_{DS}(V_{GS}) \end{cases}$$


Cold-FET advantages

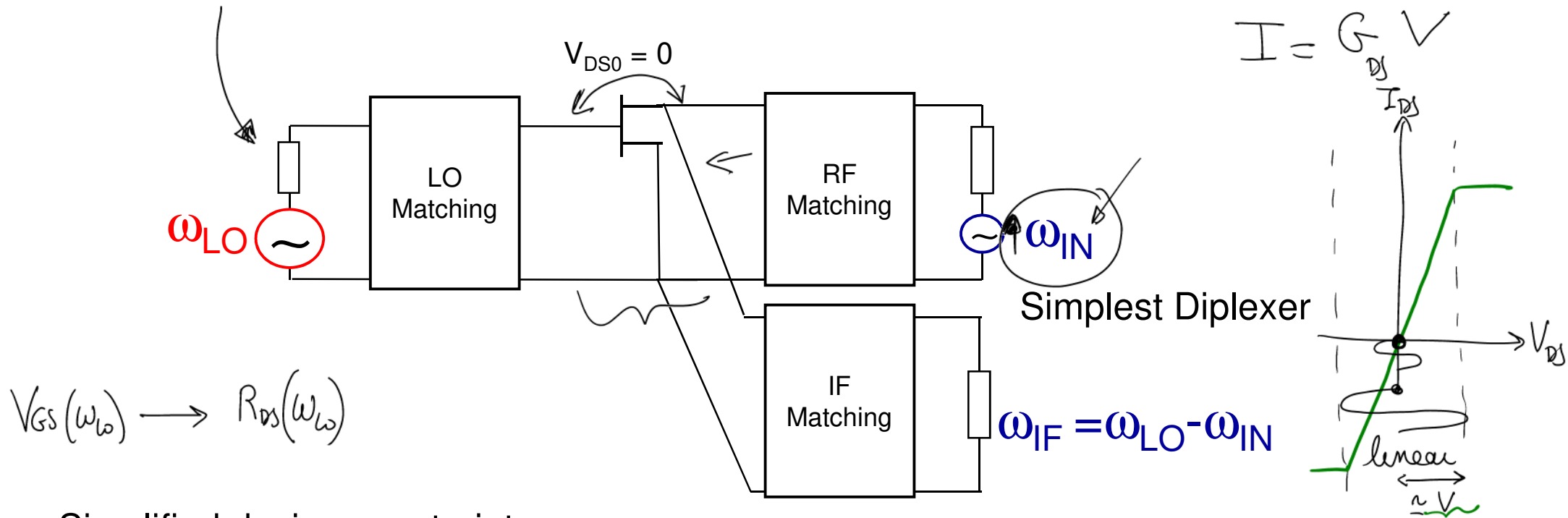

→ Simplified design constraints

- better LO-RF isolation due to the intrinsic G-D isolation of FETs (depends on C_{gd} and ω)
- limited interactions between matching circuits (LO @ gate port and $\omega_{RF} \gg \omega_{IF}$ @ drain port)
- higher linear voltage swing of RF signal from 0 to knee voltage → higher linearity
- mixer that can be efficiently used in SEM configuration

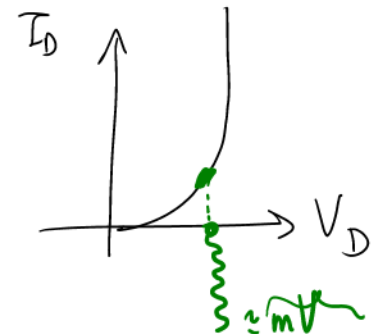→ Other solutions: SBM and DBM cold-FET mixers



Comparison (Diode / Cold FET)



- Conversion losses

→ $L_C(\text{Diode Mixers}) < L_C(\text{Cold-FET mixers})$ because $R_{\text{MIN}}(\text{Diode}) < R_{\text{MIN}}(\text{Cold-FET})$

- Linearity/Saturation

- Linearity of diode-based mixer is limited to very low level of RF signal (exponential current)

- Linearity of cold-FET mixer is limited to moderate level of RF signal (ohmic zone)

→ Higher linearity of cold-FET and higher output power

- Isolations

- Diodes do not have intrinsic isolation → can only used in complex balanced architectures

- Cold-FETs have the intrinsic G-D isolation → can be used as SEM or balanced topologies

Cold-FET SBM


Cold-FET SBM

• Example of SBM with LO and IF baluns (emission)

- Pair of cold-FETs

Single Balanced

Diplexer IF-RF

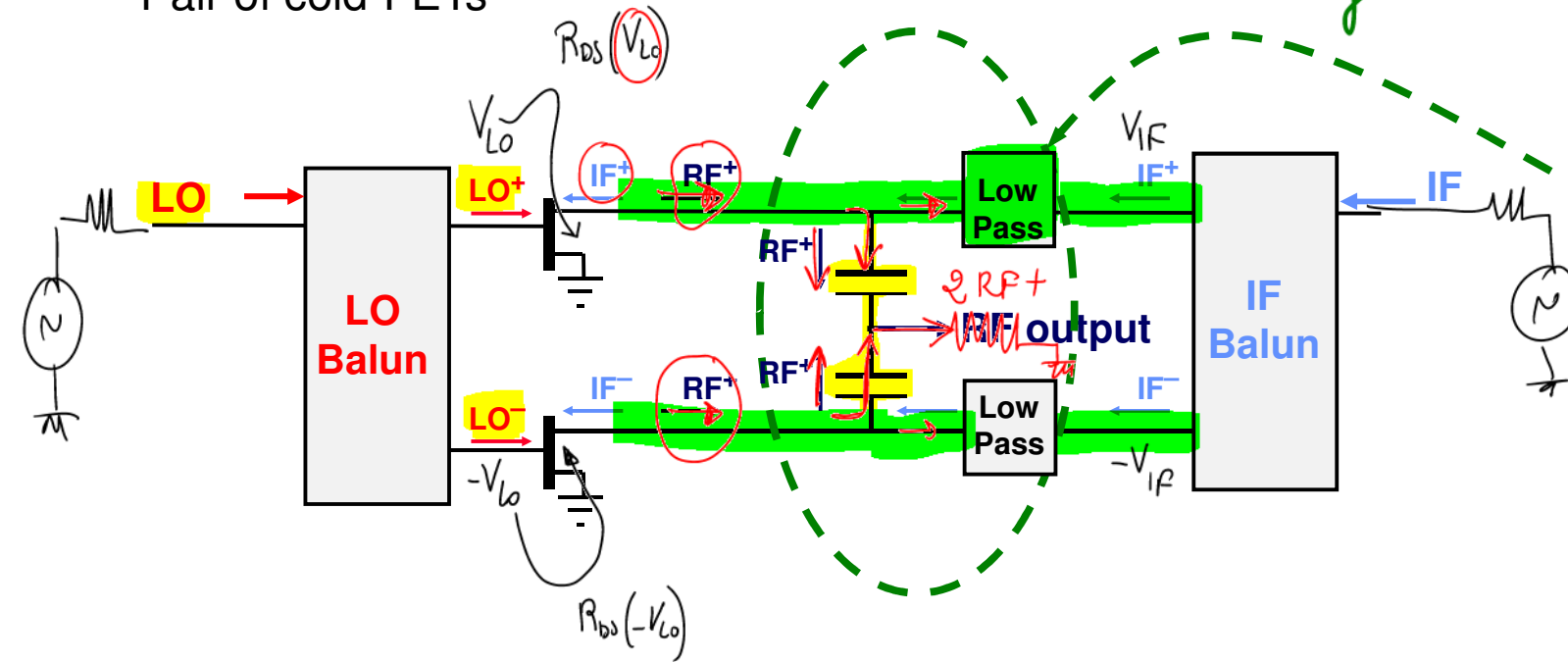

$$Z_c = \frac{1}{jC\omega}$$


$$Z_c(\omega_{IF}) \gg$$

$$I_{DS} = \underbrace{G_{DS}}_{LO} \underbrace{V_{DS}}_{IF}$$


Cold-FET SBM

- Example of SBM with LO and IF baluns (emission)

- Pair of cold-FETs

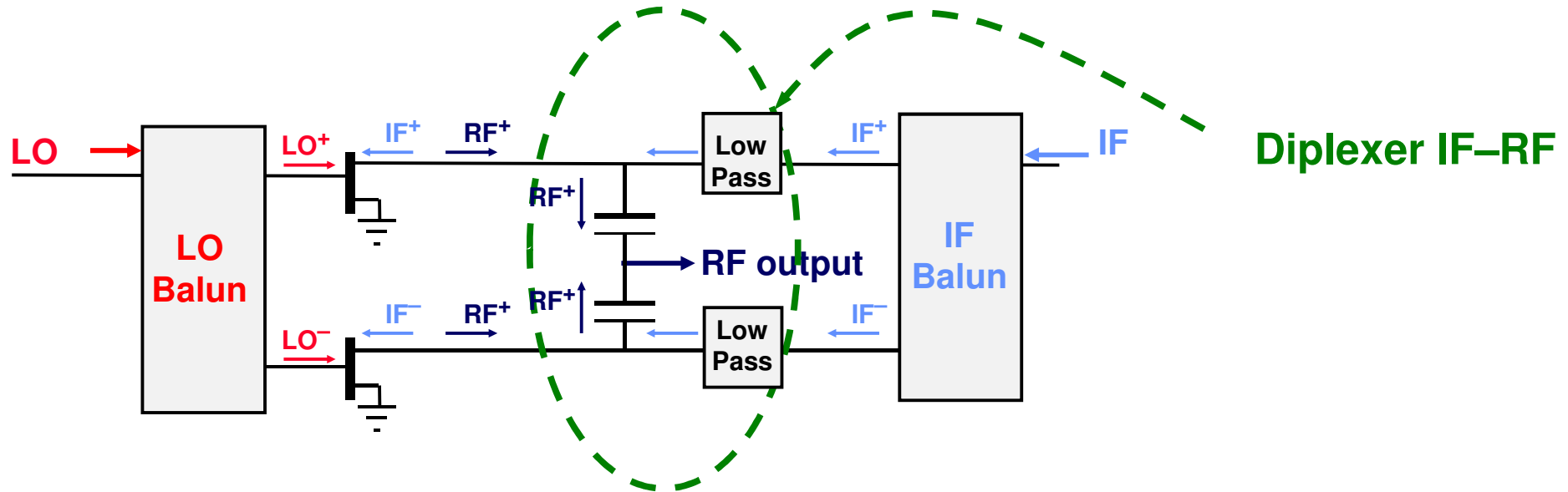

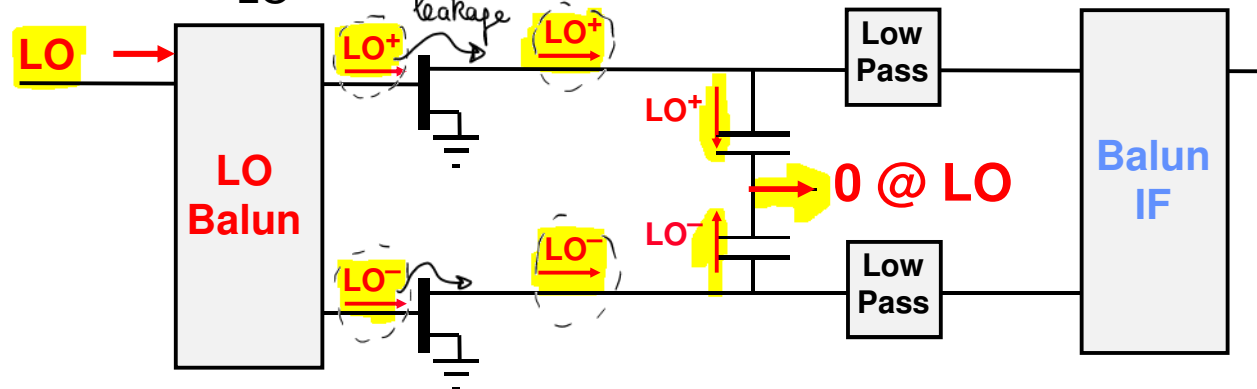- Balanced architecture $\Rightarrow \omega_{LO}$ suppressed @ drain port




Isolation LO - RF

Cold-FET DBM


Ring mixer

4 Cold-FETs + 3 Baluns (RF, IF, LO)

Switch mode of Cold-FET

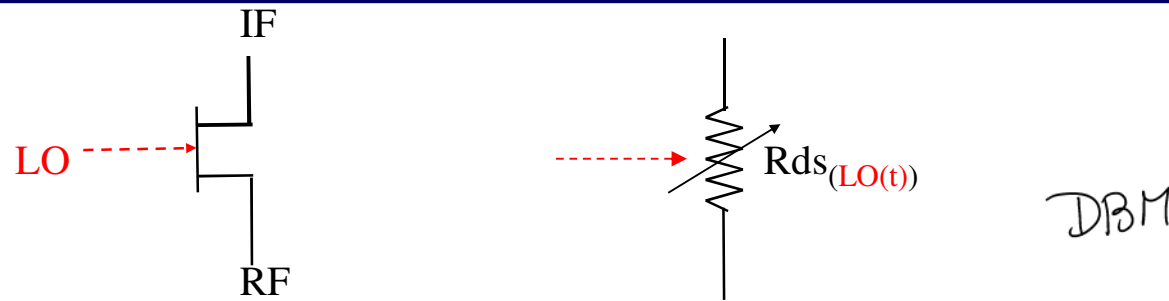


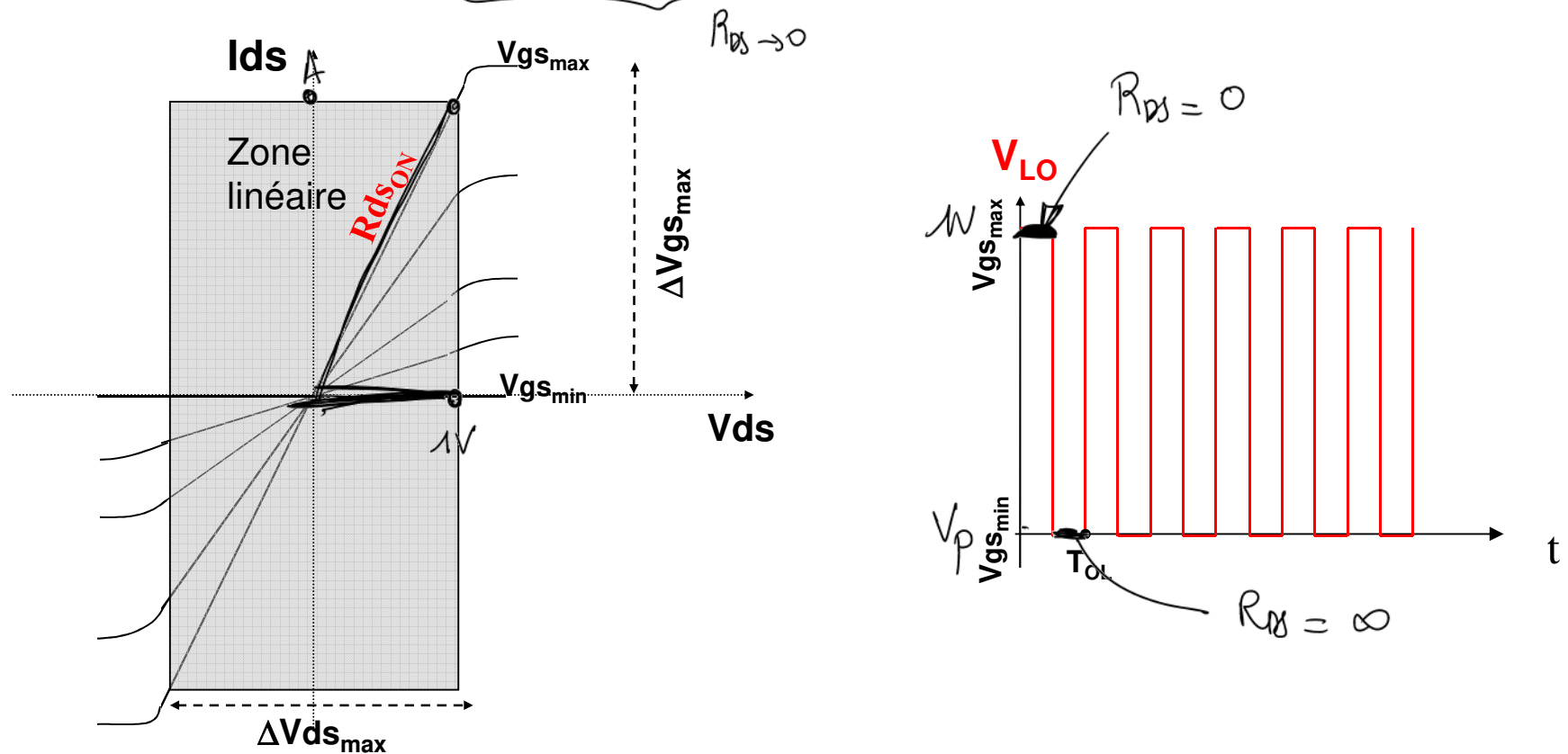The Cold-FET is switched between $R_{DS_{ON}}$ (minimum value of R_{DS}) and ∞ (maximum value of R_{DS})





If the transistor size is increased $\rightarrow \left\{ I_{DS_{MAX}} \uparrow \right\} \rightarrow \left\{ R_{DS_{ON}} \downarrow \right\} \rightarrow \left\{ \text{Conversion losses} \downarrow \right\}$
 However $\rightarrow \left\{ C_{GS} \uparrow \right\} \rightarrow \left\{ \text{Frequency limitation} \uparrow \right\}$

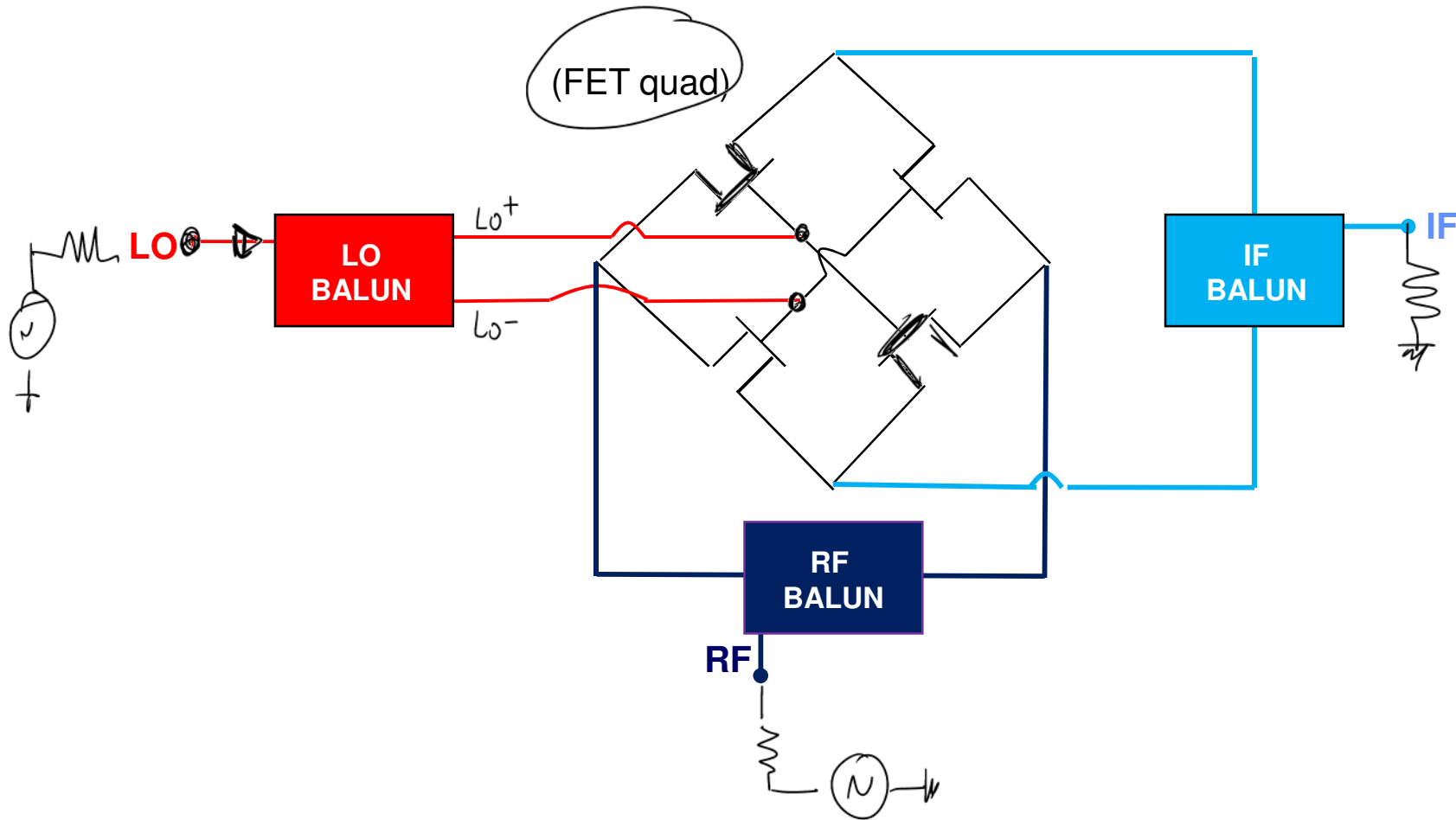Cold-FET « Switch Mode Mixer » : Ring DBM





Operating principle of the ring Cold-FET DBM
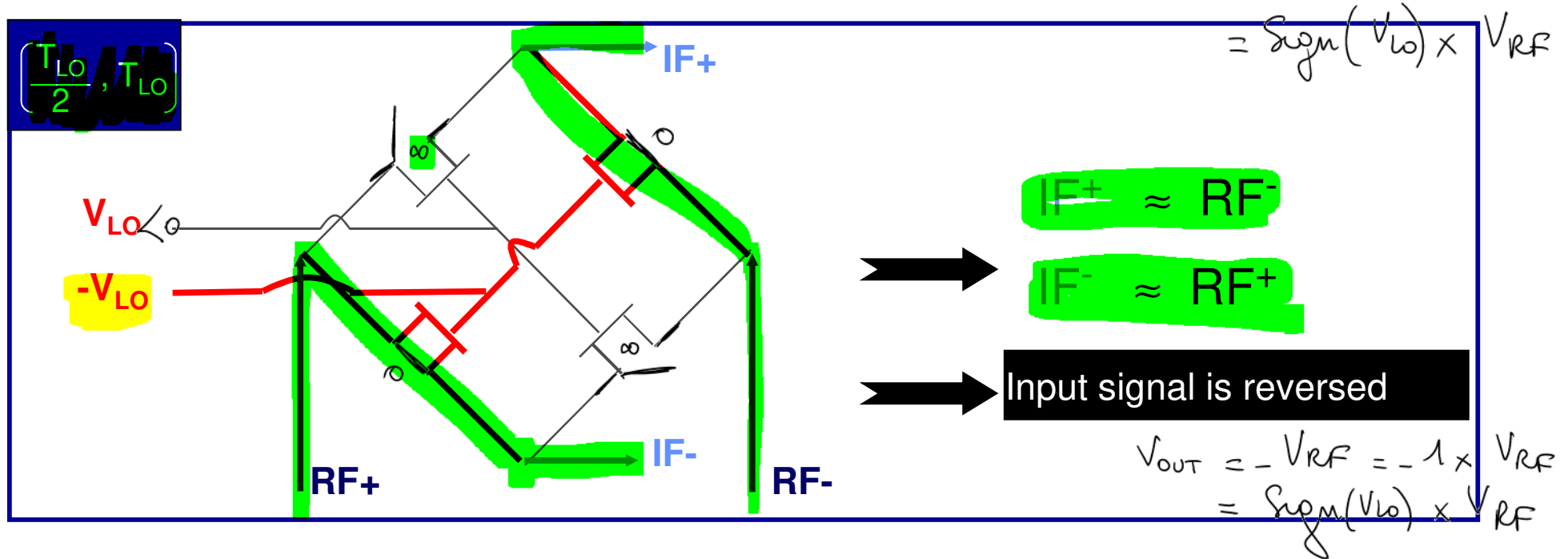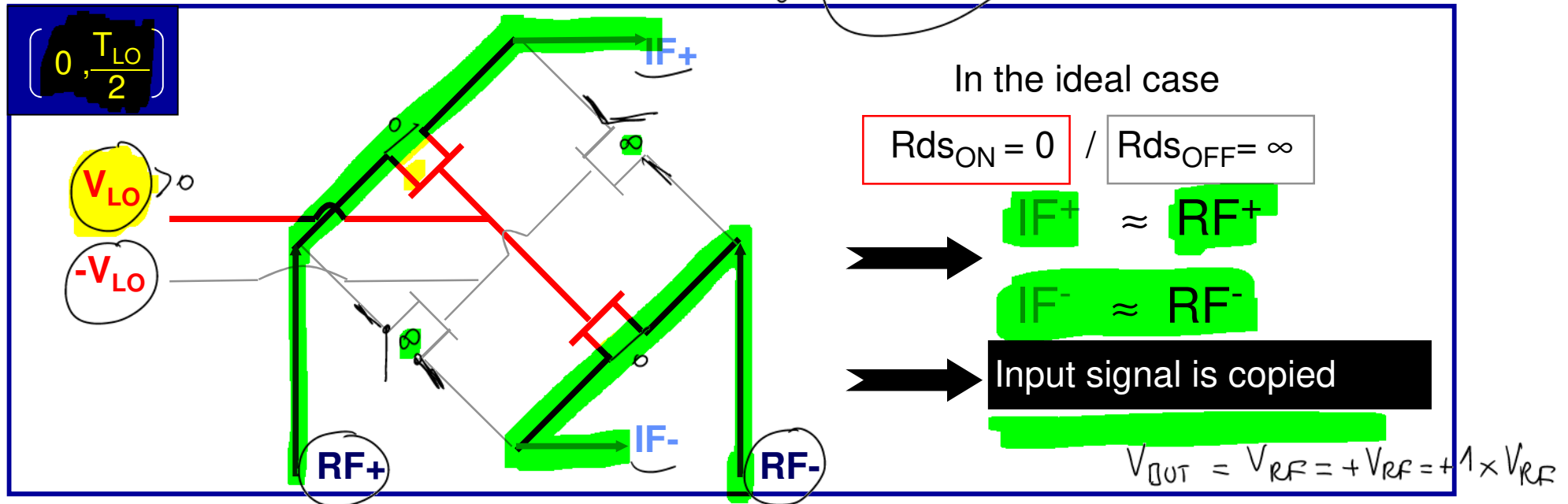
$$V_{OUT} = V_{IN} \times \text{Sign}(V_{LO}) \rightarrow (2k+1) \omega_{LO} \pm \omega_{IN}$$




Main Cold-FET mixer architectures

◆ Cold-FET Mixers

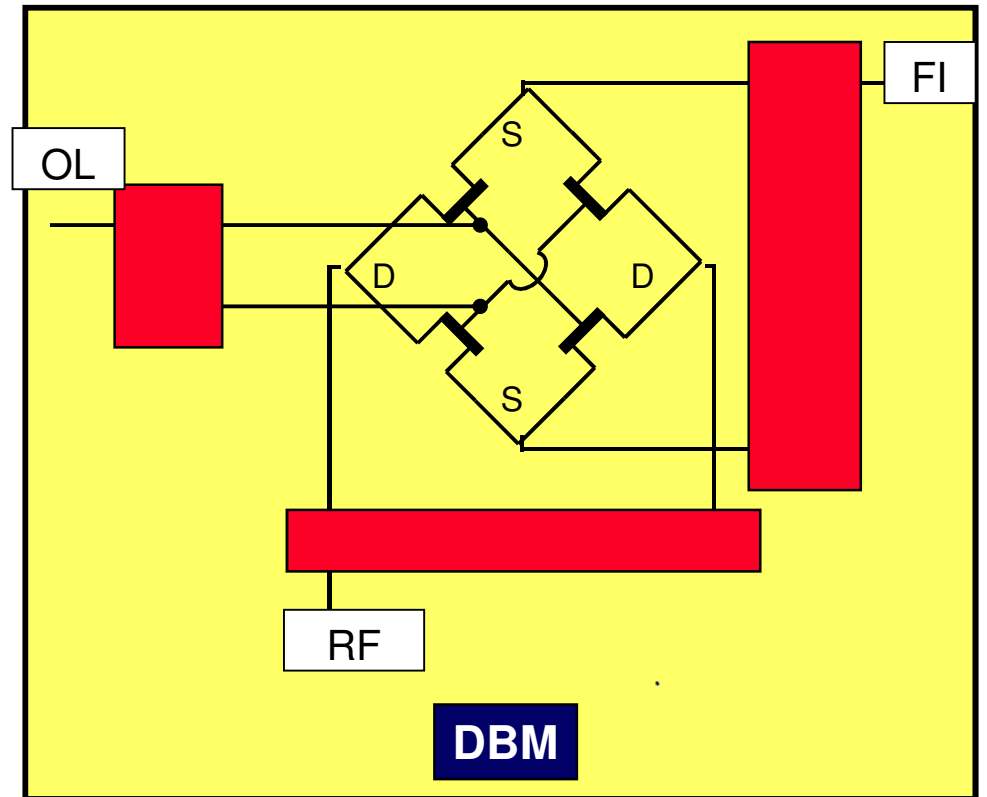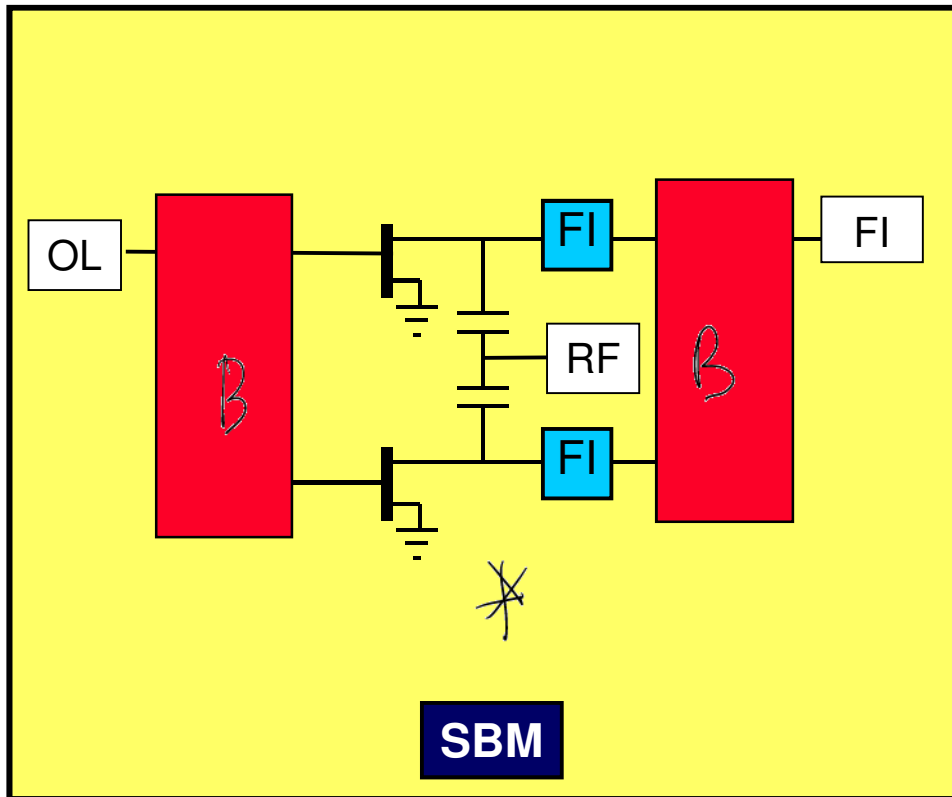


Example of IRM (Image Rejection Mixer)

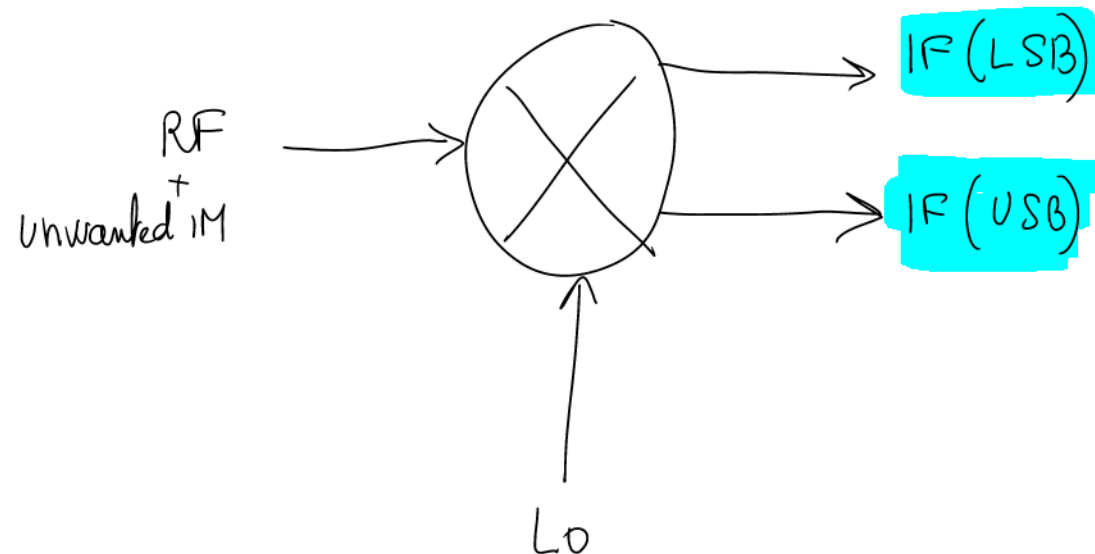




Example of IRM

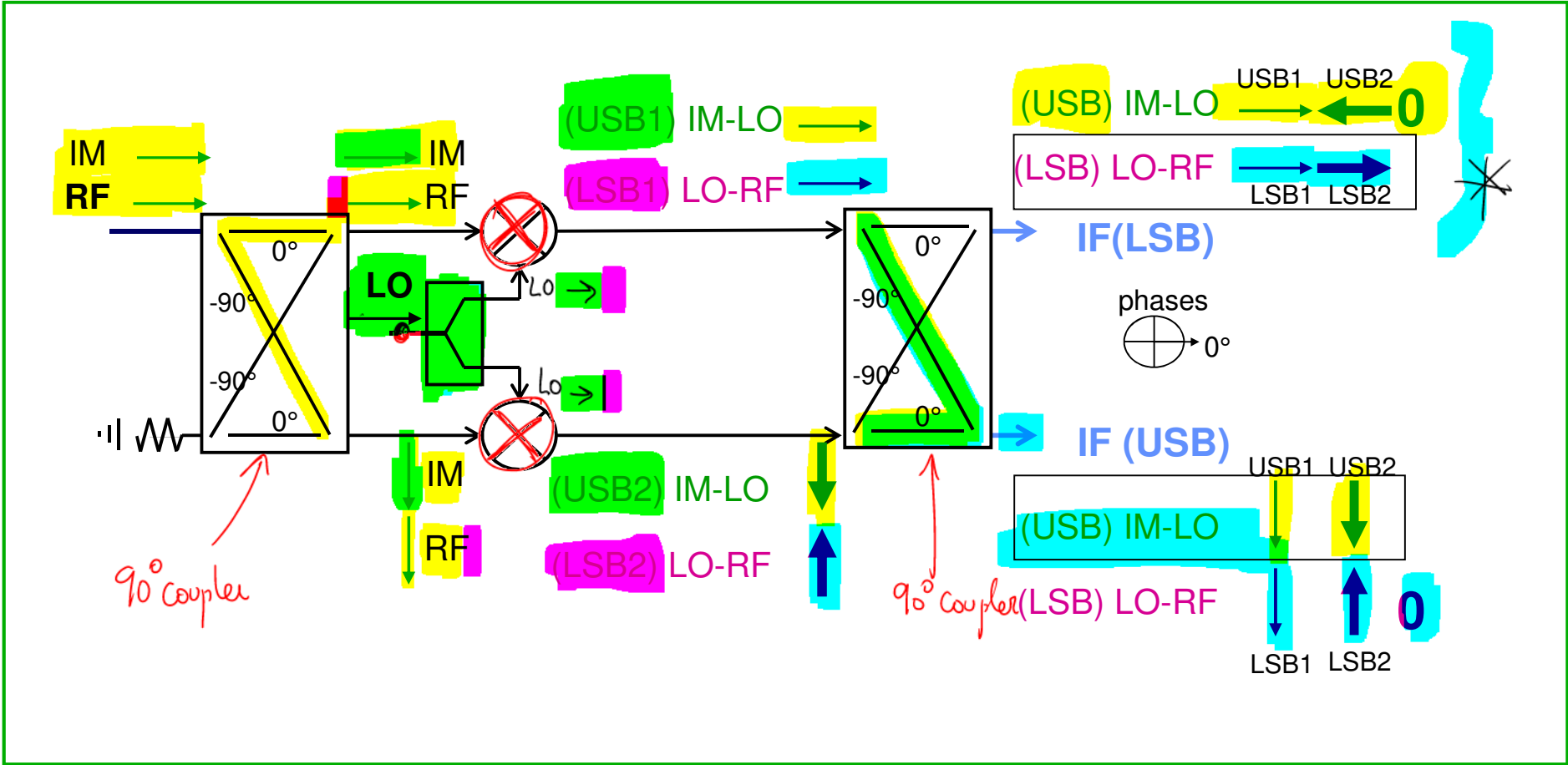

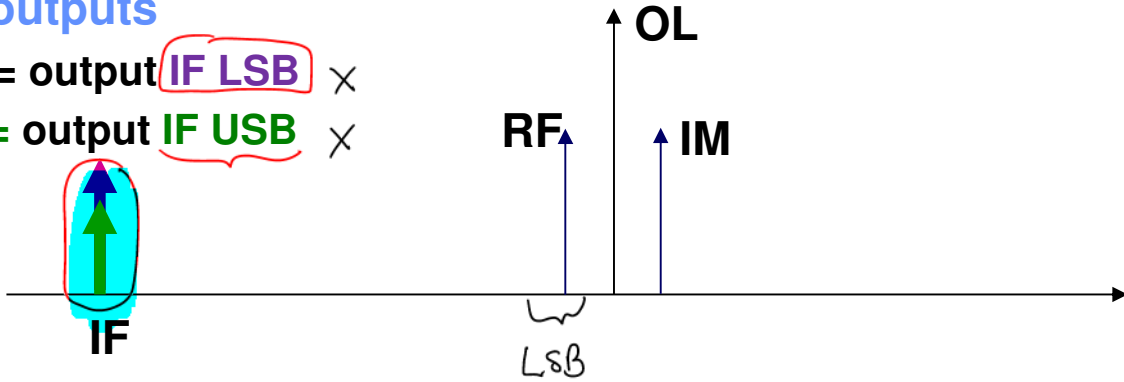IF outputs
= (LO-RF) = output IF LSB ×
= (IM-LO) = output IF USB ×



Mixer \otimes

$$(\omega_1 + \omega_2)t + (\varphi_1 + \varphi_2)$$
$$(\omega_1 - \omega_2)t + (\varphi_1 - \varphi_2)$$