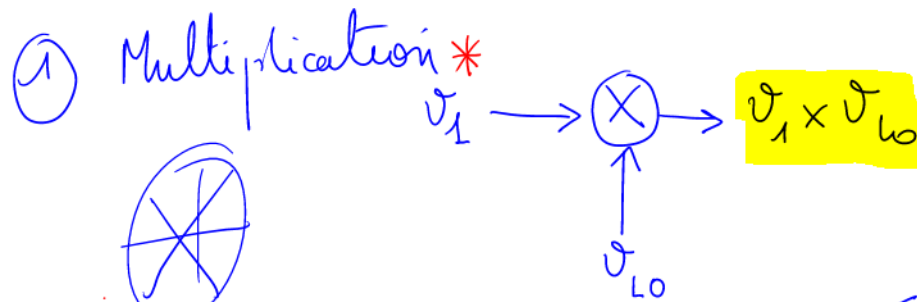



Spurs = Spurious =
 "parasitic unwanted" frequencies

Principle of frequency conversion



"Gilbert cell" only at low freq


→ only one spur

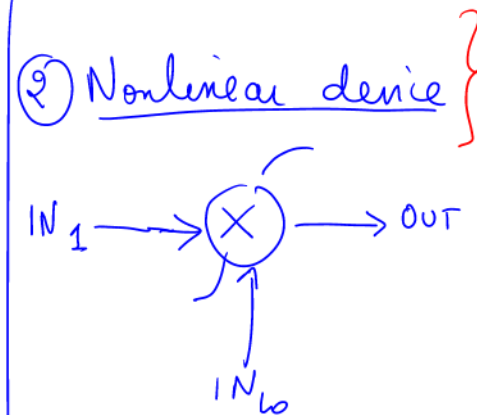


$$OUT = f_{NL}(IN_1 + IN_{LO})$$

$$= a(IN_1 + IN_{LO}) + b(IN_1 + IN_{LO})^2 + \dots$$


2b $IN_1 IN_{LO}$
 → many spurs

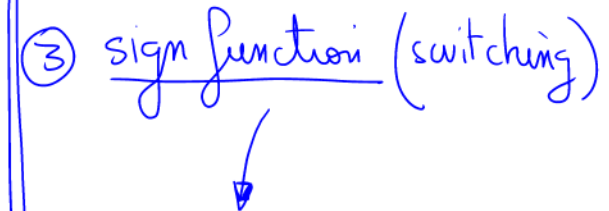

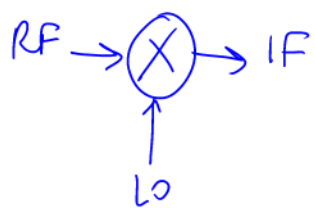

Mixing Function modelled by an ideal multiplier

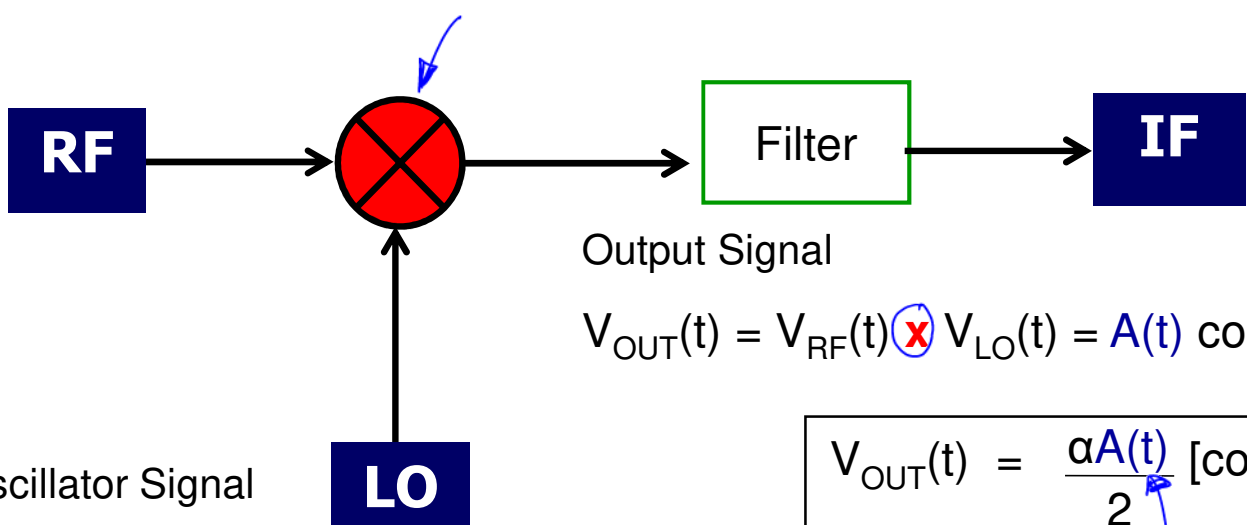Input Signal RF
 $V_{RF}(t) = A(t) \cos(\omega_{RF} \cdot t)$





Oscillator Signal
 $V_{LO}(t) = \alpha \cos(\omega_{LO} \cdot t)$

Output Signal
 $V_{OUT}(t) = V_{RF}(t) \times V_{LO}(t) = A(t) \cos(\omega_{RF} \cdot t) \times \alpha \cos(\omega_{LO} \cdot t)$

$$V_{OUT}(t) = \frac{\alpha A(t)}{2} [\cos(\omega_{\Delta} t) + \cos(\omega_{\Sigma} t)]$$

$$\omega_{\Sigma} = \omega_{LO} + \omega_{RF}$$

•USB and LSB Modes

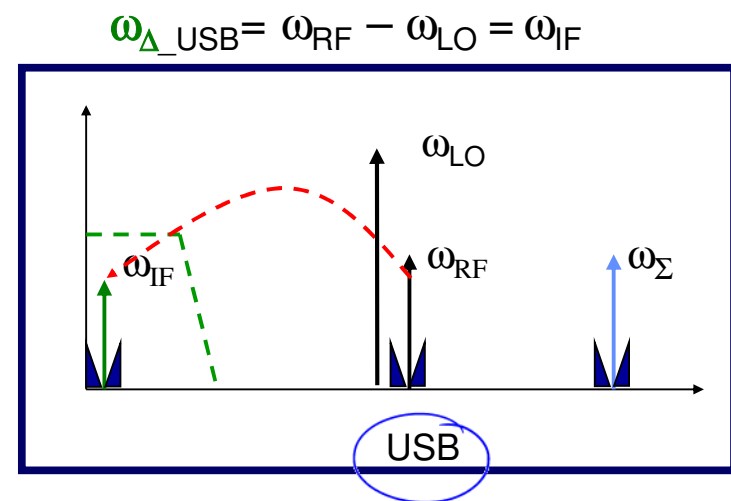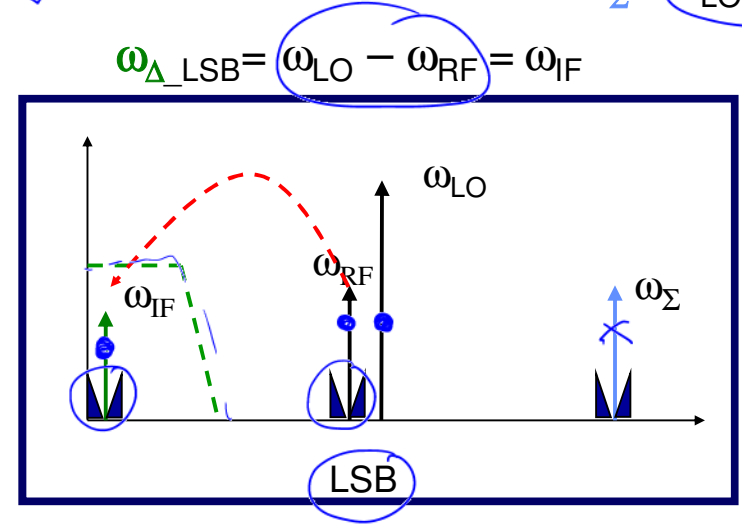

Ideal mixing because the only unwanted frequency is largely outside the useful bandwidth


$$\cos(a) \times \cos(b) = \frac{1}{2} \left(\cos(\overset{\Sigma}{a+b}) + \cos(\overset{\Delta}{a-b}) \right)$$

Example of Active Multiplier


- ◆ **Principle** : Voltage Multiplication of Input Voltages

$$V_{\text{out}}(t) = V_{i1}(t) \times V_{i2}(t)$$

- ◆ **Gilbert Cell**

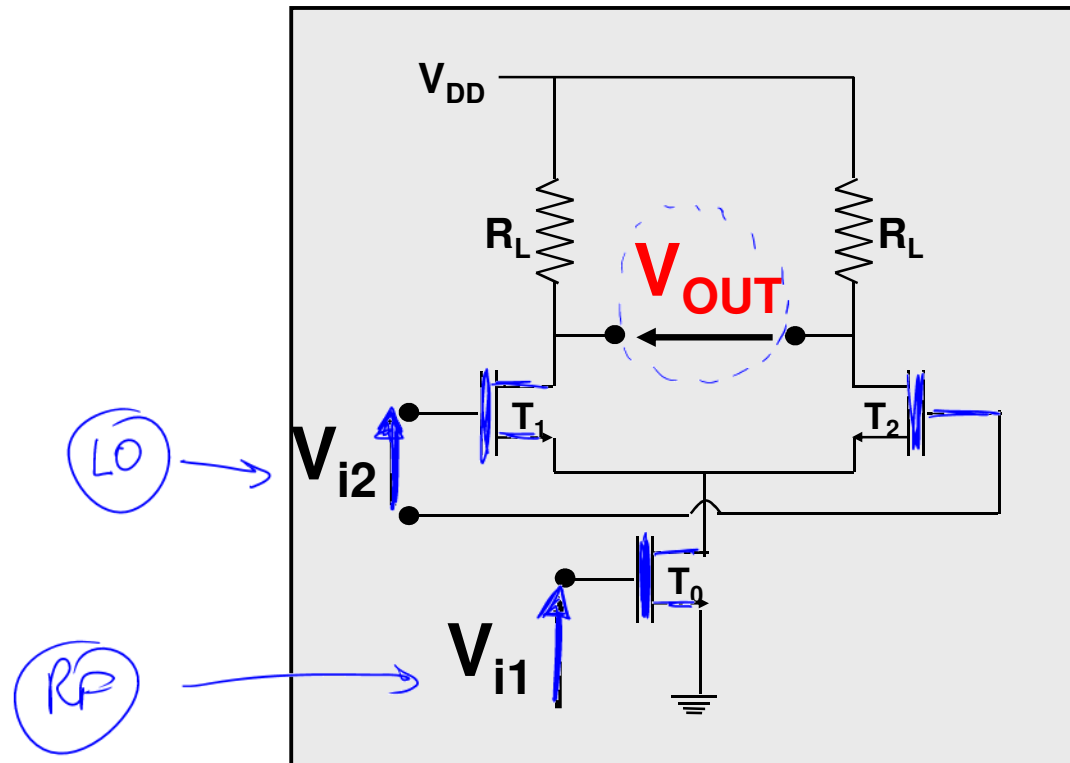


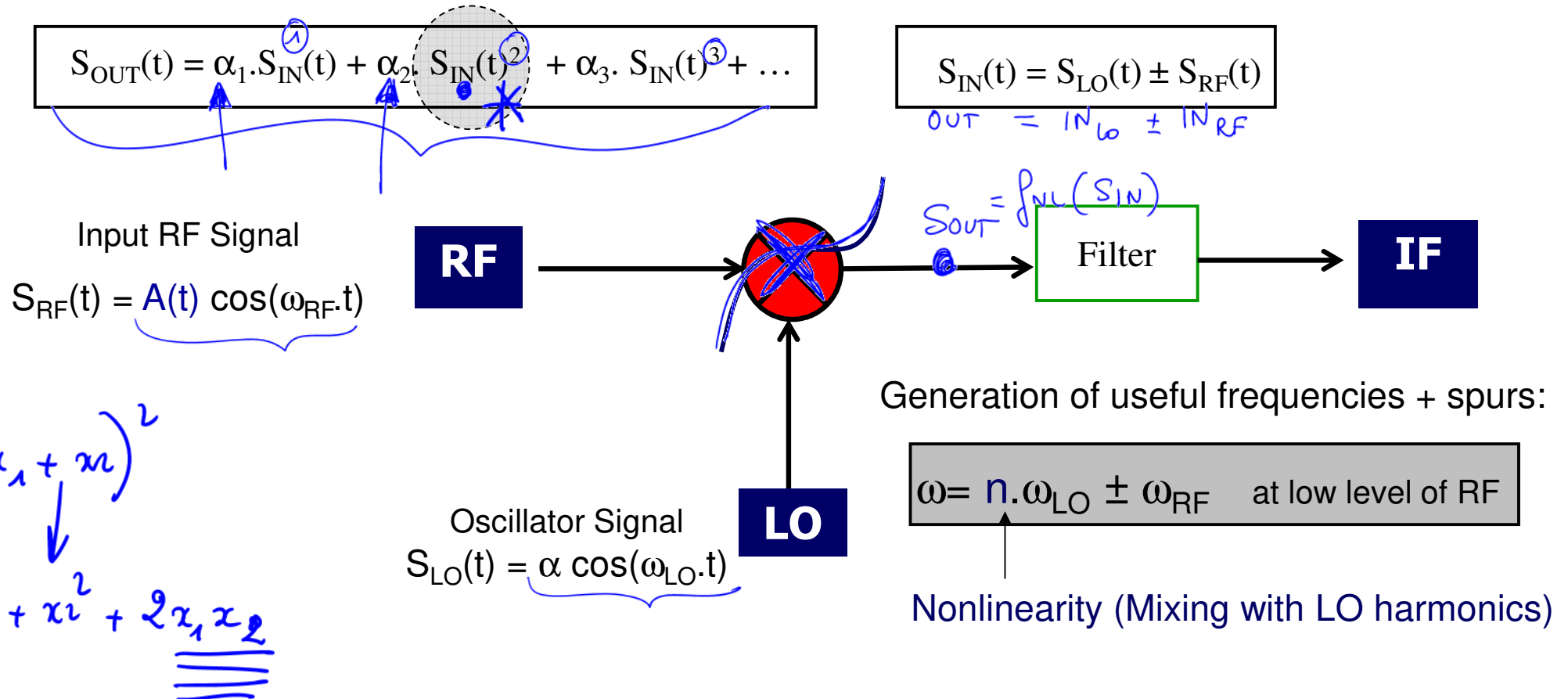
Mixing Function performed by a nonlinear device



2nd Order Nonlinearity → useful signal @ $\pm(\omega_{LO} - \omega_{RF})$


but the nonlinearity gives a lot of parasitic frequencies (spurs)

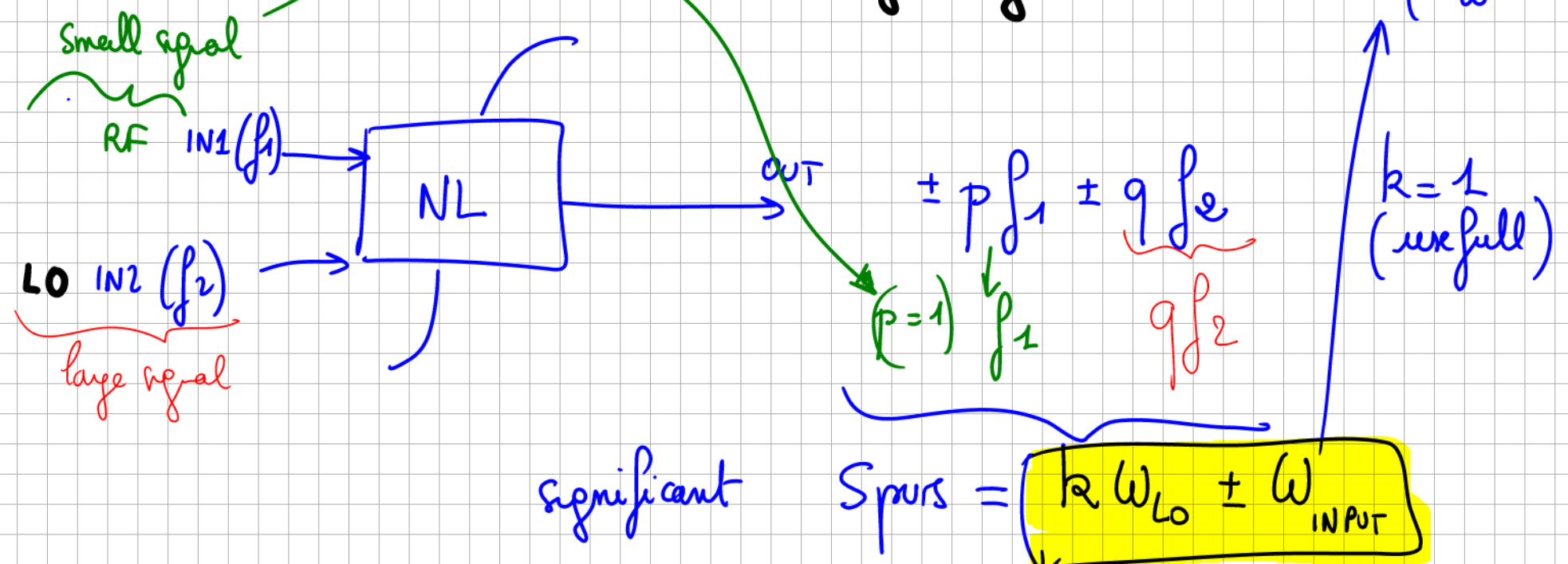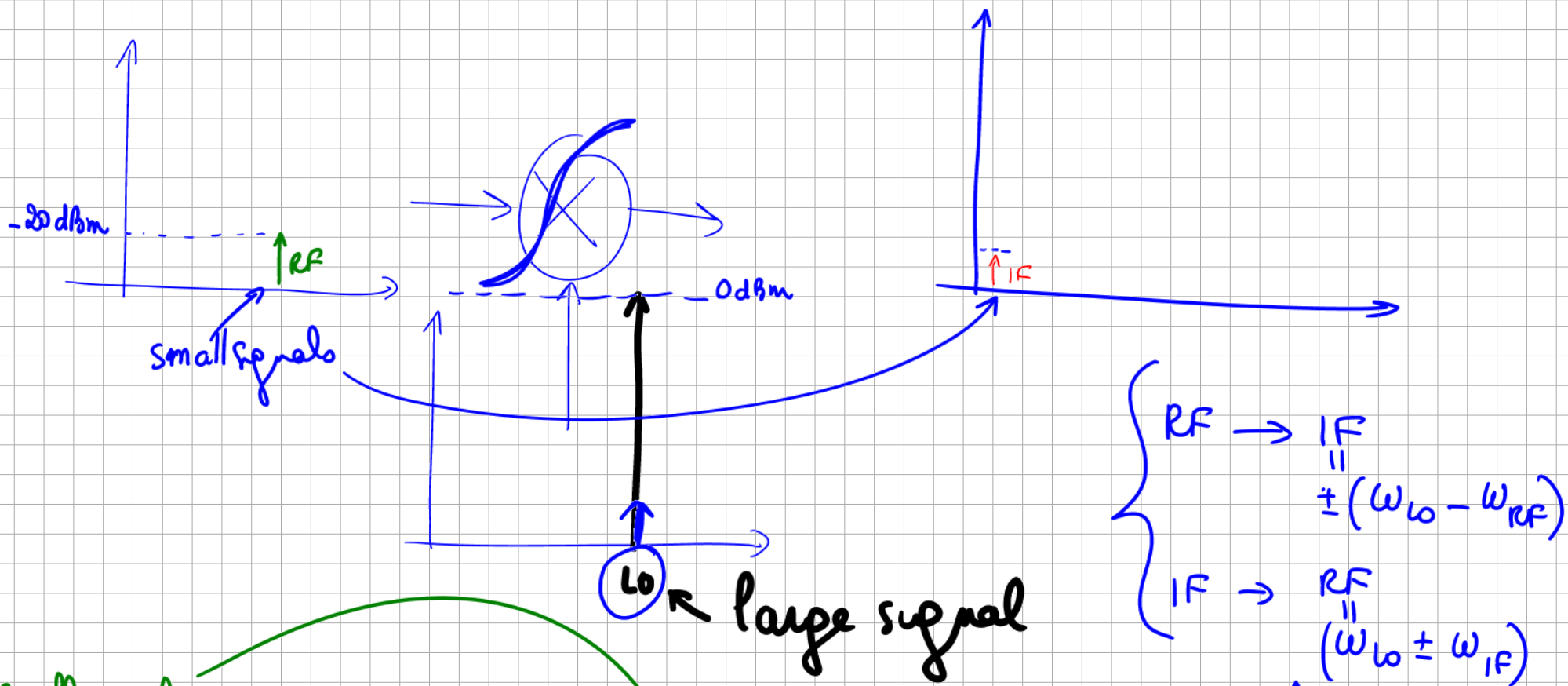Nonlinear devices used in High-Frequency Mixers : Diodes and Transistors



Mixing by LO switching : Frequency generation of a square signal « Sign Function »

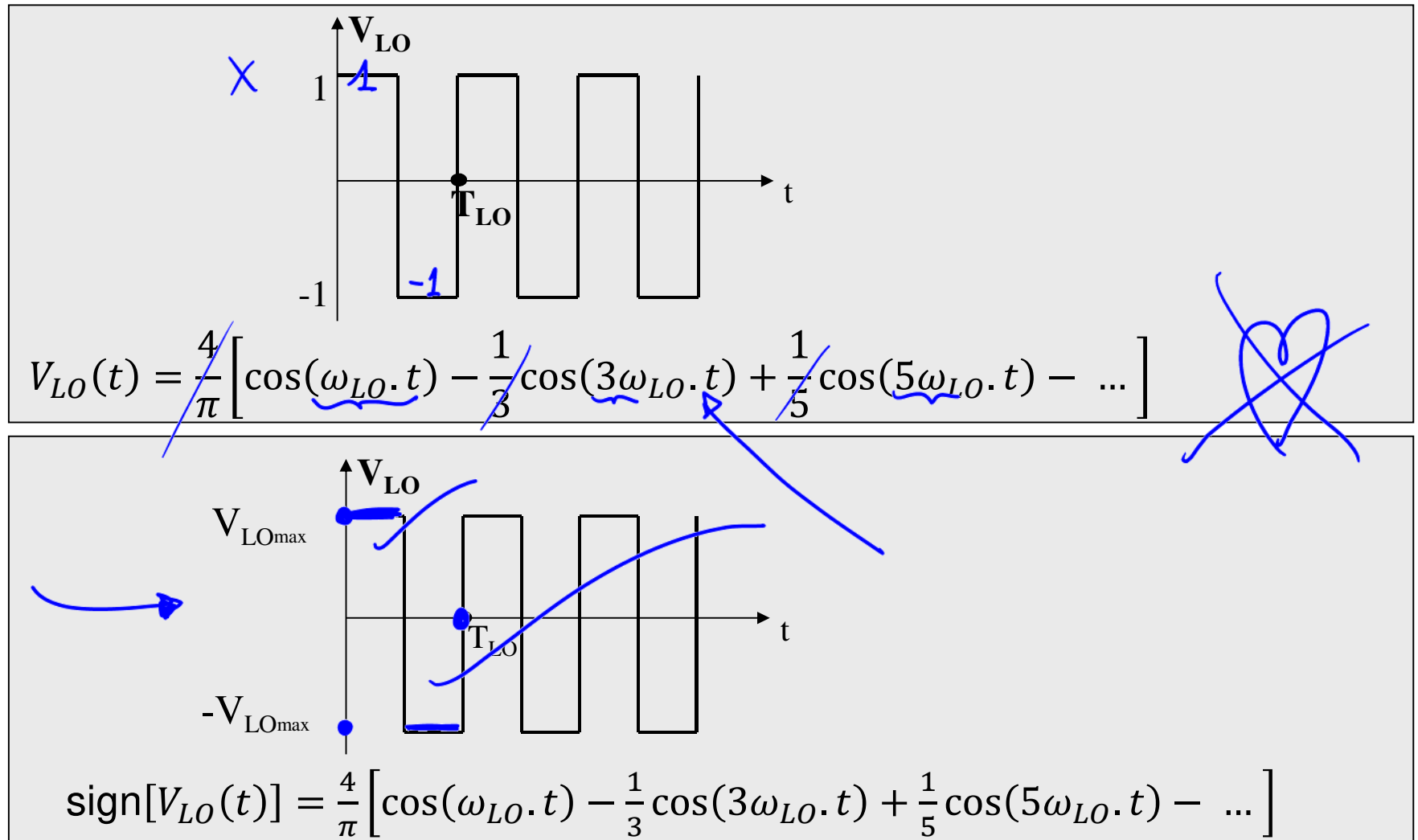Switches controlled by the LO signal along the signal path RF→IF (*Gilbert Cell*)



$V_{OUT}(t) = V_{IN}(t) \cdot \text{sign}(V_{LO}(t)) \rightarrow \text{only odd mixing products } \underbrace{(2k+1)\omega_{LO}}_{k\omega_{LO}} \pm \omega_{RF}$
 $\rightarrow \text{less spurs}$

Characteristic Performances of Mixers

Conversion Gain (example of Receiver RF \rightarrow IF)

• Voltage Conversion Gain

$$G_V = 20 \log \left(\frac{V_{out_{IF}}}{V_{in_{RF}}} \right)$$


and

Power Conversion Gain

$$G_P = 10 \log \left(\frac{P_{out_{IF}}}{P_{in_{RF}}} \right)$$

Down Conversion (Receiver)


RF \rightarrow IF

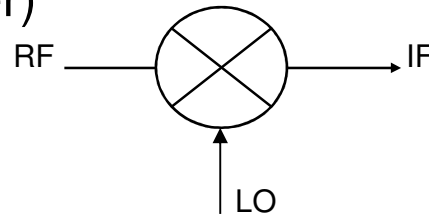


$$G_{dB_down} = P_{OUTdBm}[\omega_{IF}] - P_{INdBm}[\omega_{RF}]$$

$$L_{dB_down} = P_{INdBm}[\omega_{RF}] - P_{OUTdBm}[\omega_{IF}]$$

Example of passive down converter

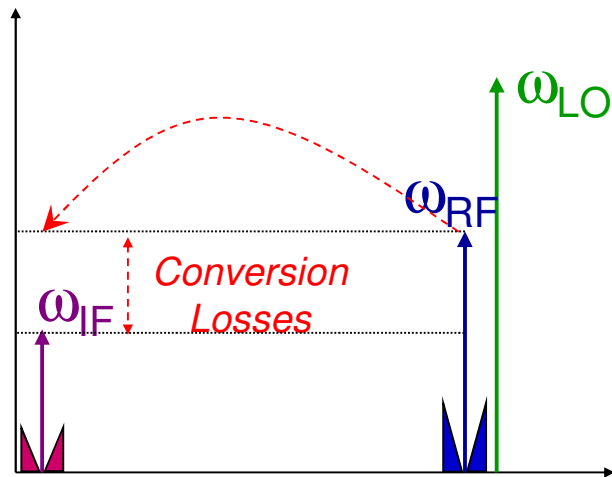


Example of active down converter

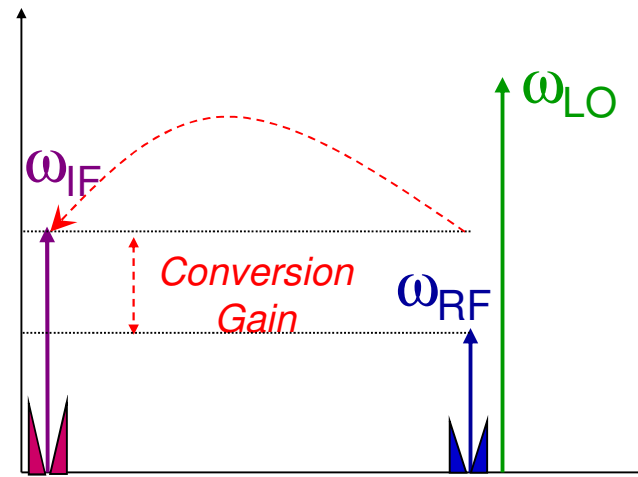



$$\text{Conversion Gain} = F(P_{LO})$$

P_{IN}
 V_{IN}

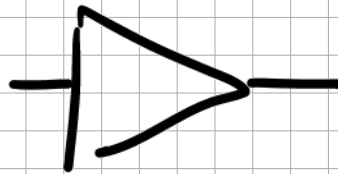

P_{OUT}
 V_{OUT}

$$G_p = \frac{P_{OUT}(f)}{P_{IN}(f)}$$

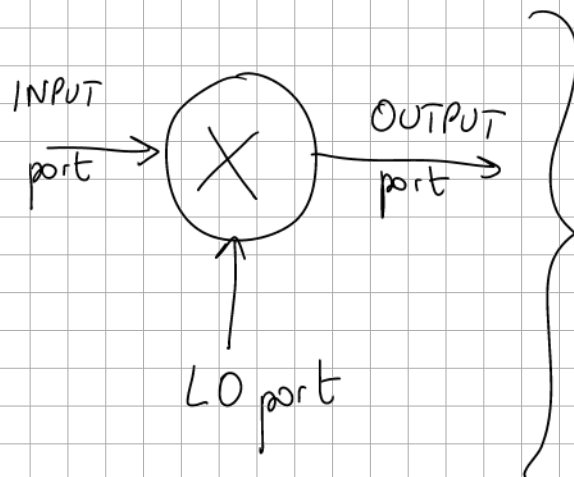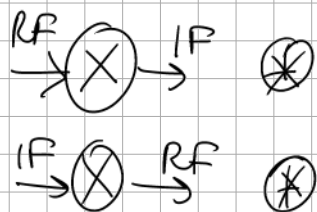

voltage conversion gain


$$G_{CV} = \frac{V_{OUTPORT}(f_{OUT})}{V_{INPUTPORT}(f_{IN})}$$

$G_p =$

LO-RF Isolation

ISOLATION = power level coupled from one port to another one within the mixer





- LO-RF Isolation :

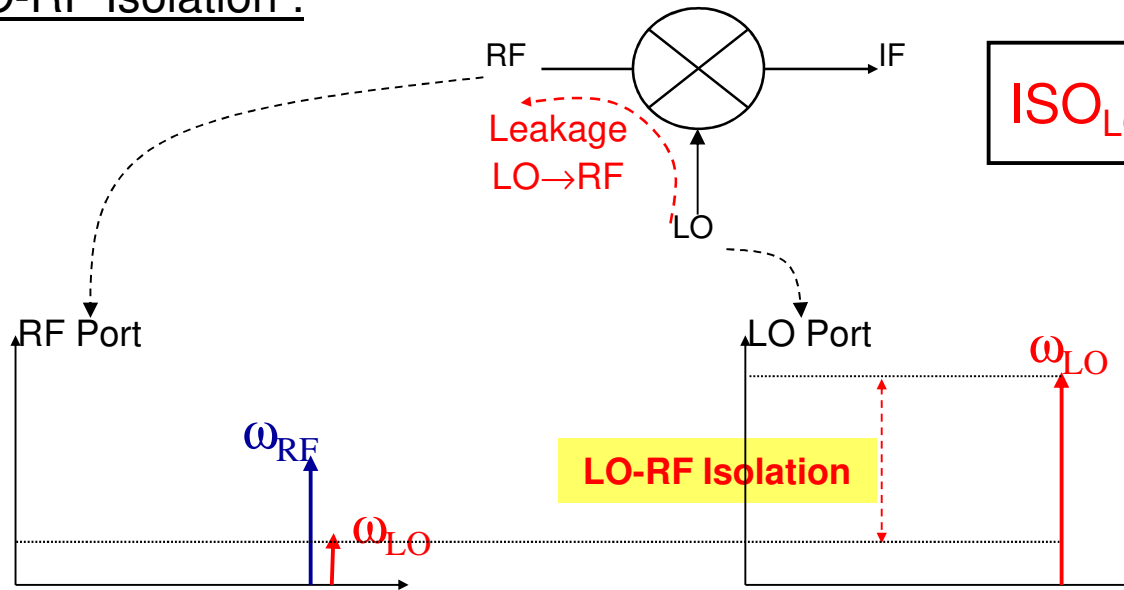

$$ISO_{\text{LO-RF}} (\text{dB}) = P_{\text{dBm}}(\omega_{\text{LO}})_{\text{LO port}} - P_{\text{dBm}}(\omega_{\text{LO}})_{\text{RF port}}$$


- Cannot be improved by filtering because RF and LO frequencies are too close
- Can be improved by Balanced Architectures
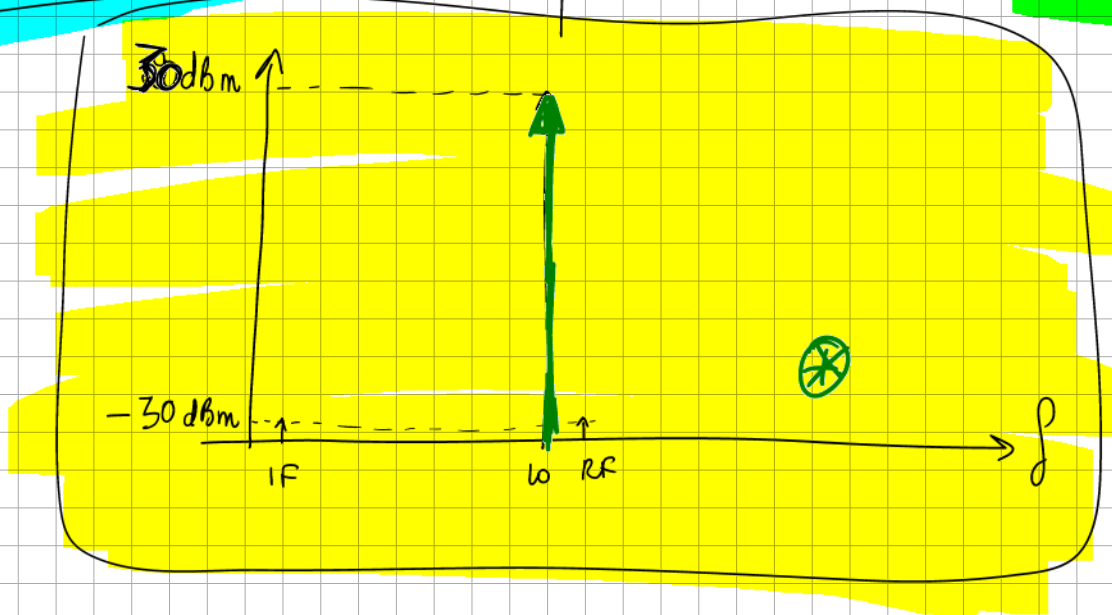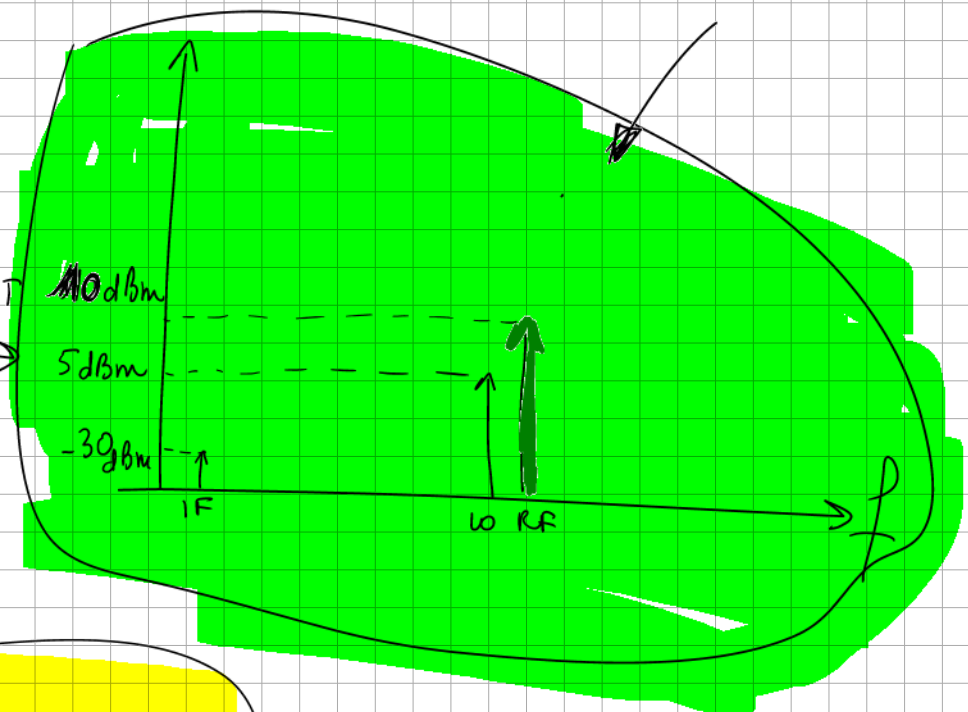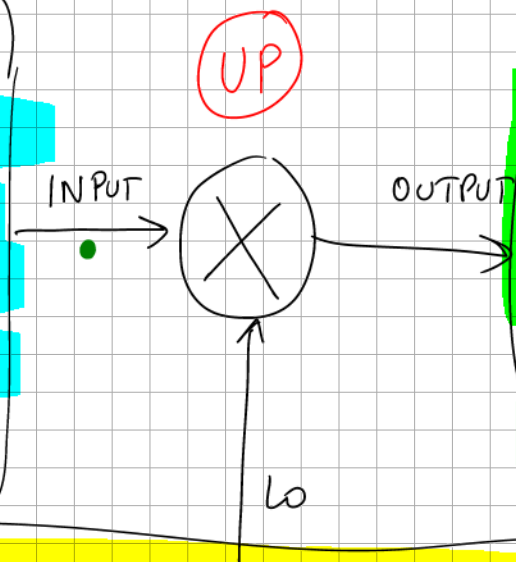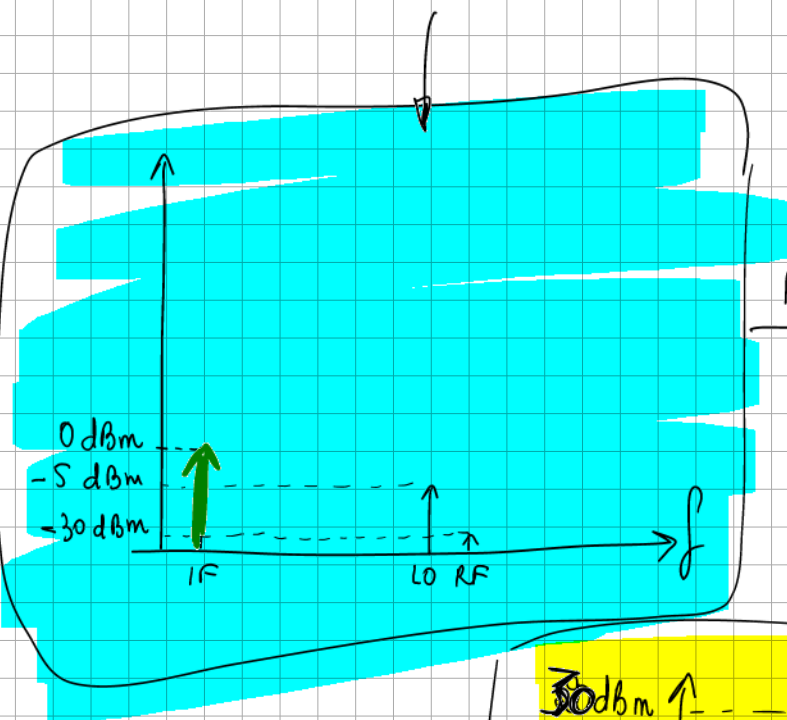
$$ISO_{\text{LO-RF}} (\text{dB}) = \text{LO leakage to the RF port (LNA, antenna)}$$





$$G_{CP, UP} = \frac{P_{OUTPUT}(W_{RF})}{P_{INPUT}(W_{IF})}$$

$$= 10 \text{ dBm} - 0 \text{ dBm}$$

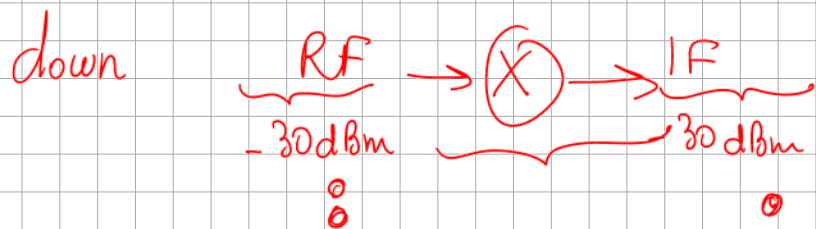

OR

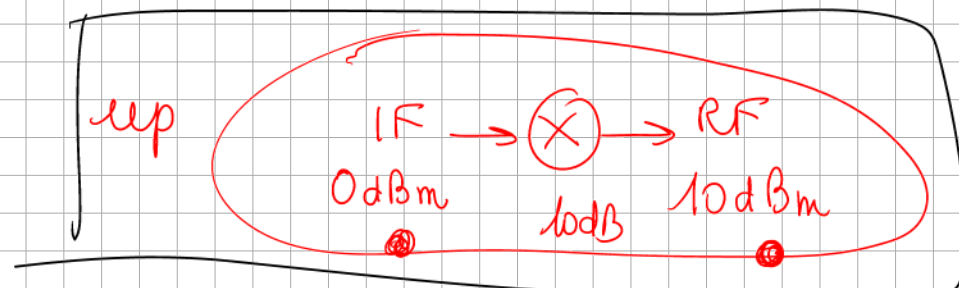

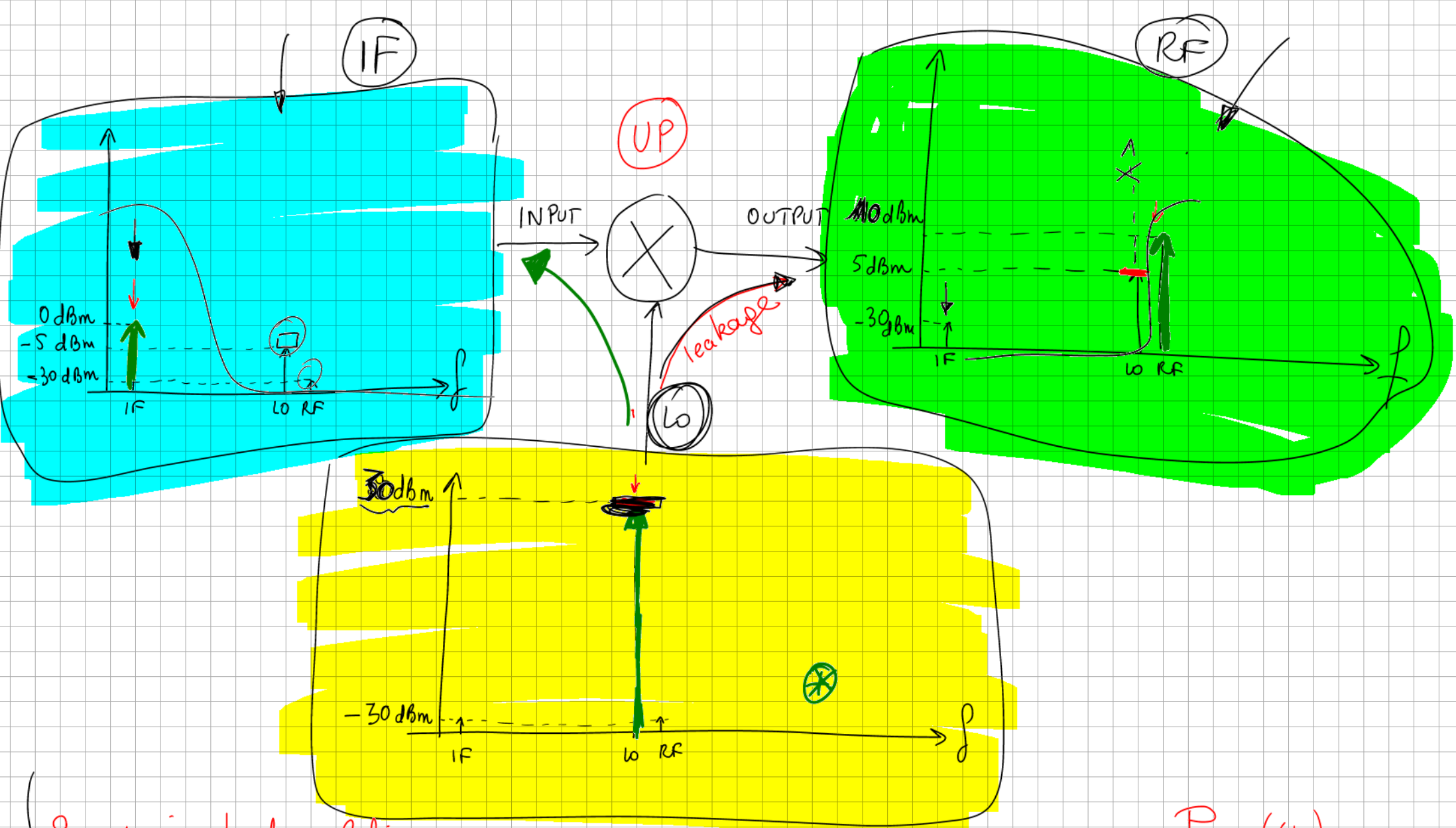

2 most important isolations are:


① LO-to-RF isolation = $ISO_{LO-RF} = \frac{P_{LO, \text{port}}(\omega_{LO})}{P_{RF, \text{port}}(\omega_{LO})} = \frac{30\text{ dBm}}{-5\text{ dBm}} = 35\text{ dB}$

② LO-to-IF isolation = $ISO_{LO-IF} = \frac{P_{LO, \text{port}}(\omega_{LO})}{P_{IF, \text{port}}(\omega_{LO})} = \frac{30\text{ dBm}}{-30\text{ dBm}} = 60\text{ dB}$

③ IF-to-RF isolation = $\frac{P_{IF, \text{port}}(\omega_{IF})}{P_{RF, \text{port}}(\omega_{IF})} = \frac{0\text{ dBm}}{-30\text{ dBm}} = 30\text{ dB}$


superheterodyne

10T

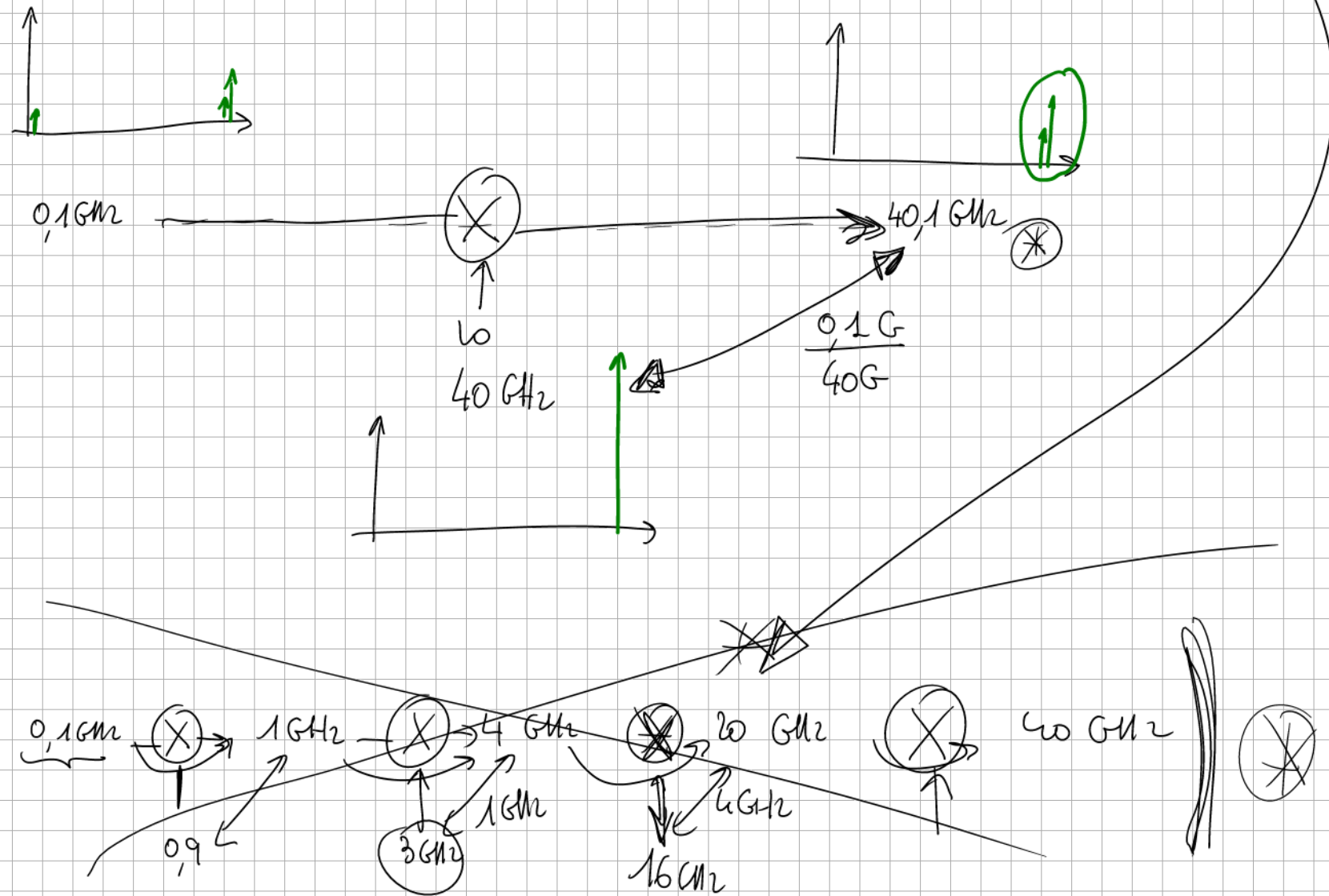

LO-IF and RF-IF Isolations

• LO-IF Isolation :

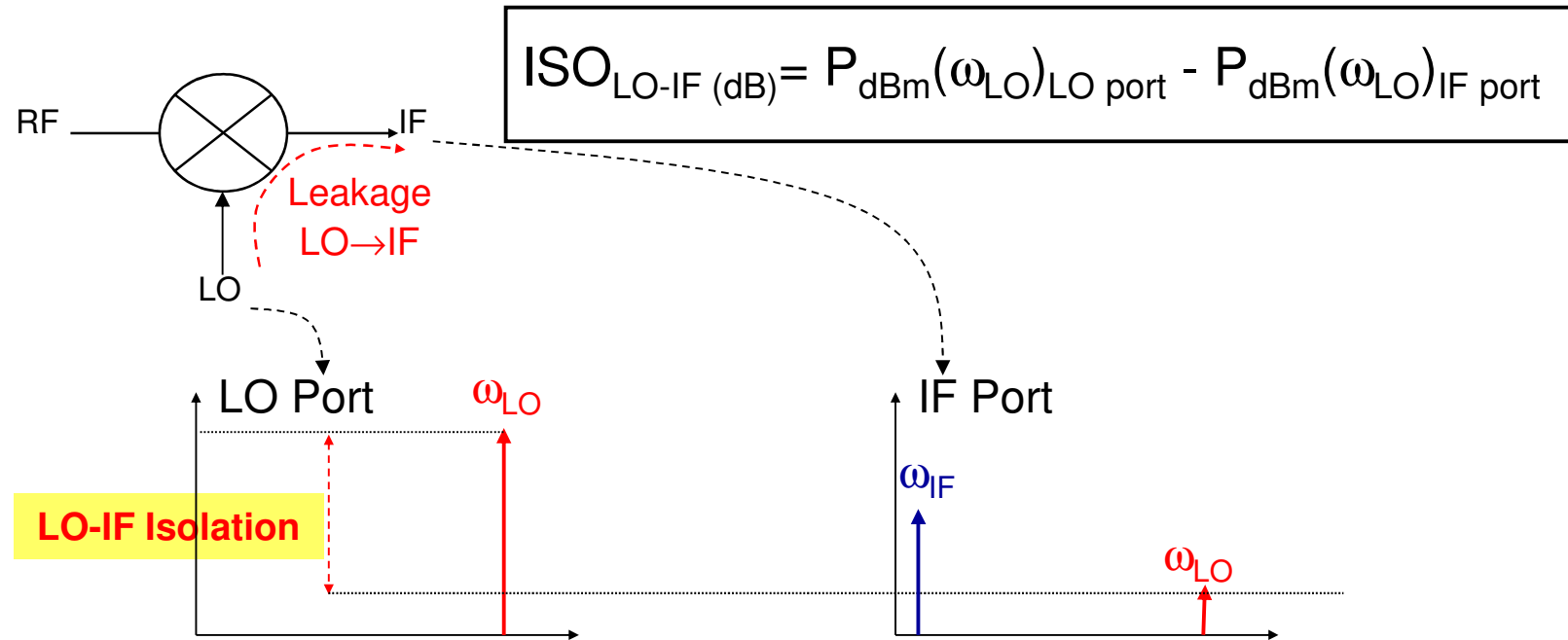

$ISO_{LO-IF} \text{ (dB)} = \text{LO leakage to the IF port}$ (saturation of following stages due to large signal)

• RF-IF and IF-RF Isolations :

$$ISO_{RF-IF} \text{ (dB)} = P_{\text{dBm}}(\omega_{RF})_{\text{RF port}} - P_{\text{dBm}}(\omega_{RF})_{\text{IF port}}$$

$$ISO_{IF-RF} \text{ (dB)} = P_{\text{dBm}}(\omega_{IF})_{\text{IF port}} - P_{\text{dBm}}(\omega_{IF})_{\text{RF port}}$$


Less critical isolations because they can be improved by filtering

Isolations

- Two critical isolations due to the very large amplitude of the LO signal:

LO- IF Isolation (less critical because filtering is easy $\omega_{LO} \gg \omega_{IF}$)

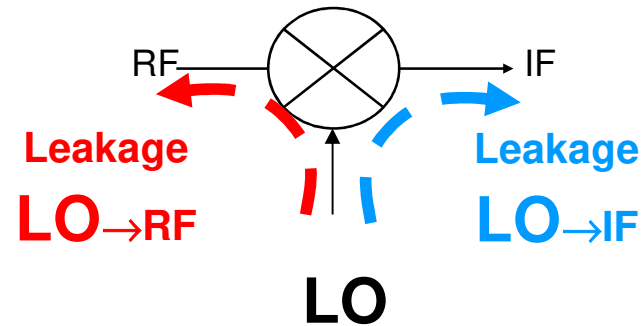and LO-RF Isolation (the most critical isolation because of impossible filtering $\omega_{LO} \approx \omega_{RF}$)





$$\text{Isolations} = F(P_{LO}, P_{IN})$$

Linearity (ex : Single carrier amplifier)

Nonlinearity $y(t) = \alpha_1 \cdot x(t) + \alpha_2 \cdot x(t)^2 - \alpha_3 \cdot x(t)^3$

$$x(t) = A \cdot \cos(\omega t) \rightarrow y(t) = \left[\frac{\alpha_2 A^2}{2} \right] + \left[\alpha_1 A - \frac{3\alpha_3 A^3}{4} \right] \cos(\omega t) + \left[\frac{\alpha_2 A^2}{2} \right] \cos(2\omega t) - \left[\frac{\alpha_3 A^3}{4} \right] \cos(3\omega t)$$
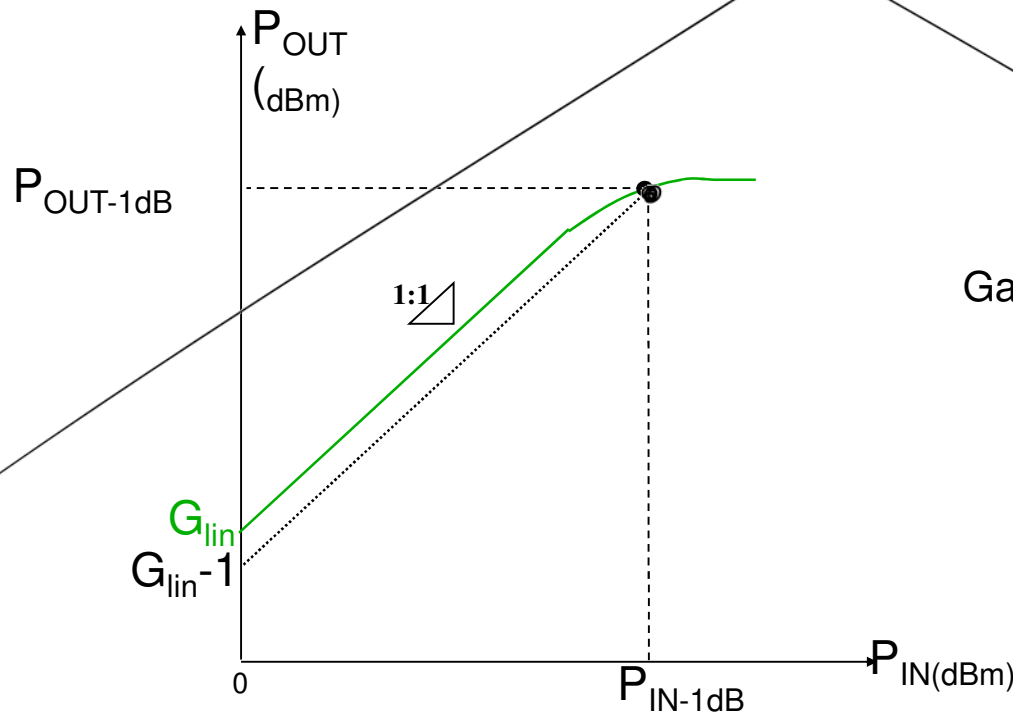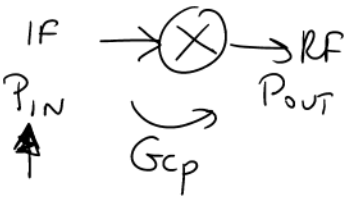
$$\rightarrow G_{\text{lin}} = \alpha_1 A$$






Example (amplifier)

Gain Saturation at the input frequency ω
with
Harmonic Generation ($n \cdot \omega$)


Gain compression of Active Mixers

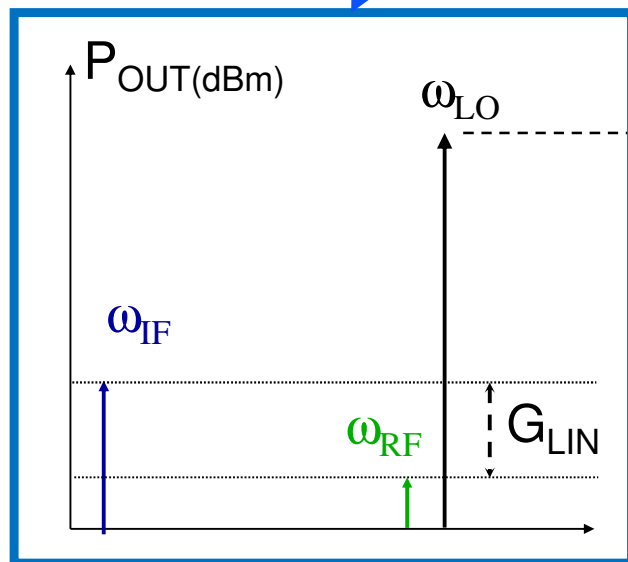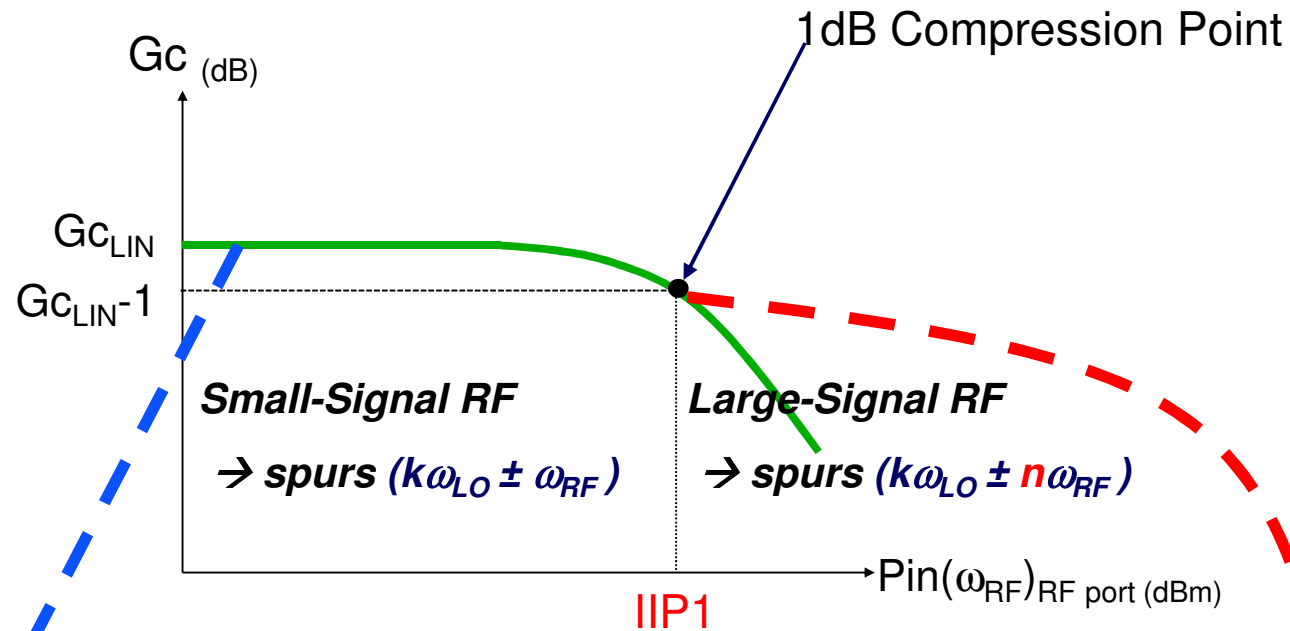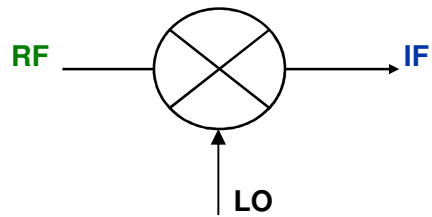- 1dB compression point at a given LO power




$P_{LO} = \text{Cst}$

$G_{LIN}, IIP1, OIP1 = f[P_{LO}]$

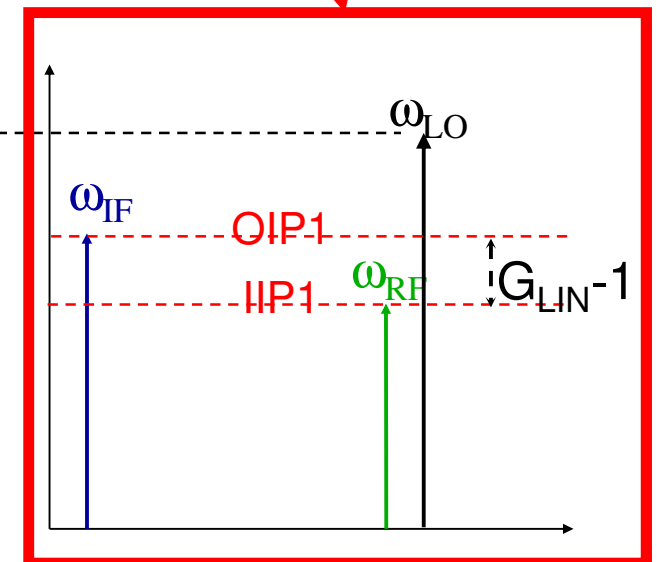


Simplified Output Spectrum

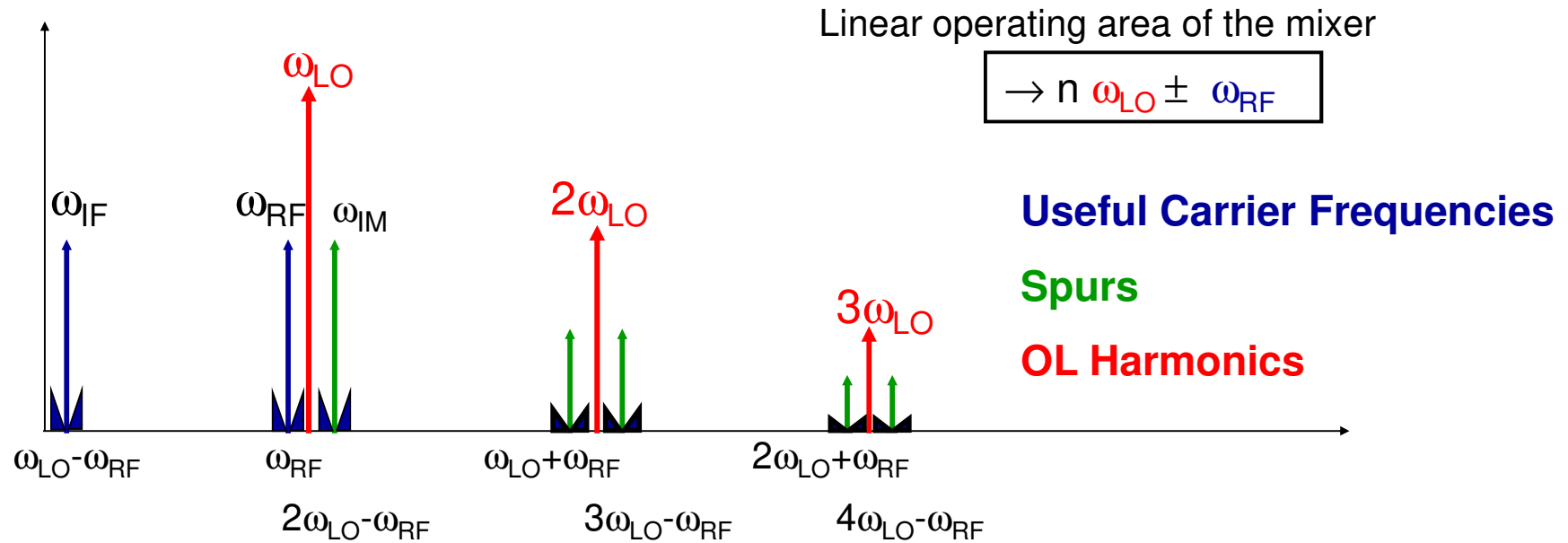


At a given level of P_{LO} ,
if P_{IN} increases \rightarrow Mixer saturation
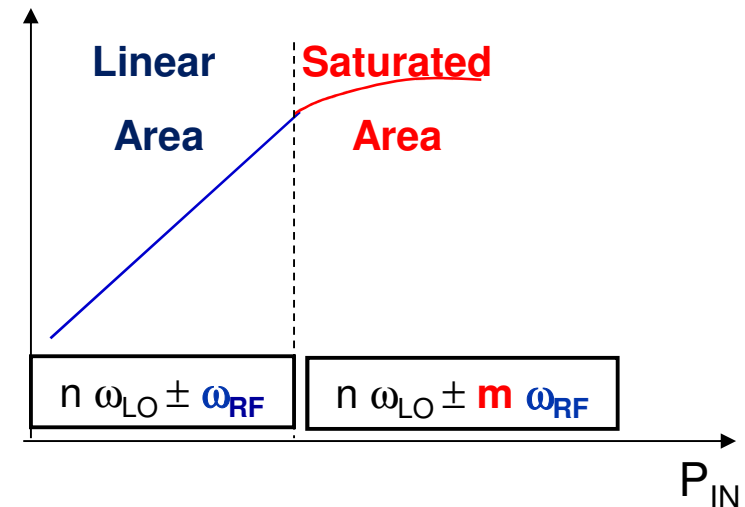
$$\rightarrow n \omega_{LO} \pm m \omega_{RF}$$



Gain Conversion as a function of P_{LO}

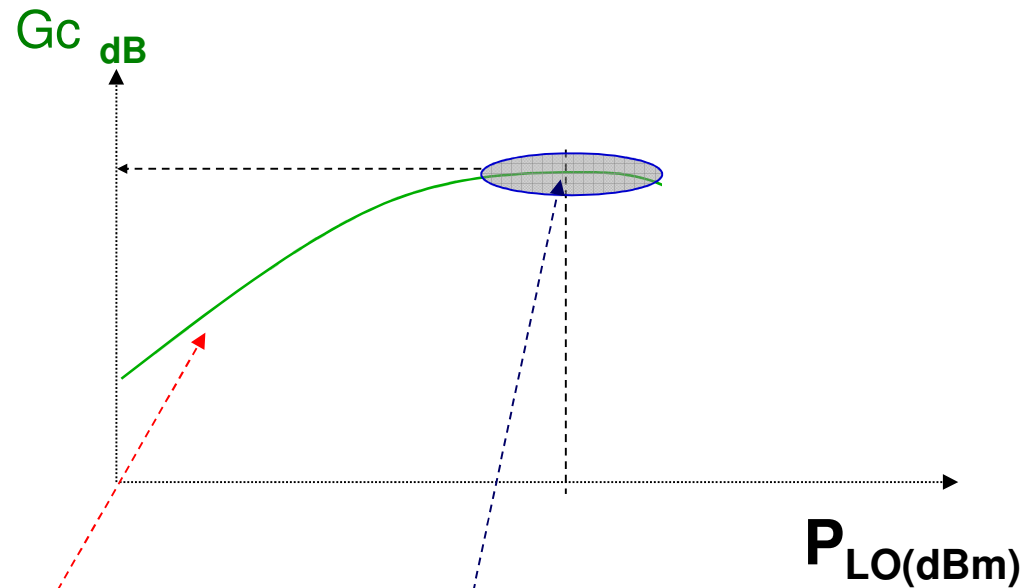

If P_{LO} is too low \rightarrow G_c varies rapidly with P_{LO} ☹️

If P_{LO} is high at its optimum value \rightarrow G_c is optimal and remains constant with P_{LO} 😊

Outline

◆ Introduction

◆ Theory of frequency conversion

◆ Characteristic performances of mixers



◆ **Active mixers**

→ Single Ended (SEM) → Gate Mixer / Drain Mixer

→ Gilbert Cell → DBDM Double Balanced Differential Mixer

◆ **Passive Mixers**

→ Diodes → SEM / SBM / DBM

→ Cold FETs → SEM / SBM

◆ **IRM: Image Reject Mixers**

Active Mixers

Active Mixers = Gain Modulation

The basic architecture of an active mixer is similar to that of an amplifier

except that the biasing conditions of the nonlinear device are chosen to get a 2nd order quadratic response

$$S_{\text{OUT}}(t) = \alpha_1 \cdot S_{\text{IN}}(t) + \alpha_2 \cdot S_{\text{IN}}(t)^2 + \alpha_3 \cdot S_{\text{IN}}(t)^3 + \dots$$

→ Active mixers can give high conversion gains

→ Active mixers require lower levels of LO power compared to passive mixers

However :

→ Active mixers saturate at very low powers

→ Active mixers require DC consumption ⊗

→ Active mixers are not well suited to IRM architectures

At high frequencies:


→ Performances of active mixers do not reach the required level → Passive mixers are preferred @ HF

◆ Active Mixers : Single Ended Mixers

FET-based SEMs


SEM → Single Ended Mixer } ← 1 NL device
SBM → " Balanced ——— } ← 2 mixers
DBM → Double balanced ——— } ← 4 mixers

FET-based SEM (Gate Mixer)

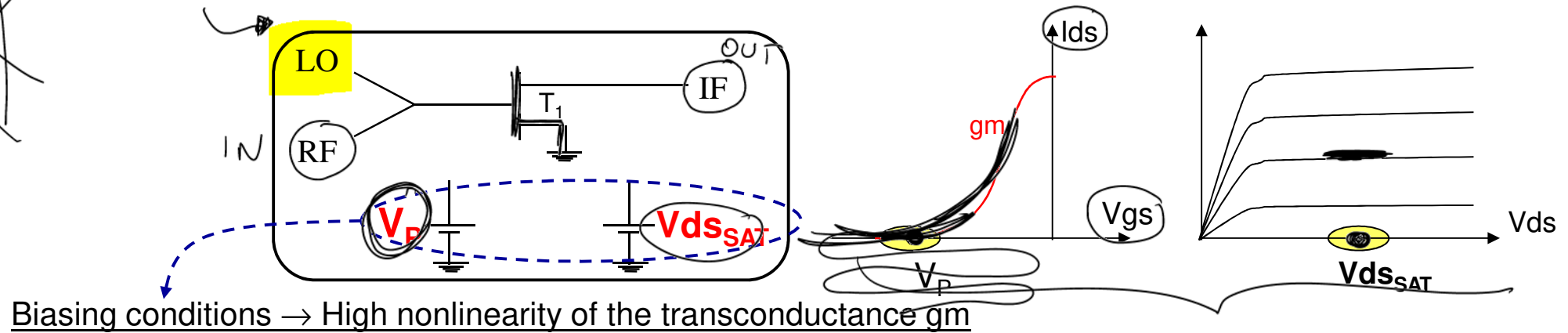

$$* g_m(t) = g_{m0} + g_{m1} \cdot \cos(\omega_{LO} t) + g_{m2} \cdot \cos(2\omega_{LO} t) + \dots$$

FET-based SEM (Drain Mixer)

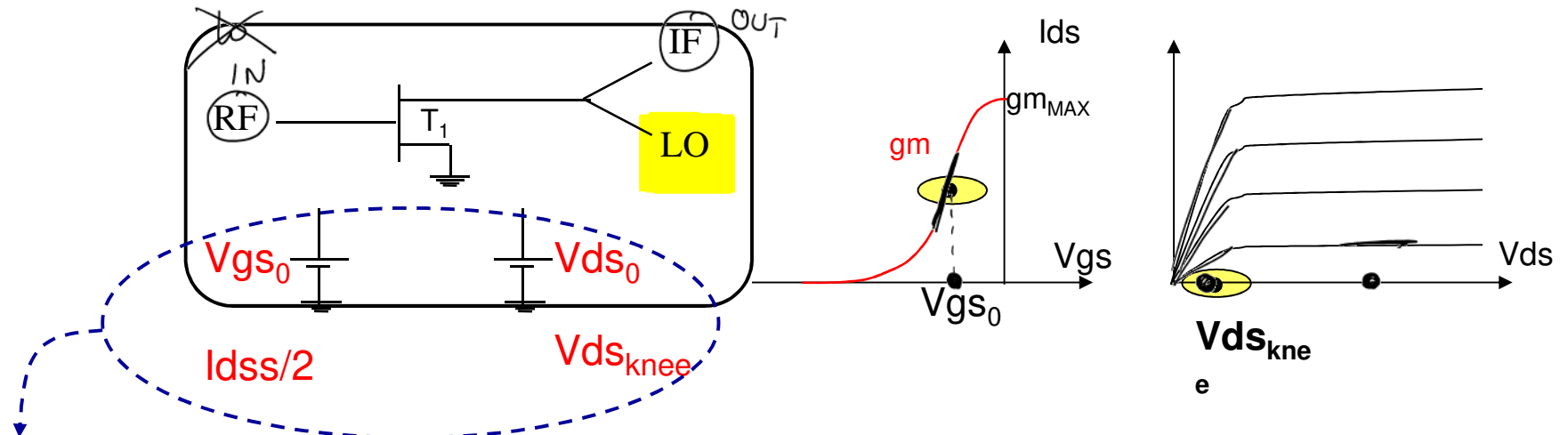


$$R_{os} \begin{cases} g_m(t) = g_{m0} + g_{m1} \cdot \cos(\omega_{LO} \cdot t) + g_{m2} \cdot \cos(2\omega_{LO} \cdot t) + \dots \\ G_d(t) = G_{d0} + G_{d1} \cdot \cos(\omega_{LO} \cdot t) + G_{d2} \cdot \cos(2\omega_{LO} \cdot t) * \dots \end{cases}$$

**Lower Conversion Gain
compared to the Gate Mixer**


◆ Active Balanced Mixers

Reminder : Coupler


Coupler

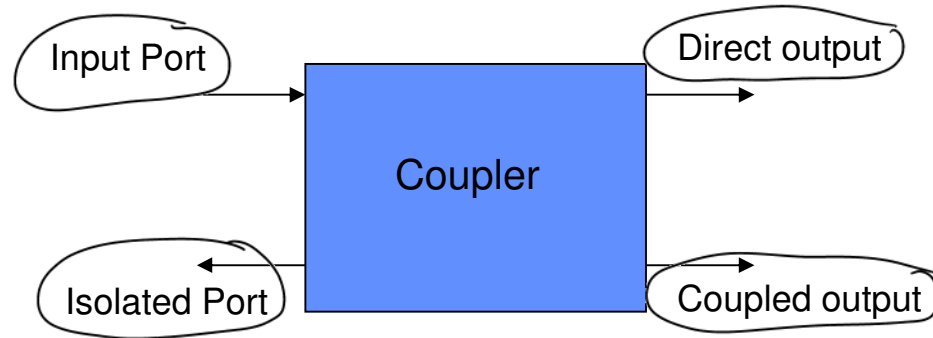

$\Sigma\Delta$ Coupler

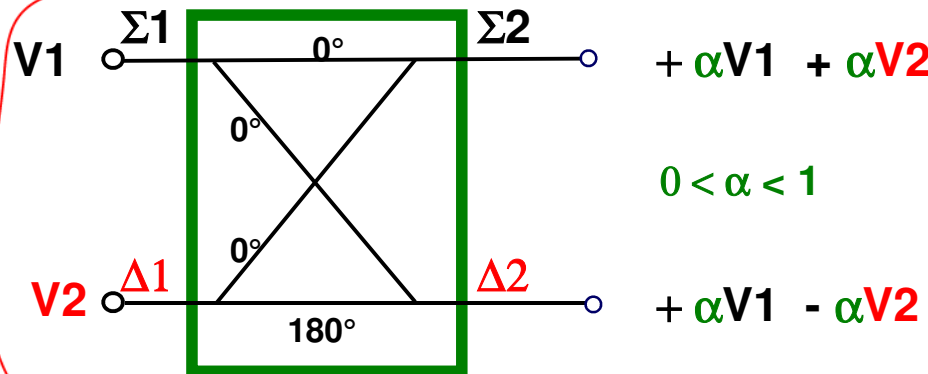



90° Coupler

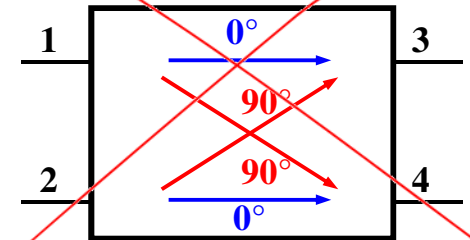

BALUN

BALanced to UNbalanced

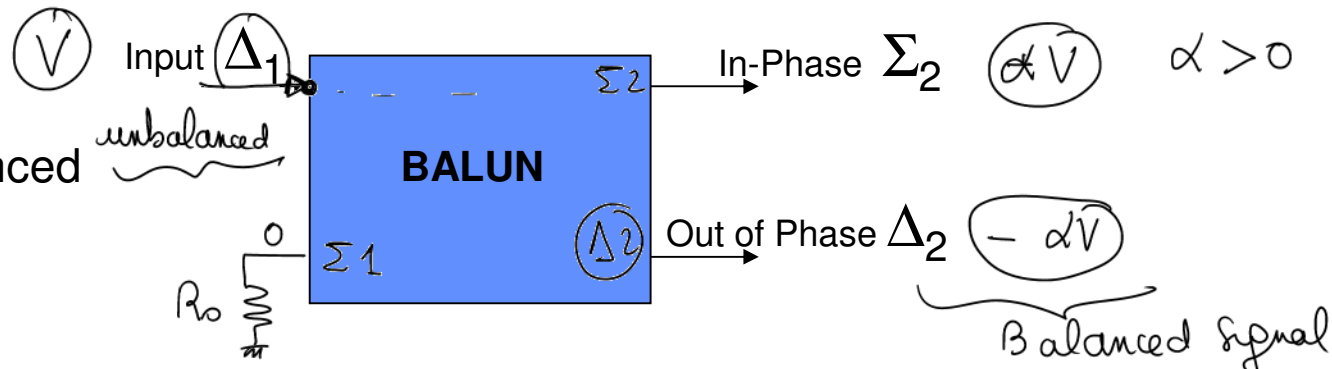

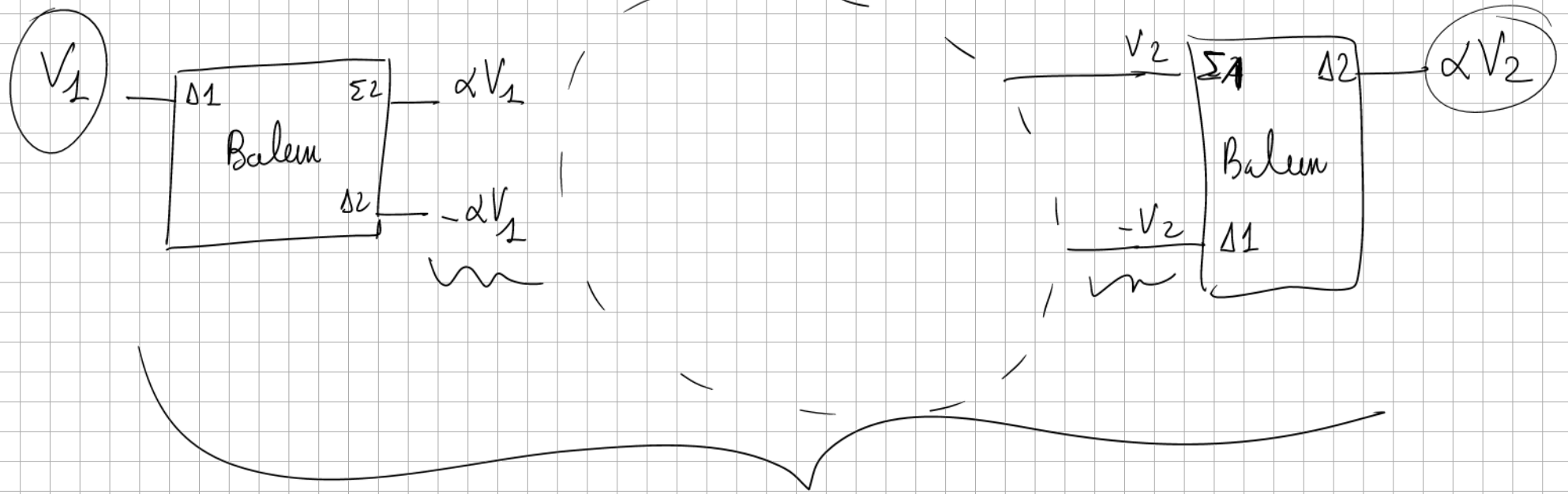

Phase relationships of frequency products

$$2 \times \underbrace{\cos(\omega_{LO}t + \phi_{LO})}_{\text{LO}} \times \underbrace{\cos(\omega_{RF}t + \phi_{RF})}_{\text{RF}} = \underbrace{\cos[(\omega_{LO} + \omega_{RF})t + (\phi_{LO} + \phi_{RF})]}_{\text{LO+RF}} + \underbrace{\cos[(\omega_{LO} - \omega_{RF})t + (\phi_{LO} - \phi_{RF})]}_{\text{LO-RF}}$$

$$(\omega_{LO} + \omega_{RF}) \rightarrow (\phi_{LO} + \phi_{RF})$$

$$(\omega_{LO} - \omega_{RF}) \rightarrow (\phi_{LO} - \phi_{RF})$$

RF \rightarrow \otimes \rightarrow IF

If $\omega_{IF} = \omega_{LO} - \omega_{RF} \rightarrow \phi_{IF} = (\phi_{LO} - \phi_{RF})$

LSB

$$f_{IF} = f_{LO} - f_{RF} \longrightarrow \phi_{IF} =$$


RF \rightarrow IF

SBM Active Mixers

$$f_{IF} = f_{LO} - f_{RF} \rightarrow \phi_{IF} = \phi_{LO} - \phi_{RF}$$

$$\omega_{IF} = \omega_{LO} - \omega_{RF} \rightarrow \text{Phase(IF)} = \text{Phase(OL)} - \text{Phase(RF)}$$

SBM with 180° Couplers

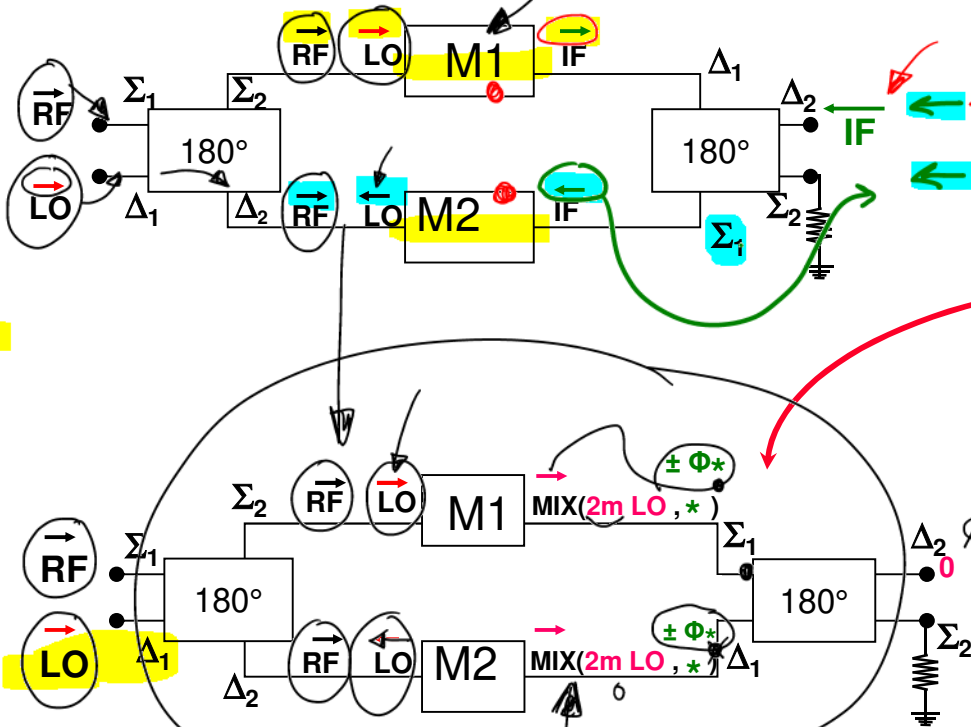

Notations

EH = Even Harmonic

OH = Odd Harmonic

Mix [EH(LO), OH(RF)] = $\pm 2m \omega_{LO} \pm 2(n+1) \omega_{RF}$ with (m,n) integers

• Good LO-RF isolation \Leftrightarrow Good Input Coupler isolation

• In all cases, mix [EH(LO), OH(RF)] are rejected at the output

• LO at Δ port (the illustrated case in this slide)

\rightarrow mix [EH(LO), *] are rejected at the output
 $\pm 2m \omega_{LO} \pm p \omega_{RF}$

• LO at Σ port

\rightarrow mix [*, OH(RF)] are rejected

$\phi_* \Leftrightarrow \phi_* + 180^\circ \Rightarrow 0$
 $\pm p \omega_{OL} \pm (2k+1) \omega_{RF}$ rejected

if $2m=0$
 $p \omega_{RF}$ rejected
 $180^\circ_{RF-IF} = \infty$

① LO - RF $180^\circ = \text{LO-RF}_{180^\circ}$ of coupler

② LO - IF 180°

③ RF - IF $180^\circ = \infty$



$$2m \omega_{LO} (\pm \omega_*)$$

$$2m \phi_{LO} \pm \phi$$

RF \rightarrow IF



Example of Gilbert Cell Mixers

Single Balanced Gilbert Cell Mixer

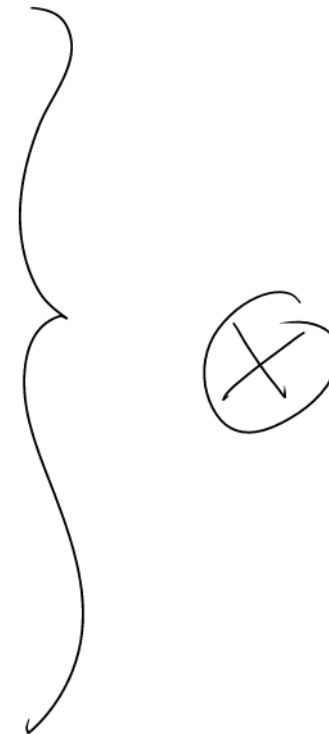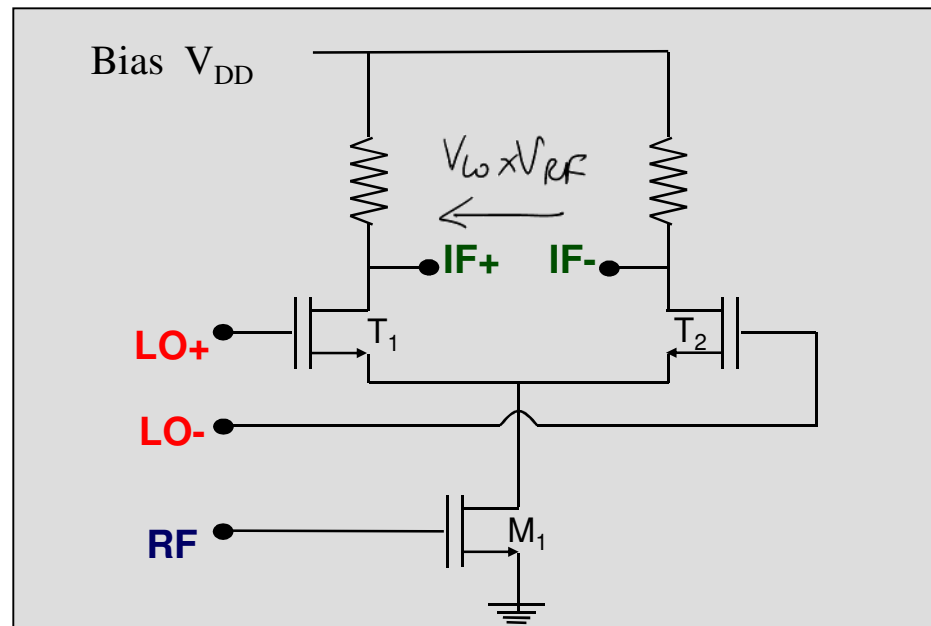


◆ Double Balanced Gilbert Cell Mixer

Double Balanced Gilbert Cell Mixer

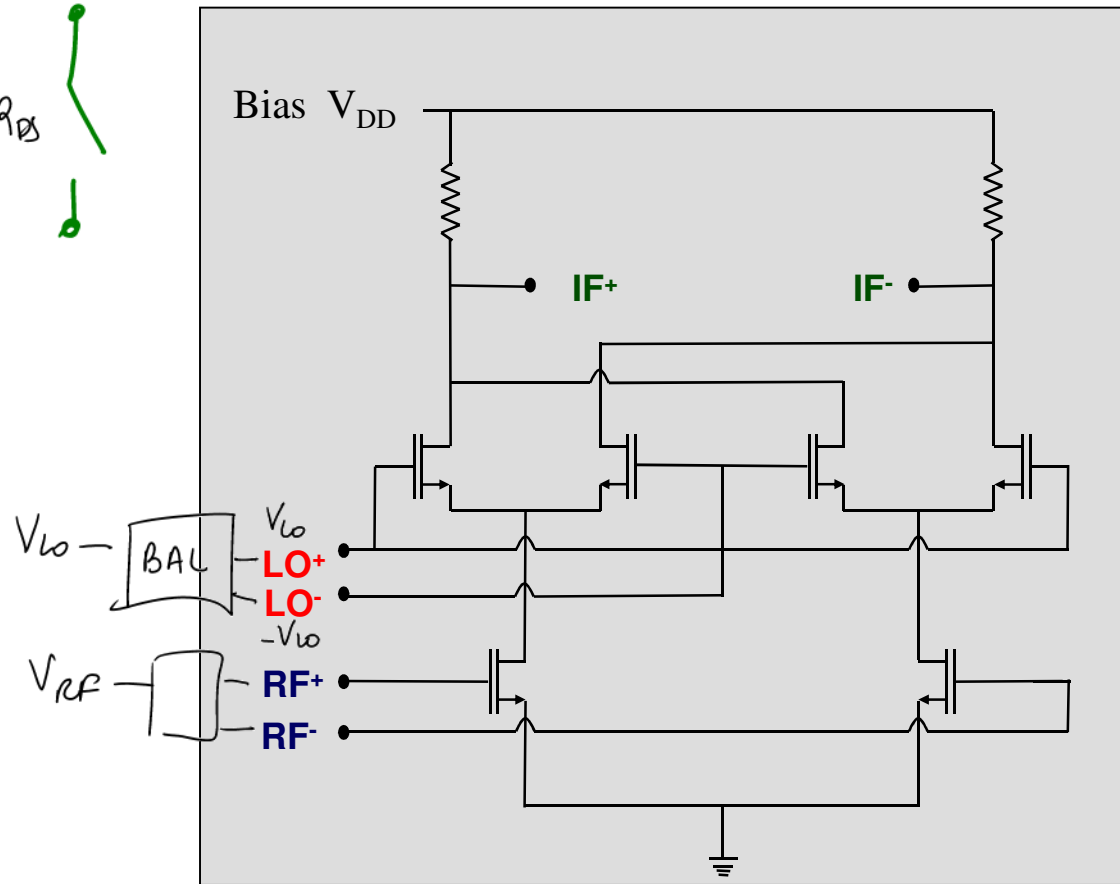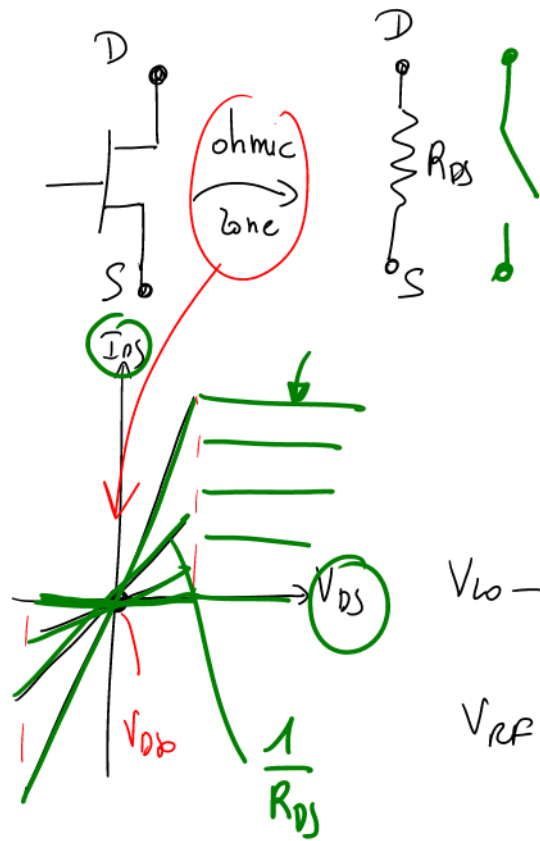

switches

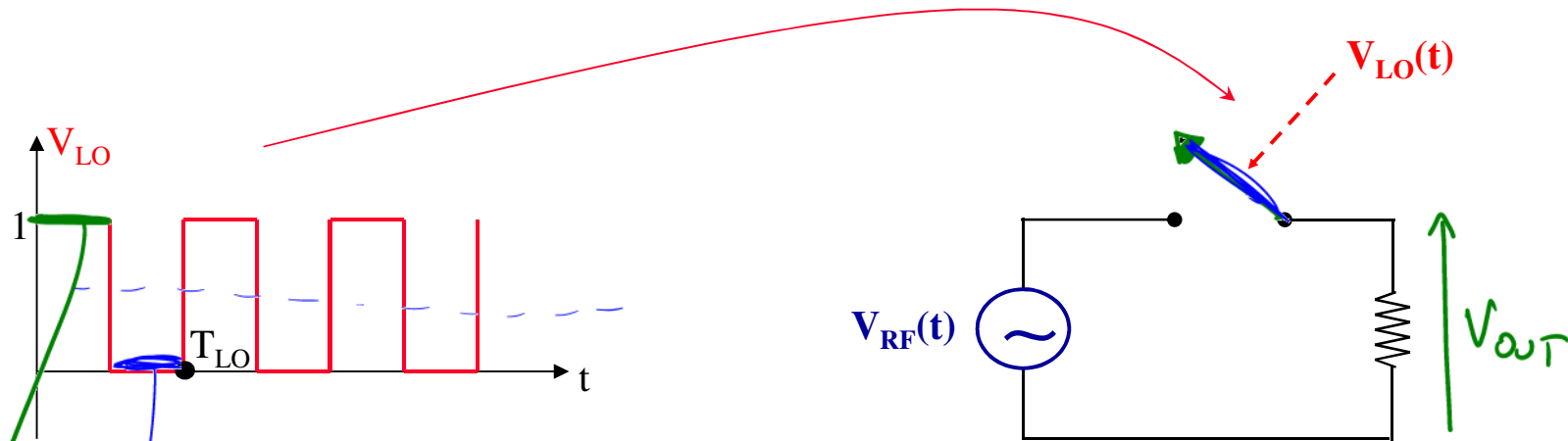Switch controlled by the LO signal Square Signal (50% duty cycle)



The linear signal path RF→IF is open and closed by a switch controlled at the LO rate

→ The output signal results from the multiplication of the RF signal by the square LO signal


→ Unfortunately, the output signal includes a parasitic RF component due to the DC component of the LO signal

$$V_{OUT} = V_{RF}$$



$$V_{OUT} = 0$$

DC component

$$V_{OUT} = V_{RF} \times V_{LO}$$

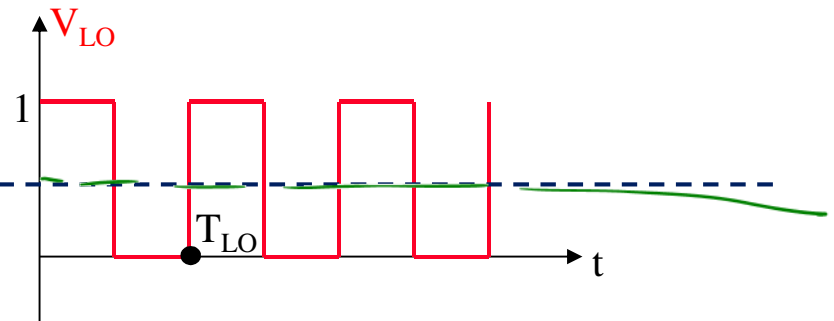

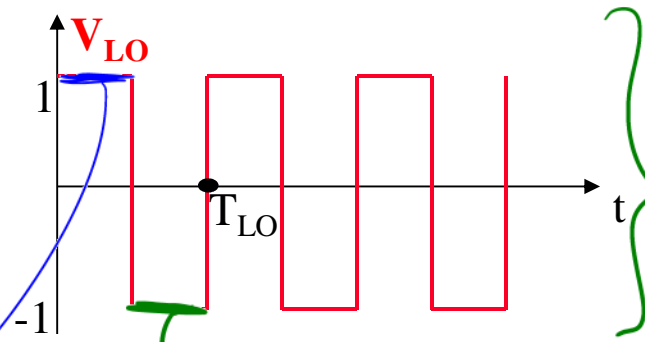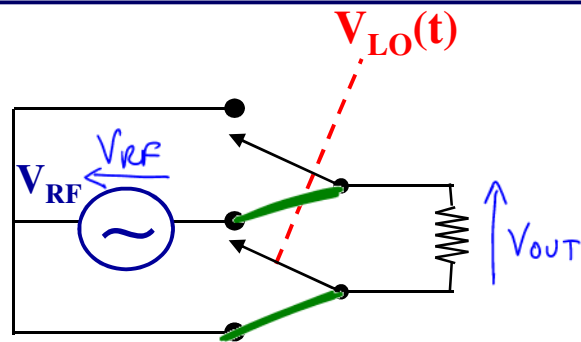Switch controlled by the LO signal with the suppression of its DC component



$$\text{sign}[V_{LO}(t)] = \frac{4}{\pi} \left[\cos(\omega_{LO} \cdot t) - \frac{1}{3} \cos(3\omega_{LO} \cdot t) + \frac{1}{5} \cos(5\omega_{LO} \cdot t) - \dots \right]$$

$$V_{OUT} = V_{RF}$$

$$V_{OUT} = -V_{RF}$$

$$V_{OUT} = V_{RF} \times \begin{matrix} +1 \\ -1 \end{matrix} \text{sign}(V_{LO})$$

\downarrow
 $(2k+1)\omega_{LO}$


The sign of the RF signal is periodically changed at the LO rate instead of being cut

→ There is no DC component and the RF signal is fully rejected at the output

→ The RF signal is fully transposed at the IF frequency


$$(2k+1)\omega_{LO} \pm \omega_{RF}$$

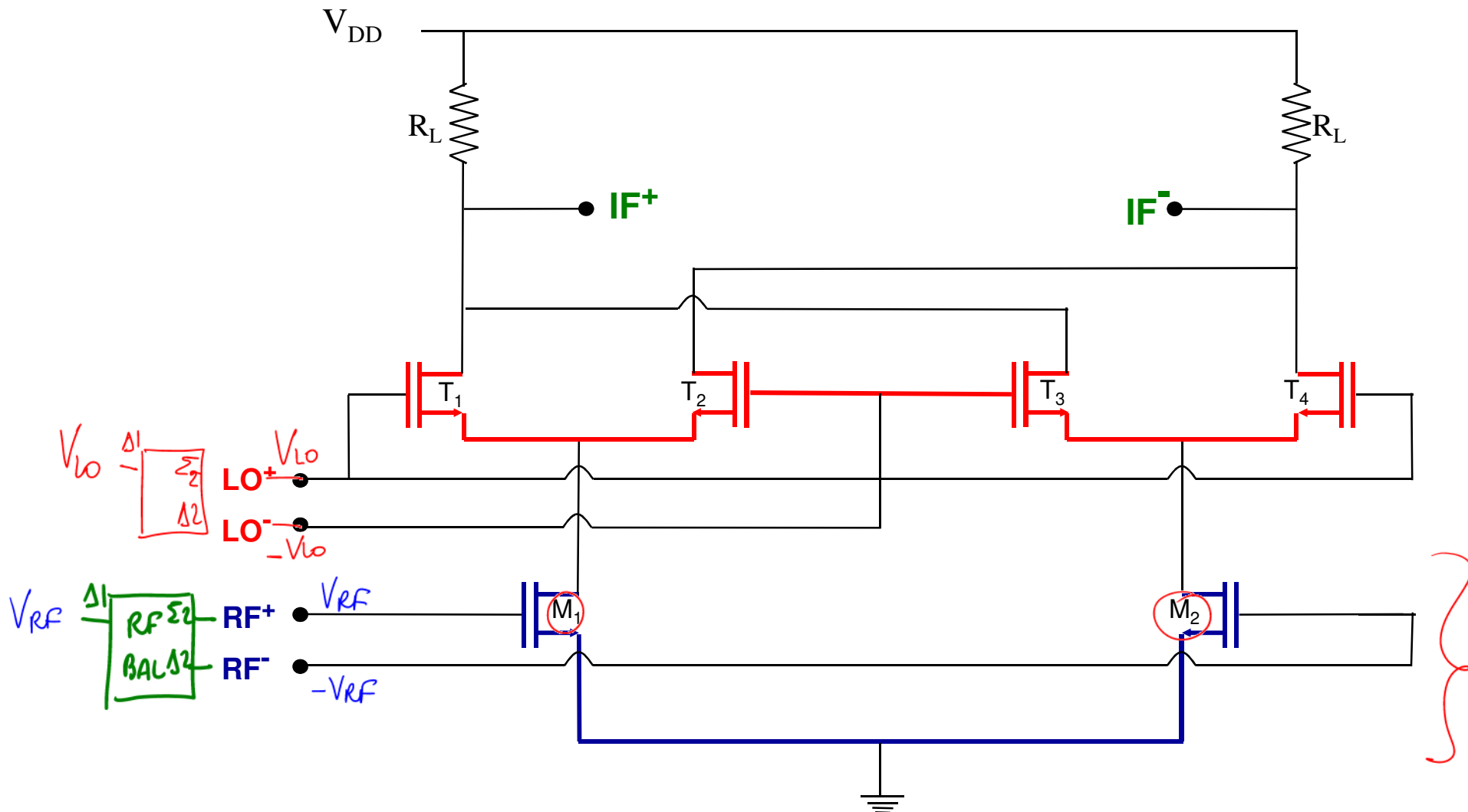Double Balanced Active Gilbert Cell Mixer




- **The differential RF pair** gives gain and the RF-IF path must be as linear as possible
- **The 2 LO pairs** work as switches to perform the frequency conversion

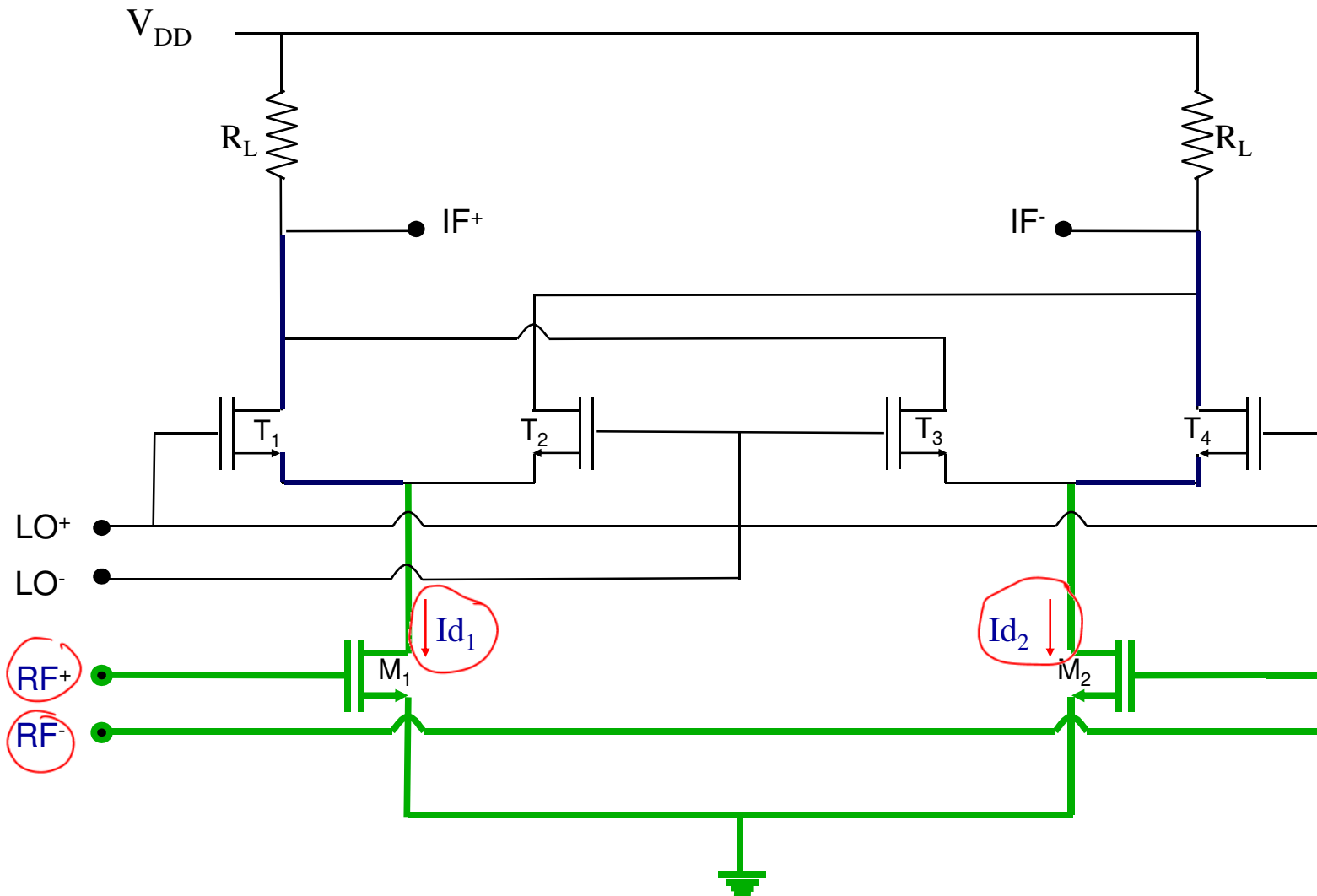Differential RF pair : Voltage-Current conversion




The differential RF pair gives the conversion gain through the drain current I_d (V_{gs})

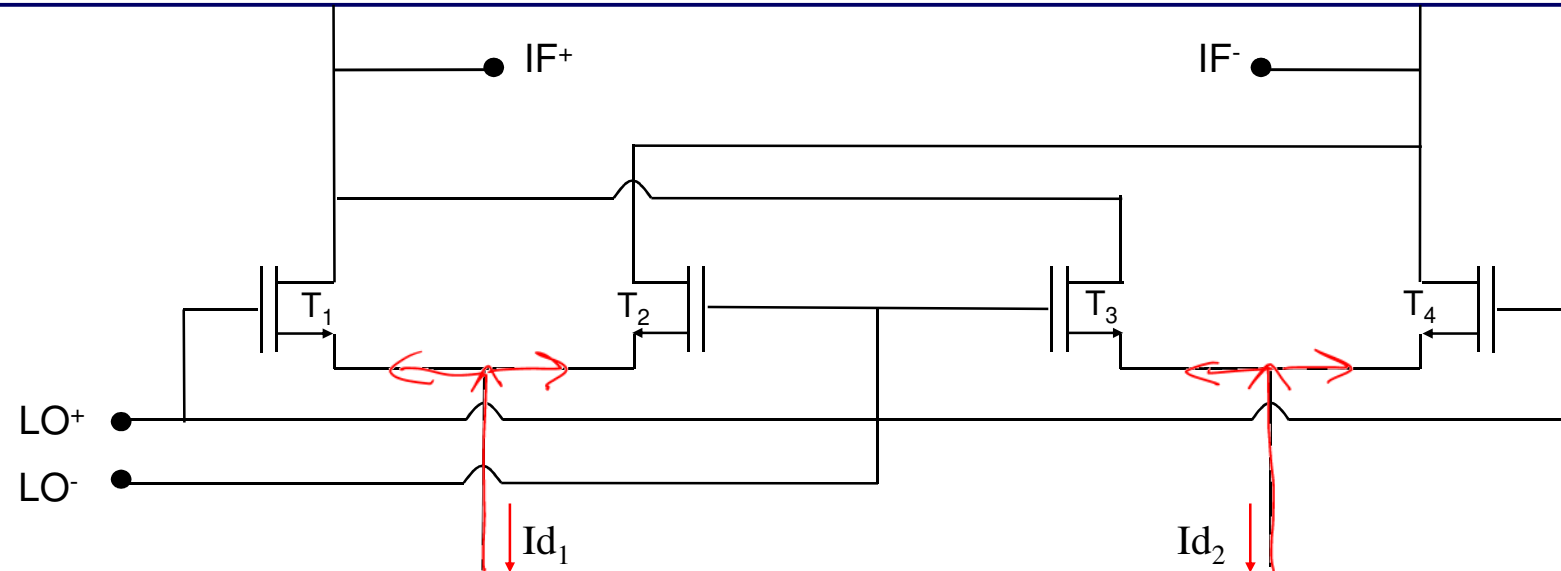Differential LO pairs operate as switches : Mixing Core




- Id_1 and Id_2 currents of the RF pair are flowing towards the two LO pairs controlled by the outphased LO signals
- The 2 LO pairs operate as switches \Leftrightarrow Requirement of a large LO power to allow an efficient ON/OFF operation

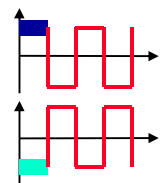
LO pair : Switching
1st Positive Alternation $[0 - T_{LO}/2]$



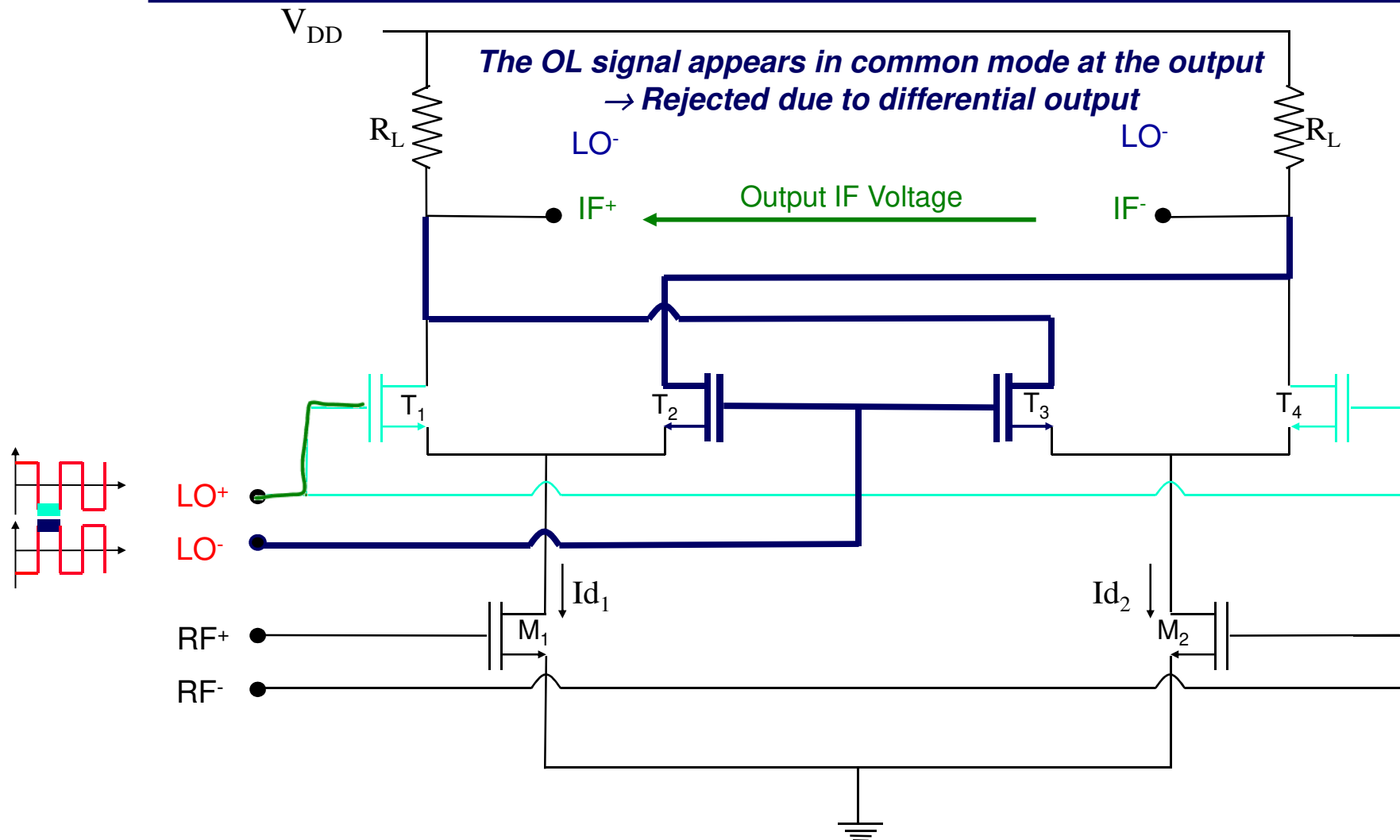LO pair : Switching 2nd Negative Alternation [$T_{LO}/2 - T_{LO}$]




Operating mode of the Gilbert DBM

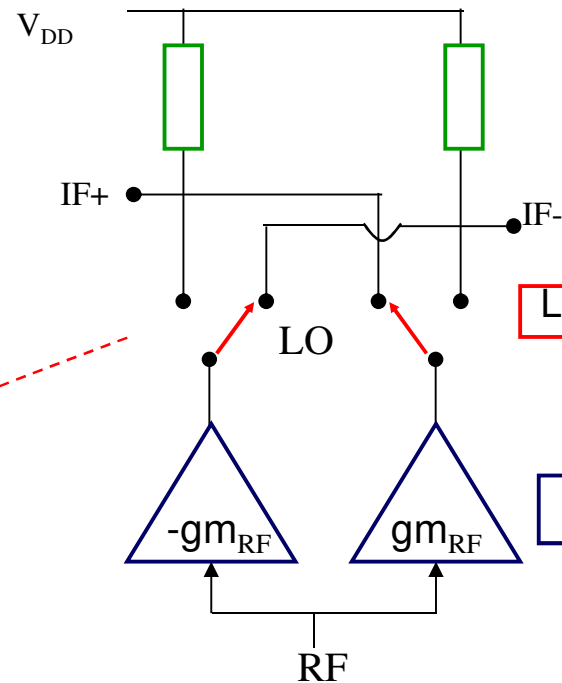

LO stage « switching - mixing »

RF stage « Linear Conversion $V \rightarrow I$ »

LO switching

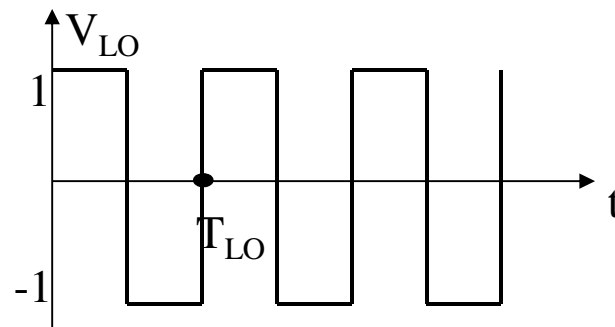


• No generation of even LO Harmonics

$$\text{sign}[V_{LO}(t)] = \frac{4}{\pi} \left[\cos(\omega_{LO} \cdot t) - \frac{1}{3} \cos(3\omega_{LO} \cdot t) + \frac{1}{5} \cos(5\omega_{LO} \cdot t) - \dots \right]$$


Example of two DBM (Active and Passive):
Active DBM mixer (Gilbert Cell) / Passive DBM mixer (Ring mixer of cold FETs)

Double Balanced Mixer « Gilbert Cell »

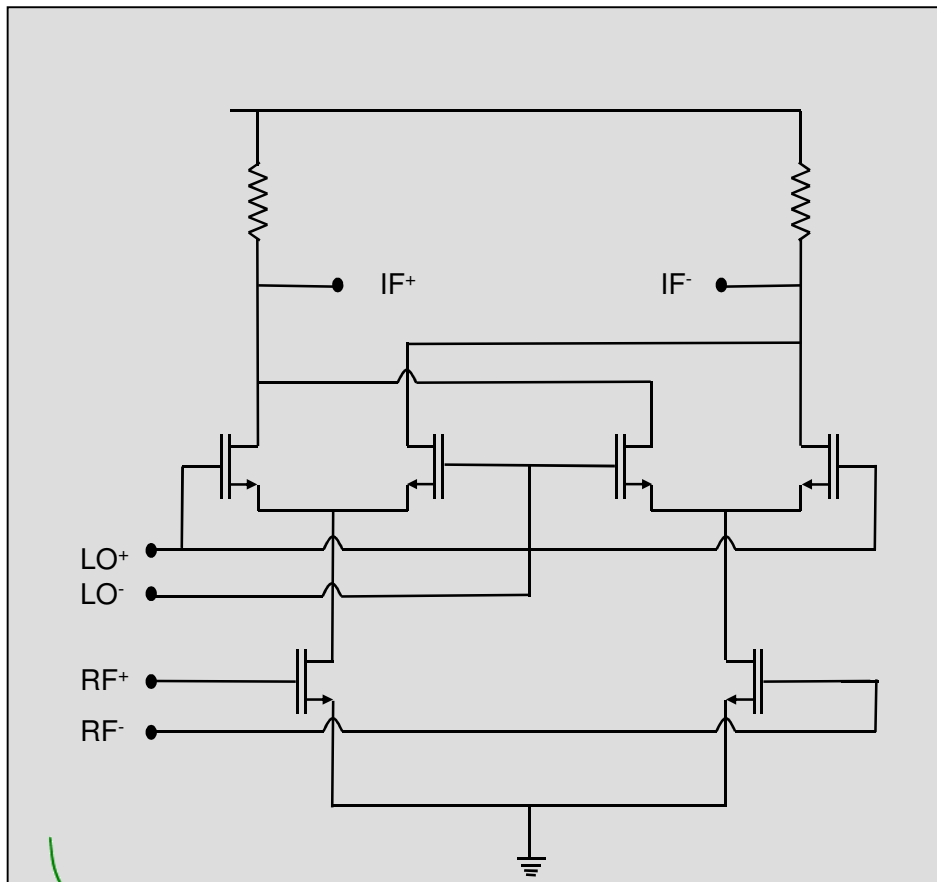

~~LF~~

« Passive ring mixer »

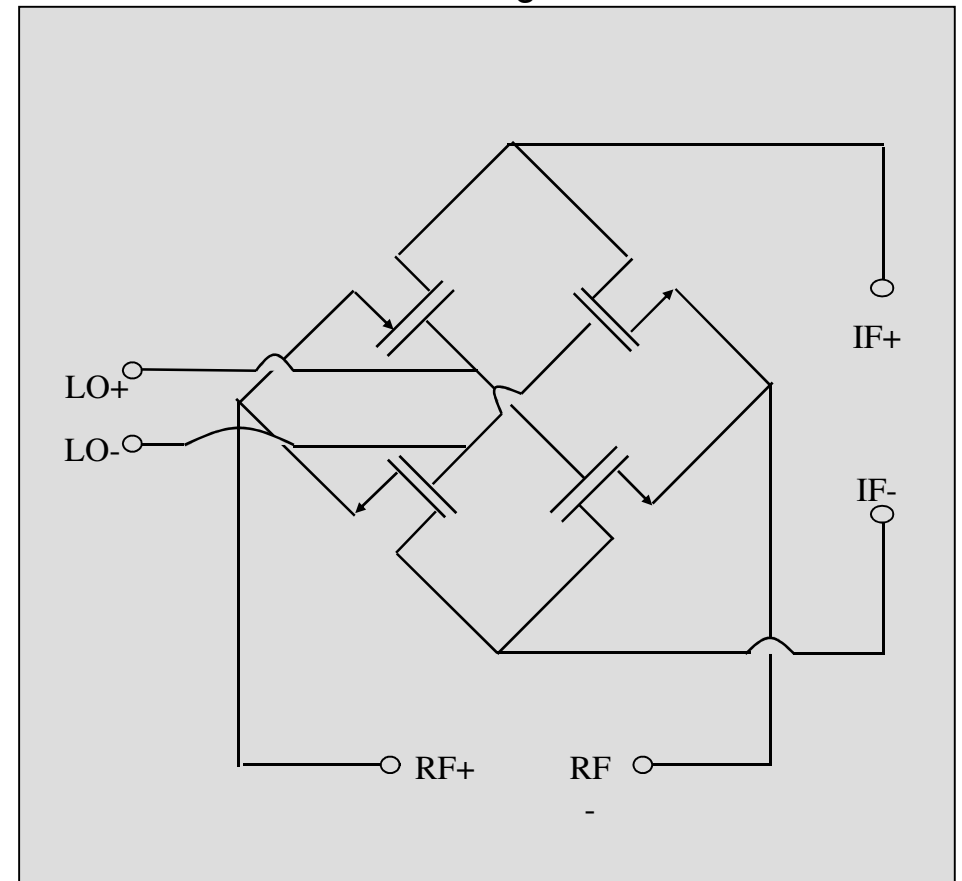

⊗