
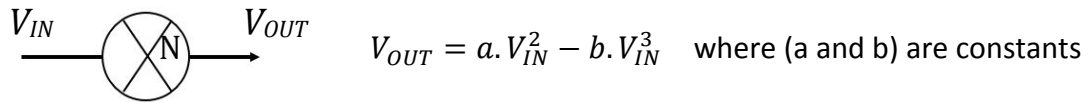


Tutorial (Balanced Mixer SBM)

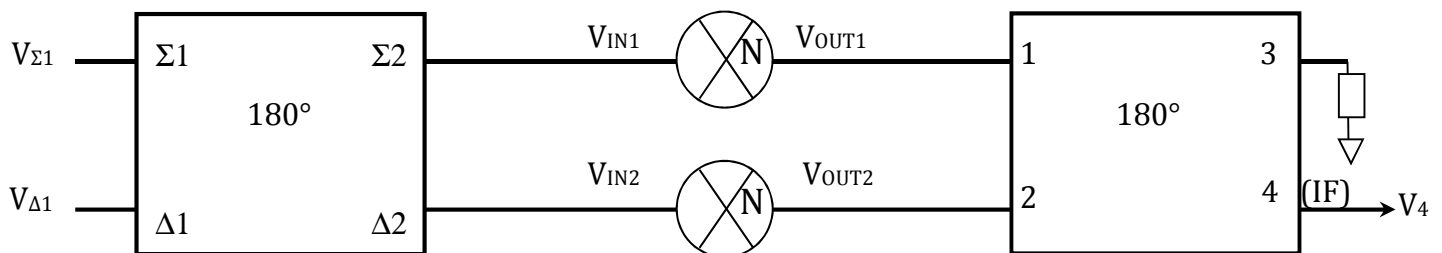- The mixer is based on a **nonlinear device N** characterized with the following 3rd order transfer function :



- The following block diagram represents a **single balanced mixer SBM** consisting of two 180° -couplers and two identical mixers N.



- 1) In the studied case, the input voltages are $V_{\Sigma 1} = (\sqrt{2} \cdot V_{RF})$ and $V_{\Delta 1} = (\sqrt{2} \cdot V_{LO})$.
Therefore, express the input control voltages V_{IN1} and V_{IN2} of N as a function of V_{LO} and V_{RF} .
- 2) Deduce the expressions of output voltages (V_{OUT1} , V_{OUT2}) as a function of V_{LO} and V_{RF} .
- 3) The SBM down-converter is designed at an IF angular frequency $\omega_{IF} = \omega_{LO} - \omega_{RF}$.
What should be the type (Σ or Δ ?) of port 4 in the output coupler?
- 4) Given that $V_{LO} = V_0 \cdot \cos(\omega_{LO} \cdot t)$ and $V_{RF} = V_1 \cdot \cos(\omega_{RF} \cdot t)$, express the output voltage spectrum V_4 of the SBM as a function of V_0 and V_1 . What are the remaining frequencies at the IF output port of the SBM?
- 5) What are the advantages of this SBM configuration (LO input at Δ port)?
- 6) Express the voltage conversion gain G_{CV} of the SBM. What is the power conversion gain G_{CP} if all 180° couplers are matched to 50Ω ?
- 7) What are the values of LO-to-RF and LO-to-IF isolations?