

EXAMS MICROWAVE - RAFAEL DOS SANTOS

6 JUN
2019

1) $Z_0 = 50\Omega$

$$[S] = \frac{1}{2} \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix}$$

a) Reciprocal \Rightarrow SYMMETRICAL MATRIX $\Rightarrow a_{ij} = a_{ji} \Rightarrow$ this is TRUE FOR THIS NETWORK

\Rightarrow THE NETWORK IS RECIPROCAL

b) Lossless \Rightarrow THE MATRIX MUST BE UNITARY \Rightarrow FOR EACH ROW OR COLUMN THE MODULUS SQUARE SUM OF EACH ELEMENT HAS TO BE EQUAL TO 1.

$$|a_{11}|^2 + |a_{12}|^2 + |a_{13}|^2 = 0^2 + \left(\frac{1}{2}\right)^2 + \left(\frac{1}{2}\right)^2 = \frac{1}{2} \neq 1 \Rightarrow \text{THE MATRIX ISN'T UNITARY.}$$

\Rightarrow THE NETWORK IS NOT LOSSLESS

c) MATCHED PORTS: $a_{ij} = 0 \quad \forall i, j \Rightarrow$ this is TRUE FOR THIS MATRIX
 \Rightarrow THE PORTS ARE MATCHED.

d) $S_{23} \neq 0$ and $S_{32} \neq 0 \Rightarrow$ THE OUTPUT PORTS AREN'T ISOLATED.

$$e) V_1^+ = 10V.$$

$$S_{21} = \frac{V_2^+}{V_1^+} = \frac{1}{2} = \frac{V_2^+}{10} \rightarrow V_2^+ = 5V$$

$$S_{31} = \frac{V_3^+}{V_1^+} = \frac{1}{2} = \frac{V_3^+}{10} \rightarrow V_3^+ = 5V$$

$$f) P_2 = \frac{1}{2} \frac{V_2^{+2}}{Z_0} = \frac{1}{2} \frac{5^2}{50} = 0,25W$$

$$P_3 = \frac{1}{2} \frac{V_3^{+2}}{Z_0} = \frac{1}{2} \frac{5^2}{50} = 0,25W$$

$$g) P_1 = \frac{1}{2} \frac{V_1^{+2}}{Z_0} = \frac{1}{2} \frac{10^2}{50} = 1W = P_{\text{available}}$$

$$P_{\text{available}} = P_{\text{diss}} + P_{\text{out}}$$

$$P_1 = P_{\text{diss}} + P_2 + P_3$$

$$P_{\text{diss}} = 0,5W$$

$$2) \text{ RESONATOR AIR-FILLED } Z_0 = 100\Omega \quad f_0 = 16Hz \quad \text{phase-sh. ft} = \pi \quad \beta L = \pi$$

$$a) \beta = \frac{2\pi}{d} = \frac{2\pi \cdot 1 \times 10^{-9}}{3 \times 10^{-8}} = 20,94 \text{ m}^{-1}$$

$$b) \beta L = \pi \rightarrow L = \frac{\pi}{20,94} = 0,15 \text{ m} = 15 \text{ cm}$$


$$c) f = f_0 + \Delta f$$

$$\beta L = \frac{2\pi}{C} \cdot (f_0 + \Delta f) \cdot L = \left(\frac{2\pi f_0}{C} + \frac{2\pi \Delta f}{C} \right) \cdot L = \pi + \frac{2\pi \cdot 0,15 \cdot \Delta f}{3 \times 10^{-8}}$$

$$\beta L = \pi + \pi \times 10^{-9} \Delta f \Rightarrow \beta L = \pi + \frac{\pi}{f_0} \Delta f$$

16 JUN
2020
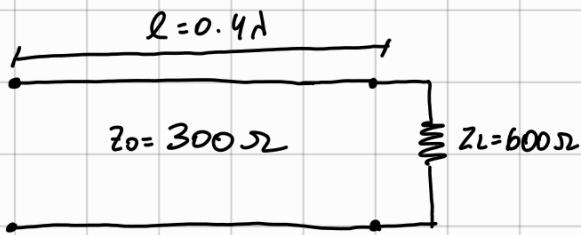
$$1) \quad Z_0 = 300 \Omega \quad R_L = 600 \Omega \quad l = 0,4 \lambda \quad f = 500 \text{ MHz}$$



a) Γ ?

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{600 - 300}{600 + 300} = \frac{1}{3}$$

b) SWR?

$$\text{SWR} = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + \frac{1}{3}}{1 - \frac{1}{3}} = 2$$

c) Z_{IN} ?

$$Z_{IN} = Z_0 \cdot \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l}$$

$$\beta l = \frac{2\pi}{\lambda} \cdot 0,4 \lambda = 2,51$$

$$\rightarrow \tan \beta l = -0,726.$$

$$Z_{IN} = 300 \cdot \frac{600 + j \cdot 300 \cdot (-0,726)}{300 + j \cdot 600 \cdot (-0,726)}$$

$$Z_{IN} = 294,77 + j 210,2 \Omega$$

$$d) \quad l = \frac{\lambda}{4} \rightarrow Z_1 = \sqrt{Z_0 \cdot Z_L} = \sqrt{300 \cdot 600} = 424,26 \Omega$$

e) Fractional BW:

$$\frac{\Delta f}{f_0} = 2 - \frac{4}{\pi} \cos^{-1} \left[\frac{\Gamma_m}{\sqrt{1 - \Gamma_m^2}} \frac{2 \sqrt{Z_0 Z_L}}{|Z_L - Z_0|} \right]$$

$$\text{SWR} \leq 1,5 \rightarrow \Gamma_m = \frac{\text{SWR} - 1}{\text{SWR} + 1} = \frac{1,5 - 1}{1,5 + 1} = \frac{1}{5} = 0,2$$

$$\frac{\Delta f}{f_0} = 2 - \frac{4}{\pi} \cos^{-1} \left[\frac{0,2}{\sqrt{1 - 0,2^2}} 2 \frac{424,6}{|600 - 300|} \right]$$

$$\frac{\Delta f}{f_0} = 0,7836 \approx 78,36\%$$

$$2) \quad \epsilon_r = 2,25 \quad \tan \delta = 0,0004 \quad f_0 = 10 \text{ GHz}.$$

a) a, b?

$$f_{c_{10}} = 0,75 f_0 = 7,5 \text{ GHz}$$

$$f_{c_{01}} = 1,25 f_0 = 12,5 \text{ GHz}$$

$$f_{c_{10}} = \frac{c}{2\pi\sqrt{\epsilon_r}} \cdot \left(\frac{\pi}{a}\right) \Rightarrow a = 1,33 \text{ cm}$$

$$f_{c_{01}} = \frac{c}{2\pi\sqrt{\epsilon_r}} \left(\frac{\pi}{b}\right) \Rightarrow b = 0,8 \text{ cm}$$

b) RECTANGULAR WAVEGUIDE CAVITY.

Perfectly conducting walls $\rightarrow T \rightarrow \infty$

$$\downarrow \\ R_S = 0$$

$$\downarrow \\ Q_C \rightarrow \infty$$

$$Q = \left(\frac{1}{Q_C} + \frac{1}{Q_d} \right)^{-1}$$

$$Q_d = \frac{1}{\tan \delta} = 2500$$


$$Q = 2500$$

3)

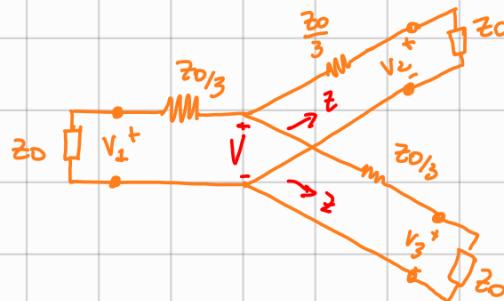a) $S_{33} = 0 \quad S_{22} = 0$ (Ports 2 and 3 matched)

$$S_{31} = \frac{1}{2} = \frac{V_3^+}{V_1^+}$$

$$Z = \frac{Z_0}{3} + Z_0 = \frac{4}{3} Z_0$$



$$V = V_1^+ \cdot \frac{Z \parallel Z}{Z \parallel Z + \frac{Z_0}{3}} = V_1^+ \cdot \frac{\frac{2}{3} Z_0}{\frac{2}{3} Z_0 + \frac{Z_0}{3}} = V_1^+ \cdot \frac{\frac{2}{3} Z_0}{Z_0} = V_1^+ \cdot \frac{2}{3} \rightarrow V = \frac{2}{3} V_1^+$$


$$V_3^+ = V \cdot \frac{Z_0}{Z_0 + \frac{Z_0}{3}} = \frac{2}{3} V_1^+ \cdot \frac{Z_0}{\frac{4}{3} Z_0} = \frac{2}{3} V_1^+ \cdot \frac{3}{4} \rightarrow V_3^+ = \frac{V_1^+}{2}$$

$$P_3 = \frac{1}{2} \frac{V_3^+}{Z_0} = \frac{1}{2} \underbrace{\frac{V_1^+}{Z_0}}_{P_1} \frac{1}{4}$$

$$P_3 = \frac{1}{4} P_1$$

$$\frac{P_3}{P_1} = \frac{1}{4}$$
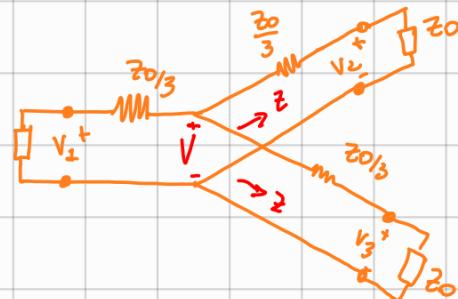
$$\left[\frac{P_3}{P_1} \right]_{dB} = 10 \log \frac{1}{4} = -6 \text{ dB}$$



$$b) \quad P_2 = 0.3 = S_{22}$$

$$P_2 = \frac{z_1 - z_{IN}}{z_1 + z_{IN}}$$


$$z_{IN} = \frac{z_0}{3} + z || z$$

$$z_{IN} = \frac{z_0}{3} + \frac{2}{3} z_0 = z_0$$

$$\rightarrow 0.3 = \frac{z_1 - z_0}{z_1 + z_0} \rightarrow 0.3 z_1 + 0.3 z_0 = z_1 - z_0$$

$$1.3 z_0 = 0.7 z_1$$

$$z_1 = 1.86 z_0$$

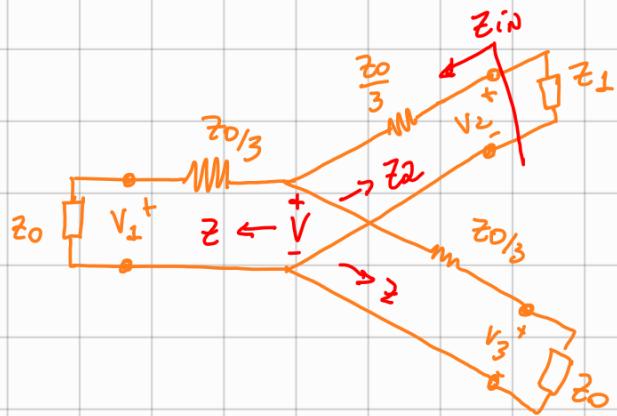

$$z_d = \frac{z_0}{3} + z_1 = 2.20 z_0$$

$$z = \frac{z_0}{3} + z_0 = \frac{4}{3} z_0$$

$$z || z_2 = \frac{\frac{4}{3} z_0 \cdot 2.20 z_0}{\frac{4}{3} z_0 + 2.20 z_0} = 0.83 z_0$$

$$V = V_1 \cdot \frac{z || z_2}{z_0 + z || z_2} = V_1 \cdot \frac{0.83 z_0}{\frac{4}{3} z_0 + 0.83 z_0} \Rightarrow V = 0.71 V_1$$

$$V_3 = V \cdot \frac{z_0}{z_0 + \frac{z_0}{3}} = 0.71 V_1 \cdot \frac{z_0}{\frac{4}{3} z_0} = 0.71 V_1 \cdot \frac{3}{4}$$

$$V_3 = 0.535 V_1$$

$$\alpha_{dB} = 20 \log (0.535) = -5,43 dB$$

29 JUN
2020

1) for $l = \frac{\lambda}{2}$, $Z_{in} = Z_L$ and it is reasonable to ignore the presence of the transmission line.

a) $30 \times 10^2 \neq \frac{1}{2} \frac{3 \times 10^8}{20 \times 10^3} \rightarrow \text{can't ignore}$

b) $50 \times 10^3 \neq \frac{1}{2} \frac{3 \times 10^8}{60} \rightarrow \text{can't ignore}$

c) $30 \times 10^{-2} \neq \frac{1}{2} \frac{3 \times 10^8}{600 \times 10^6} \rightarrow \text{can't ignore}$

2) a) lossless $\rightarrow [S]$ must be unitary.

$$(0.178 \angle 90^\circ)^2 + (0.6 \angle 45^\circ)^2 + (0.4 \angle 45^\circ)^2 \neq 1$$

\hookrightarrow The network has losses.

b) Reciprocal $\rightarrow a_{ij} = a_{ji} \rightarrow \text{TRUE} \rightarrow \text{NETWORK is RECIPROCAL.}$

c) $R_L = -20 \log (|S_11|) = -20 \log 0.178 = 15 \text{ dB.}$

d) Ports 2 and 4 $S_{24} = S_{42} = 0.3 \angle -45^\circ$

$$I_L = -20 \log (|S_{24}|) = -20 \log 0.3 = 10.45 \text{ dB.}$$

Phase delay $\Rightarrow -45^\circ$

e) SC @ Port 3 $\Rightarrow V_3^+ = V_3^-$
MATCHED @ Ports 2 and 4 $V_2^+ = V_4^+ = 0$
 $S_{11} = ?$


$$S = \begin{bmatrix} S_{11} \\ & \end{bmatrix} \quad ?$$

$$[V^-] = [S] [V^+]$$

3) RHCP plane wave

$$E_i = E_0 (\hat{x} - j \hat{y}) e^{-jk_0 z}$$

Interface with a good conductor

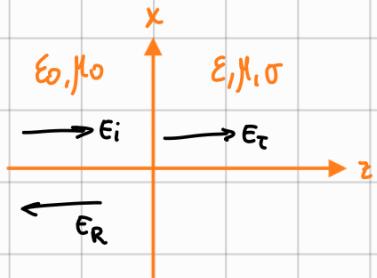

$$E_t = T E_0 (\hat{x} - j \hat{y}) e^{-jk_0 z}$$

$$H_t = T \frac{E_0}{\gamma} (\hat{x} - j \hat{y}) e^{-jk_0 z}$$

$$\gamma = \alpha + j\beta = (1+j) \sqrt{\frac{\omega \mu_0}{\sigma}} = (1+j) \frac{1}{\delta s}$$

$$\gamma = (1+j) \sqrt{\frac{\omega \mu}{\sigma \delta s}} = (1+j) \frac{1}{\sigma \delta}$$

17 JUL
2020

1)



$$a) f_0 = \frac{1}{2\pi} \frac{1}{\sqrt{LC}} = \frac{1}{2\pi} \frac{1}{\sqrt{50 \times 10^{-9} \cdot 0.79 \times 10^{-12}}} = 800 \text{ MHz}$$

$$b) Z_{in} = R + j\omega L - j \frac{1}{\omega C} = 2.5 \Omega$$

$$c) Q = \omega \frac{\text{AVERAGE ENERGY STORED}}{\text{ENERGY LOSS / SEC}} = \omega \frac{W_N + W_e}{P_{loss}}$$

at Resonance:

$$Q = \omega_0 \frac{2w_m}{P_{loss}} = \omega_0 \frac{2 \frac{1}{4} |I_0|^2 L}{\frac{1}{2} |I_0|^2 R} = \omega_0 \frac{L}{R}$$

$$Q = \frac{1}{\sqrt{LC}} \cdot \frac{L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$Q = \frac{1}{2.5} \sqrt{\frac{50 \times 10^{-9}}{0.79 \times 10^{-12}}} = 100.64. \text{ (UNLOADED)}$$


$$Q_E = \frac{\omega_0 L}{R_L} \text{ (SERIES)}$$

$$Q_E = \frac{2\pi \cdot 800 \times 10^6 \cdot 50 \times 10^{-9}}{2.5} = 100$$

$$\frac{1}{Q_L} = \frac{1}{Q} + \frac{1}{Q_F} \rightarrow Q_L = 50$$

2) T-JUNCTION
LOSSLESS

4:1 power split
40Ω source impedance.

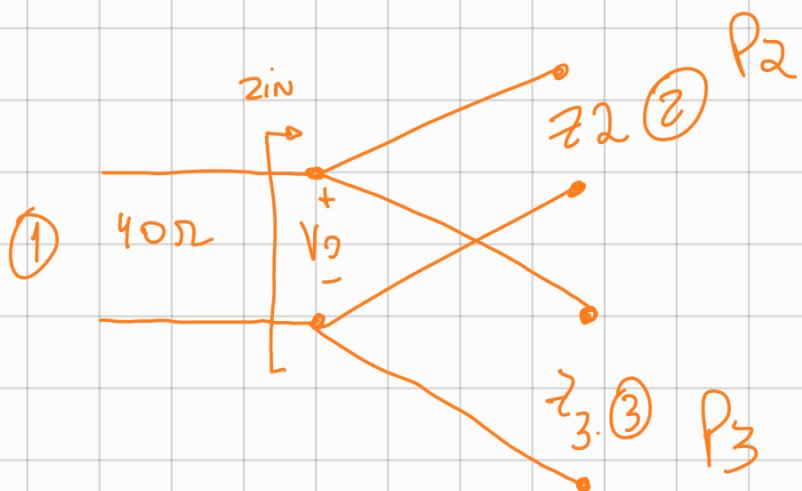

$$P_{IN} = \frac{1}{2} \frac{V_0^2}{Z_0}$$

$$\left. \begin{aligned} P_2 &= \frac{1}{2} \frac{V_0^2}{Z_2} \\ P_3 &= \frac{1}{2} \frac{V_0^2}{Z_3} \end{aligned} \right\} \boxed{P_2 = 4P_3} \rightarrow P_2 = 2 \frac{V_0^2}{Z_3}$$

$$P_{IN} = P_2 + P_3 = 2 \frac{V_0^2}{Z_3} + \frac{1}{2} \frac{V_0^2}{Z_3} = \frac{5}{2} \frac{V_0^2}{Z_3}$$

$$\frac{1}{2} \frac{V_0^2}{Z_2} = \frac{5}{2} \frac{V_0^2}{Z_3}$$

$$Z_3 = 5Z_2 = \boxed{200\Omega = Z_3}$$

$$\frac{1}{2} \frac{V_0^2}{Z_2} = 2 \frac{V_0^2}{Z_3} \rightarrow 4Z_2 = Z_3$$


$Z_2 = 50\Omega$

$\lambda/4$ LINES MATCHING:
FOR Z_2 BRANCH:

$$Z_{\text{LINE}2} = \sqrt{50 \cdot 40} = 44.72 \Omega$$

FOR Z_3 BRANCH:
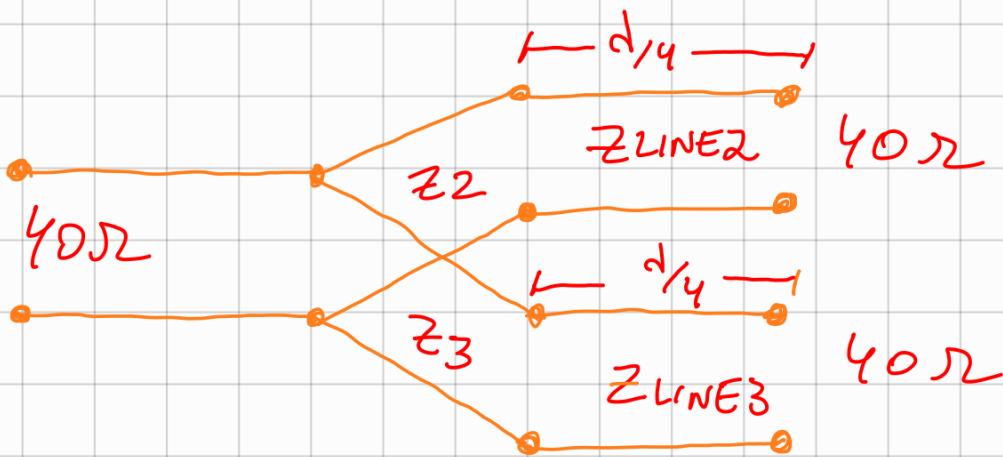
$$Z_{\text{LINE}3} = \sqrt{200 \cdot 40} = 89.44 \Omega$$



$$|S| = \begin{bmatrix} 0 & 0.8 & 0.2 \\ 0.8 & 0.11 & 0 \\ 0.2 & 0 & 0.67 \end{bmatrix}$$


$$|\Gamma_2| = \frac{50 - 40}{50 + 40} = 0.11$$

$$|\Gamma_3| = \frac{200 - 40}{200 + 40} = 0.67$$

3) FOUR-SECTION BANDPASS

fractional BW = 5% $f_0 = 2 \text{ GHz}$ $z_0 = 50 \Omega$

Prototype:

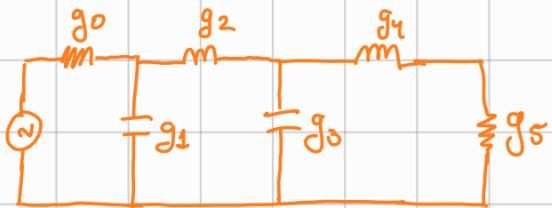

$$\Delta = \frac{\omega_2 - \omega_1}{\omega_0} = 0,05$$

$$g_0 = 1$$


$$g_1 = 1,0598$$

$$g_2 = 0,5116$$

$$g_3 = 0,3181$$

$$g_4 = 0,1104$$

$$g_5 = 1$$

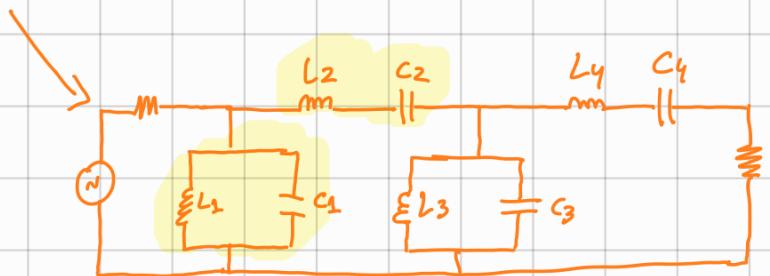

$$L_1 = \frac{\Delta}{\omega_0 C} = \frac{0,05}{2\pi \cdot 2 \cdot 10^9 \cdot 1,0598} \rightarrow L_1 = 3,75 \mu H$$

$$C_1 = \frac{C}{\omega_0 \Delta} = \frac{1,0598}{2\pi \cdot 2 \cdot 10^9 \cdot 0,05} \rightarrow C_1 = 1,69 \text{ nF}$$

$$L_2 = \frac{L}{\omega_0 \Delta} = \frac{0,5116}{2\pi \cdot 2 \cdot 10^9 \cdot 0,05} \rightarrow L_2 = 0,81 \text{ nH}$$

$$C_2 = \frac{\Delta}{\omega_0 L} = \frac{0,05}{2\pi \cdot 2 \cdot 10^9 \cdot 0,5116} \rightarrow C_2 = 7,7 \text{ pF}$$

$L_3, C_3, L_4, C_4 \rightarrow$ Same procedure!

$$1) \quad Z_0 = 60 \Omega \quad \Gamma = 0,4$$

$$a) \quad \frac{\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}}{Z_L + Z_0} \rightarrow 0,4 Z_L + 60 \cdot 0,4 = Z_L - 60$$

$$84 = 0,6 Z_L$$

$$\boxed{Z_L = 140 \Omega}$$

$$b) \quad \Gamma(l) = \Gamma e^{-\alpha l}$$

$$\underline{l = 0,3\lambda} \quad \underline{\Gamma(0,3\lambda) = 0,4 e^{-2j\beta \cdot l}}$$

$$\Gamma(0,3\lambda) = 0,4 e^{-2 \cdot j \cdot 0,6\pi}$$

$$\Gamma(0,3\lambda) = -0,324 + j 0,235$$


$$\beta l = \frac{Z_{II}}{\lambda} \cdot 0,3 \lambda = 0,6\pi$$

$$c) \quad Z_{IN} = Z_0 \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l}$$


$$Z_{IN} = 60 \cdot \frac{140 + j 60 \tan(0,6\pi)}{60 + j 140 \tan(0,6\pi)}$$

$$Z_{IN} = 27,88 + j 15,61 \Omega$$

2)

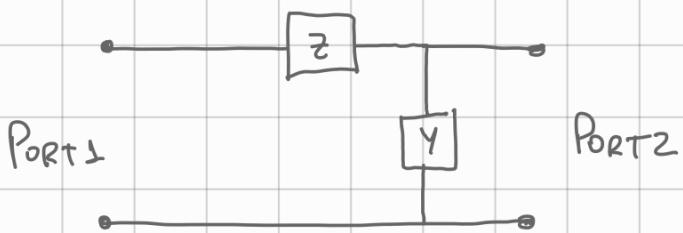
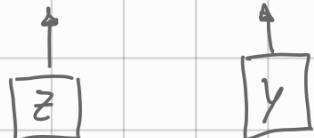
$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \cdot \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \cdot \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$




$$V_1 = A V_2 + B I_2$$

$$I_1 = C V_2 + D I_2$$



$$A = \frac{V_1}{V_2} \Big|_{\Sigma 2=0} = 1 \quad C = \frac{I_1}{V_2} \Big|_{I_2=0} = 0$$

$$B = \frac{V_1}{I_2} \Big|_{V_2=0} = Z \quad D = \frac{I_1}{I_2} \Big|_{V_2=0} = 1$$

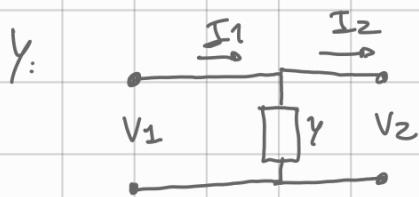


$$A = \frac{V_1}{V_2} \Big|_{\Sigma 2=0} = 1 \quad C = \frac{I_1}{V_2} \Big|_{I_2=0} = Y$$

$$B = \frac{V_1}{I_2} \Big|_{V_2=0} = 0 \quad D = \frac{I_1}{I_2} \Big|_{V_2=0} = 1$$

$$ABCD = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \cdot \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} = \boxed{\begin{bmatrix} 1+ZY & Z \\ Y & 1 \end{bmatrix}}$$

3)

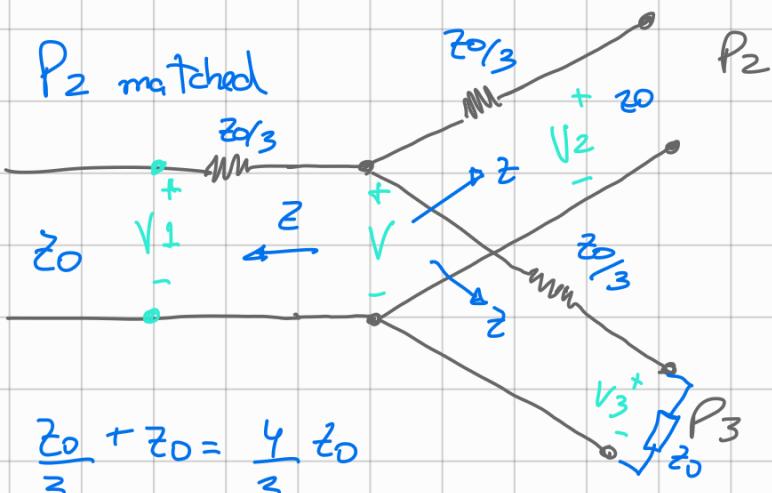a) P_2 matched

$$V = V_1 \cdot \frac{Z||Z}{\frac{Z_0}{3} + Z||Z} = V_1 \cdot \frac{\frac{2}{3} Z_0}{\frac{Z_0}{3} + \frac{4}{3} Z_0} \rightarrow V = \frac{2}{3} V_1$$

$$V_3 = V \cdot \frac{Z_0}{\frac{Z_0}{3} + Z_0} = \frac{2}{3} V_1 \cdot \frac{Z_0}{\frac{4}{3} Z_0} = \frac{2}{3} V_1 \cdot \frac{3}{4}$$


$$\boxed{V_3 = \frac{V_1}{2}}$$

$$P_1 = 1W \rightarrow P_1 = \frac{1}{2} \frac{V_1^2}{Z_0} \rightarrow V_1^2 = 2 Z_0 P_1$$

$$P_3 = \frac{1}{2} \frac{V_3^2}{Z_0} = \frac{1}{2} \frac{V_1^2}{4} \cdot \frac{1}{Z_0} = \frac{1}{2} \frac{2 Z_0 P_1}{4} \cdot \frac{1}{Z_0}$$

$$\boxed{P_3 = \frac{P_1}{4} = 0,25W}$$

b)

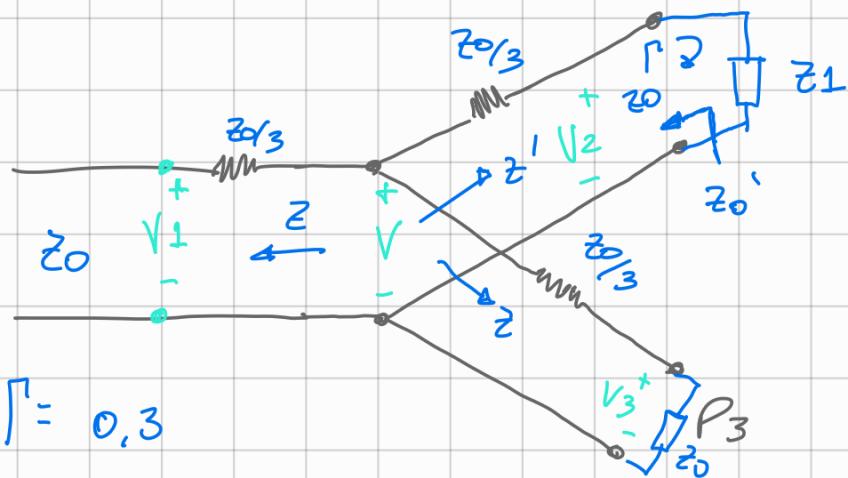

$$Z_0' = \frac{Z_0}{3} + Z \parallel Z = \frac{Z_0}{3} + \frac{Z \cdot Z_0}{3} = Z_0$$

$$\Gamma = \frac{Z_1 - Z_0'}{Z_1 + Z_0'} \rightarrow 0,3 Z_1 + 0,3 \cdot Z_0 = Z_1 - Z_0 \\ 1,3 Z_0 = 0,7 Z_1 \\ \boxed{Z_1 = 1,86 Z_0}$$

$$Z \parallel Z' = \frac{\left(\frac{Z_0}{3} + Z_0\right) \cdot \left(\frac{Z_0}{3} + 1,86 Z_0\right)}{\frac{Z_0}{3} + Z_0 + \frac{Z_0}{3} + 1,86 Z_0} = \frac{2,92 Z_0^2}{3,53 Z_0}$$

$$Z \parallel Z' = 0,828 Z_0$$

$$V = \frac{V_1 \cdot (Z \parallel Z')}{(Z \parallel Z') + \frac{Z_0}{3}} = \frac{V_1 \cdot 0,828 Z_0}{0,828 Z_0 + \frac{Z_0}{3}} \quad V = 0,713 V_1$$

$$V_3 = V \cdot \frac{Z_0}{Z_0 + \frac{Z_0}{3}} = 0,713 V_1 \cdot \frac{3}{4} = 0,535 V_1$$

$$P_1 = \frac{1}{2} \frac{V_1^2}{Z_0} \rightarrow V_3^2 = 2 P_1 Z_0$$

$$P_3 = \frac{1}{2} \frac{V_3^2}{Z_0} = \frac{1}{2} \frac{0,535^2 V_1^2}{Z_0} = \frac{1}{2} \frac{0,535^2}{Z_0} \cdot 2 P_1 Z_0 = \underline{\underline{0,286 W}}$$