

# Basics on High-Frequency Mixers

# Outline

◆ Introduction ✕

◆ Theory of frequency conversion \*

◆ Characteristic performances of mixers \*

◆ Active mixers

→ Single Ended (SEM) → Gate Mixer / Drain Mixer

→ Gilbert Cell → DBDM Double Balanced Differential Mixer

◆ Passive Mixers


→ Diodes → SEM / SBM / DBM

→ Cold FETs → SEM / SBM


◆ IRM: Image Reject Mixers
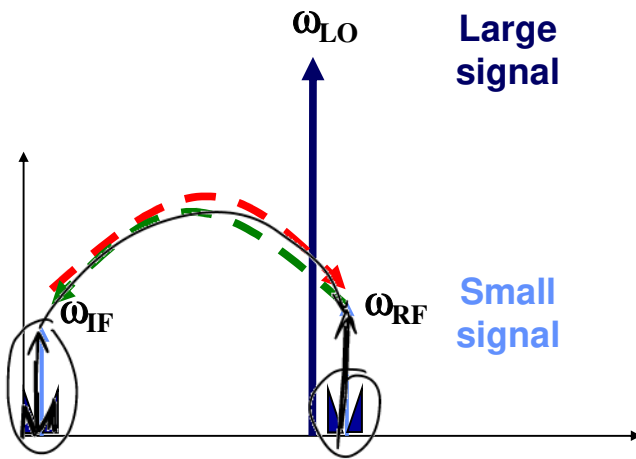
# Introduction





**A mixer is a 3-port nonlinear circuit  
which performs the frequency translation  
required by any communication system.**



Radio Frequency = (2 GHz)  
RF 40 GHz

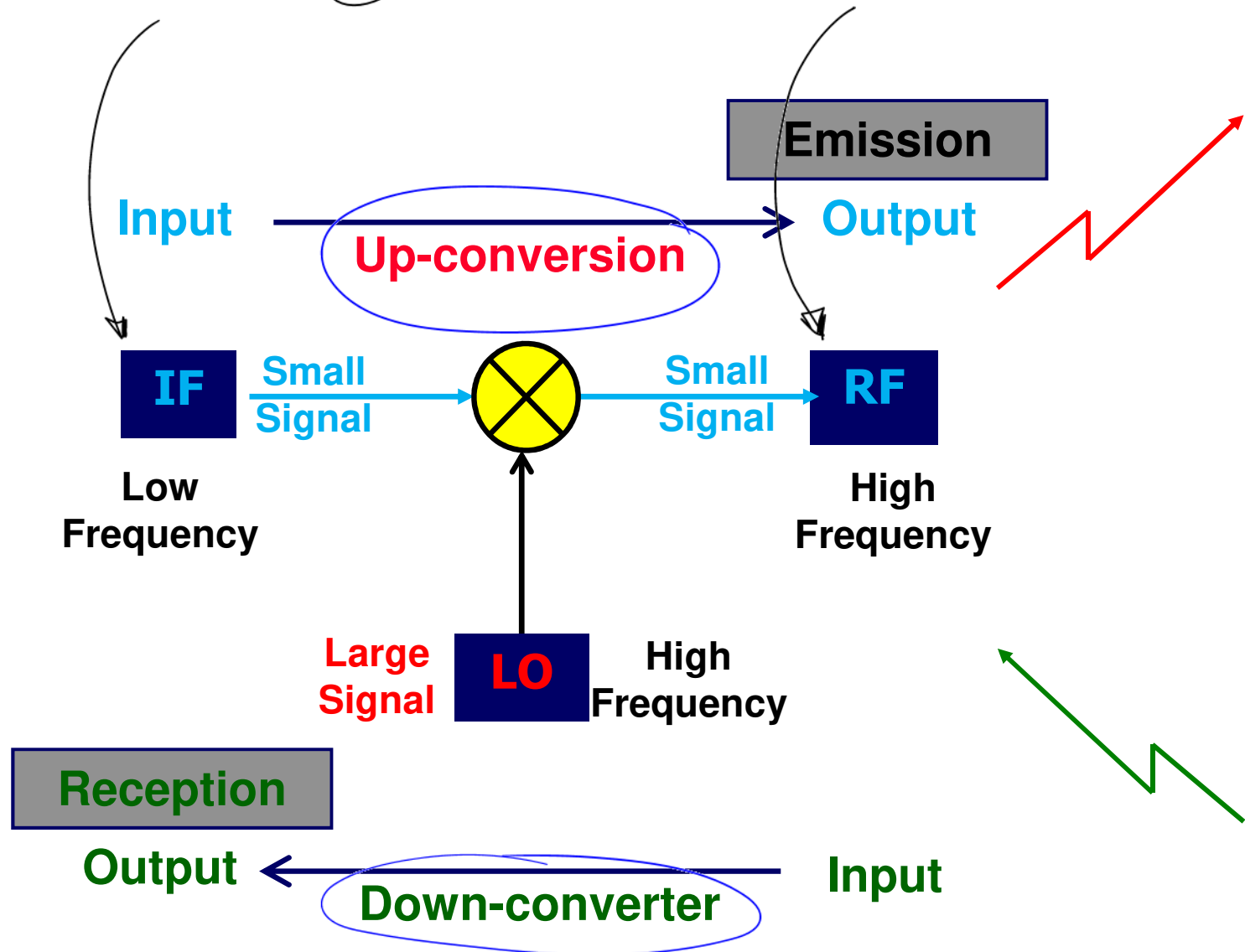



VERY HIGH  $P_{LO}$

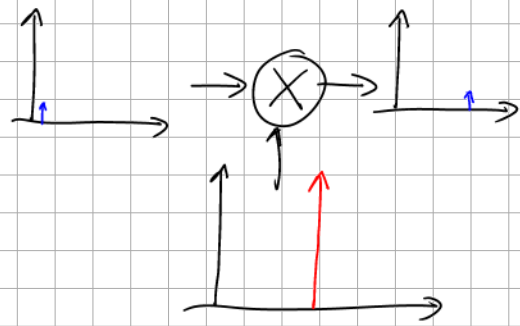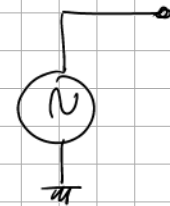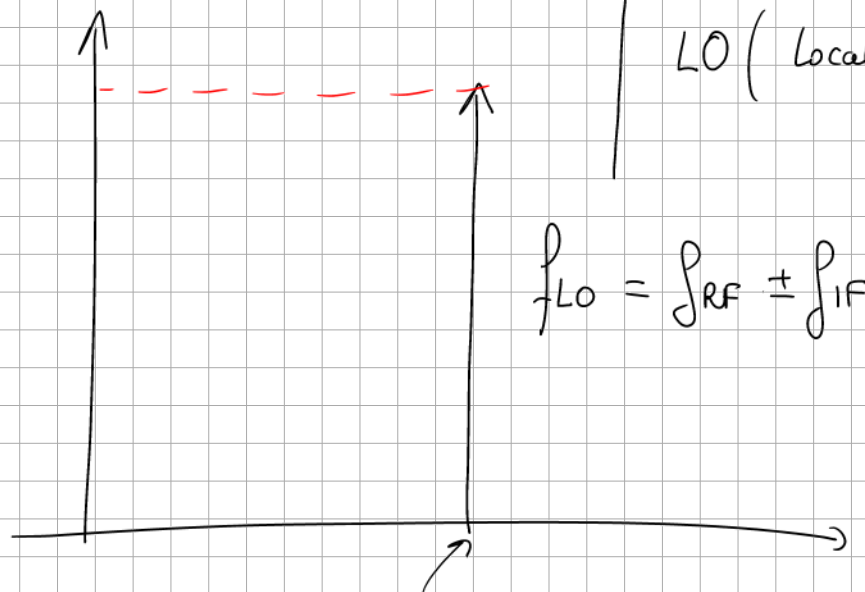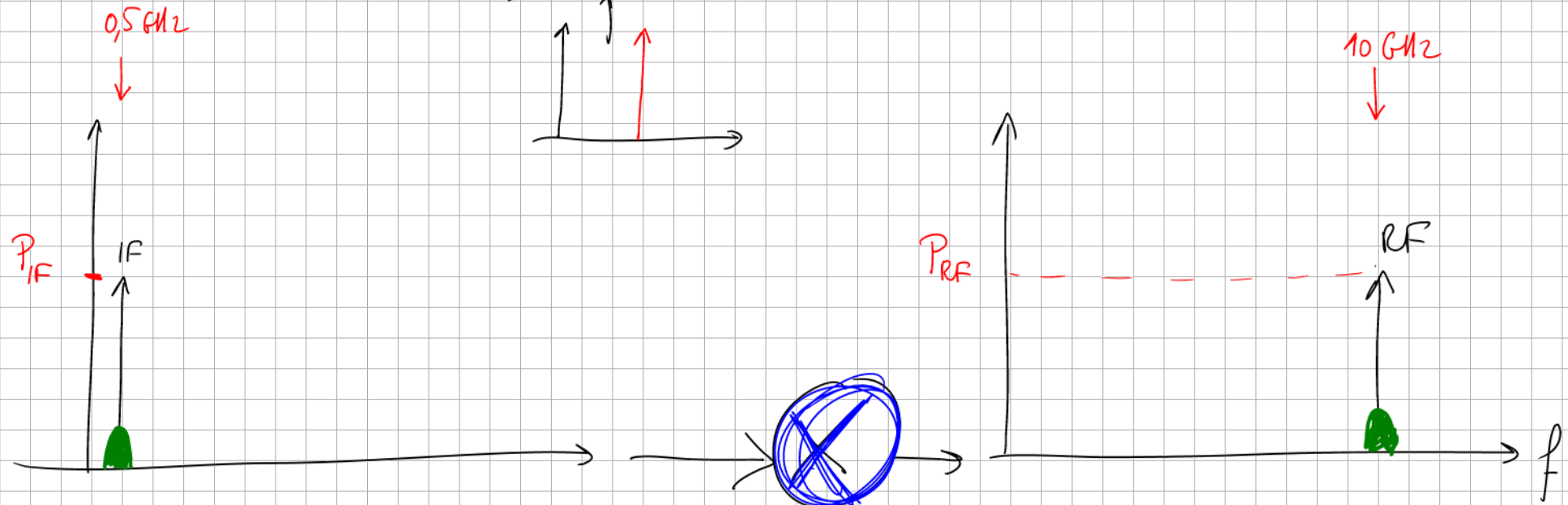
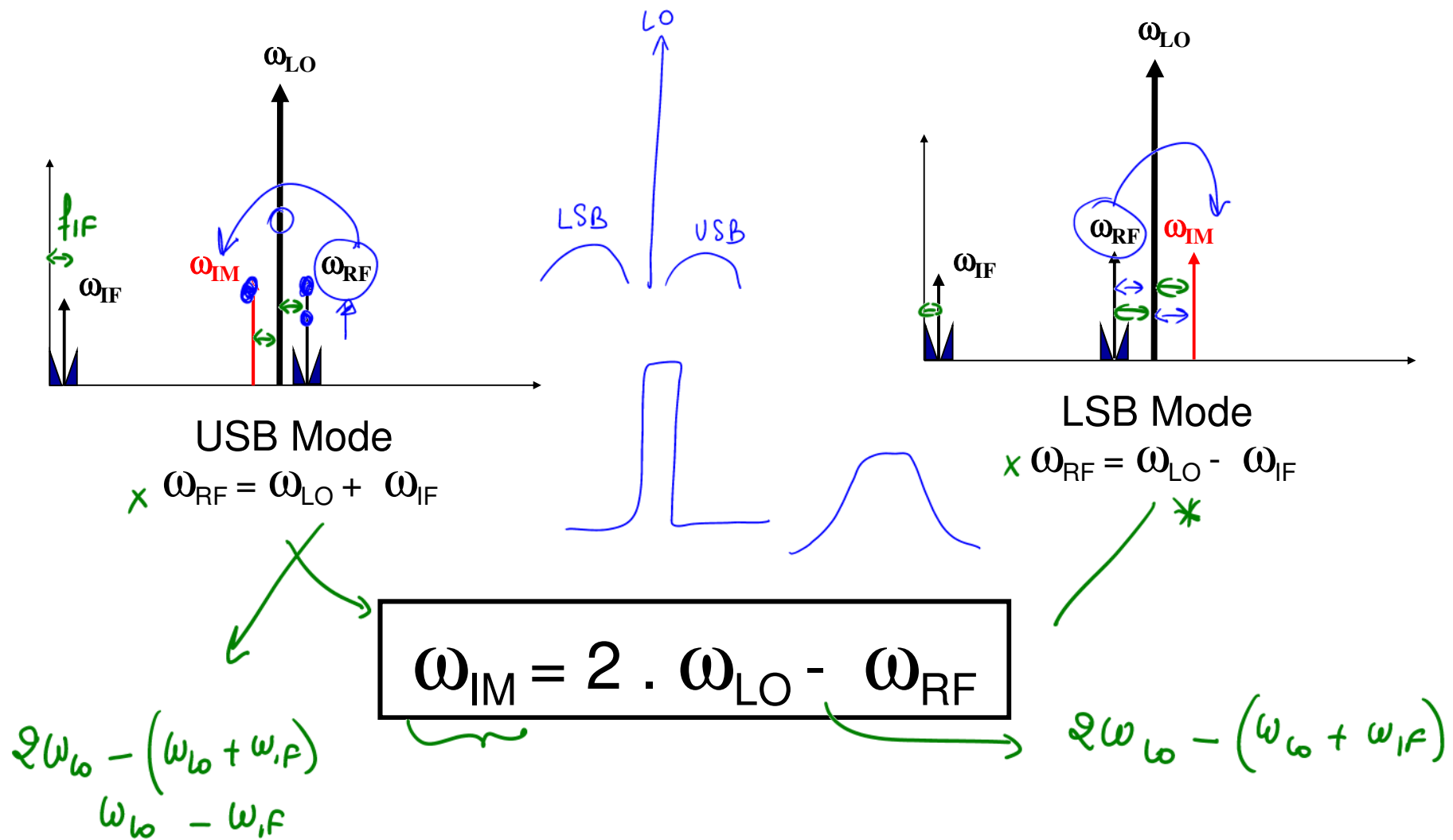
# Problem of IMAGE FREQUENCY

The **image frequency** is the symmetric of the RF frequency with respect to the LO frequency



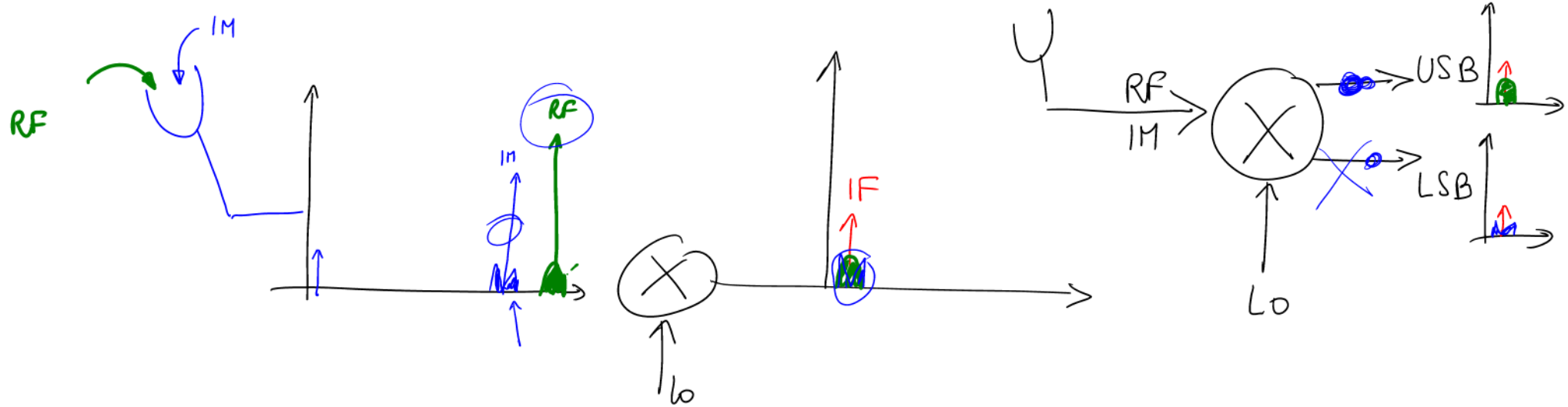

Principle of frequency conversion