
## **Transmission Lines**
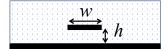
## **Transmission line**

A transmission line embedded in a polymer is presented below:



The relative permittivity of the polymer is 3. The line width is 40  $\mu$ m. The distance to the ground plane is 20  $\mu$ m.

- 1- Give the expression of the capacitance per unit length of the transmission line, using a parallel plane approximation, and compute using the given dimensions.
- 2- Give the expression of the inductance per unit length from the question 1 and the wave velocity on the line.
- 3- Deduce the expression of the characteristic impedance of the transmission line from the width, w, the distance to the ground plane, h, and the relative permittivity,  $\varepsilon_r$ , of the polymer.
- 4- Compute the width of a 50 Ohms transmission line.

## **E-MIMEO – Integrated passives – Short Transmission Lines**

- 1- A transmission line with a characteristic impedance of 10 Ohms has a line length of 1 mm. Its effective permittivity is 2.8. Compute the equivalent shunt capacitance of this transmission line section.
- 2- A transmission line with a characteristic impedance of 100 Ohms has a line length of 1 mm. Its effective permittivity is 2.8. Compute the equivalent series inductance of this transmission line section.

- 3- Synthetic transmission line. A transmission line can be made from the cascade of short transmission lines, allowing to synthetize transmission line sections.
  - 3.a To realize a synthetic transmission line, one have to cascade high/low impedance sections. On the drawing above, which metal level would you choose for the high impedance section? Which metal level would you choose for the low impedance sections?
  - 3.b Compute the width of the 10 Ohms line
  - 3.c Compute the width of the 100 Ohms line
  - 3.d. If the 10 Ohms line is 150  $\mu m$  long, what should be the length of the 100 Ohms line to obtain a 50 Ohm composite transmission line?