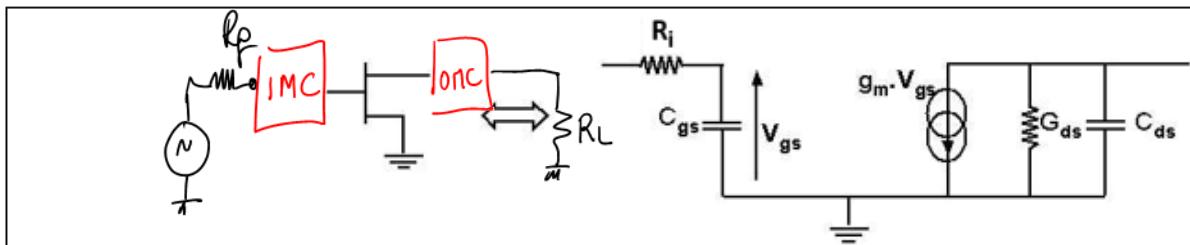




## Basics of Active and Nonlinear HF Electronics – Tutorial 2

### A ) Power gain matching of a single-stage narrow-band amplifier

This figure represents the simplified electrical model of an FET.





The model parameters are given at a bias point of ( $V_{GS0} = -2 \text{ V}$  and  $V_{DS0} = 20 \text{ V}$ )

$$R_i = 5 \Omega ; C_{GS} = 0.5 \text{ pF} ; g_m = 100 \text{ ms} ; R_{DS} = 200 \Omega ; C_{DS} = 0.15 \text{ pF}$$

The amplifier environment is :  $R_G = 50 \Omega$  ;  $R_L = 50 \Omega$  ;  $f_0 = 10 \text{ GHz}$

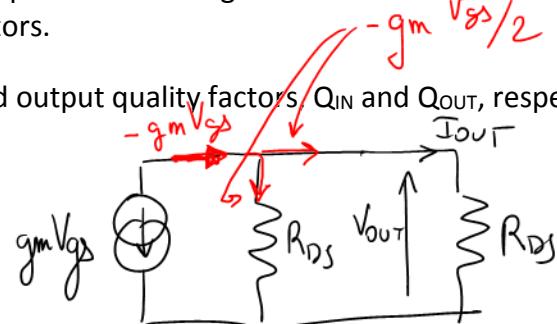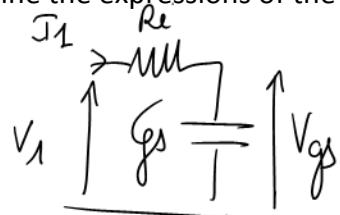- 1) Determine the expression of  $G_{MAX}$  : maximum power gain of the transistor as a function of frequency
- 2) We consider the design of a linear amplifier, which is loaded by a resistor  $R_L$ , while the input generator has an internal resistor  $R_G$ .
  - a) Draw the ideal input and output matching circuits of a narrow-band amplifier which is matched to its maximum power gain  $G_{MAX}$  at  $f_0$ .
  - b) Determine the expressions of each passive matching elements as a function of  $f_0$ , the model parameters and the  $R_G$  and  $R_L$  resistors.
- 3) Determine the expressions of the input and output quality factors,  $Q_{IN}$  and  $Q_{OUT}$ , respectively.



$$\begin{aligned} P_{IN} &= \frac{1}{2} \operatorname{Re}(V_1 I_1^*) \\ &= \frac{1}{2} \operatorname{Re}\left(\left(R_i - j \frac{1}{G_s w}\right) I_1 I_1^*\right) = \frac{1}{2} R_i |I_1|^2 \end{aligned}$$

$$I_1 = j G_s w V_{GS} \rightarrow |I_1| = G_s w |V_{GS}|$$

$$\hookrightarrow \boxed{P_{IN} = \frac{1}{2} R_i G_s^2 w^2 |V_{GS}|^2} \quad (G_{MAX} = \frac{1}{4} \frac{R_{DS} g_m^2}{R_i G_s^2 w^2})$$


$$P_{OUT} = \frac{1}{2} \operatorname{Re}(V_{OUT} I_{OUT}^*)$$

$$= \frac{1}{2} \operatorname{Re}(R_{DS} I_{OUT} I_{OUT}^*)$$

$$= \frac{1}{2} R_{DS} |I_{OUT}|^2$$

$$= \frac{1}{2} R_{DS} \left| -\frac{g_m}{2} \frac{V_{GS}}{2} \right|^2$$

$$\boxed{P_{OUT} = \frac{1}{8} R_{DS} g_m^2 |V_{GS}|^2}$$

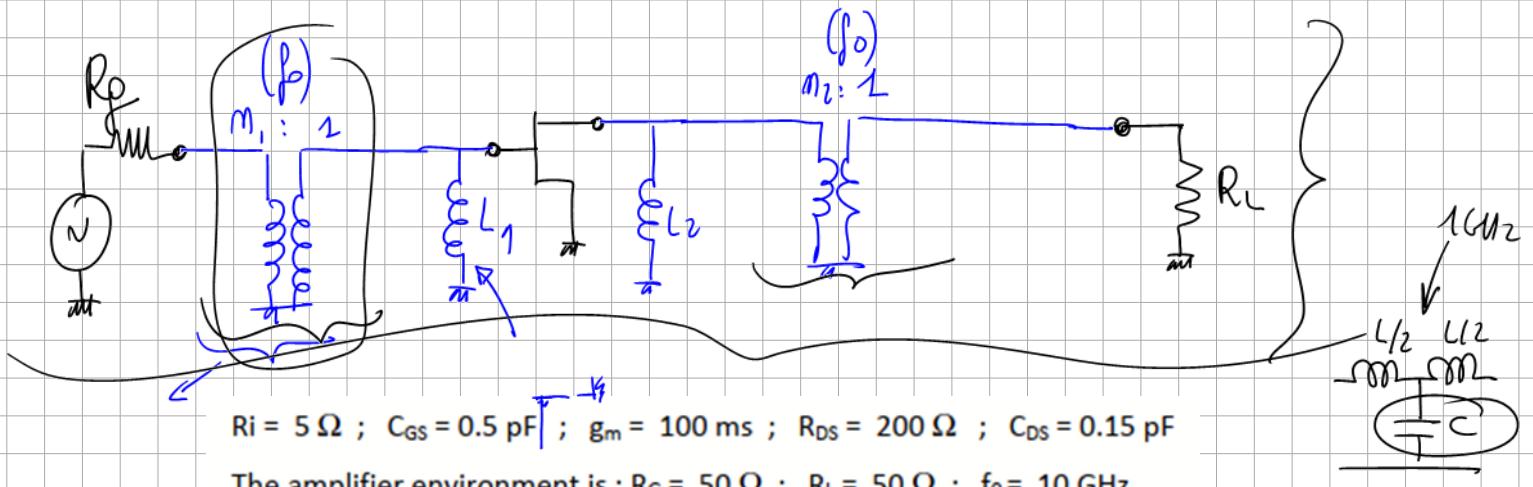

1) INPUT MATCHING ( $R_i$  or  $R_{IN}$  series parallel? to transform to  $R_G \approx 50 \Omega$ )

$$R_{IN}(10 \text{ GHz}) = \frac{1}{R_i C_{DS}^2 \omega^2} = \frac{1}{5 (0.5 \cdot 10^{-12} 2\pi \cdot 10^{10})^2} = \frac{1}{5 \times \pi^2 \cdot 10^{-4}} = \frac{10000}{5\pi^2}$$

$$\frac{R_{IN}}{R_G} = \frac{202}{50} \approx 4 \quad \text{and} \quad \frac{R_G}{R_i} = \frac{50}{5} = 10 \rightarrow \text{Best choice // matching}$$

$$L_1 = \frac{1}{C_{GS} \cdot \omega^2} = 0.5 \text{ mH}$$

$$M_1 = \sqrt{\frac{202}{50}} = 2$$

2) OUTPUT MATCHING

$$L_2 = \frac{1}{C_{DS} \cdot \omega^2} = 1.7 \text{ mH}$$

$$M_2 = \sqrt{\frac{R_{DS}}{R_L}} = \sqrt{\frac{200}{50}} = 2$$

2) Quality factors

• INPUT


$$Q_{IN} = \frac{1}{R_i C_{DS} \omega_0} = \frac{1}{5 (0.5 \cdot 10^{-12} 2\pi \cdot 10^{10})} = \frac{100}{5\pi} = 6.4 *$$

$$Q_S = \frac{1}{R_C \omega_0}$$

$$Q_H = R_C \omega_0$$

• OUTPUT
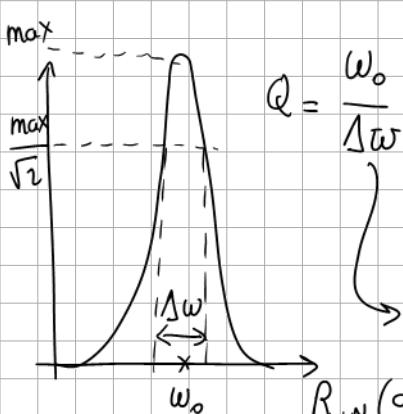
$$Q_{OUT} = R_{DS} C_{DS} \omega_0 = 200 \times 0.15 \cdot 10^{-12} 2\pi \cdot 10^{10} = 1.9$$



$$= R_{opt} C_{DS} \omega_0$$

if you match to  $R_{opt}$

$$\Delta f_{max} = \frac{\omega_0}{Q} \rightarrow R_{IN}(11 \text{ GHz})$$

$$\frac{f_0}{Q_{max}} = \frac{10 \text{ GHz}}{6.4} = 1.6 \text{ GHz}$$

$2 \text{ GHz}$



## B ) Power gain matching of a two stage narrow-band amplifier

### Main specifications of the narrow-band amplifier:

Output Power  $P_{\text{OUT}} > 1 \text{ W}$  ; Center frequency  $f_0 = 15 \text{ GHz}$  ; Power Gain  $G_p > 15 \text{ dB}$

### Selected MMIC foundry (0.15 μm GaAs HEMT) :

Power Density  $\text{PD} = 1 \text{ W/mm}$  ; Measured Gain  $G_{\text{MAX}}(@10\text{GHz}) = 16 \text{ dB}$  ;

Saturated Drain Current  $I_{\text{DS}} = 800 \text{ mA/mm}$  ; Drain Voltage range ( $V_{\text{DSmin}}=1\text{V}$  and  $V_{\text{DSmax}}=11\text{V}$ )


Pinch-off Voltage :  $V_p = -4 \text{ V}$

Optimum load impedance  $R_{\text{OPT}} = 12.5 \Omega \cdot \text{mm}$


Small-signal model:  $C_{\text{GS}} = 2.7 \text{ pF/mm}$  ;  $R_i = 1 \Omega \cdot \text{mm}$  ;  $g_m = 200 \text{ mS/mm}$  ;

$R_{\text{DS}} = 125 \Omega \cdot \text{mm}$  ;  $C_{\text{DS}} = 0.6 \text{ pF/mm}$

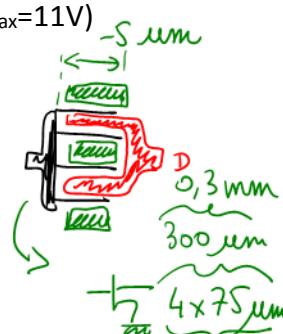Selected device size @ 15 GHz =  $4 \times 75 \mu\text{m}$  GaAs HEMT



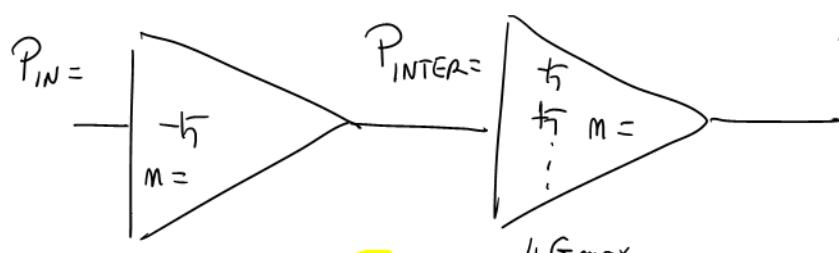- 1) Given the required specifications and the selected transistor technology, determine the initial sizing of the power amplifier (number of stages, number of amplifying cells per stage, power gain and input/output powers of each stage) using the selected device size ( $4 \times 75 \mu\text{m}$ ) as the unitary amplifying cell.
- 2) Given that only the last stage should be matched to its optimum output power while all the preceding stages should be matched to their maximum power gain, draw the input and output matching circuits of this two-stage narrow-band amplifier and calculate the values of each matching elements.
- 3) Calculate the input and output quality factors of each stage to assess what will be the bandwidth behavior.
- 4) Can you comment on the power limitations and the power added efficiency of this two-stage amplifier?



You have only  
to know  
how to find  
the  $G_{\text{max}}$   
value

$$G_p(R_{\text{opt}}) = \frac{\frac{G_{\text{opt}}}{(G_{\text{opt}} + G_{\text{DS}})^2} g_m^2}{R_i C_{\text{GS}}^2 \omega^2} = \frac{G_{\text{opt}}}{(G_{\text{opt}} + G_{\text{DS}})^2} \times \frac{4 G_{\text{max}}}{R_{\text{DS}}} \quad *$$

$$G_{\text{max}} = \frac{1}{4} \frac{R_{\text{DS}} g_m^2}{R_i C_{\text{GS}}^2 \omega^2} \quad *$$

$$= \frac{1/R_{\text{opt}}}{(1/R_{\text{opt}} + 1/R_{\text{DS}})^2} \times \frac{4 G_{\text{max}}}{R_{\text{DS}}} \quad *$$

$$G_p = \frac{G_2}{[G_2 + g_{\text{DS}}]^2} g_m^2 \quad *$$

$$G_p(R_{\text{opt}}) = \frac{4 R_{\text{opt}} R_{\text{DS}}}{(R_{\text{opt}} + R_{\text{DS}})^2} G_{\text{max}} \quad *$$

## Main specifications of the narrow-band amplifier:

Output Power  $P_{out} > 1 \text{ W}$  ; Center frequency  $f_0 = 15 \text{ GHz}$  ; Power Gain  $G_P > 15 \text{ dB}$

### Selected MMIC foundry (0.15 μm GaAs HEMT):

Power Density  $PD = 1 \text{ W/mm}$  ; Measured Gain  $G_{MAX}@10\text{GHz} = 16 \text{ dB}$  ;

Saturated Drain Current  $I_{DSS} = 800 \text{ mA/mm}$  ; Drain Voltage range ( $V_{DSmin}=1\text{V}$  and  $V_{DSmax}=11\text{V}$ )


Pinch-off Voltage :  $V_P = -4 \text{ V}$

Optimum load impedance  $R_{OPT} = 12.5 \Omega \cdot \text{mm}$


Small-signal model:  $C_{GS} = 2.7 \text{ pF/mm}$  ;  $R_i = 1 \Omega \cdot \text{mm}$  ;  $g_m = 200 \text{ mS/mm}$  ;

$R_{DS} = 125 \Omega \cdot \text{mm}$  ;  $C_{OS} = 0.6 \text{ pF/mm}$

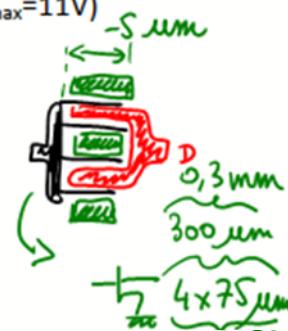Selected device size @ 15 GHz =  $4 \times 75 \mu\text{m}$  GaAs HEMT



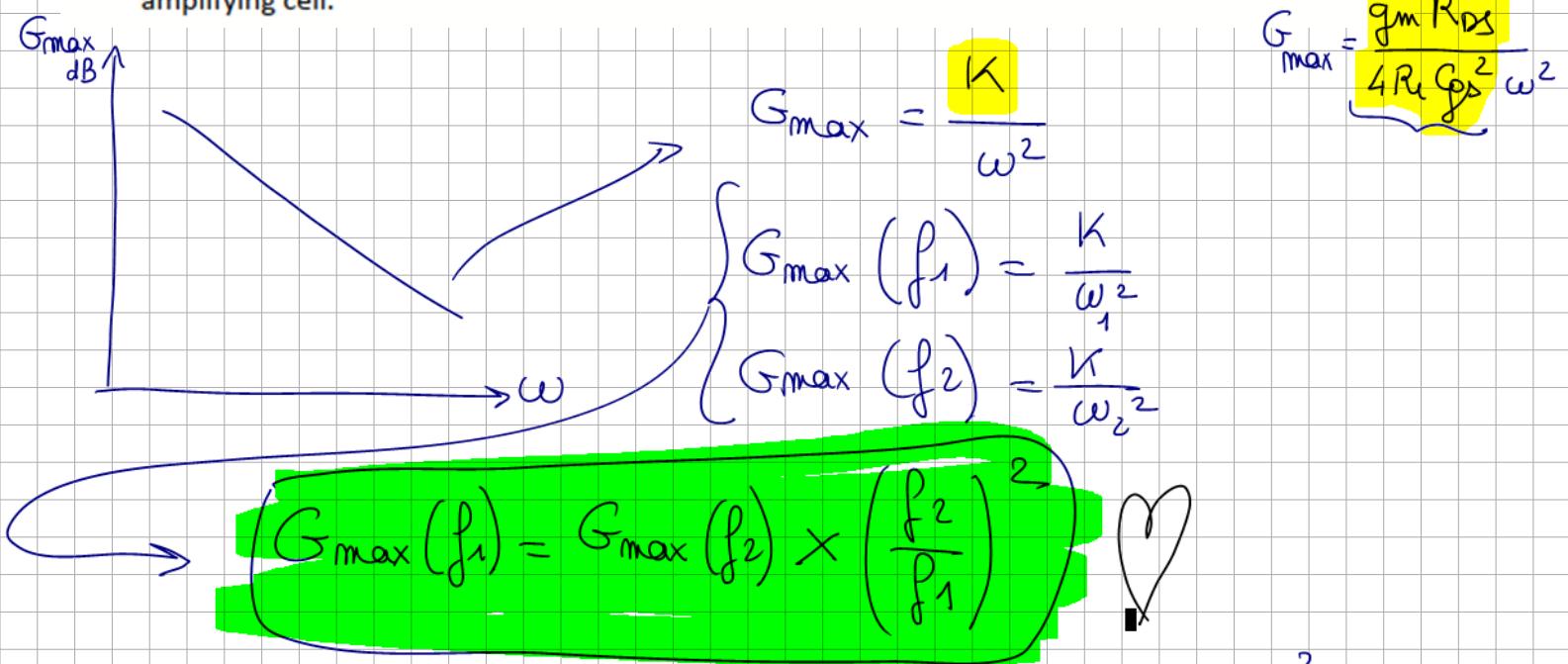- Given the required specifications and the selected transistor technology, determine the initial sizing of the power amplifier (number of stages, number of amplifying cells per stage, power gain and input/output powers of each stage) using the selected device size ( $4 \times 75 \mu\text{m}$ ) as the unitary amplifying cell.




In our case :  $G_{max}(15\text{G}) = G_{max}(10\text{G}) \times \left(\frac{10}{15}\right)^2 = 39,8 \times \left(\frac{10}{15}\right)^2 = 17,7$

$= 12,5 \text{ dB}$

$G_{max}(10\text{G}) = 16 \text{ dB} = 10^{1,6} = 39,8$

[1st case] = Optimize a stage to get  $G_{max} = 12,5 \text{ dB} = 17,7$  and  $R_{DS}$  load

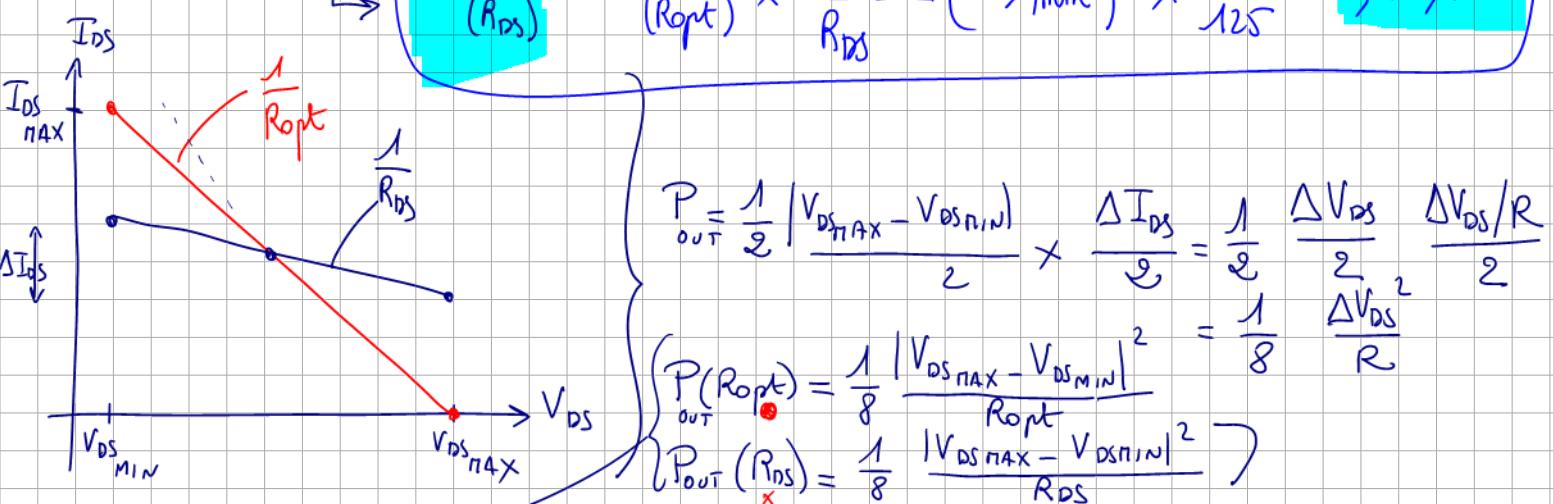$PD(R_{DS}) = PD(R_{OPT}) \times \frac{R_{OPT}}{R_{DS}} = (1 \text{ W/mm}) \times \frac{12,5}{125} = 0,1 \text{ W/mm}$





$$PD(R_{DS}) = PD(R_{opt}) \times \frac{R_{opt}}{R_{DS}}$$

gnd case Optimize a stage to get  $P_{out, MAX} \Rightarrow PD(R_{opt}) = 1 \text{ W/mm}$  and  $R_{opt, load}$

$$\cancel{\left( G_p(R_{opt}) = 4 \times \frac{R_{opt} R_{DS}}{(R_{opt} + R_{DS})^2} G_{max} \right)} = 4 \times \frac{12.5 \times 12.5}{(12.5 + 12.5)^2} \times 17.7$$

$$\cancel{\left( G_p(R_{opt}) = 5.85 = 7.7 \text{ dB} \right)}$$

① Size of Last stage

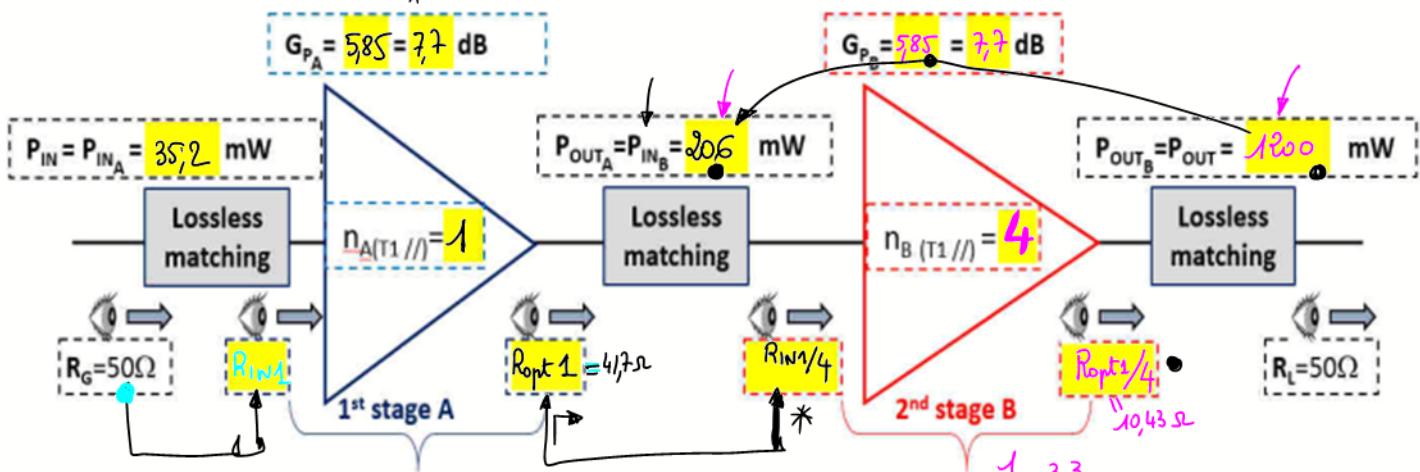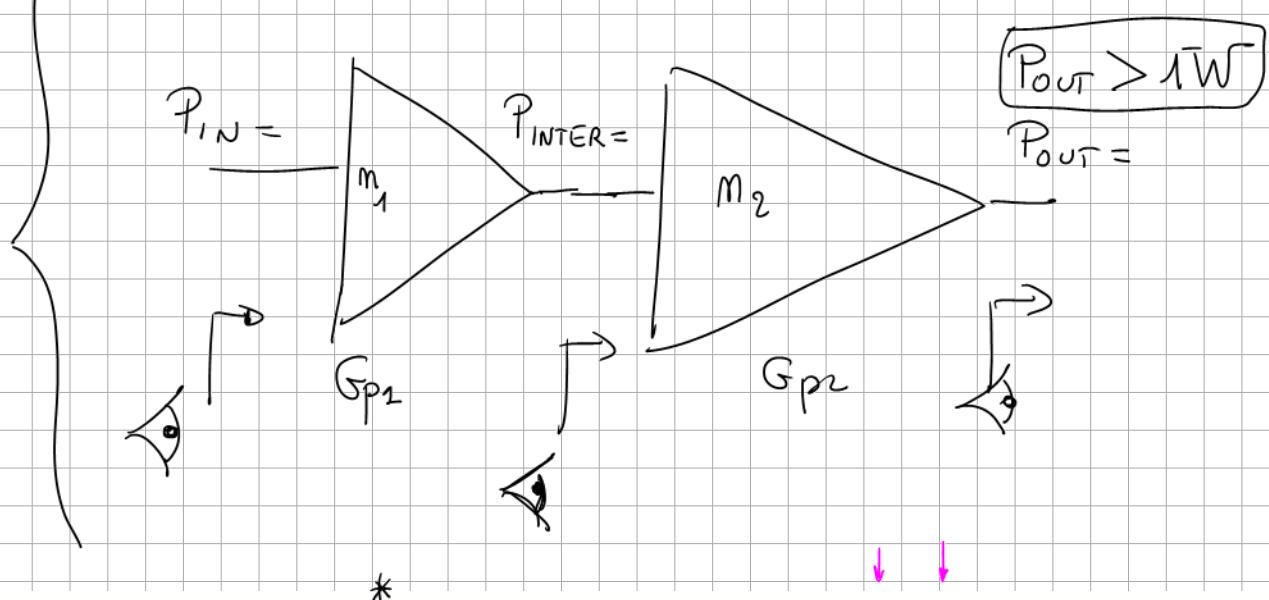

$$P_{out} > 1W$$

$$PD(R_{opt}) = 1 \text{ W/mm}$$

$$PD(R_{DS}) = 0.1 \text{ W/mm}$$

$$W_T(R_{opt}) = 1 \text{ mm} \rightarrow \text{Ineed } 4 \times 0.3 \text{ mm} = 1.2 \text{ mm}$$

$$W_T(R_{DS}) = 10 \text{ mm} \rightarrow \text{Ineed } 34 \times 0.3 \text{ mm} = 10.2 \text{ mm}$$

$$\text{each device is } 0.3 \text{ mm}$$

$$INT(\frac{10}{0.3})$$

$$R_{opt} = 125 \Omega \text{ mm} \rightarrow R_{opt1}(0.3 \text{ mm}) = \frac{125}{0.3} = 417 \Omega$$

$$\left[ \frac{R_{opt1}}{4} = \frac{417}{4} = \frac{125}{1.2} = 104.3 \Omega \right]$$

$$P_{outB} = 1.2 \text{ mm} \times PD(R_{opt}) = 1.2 \text{ mm} \times 1 \text{ W/mm} = 1.2 \text{ W}$$

$$\hookrightarrow P_{INB} = \frac{P_{outB}}{G_p(R_{opt})} = \frac{1.2 \text{ W}}{5.85} = 0.206 \text{ W} = 206 \text{ mW}$$

1st stage to reach  $206 \text{ mW}$   $\Rightarrow$  loading by  $R_{opt}$   $\rightarrow$   $PD = 1 \text{ W/mm} \rightarrow I_{need} W_{T_1} \left( \frac{0.206 \text{ W}}{1 \text{ W/mm}} \right) = 0.206 \text{ mm}$

$\hookrightarrow I_{need}$  only one device of  $0.3 \text{ mm}$

transistors in parallel are  $2^P$

$$\begin{cases} p=0 & 1 \text{ device} \\ p=1 & 2 \\ p=2 & 4 \\ \vdots & \end{cases}$$

$\Rightarrow$  if the load is  $R_{DS}$   $\rightarrow$   $PD = 0.1 \text{ W/mm} \rightarrow I_{need} W_T \left( \frac{0.206 \text{ W}}{0.1 \text{ W/mm}} \right) = 2.06 \text{ mm}$

$\hookrightarrow I_{need} \frac{2.06 \text{ mm}}{0.3 \text{ mm}} \Rightarrow 7 \text{ transistors}$   
~~not sufficient~~  
 $\Rightarrow 8 \text{ transistors} = 2^3$


$$P_{INA} = \frac{P_{outA}}{G_p(R_{opt})} = \frac{206 \text{ mW}}{5.85} = 35.2 \text{ mW}$$

To determine the input matching and interstage matching  $\rightarrow$  Calculate  $R_{IN}$

$$R_{IN} = \frac{1}{R_L G_p^2 \omega^2} \rightarrow R_{IN(1SG)} = \frac{1}{1 \times (2.7 \cdot 10^{-12} \times 2\pi \times 15 \cdot 10^9)^2} = 15.4 \Omega \text{ mm}$$

$$0.3 \text{ mm} \Rightarrow R_{IN1} = \frac{15.4 \Omega}{0.3} = 51.5 \Omega$$

$$R_{i1} = \frac{1}{0.3} = 3.33 \Omega$$

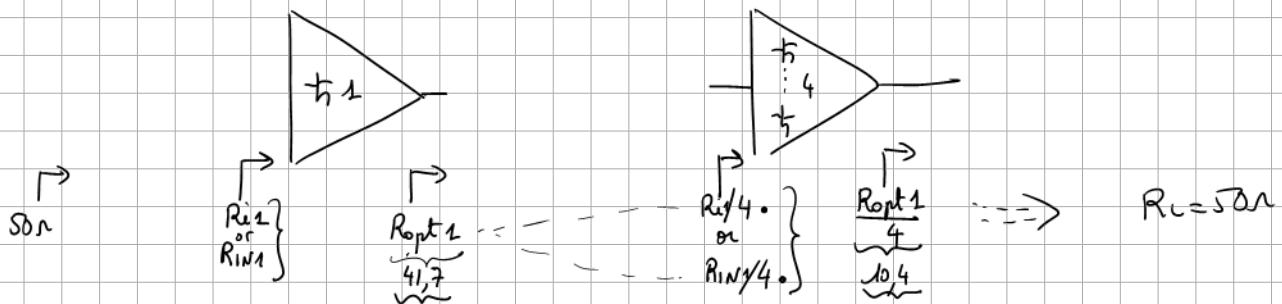

## Main specifications of the narrow-band amplifier:

Output Power  $P_{out} > 1 \text{ W}$  ; Center frequency  $f_0 = 15 \text{ GHz}$  ; Power Gain  $G_P > 15 \text{ dB}$

### Selected MMIC foundry (0.15 μm GaAs HEMT) :

Power Density PD = 1 W/mm ; Measured Gain  $G_{MAX}(10\text{GHz}) = 16 \text{ dB}$  ;

Saturated Drain Current  $I_{DS} = 800 \text{ mA/mm}$  ; Drain Voltage range ( $V_{DSmin}=1\text{V}$  and  $V_{DSmax}=11\text{V}$ )

Pinch-off Voltage :  $V_P = -4 \text{ V}$

Optimum load impedance  $R_{OPT} = 12.5 \Omega \cdot \text{mm}$

Small-signal model:  $C_{GS} = 2.7 \text{ pF/mm}$  ;  $R_i = 1 \Omega \cdot \text{mm}$  ;  $g_m = 200 \text{ mS/mm}$  ;

$R_{DS} = 125 \Omega \cdot \text{mm}$  ;  $C_{DS} = 0.6 \text{ pF/mm}$

Selected device size @ 15 GHz =  $4 \times 75 \mu\text{m} = 0.3 \text{ mm}$



### First calculations:

a) Scaled parameters for the unit size of  $[4 \times 75 \mu\text{m} = 0.3 \text{ mm}]$

$$C_{GS1} = 2.7 \text{ pF} \times 0.3 = 0.81 \text{ pF}$$

$$C_{DS1} = 0.6 \text{ pF} \times 0.3 = 0.18 \text{ pF}$$

$$R_{i1} = \frac{1}{0.3} = 3.33 \Omega$$

$$R_{DS1} = \frac{125}{0.3} = 417 \Omega$$

$$R_{OPT1} = \frac{12.5}{0.3} = 41.7 \Omega$$

$$R_{IN1} = \frac{1}{R_{i1} C_{DS1}^2 W^2} = \frac{1}{3.33 \times (0.18)^2 \times 2 \times 15 \times 10^{-9}} = 1 \Omega$$

$$\hookrightarrow R_{IN1} = 51.5 \Omega *$$

b) Power gain for optimum Power matching  $G_p(R_{opt}) @ 15 \text{ GHz}$

$$* G_{MAX}(10 \text{ GHz}) = 16 \text{ dB} = 10^{1.6} = 39.8 \rightarrow G_{MAX}(15 \text{ GHz}) = G_{MAX}(10 \text{ GHz}) \times \left(\frac{10}{15}\right)^2 = 39.8 \times \left(\frac{10}{15}\right)^2 = 13.7 = 12.5 \text{ dB}$$

$$\text{given } \left( G_p(R_{opt}) = 4 \times \frac{R_{DS} \cdot R_{opt}}{(R_{DS} + R_{opt})^2} G_{MAX} \right) \rightarrow G_p(15 \text{ GHz}) = 4 \times \frac{125 \times 12.5}{(125 + 12.5)^2} \times 13.7 = 5.85 = 7.7 \text{ dB}$$

c) Power density for maximum gain matching PD( $R_{DS}$ )

$$PD(R_{DS}) = PD(R_{opt}) \times \frac{R_{opt}}{R_{DS}} = (1 \text{ W/mm}) \times \frac{12.5 \Omega \cdot \text{mm}}{125 \Omega \cdot \text{mm}} \Rightarrow PD(R_{DS}) = 0.1 \text{ W/mm}$$

( $P_{out} > 1 \text{ W}$ )

Power specifications  $\rightarrow 2^{\text{nd}}$  stage dimensions

STAGE B

• 2<sup>nd</sup> stage loaded by  $R_{opt}$   $\Rightarrow PD(R_{opt}) = 1 \text{ W/mm}$   $\left\{ \begin{array}{l} \text{Size}_B > \frac{1 \text{ W}}{1 \text{ W/mm}} = 1 \text{ mm} \\ P_{out} > 1 \text{ W} \end{array} \right.$

$$\rightarrow M_B = 4$$

$$\rightarrow P_{outB} = (4 \times 0.3 \text{ mm}) \times 1 \text{ W/mm} = 1.2 \text{ W}$$

Possible sizes  
 $N=1 \rightarrow 0.3 \text{ mm}$ ,  
 $N=2 \rightarrow 0.6 \text{ mm}$ ,  
 $N=4 \rightarrow 1.2 \text{ mm}$ ,  
 $N=8 \rightarrow 2.4 \text{ mm}$ ,  
 $N=16 \rightarrow 4.8 \text{ mm}$

$$\rightarrow G_{PB} = G_p(R_{opt}) = 5.85 = 7.7 \text{ dB}$$

$$\rightarrow P_{INB} = P_{outA} = \frac{P_{outB}}{G_{PB}} = \frac{1.2 \text{ W}}{5.85} = 0.205 \text{ W}$$

STAGE A

• 1<sup>st</sup> stage loaded by  $R_{opt}$   $\Rightarrow PD(R_{opt}) = 1 \text{ W/mm}$   $\left\{ \begin{array}{l} \text{Size}_A > \frac{0.205 \text{ W}}{1 \text{ W/mm}} = 0.205 \text{ mm} \\ P_{out} > 0.205 \text{ W} \end{array} \right.$

$$\rightarrow M_A = 1$$

$$\rightarrow P_{outA} = 0.205 \text{ W} \quad \cancel{= 0.3 \text{ W}}$$

$$P_{IN} = 35 \text{ mW}$$

$$G_{PA} = 7.7 \text{ dB} = 5.85$$

$$R_G = 50 \Omega$$

$$P_{INTER} = 205 \text{ mW}$$

$$G_{PB} = 7.7 \text{ dB} = 5.85$$

$$R_{i1} = 3.33 \Omega$$

$$R_{IN1} = 51.5 \Omega$$

$$P_{outB} = 1.2 \text{ W}$$

$$R_{L1} = 50 \Omega$$




$$R_{opt1} = 41.7 \Omega$$

$$R_{IN1/4} = 0.83 \Omega$$

$$R_{IN1/4} = 12.9 \Omega$$

$$\rightarrow G_{PA} = G_p(R_{opt}) = 5.85 = 7.7 \text{ dB}$$
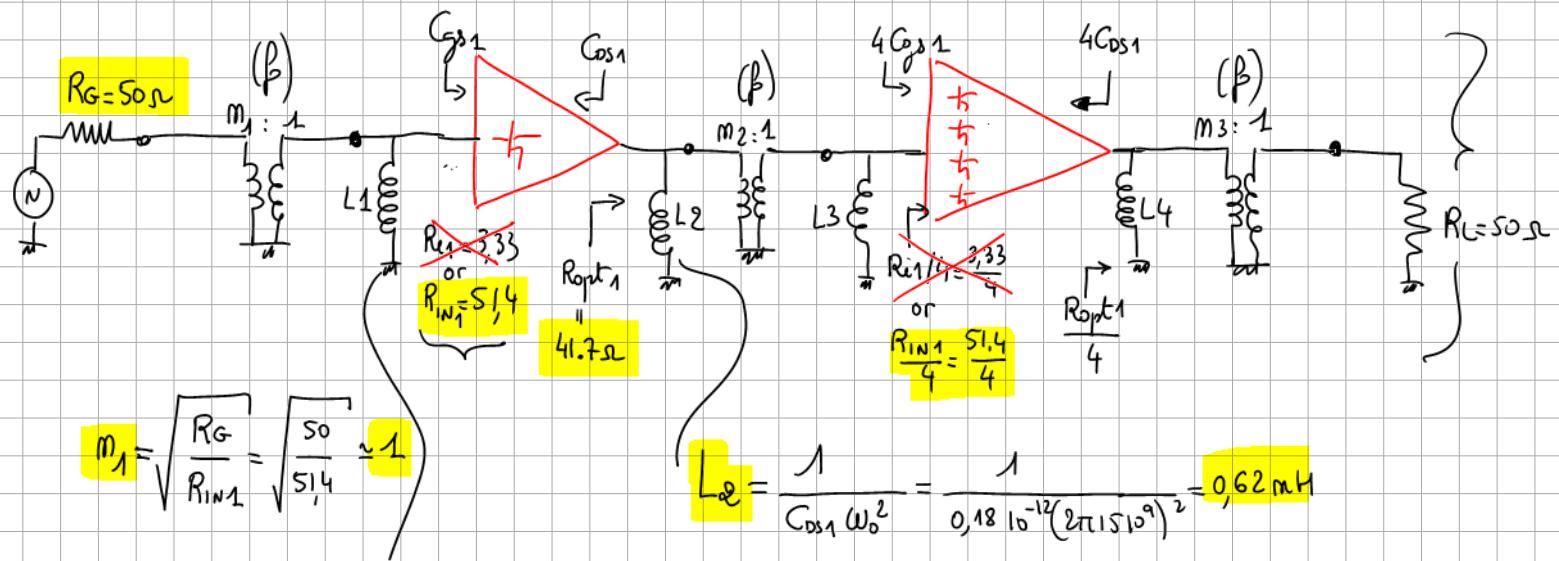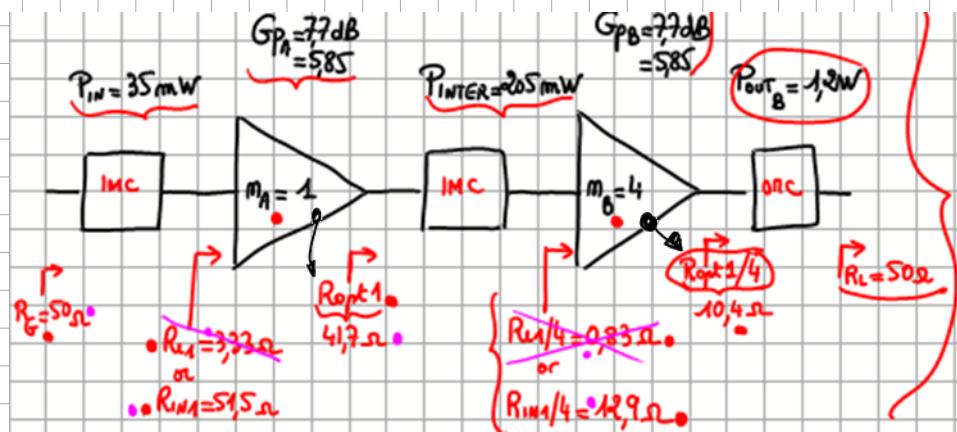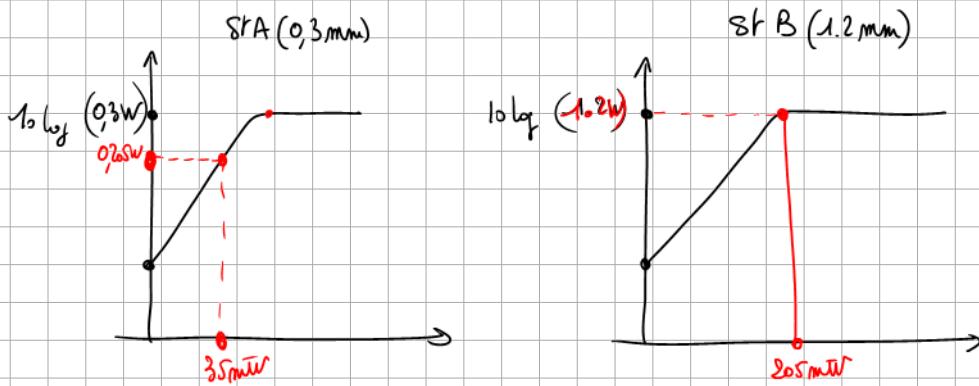
$$\rightarrow P_{INA} = \frac{P_{outA}}{G_{PA}} = \frac{0.205}{5.85} = 35 \text{ mW}$$



$$M_1 = \sqrt{\frac{R_G}{R_{IN1}}} = \sqrt{\frac{50}{51.4}} \approx 1$$

$$L_2 = \frac{1}{C_{GS1} \omega_0^2} = \frac{1}{0.18 \cdot 10^{-12} (2\pi \cdot 15 \cdot 10^9)^2} = 0.62 \text{ mH}$$

$$L_1 = \frac{1}{C_{GS1} \omega_0^2} = \frac{1}{0.81 \cdot 10^{-12} (2\pi \cdot 15 \cdot 10^9)^2} = 0.14 \text{ mH}$$

$$M_2 = \sqrt{\frac{R_{opt1}}{\left(\frac{R_{IN1}}{4}\right)}} = \sqrt{\frac{41.7}{51.4}} = 1.8 \rightarrow L_3 = \frac{1}{(4C_{GS1})\omega_0^2} = \frac{L_1}{4} = 0.035 \text{ nH}$$

$$L_4 = \frac{1}{(4C_{GS1})\omega_0^2} = \frac{L_2}{4} = 0.156 \text{ mH}$$


$$M_3 = \sqrt{\frac{R_{opt1}}{R_L}} = \sqrt{\frac{\left(\frac{41.7}{4}\right)}{50}} = 0.46$$

3) Q does not depend on  $\omega_0$

$$\left. \begin{array}{l} \text{maximum value} \\ \downarrow \\ \text{Bandwidth} \end{array} \right\} \quad \left. \begin{array}{l} Q_{IN} = \frac{1}{R_{i1} C_{D1} \omega_0} = R_{IN1} C_{D1} \omega_0 = 51,5 \times 0,81 \cdot 10^{-12} \times 2\pi 15 \cdot 10^9 \\ \Rightarrow Q_{IN}(15 \text{ GHz}) = 3,9 \\ * Q_{OUT}(R_{opt2}, 15 \text{ GHz}) = R_{opt2} \times C_{DS1} \times \omega_0 = 41,7 \times 0,18 \cdot 10^{-12} \times 2\pi 15 \cdot 10^9 \\ \rightarrow Q_{OUT}(R_{DS1}, 15 \text{ GHz}) = R_{DS1} \times C_{DS1} \times \omega_0 = 41,7 \times 0,18 \cdot 10^{-12} \times 2\pi 15 \cdot 10^9 \\ = 7 \end{array} \right.$$

$$Q = \frac{\omega_0}{\Delta\omega} \rightarrow \Delta f = \frac{f_0}{Q}$$

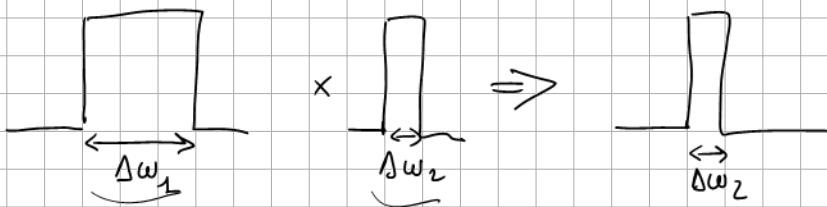The limiting factor of the maximum achievable bandwidth is  $Q_{MAX}$



In our case stage 1  $\rightarrow R_{opt}$   
stage 2  $\rightarrow R_{opt}$

$Q_{IN} = 3,9$  ← limiting factor  $Q_{MAX}$

$$Q_{OUT}(R_{opt}) = 0,7$$


$$\Delta f_{max} < \frac{f_0}{Q_{MAX}} = \frac{15G}{3,9} = 3,8 \text{ GHz}$$

was not asked


in another case

$$\left. \begin{array}{l} \text{stage 1} \rightarrow R_{DS} \\ \text{stage 2} \rightarrow R_{opt} \end{array} \right\} \Rightarrow \left\{ \begin{array}{l} Q_{IN} = 3,9 \\ Q_{OUT}(R_{opt}) = 0,7 \\ Q_{OUT}(R_{DS}) = 7 \end{array} \right.$$

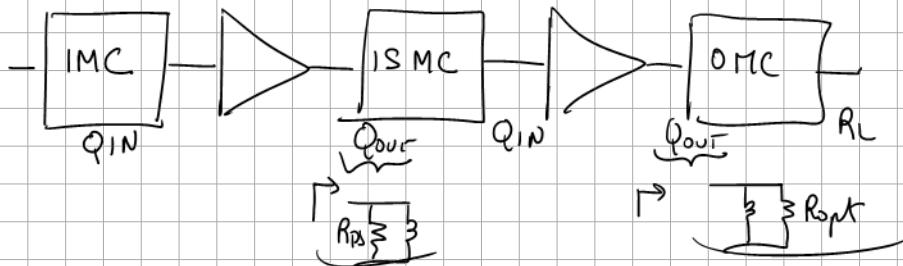
$$\Delta f_{max} < \frac{f_0}{Q_{MAX}} = \frac{15G}{7} = 2,1 \text{ GHz}$$



4)

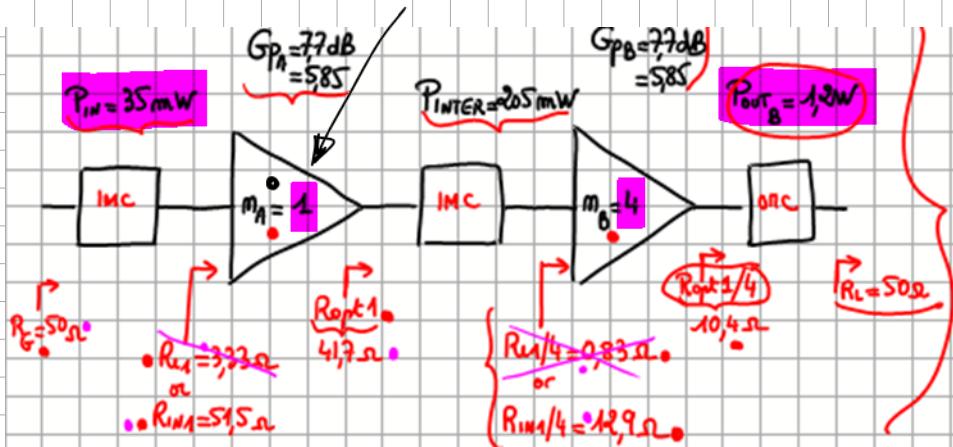

Class A

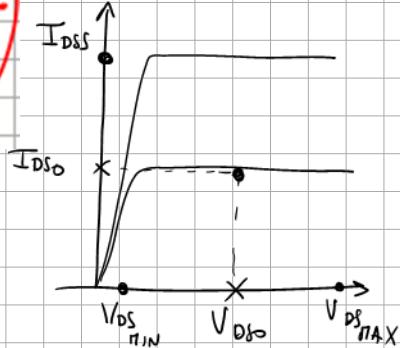

$$V_{DSS_0} = \frac{V_{DS_{MIN}} + V_{DS_{MAX}}}{2} = \frac{1 + 11}{2} = 6 \text{ V}$$

$$I_{DSS_0} = \frac{I_{DS_{MAX}}}{2} = \frac{(800 \text{ mA/mm}) \times (0.3 \text{ mm})}{2} = 120 \text{ mA} \leftarrow \text{for one transistor of } 0.3 \text{ mm size}$$

$$\rightarrow P_{DC} = (4+1) \times V_{DSS_0} \times I_{DSS_0} = 5 \times 6 \times 120 \text{ mA} = 3.6 \text{ W}$$

$$P_{IN} = 35 \text{ mW}$$

$$P_{out} = 1.2 \text{ W}$$

$$R_{opt_A} = R_{opt_B}$$

$$PAE = \frac{P_{out} - P_{IN}}{P_{DC}} = \frac{1.2 - 0.035}{3.6} = 32\%$$

0

