



Basics of Active and Nonlinear High-Frequency Electronics



UNIVERSITÀ
DEGLI STUDI
DI BRESCIA



Module Title

Date

- 1 -


Copyright notice : This material can be freely used within the E.M.I.M.E.O. Erasmus Mundus consortium. Explicit authorisation of the authors is required for its use outside this E.M.I.M.E.O. consortium. This learning Programme has been funded with support from the European Commission. This publication reflects the views only of the author, and the Commission cannot be held responsible for any use which may be made of the information contained therein.

Basics of Active and Nonlinear High-Frequency Electronics

- ❑ Chapter I : Introduction to active high-frequency circuits in communication systems
- ❑ Chapter II : Introduction to the Non-linear Electrical Modeling of microwave transistors
- ❑ Chapter III : Design method of narrow-band power amplifiers
- ❑ Chapter IV : Architectures of high-frequency mixers
- ❑ Chapter V : Architectures of wideband resistive and distributed power amplifiers
- ❑ Chapter VI : Architectures of non-linear active circuits controlled by cold HEMTs


Chapter II :

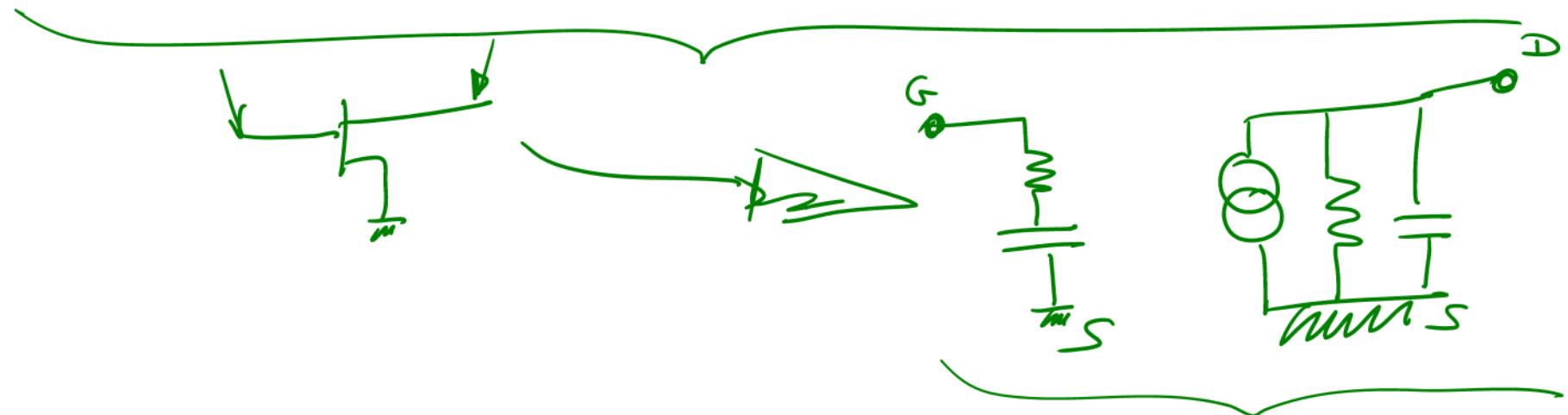Introduction to the Non-linear Electrical Modeling of microwave transistors



High-frequency Pulsed Measurement Systems

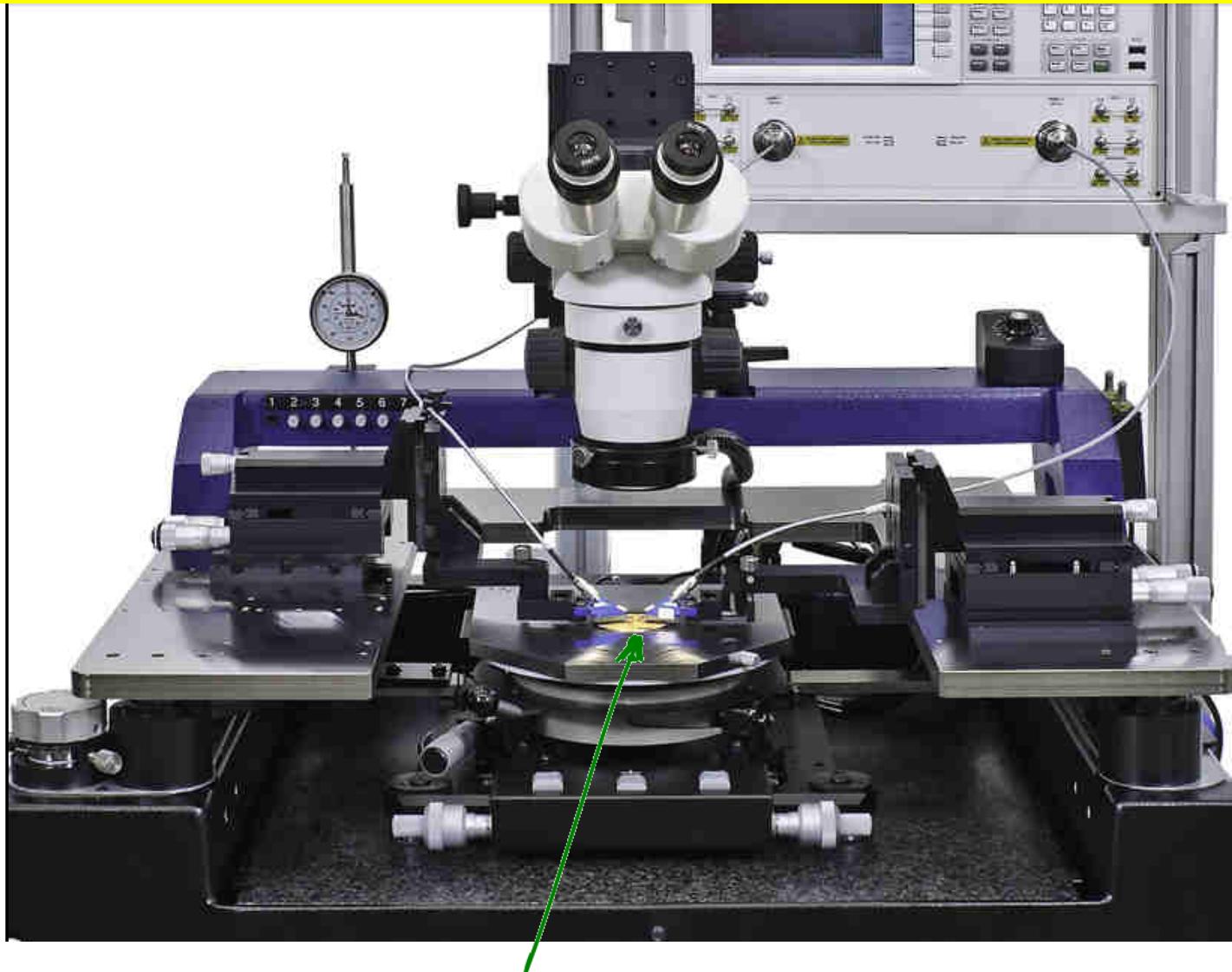{ On-wafer Probing Stations
for RF/Microwave circuits







DUT

Device Under Test
- small die (chip)
- partial or whole wafer


Wafer chuck
- to hold in place the wafer
- to heat or cool it

Anti- Vibration
Table

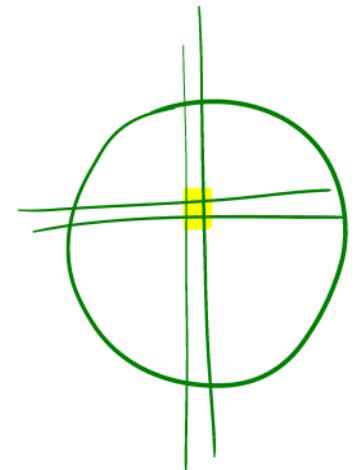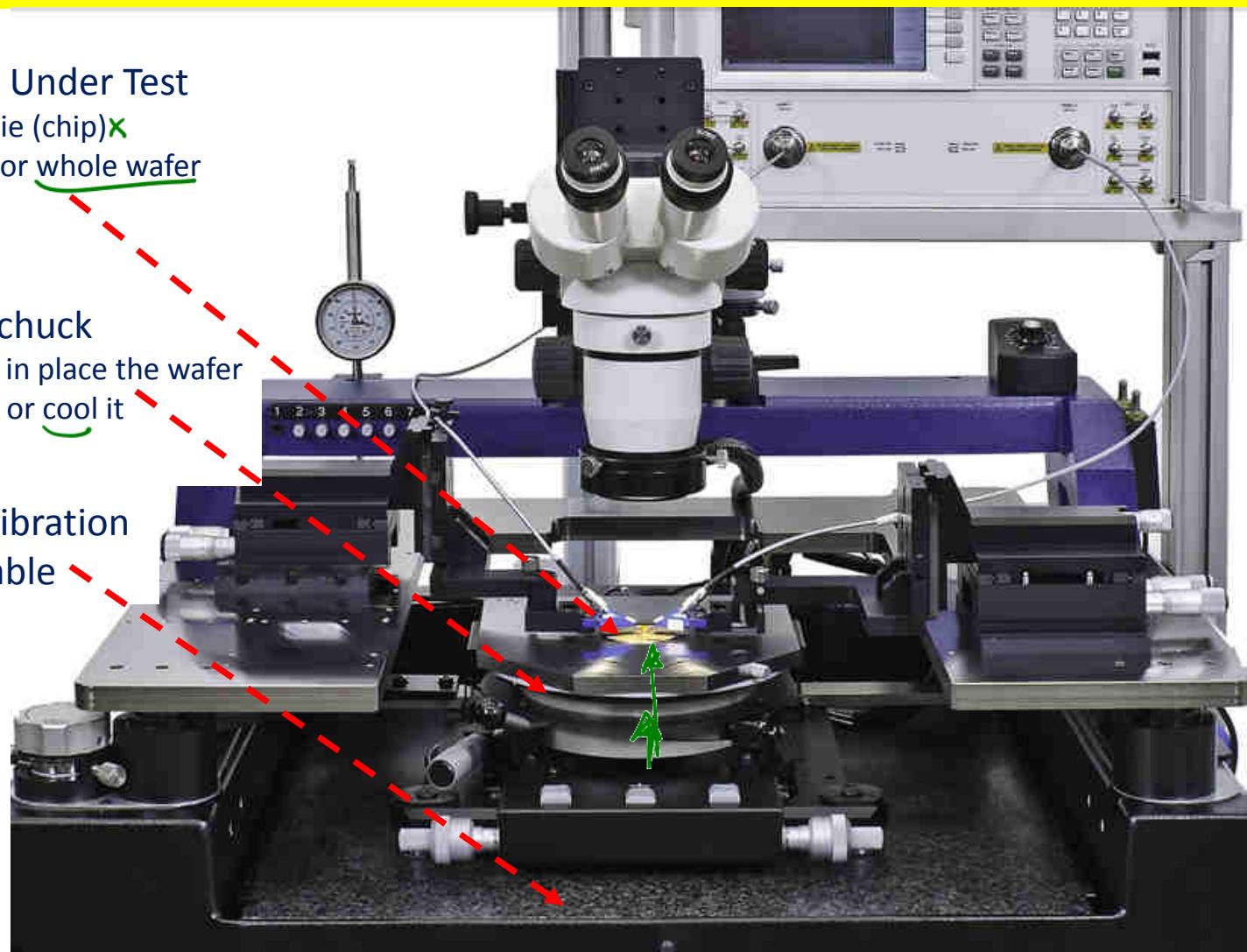


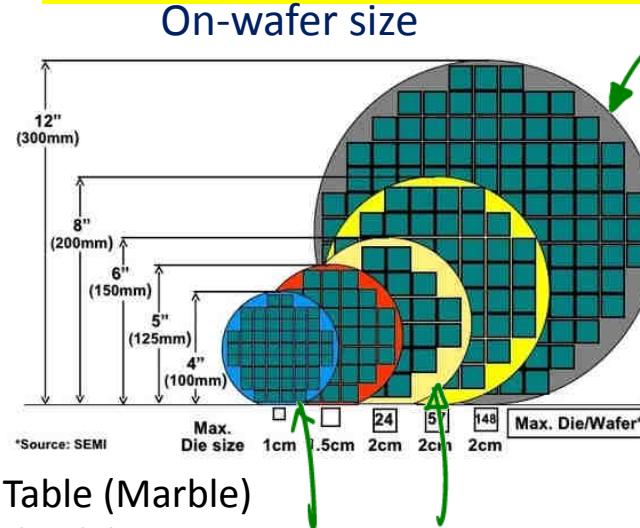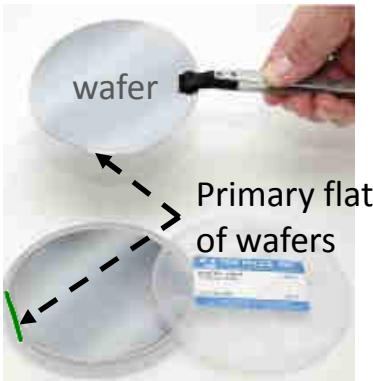

On-wafer test and sorting


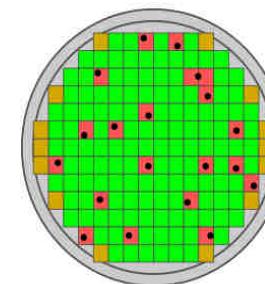


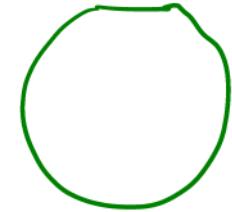- - defect
- - defective die
- - good die
- - partial edge die



Vibration Isolation Table (Marble)

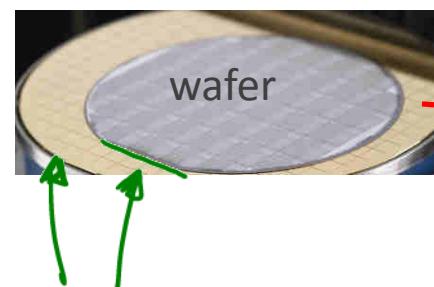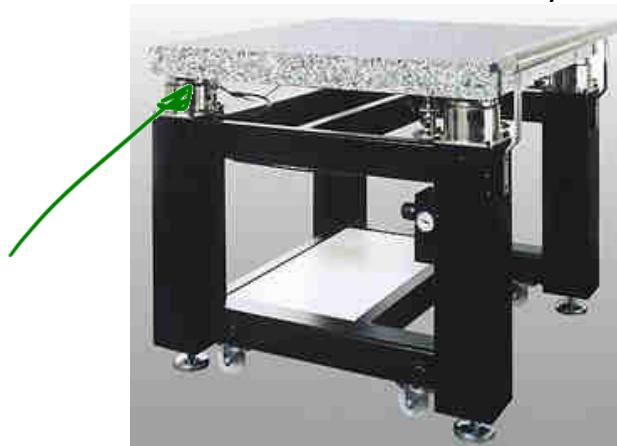
- keep high mechanical stability
- reliable sub-micron stability




Wafer Chuck → Thermal chuck (-60°C → 300°C)


Thermal enclosure

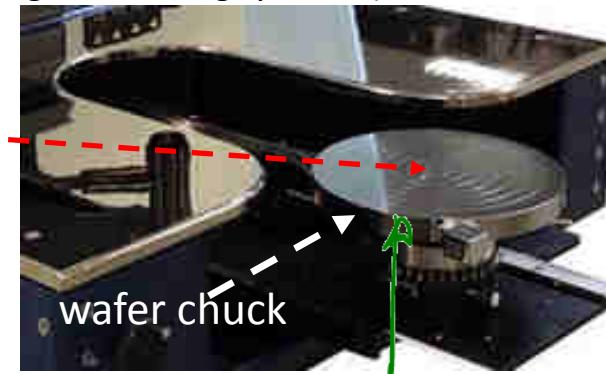- hold wafers in place while they are being probed
- apply a small amount of vacuum to the wafer backside
- can hold small die and partial or whole wafer
- cooling and heating systems (air flow conditioning)




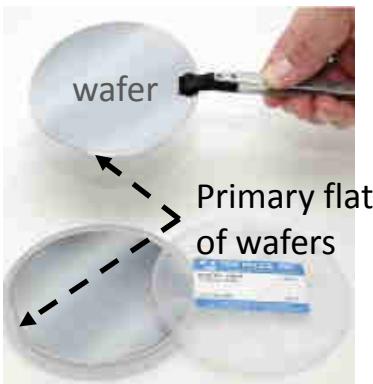




On-wafer size

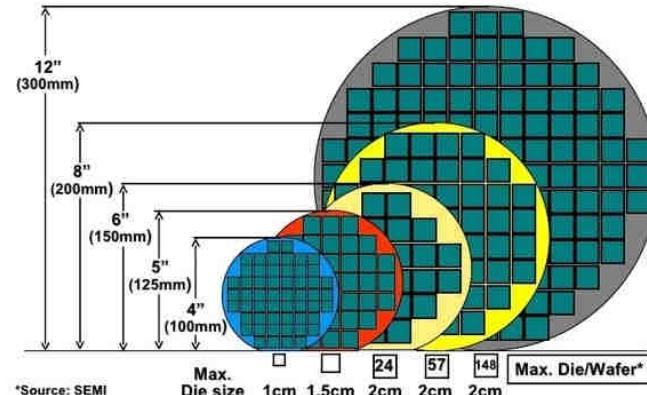


On-wafer test and sorting

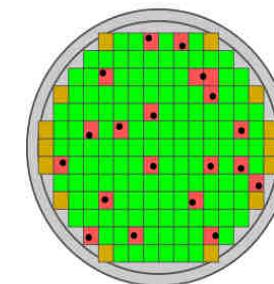


Front side of the wafer

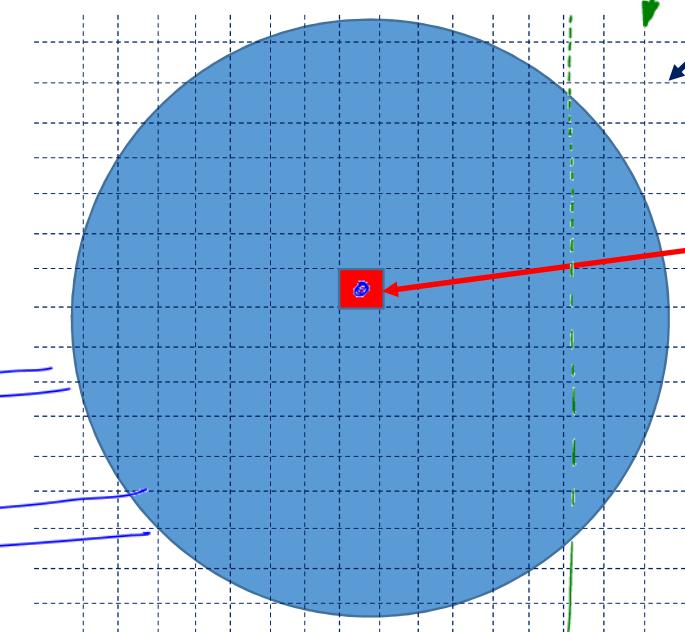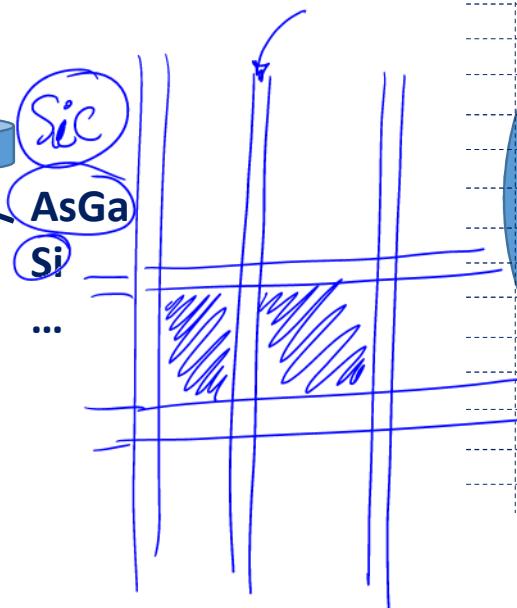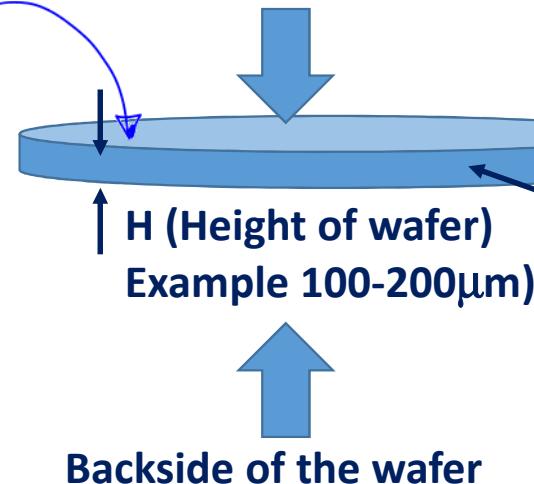



On-Wafer Probing

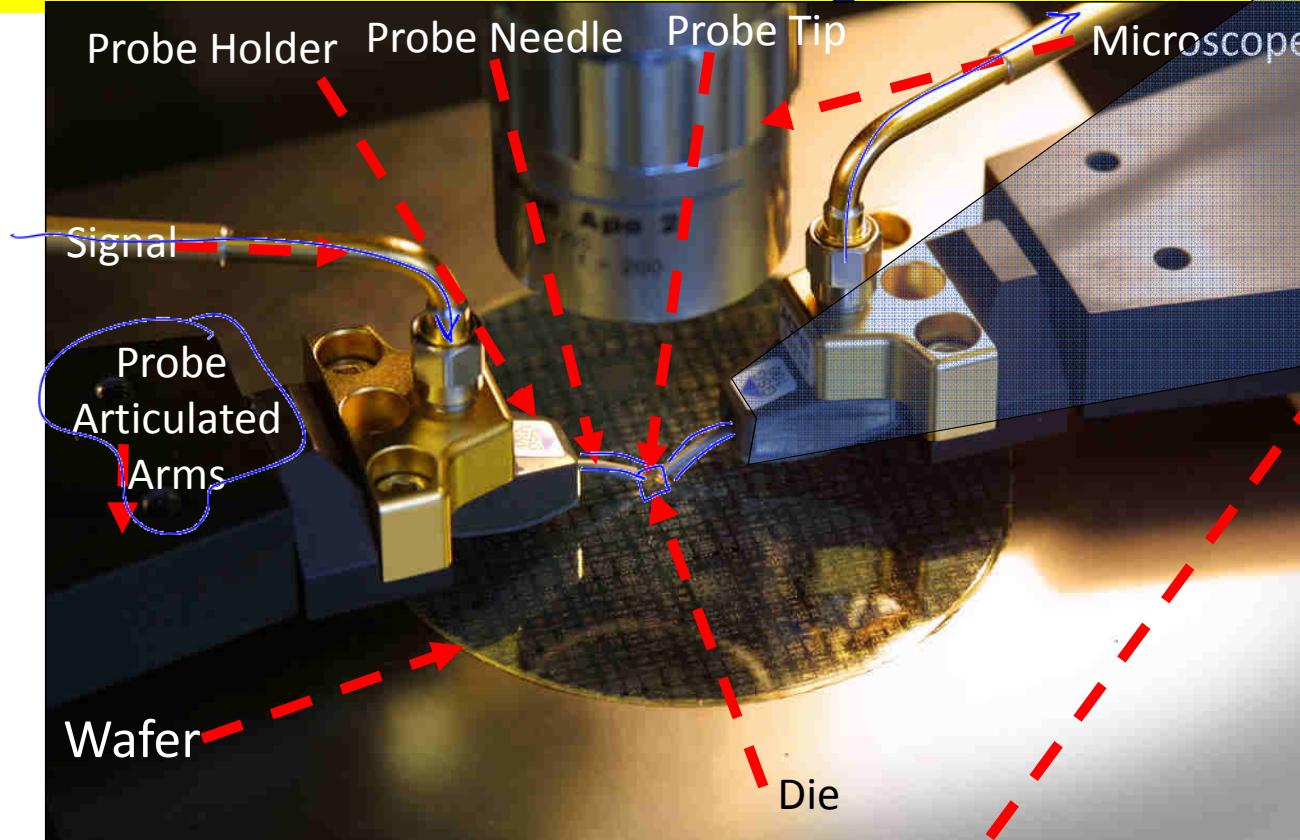


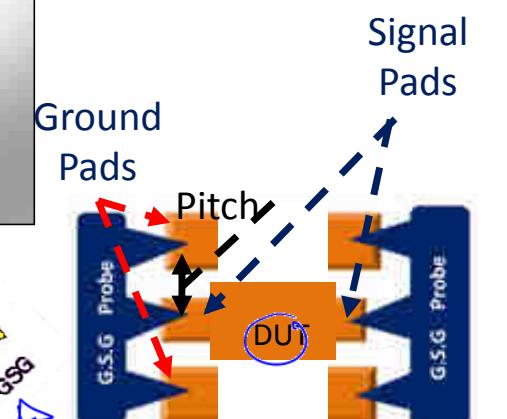
GSG is the most common type of RF probe.
Many standard pitches



GSG probes

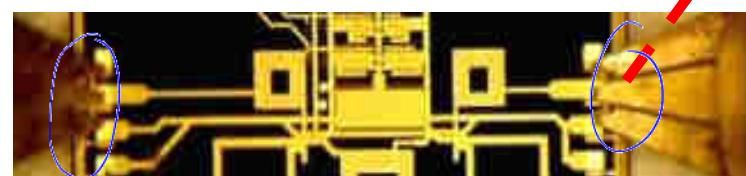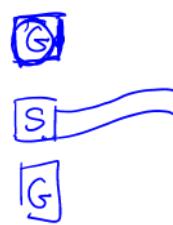


On-Wafer Probing

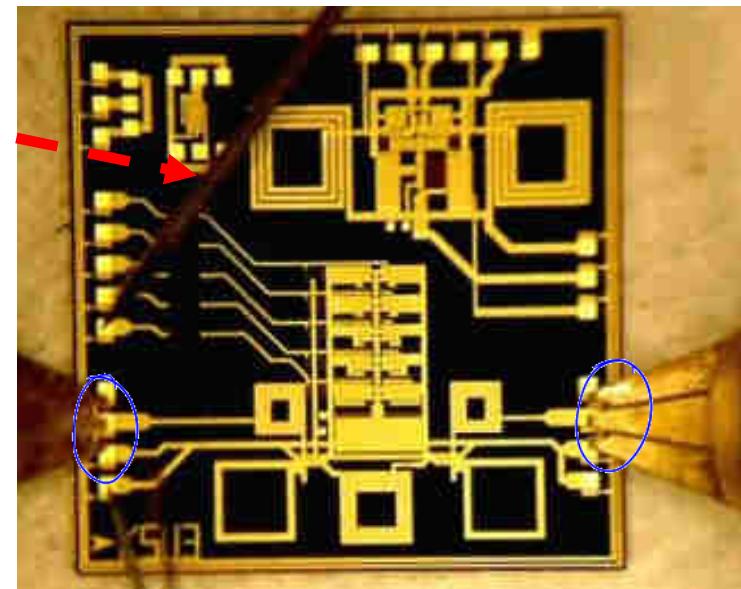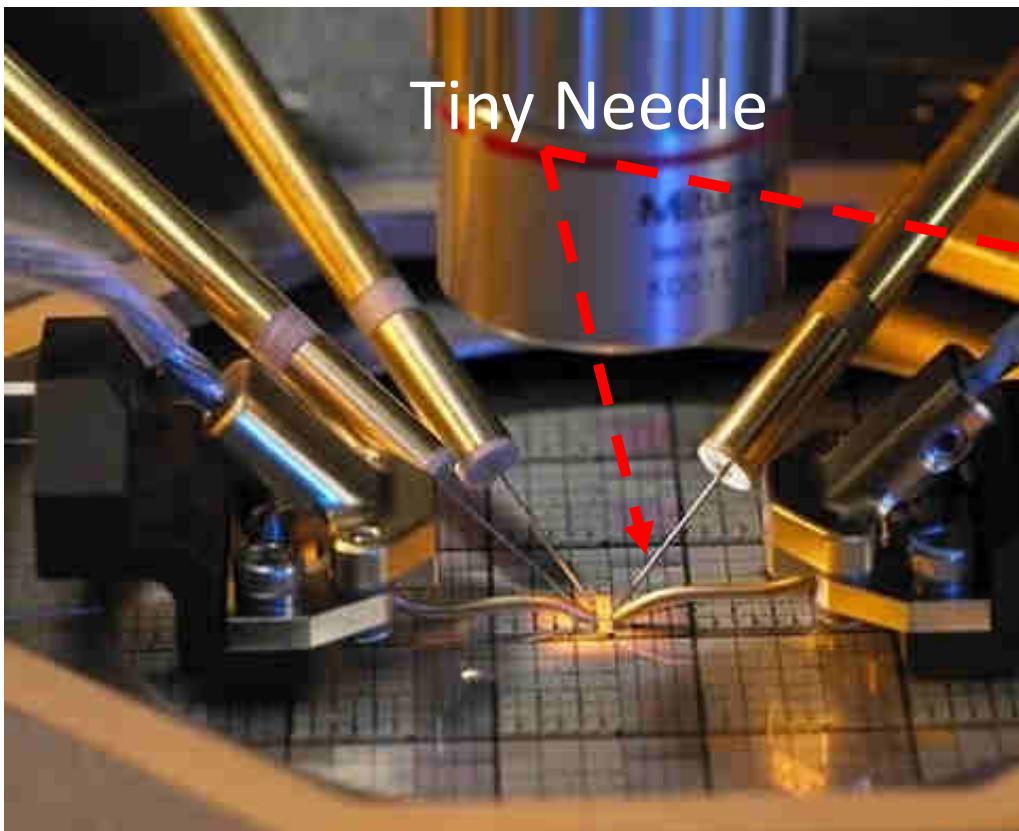

HF probe stations On-wafer Probing System

Microscope

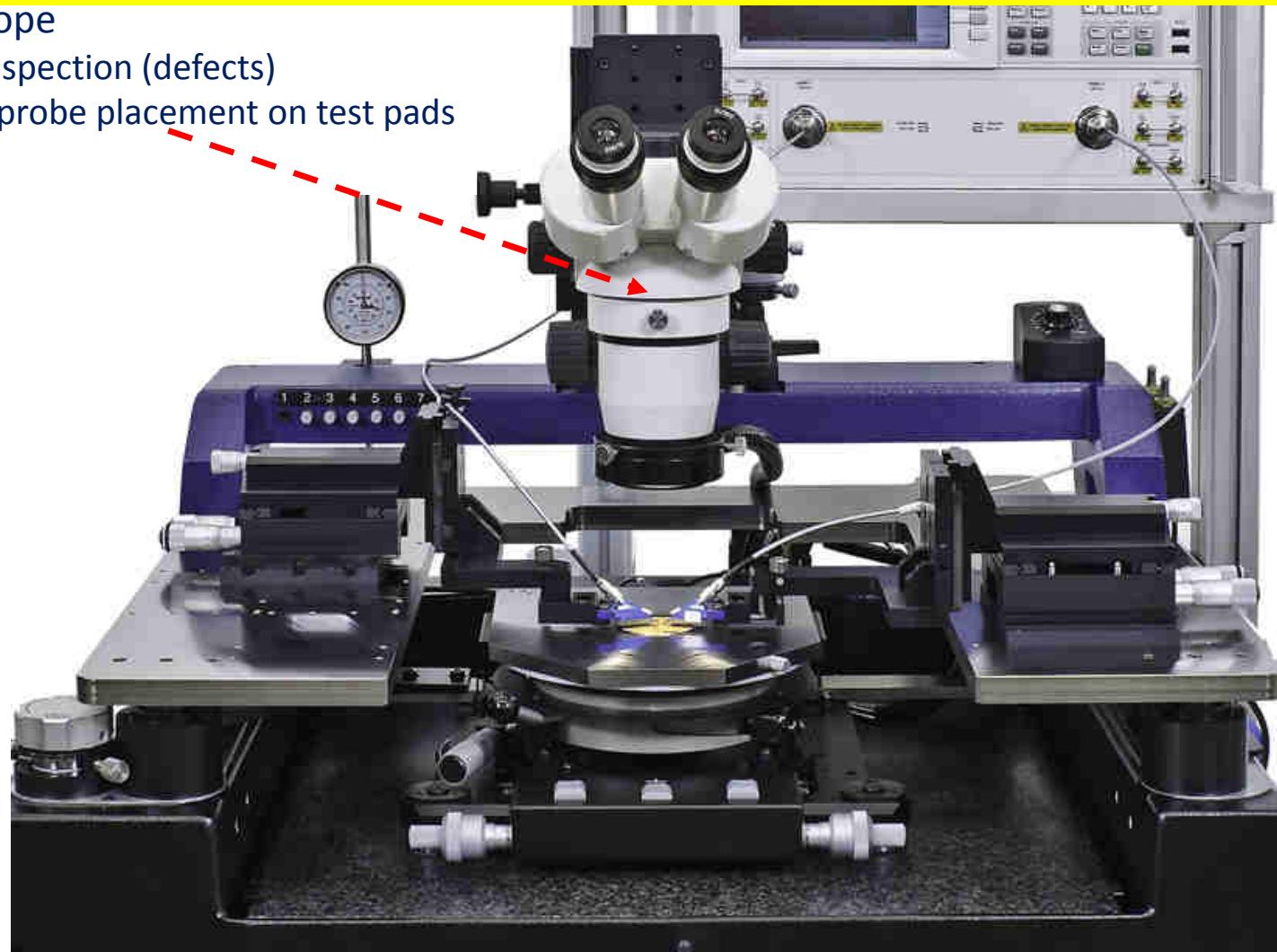
- ➊ wafer inspection (defects)
- ➋ precise probe placement on test pads



HF probe stations On-wafer Probing System

Micropositioners

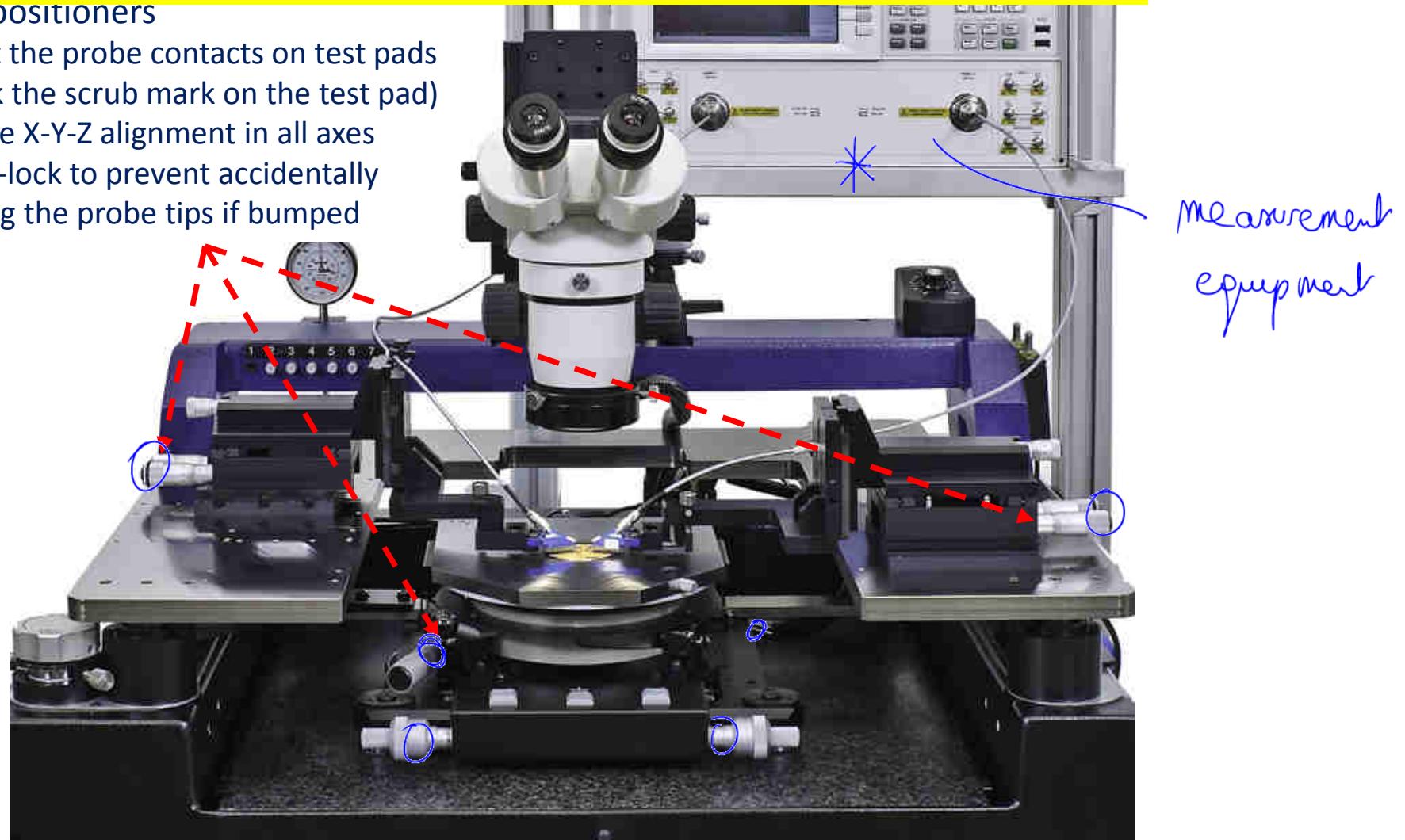- adjust the probe contacts on test pads
(check the scrub mark on the test pad)
- precise X-Y-Z alignment in all axes
- screw-lock to prevent accidentally moving the probe tips if bumped





Micropositioner of probe tips




HF probe stations On-wafer Probing System

Microwave Probes

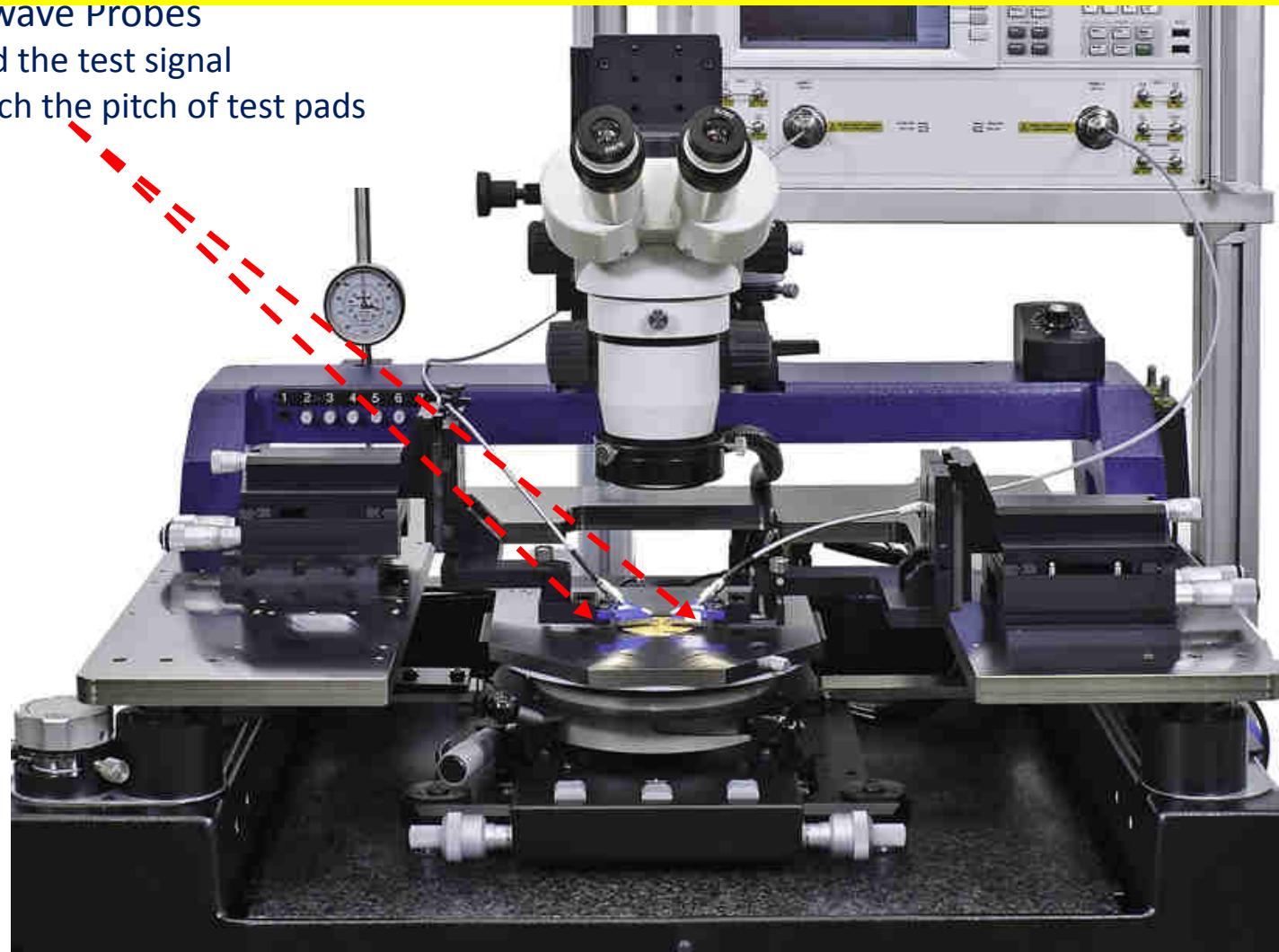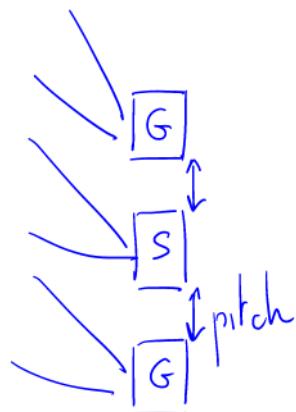- Feed the test signal
- Match the pitch of test pads



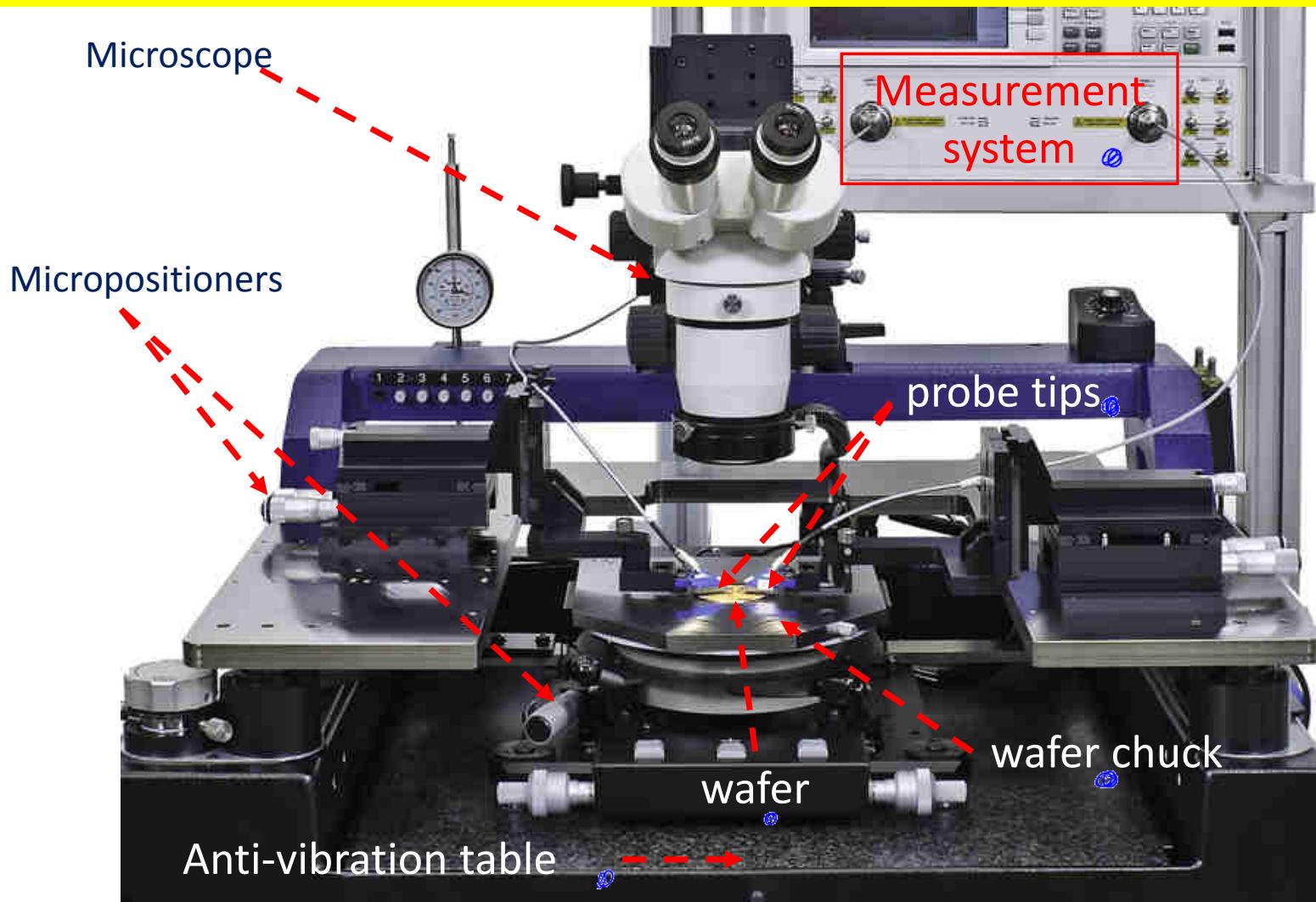HF probe stations On-wafer Probing System



I – Basics of MESFET operation

$\text{HEMT} \Rightarrow$ Same model topology

* Low-Frequency Bipolar transistors are based on the well-known PN Junction (P-type-SC / N-type-SC)

* High-Frequency MESFET (MEtal Semiconductor Field Effect Transistor) based on Schottky Junction (Metal / N-type-SC)

HEMT


→ Simplified planar representation of FETs

→ I-V transfer characteristic (Ohmic & Saturated regions, Diode conduction, Breakdown & Pinch-off voltages)



→ Localization of electrical equivalent elements that gives the nonlinear electrical model

→ Successive simplification to derive the simplified linear electrical FET model *

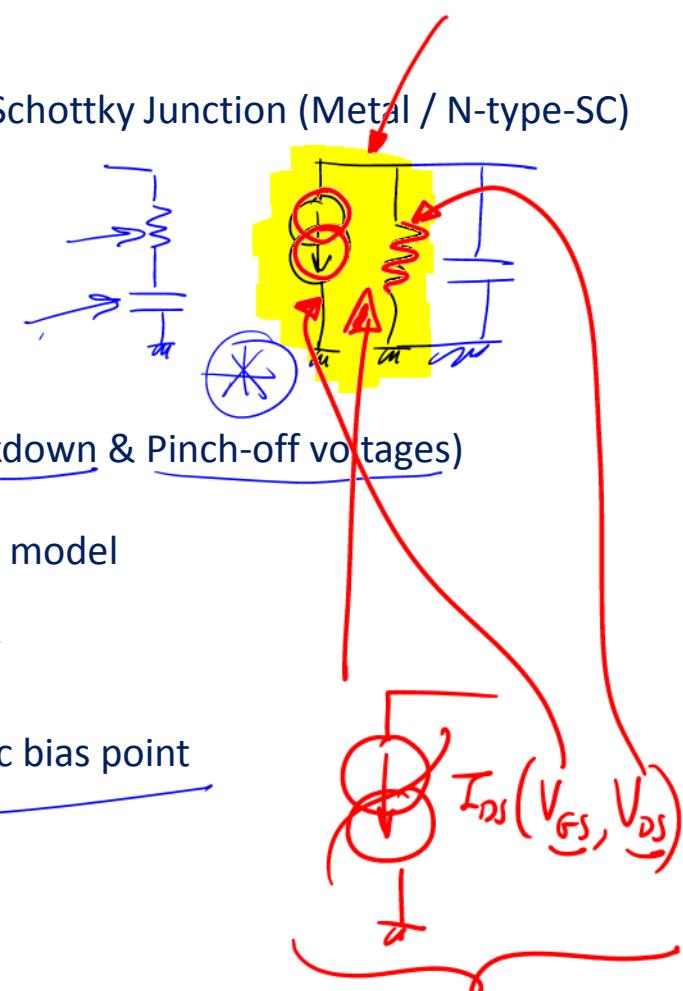→ Small-signal equivalent of the nonlinear drain current (g_m , g_d) around a specific bias point



ohmic contact

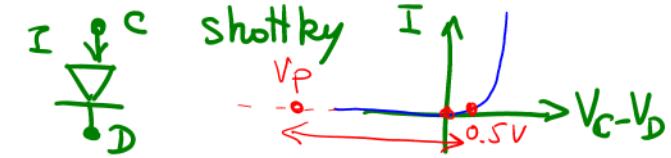
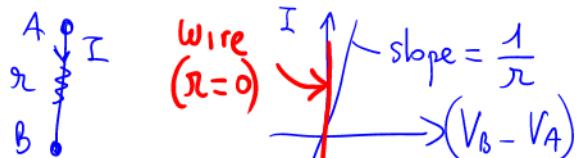


EMI MEO

E(rasmus) Mundus on Innovative Microwave Electronics and Optics

I – Basics of MESFET operation

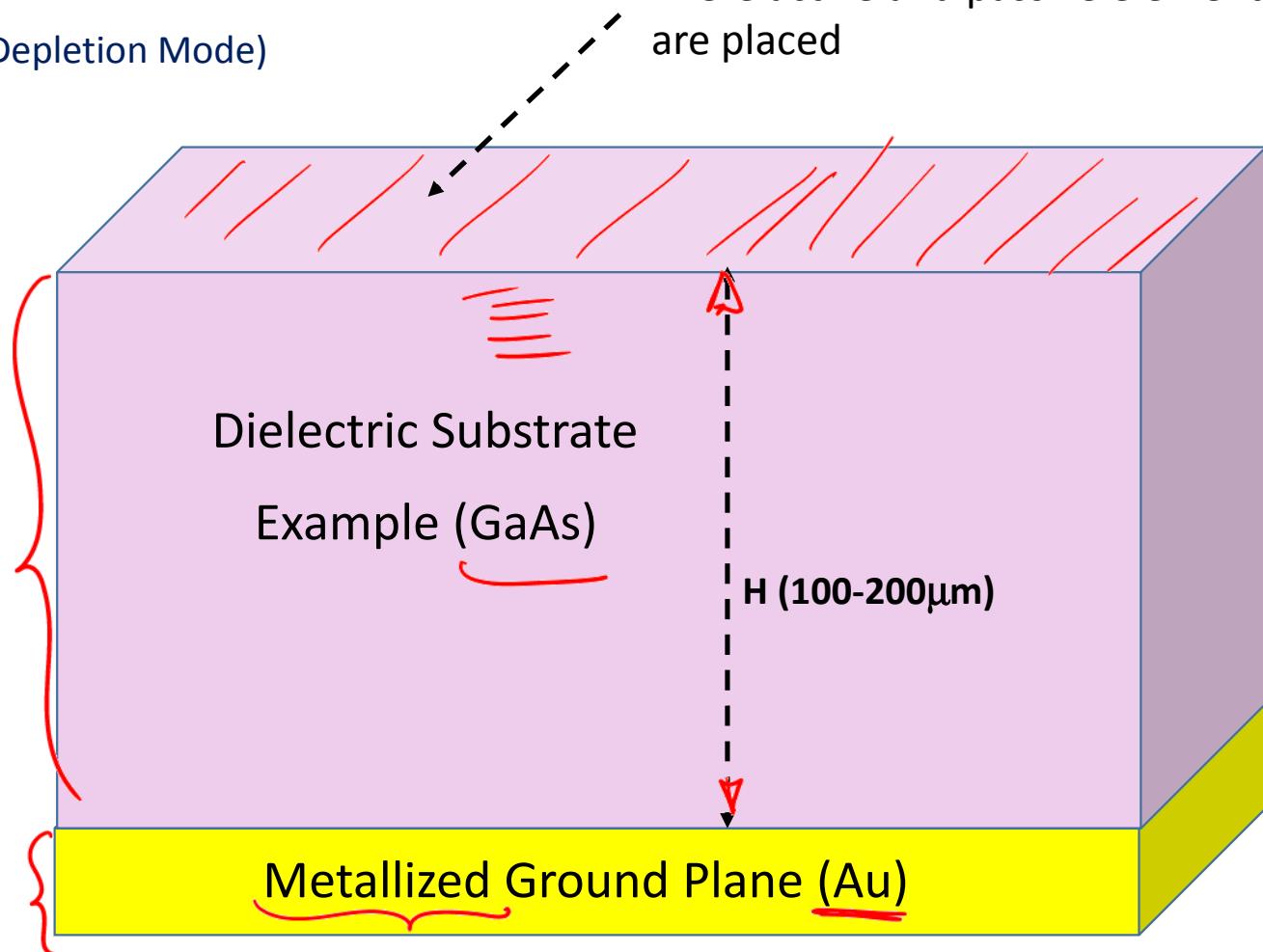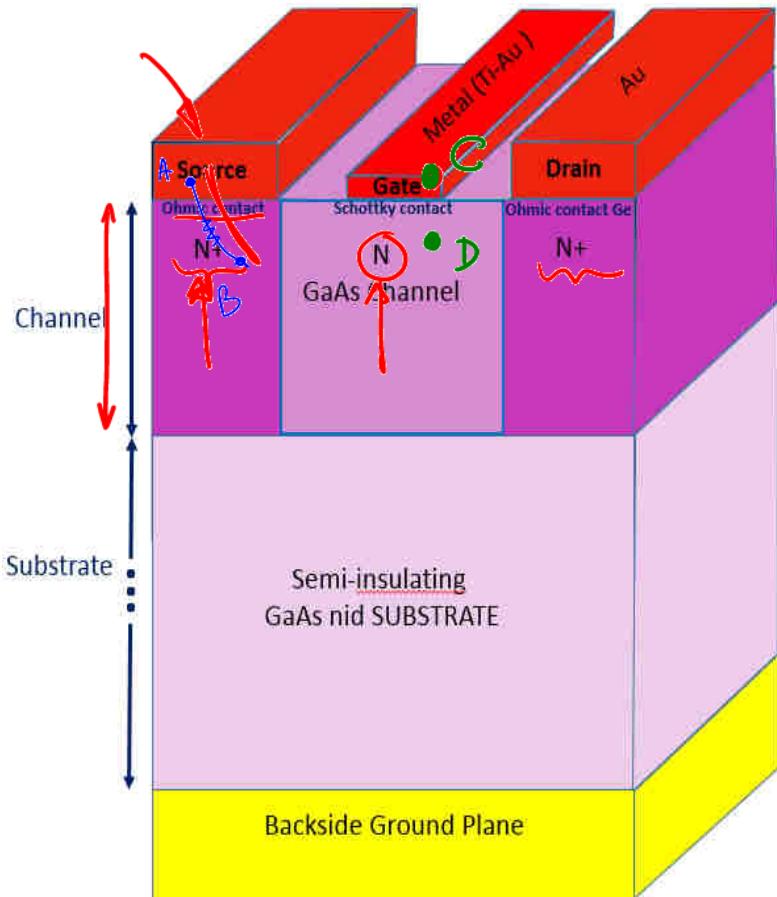→ Simplified planar representation of FETs (Depletion Mode)



Operating principles (FET / HEMT)

■ **FET** → Gate voltage controls the flow of drain current by modifying the available section W of the doped channel (Impurities, Ionized scattering → Low mobility)

→ Schottky Junction (Metal / SC_N channel) in reverse mode



■ **HEMT** → Gate voltage controls the flow of drain Current by modifying the carrier density n_s of a 2DEG in the undoped channel (no impurities → Very high mobility)

The (two-dimensional Electron Gas) **2DEG** is located at the **heterojunction** between a **wide bandgap semi-conductor (AlGaN)** and a **narrow bandgap semi-conductor (GaN)**.


The electrons of the 2 DEG are free to move in a two-dimensional plane (x,z)
but tightly confined in the 3rd dimension (y)

because they are trapped in a potential well created at the heterojunction surface


→ heterostructure (Wide bandgap SC / Narrow bandgap SC) 

I – Basics of MESFET operation

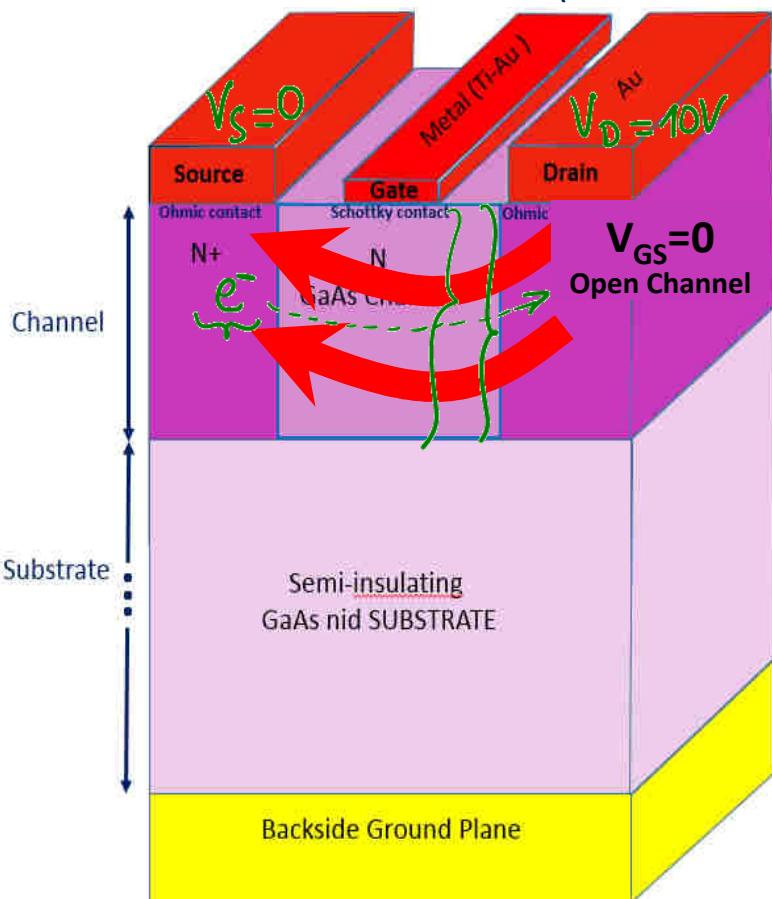→ I-V transfer characteristic (Ohmic & Saturated regions, Diode conduction, Breakdown & Pinch-off voltages)



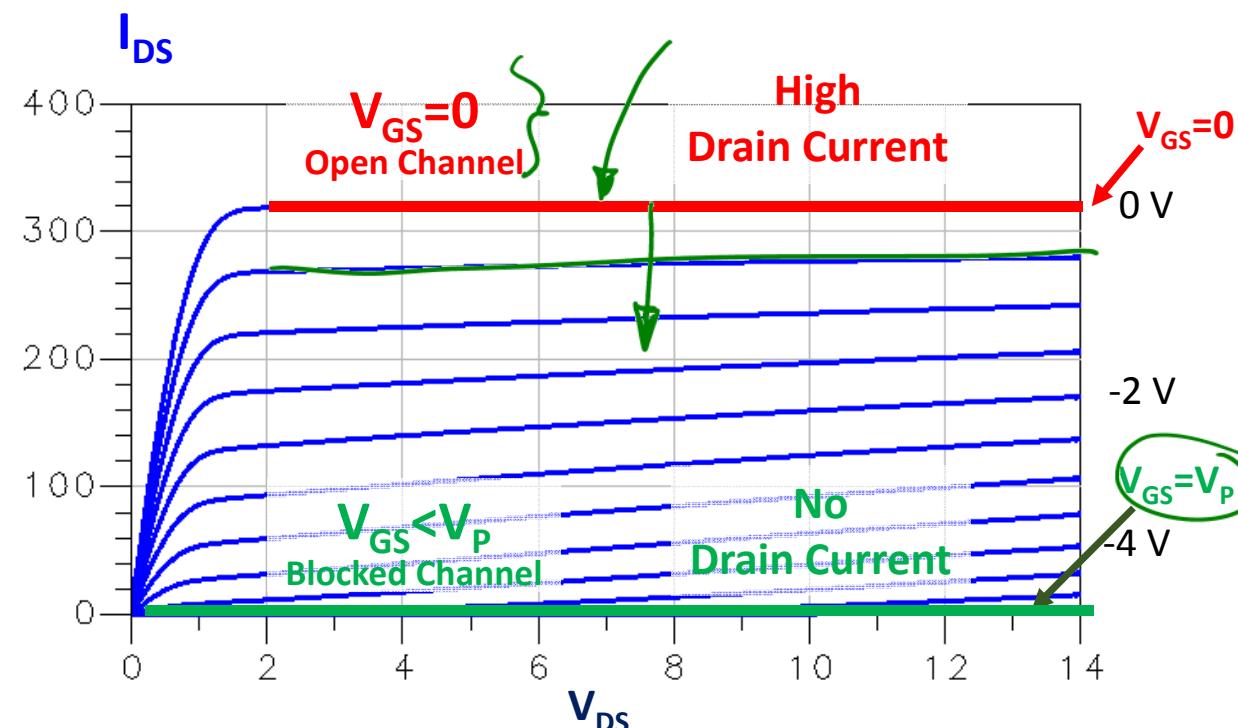FET → Gate voltage controls the flow of drain current by modifying the available section W of the doped channel (Impurities, Ionized scattering → Low mobility)



Operating principles (FET / HEMT)

■ **FET** → Gate voltage controls the flow of drain current by modifying the available section W of the doped channel (Impureties, Ionized scattering → Low mobility)


■ **HEMT** → Gate voltage controls the flow of drain Current by modifying the carrier density n_s of a 2DEG in the undoped channel (no impureties → Very high mobility)

The (two-dimensional Electron Gas) **2DEG** is located at the **heterojunction** between a **wide bandgap semi-conductor (AlGaN)** and a **narrow bandgap semi-conductor (GaN)**.


The electrons of the 2 DEG are free to move in a two-dimensional plane (x,z)
but tightly confined in the 3rd dimension (y)
because they are trapped in a potential well created at the heterojunction surface

I – Basics of HEMT operation → Same Electrical Circuit Model than FET

AlGaN/GaN HEMT on SiC

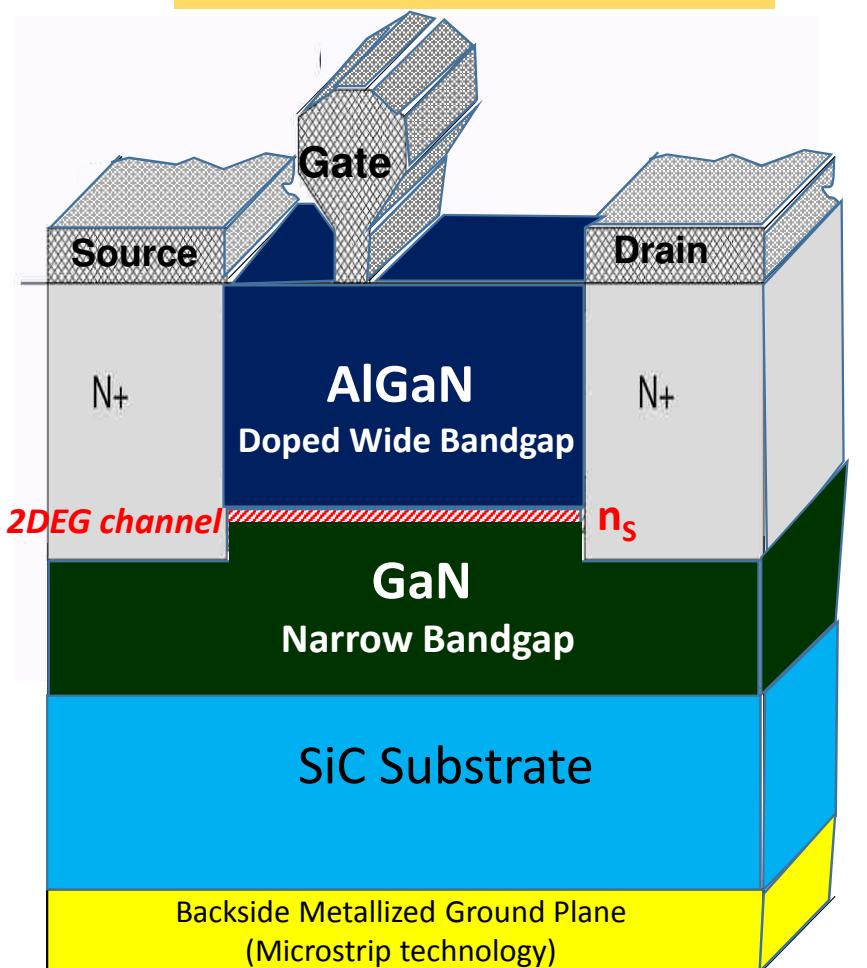

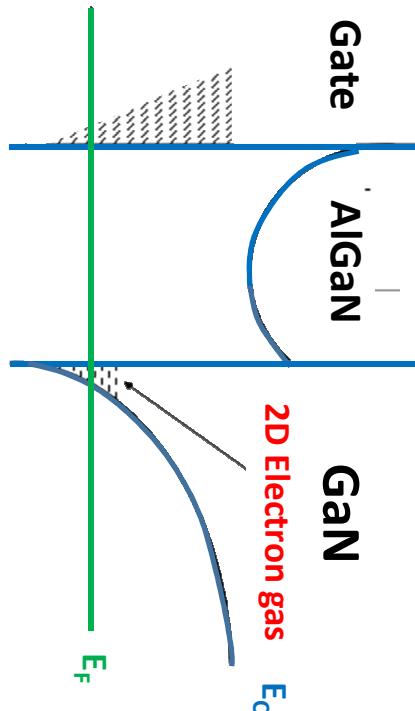HEMT → Gate voltage controls the flow of drain current by modifying the carrier density n_s of a 2DEG in the undoped channel (no impurities → Very high mobility)




The (2-dimensional Electron Gas) **2DEG** is located at the **heterojunction** between a **wide bandgap semi-conductor (AlGaN)** and a **narrow bandgap semi-conductor (GaN)**.


The electrons of the 2 DEG are free to move in a two-dimensional plane (x,z) but tightly confined in the 3rd dimension (y) because they are trapped in a potential well created at the heterojunction surface

I – Basics of MESFET operation

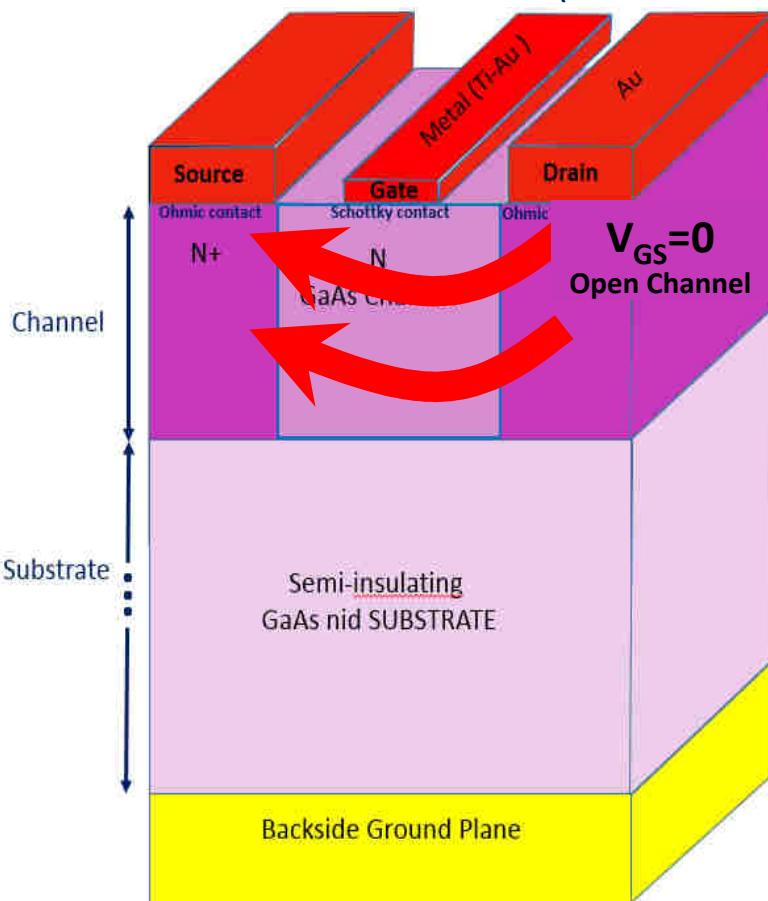→ I-V transfer characteristic (Ohmic & Saturated regions, Diode conduction, Breakdown & Pinch-off voltages)





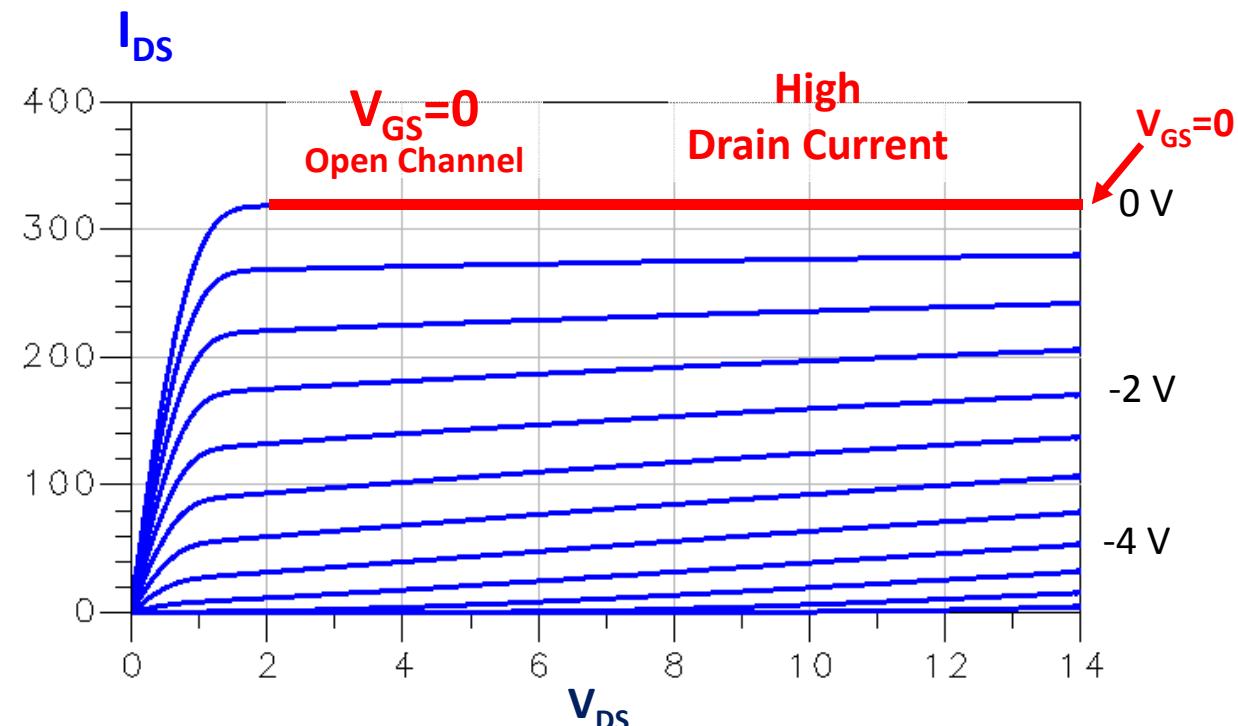FET → Gate voltage controls the flow of drain current by modifying the available section W of the doped channel (Impurities, Ionized scattering → Low mobility)





I – Basics of MESFET operation

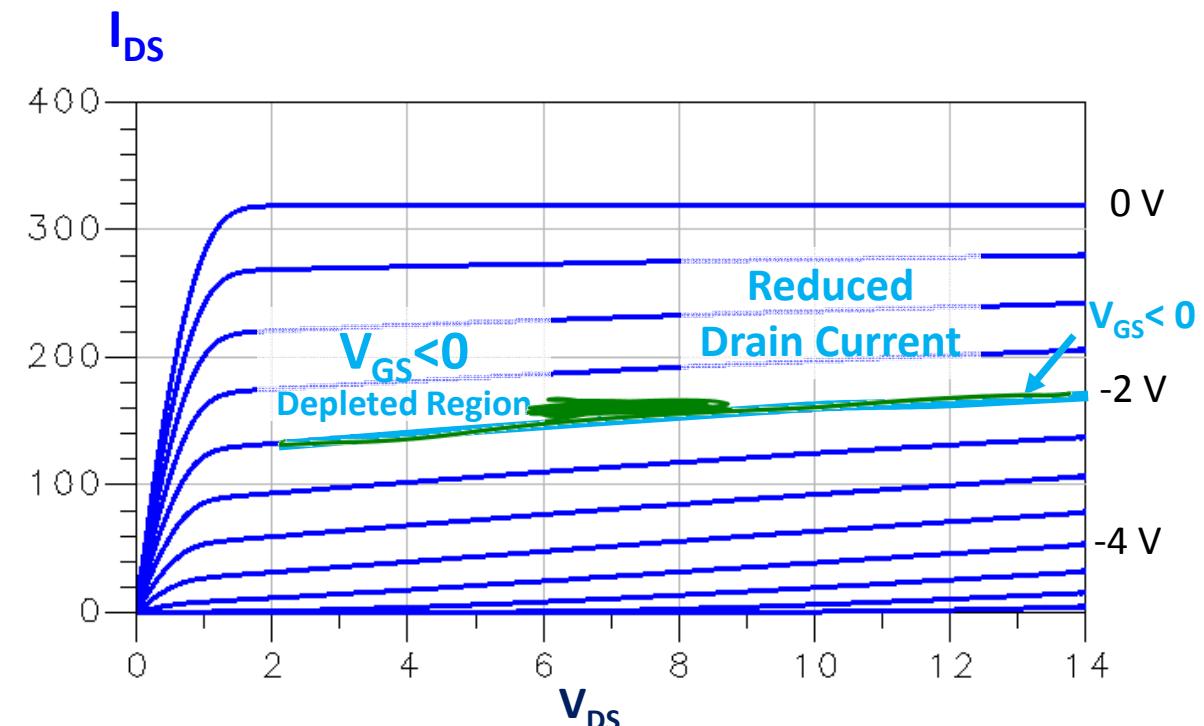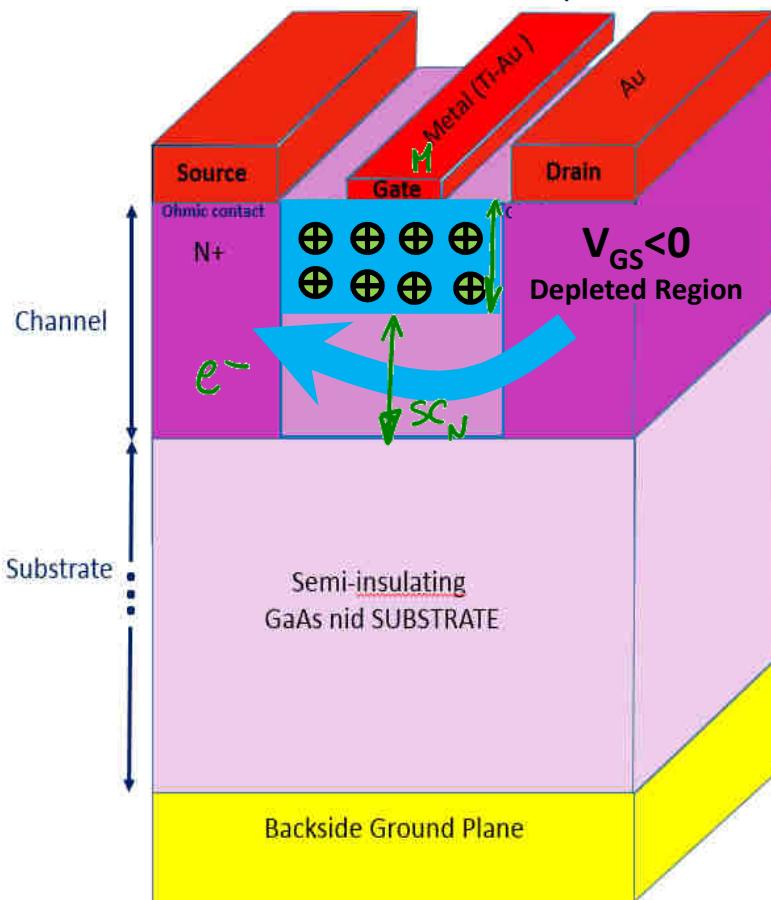→ I-V transfer characteristic (Ohmic & Saturated regions, Diode conduction, Breakdown & Pinch-off voltages)




I – Basics of MESFET operation

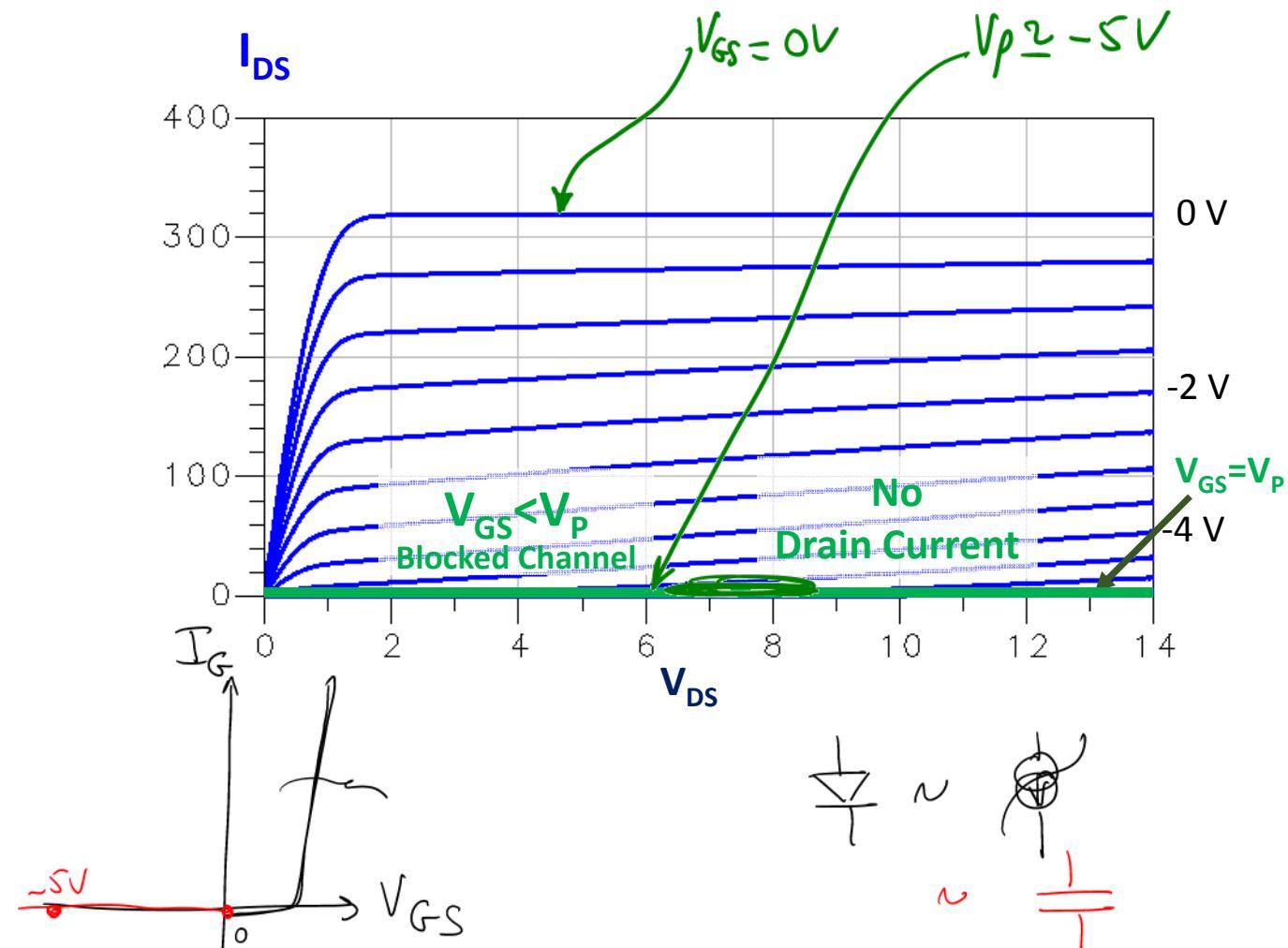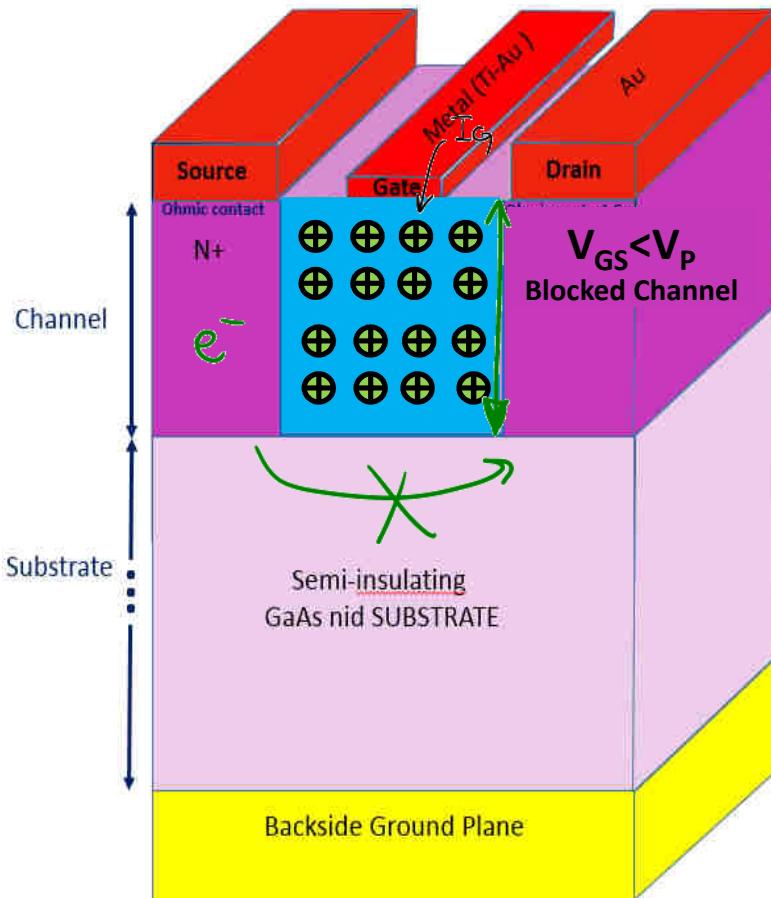→ I-V transfer characteristic (Ohmic & Saturated regions, Diode conduction, Breakdown & Pinch-off voltages)




I – Basics of MESFET operation

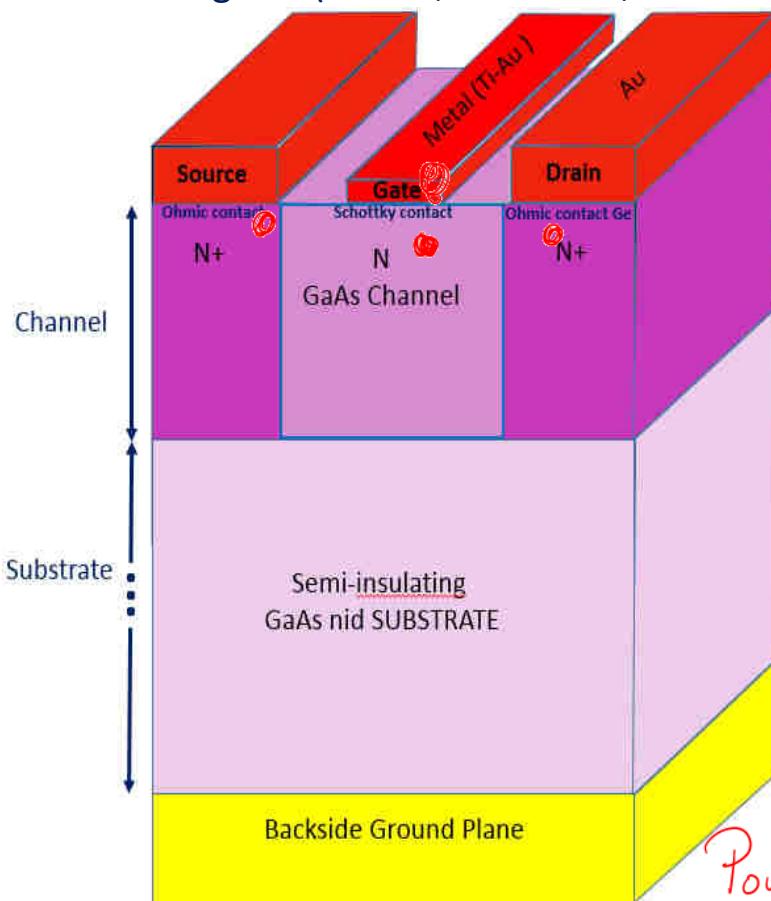→ I-V regions (Ohmic, Saturated, Diode conduction, Breakdown & Pinch-off)


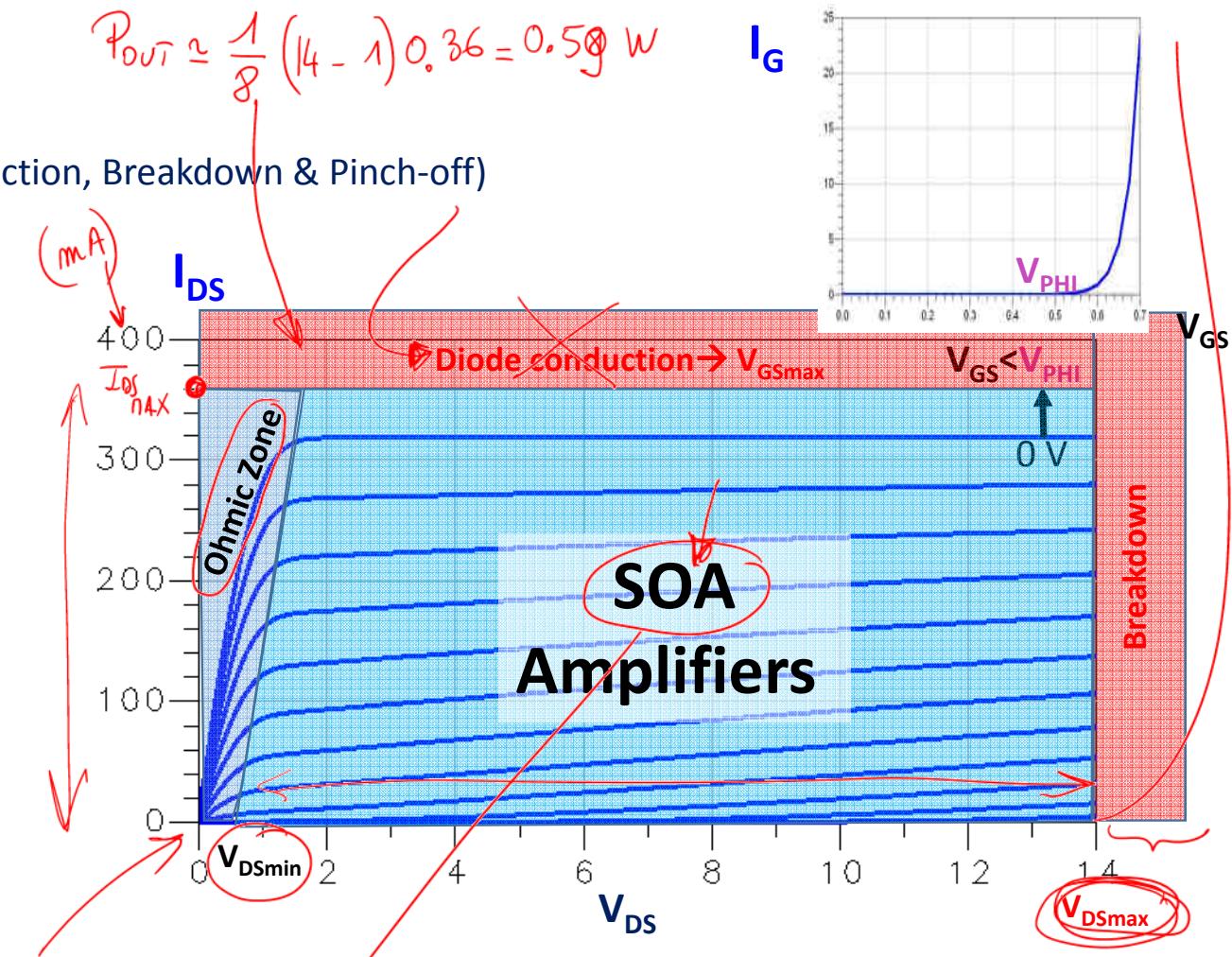
$$\approx \frac{1}{2} \times \frac{V_{DSMAX} - V_{DSMIN}}{2} \times \frac{I_{DSMAX}}{2}$$





Safe Operating Area



FET → $V_{DSMAX} \approx 80 V$
 HEMT → $V_{DSMAX} \approx 100 V$



IMC
Input Matching Circuit

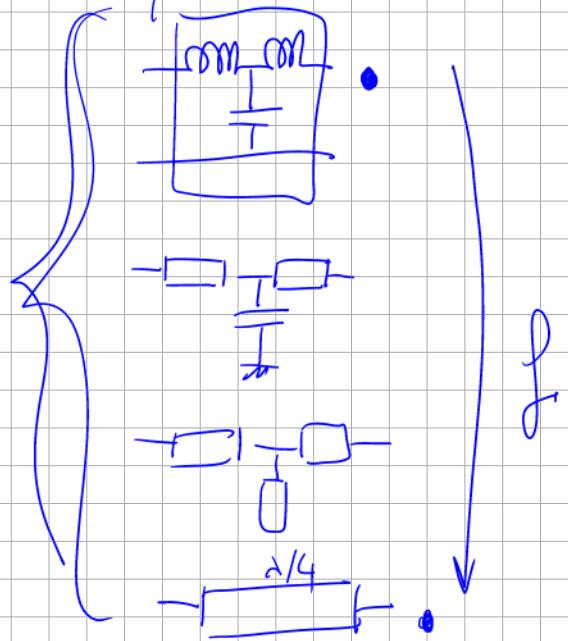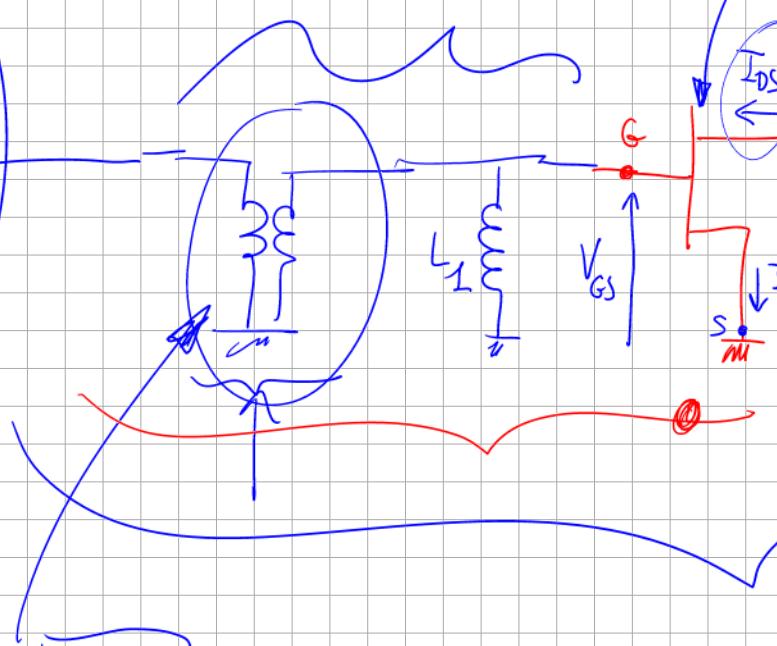

OMC

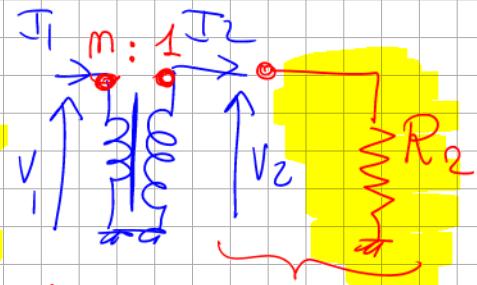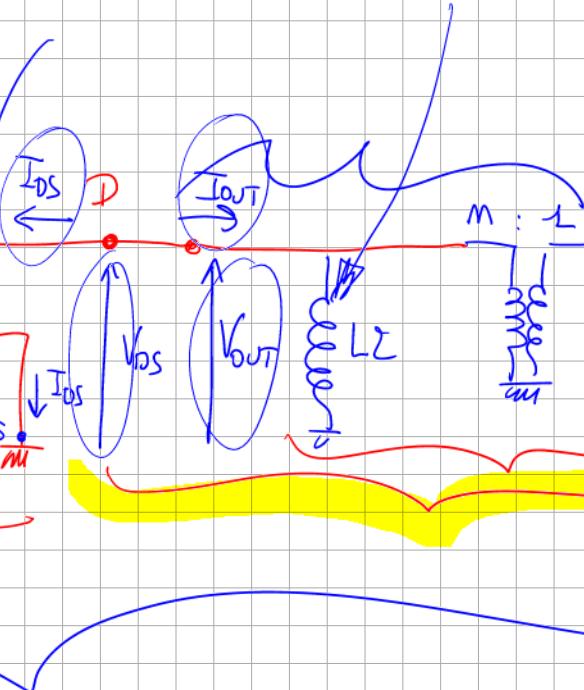


$$R_1 = \frac{V_1}{I_1}$$


$$M = \frac{M_2}{M_1}$$

$$M = \sqrt{\frac{R_2}{R_1}}$$

$$P_{out} = \frac{1}{2} \rho_e (V_{out} \times I_{out}^*)$$

$$= \frac{1}{2} |V_{out}| |I_{out}| \cos(\phi_{V_{out}} - \phi_{I_{out}})$$

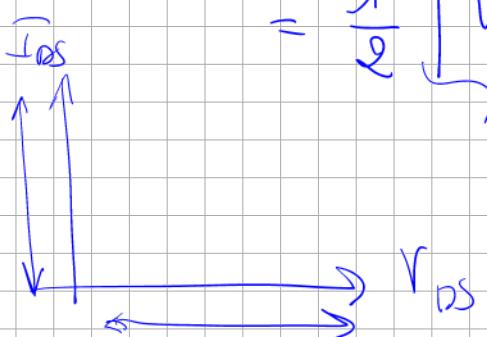

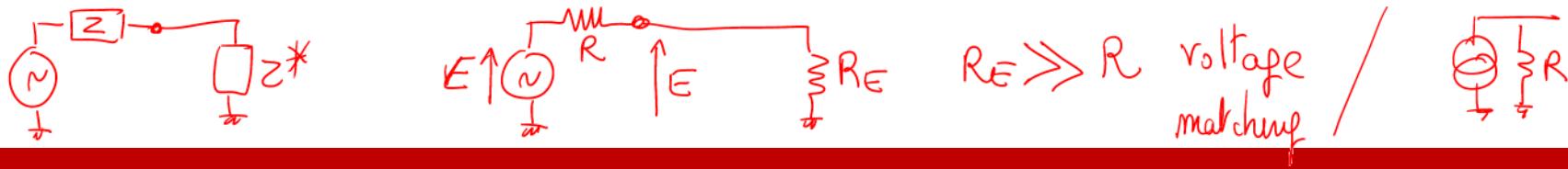


EMIMEO

E(rasmus) Mundus on Innovative Microwave Electronics and Optics



I – Basics of MESFET operation

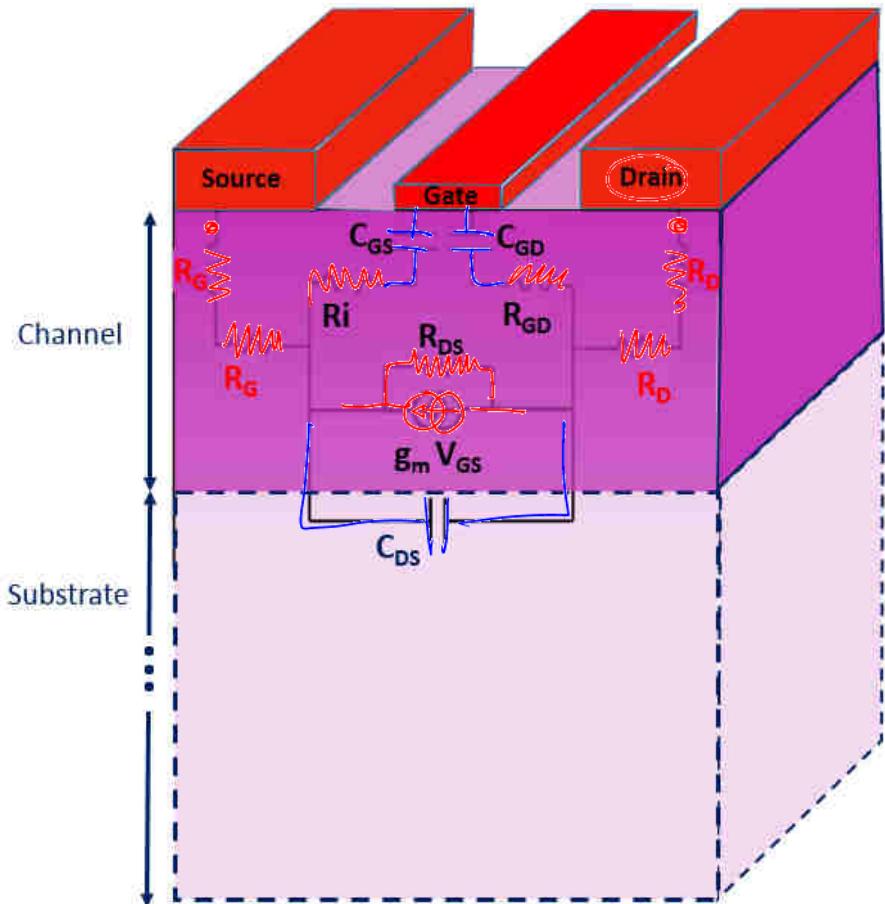→ Simplified planar representation of FETs (localization of electrical lumped elements)



I – Basics of MESFET operation

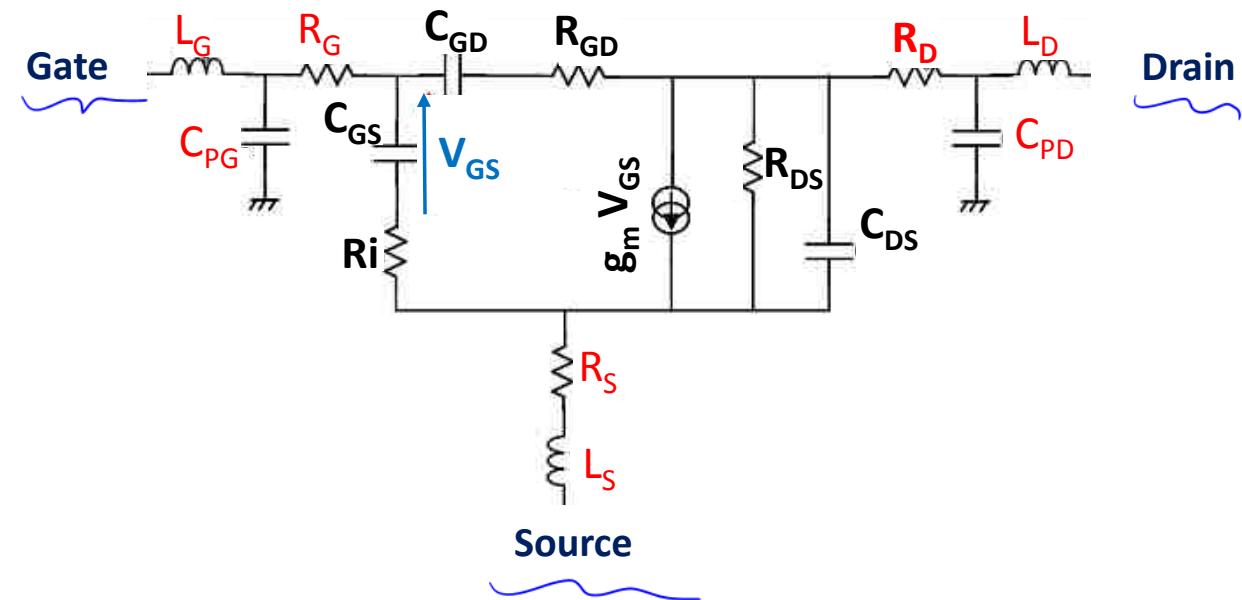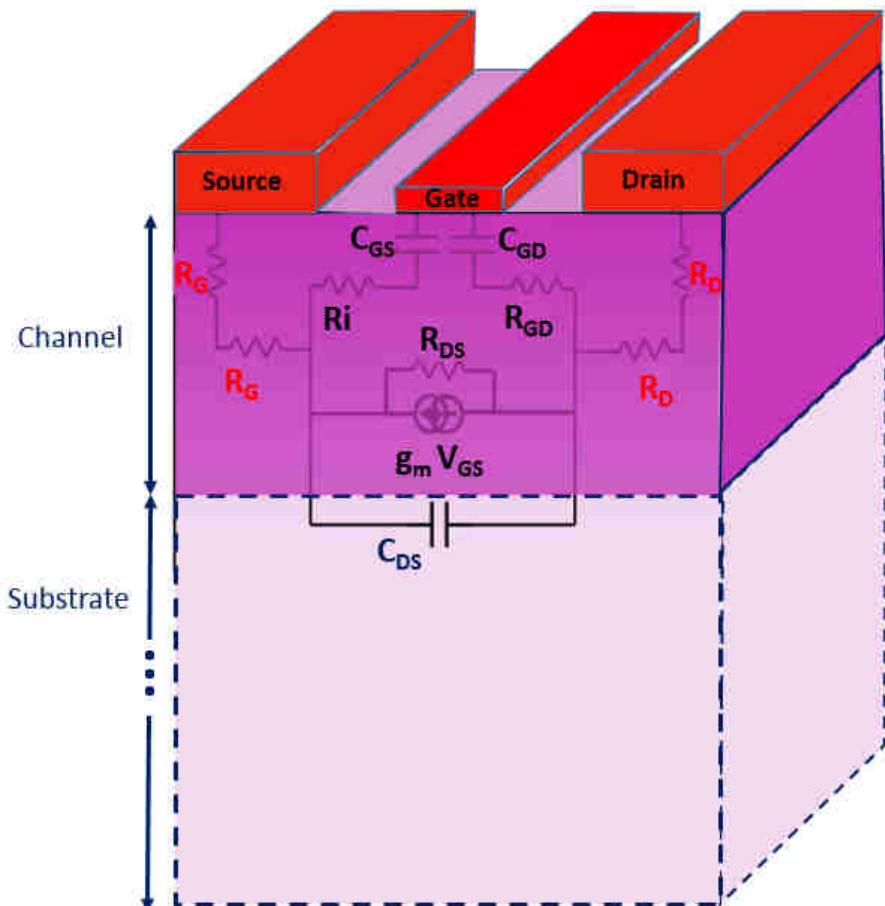
→ Simplified planar representation of FETs (localization of electrical lumped elements)




$$G = \underline{14 \text{ dB}} \quad \begin{matrix} 15 \\ 13 \end{matrix}$$

I – Basics of MESFET operation

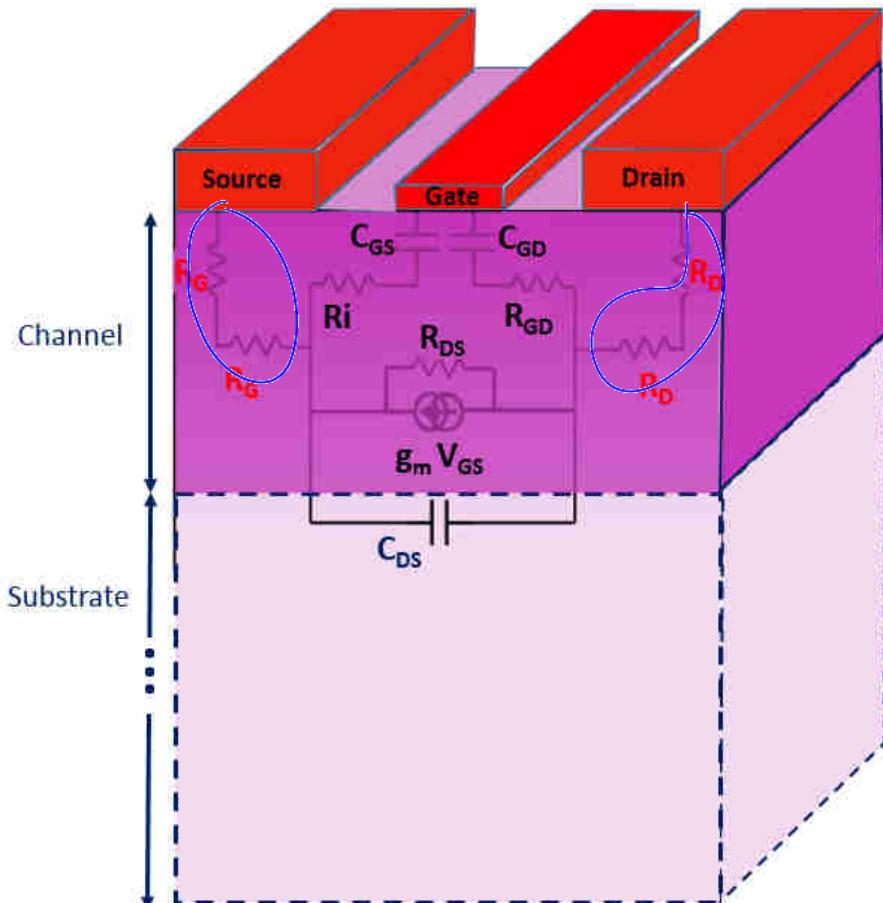→ Simplified planar representation of FETs (localization of electrical lumped elements)



Gate


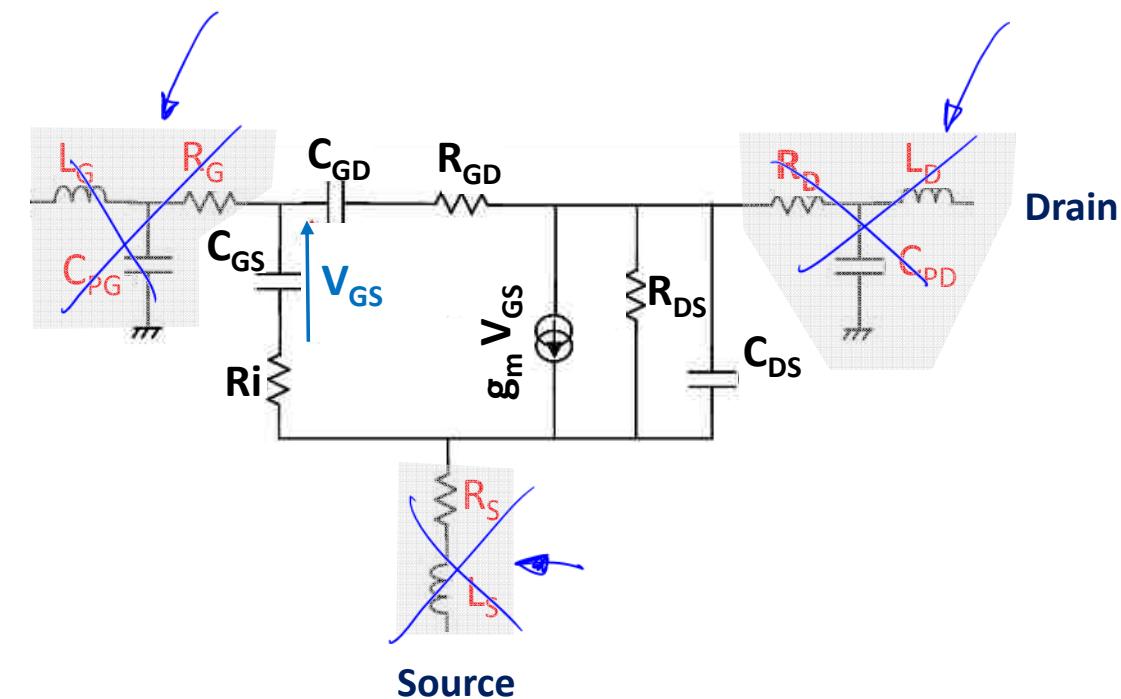


Source

Extrinsic elements are the first ones that can be neglected when compared to other elements

I – Basics of MESFET operation

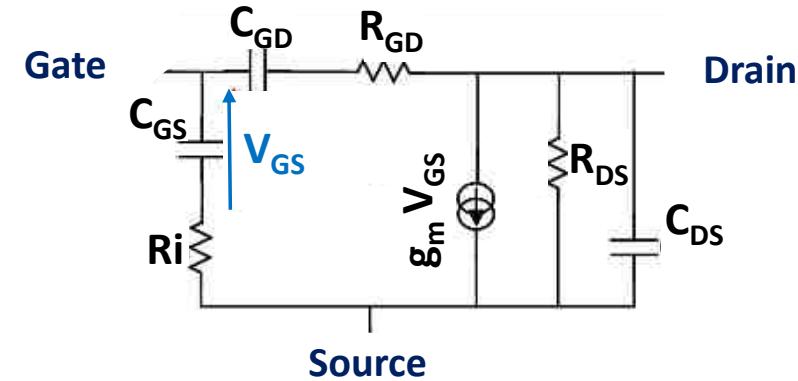
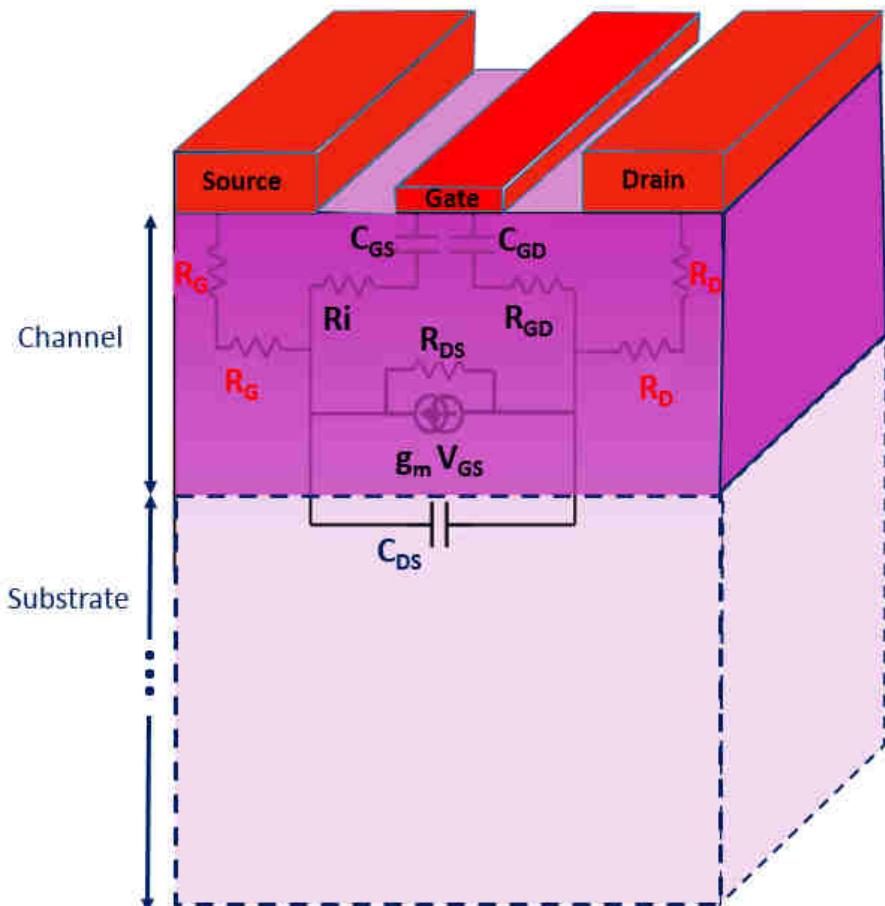
→ Simplified planar representation of FETs (localization of electrical lumped elements)




Extrinsic elements are the first ones that can be neglected when compared to other elements

I – Basics of MESFET operation

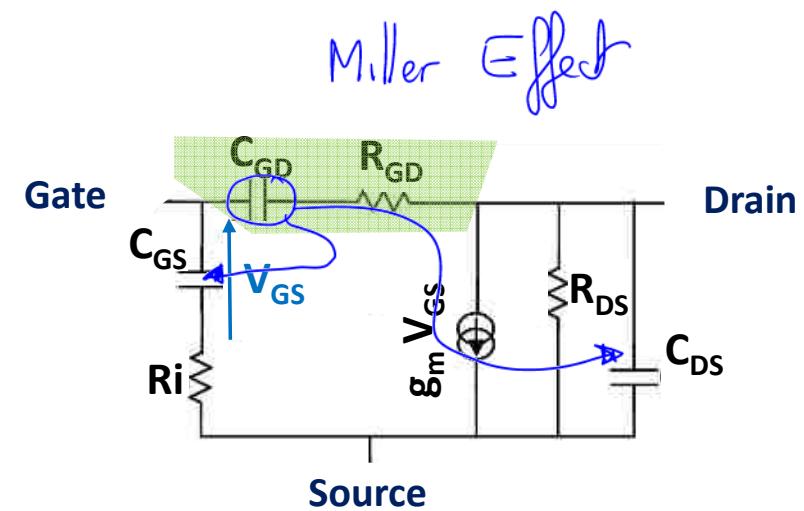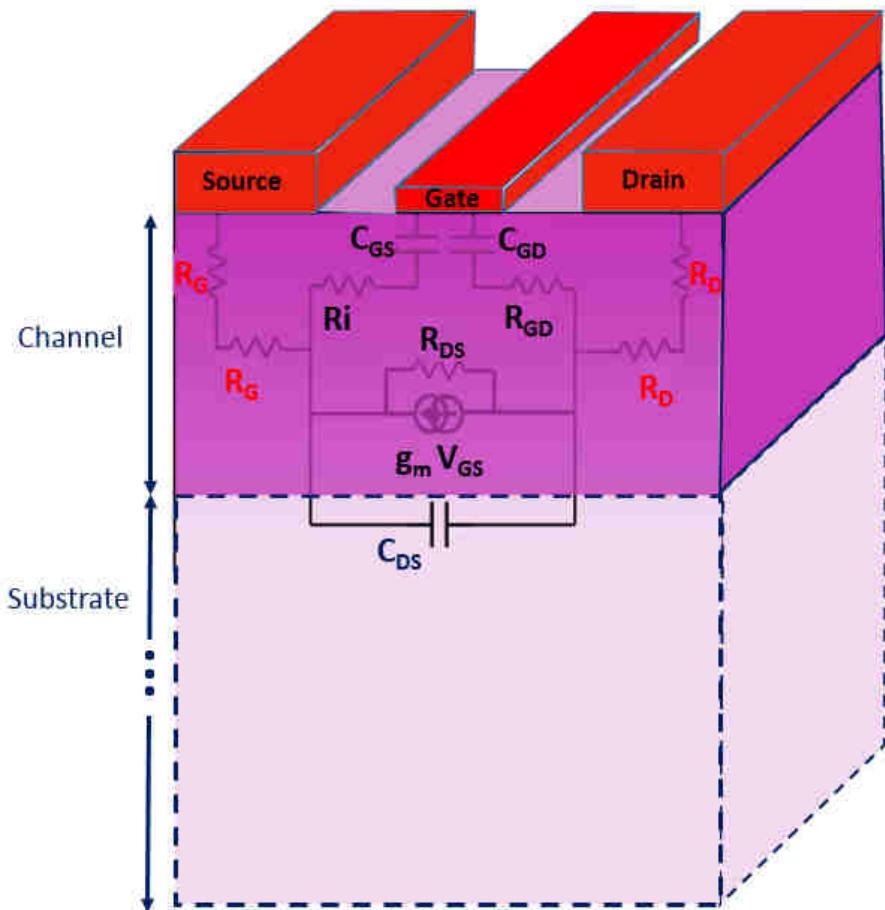→ Simplified planar representation of FETs (localization of electrical lumped elements)




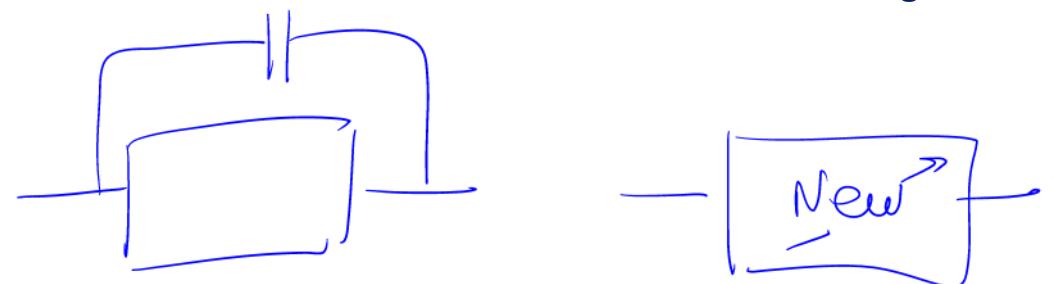Feedback elements Gate-to-Drain can also be neglected.




I – Basics of MESFET operation

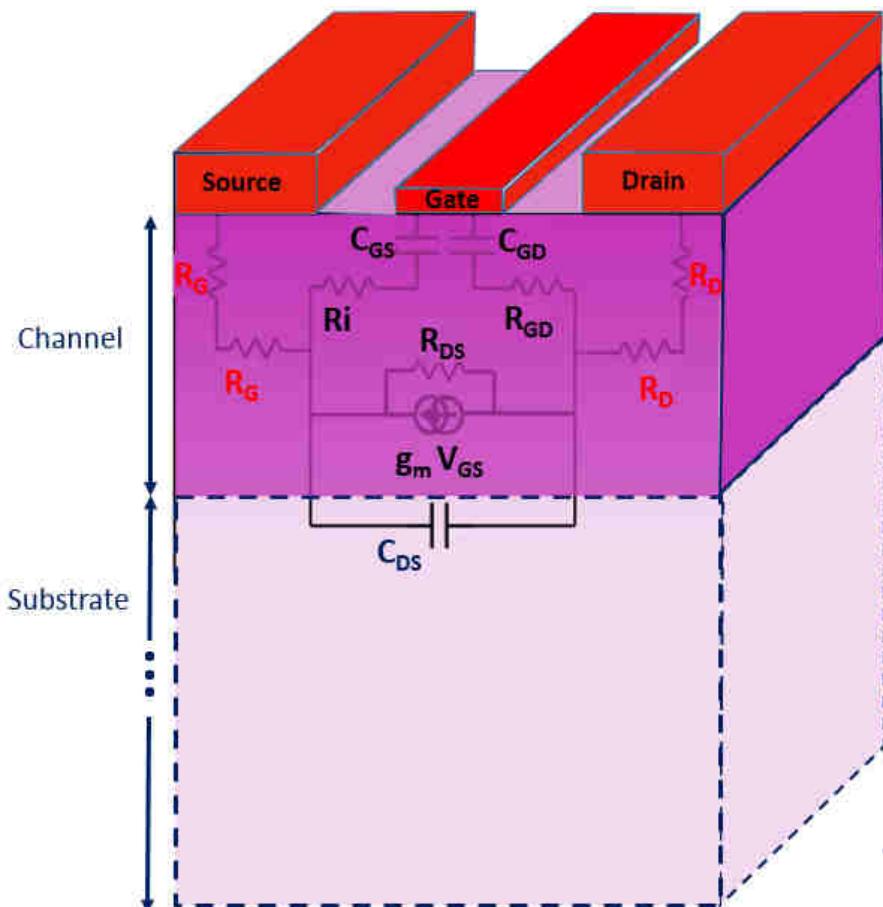→ Simplified planar representation of FETs (localization of electrical lumped elements)



$$V = R I$$

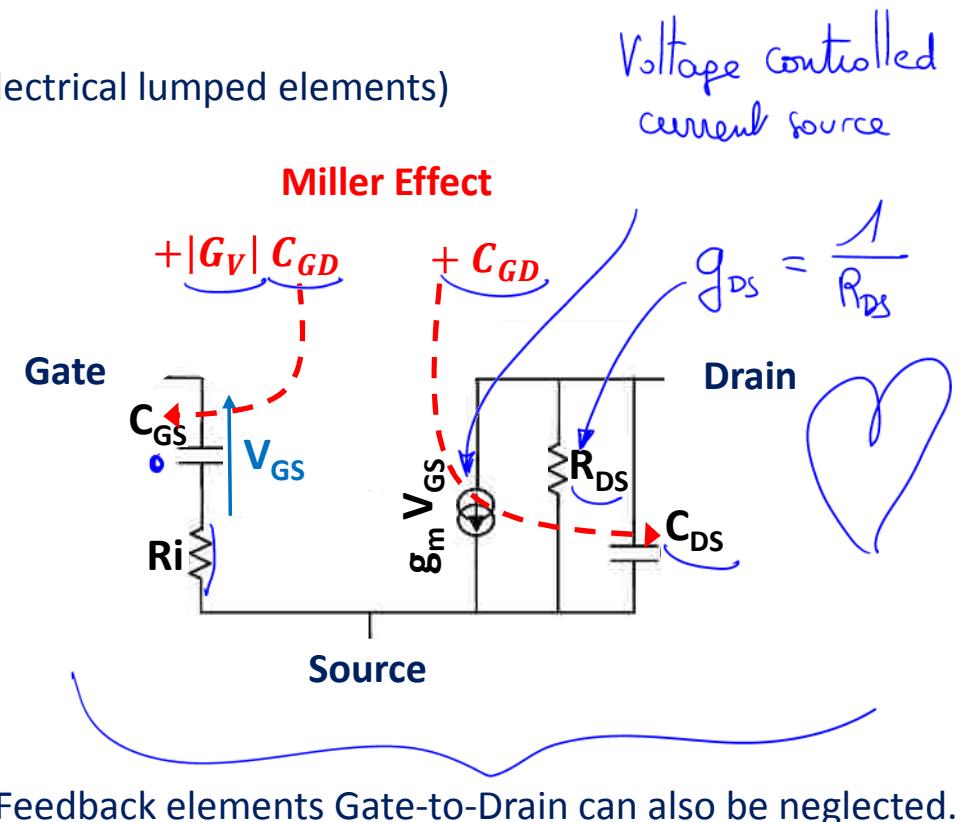
$$I = G V \quad \text{with} \quad G = 1/R$$



Feedback elements Gate-to-Drain can also be neglected.
However, the capacitive feedback is taken into account
by **Miller Effect**


I – Basics of FET operation

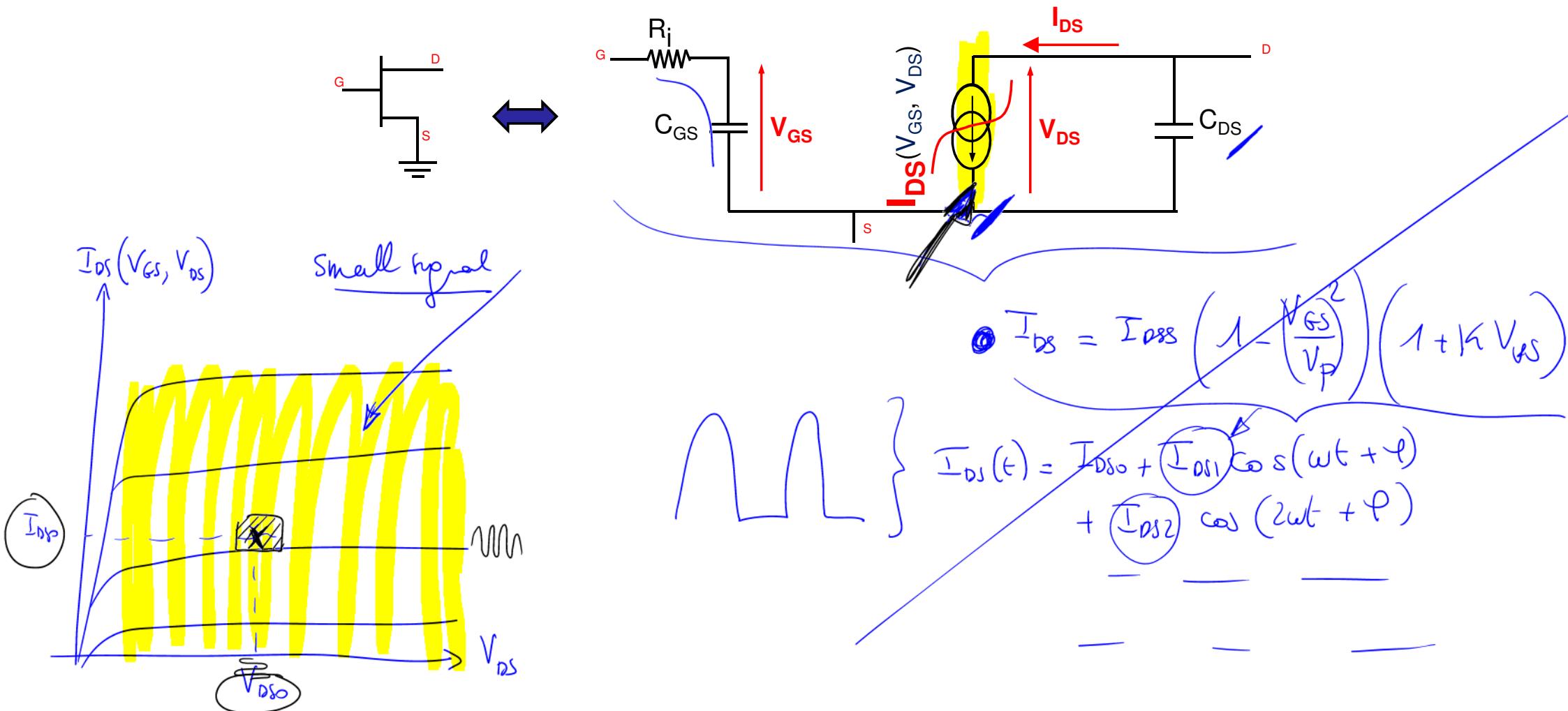→ Simplified Small-signal equivalent of the nonlinear drain current (gm , gd) around a specific bias point




I – Basics of FET operation

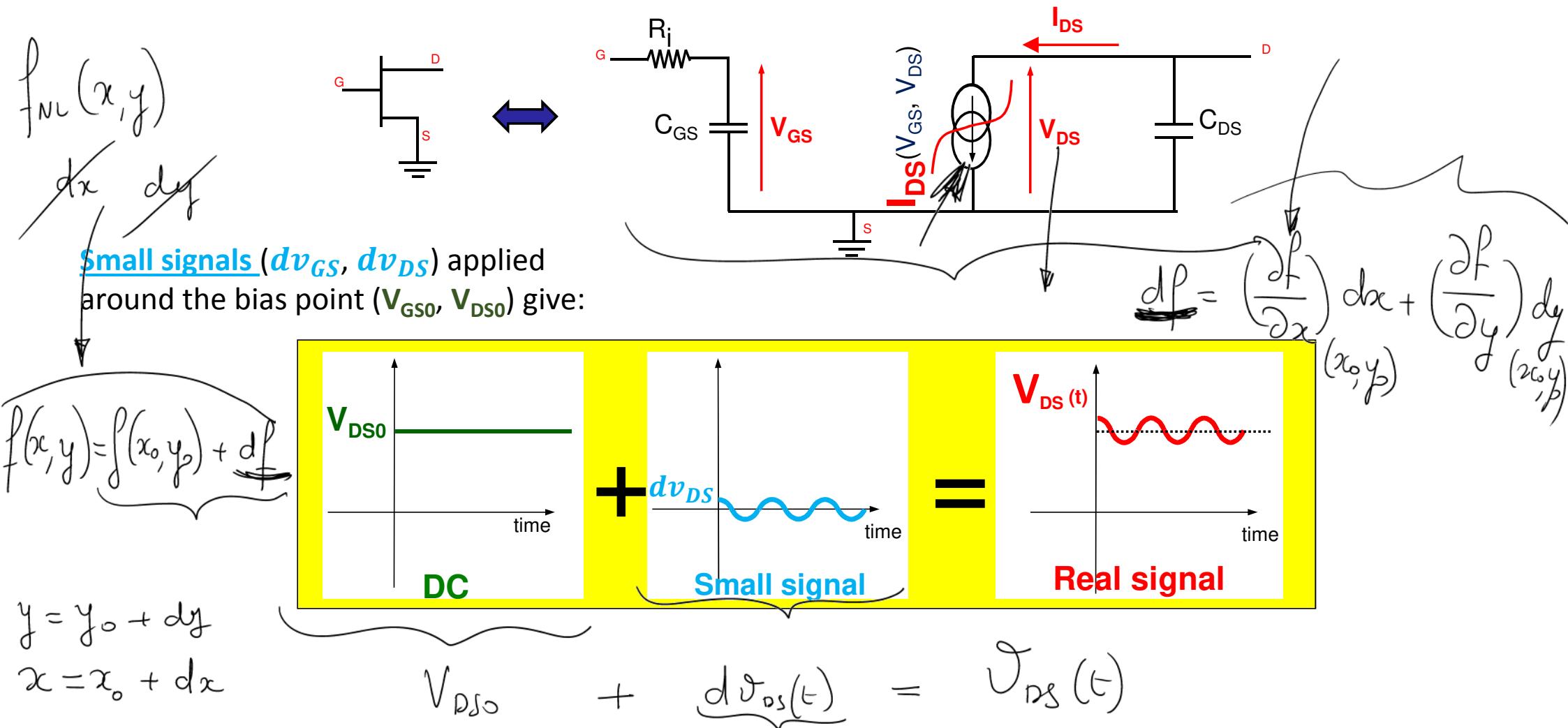→ Simplified Small-signal equivalent of the nonlinear drain current (gm , gd) around a specific bias point



I – Basics of FET operation

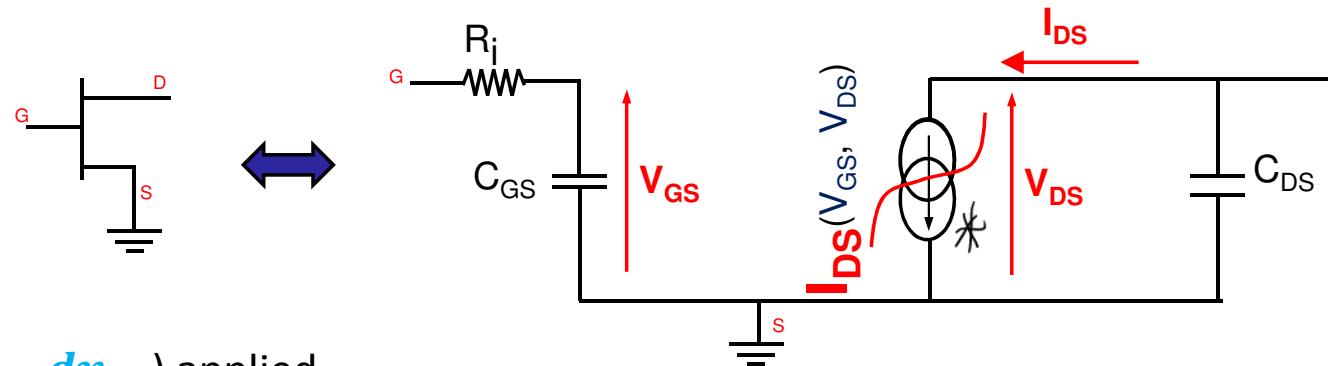→ Simplified Small-signal equivalent of the nonlinear drain current (gm , gd) around a specific bias point




Small signals (dV_{GS} , dV_{DS}) applied
around the bias point (V_{GS0} , V_{DS0}) give:

$$\begin{cases} \widetilde{V_{GS}(t)} = \widetilde{V_{GS0}} + \widetilde{dV_{GS}(t)} \\ \widetilde{V_{DS}(t)} = \widetilde{V_{DS0}} + \widetilde{dV_{DS}(t)} \end{cases}$$

I – Basics of FET operation

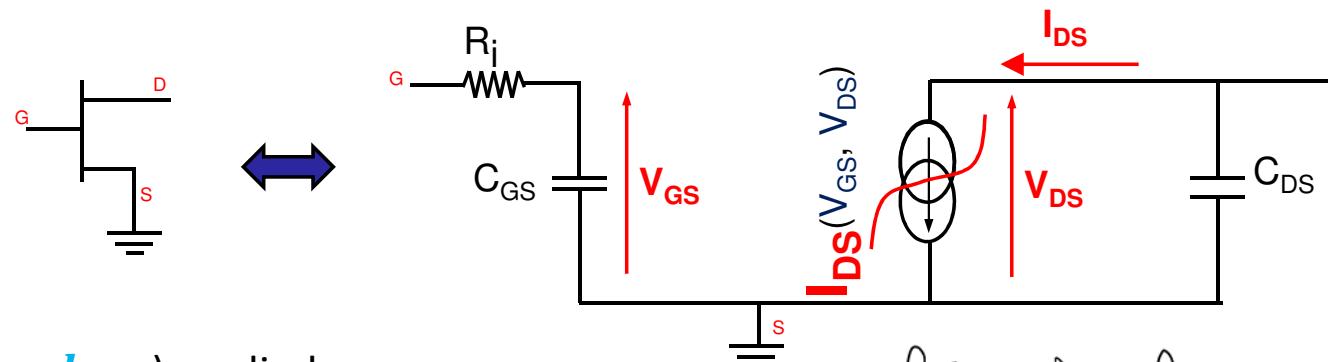
→ Simplified Small-signal equivalent of the nonlinear drain current (gm , gd) around a specific bias point



Small signals (dv_{GS} , dv_{DS}) applied around the bias point (V_{GS0} , V_{DS0}) give:

$$f(x, y) = f(x_0, y_0) + \frac{\partial f}{\partial x}(x_0, y_0)(x - x_0) + \frac{\partial f}{\partial y}(x_0, y_0)(y - y_0)$$
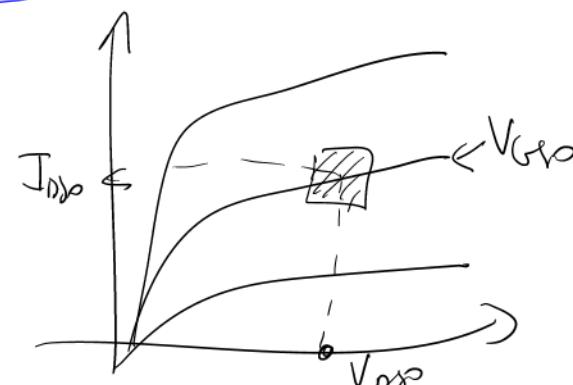
$$\begin{aligned} V_{GS}(t) &= V_{GS0} + \underbrace{dv_{GS}(t)}_{*} \\ V_{DS}(t) &= V_{DS0} + \underbrace{dv_{DS}(t)}_{*} \end{aligned} \quad \rightarrow \quad \begin{aligned} \overbrace{I_{DS}(t)} &= \overbrace{F_{NL}(V_{GS}, V_{DS})} = \overbrace{F_{NL}(V_{GS0}, V_{DS0})} + \underbrace{dF_{NL}}_{=} \\ &= \overbrace{I_{DS0}} + \underbrace{dI_{DS}}_{=} \end{aligned}$$




$$\begin{aligned} I_{DS}(t) &= \overbrace{I_{DS0}} + \underbrace{dI_{DS}}_{=} \\ &\quad + \underbrace{di_{DS}}_{\text{Taylor expansion}} \end{aligned}$$

Taylor expansion

I – Basics of FET operation

→ Simplified Small-signal equivalent of the nonlinear drain current (gm , gd) around a specific bias point

$$f(x,y) \quad d\int = () dx + () dy =$$

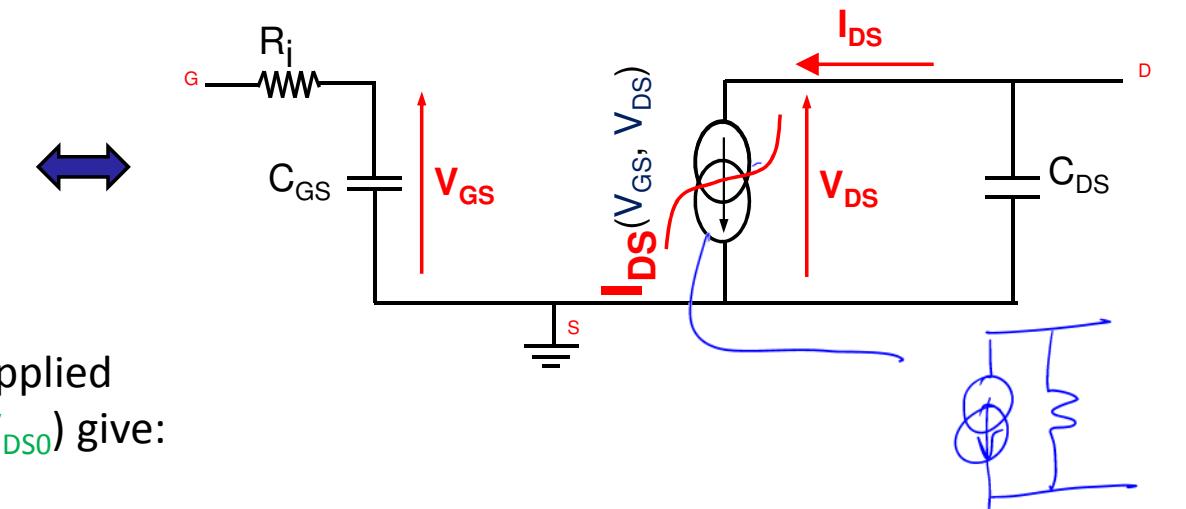

Small signals (dv_{GS} , dv_{DS}) applied
around the bias point (V_{GS0} , V_{DS0}) give:

$$V_{GS}(t) = V_{GS0} + dv_{GS}(t) \quad \rightarrow \quad I_{DS}(t) = I_{DS0} + di_{DS}$$

$$V_{DS}(t) = V_{DS0} + dv_{DS}(t)$$

Taylor expansion

$$di_{DS} = dF_{NL} = \left(\frac{\delta I_{DS}}{\delta V_{GS}} \right)_{(V_{GS0}, V_{DS0})} \cdot dv_{GS} + \left(\frac{\delta I_{DS}}{\delta V_{DS}} \right)_{(V_{GS0}, V_{DS0})} \cdot dv_{DS}$$

gm

$gd = 1/R_{DS}$


$$g_m = \left. \frac{\partial I_{DS}}{\partial V_{GS}} \right|_{(V_{GSO}, V_{DSO})} = \underline{\text{FET transconductance}} = S = \Omega^{-1}$$

$$g_D \approx g_{DS} = \left. \frac{\partial I_{DS}}{\partial V_{DS}} \right|_{(V_{GSO}, V_{DSO})} = \underline{\text{Drain-Source conductance}} = \Omega^{-1}$$

$$R_{DS} = \frac{1}{g_{DS}}$$

I – Basics of FET operation

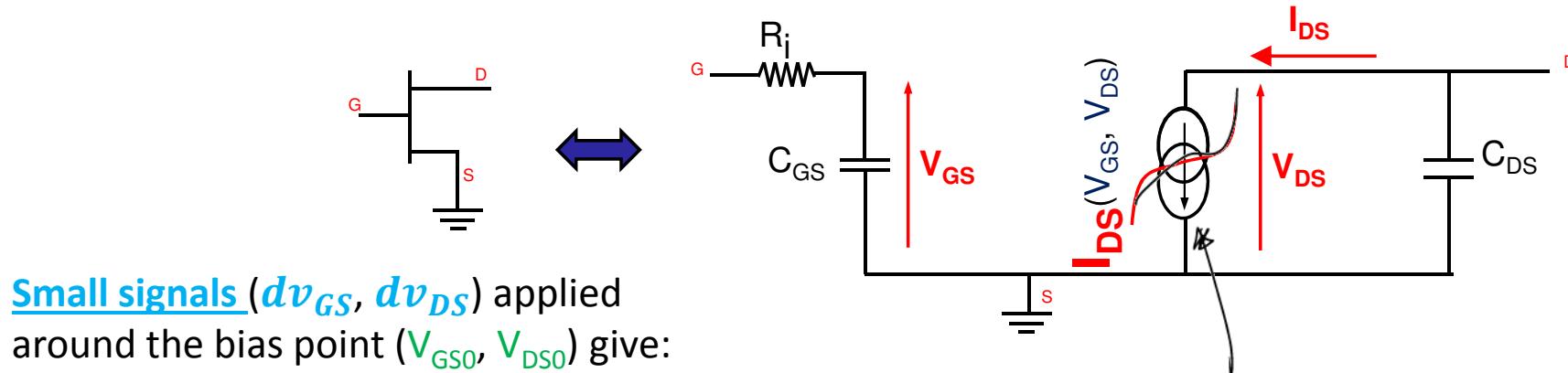→ Simplified Small-signal equivalent of the nonlinear drain current (g_m , g_d) around a specific bias point




Small signals (dV_{GS} , dV_{DS}) applied around the bias point (V_{GS0} , V_{DS0}) give:

$$\frac{dV_{GS}(t)}{dV_{DS}(t)} \longrightarrow I_{DS}(t) = I_{DS0} + di_{DS}$$

$$di_{DS} = dF_{NL} = \left(\frac{\delta I_{DS}}{\delta V_{GS}} \right)_{(V_{GS0}, V_{DS0})} \cdot dV_{GS} + \left(\frac{\delta I_{DS}}{\delta V_{DS}} \right)_{(V_{GS0}, V_{DS0})} \cdot dV_{DS} = g_m \cdot dV_{GS} + g_{DS} \cdot dV_{DS}$$

I – Basics of FET operation

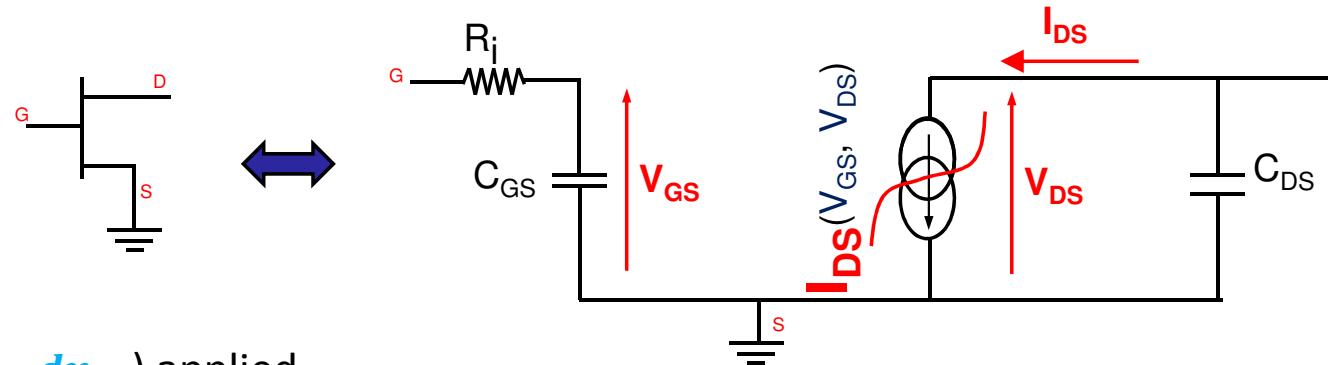→ Simplified Small-signal equivalent of the nonlinear drain current (g_m , g_d) around a specific bias point



Small signals (dV_{GS} , dV_{DS}) applied
around the bias point (V_{GSO} , V_{DSO}) give:

$$\frac{dV_{GS}(t)}{dV_{DS}(t)} \rightarrow \cancel{di_{DS}} = g_m \cdot \cancel{dv_{GS}} + g_{DS} \cdot \cancel{dv_{DS}}$$


$$g_m = \left(\frac{\delta I_{DS}}{\delta V_{GS}} \right) \Big|_{(V_{GSO}, V_{DSO})}$$

$$g_{DS} = \left(\frac{\delta I_{DS}}{\delta V_{DS}} \right) \Big|_{(V_{GSO}, V_{DSO})}$$

$$I_{DS} = g_m \cdot V_{GS} + g_{DS} \cdot V_{DS}$$

$$V_{DS} = V_{DSO} + \Delta V_{DS}$$


I – Basics of FET operation

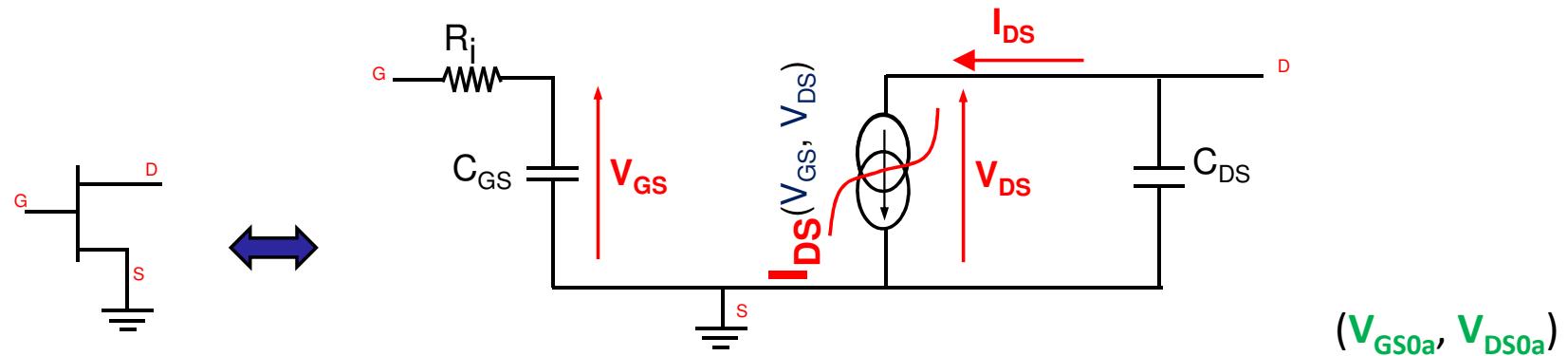


Small signals (dv_{GS} , dv_{DS}) applied around the bias point (V_{GS0} , V_{DS0}) give:

$$g_m = \left(\frac{\delta i_{DS}}{\delta v_{GS}} \right) \Big|_{(V_{GS0}, V_{DS0})}$$

$$g_{DS} = \left(\frac{\delta i_{DS}}{\delta v_{DS}} \right) \Big|_{(V_{GS0}, V_{DS0})}$$

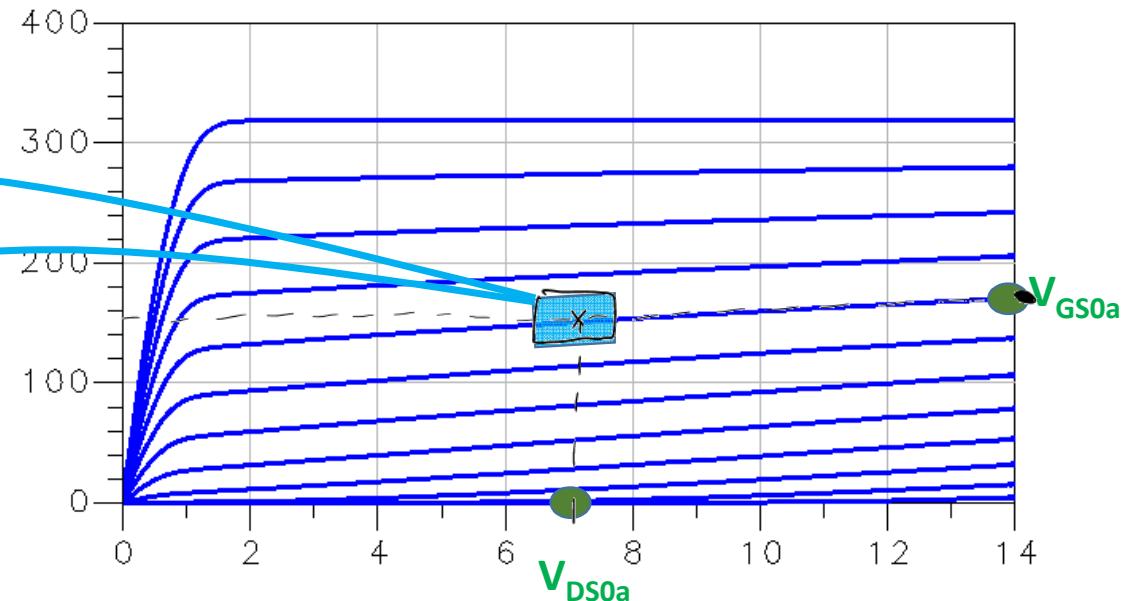


I – Basics of FET operation

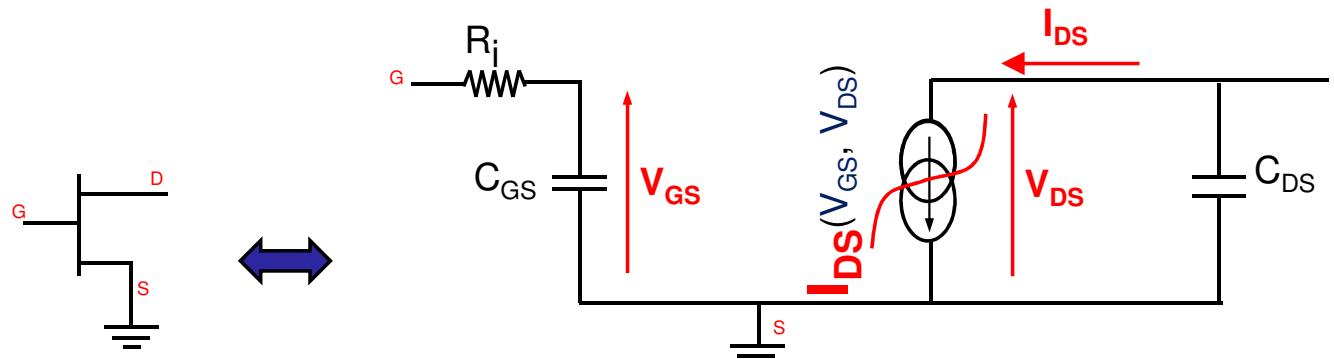



Small signals (δV_{GS} , δV_{DS}) applied around the bias point (V_{GS0} , V_{DS0}) give:

$$g_m = \left(\frac{\delta I_{DS}}{\delta V_{GS}} \right)_{(V_{GS0}, V_{DS0})}$$
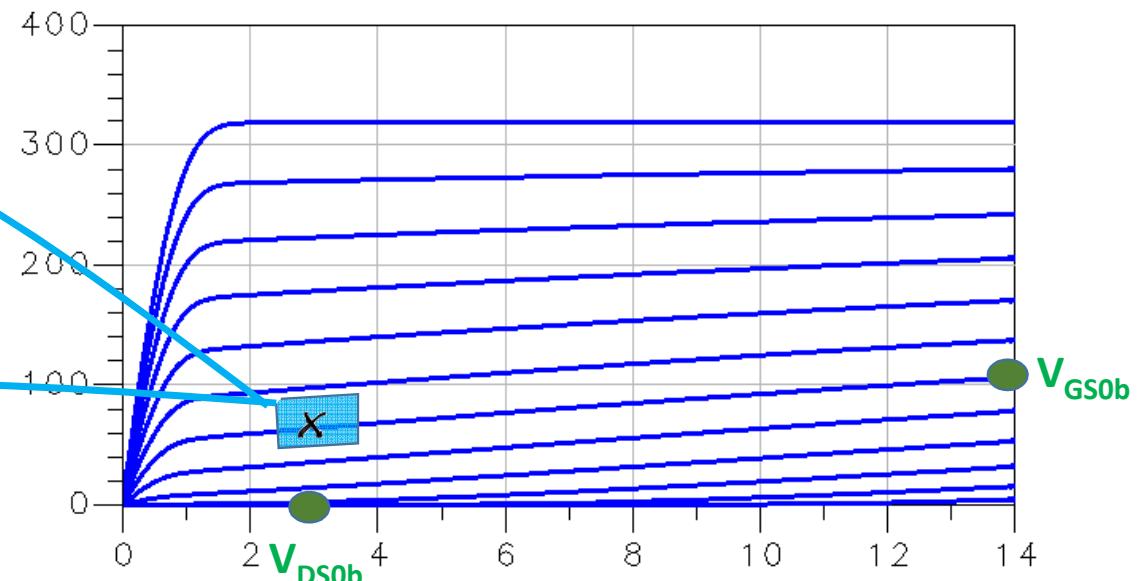
$$g_{DS} = \left(\frac{\delta I_{DS}}{\delta V_{DS}} \right)_{(V_{GS0}, V_{DS0})}$$




I – Basics of FET operation

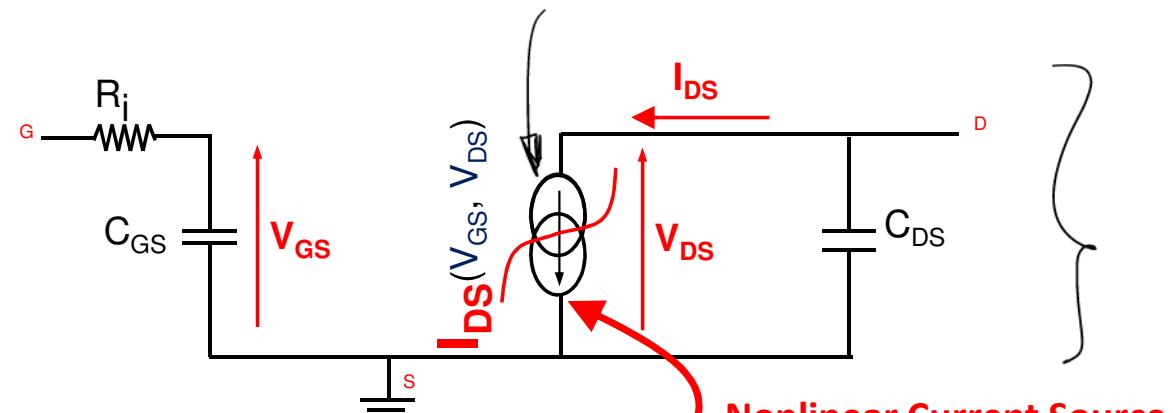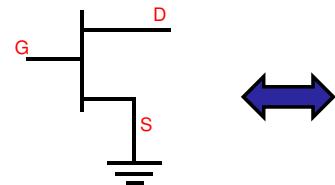

Large signals (ΔV_{GS} , ΔV_{DS}) applied around the bias point (V_{GSO} , V_{DSO}) give:


~~$$g_m = \left(\frac{\delta I_{DS}}{\delta V_{GS}} \right) \Big|_{(V_{GSO}, V_{DSO})}$$~~

~~$$g_{DS} = \left(\frac{\delta I_{DS}}{\delta V_{DS}} \right) \Big|_{(V_{GSO}, V_{DSO})}$$~~

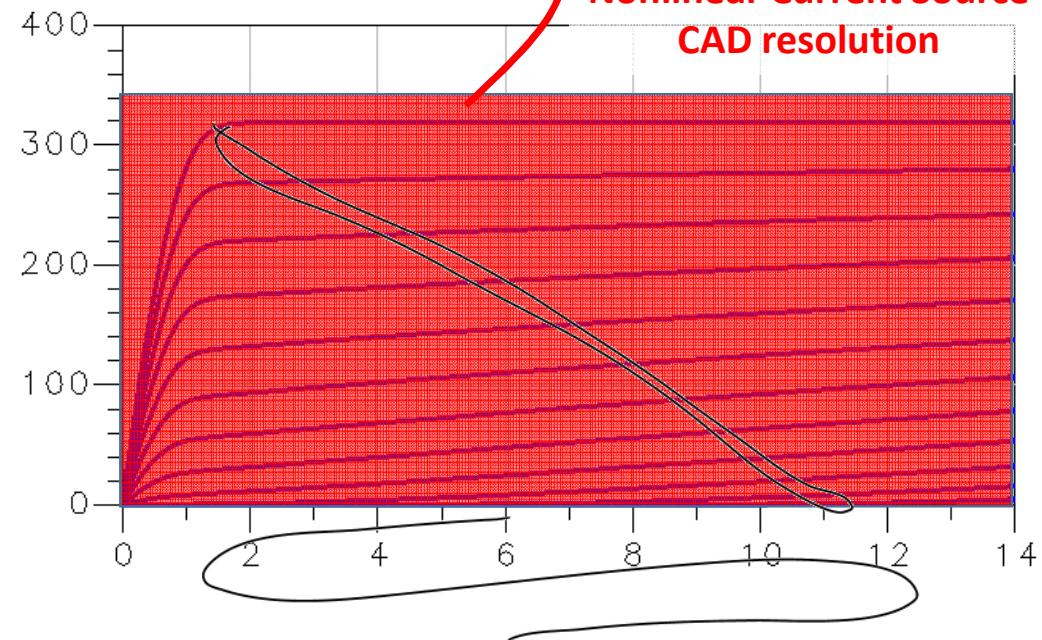

I – Basics of FET operation

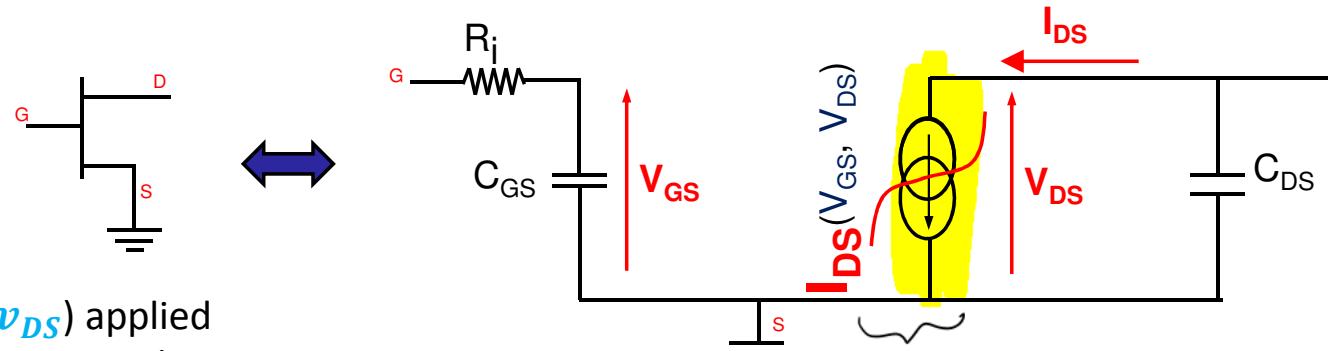→ Simplified Small-signal equivalent of the nonlinear drain current (g_m , g_d) around a specific bias point




Small signals (dv_{GS} , dv_{DS}) applied around the bias point (V_{GS0} , V_{DS0}) give:

$$\begin{aligned} V_{GS} &= V_{GS0} + dv_{GS} \\ V_{DS} &= V_{DS0} + dv_{DS} \end{aligned} \quad \left\{ \right.$$

$$di_{DS} = g_m \times dv_{GS} + g_d \times dv_{DS}$$
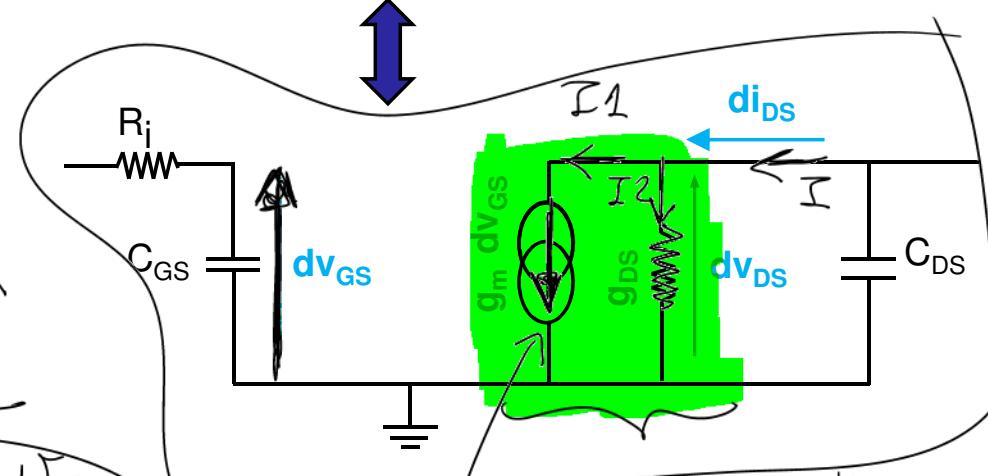
$$I = I_1 + I_2 = \frac{dI_{DS}}{R_{DS}}$$




$$\begin{aligned} I &\downarrow \\ R &\quad \uparrow \\ V &= RI \\ I &= \frac{V}{R} \end{aligned}$$

Ohm's Law

I – Basics of FET operation

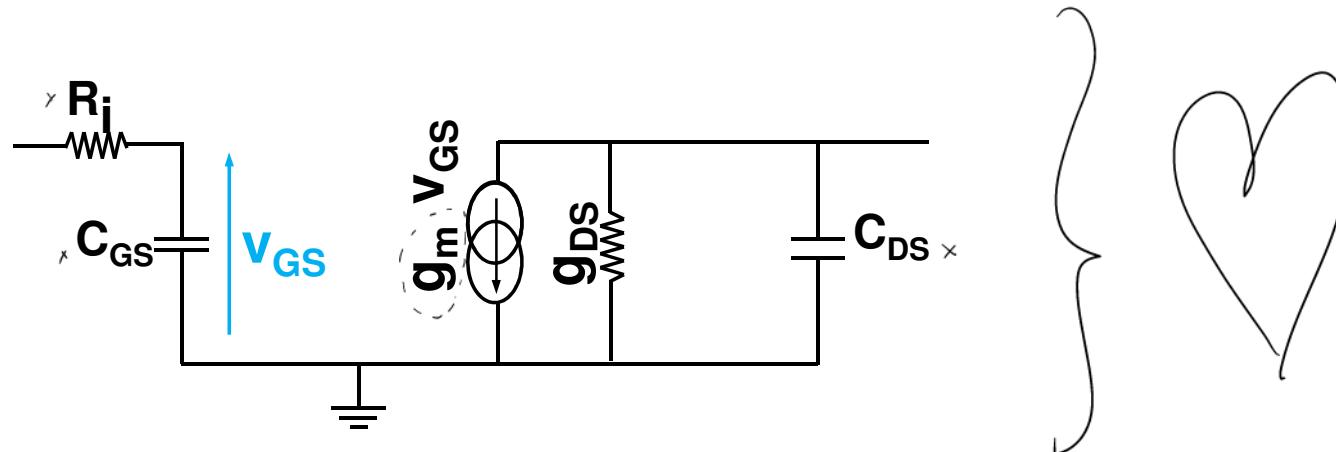
→ Simplified Small-signal equivalent of the nonlinear drain current (g_m , g_d) around a specific bias point



II – Intrinsic figures of merit for FETs

1) Low-Pass Frequency (Low-Pass Input RC circuit)

$$f_{LP} = \frac{1}{2\pi R_i C_{GS}}$$

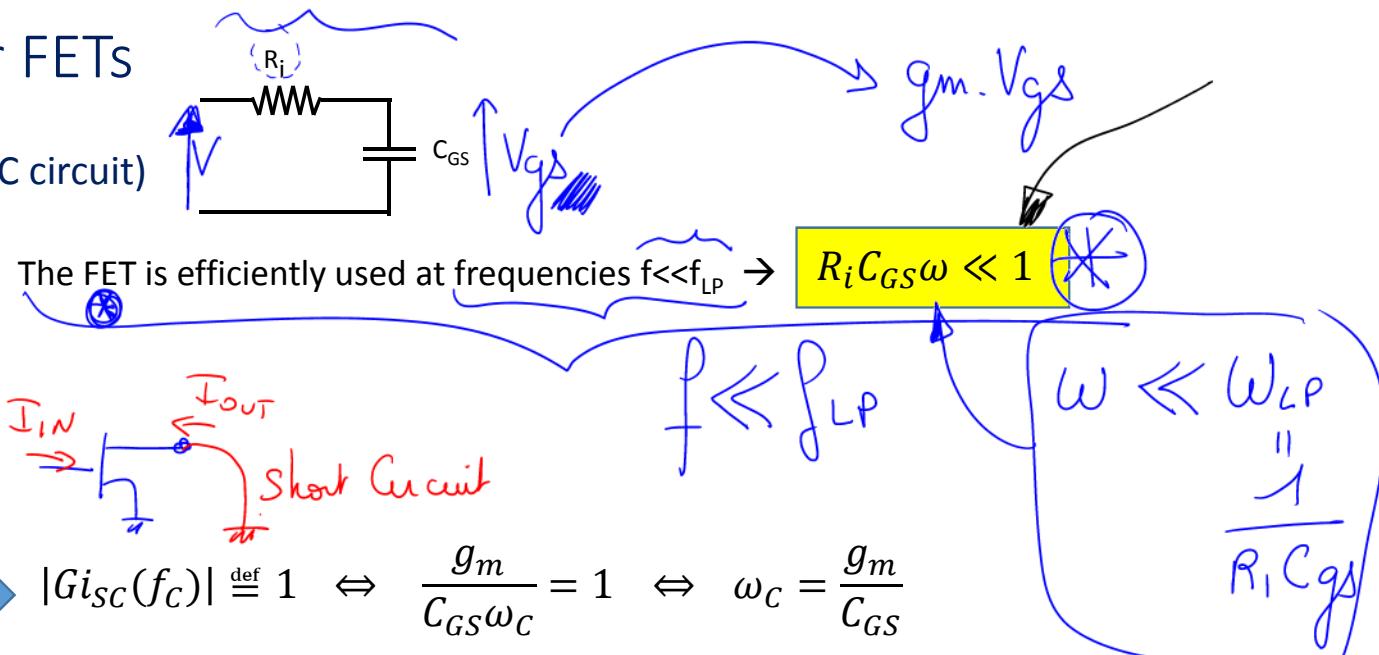

2) Cutoff frequency of gain current



Current Gain in Short-Circuit

$$G_{ISC} = \frac{I_{OUTSC}}{I_{IN}} = \frac{g_m V_{GS}}{j C_{GS} \omega V_{GS}} = \frac{g_m}{j C_{GS} \omega} \rightarrow |G_{ISC}(f_c)| \stackrel{\text{def}}{=} 1 \Leftrightarrow \frac{g_m}{C_{GS} \omega_c} = 1 \Leftrightarrow \omega_c = \frac{g_m}{C_{GS}}$$

$$f_c = \frac{g_m}{2\pi C_{GS}}$$

f_c is widely used to compare FETs with each other

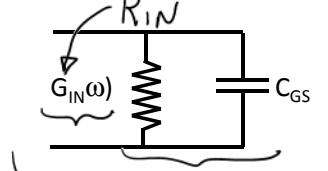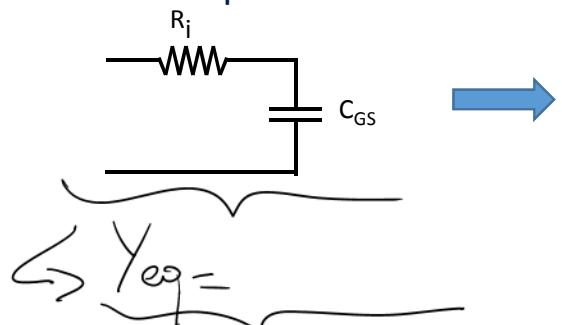
→ Narrowband equivalence between (series RC) and (parallel RC) circuit at the FET input



$$G_{IN}(\omega) = R_i C_{GS}^2 \omega^2$$

$$R_{IN} = \frac{1}{G_{IN}}$$
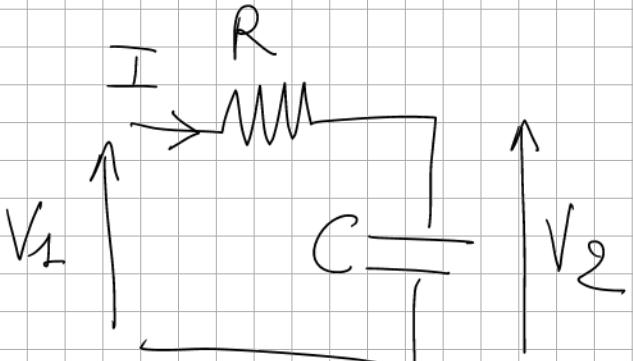
$$Y_{eq} = \left(\frac{1}{R_{IN}} \right) + j (C_{GS} \omega)$$



$$\begin{cases} V_2 = Z_C \times I \\ V_1 = (R + Z_C) I \end{cases}$$


$$Z_C = \frac{1}{j C \omega}$$





$$\frac{V_2}{V_1} = \frac{Z_C}{R + Z_C} = \frac{1}{1 + \frac{R}{Z_C}}$$

$$\frac{V_2}{V_1} = \frac{1}{1 + j RC\omega}$$

$$\rightarrow \left| \frac{V_2}{V_1} \right| = \frac{1}{\sqrt{1 + (RC\omega)^2}} = |G_V|$$
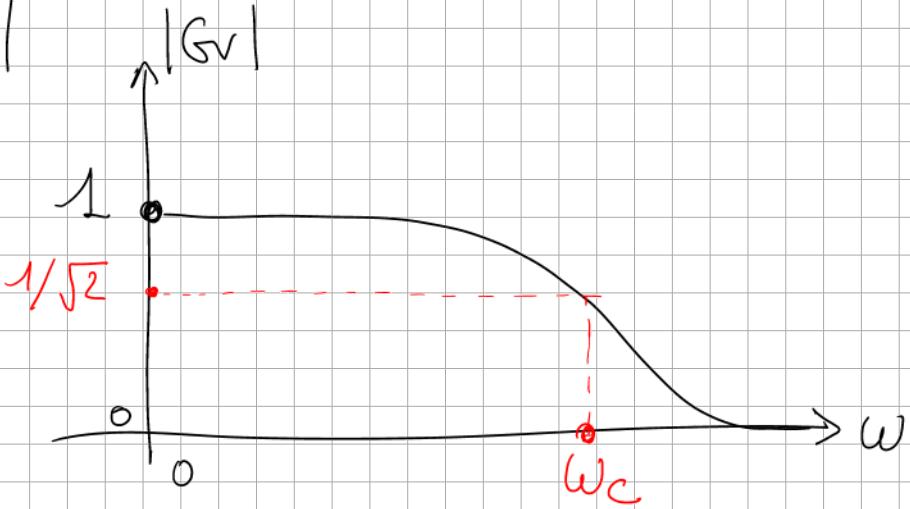
$$\omega_C = \frac{1}{RC} \rightarrow f_C = \frac{1}{2\pi RC}$$



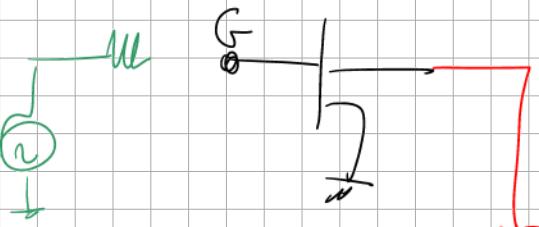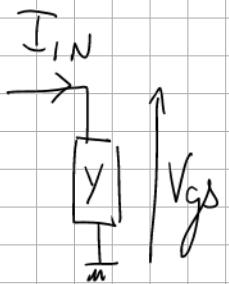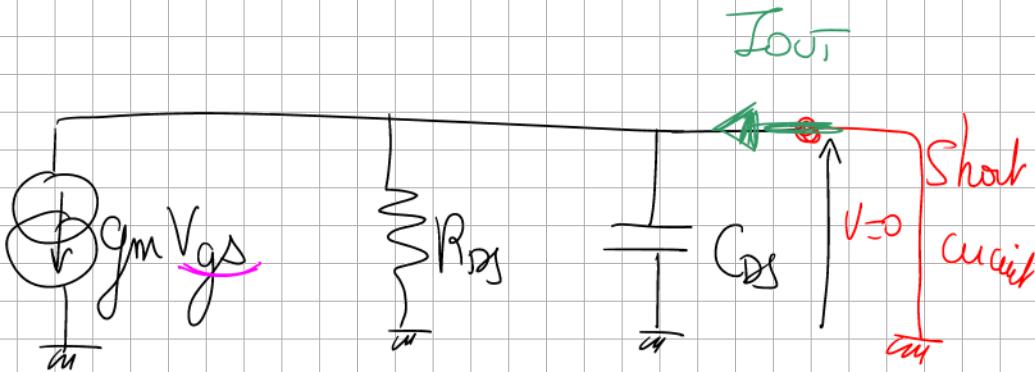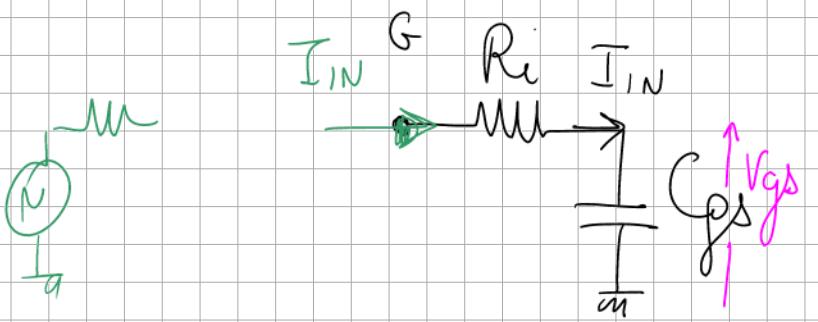

$$V = Z I$$

$$Z = \frac{V}{I} = Y \times V$$

$$I_{IN} = Y_{GS} \times V_{GS}$$

$$\boxed{I_{IN} = (j C_{GS} \omega) V_{GS}}$$

$$\boxed{I_{OUT} = g_m \cdot V_{GS}}$$


$$\left| G_{I_{SC}}(f_c) \right| = 1$$

$$\frac{g_m}{C_{GS} \omega_c} \stackrel{\triangle}{=} 1$$




$$G_{I_{SC}} = \frac{f_{OUT}}{I_{IN}} = \frac{g_m \cdot V_{GS}}{(j C_{GS} \omega) V_{GS}} = \frac{g_m}{j C_{GS} \omega}$$

$$\frac{g_m}{j C_{GS} \omega}$$

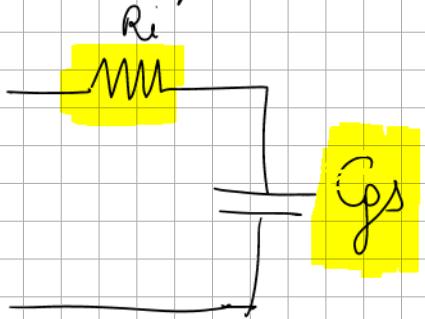Equivalent parallel circuit at the output



\equiv

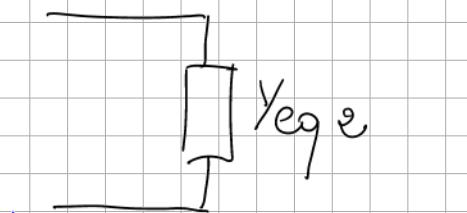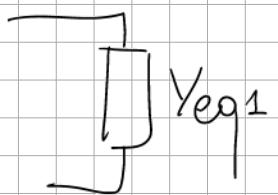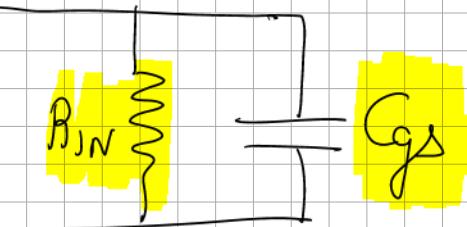

$$Z_{eq1} = R_i + \frac{1}{j G_s \omega} = \frac{1 + j R_i G_s \omega}{j G_s \omega}$$

$$Y_{eq1} = \frac{j G_s \omega}{1 + j R_i G_s \omega}$$

$$= \frac{j G_s \omega (1 - j R_i G_s \omega)}{1 + (R_i G_s \omega)^2}$$

$f \ll f_{LP}$





$$|R_i G_s \omega| \ll 1$$

$$Y_{eq2} = \frac{1}{R_{IN}} + j G_s \omega$$


$$(R_i G_s \omega)^2$$

$$j G_s \omega$$
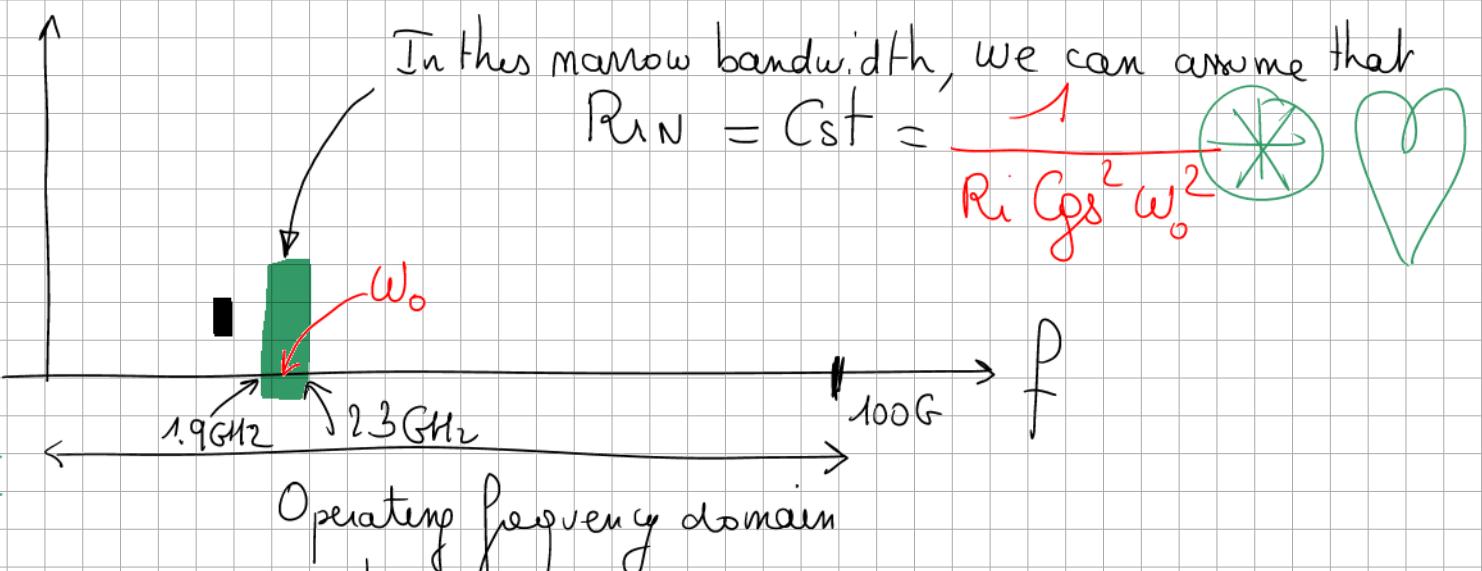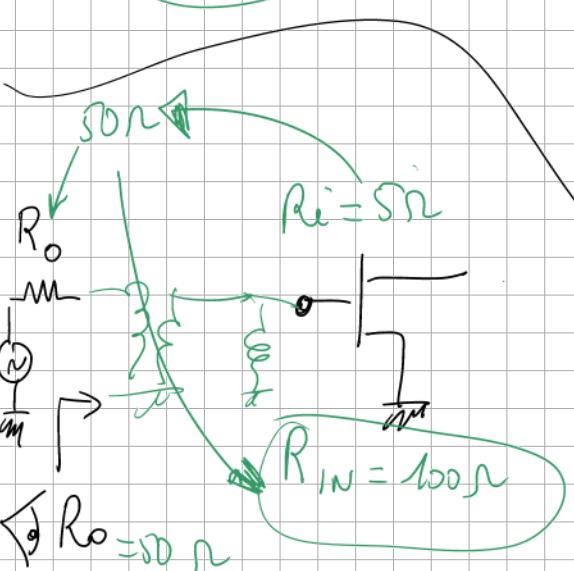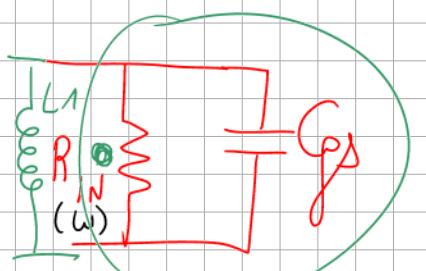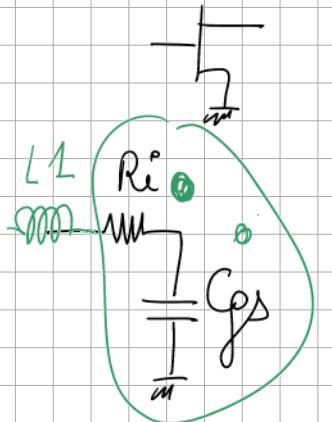
$$R_{IN} = \frac{1}{R_i G_s^2 \omega^2} = R_{IN}(\omega)$$





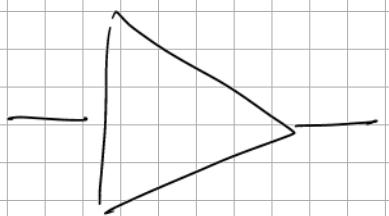
e.g.: $R_i = 4 \Omega$
 $C_{gs} = 2 \text{ pF}$



$\leftrightarrow R_{IN} = 10$


$R_o \propto R_{IN}$

II – Intrinsic figures of merit for FETs

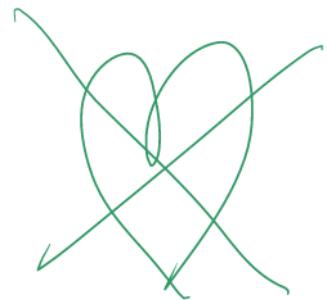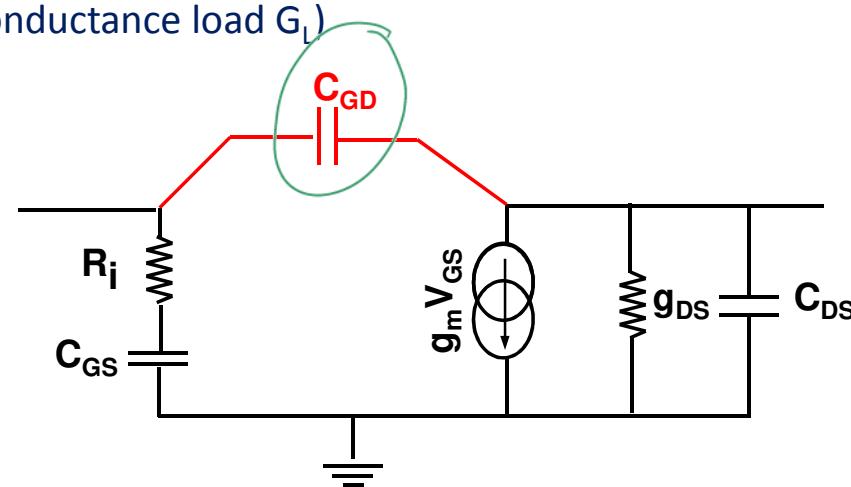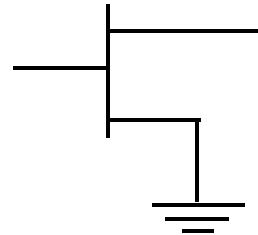3) Miller Effect (Feedback admittance Y_R and conductance load G_L)

II – Intrinsic figures of merit for FETs

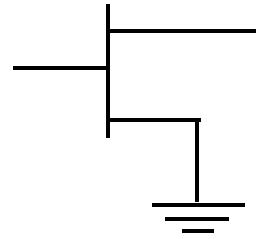3) Miller Effect (Feedback admittance Y_R and conductance load G_L)




$$Y_R = j C_{GD} \omega$$

$$Y_R = j C_{GD} \omega$$




$$Y_{GS} = \frac{1}{R_i + \frac{1}{j C_{GS} \omega}}$$
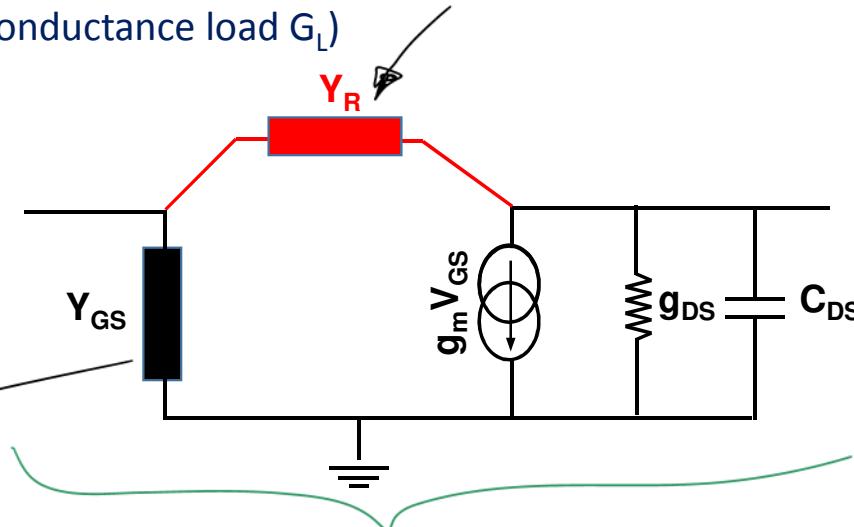
$$Y_{GS} = \frac{1}{R_{IN}} + j C_{GS} \omega$$





II – Intrinsic figures of merit for FETs

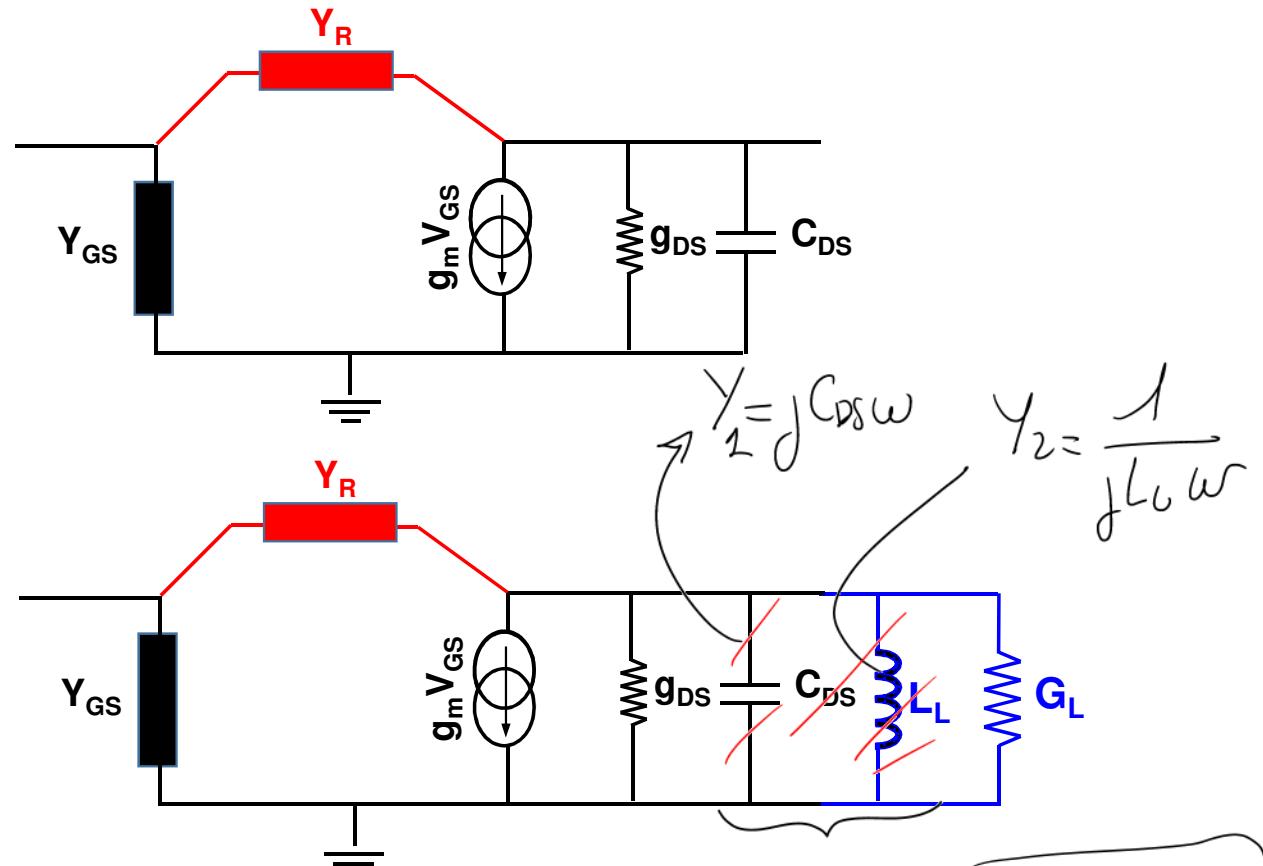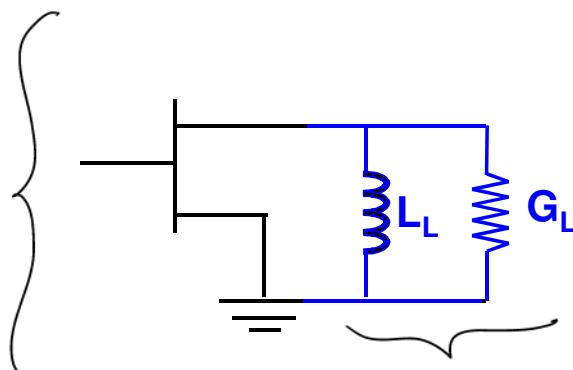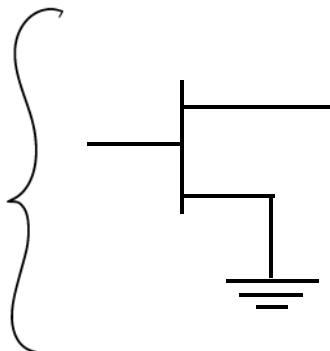3) Miller Effect (Feedback admittance Y_R and conductance load G_L)





$$Y_1 + Y_2 = 0 \rightarrow \Leftrightarrow j C_{DS} \omega = \frac{-1}{j L_L \omega} \Rightarrow \boxed{L_L C_{DS} \omega^2 = 1}$$

II – Intrinsic figures of merit for FETs

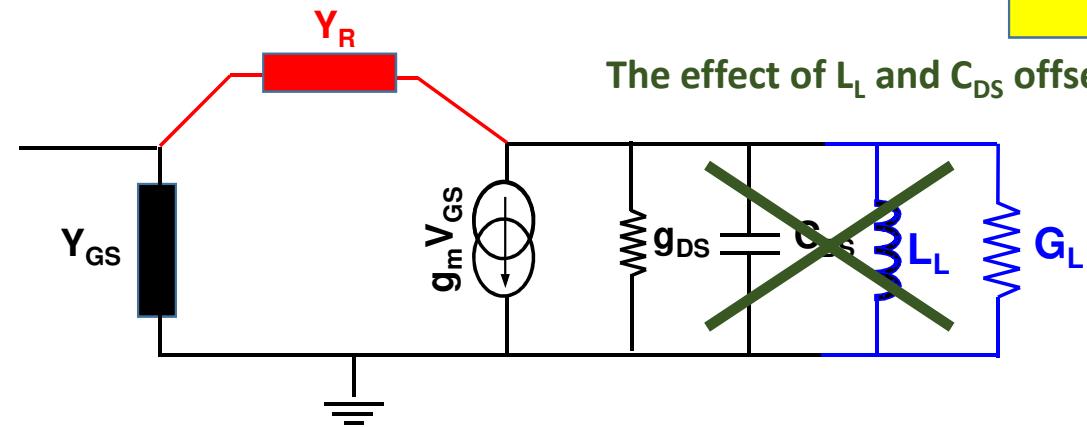
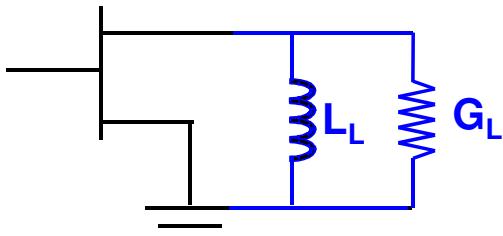
3) Miller Effect (Feedback admittance Y_R and conductance load G_L)

$$L_L C_{DS} \omega_0^2 = 1 \rightarrow \textcolor{blue}{L_L} = \frac{1}{C_{DS} \omega_0^2}$$

II – Intrinsic figures of merit for FETs

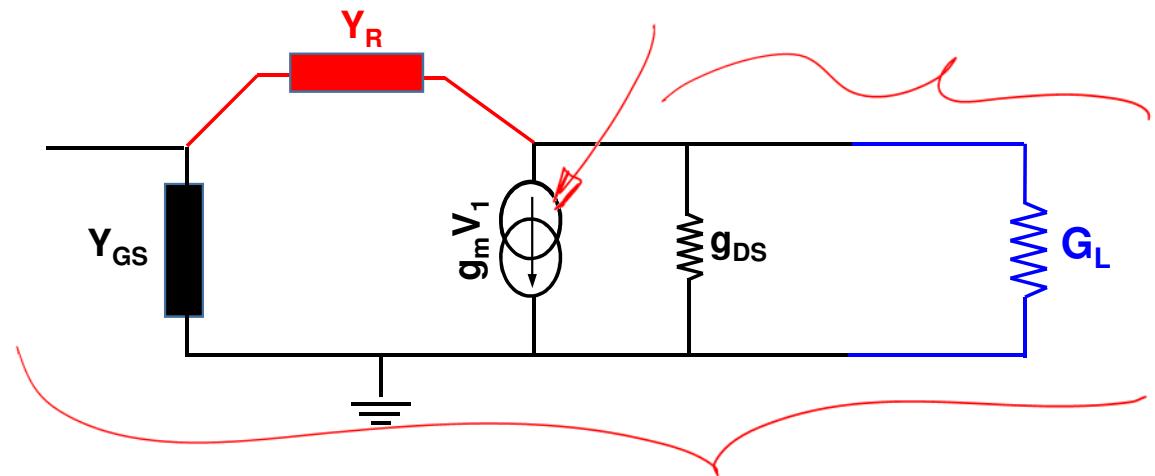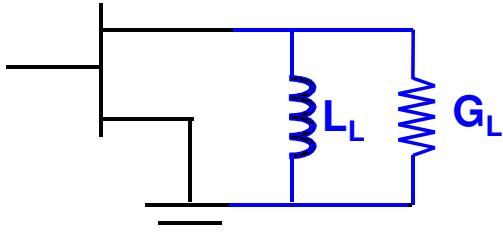3) Miller Effect (Feedback admittance Y_R and conductance load G_L)


II – Intrinsic figures of merit for FETs

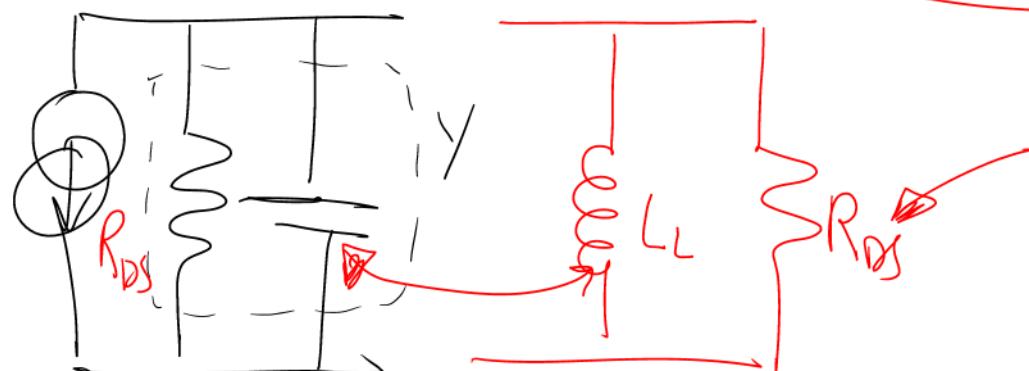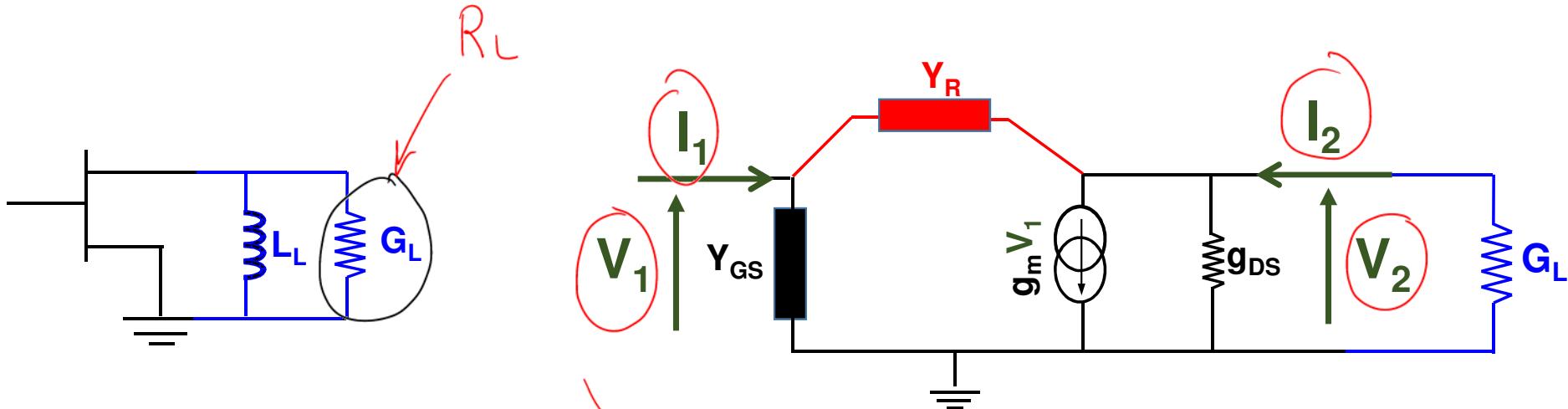3) Miller Effect (Feedback admittance Y_R and conductance load G_L)

II – Intrinsic figures of merit for FETs

3) Miller Effect (Feedback admittance Y_R and conductance load G_L)

a) Voltage gain G_V

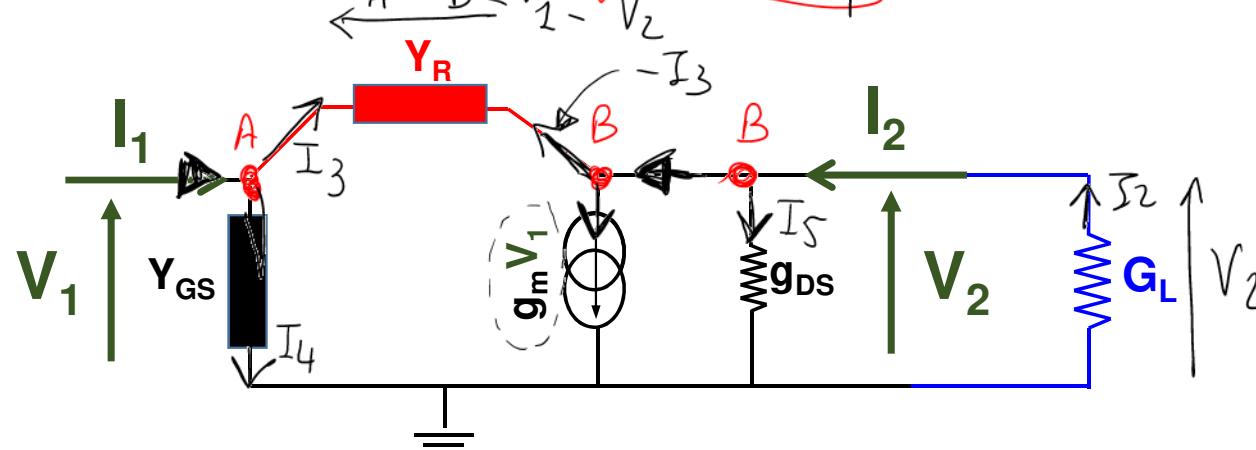

$$G_V = \frac{V_2}{V_1} = -\frac{g_m - Y_R}{g_{DS} + G_L + Y_R}$$

$$\frac{V_A - V_B}{V_1 - V_2} \approx \frac{V_A - V_B}{V_1 - V_2}$$

$$-\frac{g_m}{g_{DS} + G_L} \rightarrow -\frac{g_m}{2g_{DS}}$$

$$Z = \frac{V}{I}$$

$$V = Z I$$

$$I = Y V$$

$$\textcircled{1} \quad I_1 = I_3 + I_4 = Y_R (V_1 - V_2) + Y_{GS} V_1$$

$$\textcircled{2} \quad I_2 = I_5 + g_m V_1 - I_3 = g_{DS} V_2 + g_m V_1 - Y_R (V_1 - V_2) = -G_L V_2$$

$$Q \rightarrow V_2 \left[g_{DS} + Y_R + G_L \right] = \left(-g_m + Y_R \right) V_1$$

· ↴

$$\frac{V_2}{V_1} = \frac{-g_m + Y_R}{g_{DS} + G_L + Y_R} = -\frac{(g_m - Y_R)}{g_{DS} + G_L + Y_R}$$


$$Y_{IN} = \frac{I_1}{V_1}$$

II – Intrinsic figures of merit for FETs

3) Miller Effect (Feedback admittance Y_R and conductance load G_L)

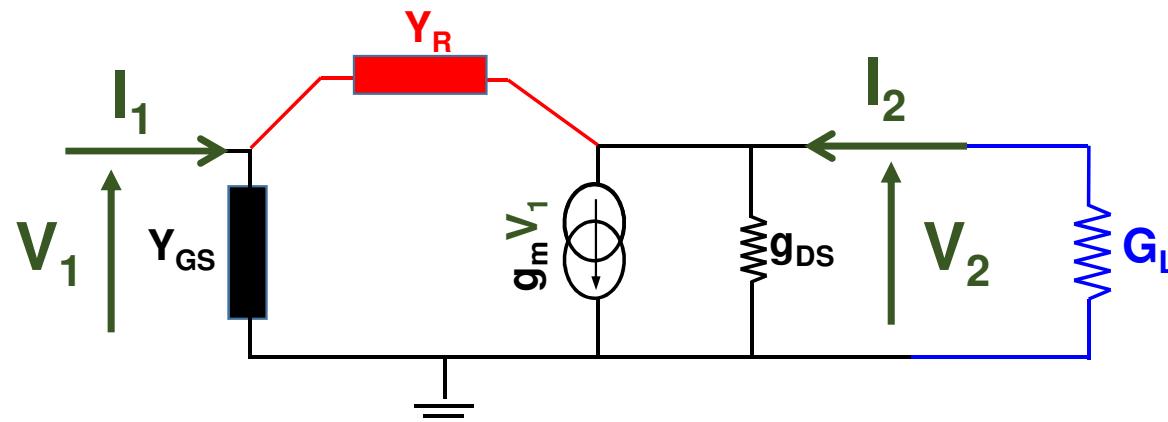b) Input admittance Y_{IN}


$$Y_{IN} = \frac{I_1}{V_1} = Y_{GS} + Y_R[1 - G_V]$$




$$\textcircled{1} \quad I_1 = Y_{GS} V_1 + Y_R (V_1 - V_2) \rightarrow Y_{IN} = \frac{I_1}{V_1} = Y_{GS} + Y_R (1 - G_V)$$

In the case of FETs, $|G_V| \gg 1$

G_V negative

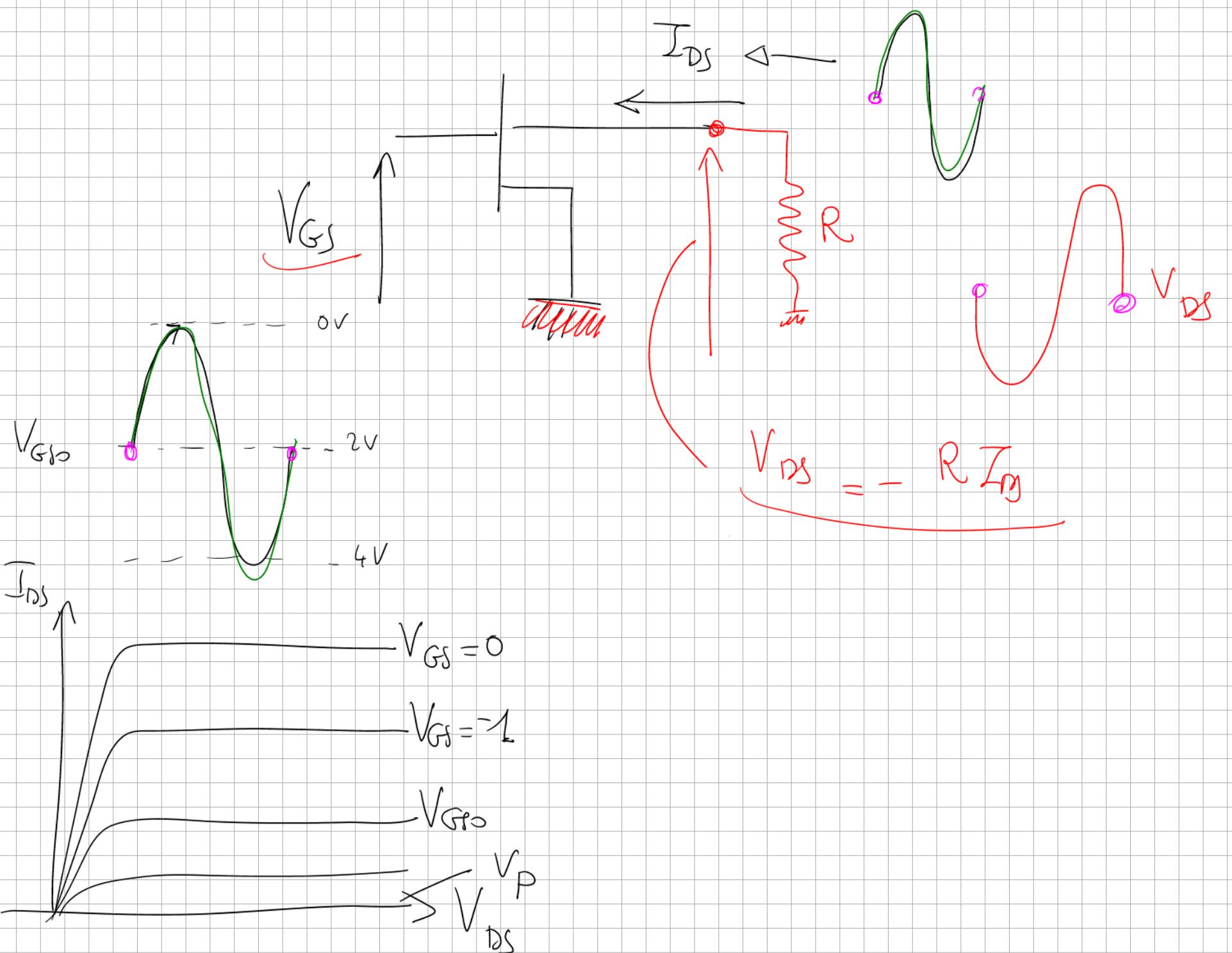

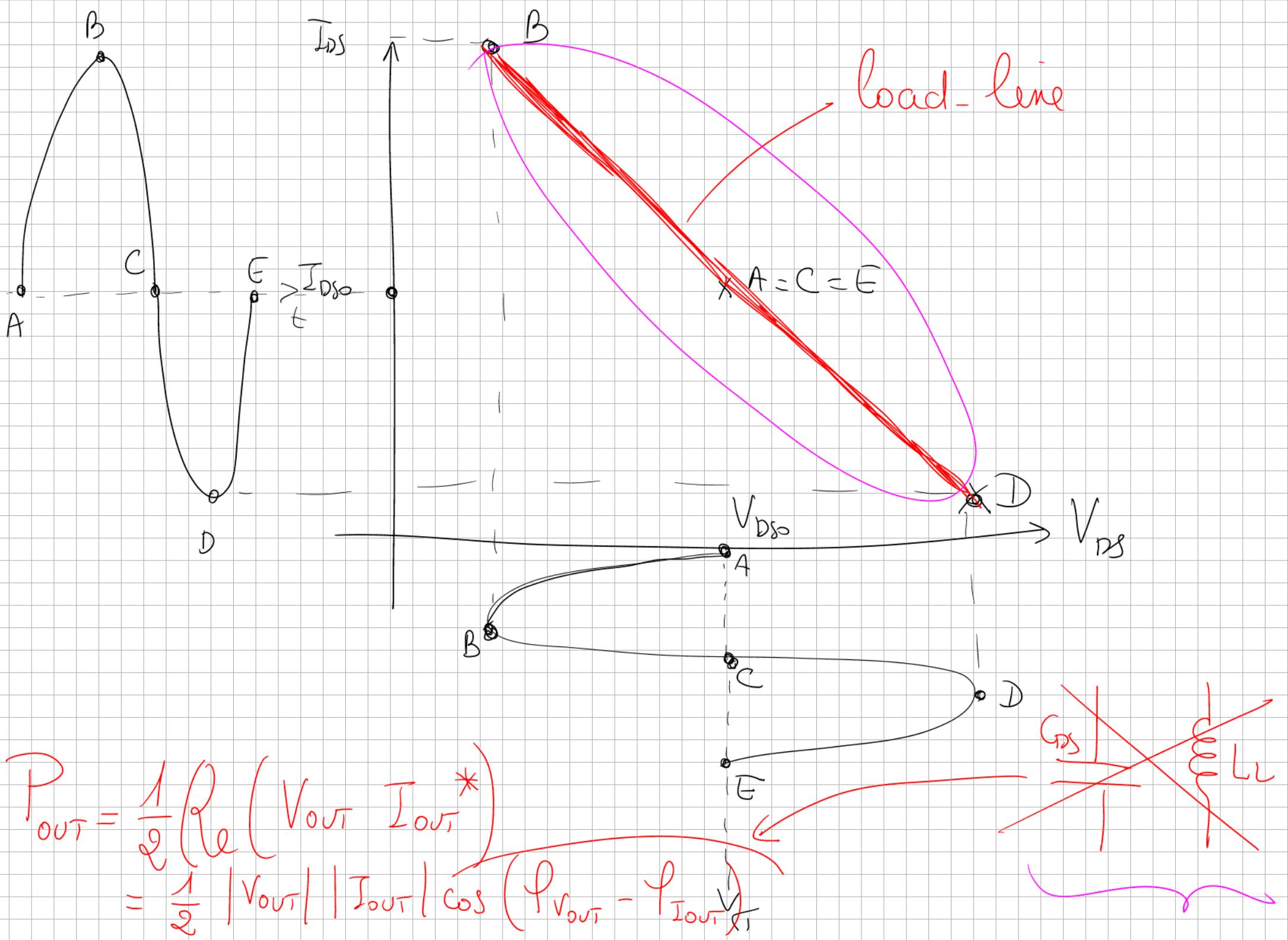


II – Intrinsic figures of merit for FETs

3) Miller Effect (Feedback admittance Y_R and conductance load G_L)

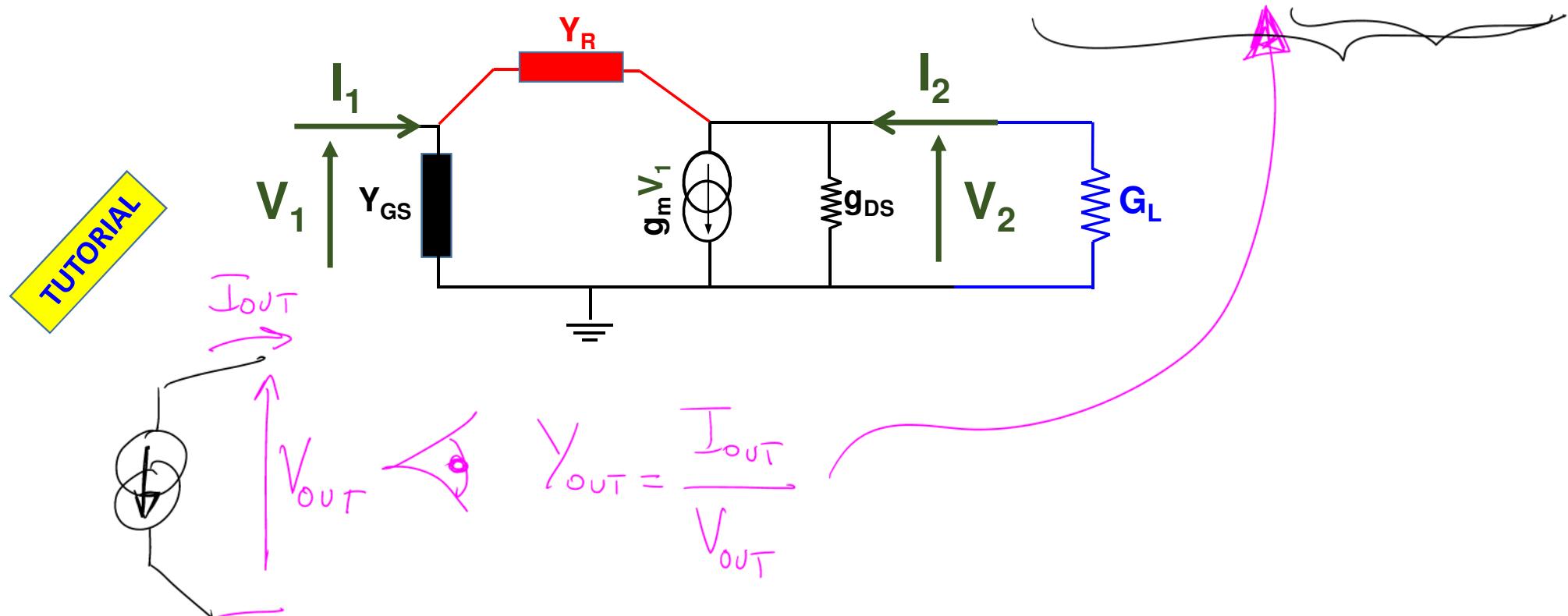c) Output admittance seen by the drain current source Y_{OUT}

$$Y_{OUT} = \frac{-g_m V_1}{V_2} = g_{DS} + G_L + Y_R \left[1 - \frac{1}{G_V} \right]$$



$$① I_1 = Y_{GS} V_1 + Y_R (V_1 - V_2)$$

$$② I_2 = g_{DS} V_2 + \underbrace{g_m V_1}_{+} + Y_R (V_2 - V_1) = -G_L V_2$$

$$Y_{OUT} = \frac{I_{OUT}}{V_{OUT}} = \frac{-g_m V_1}{V_2} = \frac{-g_m}{G_V} = \frac{-g_m}{\cancel{g_m - Y_R}}$$

$$\Rightarrow g_m V_1 = -g_{DS} V_2 - Y_R (V_2 - V_1) - G_L V_2$$

$$\Rightarrow Y_{OUT} = \frac{-g_m V_1}{V_2} = g_{DS} + Y_R \left(1 - \frac{V_1}{V_2} \right) + G_L$$

$$Y_{OUT} = g_{DS} + G_L + \left(Y_R \left(1 - \frac{1}{G_V} \right) \right)$$




II – Intrinsic figures of merit for FETs

3) Miller Effect (Feedback admittance Y_R and conductance load G_L)


b) Input admittance Y_{IN}

$$Y_{IN} = Y_{GS} + Y_R [1 - G_V]$$

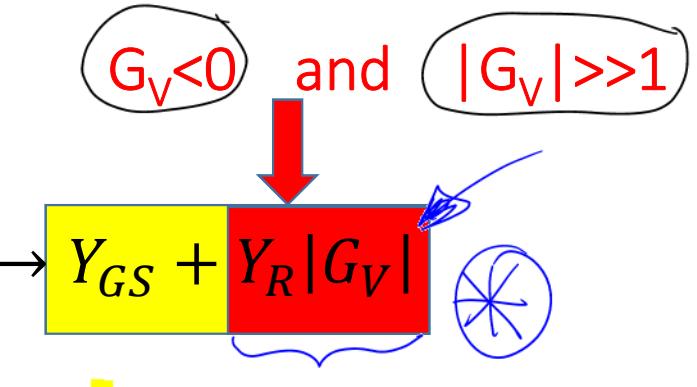

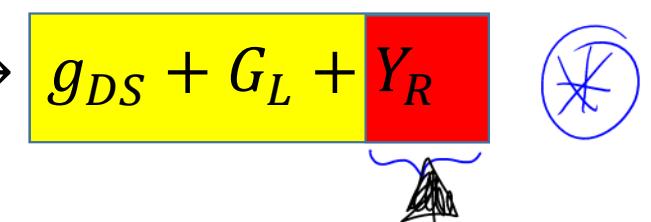c) Output admittance seen by the drain current source Y_{OUT}

$$Y_{OUT} = g_{DS} + G_L + Y_R \left[1 - \frac{1}{G_V} \right]$$



$$1 - \frac{1}{G_V} = 1 + \frac{1}{|G_V|}$$

$$1 - G_V = 1 + |G_V| \rightarrow |G_V|$$


because $G_V < 0$

$$|G_V| \gg 1$$

$$j C_{GD} \omega$$

II – Intrinsic figures of merit for FETs

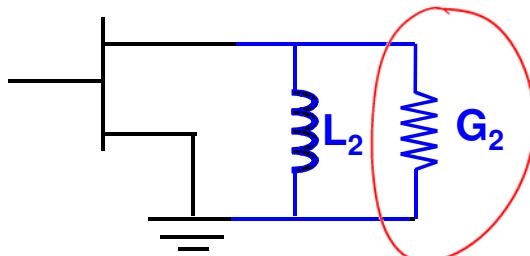
3) Maximum Power Gain G_{MAX} → Simplified Electrical Small-Signal FET Model



$$Y_R = j C_{GD} \omega$$

$$C_{GS} = C_{GS} + |G_V| G_d$$
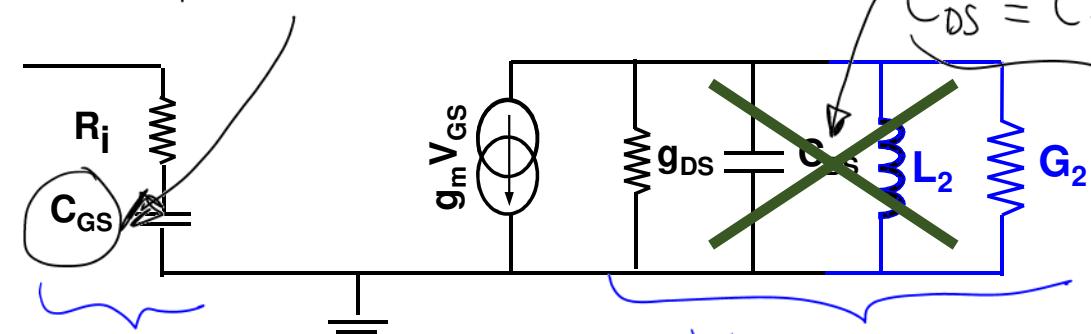
$$L_2 C_{DS} \omega^2 = 1 \rightarrow L_2 = \frac{1}{C_{DS} \omega^2}$$




$$Y_{IN} = Y_{GS}$$

$$Y_{IN} = \frac{1}{R_{IN}} + j C_{eq} \omega + j |G_V| C_{GD} \omega$$

$$j C_{eq} \omega \text{ where } C_{eq} = C_{GS} + |G_V| C_{GD}$$

II – Intrinsic figures of merit for FETs


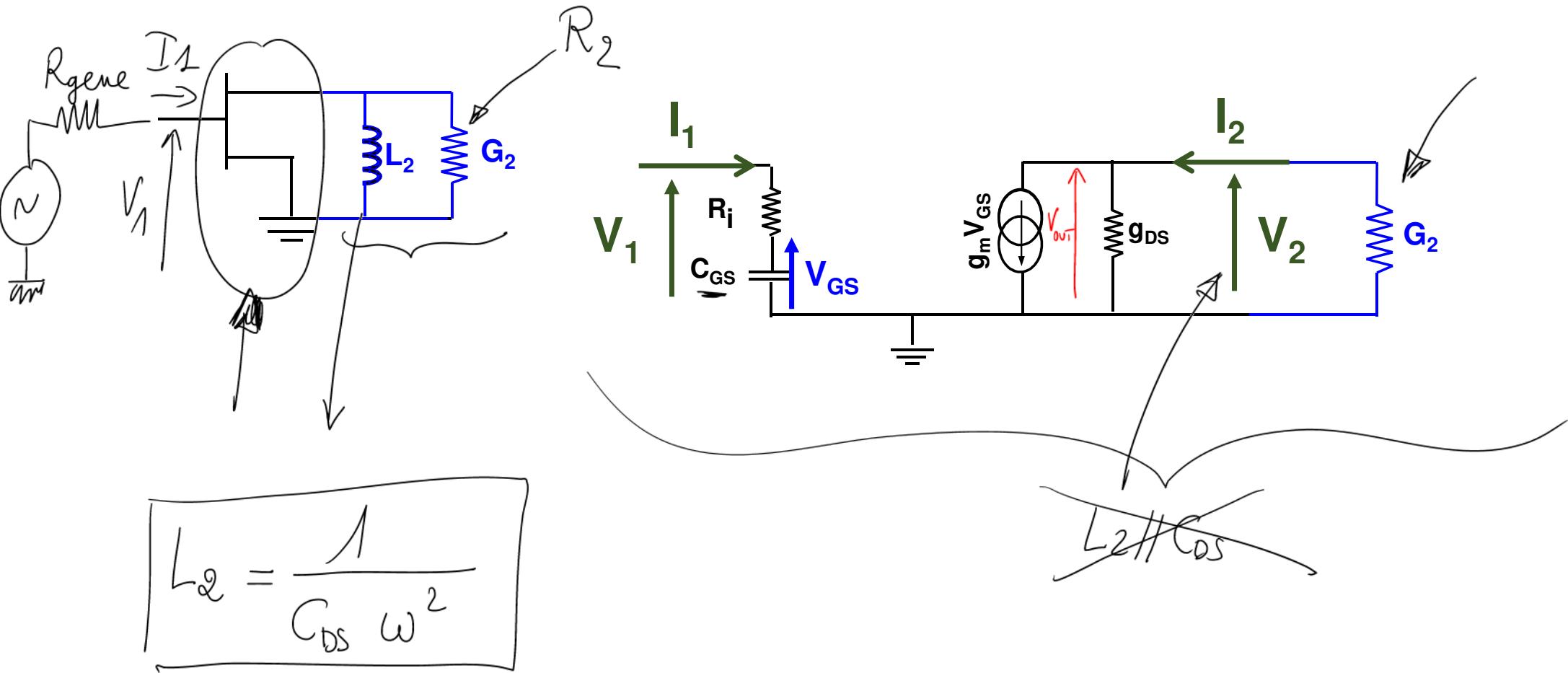
3) Maximum Power Gain G_{MAX} → Simplified Electrical Small-Signal FET Model



II – Intrinsic figures of merit for FETs

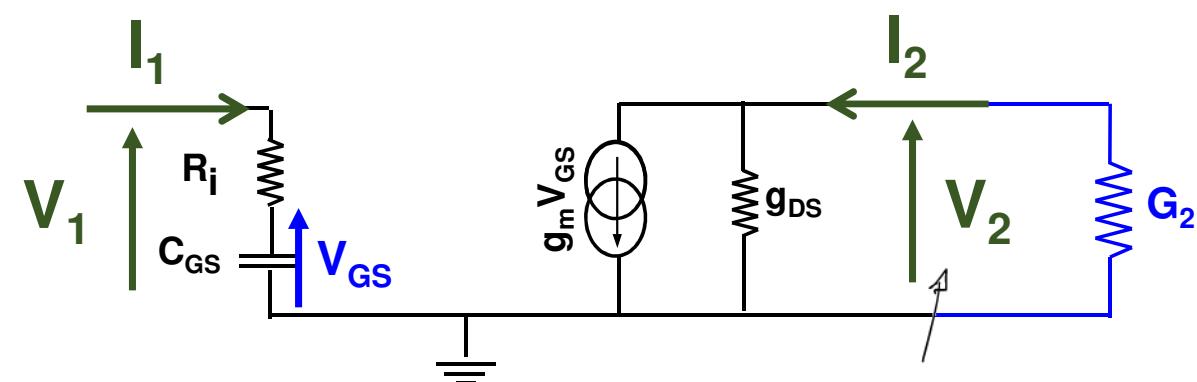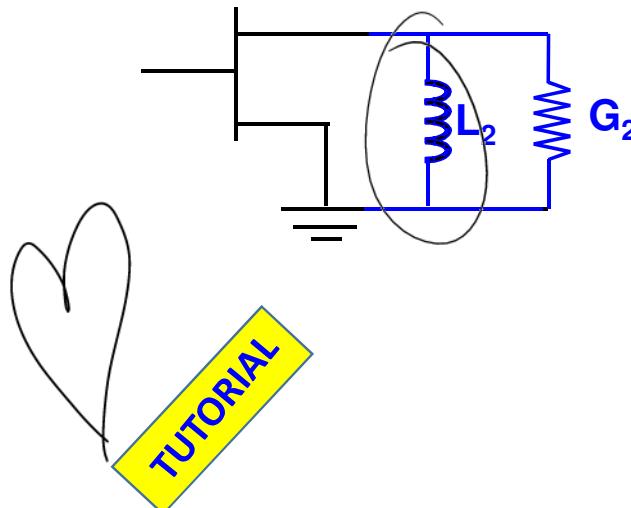3) Maximum Power Gain G_{MAX} → Simplified Electrical Small-Signal FET Model

$$\textcircled{1} R_2 = R_{DS} \quad \text{or} \quad R_2 = R_{out} \textcircled{2}$$




$$R_{DS} \left(g_m V_{GS} \right)$$

General case ($G_2 \neq g_{DS}$) → Not maximum Power Gain G_P

$$\left. \begin{aligned} P_{IN} &= \frac{1}{2} \operatorname{Re} (V_1 I_1^*) \\ P_{OUT} &= \frac{1}{2} \operatorname{Re} (V_{OUT} I_{OUT}^*) \end{aligned} \right\}$$
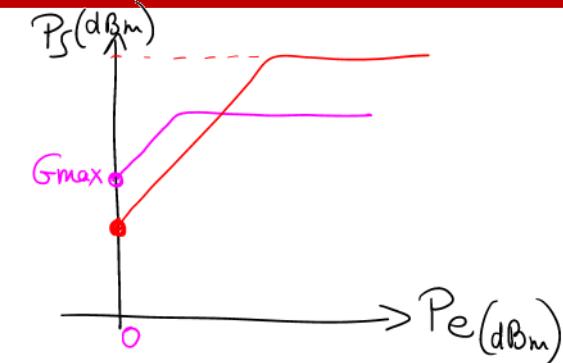
$$G_P = \frac{G_2}{[G_2 + g_{DS}]^2} \frac{g_m^2}{R_i C_{GS}^2 \omega^2}$$




Calculation of Input Power


$$I_1 = j G_s \omega \times V_{GS}$$


$$V_1 = \left(R_i + \frac{1}{j G_s \omega} \right) I_1$$

$$\begin{aligned} \operatorname{Re}(V_1 I_1^*) &= \operatorname{Re} \left[\left(R_i + \frac{1}{j G_s \omega} \right) \underbrace{I_1 I_1^*}_{|I_1|^2} \right] = |I_1|^2 \operatorname{Re} \left(R_i + \frac{1}{j G_s \omega} \right) \\ P_{IN} &= \frac{1}{2} R_i G_s^2 \omega^2 |V_{GS}|^2 \end{aligned}$$

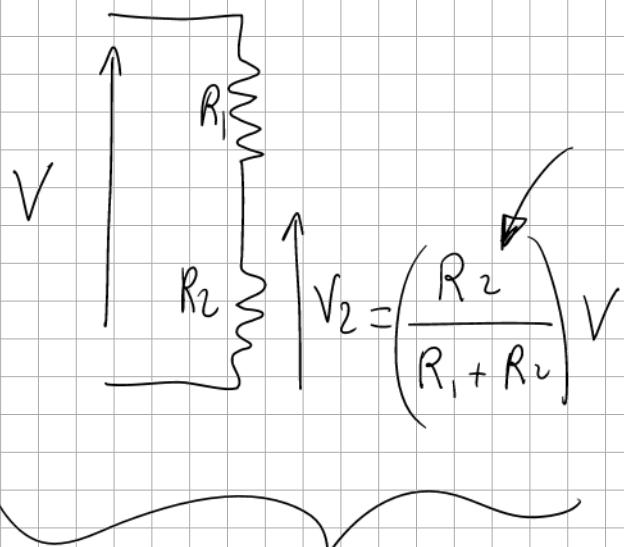

Voltage Div. der

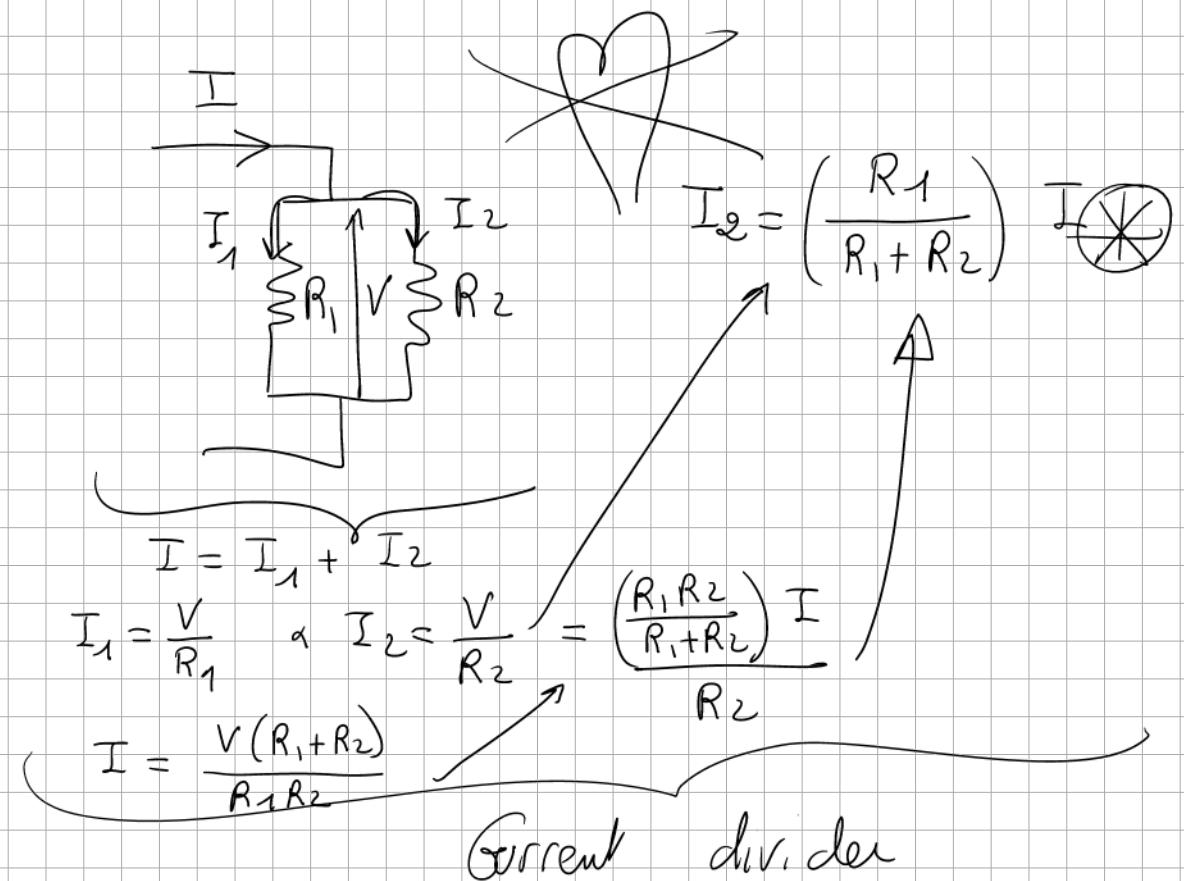

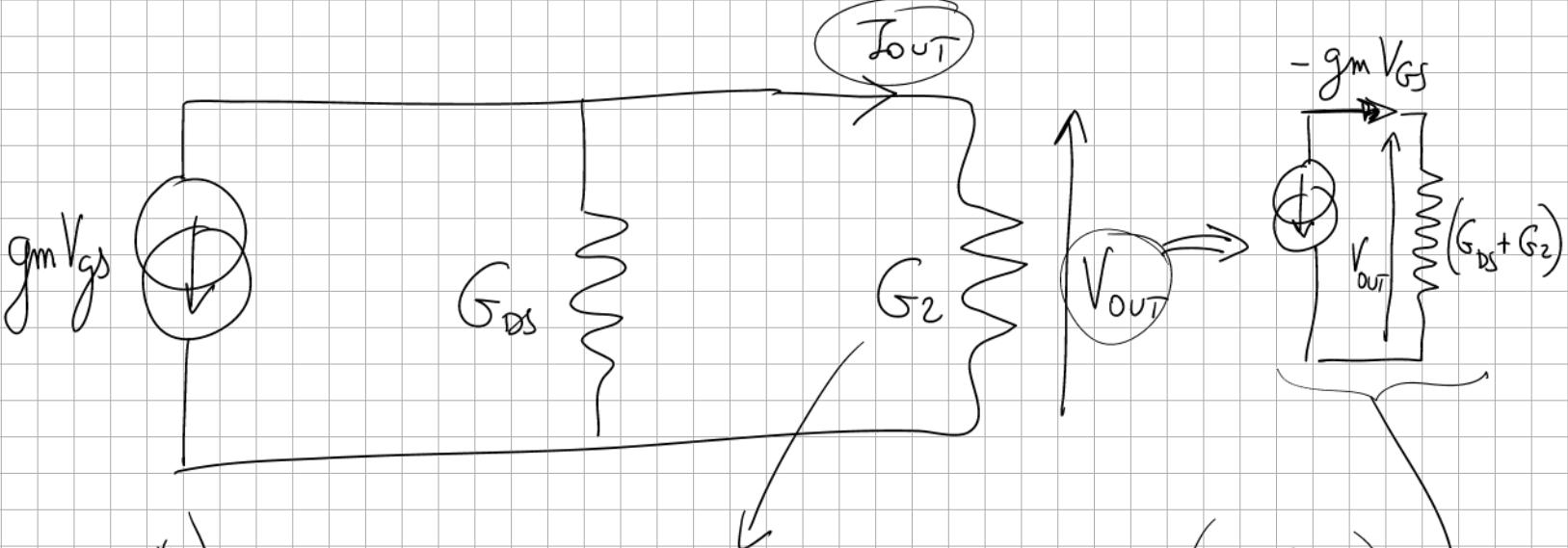

$$P_{\text{out}} = \frac{1}{2} \operatorname{Re} (V_{\text{out}} I_{\text{out}}^*)$$

$$I_{\text{out}} = G_2 V_{\text{out}}$$

$$V_{\text{out}} = (V_{\text{gs}})$$

$$= \frac{1}{2} \operatorname{Re} (V_{\text{out}} (G_2 V_{\text{out}})^*)$$


$$= \frac{1}{2} \operatorname{Re} \left(V_{\text{out}} V_{\text{out}}^* \underbrace{|V_{\text{out}}|^2}_{G_2} \right)$$

$$V_{\text{out}} = \frac{-g_m V_{\text{gs}}}{G_2 + G_{\text{DS}}}$$

$$P_{\text{out}}$$

$$= \frac{1}{2} G_2 |V_{\text{out}}|^2 = \frac{1}{2} G_2$$

$$\left| \frac{-g_m V_{\text{gs}}}{G_2 + G_{\text{DS}}} \right|^2 = \frac{1}{2} \frac{G_2}{(G_2 + G_{\text{DS}})^2} g_m^2 |V_{\text{gs}}|^2$$

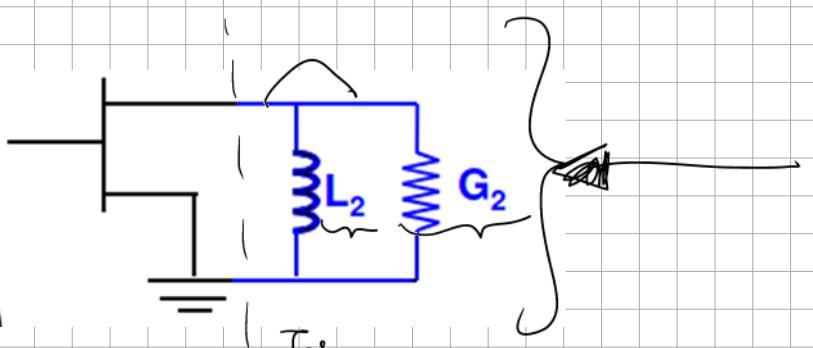


$$G_P = \frac{G_2}{[G_2 + g_{DS}]^2} g_m^2$$

$$\overline{I}_{DS} \uparrow \quad P_{OUT} = \frac{1}{2} |V_{out}| |\overline{I}_{out}| \cos(\phi_{V_{out}} - \phi_{I_{out}})$$



slope $\frac{1}{R_2} = G_2$

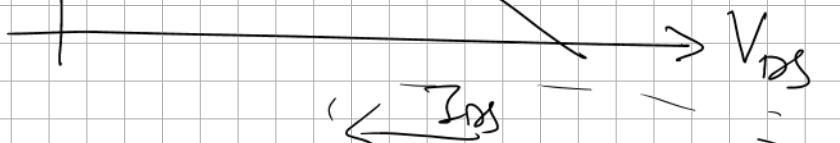


$$Y_{C_{DS}} = j G_{DS} \omega_0$$

$$Y_{L_2} = -\frac{j}{L_2 \omega_0}$$



$$(Y_{C_{DS}} + Y_{L_2} = 0 \text{ (compensation)})$$
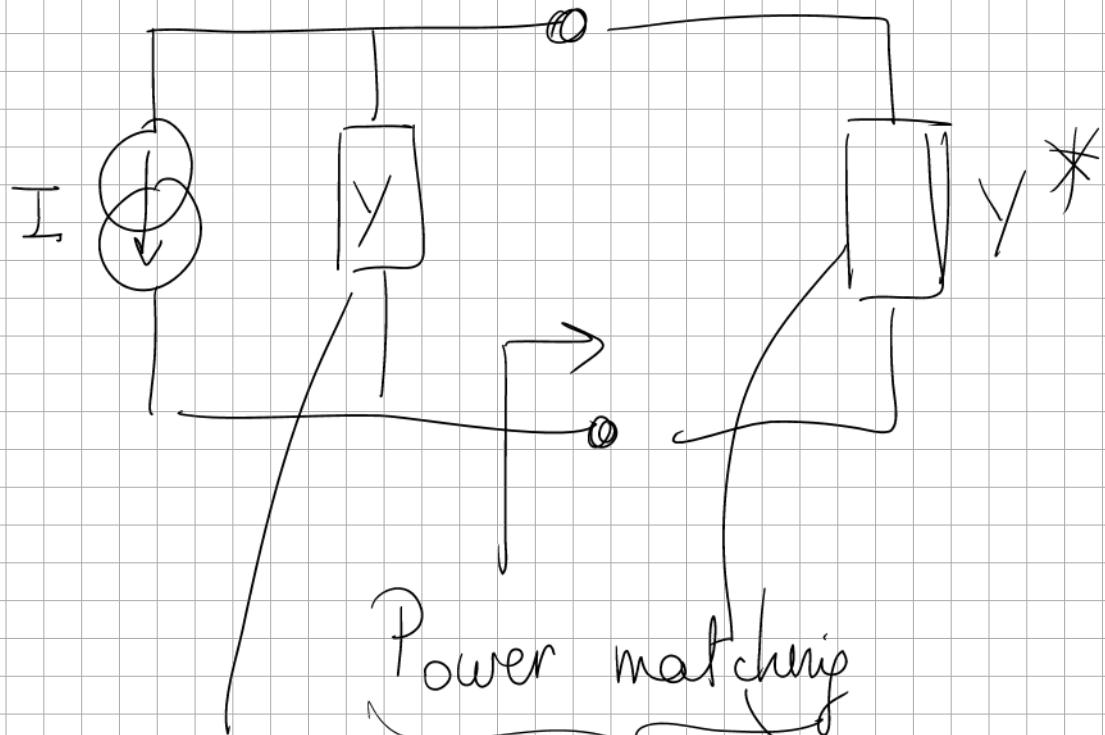
$$G_{DS} \omega_0 = \frac{1}{L_2 \omega_0} \Rightarrow L_2 = \frac{1}{G_{DS} \omega_0^2}$$





Power matching

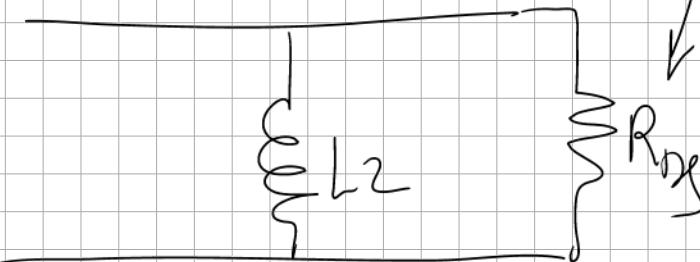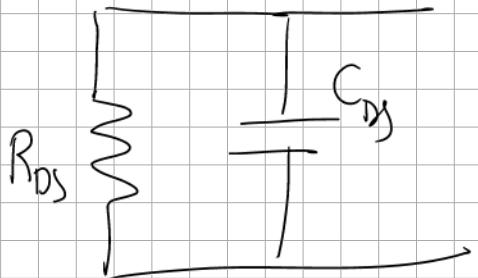

R_2

Maximum power gain $\Rightarrow G_{\max} (R_2 = R_{DS})$
 $G_2 = G_{DS}$


$$G_{\max} = \frac{R_{DS} g_m^2}{4 R_i G_s^2 \omega_o^2}$$

Difference between (Maximum power gain) and (Maximum output power)


$$R_L = R_{DS}$$

$$R_L = R_{opt}$$

I-V characteristic

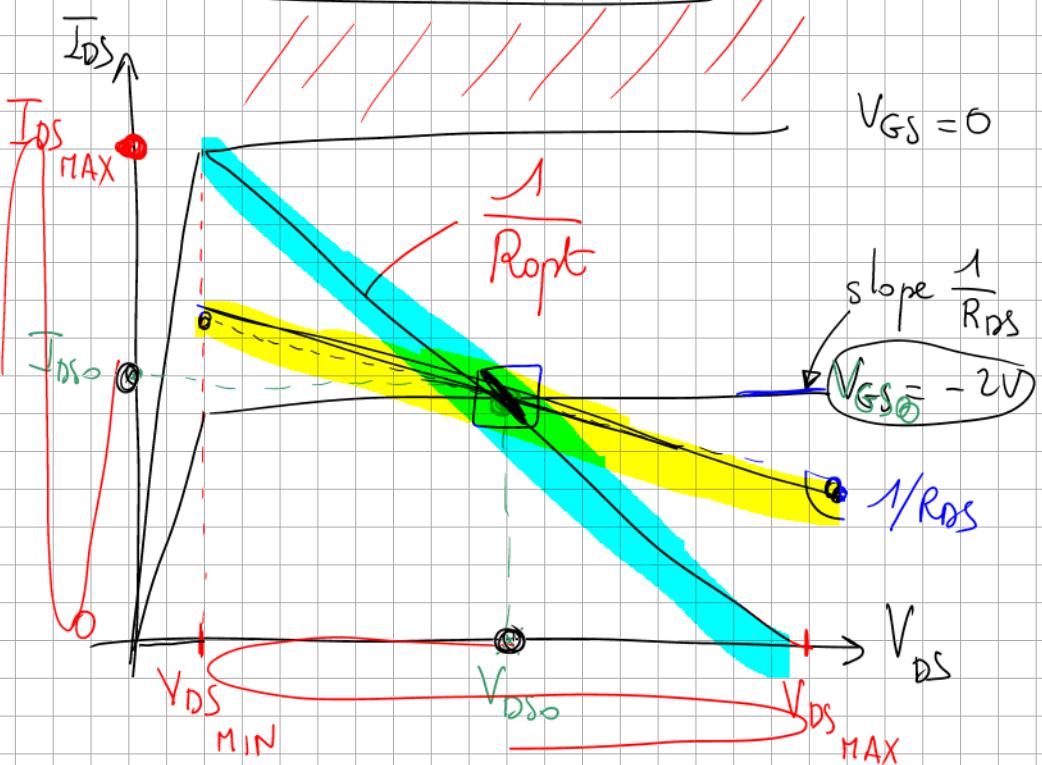

Power transfer characteristic

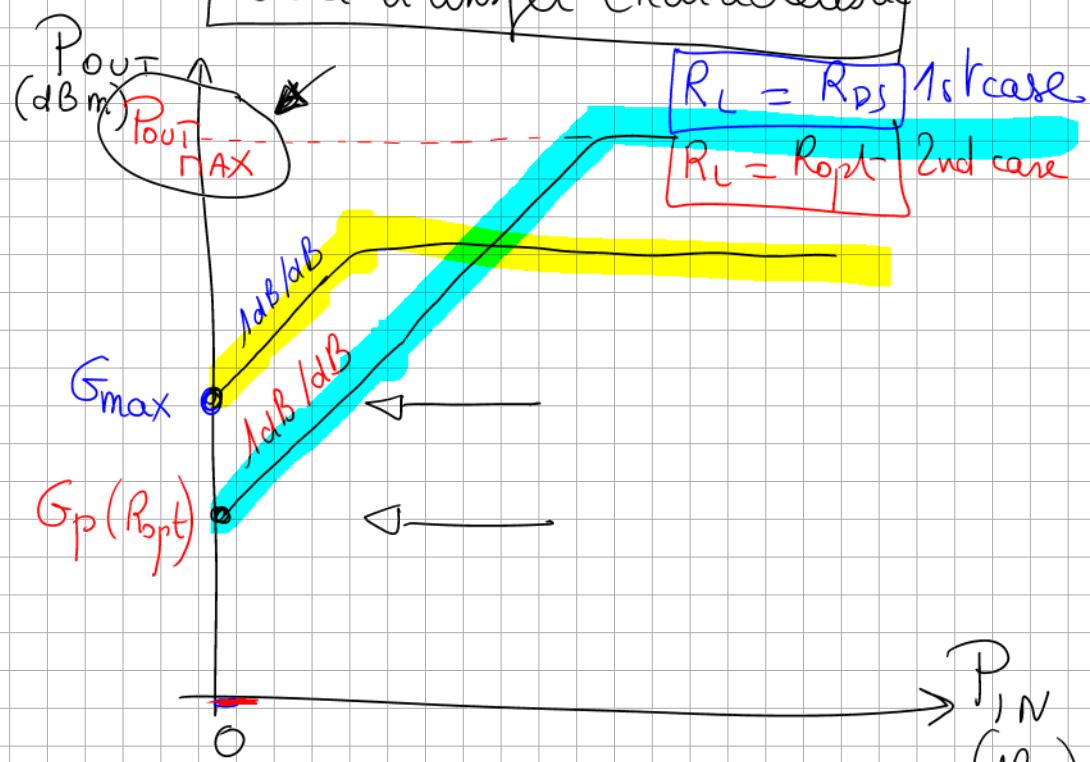


$$P_{out_max} = \frac{1}{2} Re(V I^*) = \frac{1}{2} |V| |I| \cos(\phi_V - \phi_I)$$

(A class)

$$P_{MAX} = \frac{1}{2} \times \frac{V_{DS_MAX} - V_{DS_MIN}}{2} \times \frac{I_{DS_MAX}}{2}$$

$$R_{opt} = \frac{V_{DS_MAX} - V_{DS_MIN}}{I_{DS_MAX}}$$

Class A

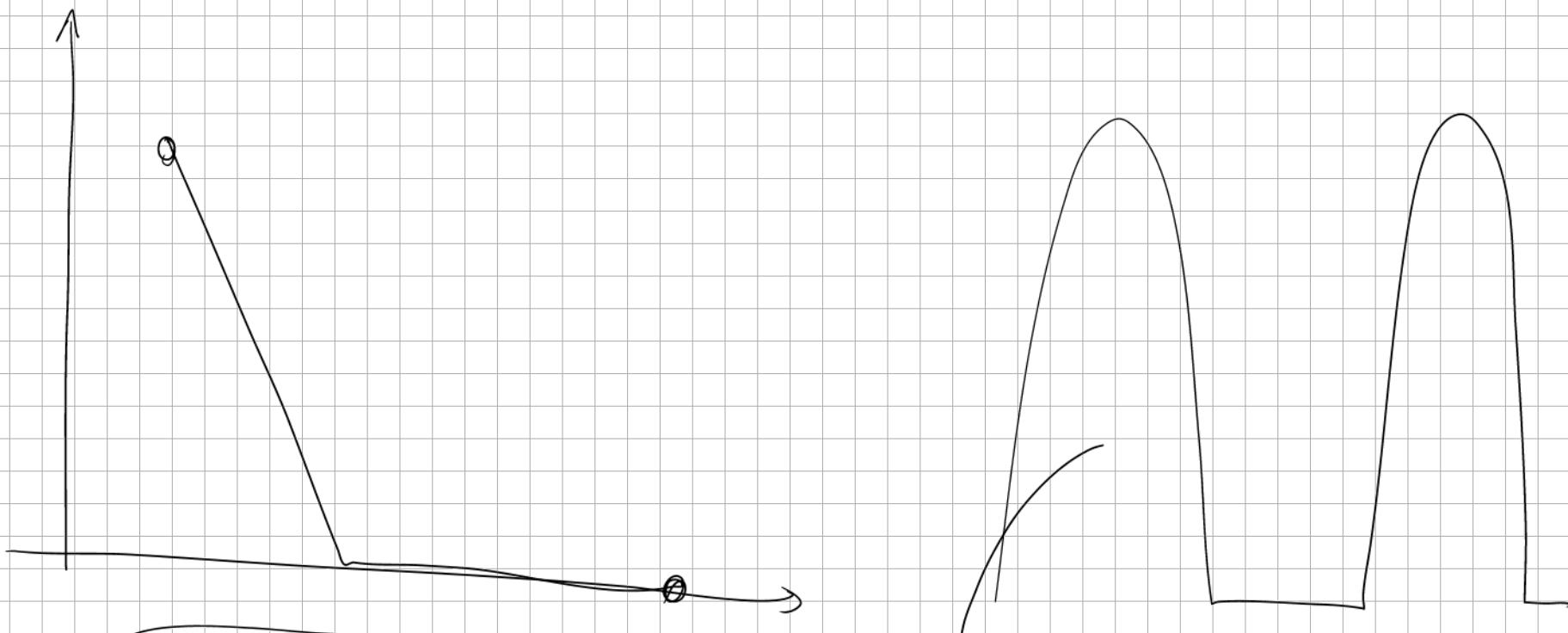


$$V_{DS} = V_{DS0} + \underline{V_{DS1}} \cos(\omega_0 t + \underline{\theta_1})$$


$$\underline{I_{DS0}} + \underline{I_{DS1}} \cos(\omega_0 t + \underline{\theta_1}) + \underline{I_{DS2}} \cos(\omega_0 t + \underline{\theta_2})$$


$$R_{opt}^t_{AB} \sim R_{opt}^t_A$$

$$\underbrace{R_{opt}^t}_B = \frac{V_{DS1}}{I_{DS1}} = \underbrace{R_{opt}^t}_A$$


easy to calculate

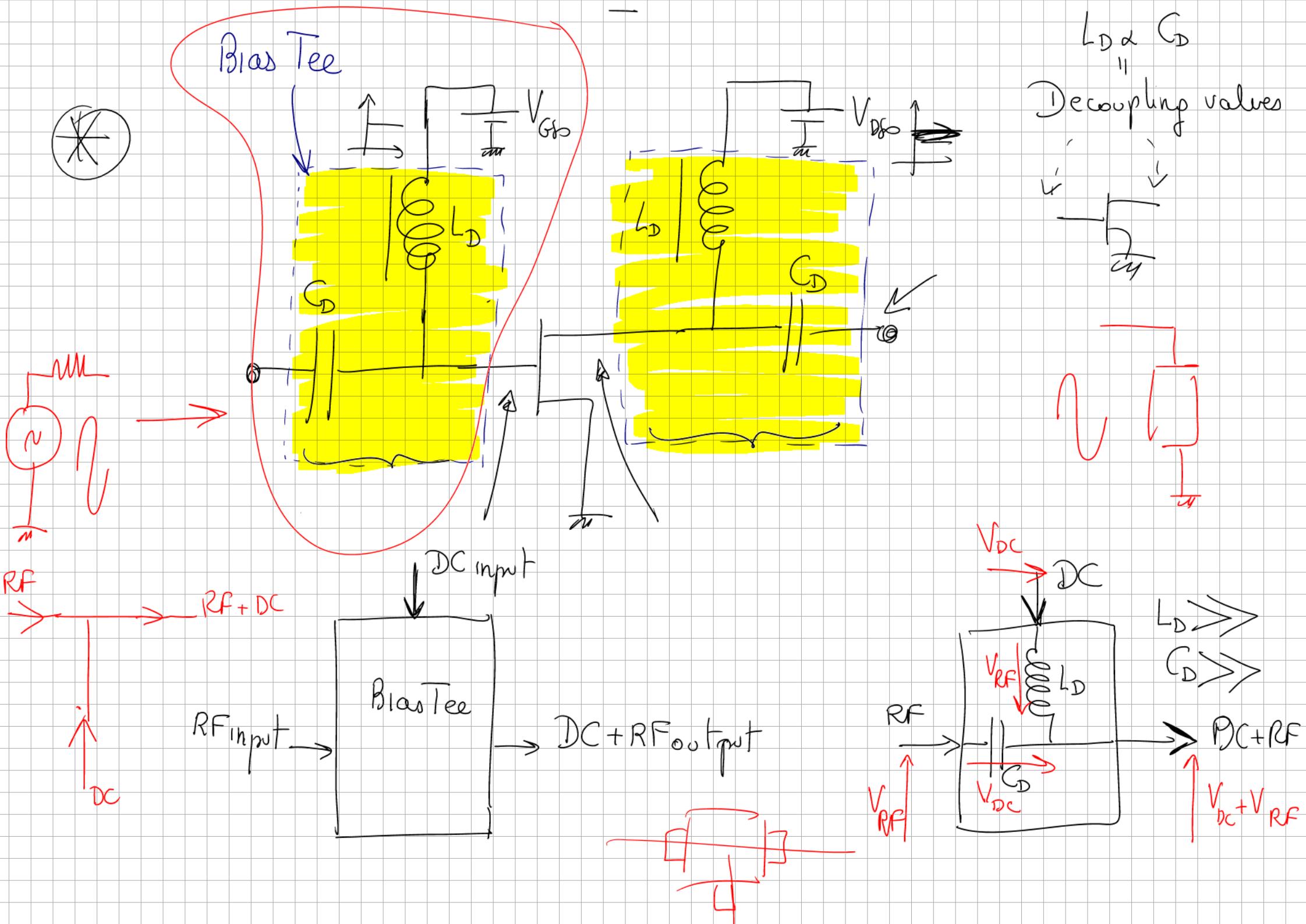

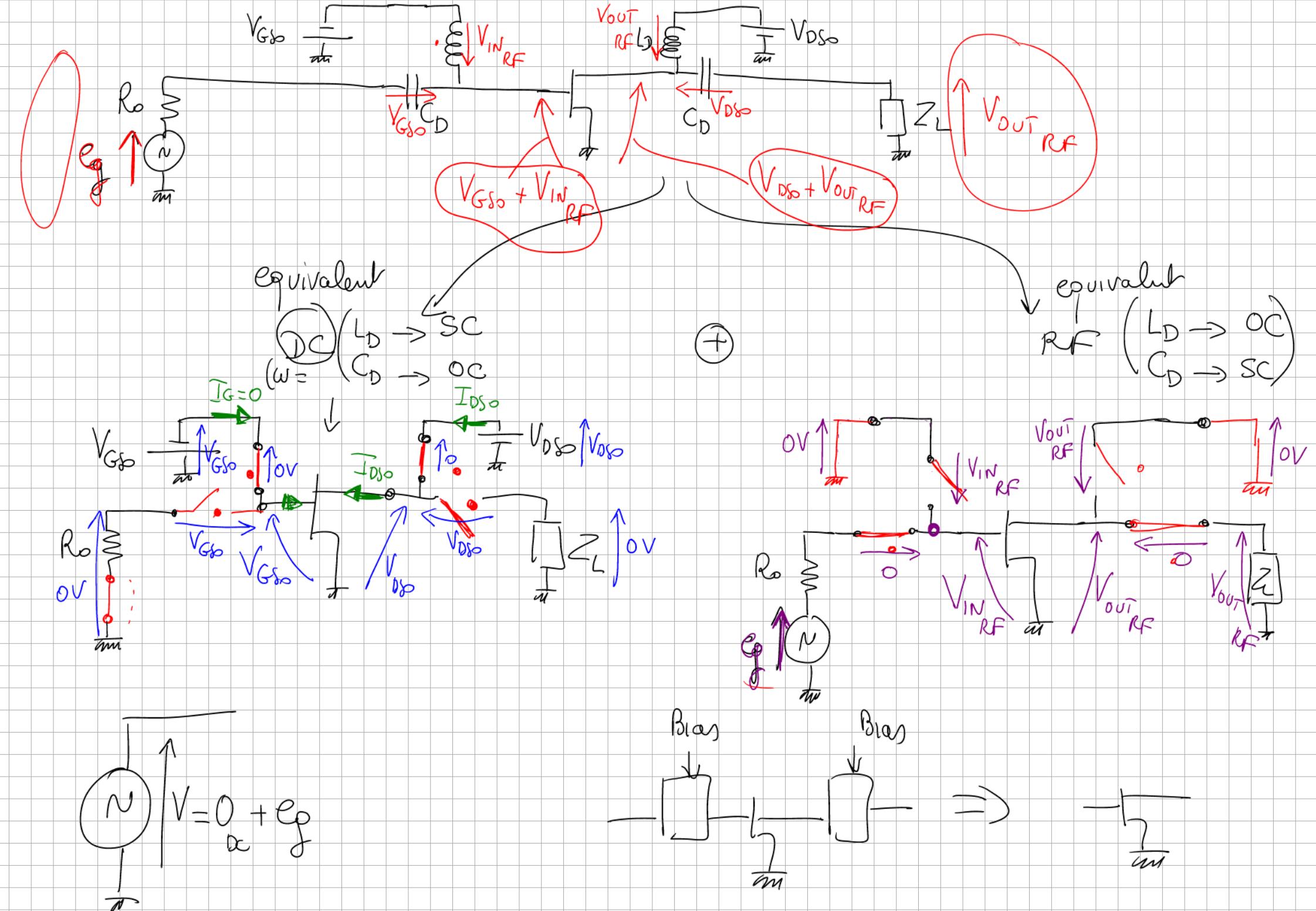


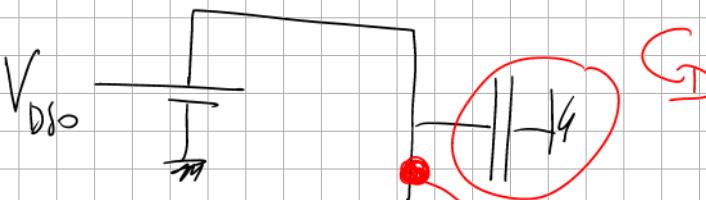



SC G RF ($Z_L = \infty$)

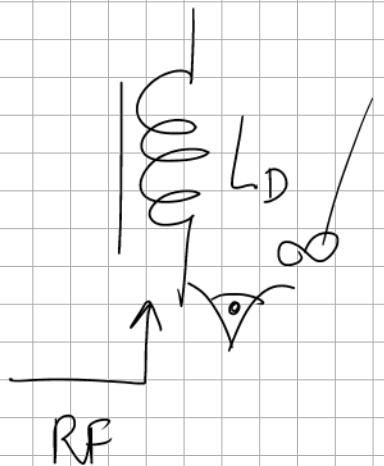

$$Z_{IN} = \frac{Z_0^2}{Z_L} = \infty \text{ OC}$$

$$\ell = \frac{d_0}{4}$$

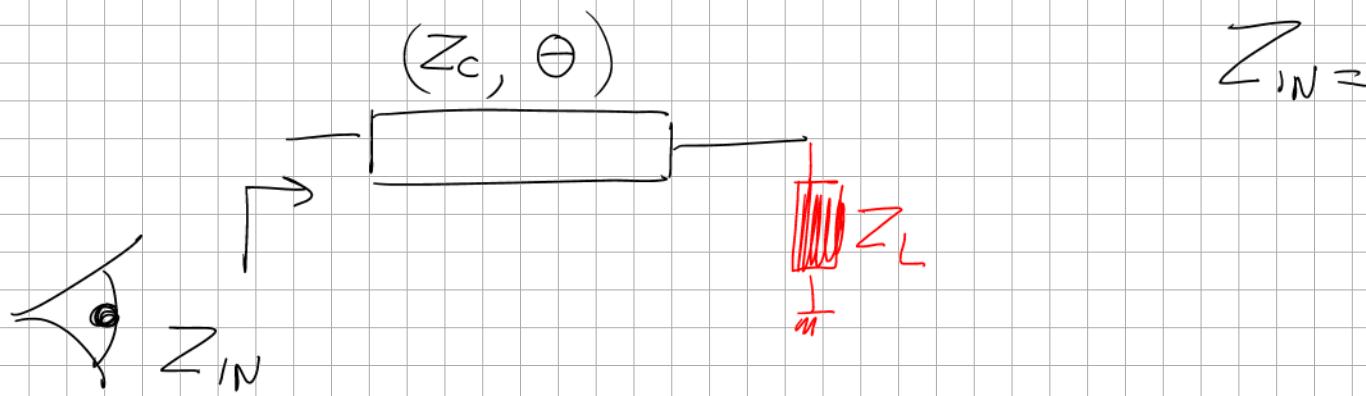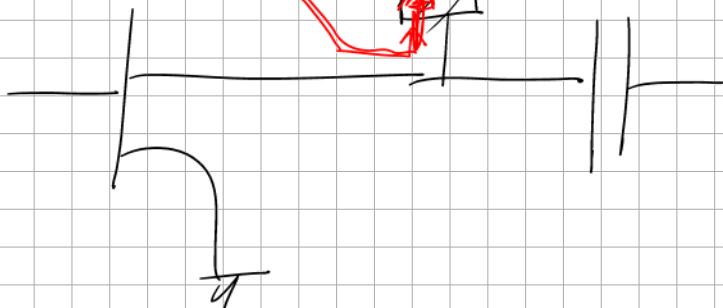

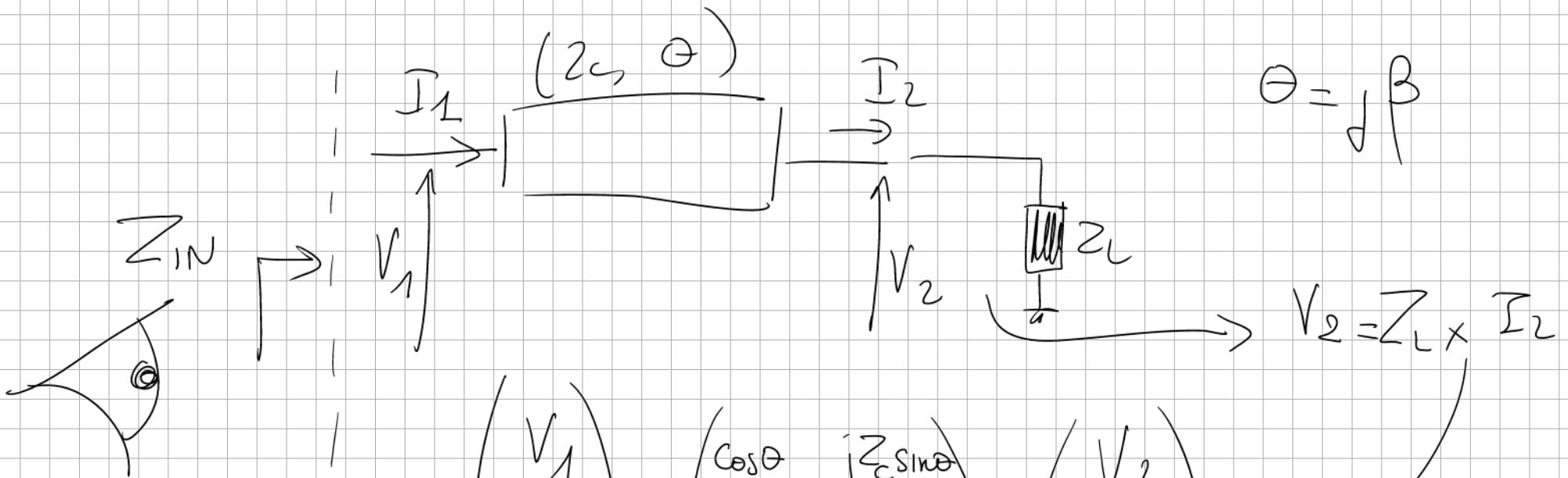

$$\begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \begin{pmatrix} \cos\theta & jZ_c \sin\theta \\ j \frac{\sin\theta}{Z_c} & \cos\theta \end{pmatrix} \begin{pmatrix} V_2 \\ I_2 \end{pmatrix}$$

$$Z_{IN} = \frac{V_1}{I_1} = \frac{\cos\theta V_2 + j Z_c \sin\theta I_2}{j \frac{\sin\theta}{Z_c} V_2 + \cos\theta I_2} = \frac{Z_L \cos\theta + j Z_c \sin\theta}{j \frac{\sin\theta}{Z_c} Z_L + \cos\theta}$$

$$\boxed{Z_{IN} = Z_c \frac{Z_L \cos\theta + j Z_c \sin\theta}{Z_c \cos\theta + j Z_L \sin\theta}}$$


if $\ell = \frac{d_0}{4} \Rightarrow \theta = 2\pi \frac{\ell}{d_0} = 2\pi \frac{d_0/4}{d_0} = \frac{\pi}{2}$

$Z_{IN} = \frac{Z_c}{Z_L}$


if $\ell = \frac{d_0}{2} \Rightarrow \theta = \pi \Rightarrow Z_{IN} = Z_L$

II – Intrinsic figures of merit for FETs

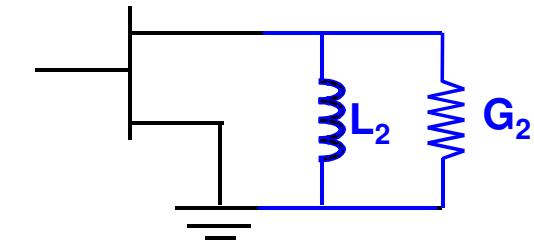3) Maximum Power Gain G_{MAX} → Simplified Electrical Small-Signal FET Model



TUTORIAL

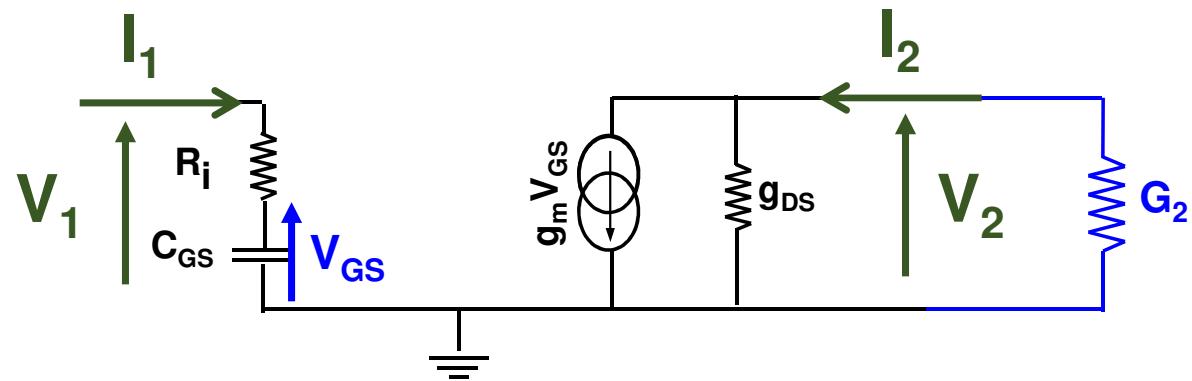

Optimum case ($G_2 = g_{DS}$) → Not maximum Power Gain G_{max}

$$G_{max} = \frac{g_m^2}{4 g_{DS} R_i C_{GS}^2 \omega^2}$$



$$G_{\max} = \frac{g_m^2 R_{DS}}{4 R_i G_s^2 \omega^2} = \frac{K = Cst}{\omega^2}$$

$G_{\max} (\text{dB})$

$$G_{\max}(\omega_0) - 6 \text{ dB}$$

$$G_{\max}(\omega_0) - 6 \text{ dB}$$

0 dB

$$\omega_0$$

$$2\omega_0$$

$$\omega_{\max}$$

$\frac{6 \text{ dB}}{\text{octave}}$

(15 GHz)

$$G_{\max}(f_1) = G_{\max}(f_2) \times \left(\frac{f_2}{f_1} \right)^2$$

$$\frac{K}{\omega_1^2}$$

$$\frac{K}{\omega_2^2}$$

$\log(f)$

$$G_{\max}(\omega) \left(2\omega \right) - G_{\max}(\omega) = 10 \log \left(\frac{K}{(2\omega)^2} \right) - 10 \log \left(\frac{K}{\omega^2} \right)$$

octave

$$= 10 \log \left(\frac{K}{4\omega^2} \times \frac{\omega^2}{K} \right) = 10 \log \left(\frac{1}{4} \right) = -6 \text{ dB}$$

GaN HEMT (vs Northup)




$$G_{\max}(10 \text{ GHz}) = 20 \text{ dB}$$

$$= 100$$

$$G_{\max}(10 \text{ GHz}) = 20 \text{ dB} = 10^2 = 100$$




$$G_{\max}(15 \text{ GHz}) = G_{\max}(10 \text{ GHz}) \times \left(\frac{10}{15}\right)^2 \\ = 100 \times \left(\frac{10}{15}\right)^2 = 44$$





$$= 10 \log(44) = 16.4 \text{ dB}$$


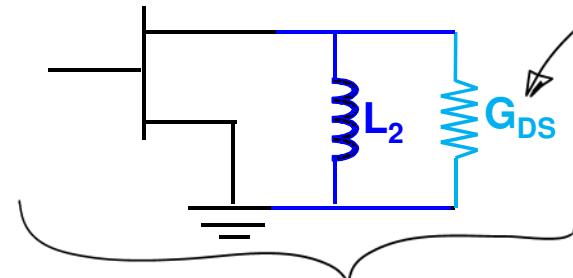
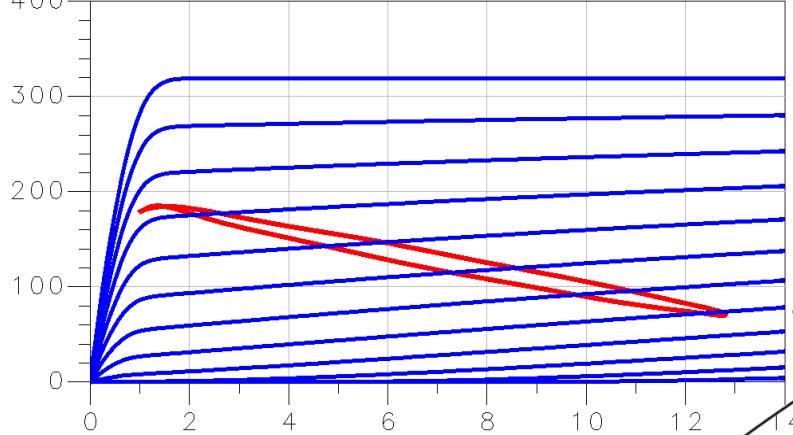
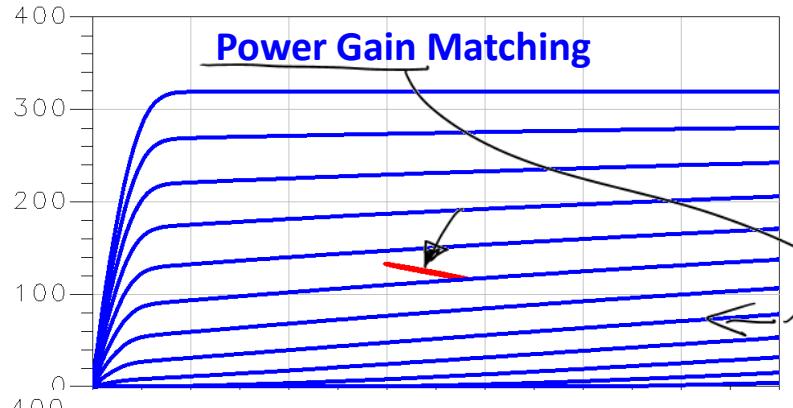




linear regime →

Saturated regime ←


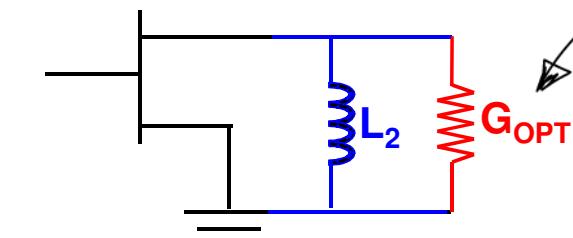
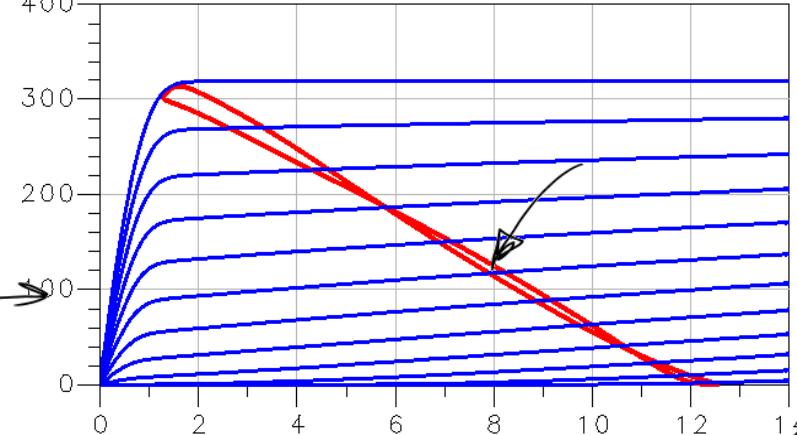
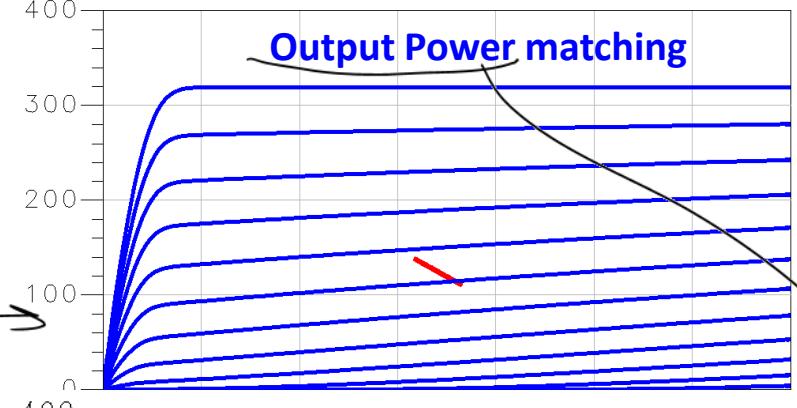


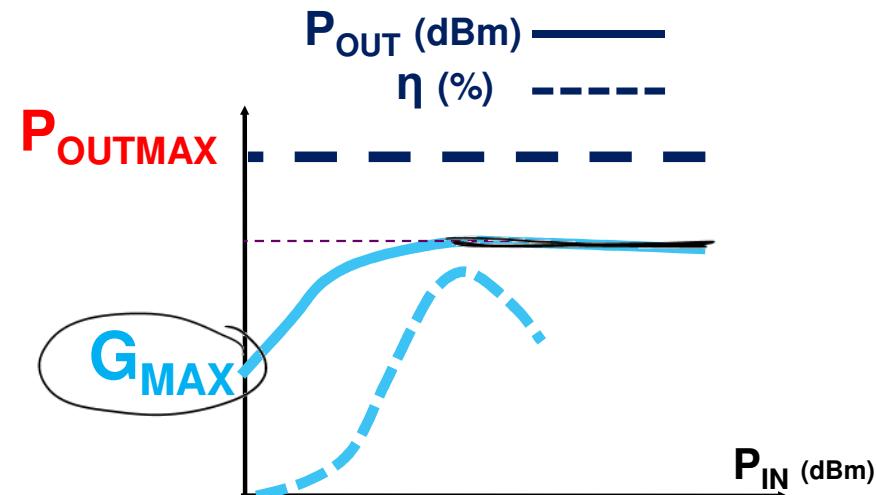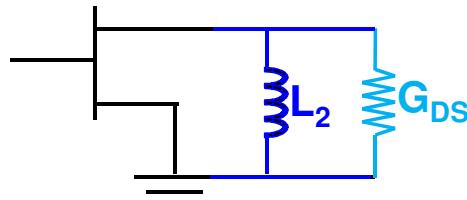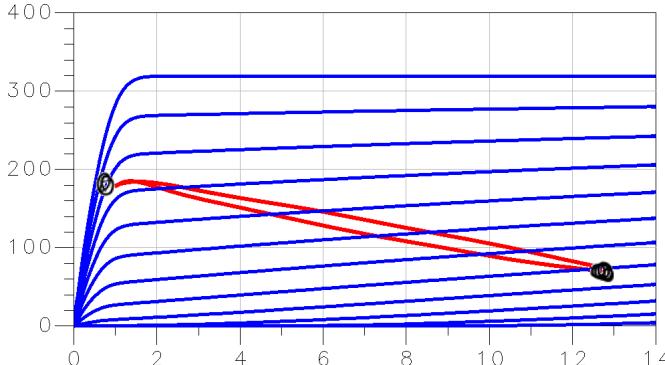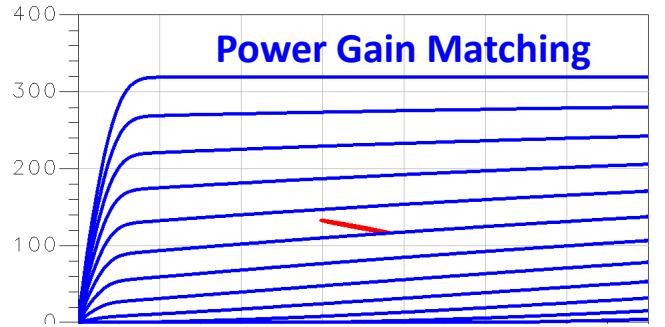

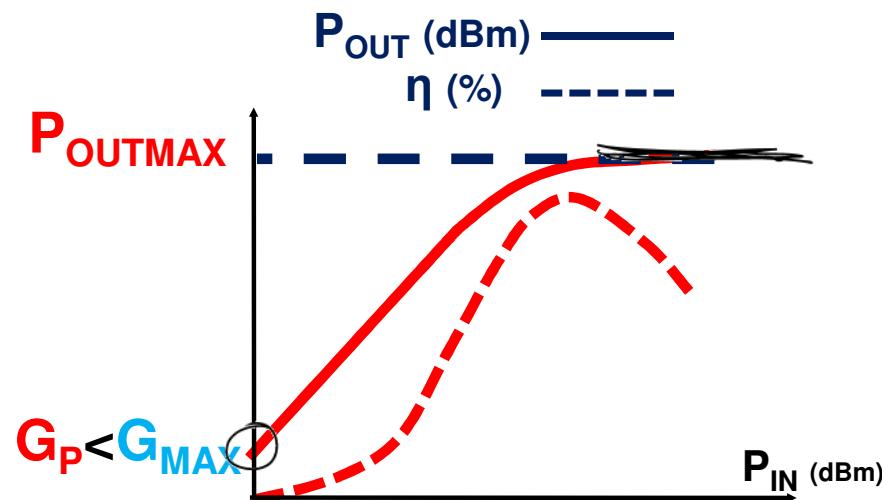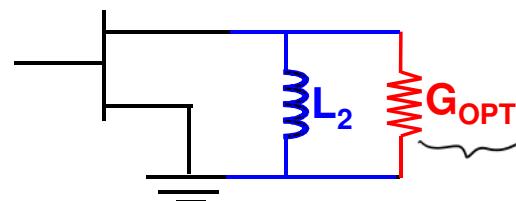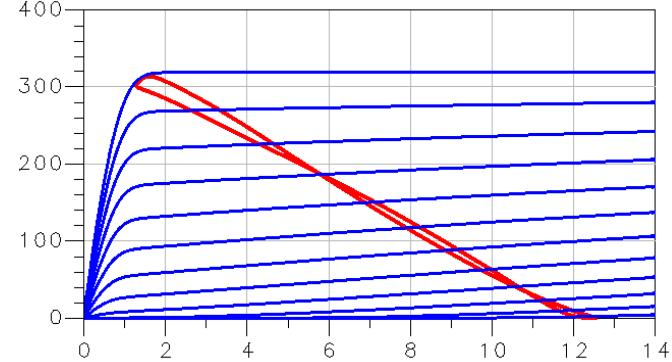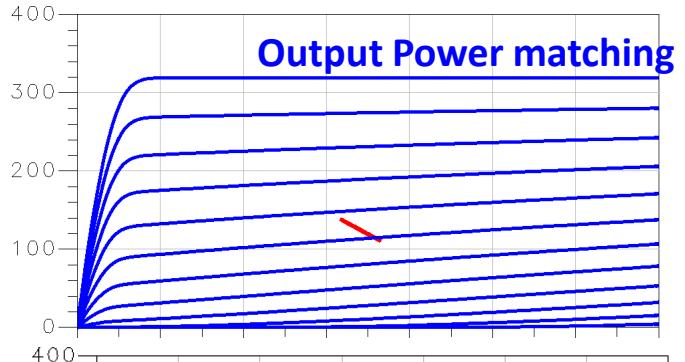

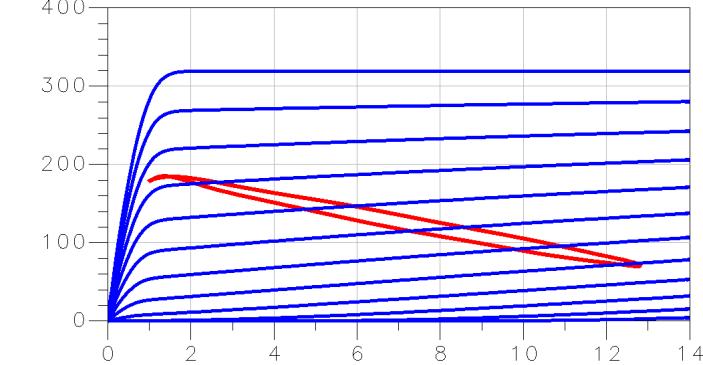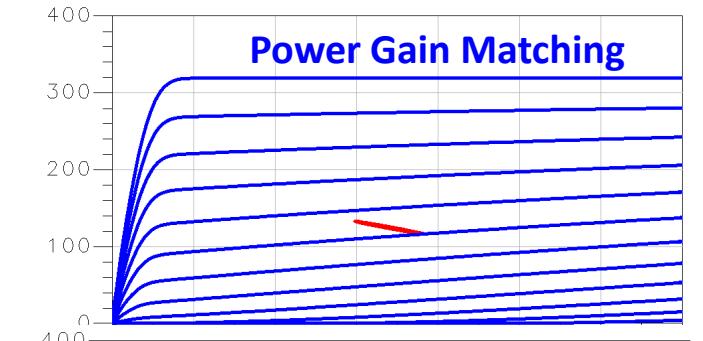

P_{OUT} (dBm) ———
 η (%) - - -

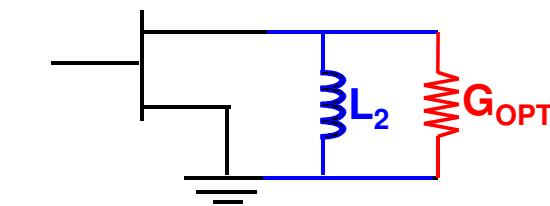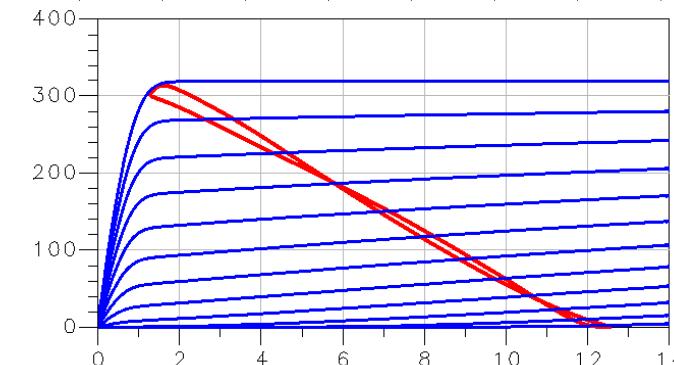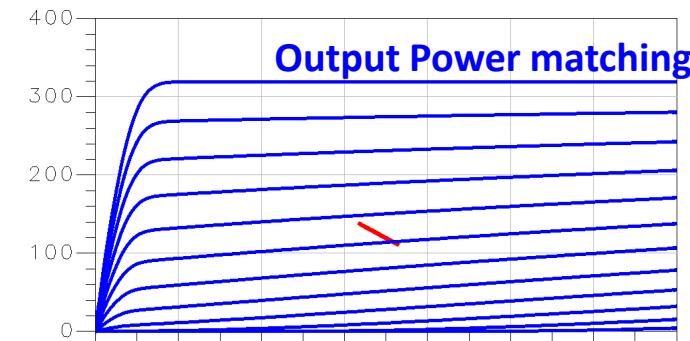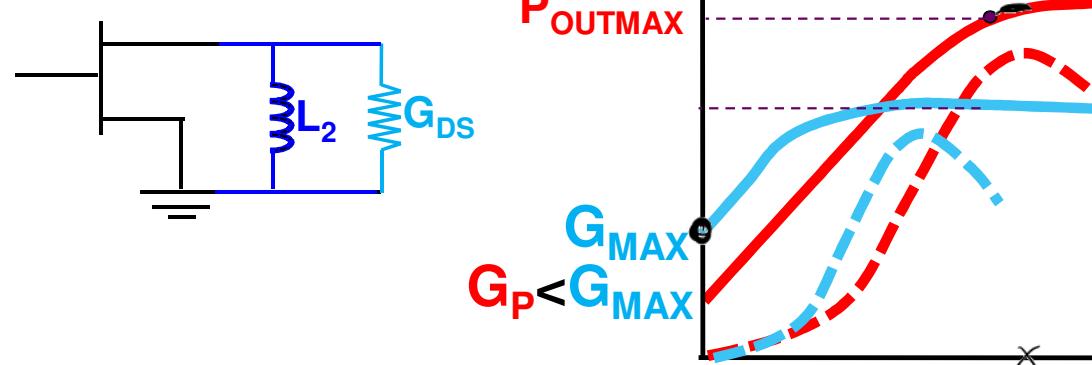

Power combination (Power Bars) and power matching

$$\begin{cases} L_g \approx 0.25 \mu\text{m} \\ W_g \approx 50 - 300 \mu\text{m} \end{cases}$$



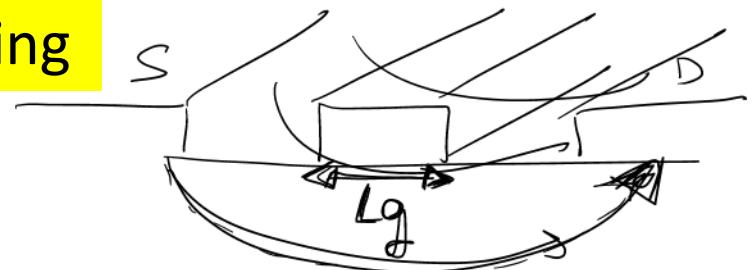



Illustration of critical issues in power matching

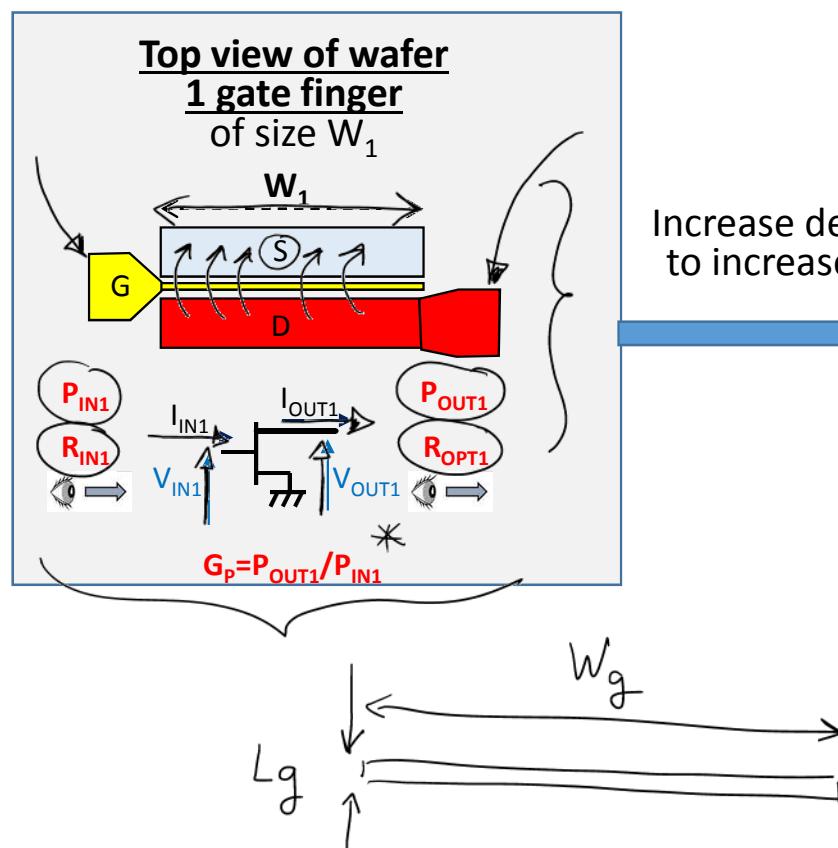

Increase device size to increase power

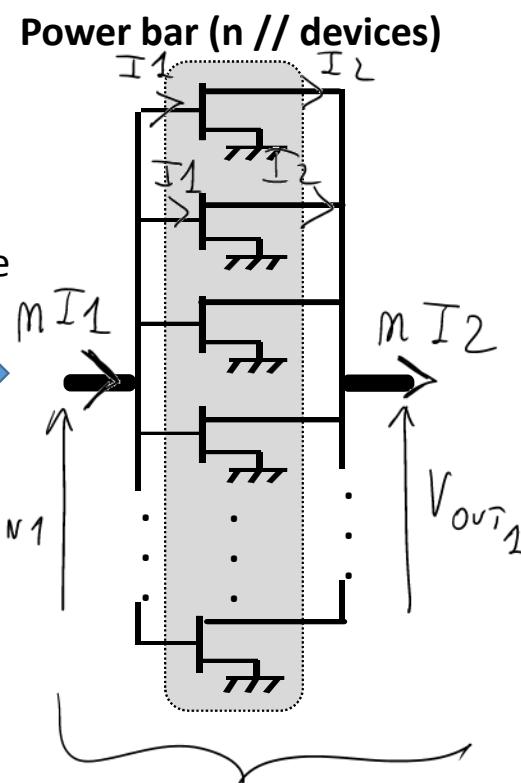

Power bar (matching in package)



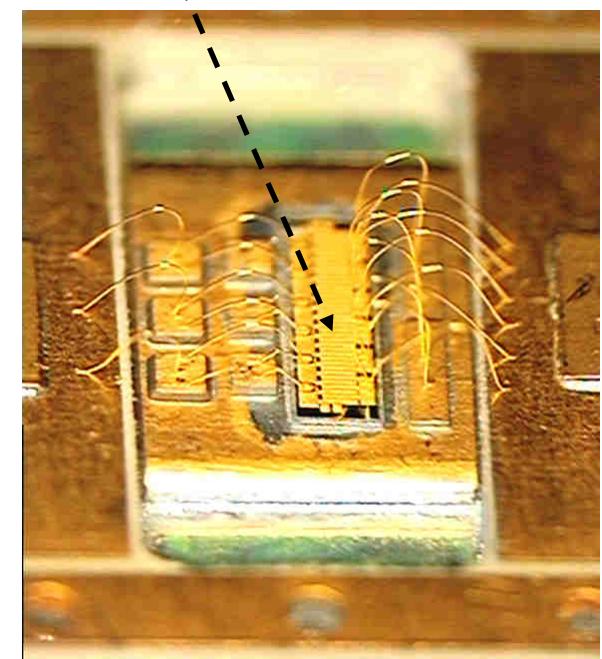


Power combination (Power Bars) and power matching

■ Illustration of critical issues in power matching

$$I = Y V$$

$$2I = 2YV$$

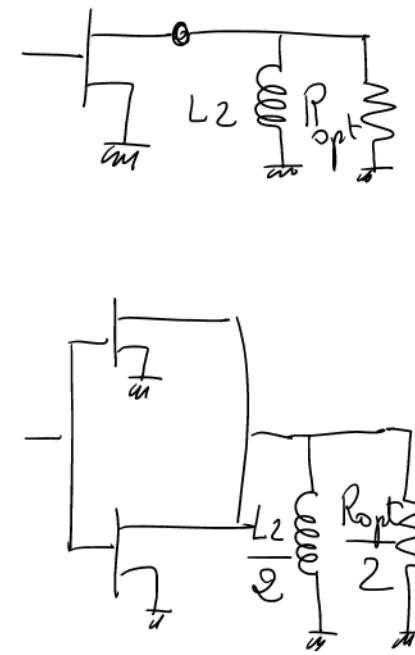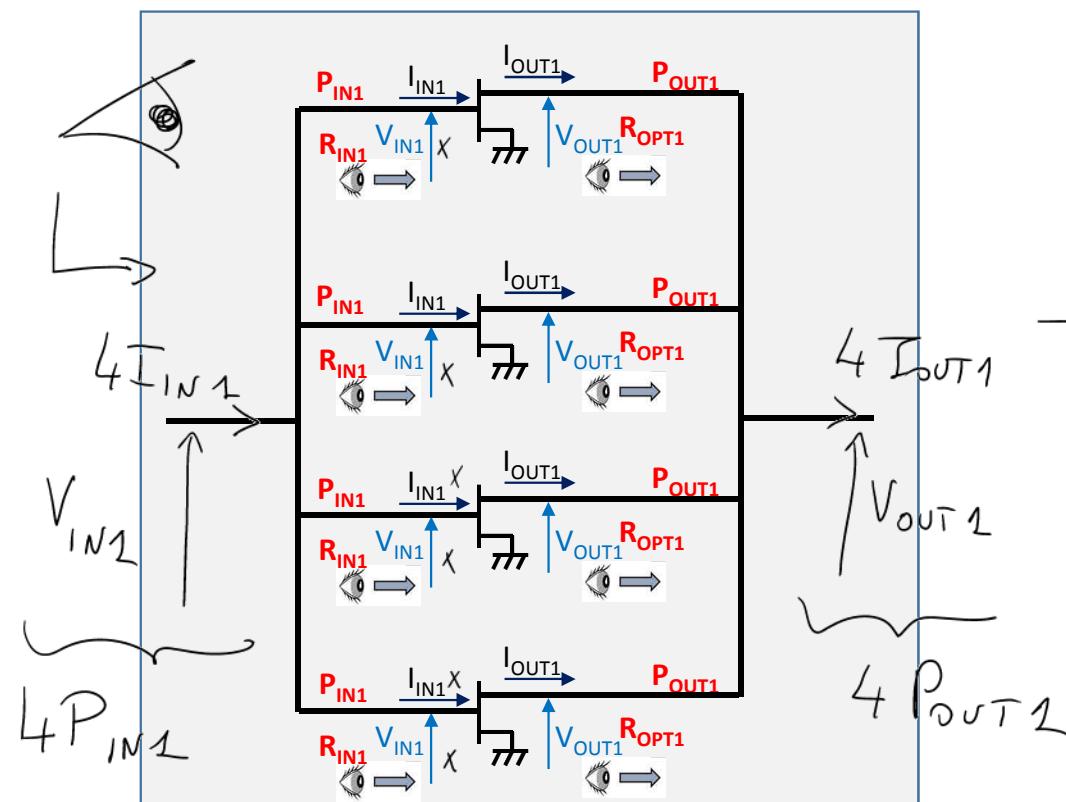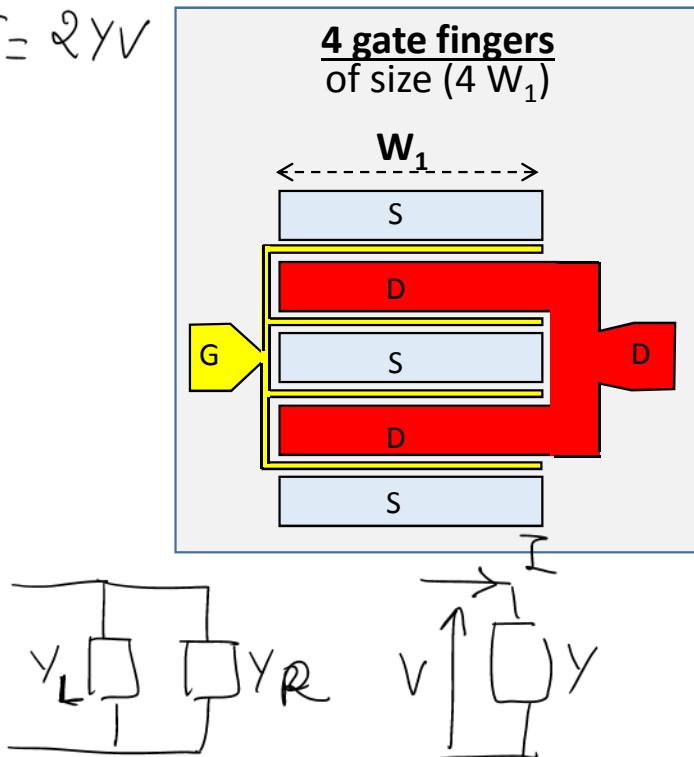


$$\text{Device size} = \text{Total gate width} = (\text{N}^{\circ} \text{ of // gates}) \times (\text{gate width}) = 4 \times W_1$$

$$\frac{2I}{V} = \frac{2Y}{2Y_L + 2Y_R} = \frac{2}{R} = G_p$$

$$L = \frac{1}{C \omega_0^2}$$


Power combination (Power Bars) and power matching

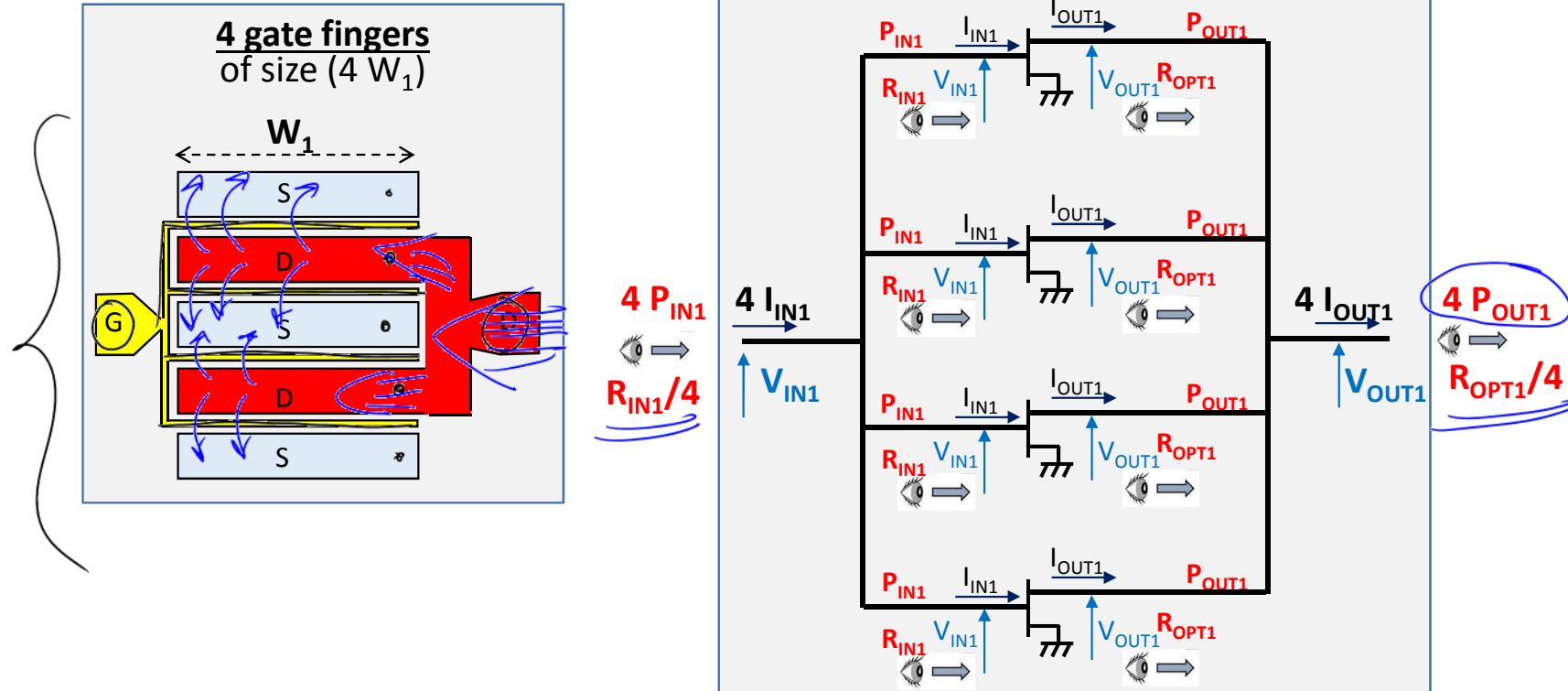■ Illustration of critical issues in power matching




Power combination (Power Bars) and power matching

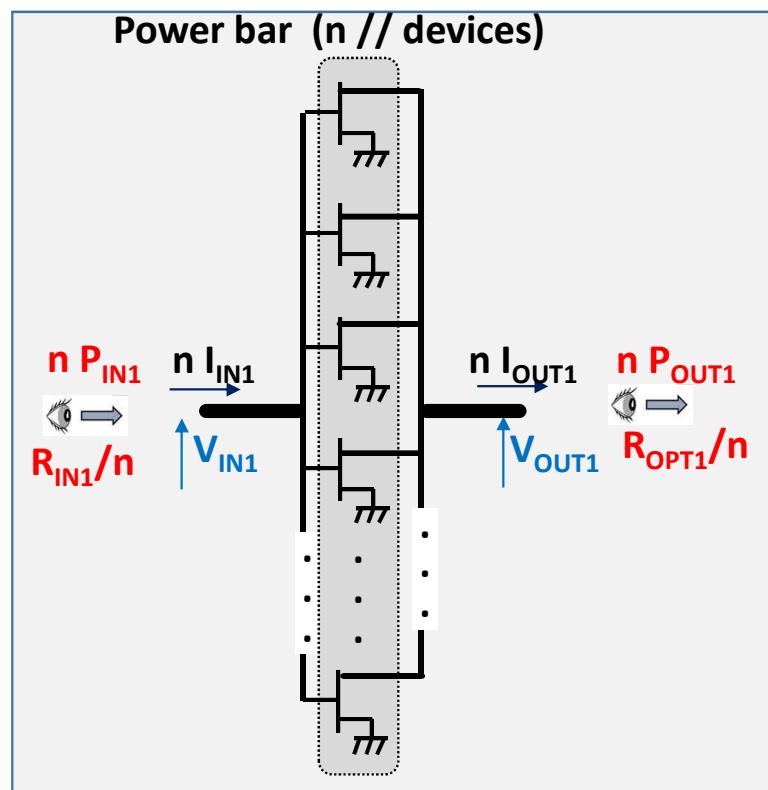- Illustration of critical issues in power matching



$W_G = 75 \mu\text{m}$

4 gate fingers

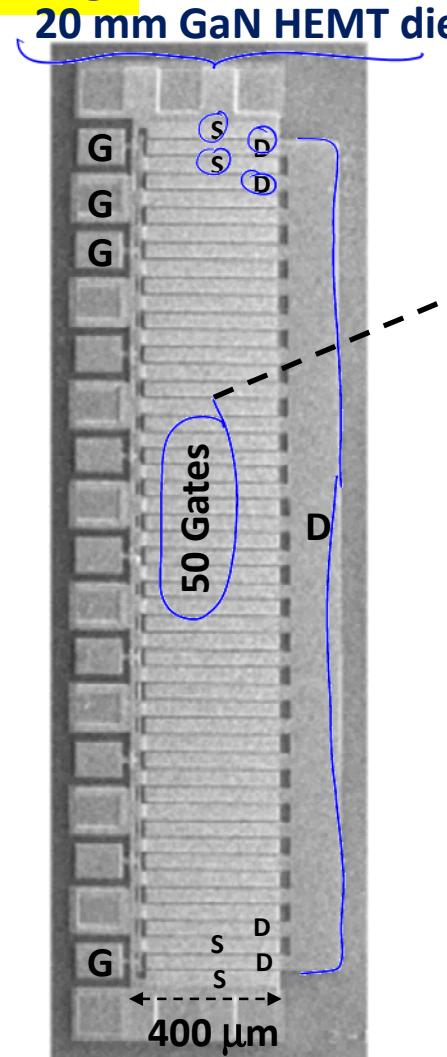


$$\begin{aligned} \text{Size} &= 4 \times W_G \\ &= 4 \times 75 \mu\text{m} = 300 \mu\text{m} = 0,3 \text{ mm} \end{aligned}$$

Device Size
= Total Gate Width
= (N^o of // gates) x (Gate width)
= $50 \times 400 \mu\text{m} = 20 \text{ mm}$

Scaling Rules:

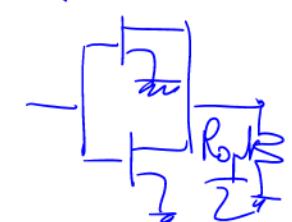- Drain Current** I_{DS} (mA/mm)
- Voltages** V_{GS} and V_{DS} (V)
- Output Power** P_{OUT} (W/mm) *
- Optimum Output Load** R_{OPT} ($\Omega \cdot \text{mm}$) *




Main transmission lines and Passive elements used in MMIC designs

MMIC (Monolithic Microwave and Millimeterwave Integrated Technology)



- Recall on Transmission lines
- Microstrip inductors/capacitors/resistors
- Harmonic loading and bias using $\lambda/4$ lines
- Matrix chain of a line and impedance transformation

Microstrip lines

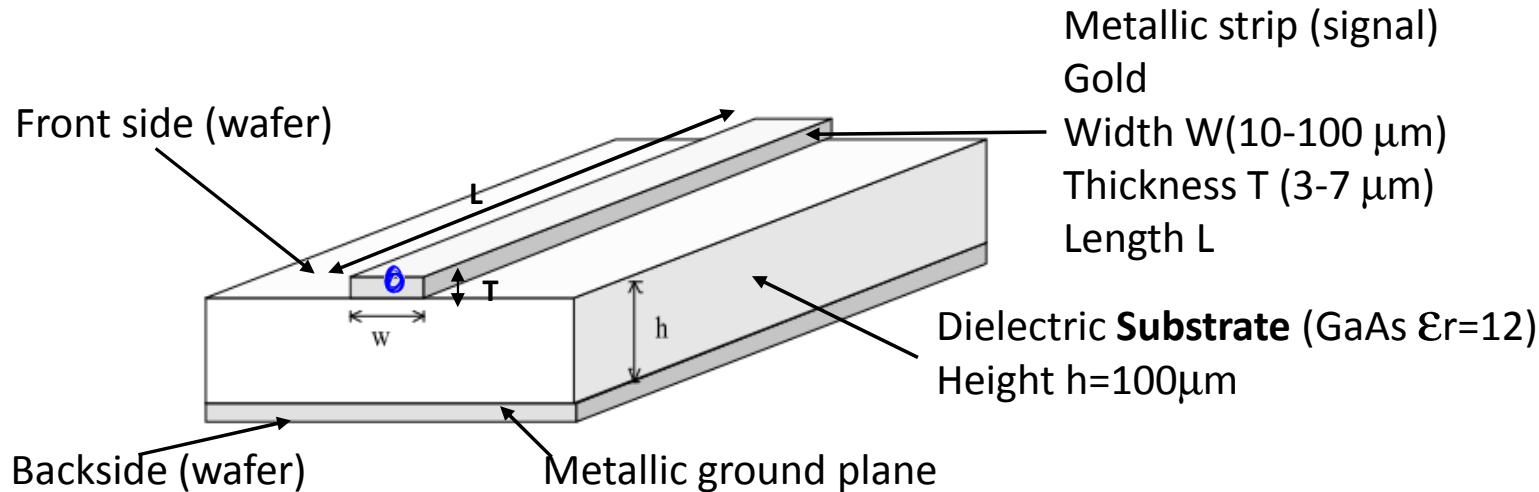

Metallic strip (signal)

Gold

Width $W(10-100\mu\text{m})$


Thickness $T(3-7\mu\text{m})$

Length L

Dielectric Substrate (GaAs $\epsilon_r=12$)

Height $h=100\mu\text{m}$

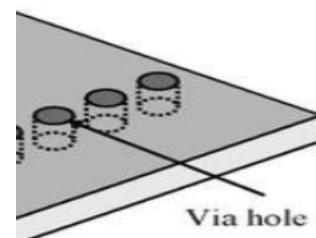- Requirement of **metallized via holes** through the substrate to connect electrical elements from the front side to the metallic ground plane
 - expensive backside process after the front side process 😞
 - easier design of the signal paths on the front side when compared to coplanar
 - the most effective integrated technology at high frequencies 😊




Microstrip lines


= wires at low frequencies

In order to drive the signal, these are some of the main shapes of line connections


CORNER

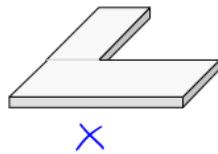


BEND

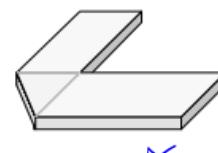


STEP (change of Z_c)

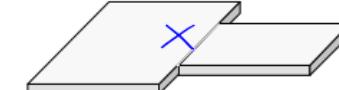


ROUND

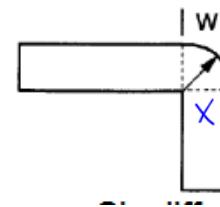




TEE junction (3 lines)

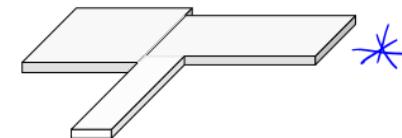


CROSS junction (4 lines)

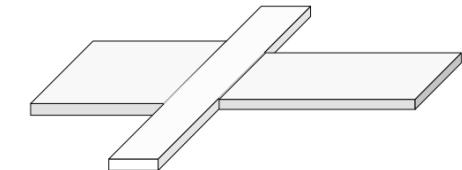

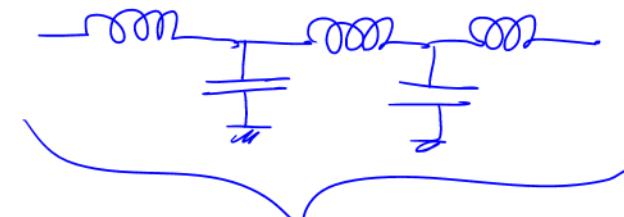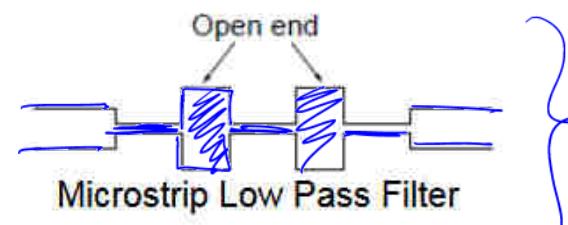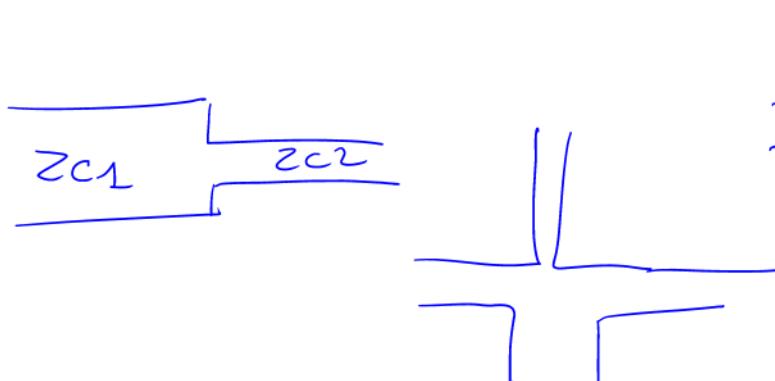In order to design passive circuits → Narrow Lines (Inductive) Wide Lines (Capacitive)



Coplanar lines

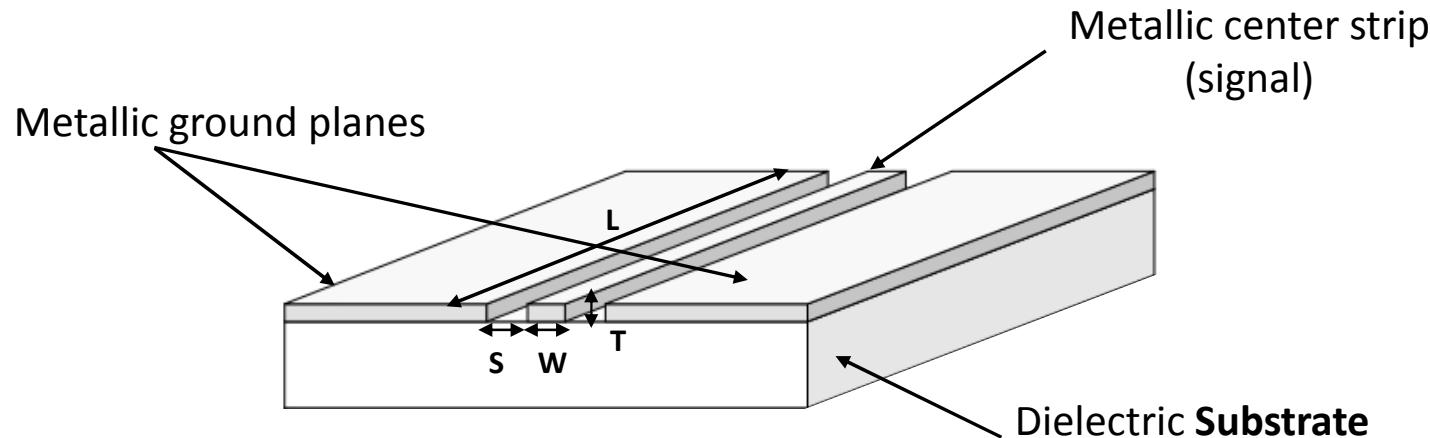


- No requirement of metallized via holes through the substrate to connect electrical elements from the front side to the metallic ground plane
 - no expensive backside process after the front side process 
 - complex design of the signal paths on the front side 
 - lower performances than microstrip designs 

Line = Matrix chain

Propagation constant $\Gamma = \alpha + j \beta \rightarrow$ Attenuation constant α and Phase constant β


$$\beta = 2\pi/\lambda$$

$$\theta = \beta L$$

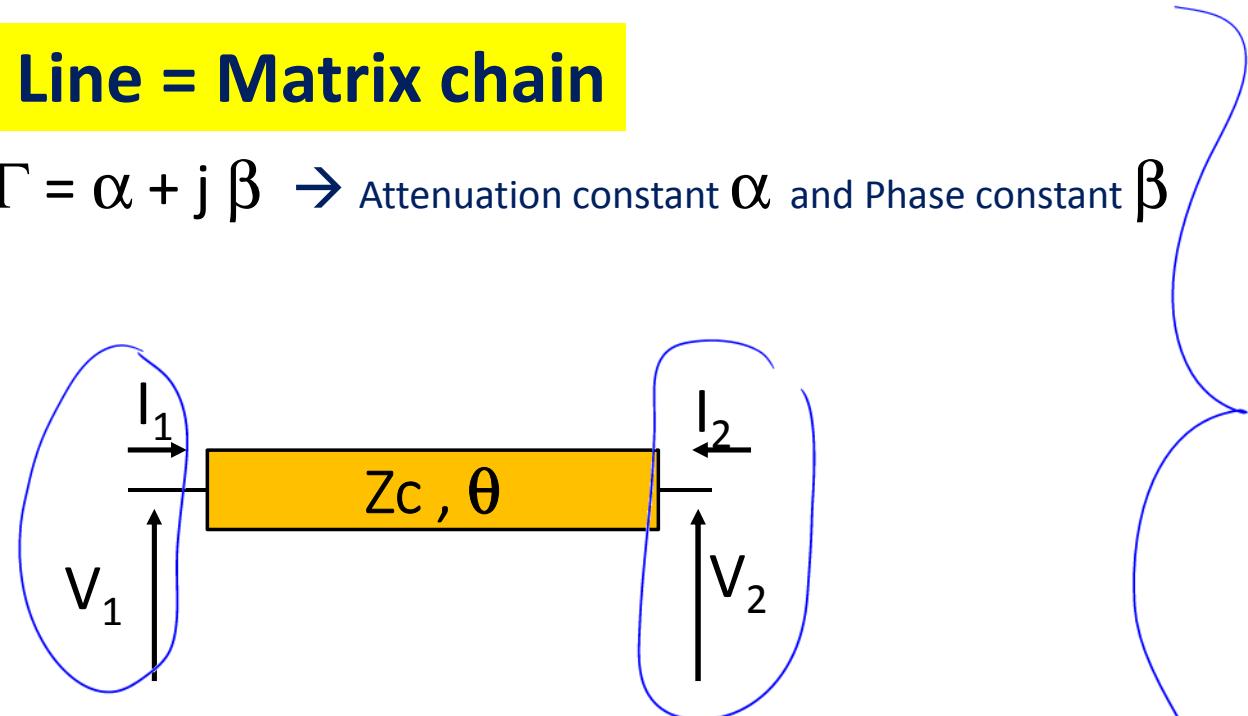

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} \cos(\theta) & jZ_c \sin(\theta) \\ j \sin(\theta)/Z_c & \cos(\theta) \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

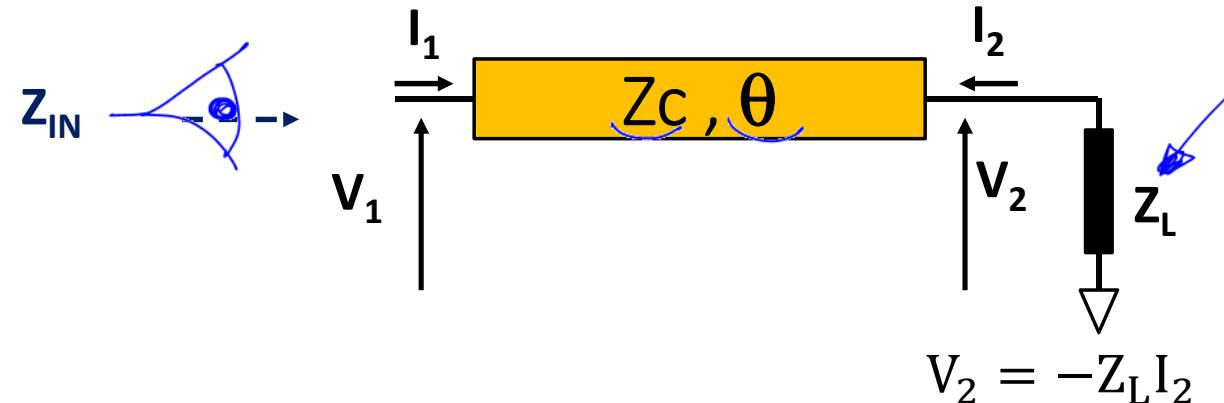Equivalent input impedance of a loaded line




$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} \cos(\theta) & jZ_C \sin(\theta) \\ j \sin(\theta)/Z_C & \cos(\theta) \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$V_2 = -Z_L I_2$$

$$Z_{IN} = \frac{V_1}{I_1} = \frac{\cos(\theta) V_2 - jZ_C \sin(\theta) I_2}{\left(\frac{j \sin(\theta)}{Z_C}\right) V_2 - \cos(\theta) I_2} = \frac{\cos(\theta) (-Z_L I_2) - jZ_C \sin(\theta) I_2}{\left(\frac{j \sin(\theta)}{Z_C}\right) (-Z_L I_2) - \cos(\theta) I_2}$$

$$Z_{IN} = \frac{\cos(\theta) (Z_L) + jZ_C \sin(\theta)}{\left(\frac{j \sin(\theta)}{Z_C}\right) (Z_L) + \cos(\theta)} = Z_C \frac{Z_L \cos(\theta) + jZ_C \sin(\theta)}{jZ_L \sin(\theta) + Z_C \cos(\theta)}$$

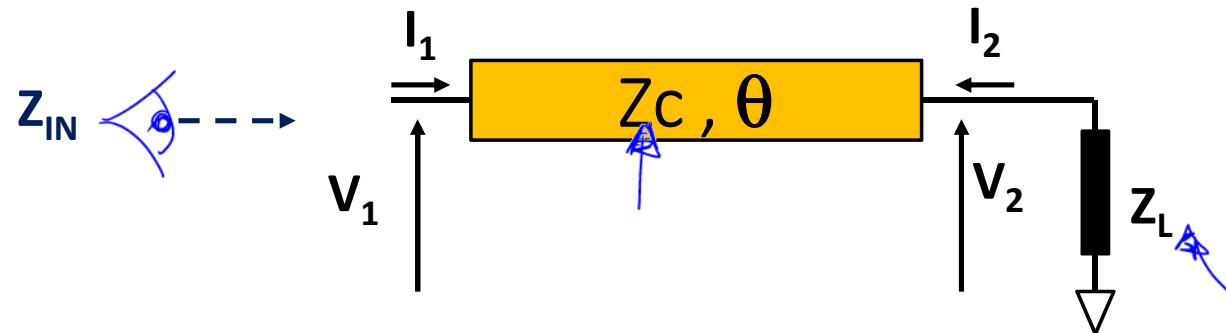Equivalent input impedance of $\lambda/4$ and $\lambda/2$ loaded lines



$$Z_{IN} = Z_C \frac{Z_L \cos(\theta) + j Z_C \sin(\theta)}{j Z_L \sin(\theta) + Z_C \cos(\theta)}$$

if $L = \frac{\lambda}{4}$ * $\rightarrow \theta = \frac{2\pi L}{\lambda} = \frac{\pi}{2}$ * $\rightarrow Z_{IN} = \frac{Z_C^2}{Z_L}$ Impedance inverter
 if $L = \frac{\lambda}{2}$ $\rightarrow \theta = \frac{2\pi L}{\lambda} = \pi \rightarrow Z_{IN} = Z_L$

High- and Low-impedance short lines (Inductive or capacitive)




High-impedance short-line element and the Equivalent circuit




Low-impedance short-line element and the Equivalent circuit

Open and short-circuited stubs

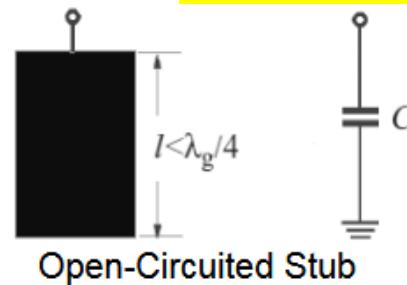


Open-Circuited Stub

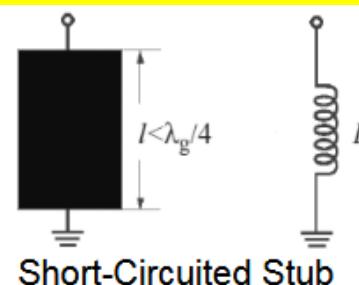


Short-Circuited Stub

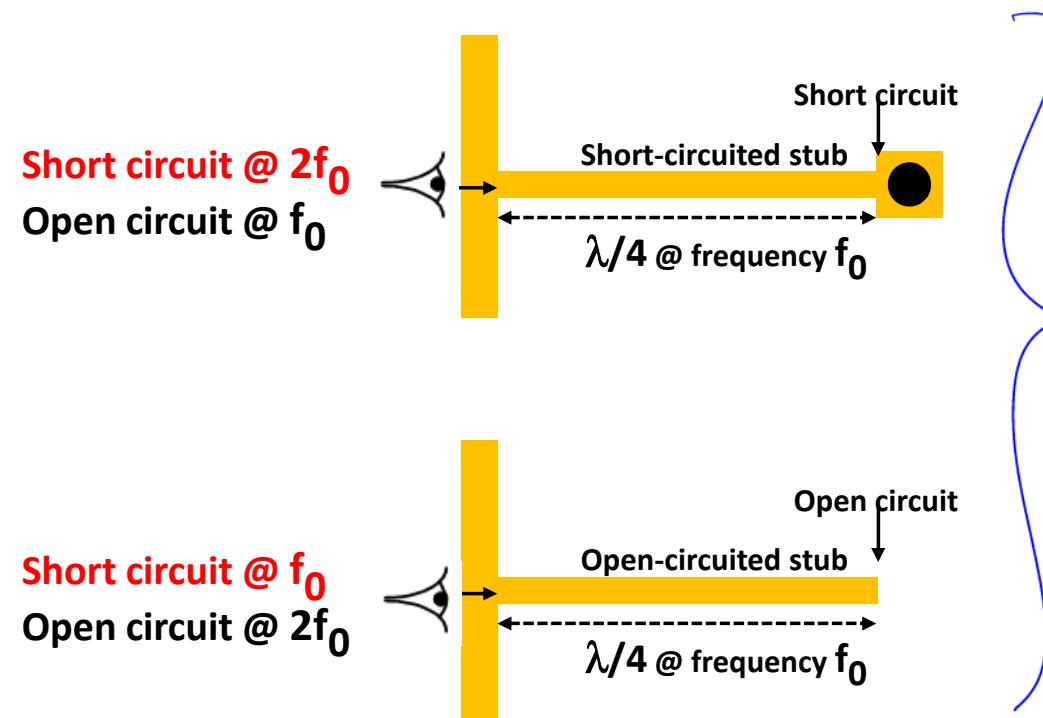Narrowband Harmonic loading using quarter wavelength line ($\lambda/4$)





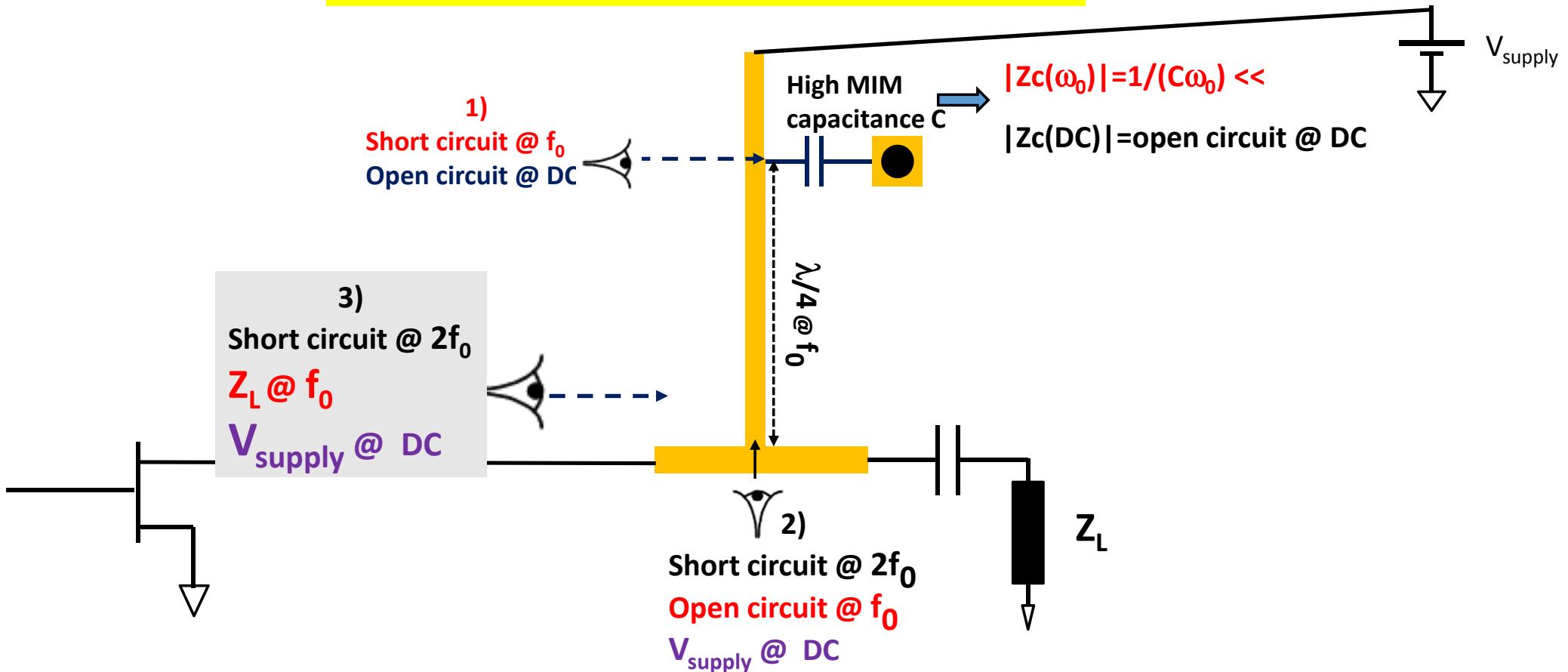Bias network decoupling using quarter wavelength line ($\lambda/4$)



**Reminder = Electrical lumped equivalent (RLC)
of transmission lines**

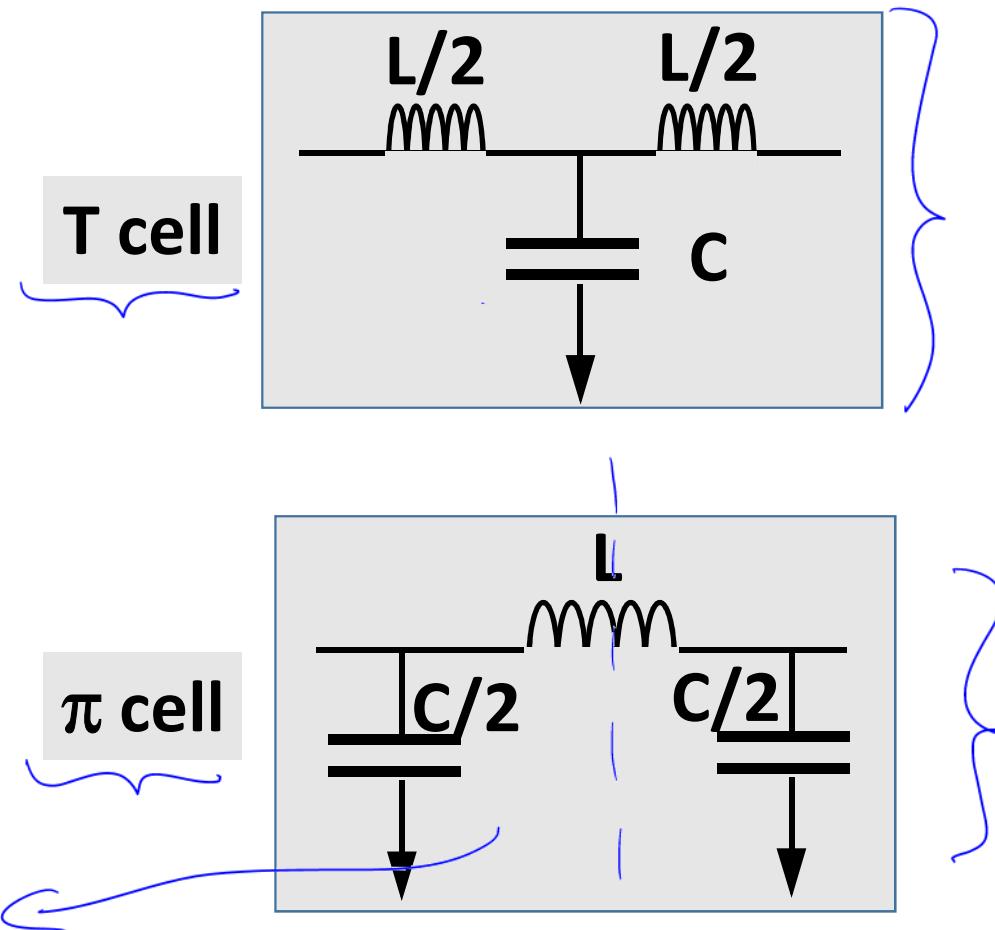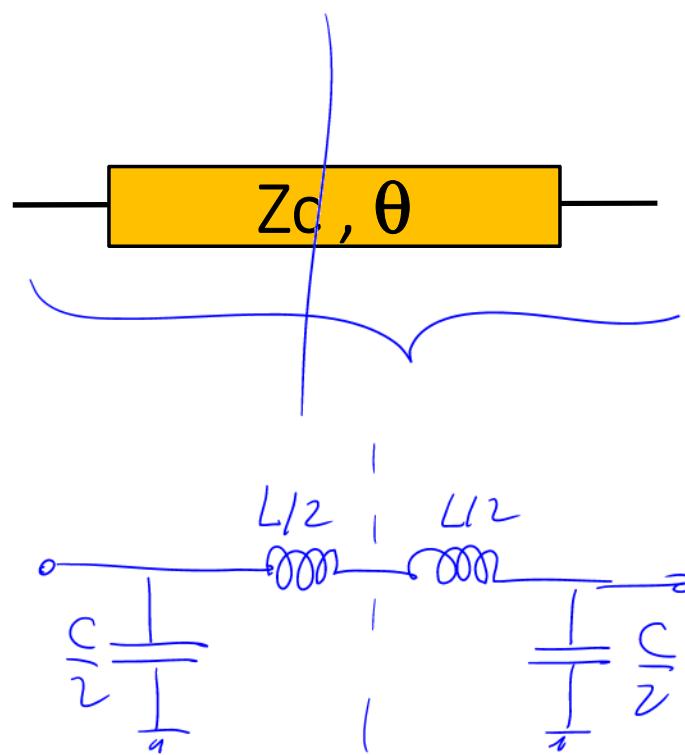Electrical lumped equivalent (LC) of a lossless line (Z_c, θ)




Electrical lumped equivalent (LC) of a lossless line (Z_c, θ)

Cut-off frequency

$$f_c = \frac{1}{\pi\sqrt{LC}}$$

T cell

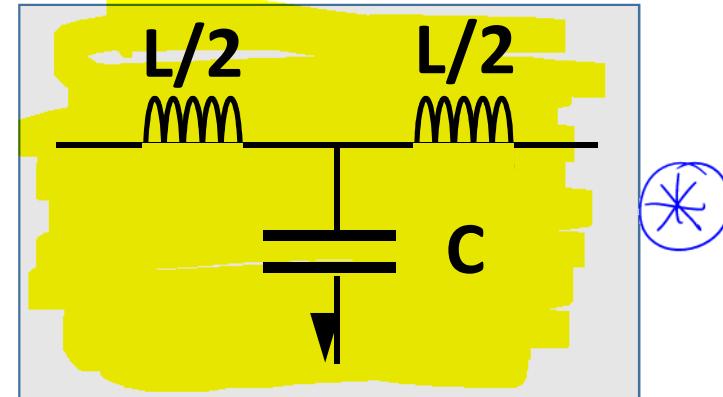

Characteristic Impedance

$$Z_c = \sqrt{\frac{L}{C}} \sqrt{1 - \left[\frac{f}{f_c}\right]^2} *$$





$f < f_c$

$$\sqrt{1 - \left[\frac{f}{f_c}\right]^2} > 0.9 \Leftrightarrow f < 0.44 f_c$$

$$\theta = \omega \sqrt{LC} \sqrt{1 - \left[\frac{f}{f_c}\right]^2}$$

$Z_c = \sqrt{\frac{L}{C}}$

and $\theta = \omega \sqrt{LC}$

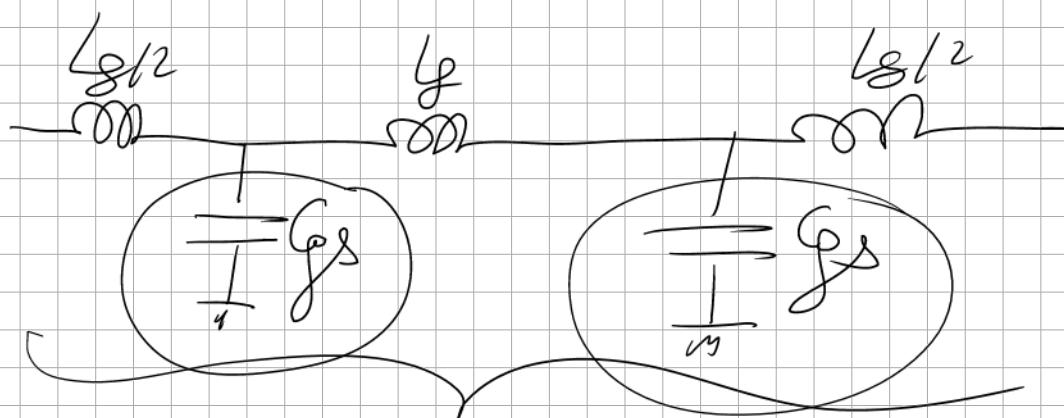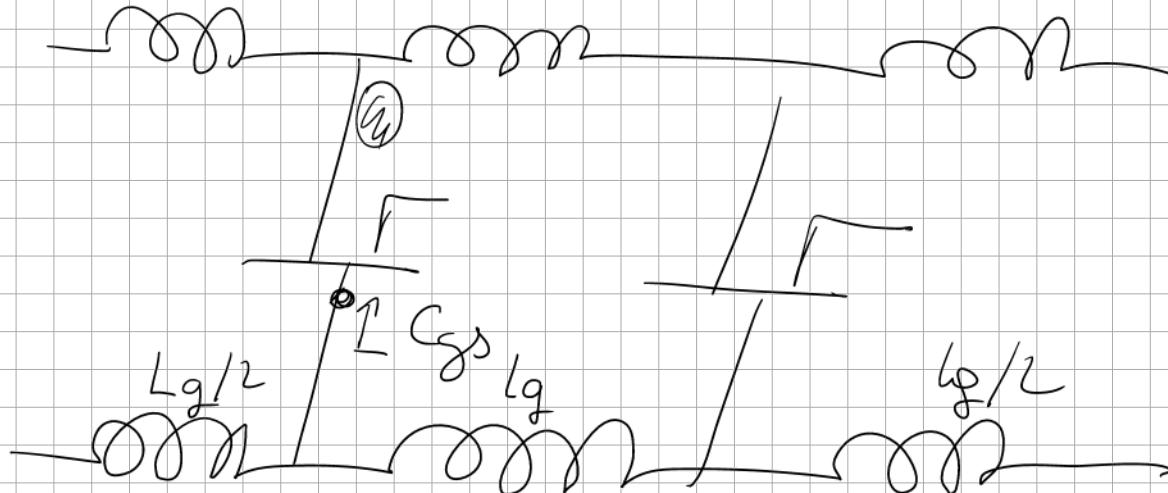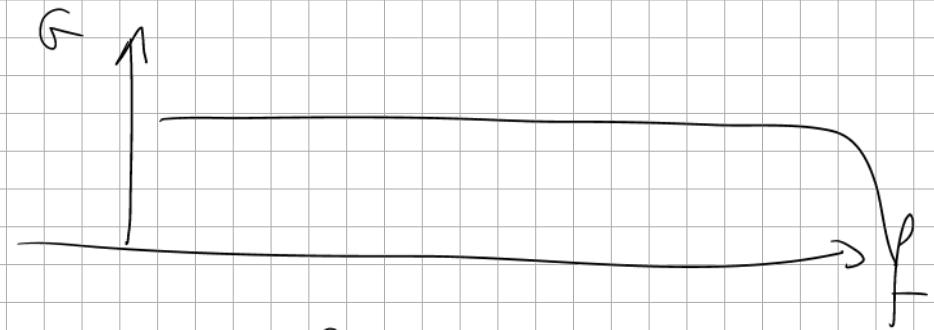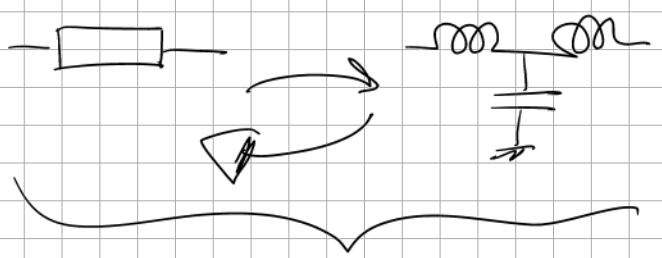


Electrical lumped equivalent (LC) of a lossless line (Z_c, θ)



Cut-off frequency

$$f_c = \frac{1}{\pi\sqrt{LC}}$$

T cell

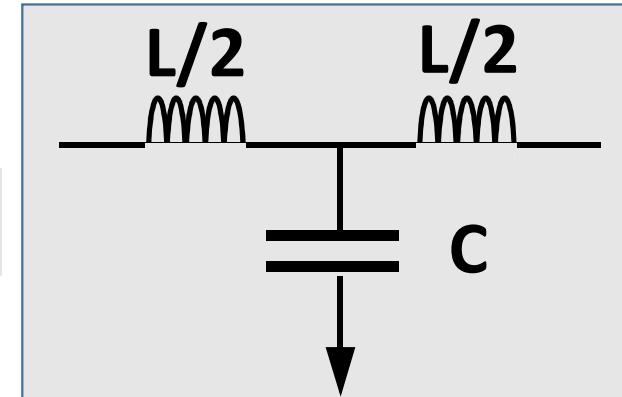

Characteristic Impedance

If $f \ll f_c \rightarrow f < 0.44 f_c$

$$Z_c \approx \sqrt{\frac{L}{C}}$$


Phase Shift

$$\text{If } f \ll f_c \rightarrow \theta \approx \omega\sqrt{LC}$$




Microstrip passive inductors, capacitors and resistors


Microstrip Inductors

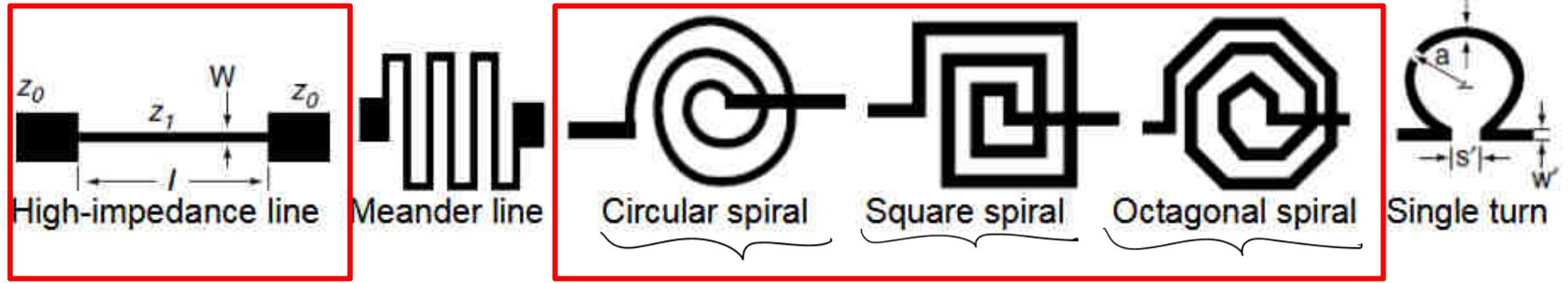


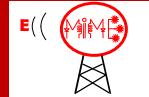
Only used at lower frequencies up to 3-4GHz because of very high losses
Achievable values up to few nH



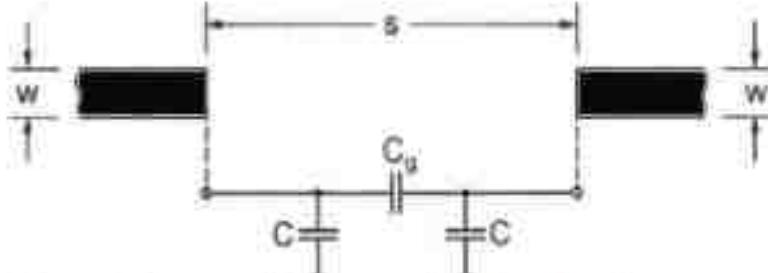Microstrip Capacitors (MIM : Metal Insulator Metal)



Gap Capacitor and Equivalency

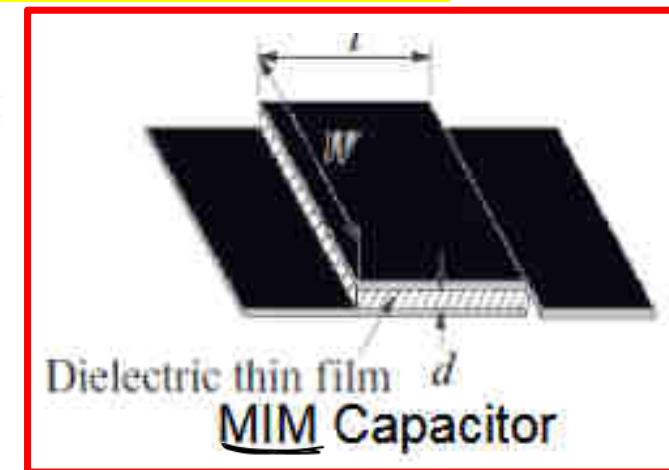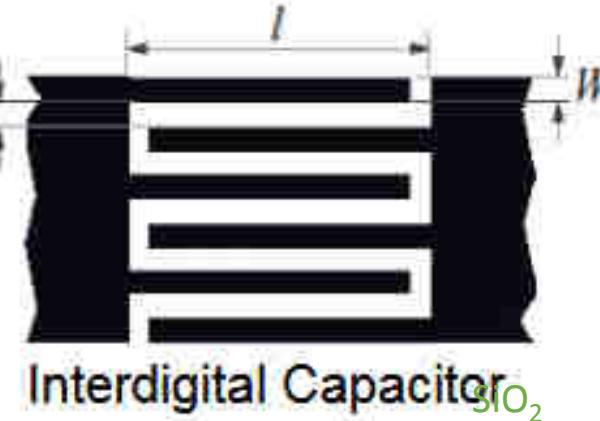

$$CD = \frac{\epsilon}{d}$$

Capacitance density (F/m^2)

Ex : $300 \text{ pF/mm}^2 \rightarrow$ Achievable values $0.2\text{pF} \rightarrow 20\text{pF}$


$$C = \epsilon \frac{S}{d} = \epsilon \frac{l \times W}{d}$$

$$C = \frac{\epsilon}{d} (l \times W)$$

$$C = CD \times S$$

Gold
1 m S/sq

Microstrip Resistors (TaN)

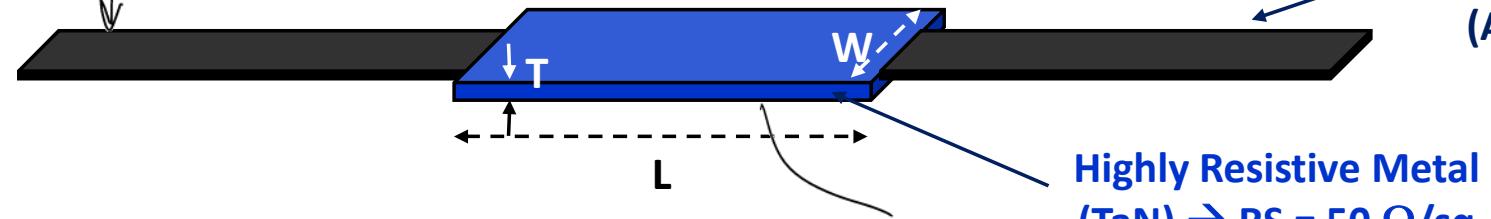

Microstrip Lines
Highly Conductive Metal
(Au) → $R_S = 0.001 \Omega/\text{sq}$

Highly Resistive Metal
(TaN) → $R_S = 50 \Omega/\text{sq}$

$$R = \rho_{\text{TaN}} \frac{L}{S} = \rho_{\text{TaN}} \frac{L}{T \times W}$$


$$R = \frac{\rho_{\text{TaN}}}{T} \frac{L}{W} = R_S \frac{L}{W}$$

$$R_S = \frac{\rho_{\text{TaN}}}{T}$$

$$R = R_S \frac{L}{W}$$

Sheet resistance $R_S (\Omega/\text{sq})$
 $(\Omega/)$

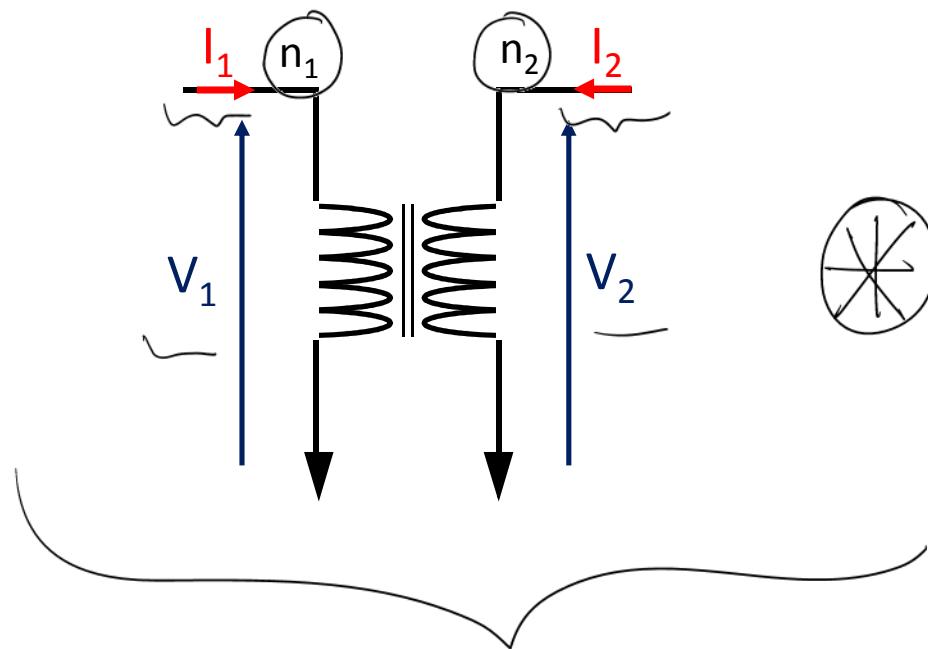Reminder = Ideal Electrical transformers How are they realized at high frequencies ?




Reminder = Ideal Electrical transformer

$$\frac{V_2}{V_1} = \frac{n_2}{n_1}$$

$$\frac{I_2}{I_1} = -\frac{n_1}{n_2}$$


Conservation of energy

Primary Winding
(n_1 turns)

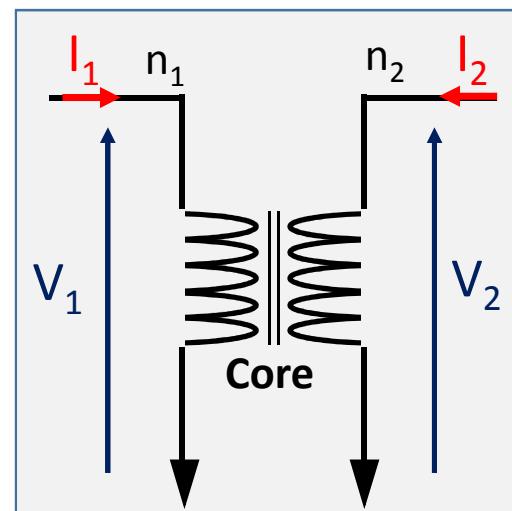

Secondary Winding
(n_2 turns)

Reminder = Impedance transformation

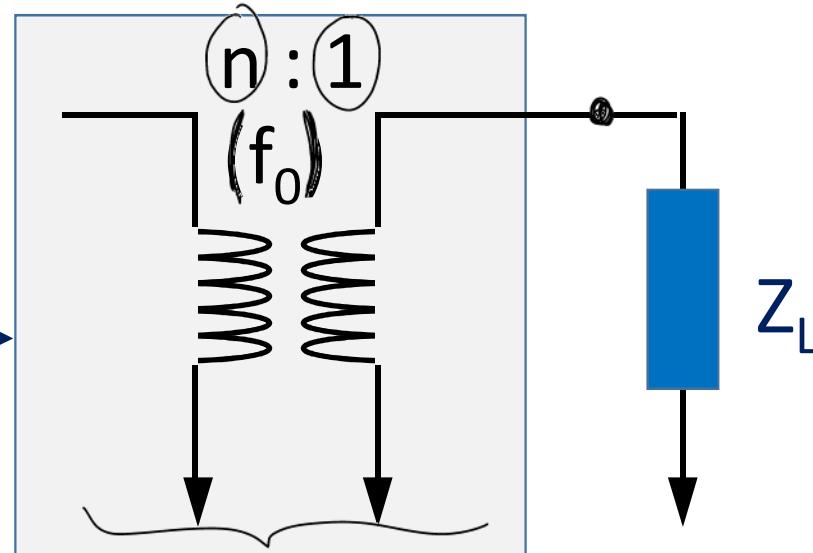 Z_{IN} 

Criterion

- Transformation ratio
- Bandwidth
- Technology

$$m = \sqrt{\frac{Z_L}{Z_{IN}}} \times$$

$$Z_{IN} = n^2 Z_L$$

$$n = \sqrt{\frac{Z_{IN}}{Z_L}} \times$$



$$m = 0.1 \quad \text{or} \quad m = 10$$

$$m = 1$$

$$\underbrace{m = 1}$$

$$\underbrace{m = 0, 1}$$

$$m = 3$$

$$\underbrace{m = 10}$$

$$n = 0, 1$$


$$0, 1$$

$$1 \text{ ideal}$$


$$\frac{1}{3} = 0.\overline{3}$$

$$3$$


$$\frac{1}{0,1} = 10$$

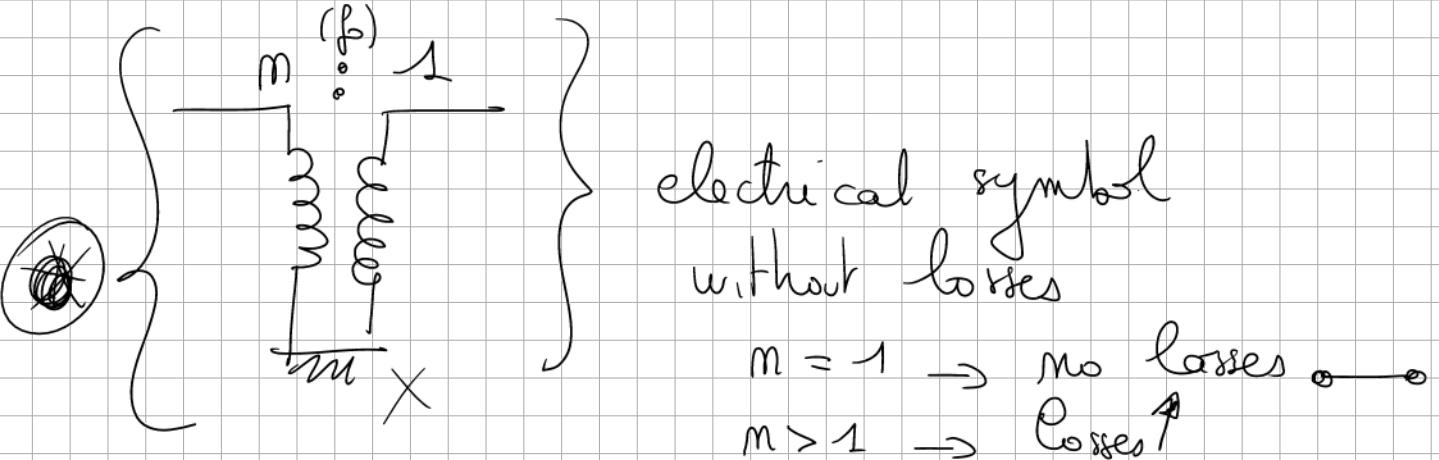

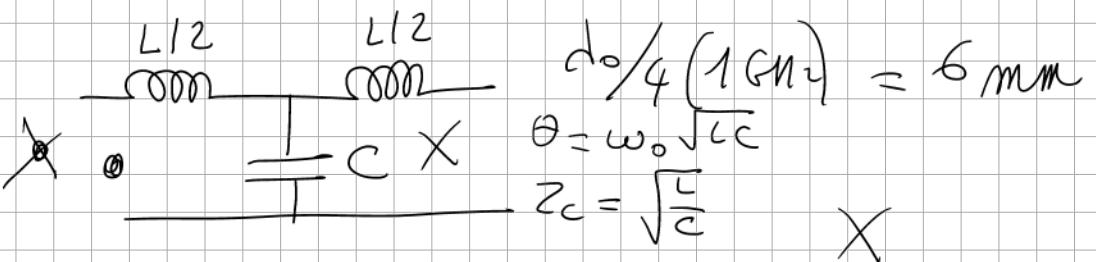
⑥ low frequencies ($\approx 1\text{GHz}$)



⑥ medium frequencies (5GHz)

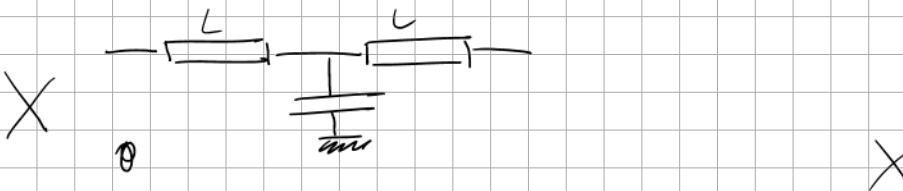

⑥ - - - - .

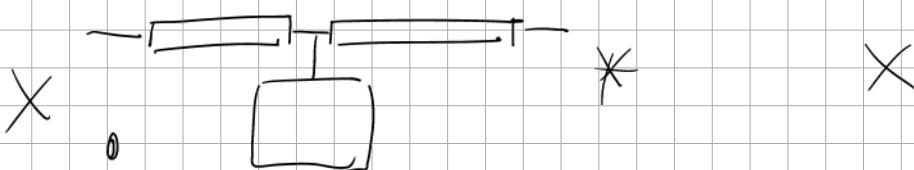

$$d = \frac{\lambda}{f}$$


⑥ very high frequencies (40GHz ...)

$$Z_C (l = d_0/4) \rightarrow 200\mu\text{m}$$

Reminder = Impedance transformation

$$\frac{V_2}{V_1} = \frac{n_2}{n_1}$$

$$\frac{I_2}{I_1} = -\frac{n_1}{n_2}$$

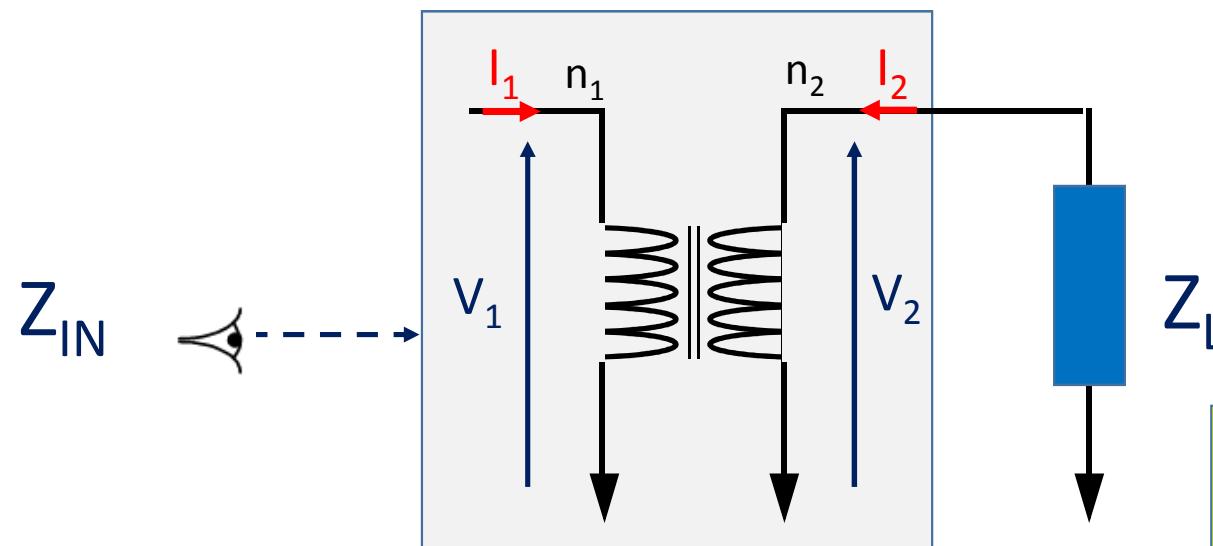

$$Z_{IN} = \frac{V_1}{I_1} = \frac{V_1}{V_2} \frac{V_2}{I_2} \frac{I_2}{I_1} = \frac{n_1}{n_2} (-Z_L) \frac{-n_1}{n_2} = \left[\frac{n_1}{n_2} \right]^2 Z_L$$

Load

$$V_2 = -Z_L I_2$$

$$Z_{IN} = \left[\frac{n_1}{n_2} \right]^2 Z_L$$

$$n = \left[\frac{n_1}{n_2} \right] = \sqrt{\frac{Z_{IN}}{Z_L}}$$