


MICROWAVE ENGINEERING

Lecture 29:
Problems on periodic
structures and
Filters

Problem 1

Analysis of a periodic structure

Consider the following line:

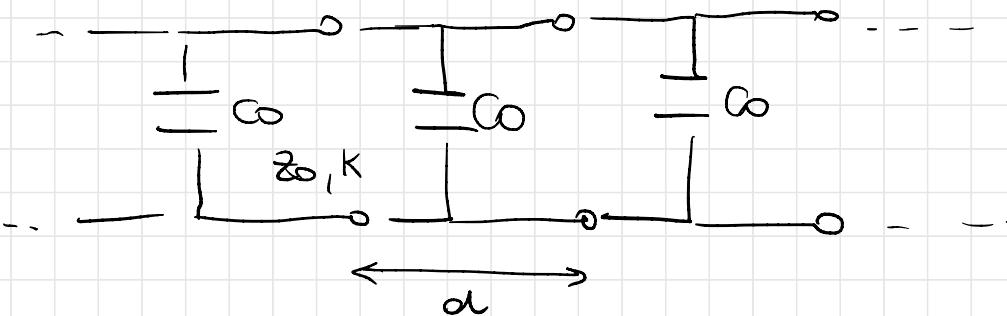

$$z_0 = 50 \Omega$$

$$d = 1 \text{ cm}$$

$$C_0 = 2.666 \text{ pF}$$

Calculate the propagation constant, phase velocity and Bloch impedance at $f = 3 \text{ GHz}$. Assume $k = k_0$.

At 3 GHz we have

$$\begin{aligned} k_0 d &= \frac{2\pi f}{c} \cdot d = \frac{2\pi (3 \cdot 10^9)}{3 \cdot 10^8} \cdot 0.01 = \\ &= 0.6283 \text{ rad} = 36^\circ \end{aligned}$$

Assuming to work in a passband mode. For an infinite structure

$$\boxed{\cos \beta d = \cos \theta - \frac{b}{2} \sin \theta}$$

$$\cos \beta d = \cos k d - \frac{b}{2} \sin k d$$

$$\frac{b}{2} = \frac{\omega C_0 Z_0}{2} =$$

$$\cos \beta d = \cos(0.6283) - \frac{b}{2} \sin(0.6283) = 0.07$$

by

$$\beta d = 1.5$$

$$= 1.256$$

$$\underline{\underline{\beta = 1.5 / 0.01 = 150 \frac{\text{rad}}{\text{m}}}}$$

The phase velocity is:

$$V_p = \frac{k_0 c}{\beta} = \frac{k_0 d c}{\beta d} = \frac{0.6283}{1.5} \cdot c = 0.42 c$$

—

Slow wave
regime

The Block Impedance is

$$Z_B = \frac{B Z_0}{\sqrt{A^2 - 1}}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cos\theta - \frac{b}{2} \sin\theta & j \left(\sin\theta + \frac{b}{2} \cos\theta - \frac{b}{2} \right) \\ j \left(\sin\theta + \frac{b}{2} \cos\theta + \frac{b}{2} \right) & \cos\theta - \frac{b}{2} \sin\theta \end{bmatrix}$$

$$\frac{b}{2} = 1.256$$

$$\theta = \text{kod} = 36^\circ$$

$$A = \cos\theta - \frac{b}{2} \sin\theta = 0.0707$$


$$B = j \left(\sin\theta + \frac{b}{2} \cos\theta - \frac{b}{2} \right) = j 0.3479$$

$$Z_B = \frac{B Z_0}{\sqrt{A^2 - 1}} = \frac{j 0.3479 \cdot 50}{\sqrt{0.0707^2 - 1}} =$$

$$= \frac{j 0.3479 \cdot 50}{j(\sqrt{1 - 0.0707^2})} = 17.6 \Omega$$

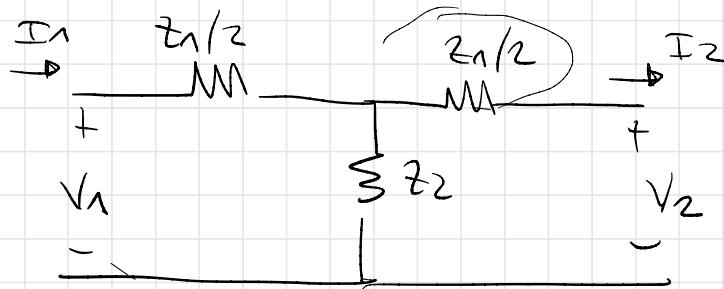Problem 2

Extract the image impedance and propagation constant of the following T-network:



$$Z_{IT} = \sqrt{\frac{AB}{CD}}$$

$$e^r = \sqrt{AD} + \sqrt{BC}$$

let's calculate the ABCD parameters for the network:

$$A = \frac{V_1}{V_2} \Big|_{I_2=0} = 1 + \frac{z_1}{2z_2}$$

$$B = \frac{V_1}{I_2} \Big|_{V_2=0} = z_1 + \frac{z_1^2}{4z_2}$$

$$C = \frac{I_1}{V_2} \Big|_{I_2=0} = \frac{1}{z_2}$$

$$D = \frac{I_1}{I_2} \Big|_{V_2=0} = 1 + \frac{z_1}{2z_2}$$

$$z_T = \sqrt{\frac{AB}{CD}} = \sqrt{\frac{\left(1 + \frac{z_1}{2z_2}\right) \left(z_1 + \frac{z_1^2}{4z_2}\right)}{\frac{1}{z_2} \left(1 + \frac{z_1}{2z_2}\right)}} =$$

$$= \sqrt{z_2 z_1 + \frac{z_1^2}{4}} = \sqrt{z_1 z_2} \sqrt{1 + \frac{z_1}{4z_2}}$$


$$e^x = \sqrt{AD} + \sqrt{BC} = 1 + \frac{z_1}{2z_2} + \sqrt{\frac{1}{z_2} \left(z_1 + \frac{z_1^2}{4z_2}\right)} =$$

$$= 1 + \frac{z_1}{2z_2} + \sqrt{\frac{z_1}{z_2} + \frac{z_1^2}{4z_2^2}}$$

Problem 3Low-pass composite filter design

Design a low-pass composite filter with a cutoff frequency at $f_c = 2 \text{ MHz}$ and impedance $R_o = 75 \Omega$. Consider the infinite attenuation pole $f_{\infty} = 2.05 \text{ MHz}$.

The constant-k T section circuit

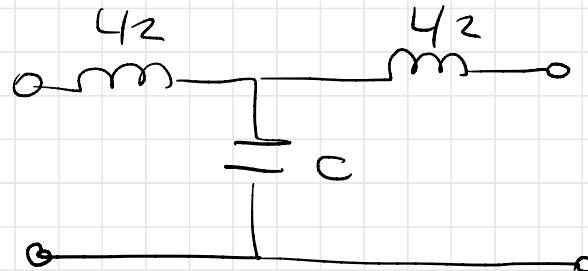


$$R_o = \sqrt{\frac{L}{C}}$$

$$\omega_c = \frac{2}{\sqrt{LC}}$$

$$L = \frac{2R_o}{\omega_c} = \frac{2R_o}{2\pi f_c} = \frac{2 \cdot 75}{2\pi \cdot 2 \cdot 10^6} = 11.93 \mu\text{H}$$

$$C = \frac{2}{\omega_c R_0} = \frac{2}{2\pi f_c R_0} = \frac{2}{2\pi 2 \cdot 10^6 \cdot 75} = 2.12 \text{ nF}$$

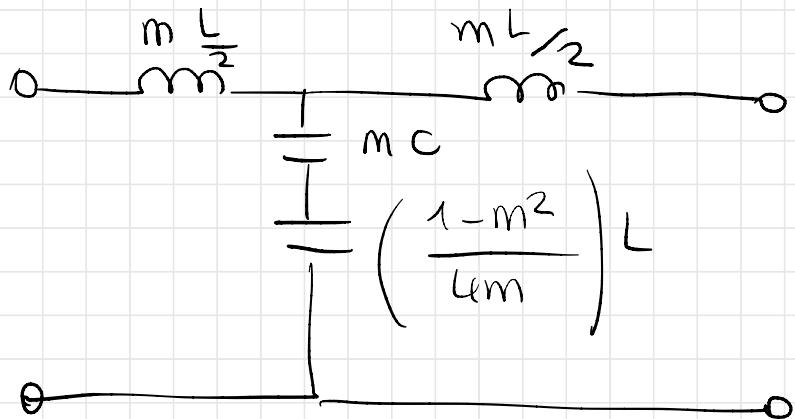We will then add a sharp cut-off section :




$$m = \sqrt{1 - \left(\frac{\omega_c}{\omega_\infty}\right)^2} = \sqrt{1 - \left(\frac{f_c}{f_\infty}\right)^2} = 0.2195$$

$$\frac{mL}{2} = 1.31 \mu\text{H}$$

$$mC = 465.8 \text{ pF}$$

$$\frac{1-m^2}{4m} L = 12.94 \mu\text{H}$$

Finally we add a matching section :

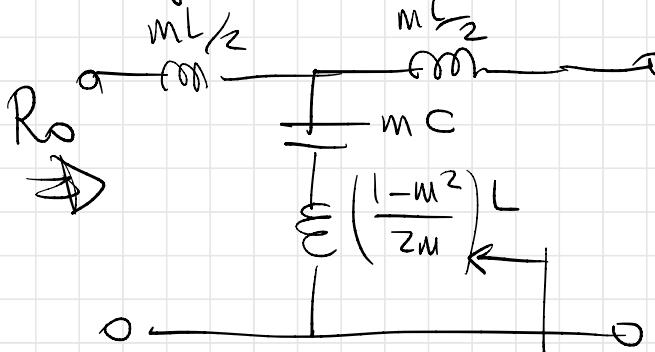


$$m = 0.6$$

$$\frac{mL}{2} = 3.582 \mu\text{H}$$

$$mC = 636.5 \text{ pF}$$

$$\frac{1-m^2}{2m} L = 6.368 \mu\text{H}$$


The composite filter then is:

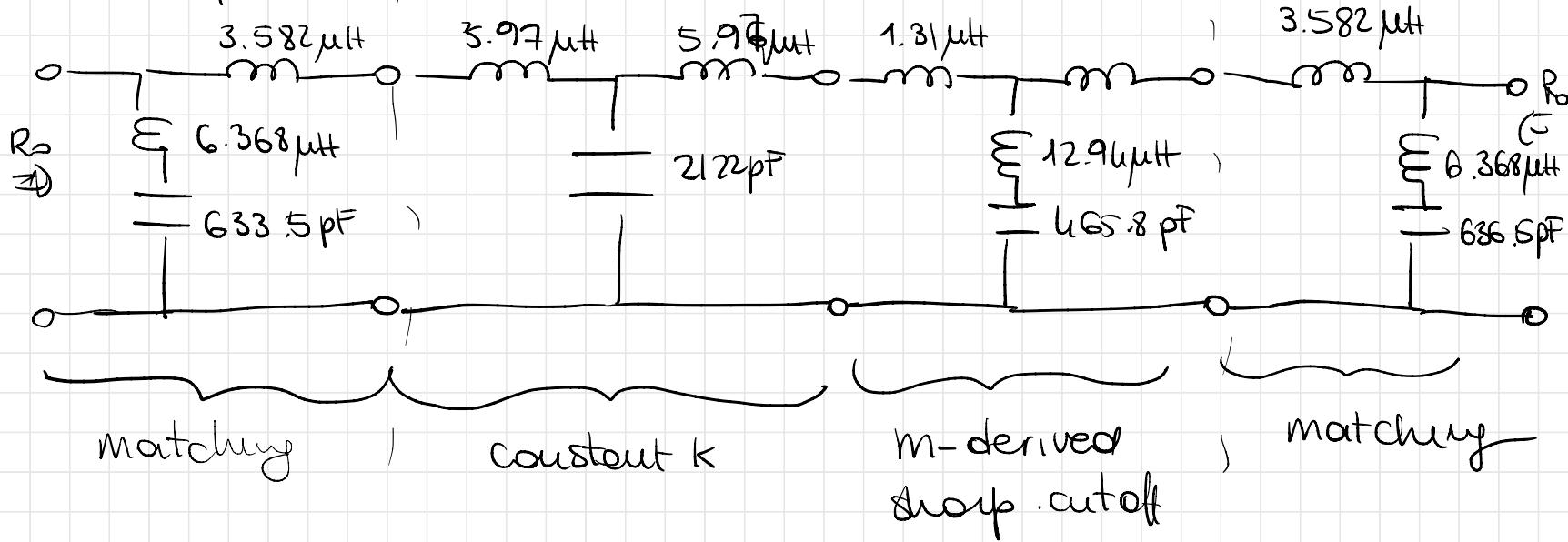

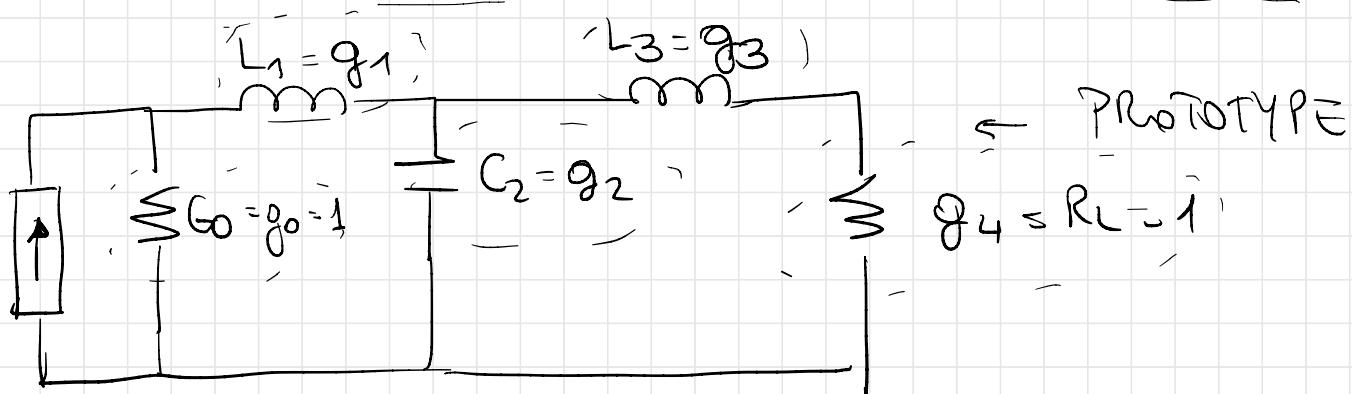Problem 4

Band pass filter design

Design a bandpass filter having a 0.5 dB equal ripple response with $N=3$. The center frequency is 16Hz, the bandwidth is 10%, and the impedance is 50Ω .



$$g_1 = L_1 = 1.5963$$

$$g_2 = C_2 = 1.0967$$

$$g_3 = L_3 = 1.5963$$

$$g_4 = R_L = 1$$

$$\Delta = \frac{\omega_2 - \omega_1}{\omega_0} = 0.1$$

$$\omega_0 = 1 \cdot 10^9 \text{ Hz}$$



$$t_0 = 50 \Omega$$

We can scale the low-pass prototype elements into a bandpass elements values (scaling also for impedance)

$$\sum L \Rightarrow$$

$$\sum \frac{Lz_0}{1/\omega_0 \Delta}$$
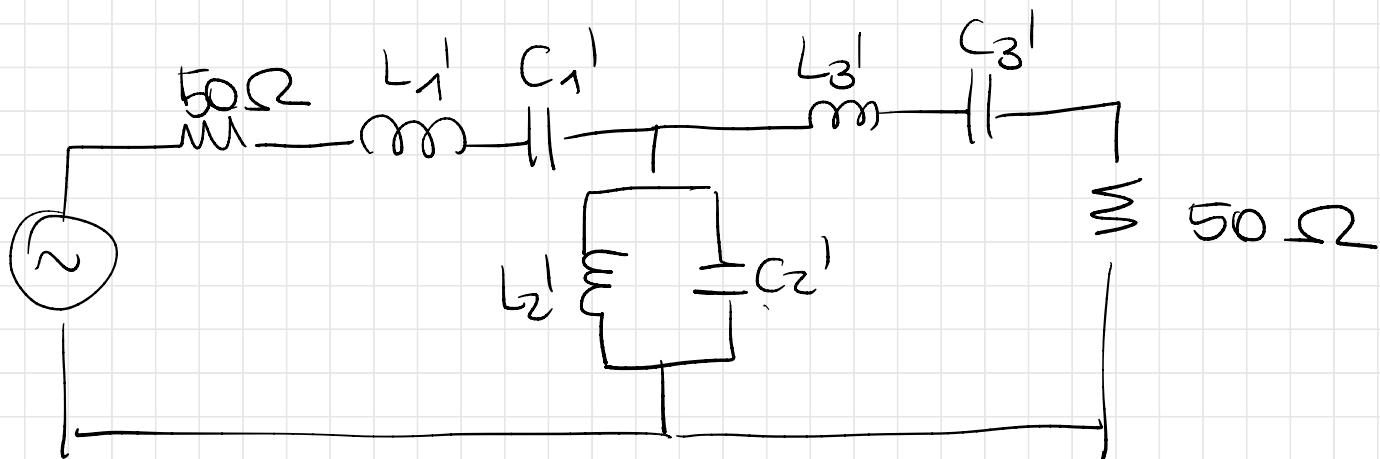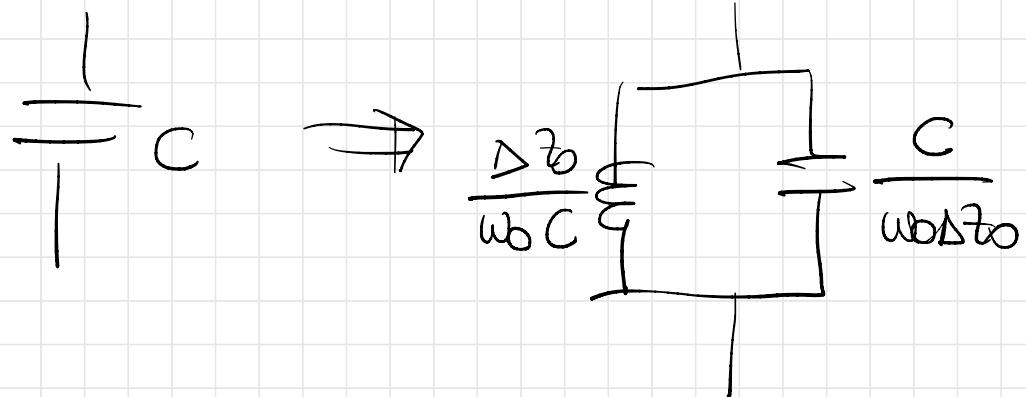
$$\frac{1}{T} \frac{\Delta}{\omega_0 L z_0}$$



$$L_1' = \frac{L_1 Z_0}{\omega_0 \Delta} = 127 \text{ nH}$$

$$C_1' = \frac{\Delta}{\omega_0 L_1 Z_0} = 0.199 \text{ pF}$$

$$L_2' = \frac{\Delta Z_0}{\omega_0 C_2} = 0.726 \text{ nH}$$

$$C_2' = \frac{C_2}{\omega_0 \Delta Z_0} = 34.91 \text{ pF}$$

$$L_3' = \frac{L_3 Z_0}{\omega_0 \Delta} = 127 \text{ nH}$$

$$C_3' = \frac{\Delta}{\omega_0 L_3 Z_0} = 0.199 \text{ pF}$$