

MICROWAVE ENGINEERING

Lecture 27:
Microwave
Filters - part I



MICROSTRUCTURE FILTERS

Typical Response :

- LOW-PASS
- HIGH-PASS
- BAND-PASS
- BAND-REJECT (STOP-BAND)

Filter is composed of WAVEGUIDE or transmission line periodically loaded with reactive elements

Methods for design



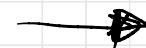


IMAGE PARAMETER
METHOD

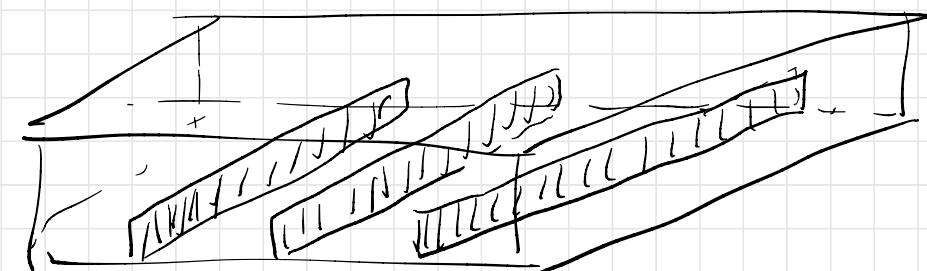

INSERTION LOSS
METHOD

FLUTERS ARE PERIODIC STRUCTURES

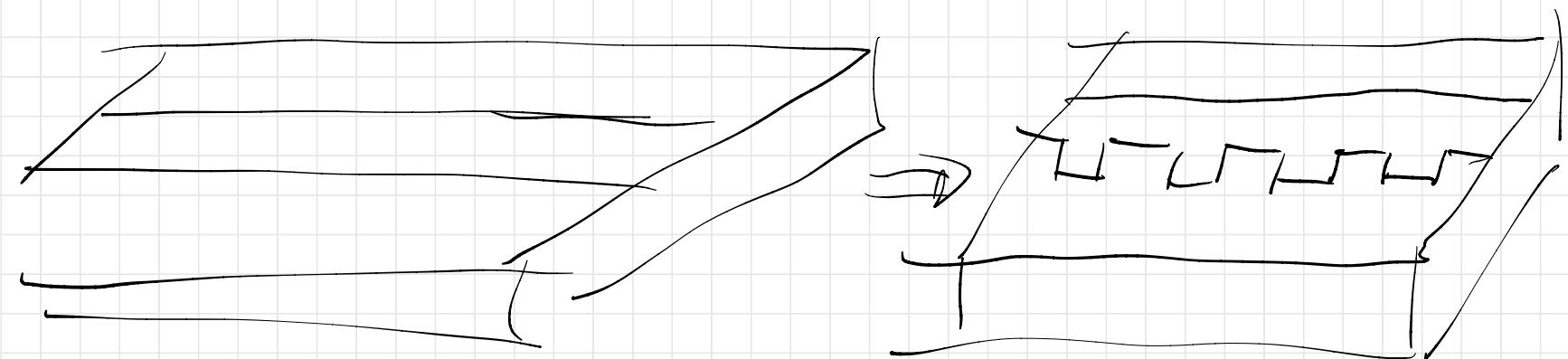

Analysis of infinite periodic structures

An intitely long periodic structure can be modeled through small cells of length d ^{with susceptance b} , which will be described with ABCD matrix:

$$\begin{bmatrix} V_n \\ I_n \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_{n+1} \\ I_{n+1} \end{bmatrix}$$

$$\left[\frac{d}{2} \right] \left[b \right] \left[\frac{d}{2} \right]$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \underbrace{\begin{bmatrix} \cos \frac{\theta}{2} & j \sin \frac{\theta}{2} \\ j \sin \frac{\theta}{2} & \cos \frac{\theta}{2} \end{bmatrix}}_{d/2 \text{ line}} \underbrace{\begin{bmatrix} 1 & 0 \\ jb & 1 \end{bmatrix}}_{\substack{\text{shunt} \\ \text{ susceptance}}} \underbrace{\begin{bmatrix} \cos \frac{\theta}{2} & j \sin \frac{\theta}{2} \\ j \sin \frac{\theta}{2} & \cos \frac{\theta}{2} \end{bmatrix}}_{d/2 \text{ line}}$$

$$= \begin{bmatrix} \left(\cos \theta - \frac{b}{2} \sin \theta \right) & j \left(\sin \theta + \frac{b}{2} \cos \theta - \frac{b}{2} \right) \\ j \left(\sin \theta + \frac{b}{2} \cos \theta + \frac{b}{2} \right) & \left(\cos \theta - \frac{b}{2} \sin \theta \right) \end{bmatrix}$$

$\theta = kd$ k propagation constant of the UNLOADED LINE

At the n^{th} all we can also write:

$$V_{n+1} = V_n e^{-rd} \quad \leftarrow$$

$$I_{n+1} = I_n e^{-rd} \quad \leftarrow$$

$$\begin{bmatrix} V_n \\ I_n \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_{n+1} \\ I_{n+1} \end{bmatrix} = \begin{bmatrix} V_{n+1} e^{rd} \\ I_{n+1} e^{rd} \end{bmatrix}$$

$$\begin{bmatrix} A - e^{rd} & B \\ C & D - e^{rd} \end{bmatrix} \begin{bmatrix} V_{n+1} \\ I_{n+1} \end{bmatrix} = 0$$

The only non-trivial solution is:

$$AD + e^{2\gamma d} - (A+D)e^{\gamma d} - BC = 0$$

Since the network is reciprocal $AD - BC = 1$

$$\rightarrow 1 + e^{2\gamma d} - (A+D)e^{\gamma d} = 0 \quad \text{dividing by } e^{\gamma d}$$

$$e^{-\gamma d} + e^{\gamma d} = A+D$$

From ABCD Matrix

$$\frac{A+D}{2} = \cos\theta - \frac{b}{2} \sin\theta = \cosh\gamma d$$

From matrix

We recall that $\gamma = \alpha + j\beta$

$$\begin{aligned} \cosh \gamma d &= \underline{\cosh(\alpha d)} \underline{\cos(\beta d)} + j \underline{\sinh(\alpha d)} \underline{\sin(\beta d)} \quad (1) \\ &= \cos \theta - \frac{b}{2} \sin \theta \\ &\quad \underbrace{\qquad\qquad\qquad}_{\text{purely real}} \end{aligned}$$

CASE 1 $\alpha = 0 \quad \beta \neq 0$ NON ATTENUATING PROPAGATING WAVE
(DEFINES A PASS-BAND)

Eq 1 reduces to

$$\cosh \beta d = \cos \theta - \frac{b}{2} \sin \theta \Rightarrow \underline{\text{solved for } \beta}$$

CASE $\alpha \neq 0, \beta = 0, \pi$

NON-PROPAGATING, ATTENUATED
WAVES

(define Stopband)

Eq 1 reduces to

$$\cosh \alpha d = \left| \cos \theta - \frac{b}{2} \sin \theta \right| \geq 1$$

\downarrow
1 solution ($\alpha > 0$) for positive travel
waves

The characteristic Impedance of the cell is $Z_B = Z_0 \frac{\sqrt{r+i}}{J+i}$

BLOCK
IMPEDANCE

From the ABCD matrix

$$\begin{bmatrix} A - e^{\gamma d} & B \\ C & D - e^{\gamma d} \end{bmatrix} \begin{bmatrix} V_{n+1} \\ I_{n+1} \end{bmatrix} = 0$$

$$(A - e^{\gamma d}) V_{n+1} + B I_{n+1} = 0$$

$$z_B = z_0 \frac{-B}{A - e^{\gamma d}}$$

$e^{\gamma d}$ can be expressed as a function of A and D

$$1 + e^{2\gamma d} - (A + D)e^{\gamma d} = 0$$

If $x = e^{\gamma d}$

$$e^{\gamma d} = \frac{(A+D) \pm \sqrt{(A+D)^2 - 4}}{2}$$

//

The Bloch impedance has 2 possible solutions:


$$Z_B^{\pm} = \frac{-2BZ_0}{2A - A - D \mp \sqrt{(A+D)^2 - 4}}$$

In a symmetric all the expression reduces to:

$$Z_0^{\pm} = \frac{\pm Z_0}{\sqrt{A^2 - 1}}$$

(\pm indicate positive/negative travelling waves)

TERMINATED PERIODIC STRUCTURE

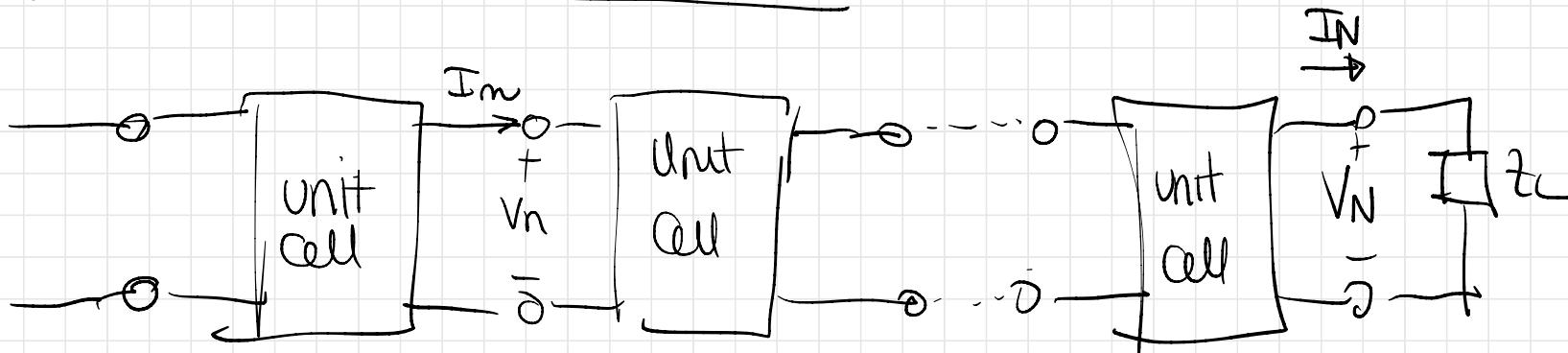

If we have no losses we can replace r_d with $j\beta n_d$
 So at the n^{th} cell we have:

$$V_n = V_0^+ e^{-j\beta n d} + V_0^- e^{j\beta n d}$$

$$I_n = I_0^+ e^{-j\beta n d} + I_0^- e^{j\beta n d} = \frac{V_0^+}{Z_B^+} e^{-j\beta n d} + \frac{V_0^-}{Z_B^-} e^{j\beta n d}$$

The incident and reflected voltages at the n^{th} cell

$$V_n^+ = V_0^+ e^{-j\beta n d}$$

$$V_n^- = V_0^- e^{j\beta n d}$$

$$V_n = V_n^+ + V_n^-$$

$$I_n = I_n^+ + I_n^- = \frac{V_n^+}{Z_B^+} + \frac{V_n^-}{Z_B^-}$$

At $n=N$

$$V_N = V_N^+ + V_N^- = Z_L I_N = Z_L \left(\frac{V_N^+}{Z_B^+} + \frac{V_N^-}{Z_B^-} \right)$$


The reflection coeff. at the load is:

$$\Gamma = \frac{V_N^-}{V_N^+} = - \frac{\frac{Z_L}{Z_B^+} - 1}{\frac{Z_L}{Z_B^-} - 1}$$

If the cells are symmetric ($A=D$) $\Rightarrow Z_B^+ = -Z_B^- = Z_B$
so the reflection coeff. is:

$$\Gamma = \frac{Z_L - Z_B}{Z_L + Z_B}$$

IMAGE PARAMETER METHOD

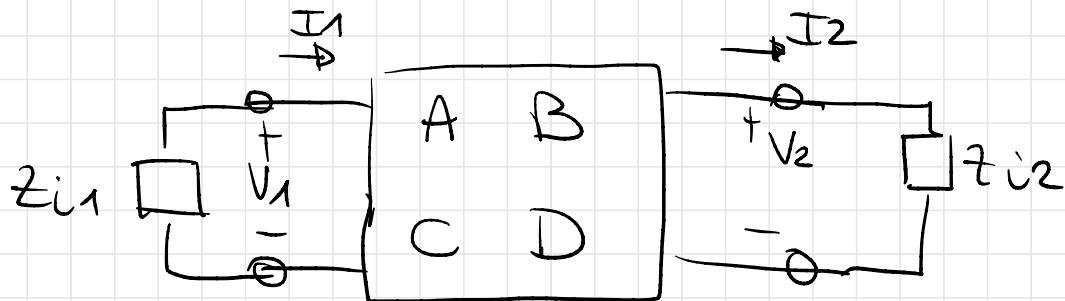

Z_{i1} and Z_{i2} are the input impedances of ports 1 and 2 when they are terminated with Z_{i2} and Z_{i1} .

$$Z_{i1} = \sqrt{\frac{AB}{CD}}$$

$$Z_{i2} = \sqrt{\frac{BD}{AC}} \quad \text{and} \quad Z_{i2} = \frac{D}{A} Z_{i1}$$

If the network is symmetric


$$Z_{i2} = Z_{i1}$$

$$e^{-\gamma} = \sqrt{AD} - \sqrt{BC}$$



$$\cosh \gamma$$

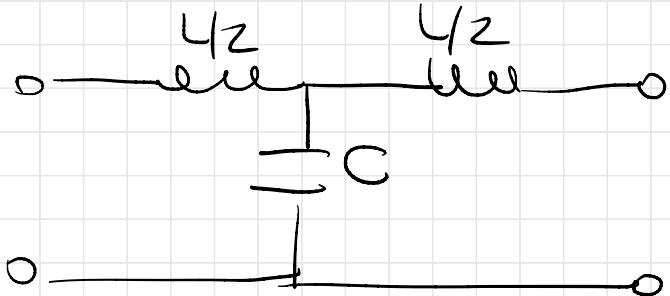CONSTANT-K FILTER SECTIONS (CONSTANT-K LOW-PASS PROTOTYPE)



works as a low-pass filter

For a generic T-network

$$Z_{iT} = \sqrt{Z_1 Z_2} \sqrt{1 + \frac{Z_1}{4Z_2}}$$

$$Z_1 = j\omega L$$

$$Z_2 = \frac{1}{j\omega C}$$

$$Z_{iT} = \sqrt{\frac{L}{C}} \sqrt{1 - \frac{\omega^2 LC}{4}}$$

If the cut-off frequency is $w_c = \frac{2}{\sqrt{LC}}$ and $R_o = \sqrt{\frac{L}{C}} = K =$ constant

then

$$Z_{IT} = R_o \sqrt{1 - \frac{\omega^2}{w_c^2}}$$

$$\text{If } \omega = 0 \Rightarrow Z_{IT} = R_o$$

For a generic T-network

$$Z_T = 1 + \frac{Z_1}{2Z_2} + \sqrt{\frac{Z_1}{Z_2} + \frac{Z_1^2}{4Z_2^2}} = 1 - \frac{2\omega^2}{w_c^2} + \frac{2\omega}{w_c} \sqrt{\frac{\omega^2}{w_c^2} - 1}$$

We can identify two frequency regions

①

$\omega < \omega_C$: PASSBAND

z_{it} IS REAL

γ IS IMAGINARY ($\alpha=0$)
 $\beta\neq 0$


②

$\omega > \omega_C$: STOPBAND


z_{it} IS IMAGINARY

γ IS REAL $\left(\begin{array}{l} \alpha \neq 0 \\ \beta = 0 \end{array}\right)$

HIGH-PASS CONSTANT-K SECTIONS

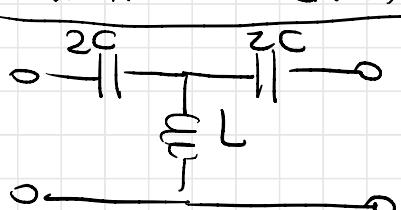

or

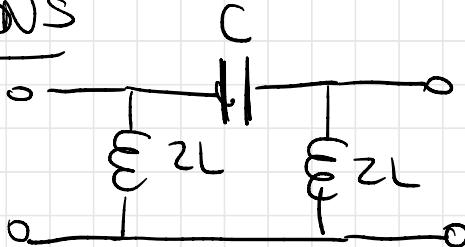


$$R_0 = \sqrt{\frac{L}{C}}$$


$$\omega_C = \frac{1}{2\sqrt{LC}}$$

M-DERIVED FILTER SECTIONS

LOW-PASS T- SECTION

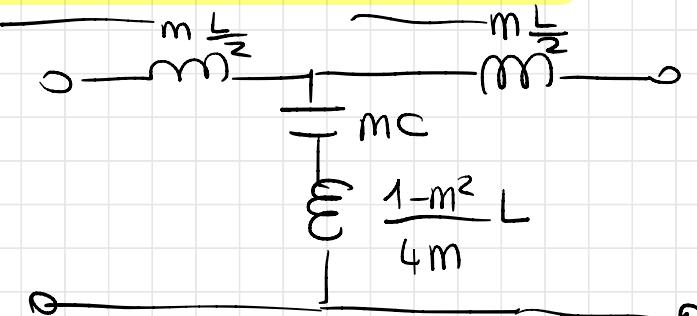

HIGH-PASS T- SECTION

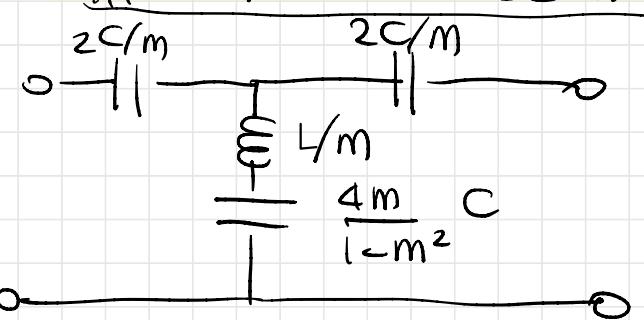


COMPOSITE FILTER

Combining k-constant and M-derived sections we can realize the filters of desired properties

SUMMARY FOR DESIGN

LOW-PASS

Constant-k T section

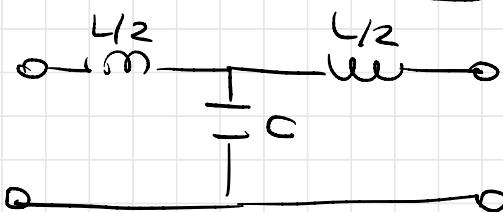

$$R_o = \sqrt{4C}$$


$$L = \frac{2R_o}{\omega_c}$$

$$\omega_c = \frac{2}{\sqrt{LC}}$$

$$C = \frac{1}{\omega_c R_o}$$

HIGH-PASS

Constant-k T-section

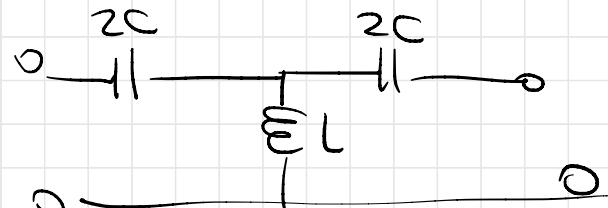

$$R_o = \sqrt{4C}$$


$$L = \frac{R_o}{2\omega_c}$$

$$\omega_c = \frac{1}{2} \sqrt{LC}$$

$$C = \frac{1}{2\omega_c R_o}$$

LOW-PASS

m-derived T-section

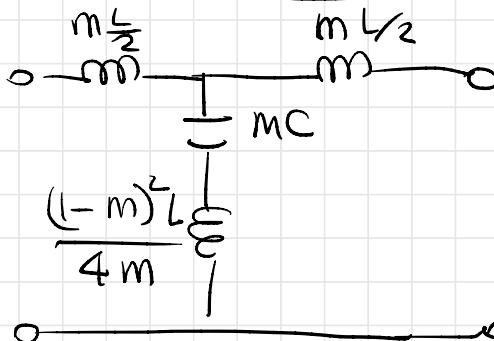


$L, C \propto m$ constant k

$$m = \begin{cases} \sqrt{1 - (\omega_c/\omega_0)^2} & \text{sharp cut-off} \\ 0.6 & \text{for matching} \end{cases}$$

HIGH-PASS

m-derived T-section

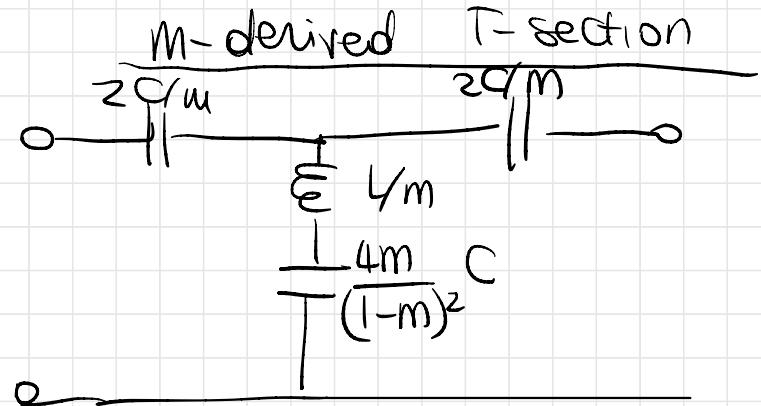

$L, C \propto m$ constant $-k$

$$m = \begin{cases} \sqrt{1 - (\omega_0/\omega_c)^2} & \text{for sharp cut-off} \\ 0.6 & \text{for matching} \end{cases}$$