

MICROWAVE ENGINEERING

Lecture 10:
Transmission
lines problems



④ A transmission line has the following per unit length parameters :

$$L = 0.2 \frac{\mu H}{m}$$

$$C = 30 \frac{pF}{m}$$

$$R = 5 \frac{\Omega}{m}$$

$$G = 0.01 \frac{S}{m}$$

Calculate the propagation constant and characteristic impedance of this line for $f = 500 \text{ MHz}$. Recalculate those quantities in absence of losses.

The propagation constant is:

$$\gamma = \sqrt{(R+j\omega L)(G+j\omega C)}$$

$$\omega = 2\pi f = 2\pi \cdot 500 \cdot 10^6 = 3.14 \cdot 10^9 \frac{\text{rad}}{\text{s}}$$

$$\begin{aligned}\gamma &= \sqrt{\left[5 + j \cdot 3.14 \cdot 10^9 \cdot 0.2 \cdot 10^{-6} \right] \left[0.01 + j 3.14 \cdot 10^9 \cdot 30 \cdot 10^{-12} \right]} = \\ &= \sqrt{[5 + j 628] [0.01 + j 0.094]} = 0.43 + j 7.69 \frac{\text{hp}}{\text{m}}, \frac{\text{rad}}{\text{m}}\end{aligned}$$

The characteristic impedance of the line are:

$$Z_0 = \sqrt{\frac{R+j\omega L}{G+j\omega C}} = 81 + j 3.97 \Omega$$


If we suppose losses are absent ($R = G = 0$)
then we get:

$$f = \omega \sqrt{LC} = 7.69 \frac{\text{rad}}{\text{m}}$$

$$Z_0 = \sqrt{\frac{L}{C}} = 81.65 \Omega$$

② A lossless transmission line of electrical length 0.3λ is terminated with a load impedance as in figure. Find:

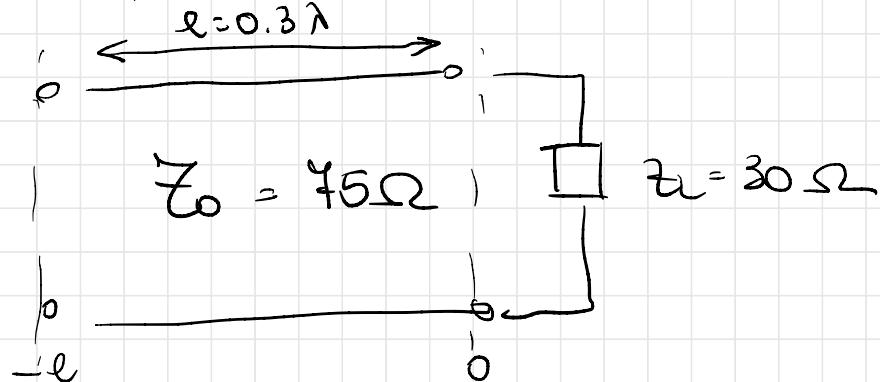- the reflection coefficient at the load ;
- the SWR on the line ;
- the reflection coefficient at the input of the line ;
- the input impedance on the line .



The reflection coefficient at the load :

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{30 - 75}{30 + 75} = \frac{-45}{105} = -0.43$$

The standing wave ratio is:

$$SWR = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 0.43}{1 - 0.43} = 2.5$$

The reflection at the input of the line is:

$$\Gamma_{IN} = \Gamma_L e^{-j\beta l} = \quad \beta = \frac{2\pi}{\lambda} \quad l = 0.3\lambda$$

$$= -0.43 e^{-j0.6\pi} = 0.13 + j0.4 \quad \beta l = \frac{2\pi}{\lambda} \cdot 0.3\lambda = 0.6\pi$$

The input impedance is:


$$Z_{IN} = Z_0 \frac{Z_L + jZ_0 \tan \beta}{Z_0 + jZ_L \tan \beta} = 75 \frac{30 + j75 \tan(0.6\pi)}{75 + j30 \tan(0.6\pi)} =$$
$$= 124.9 + j 77 \quad \Omega$$

③ A lossless transmission line is terminated with 100Ω load. If the SWR = 1.5 find the two possible characteristic impedance of the line.

We know that $\text{SWR} = \frac{1+|\Gamma|}{1-|\Gamma|}$

$$1+|\Gamma| = \text{SWR} - \text{SWR}|\Gamma| \Rightarrow |\Gamma| + |\Gamma|\text{SWR} = \text{SWR} - 1$$

$$\Rightarrow |\Gamma| = \frac{\text{SWR} - 1}{\text{SWR} + 1} = \frac{0.5}{2.5} = 0.2$$

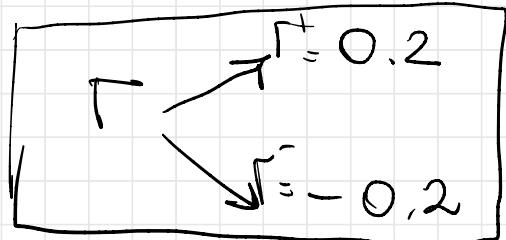

We also know that

$$F = \frac{Z_L - Z_0}{Z_L + Z_0}$$


$$\left\{ \begin{array}{l} F^+ = \frac{Z_L - Z_0}{Z_L + Z_0} = 0.2 \\ F^- = \frac{Z_L - Z_0}{Z_L + Z_0} = -0.2 \end{array} \right.$$

$$\left\{ \begin{array}{l} Z_0 = Z_L \frac{1 - F^+}{1 + F^+} = 100 \frac{1 - 0.2}{1 + 0.2} = 66.7 \Omega \end{array} \right.$$

$$\left\{ \begin{array}{l} Z_0 = Z_L \frac{1 - F^-}{1 + F^-} = 100 \frac{1 + 0.2}{1 - 0.2} = 150 \Omega \end{array} \right.$$

④

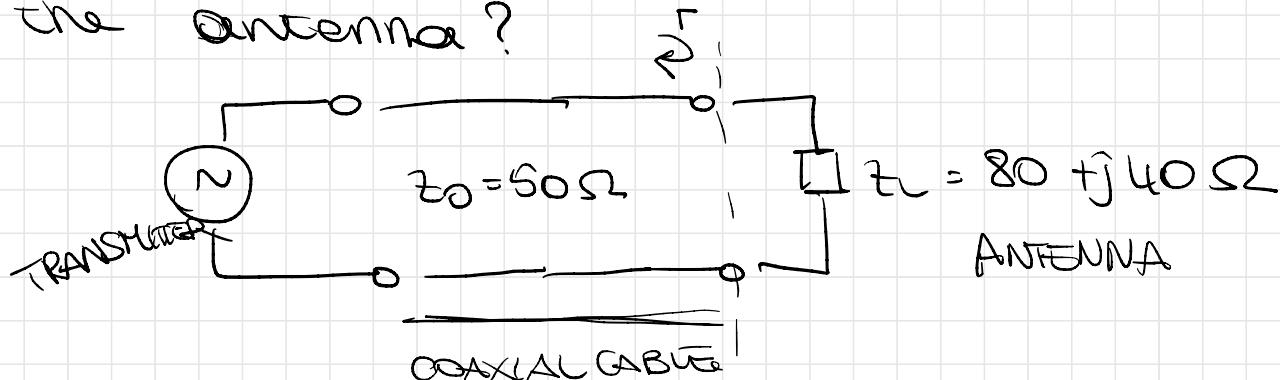A Radio transmitter is connected to an antenna having an impedance $Z_L = 80 + j 40 \Omega$ with a 50Ω coaxial cable. If the 50Ω transmitter can deliver 30W when connected to a 50Ω load, how much power is delivered to the antenna?



$$P_{IN} = 30W$$

The reflection coefficient at the load is:

$$\Gamma = \frac{z_L - z_0}{z_L + z_0} = \frac{80 + j40 - 50}{80 + j40 + 50} = \frac{30 + j40}{130 + j40} = 0.29 + j0.2$$

$$|\Gamma|^2 = 0.135$$

$$\begin{aligned} P_{LOAD} &= P_{IN} - P_{REF} = \frac{|V_o + I|^2}{2Z_0} - |\Gamma|^2 \frac{|V_o + I|^2}{2Z_0} = \\ &= \frac{|V_o + I|^2}{2Z_0} (1 - |\Gamma|^2) = P_{IN} (1 - |\Gamma|^2) = \end{aligned}$$

$$30 (1 - 0.135) = \underline{25.94 \text{ W}}$$

