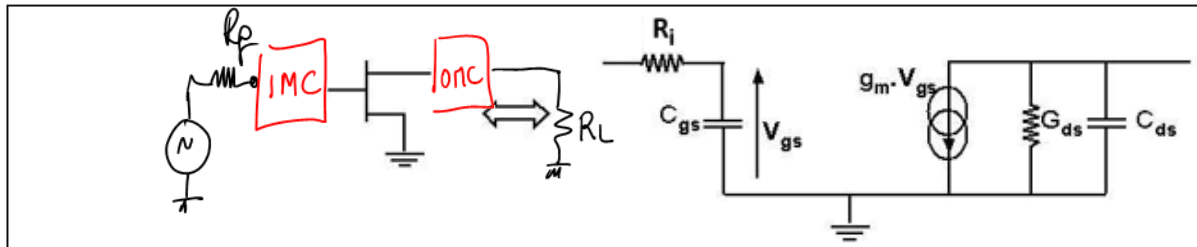


## Basics of Active and Nonlinear HF Electronics – Tutorial 2

### A ) Power gain matching of a single-stage narrow-band amplifier

This figure represents the simplified electrical model of an FET.





The model parameters are given at a bias point of ( $V_{GS0} = -2$  V and  $V_{DS0} = 20$  V)

$R_i = 5 \Omega$  ;  $C_{GS} = 0.5$  pF ;  $g_m = 100$  ms ;  $R_{DS} = 200 \Omega$  ;  $C_{DS} = 0.15$  pF

The amplifier environment is :  $R_G = 50 \Omega$  ;  $R_L = 50 \Omega$  ;  $f_0 = 10$  GHz

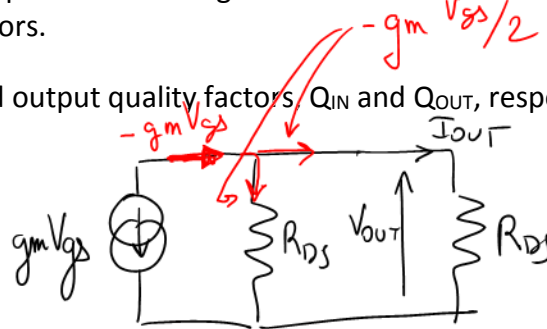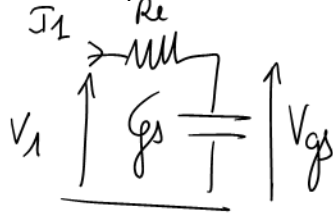- 1) Determine the expression of  $G_{MAX}$  : maximum power gain of the transistor as a function of frequency
- 2) We consider the design of a linear amplifier, which is loaded by a resistor ( $R_L$ ) while the input generator has an internal resistor ( $R_G$ ).
  - a) Draw the ideal input and output matching circuits of a narrow-band amplifier which is matched to its maximum power gain  $G_{MAX}$  at  $f_0$ .
  - b) Determine the expressions of each passive matching elements as a function of  $f_0$ , the model parameters and the  $R_G$  and  $R_L$  resistors.
- 3) Determine the expressions of the input and output quality factors,  $Q_{IN}$  and  $Q_{OUT}$ , respectively.



$$P_{IN} = \frac{1}{2} \text{Re}(V_1 I_1^*)$$

$$= \frac{1}{2} \text{Re}\left(\underbrace{\left(R_i - j \frac{1}{G_{gs} \omega}\right)}_{V_1} I_1 I_1^*\right) = \frac{1}{2} R_i |I_1|^2$$

$$I_1 = j G_{gs} \omega V_{gs} \rightarrow |I_1| = G_{gs} \omega |V_{gs}|$$

$$P_{IN} = \frac{1}{2} R_i G_{gs}^2 \omega^2 |V_{gs}|^2$$

$$G_{MAX} = \frac{1}{4} \frac{R_{DS} g_m^2}{R_i C_{gs}^2 \omega^2}$$

$$P_{OUT} = \frac{1}{2} \text{Re}(V_{OUT} I_{OUT}^*)$$


$$= \frac{1}{2} \text{Re}(R_{DS} I_{OUT} I_{OUT}^*)$$

$$= \frac{1}{2} R_{DS} |I_{OUT}|^2$$

$$= \frac{1}{2} R_{DS} \left| -g_m \frac{V_{gs}}{2} \right|^2$$

max gain

$$P_{OUT} = \frac{1}{8} R_{DS} g_m^2 |V_{gs}|^2$$

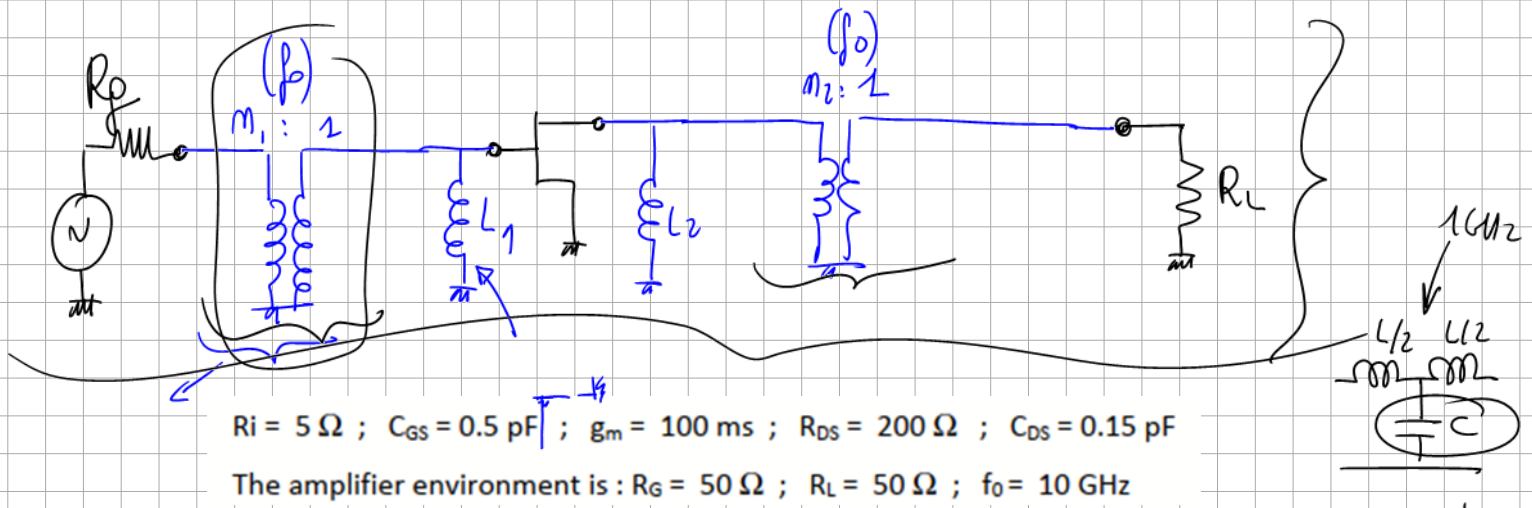

1) INPUT MATCHING ( $R_i$  or  $R_{IN}$  parallel? to transform to  $R_G \approx 50 \Omega$ )

$$R_{IN}(10 \text{ GHz}) = \frac{1}{R_i C_{GS}^2 \omega^2} = \frac{1}{5 (0.5 \cdot 10^{-12} 2\pi \cdot 10^{10})^2} = \frac{1}{5 \times \pi^2 \cdot 10^{-4}} = \frac{10000}{5 \pi^2} = 202 \Omega$$

$\frac{R_{IN}}{R_G} = \frac{202}{50} \approx 4$  and  $\frac{R_G}{R_i} = \frac{50}{5} = 10 \rightarrow$  Best choice // matching  $m_1 = \sqrt{\frac{202}{50}} = 2$   
 $L_1 = \frac{1}{C_{GS} \omega^2} = 0.5 \text{ mH}$


• OUTPUT MATCHING

$L_2 = \frac{1}{C_{DS} \omega^2} = 1.7 \text{ mH}$   
 $m_2 = \sqrt{\frac{R_{DS}}{R_L}} = \sqrt{\frac{200}{50}} = 2$

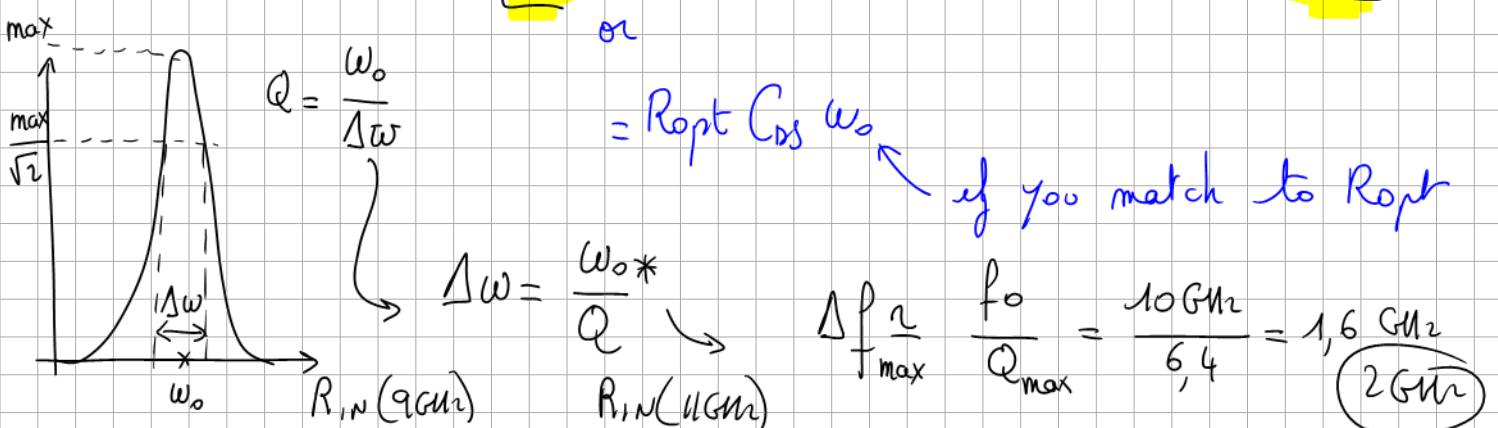2) Quality factors

• INPUT  $Q_{IN} = \frac{1}{R_i C_{GS} \omega_0} = \frac{1}{5 (0.5 \cdot 10^{-12} 2\pi \cdot 10^{10})} = \frac{100}{5\pi} = 6.4 *$

$Q_{OUT} = R_{DS} C_{DS} \omega_0 = 200 \times 0.15 \cdot 10^{-12} 2\pi \cdot 10^{10} = 1.9$   
 or  $Q_{OUT} = R_{opt} C_{DS} \omega_0$  if you match to  $R_{opt}$



## B ) Power gain matching of a two stage narrow-band amplifier

### Main pecifications of the narrow-band amplifier:

Output Power  $P_{OUT} > 1 \text{ W}$  ; Center frequency  $f_0 = 15 \text{ GHz}$  ; Power Gain  $G_P > 15 \text{ dB}$

### Selected MMIC foundry (0.15 $\mu\text{m}$ GaAs HEMT) :

Power Density  $PD = 1 \text{ W/mm}$  ; Measured Gain  $G_{MAX}(@10\text{GHz}) = 16 \text{ dB}$  ;

Saturated Drain Current  $I_{DSS} = 800 \text{ mA/mm}$  ; Drain Voltage range ( $V_{DSmin}=1\text{V}$  and  $V_{DSmax}=11\text{V}$ )


Pinch-off Voltage :  $V_P = -4 \text{ V}$

Optimum load impedance  $R_{OPT} = 12.5 \Omega \cdot \text{mm}$

Small-signal model:  $C_{GS} = 2.7 \text{ pF/mm}$  ;  $R_i = 1 \Omega \cdot \text{mm}$  ;  $g_m = 200 \text{ mS/mm}$  ;


$R_{DS} = 125 \Omega \cdot \text{mm}$  ;  $C_{DS} = 0.6 \text{ pF/mm}$

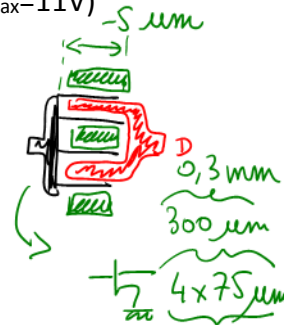Selected device size @ 15 GHz =  $4 \times 75 \mu\text{m}$  GaAs HEMT



- 1) Given the required specifications and the selected transistor technology, determine the initial sizing of the power amplifier (number of stages, number of amplifying cells per stage, power gain and input/output powers of each stage) using the selected device size ( $4 \times 75 \mu\text{m}$ ) as the unitary amplifying cell.
- 2) Given that only the last stage should be matched to its optimum output power while all the preceding stages should be matched to their maximum power gain, draw the input and output matching circuits of this two-stage narrow-band amplifier and calculate the values of each matching elements.
- 3) Calculate the input and output quality factors of each stage to assess what will be the bandwidth behavior.
- 4) Can you comment on the power limitations and the power added efficiency of this two-stage amplifier?

Diagram of a two-stage narrow-band amplifier:

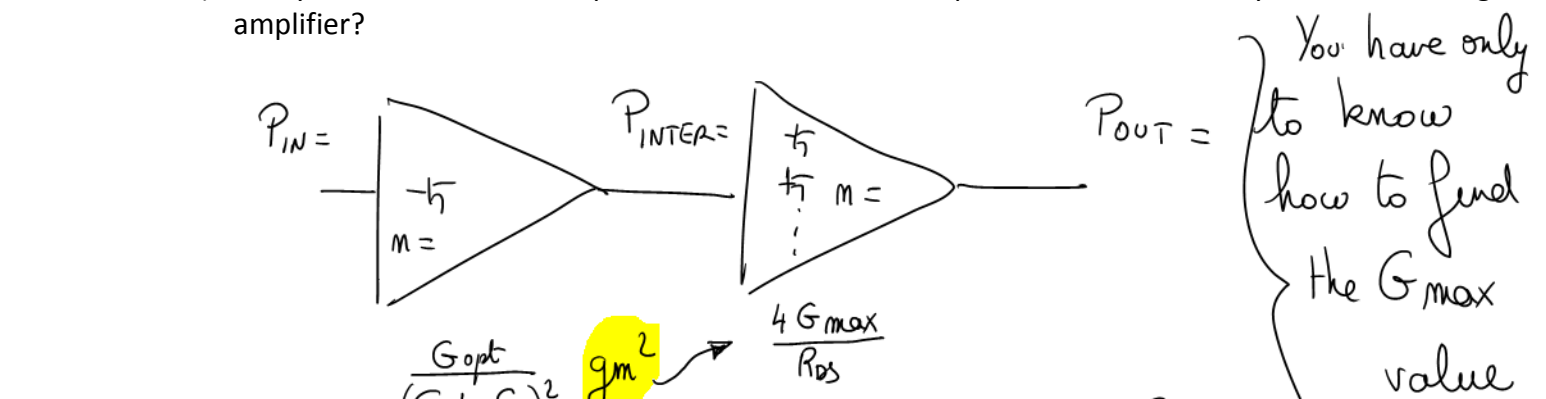

Handwritten notes and equations:

You have only to know how to find the  $G_{max}$  value

$$G_P(R_{opt}) = \frac{\frac{G_{opt}}{(G_{opt} + G_{DS})^2} g_m^2}{R_i C_{GS}^2 \omega^2} = \frac{G_{opt}}{(G_{opt} + G_{DS})^2} \times \frac{4 G_{max}}{R_{DS}}$$

$$G_{max} = \frac{1}{4} \frac{R_{DS} g_m^2}{R_i C_{GS}^2 \omega^2} \times \frac{1/R_{opt}}{(1/R_{opt} + 1/R_{DS})^2} \times \frac{4 G_{max}}{R_{DS}}$$

$$G_P = \frac{G_2}{[G_2 + g_{DS}]^2} \frac{g_m^2}{R_i C_{GS}^2 \omega^2} \times$$

$$G_P(R_{opt}) = \frac{4 R_{opt} R_{DS}}{(R_{opt} + R_{DS})^2} G_{max}$$

### Main specifications of the narrow-band amplifier:

Output Power  $P_{OUT} > 1 \text{ W}$  ; Center frequency  $f_0 = 15 \text{ GHz}$  ; Power Gain  $G_P > 15 \text{ dB}$

### Selected MMIC foundry (0.15 $\mu\text{m}$ GaAs HEMT) :

Power Density  $PD = 1 \text{ W/mm}$  ; Measured Gain  $G_{MAX}(@10\text{GHz}) = 16 \text{ dB}$  ;

Saturated Drain Current  $I_{DSS} = 800 \text{ mA/mm}$  ; Drain Voltage range ( $V_{DSmin} = 1\text{V}$  and  $V_{DSmax} = 11\text{V}$ )


Pinch-off Voltage :  $V_P = -4 \text{ V}$

Optimum load impedance  $R_{OPT} = 12.5 \Omega \cdot \text{mm}$  •


Small-signal model:  $C_{GS} = 2.7 \text{ pF/mm}$  ;  $R_i = 1 \Omega \cdot \text{mm}$  ;  $g_m = 200 \text{ mS/mm}$  ;

$R_{DS} = 125 \Omega \cdot \text{mm}$  ;  $C_{DS} = 0.6 \text{ pF/mm}$

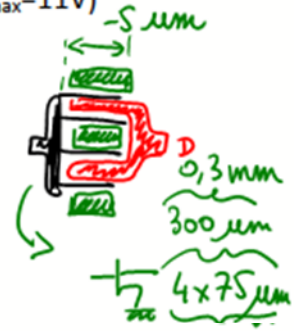Selected device size @ 15 GHz =  $4 \times 75 \mu\text{m}$  GaAs HEMT



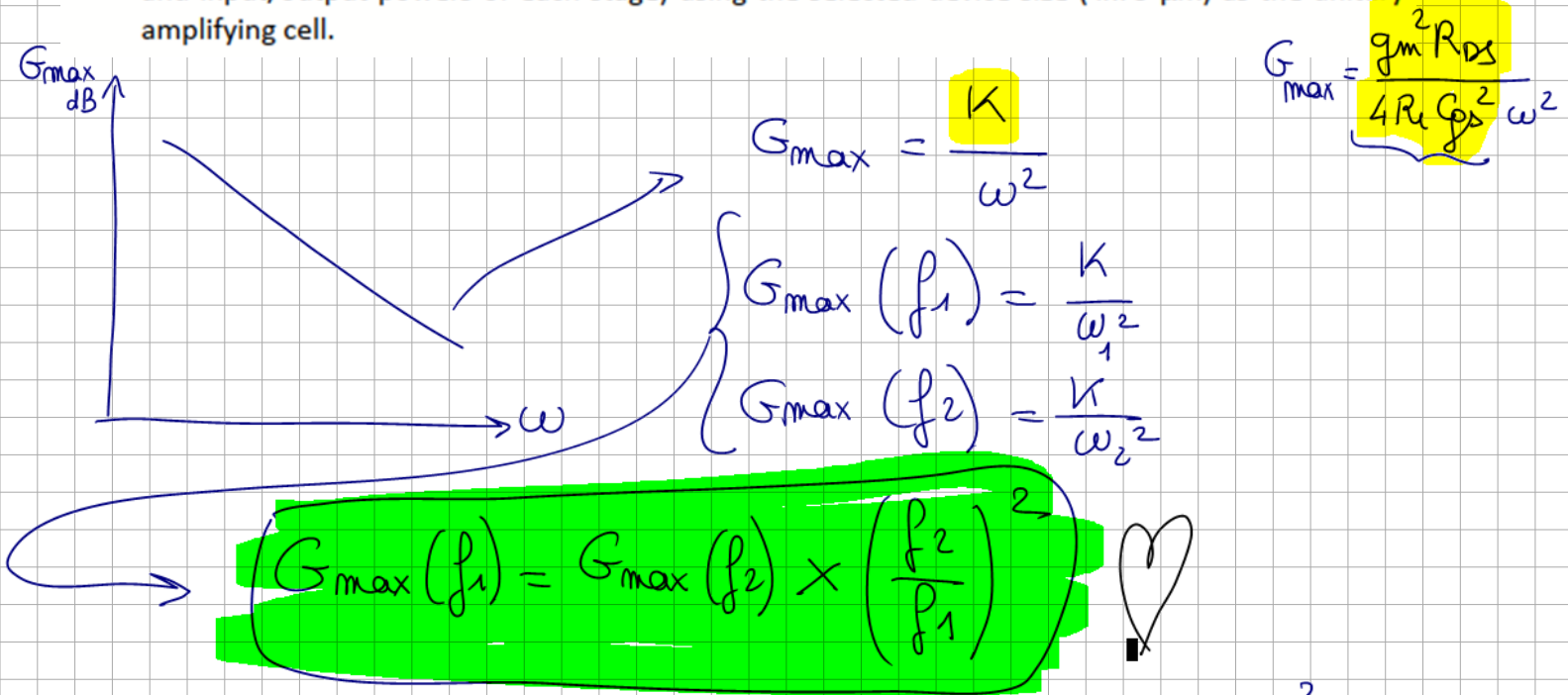- 1) Given the required specifications and the selected transistor technology, determine the initial sizing of the power amplifier (number of stages, number of amplifying cells per stage, power gain and input/output powers of each stage) using the selected device size ( $4 \times 75 \mu\text{m}$ ) as the unitary amplifying cell.




In our case :  $G_{\max}(15\text{G}) = G_{\max}(10\text{G}) \times \left(\frac{10}{15}\right)^2 = 39,8 \times \left(\frac{10}{15}\right)^2 = 17,7$

$G_{\max}(10\text{G}) = 16\text{dB} = 10^{1,6} = 39,8$

$\underline{\underline{= 12,5\text{dB}}}$

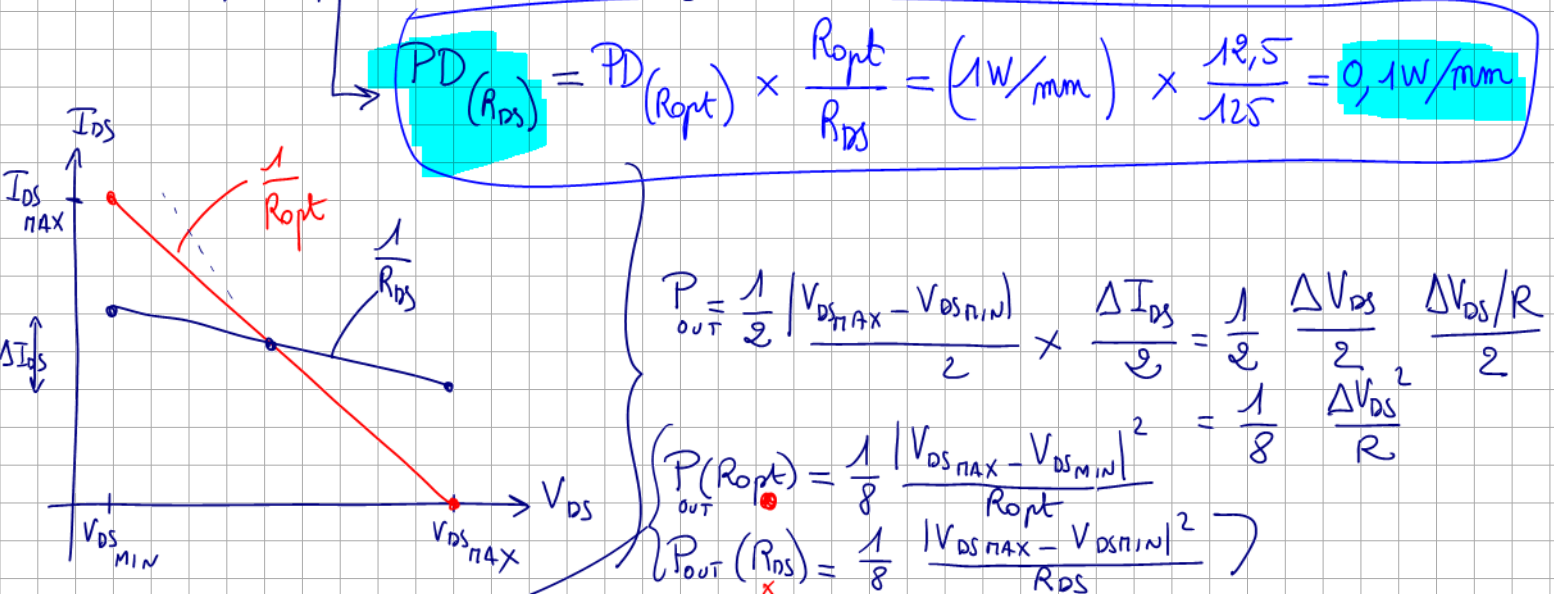1<sup>st</sup> case = Optimize a stage to get  $G_{\max} = 12,5\text{dB} = 17,7$  and  $R_{DS}$  load







$$PD(R_{DS}) = PD(R_{opt}) \times \frac{R_{opt}}{R_{DS}}$$

2<sup>nd</sup> case Optimize a stage to get  $P_{OUT\ MAX} \Rightarrow PD(R_{opt}) = 1\text{ W/mm}$  and  $R_{opt}$  load

$$G_p(R_{opt}) = 4 \frac{R_{opt} R_{DS}}{(R_{opt} + R_{DS})^2} G_{max} = 4 \times \frac{12.5 \times 125}{(12.5 + 125)^2} \times 17.7$$

$$G_p(R_{opt}) = 5.85 = 7.7\text{ dB}$$

1 Size of Last stage

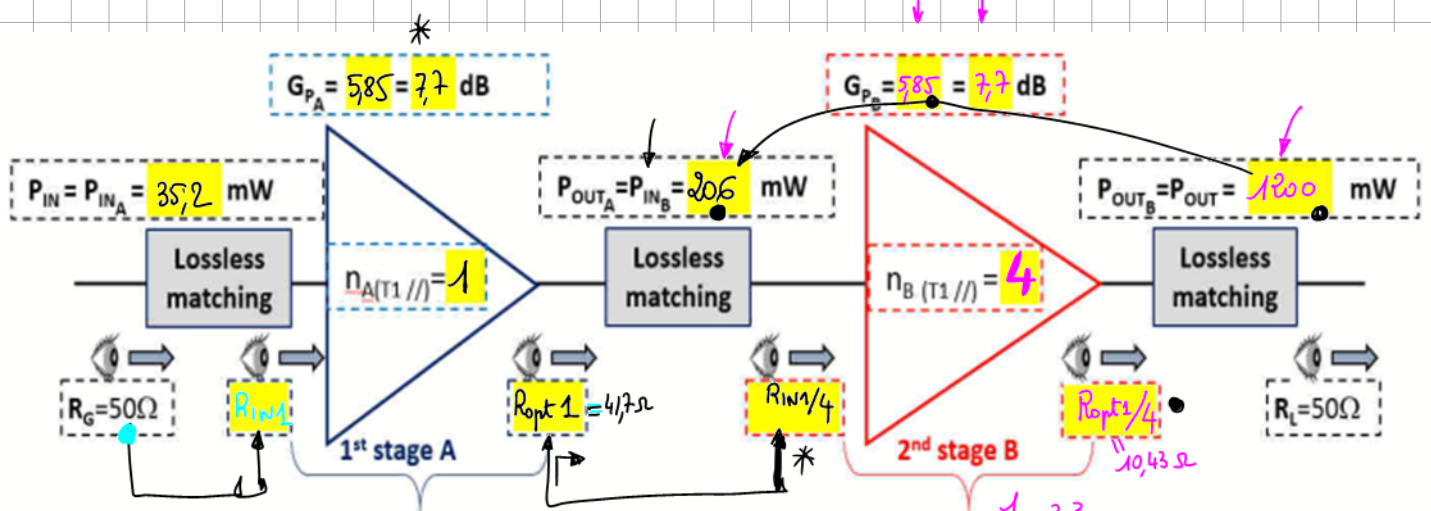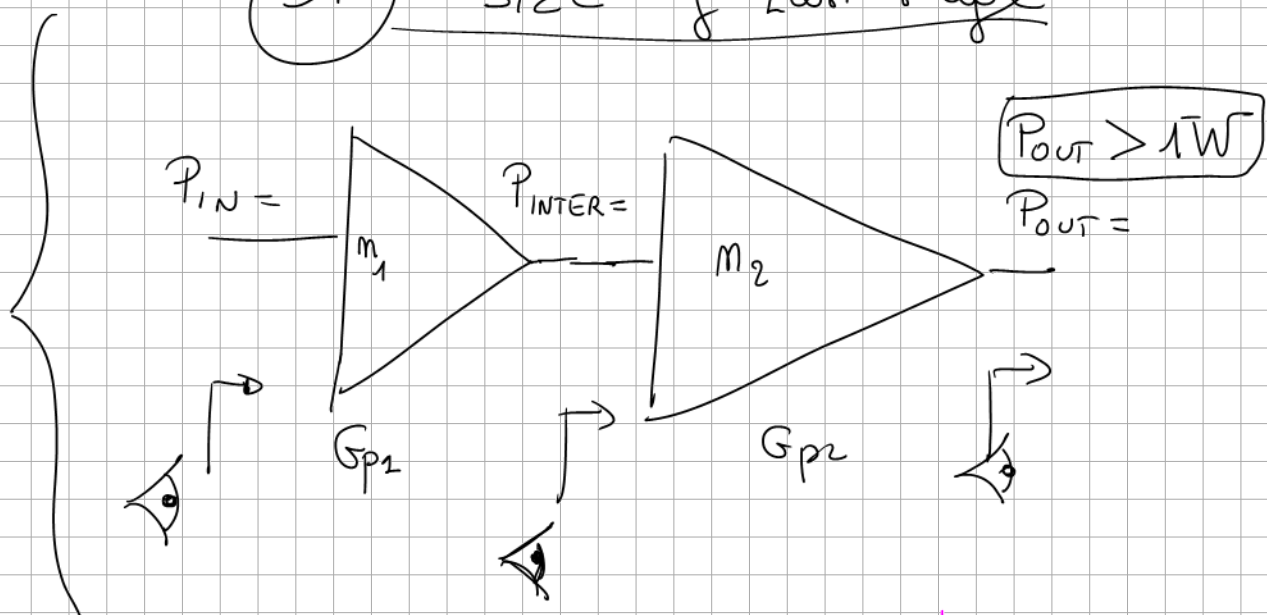

$P_{OUT} > 1\text{ W}$

$PD(R_{opt}) = 1\text{ W/mm}$

$PD(R_{DS}) = 0.1\text{ W/mm}$

$W_T(R_{opt}) = 1\text{ mm} \xrightarrow{2\text{ mm}} \text{Ineed } 4 \times 0.3\text{ mm} = 1.2\text{ mm}$

$W_T(R_{DS}) = 10\text{ mm} \xrightarrow{20\text{ mm}} \text{Ineed } 34 \times 0.3\text{ mm} = 10.2\text{ mm}$

each device is 0.3 mm

$\frac{1}{0.3} = 3.3 \dots$

$INT(\frac{10}{0.3})$

$$R_{opt} = 12,5 \Omega \cdot \text{mm} \rightarrow R_{opt,1}(0,3 \text{ mm}) = \frac{12,5}{0,3} = 41,7 \Omega$$

$$\frac{R_{opt,1}}{4} = \frac{41,7}{4} = \frac{12,5}{1,2} = 10,43 \Omega$$

$$P_{out,0} = 1,2 \text{ mm} \times PD(R_{opt}) = 1,2 \text{ mm} \times 1 \text{ W/mm} = 1,2 \text{ W}$$

$$P_{IN,B} = \frac{P_{out,0}}{G_p(R_{opt})} = \frac{1,2 \text{ W}}{5,85} = 0,206 \text{ W} = 206 \text{ mW}$$

1st stage to reach 206 mW → loading by  $R_{opt} \rightarrow PD = 1 \text{ W/mm} \rightarrow I \text{ need } W_T = \left( \frac{0,206 \text{ W}}{1 \text{ W/mm}} \right) = 0,206 \text{ mm}$   
 → I need only one device of 0,3 mm

transistors in // are  $2^p$   $\left\{ \begin{array}{l} p=0 \rightarrow 1 \text{ device} \\ p=1 \rightarrow 2 \\ p=2 \rightarrow 4 \\ \vdots \end{array} \right.$   
 if the load is  $R_{DS} \rightarrow PD = 0,1 \text{ W/mm} \rightarrow I \text{ need } W_T = \left( \frac{0,206 \text{ W}}{0,1 \text{ W/mm}} \right) = 2,06 \text{ mm}$   
 → I need  $\frac{2,06 \text{ mm}}{0,3 \text{ mm}} \Rightarrow 7 \text{ transistors} \Rightarrow 8 \text{ transistors} = 2^3$   
 not efficient


$$P_{IN,A} = \frac{P_{out,A}}{G_p(R_{opt})} = \frac{206 \text{ mW}}{5,85} = 35,2 \text{ mW}$$

• To determine the input matching and interstage matching → Calculate  $R_{IN}$

$$R_{IN} = \frac{1}{R_i G_p^2 \omega^2} \rightarrow R_{IN}(15 \text{ GHz}) = \frac{1}{1 \times (2,2 \cdot 10^{12} \times 2\pi \times 15 \cdot 10^9)^2} = 15,4 \Omega \cdot \text{mm}$$

$$0,3 \text{ mm} \Rightarrow R_{IN,1} = \frac{15,4 \Omega}{0,3} = 51,5 \Omega$$
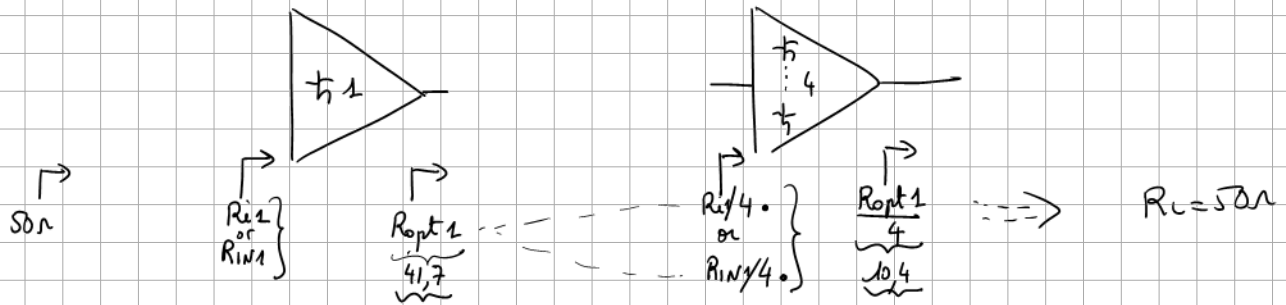
$$R_{i,1} = \frac{1}{0,3} = 3,33 \Omega$$



## Main specifications of the narrow-band amplifier:

Output Power  $P_{OUT} > 1 \text{ W}$  ; Center frequency  $f_0 = 15 \text{ GHz}$  ; Power Gain  $G_P > 15 \text{ dB}$

## Selected MMIC foundry (0.15 $\mu\text{m}$ GaAs HEMT) :

Power Density  $PD = 1 \text{ W/mm}$  ; Measured Gain  $G_{MAX}(@10\text{GHz}) = 16 \text{ dB}$  ;

Saturated Drain Current  $I_{DSS} = 800 \text{ mA/mm}$  ; Drain Voltage range ( $V_{DSmin} = 1\text{V}$  and  $V_{DSmax} = 11\text{V}$ )

Pinch-off Voltage :  $V_P = -4 \text{ V}$

Optimum load impedance  $R_{OPT} = 12.5 \Omega \cdot \text{mm}$

Small-signal model:  $C_{GS} = 2.7 \text{ pF/mm}$  ;  $R_i = 1 \Omega \cdot \text{mm}$  ;  $g_m = 200 \text{ mS/mm}$  ;

$R_{DS} = 125 \Omega \cdot \text{mm}$  ;  $C_{DS} = 0.6 \text{ pF/mm}$

Selected device size @ 15 GHz =  $4 \times 75 \mu\text{m}$  GaAs HEMT



## First calculations:

a) Scaled parameters for the unit size of  $4 \times 75 \mu\text{m} = 0.3 \text{ mm}$

$$C_{GS1} = 2.7 \text{ pF} \times 0.3 = 0.81 \text{ pF}$$

$$C_{DS1} = 0.6 \text{ pF} \times 0.3 = 0.18 \text{ pF}$$

$$R_{i1} = \frac{1}{0.3} = 3.33 \Omega$$

$$R_{DS1} = \frac{125}{0.3} = 417 \Omega$$

$$R_{opt1} = \frac{12.5}{0.3} = 41.7 \Omega$$

$$R_{IN1} = \frac{R_{i1} C_{GS1}^2 \omega^2}{1} = \frac{3.33 \times (0.81 \times 10^{-12})^2 \times 2\pi \times 15 \times 10^9}{1} = 51.5 \Omega$$

b) Power gain for optimum Power matching  $G_P(R_{opt})$  @ 15 GHz

$$* G_{max}(10 \text{ GHz}) = 16 \text{ dB} = 10^{1.6} = 39.8 \rightarrow G_{max}(15 \text{ GHz}) = G_{max}(10 \text{ GHz}) \times \left(\frac{10}{15}\right)^2 = 39.8 \times \left(\frac{10}{15}\right)^2 = 17.7 = 12.5 \text{ dB}$$

$$\text{given } G_P(R_{opt}) = 4 \times \frac{R_{DS} R_{opt}}{(R_{DS} + R_{opt})^2} G_{max} \rightarrow G_P(R_{opt})_{15 \text{ GHz}} = 4 \times \frac{125 \times 12.5}{(125 + 12.5)^2} \times 17.7 = 5.85 = 7.7 \text{ dB}$$

c) Power density for maximum gain matching  $PD(R_{DS})$

$$PD(R_{DS}) = PD(R_{opt}) \times \frac{R_{opt}}{R_{DS}} = (1 \text{ W/mm}) \times \frac{12.5 \Omega \cdot \text{mm}}{125 \Omega \cdot \text{mm}} \Rightarrow PD(R_{DS}) = 0.1 \text{ W/mm}$$

## Power specifications $\rightarrow$ 2nd stage dimensions

STAGE B

2nd stage loaded by  $R_{opt} \Rightarrow PD(R_{opt}) = 1 \text{ W/mm}$

$$P_{OUT} > 1 \text{ W}$$

$$\text{Size}_B > \frac{1 \text{ W}}{1 \text{ W/mm}} = 1 \text{ mm}$$

$$m_B = 4$$

$$P_{OUTB} = (4 \times 0.3 \text{ mm}) \times 1 \text{ W/mm} = 1.2 \text{ W}$$

$$G_{PB} = G_P(R_{opt}) = 5.85 = 7.7 \text{ dB}$$

$$P_{INB} = P_{OUTA} = \frac{P_{OUTB}}{G_{PB}} = \frac{1.2 \text{ W}}{5.85} = 0.205 \text{ W}$$

Possible sizes  
 $N=1 \rightarrow 0.3 \text{ mm}$   
 $N=2 \rightarrow 0.6 \text{ mm}$   
 $N=4 \rightarrow 1.2 \text{ mm}$   
 $N=8 \rightarrow 2.4 \text{ mm}$   
 $N=16 \rightarrow 4.8 \text{ mm}$

STAGE A

1st stage loaded by  $R_{opt} \Rightarrow PD(R_{opt}) = 1 \text{ W/mm}$

$$P_{OUT} > 0.205 \text{ W}$$


$$\text{Size}_A > \frac{0.205 \text{ W}}{1 \text{ W/mm}} = 0.205 \text{ mm}$$

$$m_A = 1$$


$$P_{OUTA} = 0.205 \text{ W}$$

$$G_{PA} = G_P(R_{opt}) = 5.85 = 7.7 \text{ dB}$$
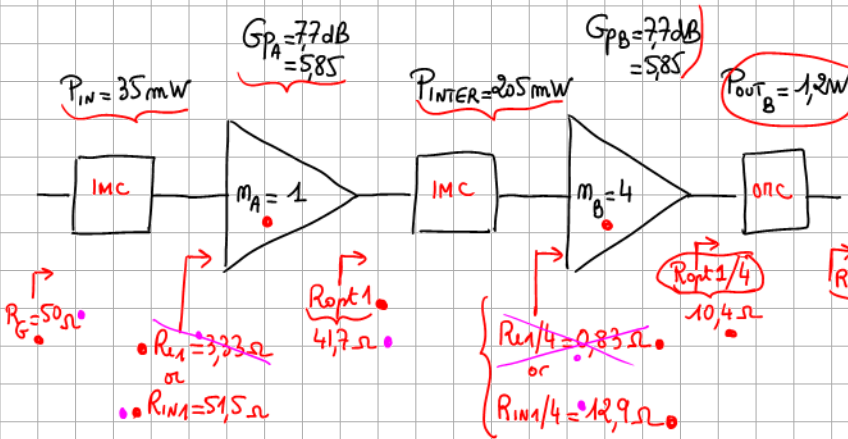
$$P_{INA} = \frac{P_{OUTA}}{G_{PA}} = \frac{0.205}{5.85} = 35 \text{ mW}$$



srA (0,3mm)

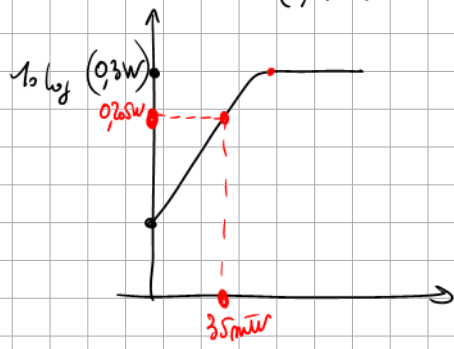

srB (1,2mm)

