

# **Semester S1 –Basics of active and non linear electronics**

## **RF Power amplifiers ( JM Nebus )**

### **TUTORIAL N° 2**

## I ] Transistor biasing conditions and aperture angles

The static characteristic of a Field effect transistor is plotted in figure 1

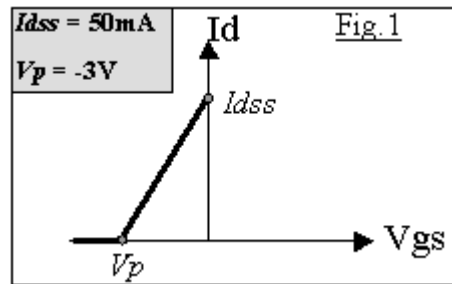


Figure 1

The simplified large signal equivalent model of the transistor is given in figure 2

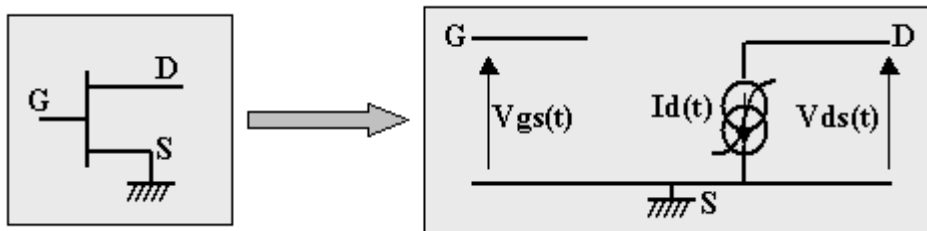


Figure 2

The transistor is connected to a sinusoidal voltage generator  $e(t)$ , DC voltage generators ( $V_{gso}$  and  $V_{dso}$ ) and a load impedance ( $Z_{ch}$ ) as represented in figure 3

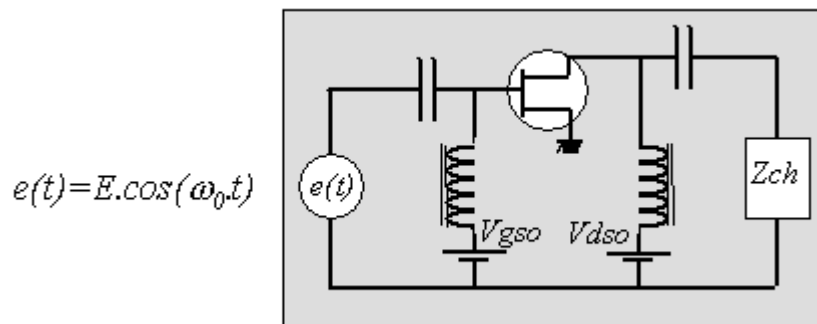


Figure 3

We will consider the study of four different cases respectively named  
P1 , P2 , P3 , P4

**P1:**  $V_{gso} = -1.5 \text{ V}$  and  $e(t) = 1.5 \cos(\omega_0 t)$

**P2:**  $V_{gso} = -2 \text{ V}$  and  $e(t) = 2 \cos(\omega_0 t)$

**P3:**  $V_{gso} = -3 \text{ V}$  and  $e(t) = 2 \cos(\omega_0 t)$

**P4:**  $V_{gso} = -4 \text{ V}$  and  $e(t) = 3 \cos(\omega_0 t)$


For each one of the four cases

- 1) Plot the time domain waveforms of  $V_{gs}(t)$  and  $I_d(t)$  on the graph given in Fig 1.
- 2) Calculate the aperture angle  $\varphi$  and the spectral components of the drain current  $I_d(t)$ :  
(  $I_{d0}$  is the DC component and  $I_{d1}$  is the fundamental frequency component )
- 3) If we choose  $V_{gso} = -2 \text{ V}$ , calculate the magnitude  $E$  of the input sinusoidal voltage in order to have an aperture angle equal to  $160^\circ$

On donne:

$$I_{d0} = \frac{I_p}{\pi} \cdot \frac{\sin(\varphi) - \varphi \cdot \cos(\varphi)}{1 - \cos(\varphi)} \quad \text{et} \quad I_{d1} = \frac{I_p}{\pi} \cdot \frac{\varphi - \sin(\varphi) \cdot \cos(\varphi)}{1 - \cos(\varphi)}$$

$I_p$  is the peak value of the current

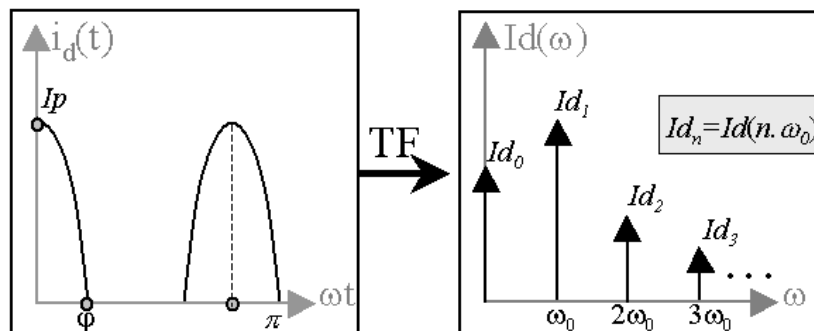

## II Drain source voltage $V_{ds}(t)$ and load line

The DC drain source voltage is fixed at  $V_{dso} = 6V$

The simplified  $I_d$  versus  $V_{ds}$  characteristic of the transistor is given in figure 4

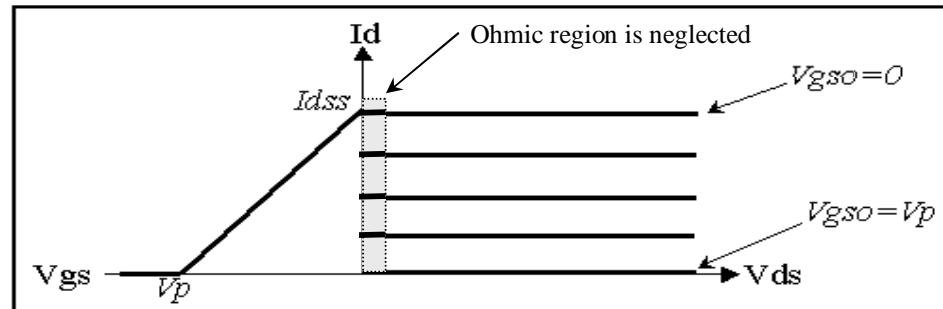


Figure 4

- 1) For the first case P1, we choose  $Z_{ch} = 240\Omega$ .  
Plot the shape of the drain source voltage  $V_{ds}(t)$   
Plot the shape of the dynamic load line
- 2) Same question than 1) for the second case P2 and for  $Z_{ch} = 200\Omega$ .
- 3) Same question for the third case P3 and for a load impedance  $Z_{ch}$  composed of a parallel resonant circuit as represented below in figure 5.

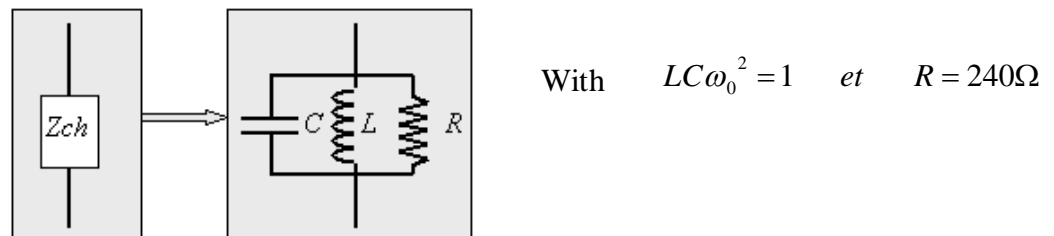


Figure 5

- 4) For the last case P4, we change the resistance of the parallel resonant circuit which is now  $R'$  as represented in Figure 6. Calculate the value of  $R'$  in order to get a maximum magnitude of  $V_{ds}(t)$ . Plot also the corresponding load line.

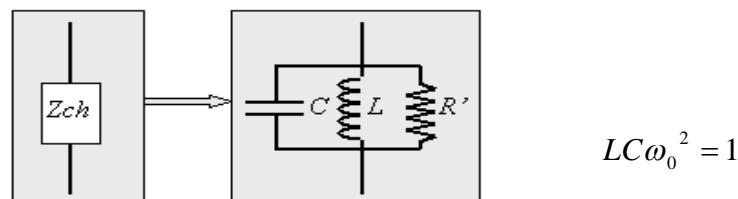


Figure 6