



**PRACTICAL WORK
PW5:
DESIGN OF A LINEAR AMPLIFIER AT 2GHZ
USINKEYSIGHT ADS**


- Student Help Manual for PW 3, 4 and 5

Copy to be left
on site




UNIVERSITÀ
DEGLI STUDI
DI BRESCIA



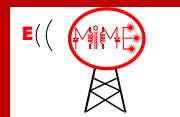


This booklet presents the architecture of the ADS project you will use.

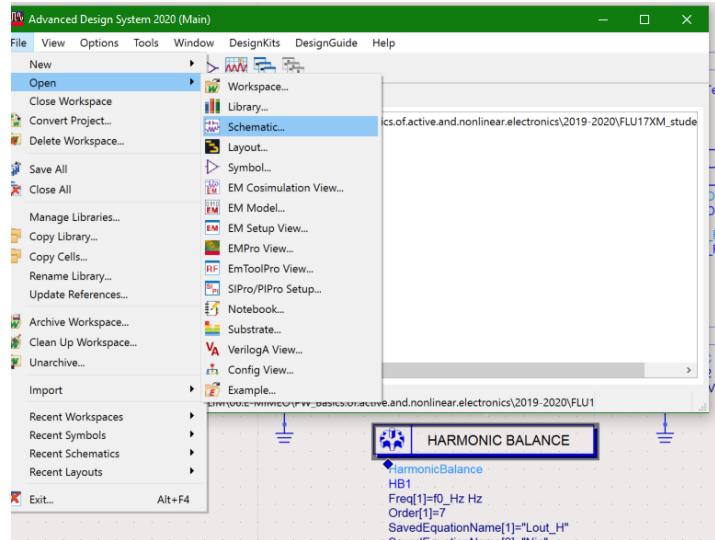After launching ADS, click on *file/open Schematic* to obtain the following list of schematics :




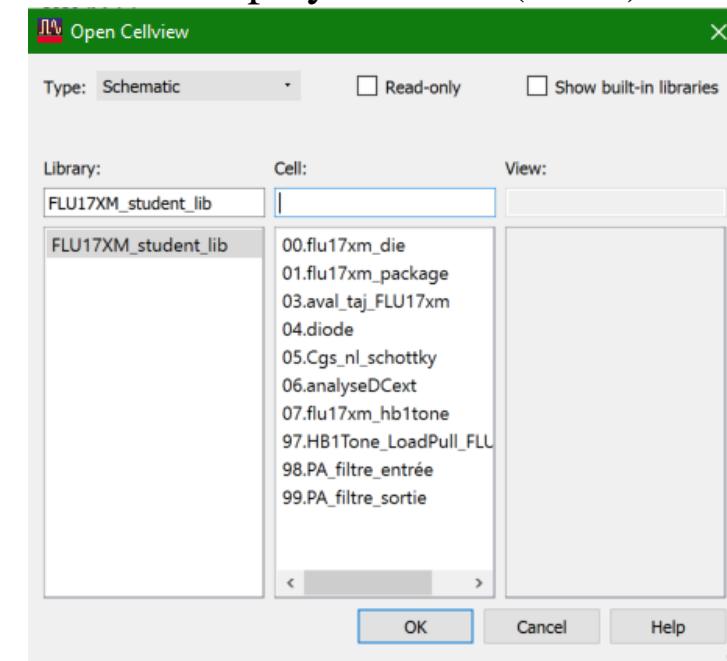Each schematic file (*.dsn) is detailed hereafter as well as the corresponding data display window (*.dds).







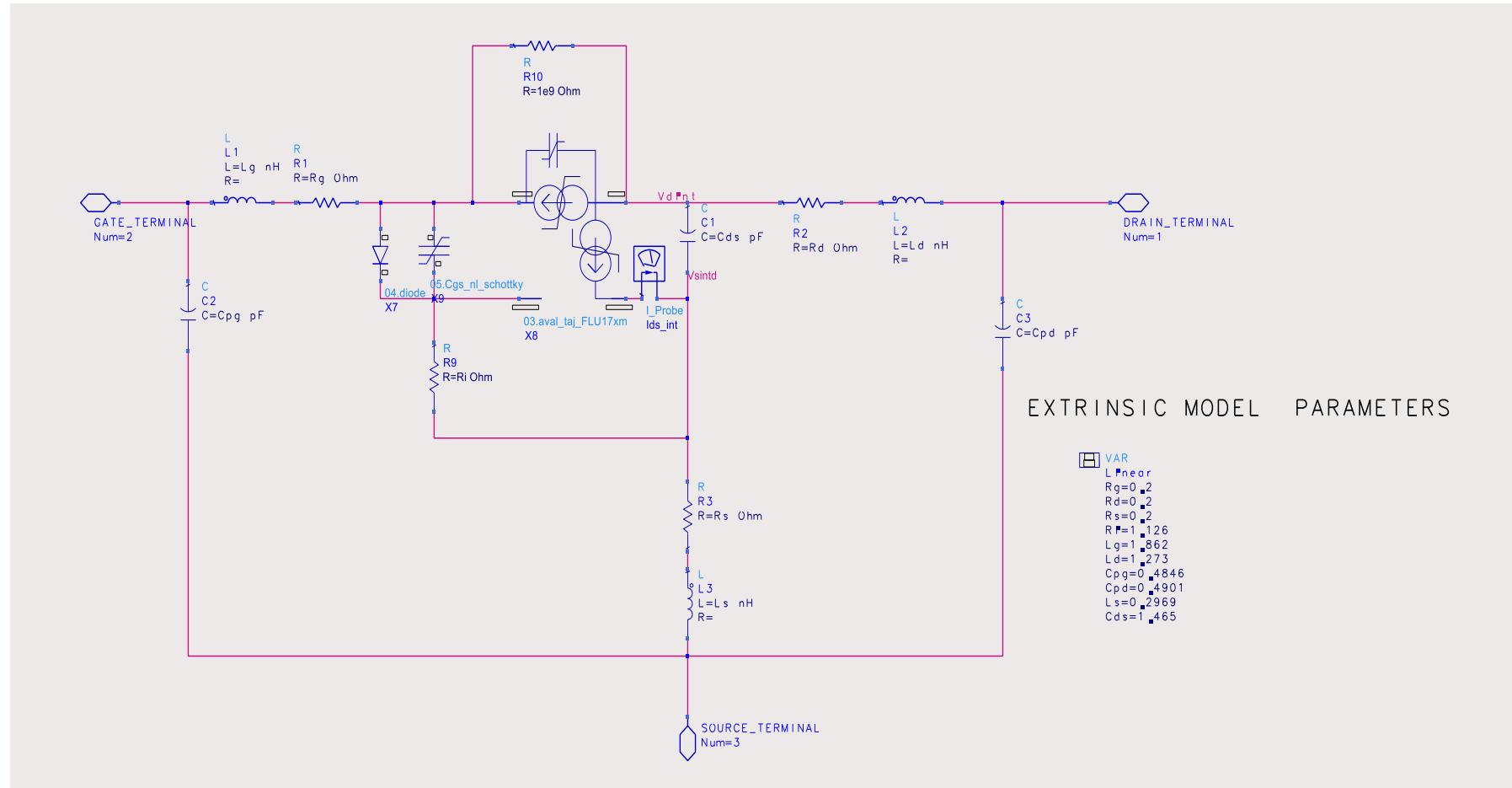
The *01.flu17xm_package.dsn* file defines the non-linear packaged model of the FET. The figure below represents the symbol associated to this model (and to this file). You can click on *Window/symbol* in the *Window* menu.



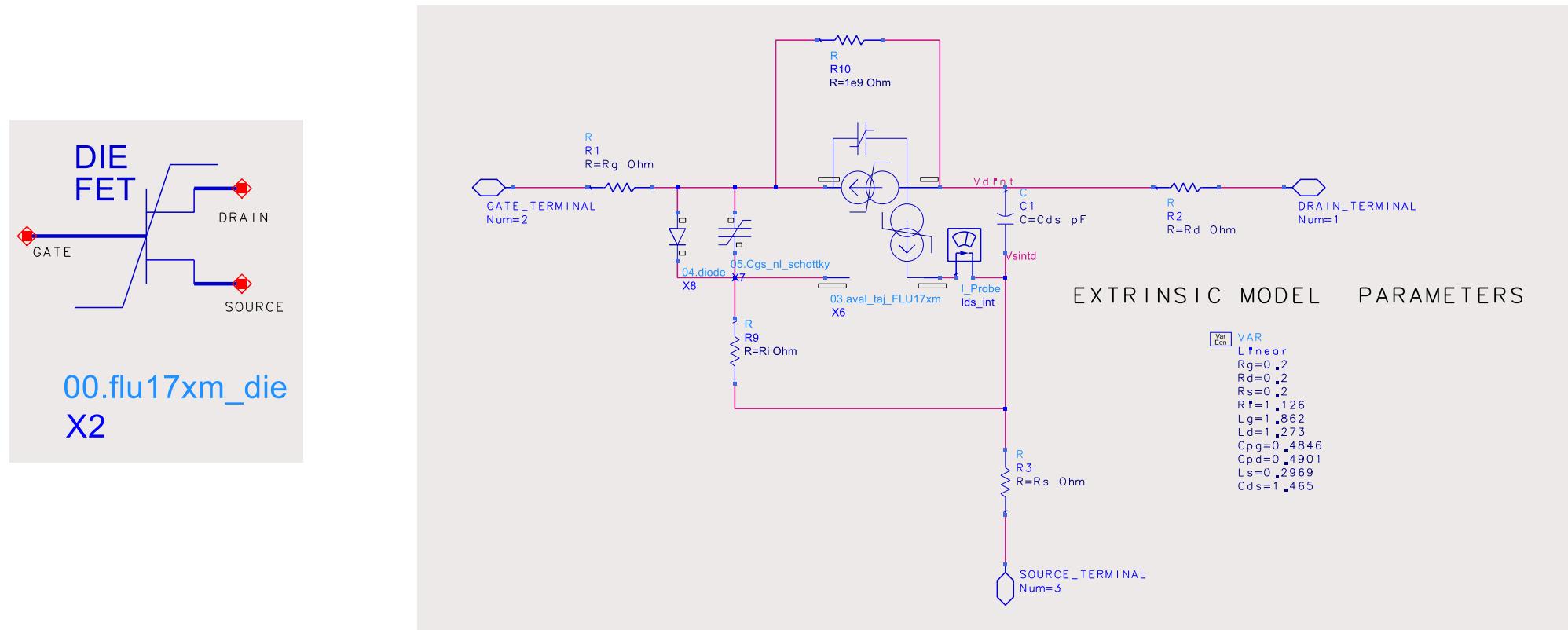
The *00.flu17xm_package.dsn* file defines the non-linear packaged model of the FET. The figure below represents the symbol associated to this model (and to this file). You can click on *Window/symbol* in the *Window* menu.



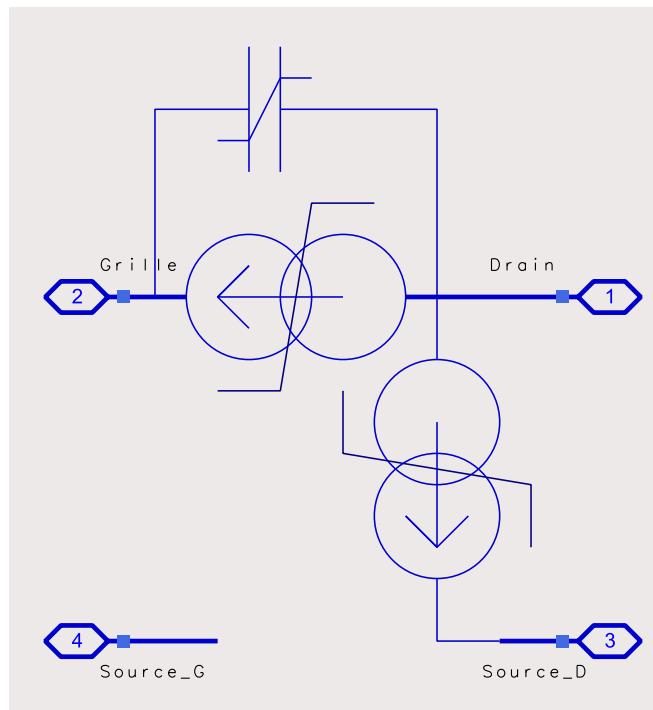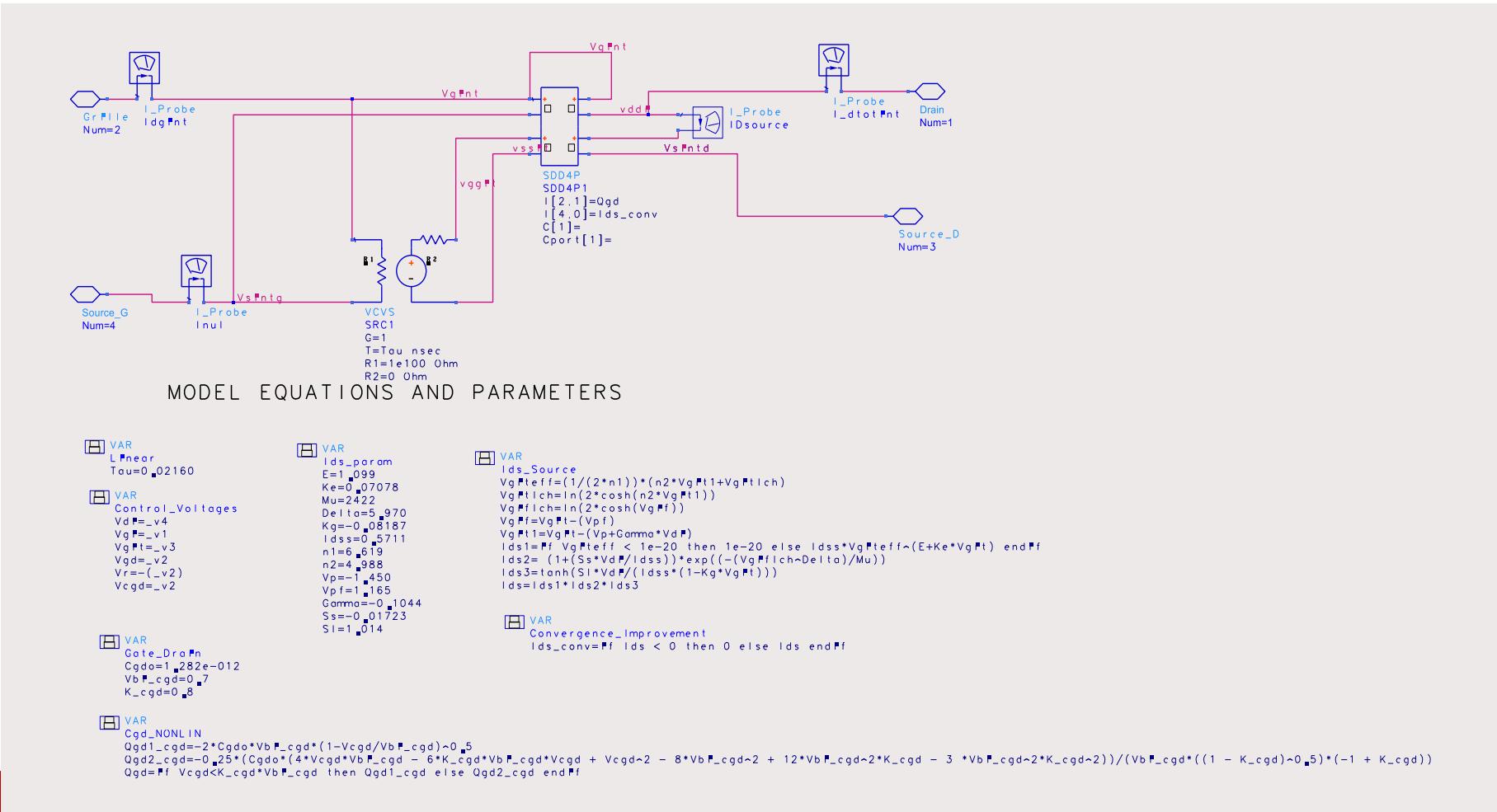The *aval_taj.dsn* file defines the non-linear intrinsic model of the FET. The figure below represents the symbol associated to this model (and to this file). You can click on *Window/symbol* in the *Window* menu.



Cgs Non linear EQUATIONS AND PARAMETERS

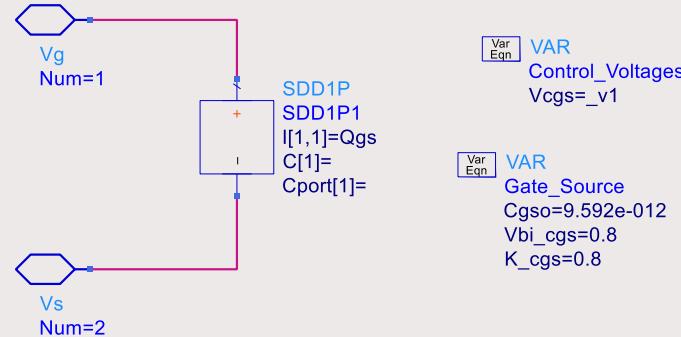


Var Eqn
VAR
Control_Voltages
Vcgs=_v1

Var Eqn
VAR
Gate_Source
Cgso=9.592e-012
Vbi_cgs=0.8
K_cgs=0.8


Var Eqn
VAR
Cgs_NONLIN
Qgs1_cgs=-2*Cgso*Vbi_cgs*(1-Vcgs/Vbi_cgs)^0.5
Qgs2_cgs=-0.25*(Cgso*(4*Vcgs*Vbi_cgs - 6*K_cgs*Vbi_cgs*Vcgs + Vcgs^2 - 8*Vbi_cgs^2 + 12*Vbi_cgs^2*K_cgs - 3 *Vbi_cgs^2*K_cgs^2))/(Vbi_cgs*((1 - K_cgs)^0.5*(-1 + K_cgs)))
Qgs;if Vcgs<K_cgs*Vbi_cgs then Qgs1_cgs else Qgs2_cgs endif

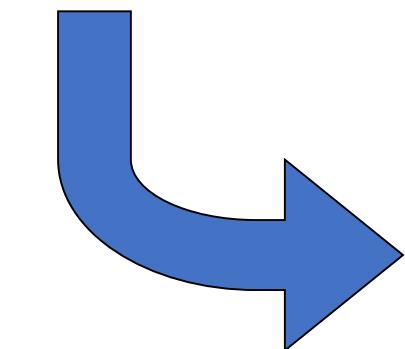The
Cgs_nl_schottky.dsn
file defines the non-
linear model of the
C_{GS} capacitance of the
FET.



Associated symbol



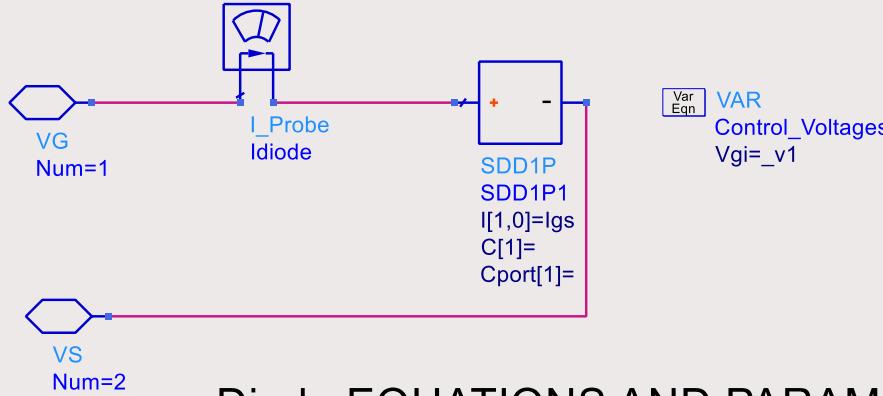


Diode EQUATIONS AND PARAMETERS

Var Eqn VAR
lgS_NONLIN
as_igs=Alphas_igs*Vgi
bs_igs=Alphas_igs*Vgi-Ms_igs
I1_igs=Ins_igs*(exp(Ms_igs)*(1+bs_igs+bs_igs^2/2)-1)
I2_igs;if as_igs<-20 then -Ins_igs else Ins_igs*(exp(as_igs)-1) endif
Igs;if bs_igs>0 then I1_igs else I2_igs endif

Var Eqn VAR
Gate_Source
Ins_igs=4.822e-011
Ms_igs=40
Alphas_igs=29.1
Cgso=9.592e-012
Vbi_cgs=0.8
K_cgs=0.8

Associated symbol

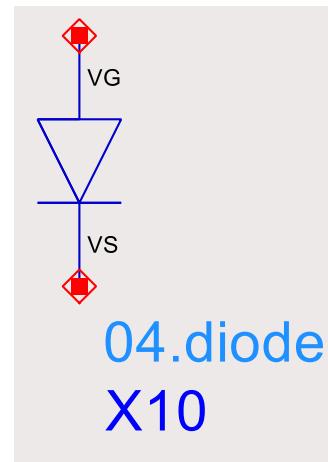

The *Diode.dsn* file defines the non-linear model of the input Diode of the FET.




I/V Static Characteristics




UNIVERSITÀ
DEGLI STUDI
DI BRESCIA




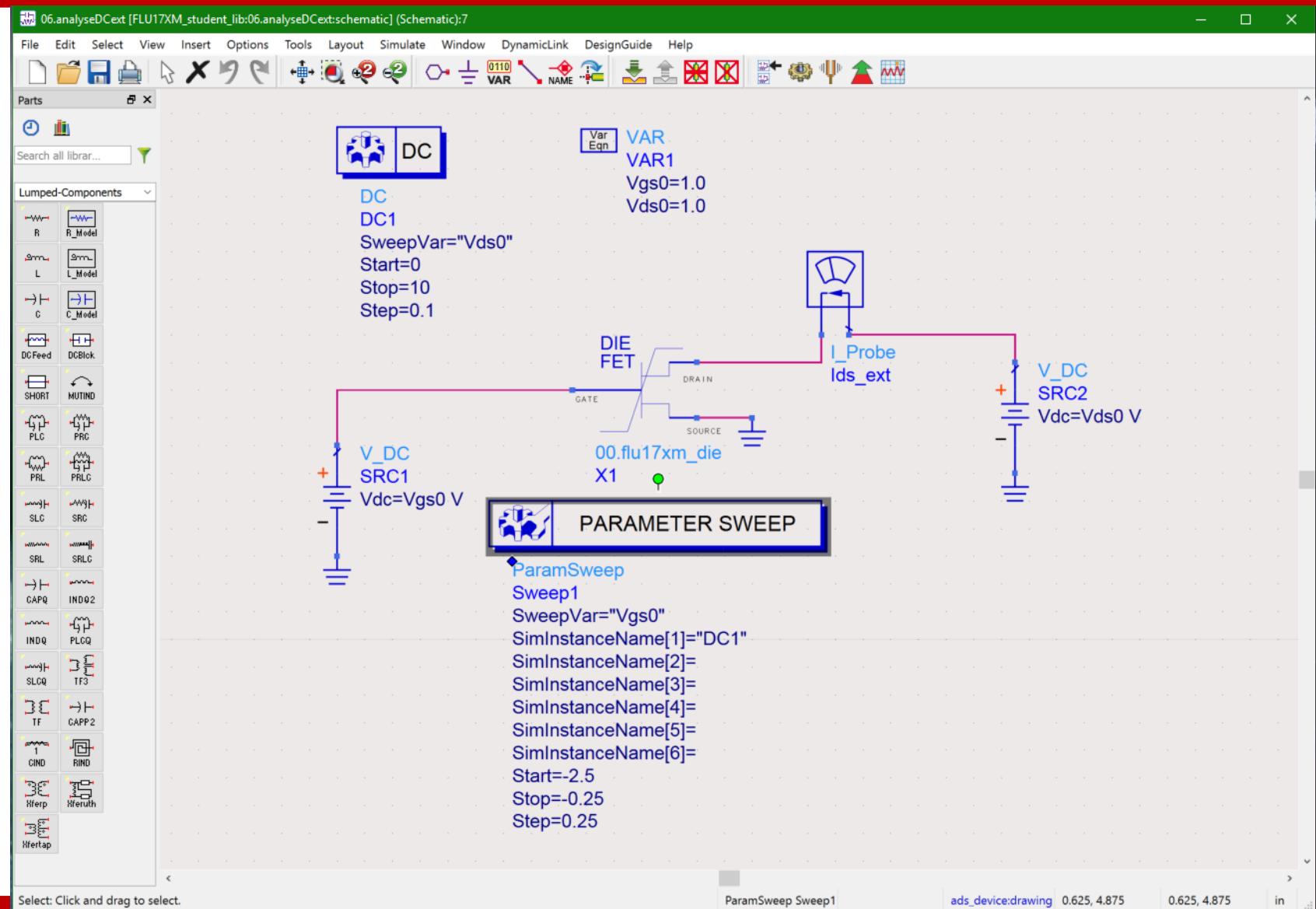Schematic to plot the extrinsic I/V curves of the Die transistor




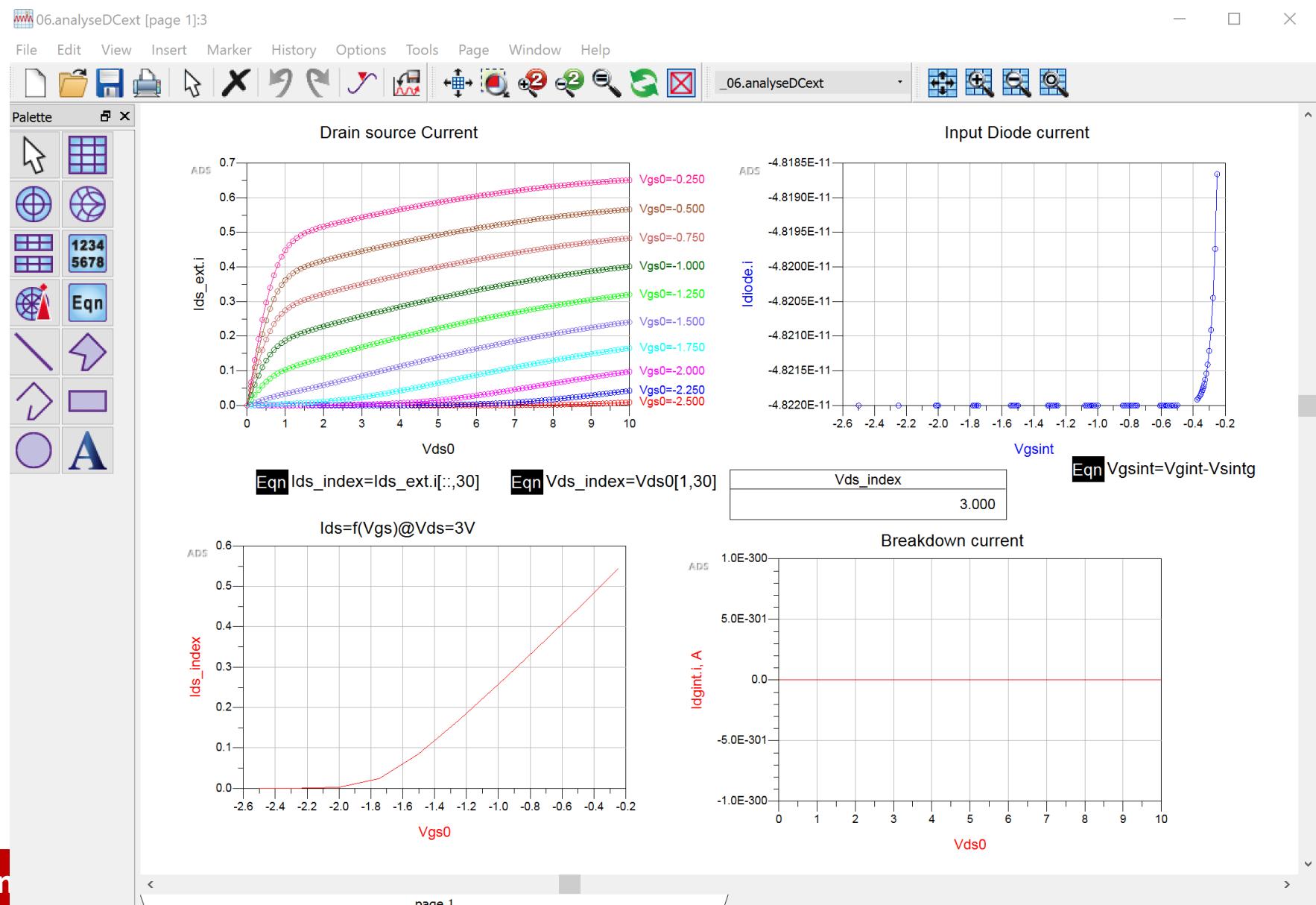

Drain Source Current

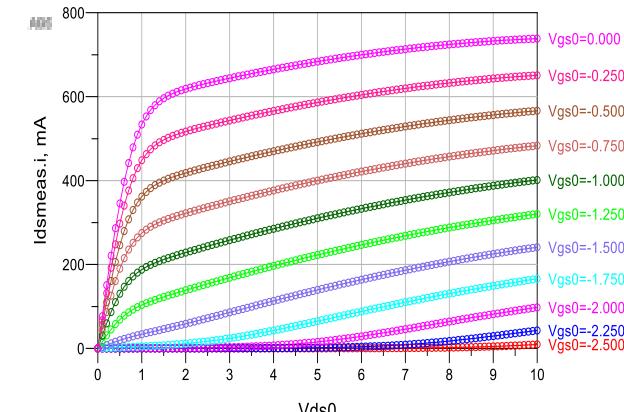

Input Diode Current

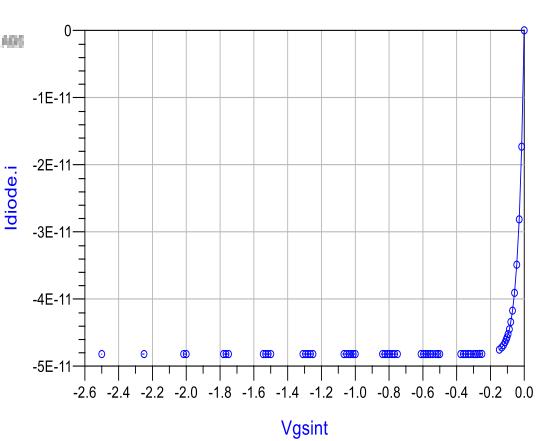


Eqn lds_index=ldsmeas.i[::,30] Eqn Vds_index=Vds0[1,30]


Vds_index
3.000

Eqn Vgsint=Vgint-Vsintg

Ids=f(Vgs) @ Vds=3V

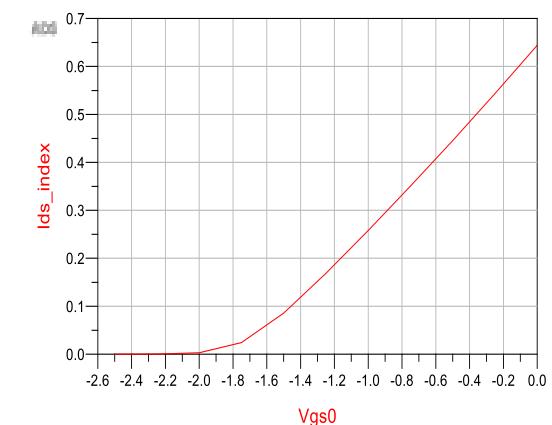


Breakdown Current

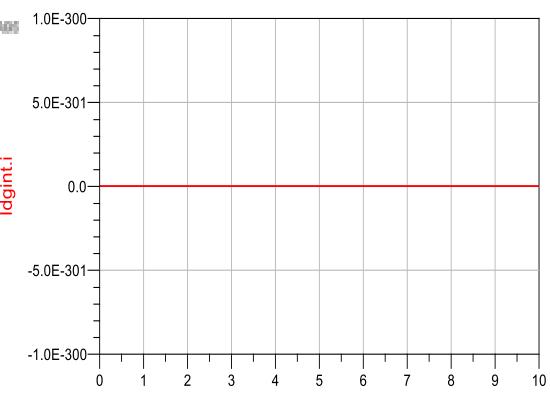


Vds0	ldsmeas.i										
	...0=-2.500	...0=-2.250	...0=-2.000	...0=-1.750	...0=-1.500	...0=-1.250	...0=-1.000	...0=-0.750	...0=-0.500	...0=-0.250	...0=0.000
0.000	2.500 nA	2.250 nA	2.000 nA	1.750 nA	1.500 nA	1.250 nA	1000 pA	750.0 pA	500.0 pA	250.0 pA	0.0000 A
0.100	312.6 nA	3.492 uA	38.72 uA	425.2 uA	3.831 mA	15.57 mA	30.48 mA	44.15 mA	56.21 mA	66.90 mA	76.51 mA
0.200	651.9 nA	7.338 uA	81.70 uA	897.4 uA	7.905 mA	30.89 mA	59.73 mA	86.46 mA	110.3 mA	131.5 mA	150.7 mA
0.300	997.2 nA	11.29 uA	126.3 uA	1.389 mA	11.97 mA	45.15 mA	86.57 mA	125.5 mA	160.6 mA	192.3 mA	221.0 mA
0.400	1.333 uA	15.19 uA	170.7 uA	1.878 mA	15.84 mA	57.87 mA	110.2 mA	160.2 mA	206.1 mA	247.9 mA	286.2 mA
0.500	1.654 uA	18.95 uA	213.9 uA	2.356 mA	19.42 mA	68.85 mA	130.3 mA	190.1 mA	245.8 mA	297.4 mA	345.2 mA
0.600	1.962 uA	22.58 uA	256.1 uA	2.820 mA	22.71 mA	78.16 mA	147.0 mA	215.0 mA	279.5 mA	340.2 mA	397.1 mA
0.700	2.262 uA	26.15 uA	297.7 uA	3.276 mA	25.74 mA	85.99 mA	160.5 mA	235.3 mA	307.4 mA	376.2 mA	441.6 mA
0.800	2.562 uA	29.73 uA	339.5 uA	3.730 mA	28.55 mA	92.62 mA	171.5 mA	251.6 mA	329.9 mA	405.7 mA	478.8 mA
0.900	2.869 uA	33.41 uA	382.5 uA	4.191 mA	31.20 mA	98.30 mA	180.4 mA	264.5 mA	347.8 mA	429.4 mA	509.2 mA
1.000	3.189 uA	37.24 uA	427.5 uA	4.668 mA	33.75 mA	103.3 mA	187.7 mA	274.8 mA	361.9 mA	448.2 mA	533.6 mA
1.100	3.528 uA	41.32 uA	475.2 uA	5.166 mA	36.24 mA	107.7 mA	193.9 mA	283.1 mA	373.0 mA	462.9 mA	552.8 mA
1.200	3.892 uA	45.69 uA	526.4 uA	5.693 mA	38.69 mA	111.8 mA	199.1 mA	289.9 mA	381.8 mA	474.5 mA	567.8 mA
1.300	4.285 uA	50.41 uA	581.7 uA	6.253 mA	41.14 mA	115.5 mA	203.7 mA	295.6 mA	389.0 mA	483.6 mA	579.5 mA
1.400	4.712 uA	55.55 uA	641.8 uA	6.852 mA	43.59 mA	119.1 mA	207.9 mA	300.4 mA	394.9 mA	491.0 mA	588.8 mA
1.500	5.177 uA	61.17 uA	707.4 uA	7.494 mA	46.05 mA	122.6 mA	211.7 mA	304.8 mA	399.9 mA	497.0 mA	596.2 mA
1.600	5.686 uA	67.30 uA	779.1 uA	8.182 mA	48.54 mA	125.9 mA	215.3 mA	308.7 mA	404.3 mA	502.0 mA	602.2 mA
1.700	6.242 uA	74.03 uA	857.6 uA	8.920 mA	51.05 mA	129.1 mA	218.8 mA	312.3 mA	408.1 mA	506.3 mA	607.2 mA
1.800	6.852 uA	81.41 uA	943.6 uA	9.710 mA	53.59 mA	132.3 mA	222.1 mA	315.7 mA	411.7 mA	510.1 mA	611.4 mA
1.900	7.519 uA	89.51 uA	1.038 mA	10.56 mA	56.17 mA	135.5 mA	225.3 mA	318.9 mA	415.0 mA	513.6 mA	615.1 mA
2.000	8.252 uA	98.40 uA	1.141 uA	11.46 mA	58.76 mA	138.6 mA	228.5 mA	322.0 mA	418.1 mA	516.8 mA	618.5 mA
2.100	9.055 uA	108.2 uA	1.255 uA	12.43 mA	61.39 mA	141.7 mA	231.6 mA	325.1 mA	421.1 mA	519.8 mA	621.5 mA
2.200	9.935 uA	118.9 uA	1.379 mA	13.46 mA	64.04 mA	144.8 mA	234.6 mA	328.1 mA	424.0 mA	522.6 mA	624.4 mA
2.300	10.90 uA	130.7 uA	1.515 uA	14.55 mA	66.71 mA	147.8 mA	237.6 mA	331.0 mA	426.9 mA	525.4 mA	627.1 mA
2.400	11.96 uA	143.6 uA	1.664 uA	15.71 mA	69.40 mA	150.8 mA	240.6 mA	333.9 mA	429.7 mA	528.1 mA	629.7 mA
2.500	13.12 uA	157.8 uA	1.827 mA	16.93 mA	72.10 mA	153.8 mA	243.6 mA	336.7 mA	432.4 mA	530.7 mA	632.2 mA
2.600	14.40 uA	173.4 uA	2.006 mA	18.22 mA	74.82 mA	156.8 mA	246.5 mA	339.5 mA	435.1 mA	533.2 mA	634.6 mA
2.700	15.80 uA	190.6 uA	2.201 mA	19.58 mA	77.55 mA	159.8 mA	249.4 mA	342.3 mA	437.7 mA	535.7 mA	637.0 mA
2.800	17.33 uA	209.4 uA	2.415 mA	21.00 mA	80.29 mA	162.7 mA	252.3 mA	345.1 mA	440.3 mA	538.2 mA	639.3 mA
2.900	19.01 uA	230.1 uA	2.648 mA	22.49 mA	83.03 mA	165.7 mA	255.1 mA	347.8 mA	442.9 mA	540.7 mA	641.6 mA
3.000	20.86 uA	252.8 uA	2.902 mA	24.04 mA	85.78 mA	168.6 mA	258.0 mA	350.5 mA	445.5 mA	543.1 mA	643.9 mA
3.100	22.89 uA	277.8 uA	3.179 uA	25.66 mA	88.53 mA	171.5 mA	260.8 mA	353.2 mA	448.0 mA	545.5 mA	646.1 mA
3.200	25.11 uA	305.2 uA	3.481 mA	27.34 mA	91.29 mA	174.3 mA	263.6 mA	355.9 mA	450.5 mA	547.8 mA	648.3 mA
3.300	27.54 uA	335.2 uA	3.810 mA	29.08 mA	94.04 mA	177.2 mA	266.3 mA	358.5 mA	453.0 mA	550.1 mA	650.4 mA
3.400	30.22 uA	368.2 uA	4.166 mA	30.88 mA	96.78 mA	180.0 mA	269.1 mA	361.1 mA	455.5 mA	552.5 mA	652.6 mA
3.500	33.15 uA	404.4 uA	4.554 mA	32.73 mA	99.53 mA	182.9 mA	271.8 mA	363.7 mA	457.9 mA	554.7 mA	654.7 mA
3.600	36.36 uA	444.2 uA	4.973 mA	34.64 mA	102.3 mA	185.7 mA	274.5 mA	366.3 mA	460.4 mA	557.0 mA	656.8 mA
3.700	39.89 uA	487.8 uA	5.427 mA	36.59 mA	105.0 mA	188.4 mA	277.2 mA	368.8 mA	462.8 mA	559.2 mA	658.9 mA
3.800	43.76 uA	535.6 uA	5.918 mA	38.59 mA	107.7 mA	191.2 mA	279.8 mA	371.4 mA	465.1 mA	561.4 mA	660.9 mA
3.900	48.00 uA	588.1 uA	6.448 mA	40.63 mA	110.4 mA	193.9 mA	282.5 mA	373.9 mA	467.5 mA	563.6 mA	662.9 mA
4.000	52.65 uA	645.6 uA	7.018 mA	42.71 mA	113.1 mA	196.6 mA	285.1 mA	376.3 mA	469.8 mA	565.8 mA	664.9 mA
4.100	57.75 uA	708.6 uA	7.631 mA	44.82 mA	115.8 mA	199.3 mA	287.7 mA	378.8 mA	472.1 mA	567.9 mA	666.9 mA
4.200	63.35 uA	777.7 uA	8.288 mA	46.97 mA	118.5 mA	202.0 mA	290.3 mA	381.2 mA	474.4 mA	570.0 mA	668.8 mA
4.300	69.48 uA	853.4 uA	8.992 mA	49.15 mA	121.1 mA	204.7 mA	292.8 mA	383.7 mA	476.7 mA	572.1 mA	670.7 mA
4.400	76.21 uA	936.3 uA	9.744 mA	51.35 mA	123.8 mA	207.3 mA	295.4 mA	386.0 mA	478.9 mA	574.2 mA	672.6 mA
4.500	83.58 uA	1.027 mA	10.55 mA	53.58 mA	126.4 mA	209.9 mA	297.9 mA	388.4 mA	481.1 mA	576.2 mA	674.5 mA
4.600	91.67 uA	1.126 mA	11.40 mA	55.82 mA	129.0 mA	212.5 mA	300.4 mA	390.8 mA	483.3 mA	578.3 mA	676.3 mA

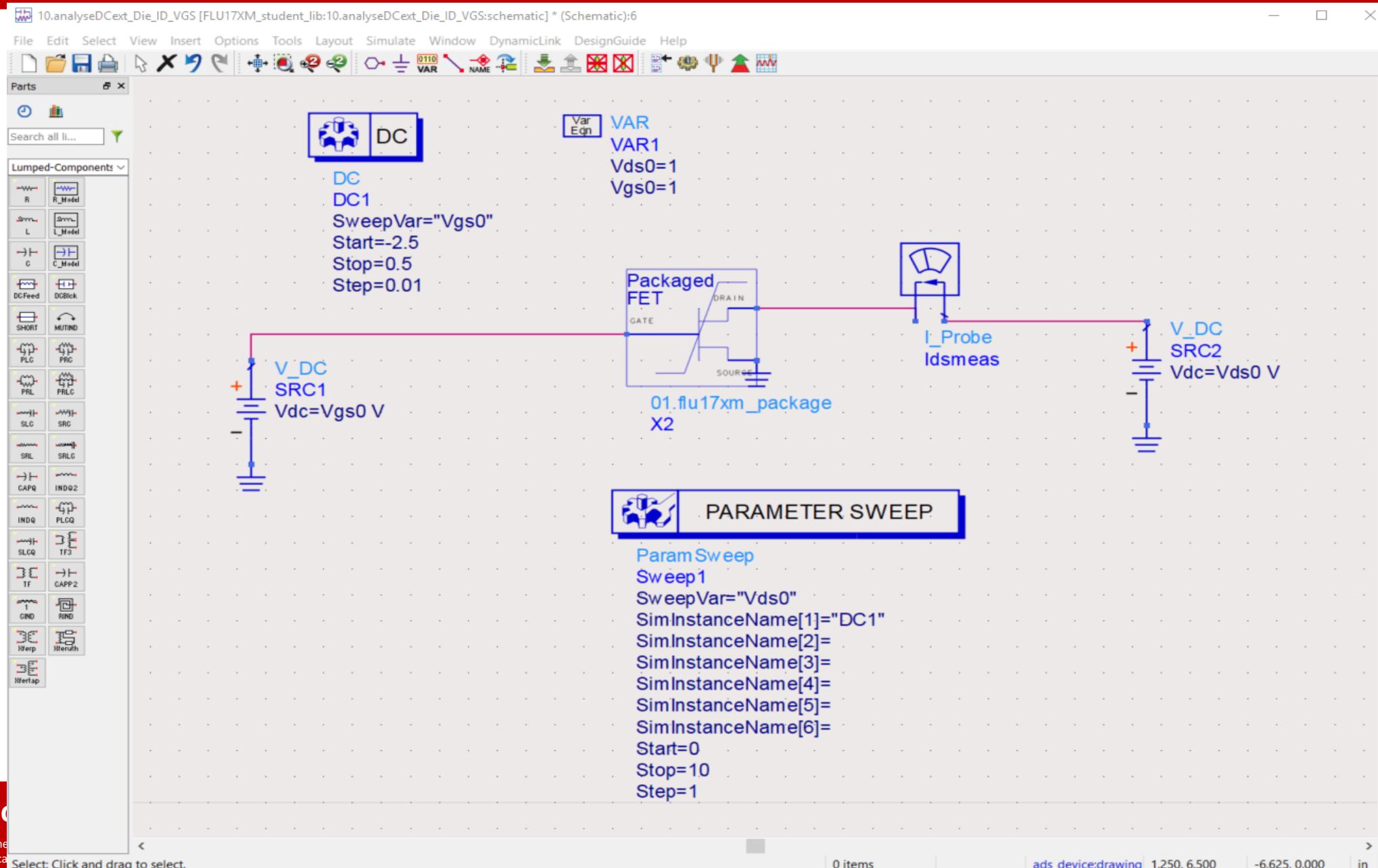Schematic to plot the
extrinsic I/V curves of the
Packaged transistor




Drain Source Current

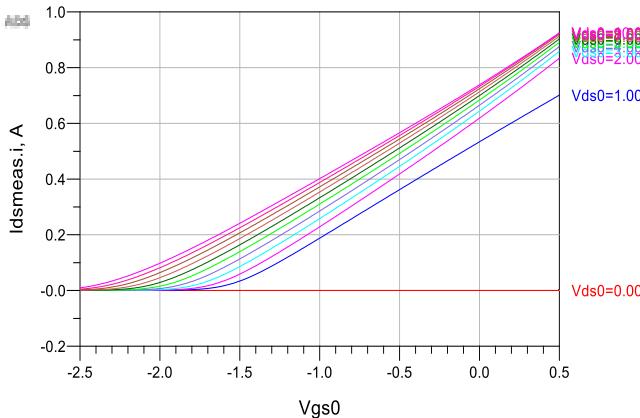

Eqn $Ids_index = Idsmeas.i[:, 150]$ **Eqn** $Vgs_index = Vgs0[1, 150]$


Vgs_index
-1.000


Ids=f(Vds) @ Vgs=-1V

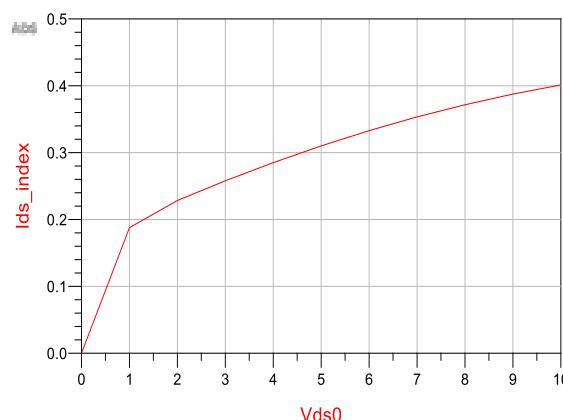

Vgs0	Idsmeas.i										
	$Vds0=0.000$	$Vds0=1.000$	$Vds0=2.000$	$Vds0=3.000$	$Vds0=4.000$	$Vds0=5.000$	$Vds0=6.000$	$Vds0=7.000$	$Vds0=8.000$	$Vds0=9.000$	$Vds0=10.000$
-2.500	2.500 nA	3.189 uA	8.252 uA	20.86 uA	52.65 uA	132.6 uA	332.5 uA	825.6 uA	2.002 mA	4.593 mA	9.464 mA
-2.490	2.490 nA	3.520 uA	9.118 uA	23.07 uA	58.26 uA	146.8 uA	368.2 uA	913.7 uA	2.209 mA	5.034 mA	10.24 mA
-2.480	2.480 nA	3.886 uA	10.07 uA	25.50 uA	64.46 uA	162.5 uA	407.7 uA	1.011 mA	2.437 mA	5.510 mA	11.06 mA
-2.470	2.470 nA	4.289 uA	11.13 uA	28.20 uA	71.31 uA	179.9 uA	451.3 uA	1.118 mA	2.686 mA	6.024 mA	11.93 mA
-2.460	2.460 nA	4.734 uA	12.29 uA	31.17 uA	78.89 uA	199.1 uA	499.5 uA	1.236 mA	2.959 mA	6.578 mA	12.85 mA
-2.450	2.450 nA	5.225 uA	13.58 uA	34.46 uA	87.26 uA	220.3 uA	552.8 uA	1.366 mA	3.257 mA	7.174 mA	13.82 mA
-2.440	2.440 nA	5.767 uA	15.00 uA	38.09 uA	96.52 uA	243.8 uA	611.7 uA	1.510 mA	3.582 mA	7.813 mA	14.83 mA
-2.430	2.430 nA	6.364 uA	16.57 uA	42.10 uA	106.8 uA	269.8 uA	676.7 uA	1.667 mA	3.936 mA	8.497 mA	15.89 mA
-2.420	2.420 nA	7.023 uA	18.30 uA	46.53 uA	118.1 uA	298.5 uA	748.4 uA	1.841 mA	4.322 mA	9.227 mA	17.00 mA
-2.410	2.410 nA	7.750 uA	20.21 uA	51.43 uA	130.6 uA	330.2 uA	827.6 uA	2.031 mA	4.741 mA	10.01 mA	18.15 mA
-2.400	2.400 nA	8.551 uA	22.32 uA	56.83 uA	144.4 uA	365.2 uA	915.0 uA	2.240 mA	5.195 mA	10.83 mA	19.36 mA
-2.390	2.390 nA	9.435 uA	24.65 uA	62.80 uA	159.6 uA	403.9 uA	1.011 mA	2.469 mA	5.687 mA	11.71 mA	20.61 mA
-2.380	2.380 nA	10.41 uA	27.22 uA	69.40 uA	176.5 uA	446.6 uA	1.118 mA	2.720 mA	6.219 mA	12.64 mA	21.91 mA
-2.370	2.370 nA	11.48 uA	30.05 uA	76.68 uA	195.1 uA	493.8 uA	1.235 mA	2.995 mA	6.792 mA	13.62 mA	23.25 mA
-2.360	2.360 nA	12.67 uA	33.18 uA	84.72 uA	215.7 uA	545.9 uA	1.363 mA	3.296 mA	7.410 mA	14.65 mA	24.64 mA
-2.350	2.350 nA	13.98 uA	36.64 uA	93.60 uA	238.4 uA	603.4 uA	1.505 mA	3.624 mA	8.073 mA	15.74 mA	26.07 mA
-2.340	2.340 nA	15.42 uA	40.45 uA	103.4 uA	263.5 uA	666.8 uA	1.661 mA	3.981 mA	8.784 mA	16.88 mA	27.55 mA
-2.330	2.330 nA	17.01 uA	44.65 uA	114.2 uA	291.2 uA	736.8 uA	1.833 mA	4.371 mA	9.544 mA	18.07 mA	29.07 mA
-2.320	2.320 nA	18.76 uA	49.29 uA	126.2 uA	321.7 uA	814.0 uA	2.021 mA	4.794 mA	10.36 mA	19.31 mA	30.63 mA
-2.310	2.310 nA	20.69 uA	54.42 uA	139.4 uA	355.5 uA	899.2 uA	2.228 mA	5.254 mA	11.22 mA	20.61 mA	32.23 mA
-2.300	2.300 nA	22.82 uA	60.07 uA	153.9 uA	392.8 uA	993.0 uA	2.454 mA	5.752 mA	12.14 mA	21.96 mA	33.87 mA
-2.290	2.290 nA	25.17 uA	66.30 uA	170.0 uA	433.9 uA	1.096 mA	2.703 mA	6.292 mA	13.11 mA	23.36 mA	35.55 mA
-2.280	2.280 nA	27.76 uA	73.19 uA	187.8 uA	479.3 uA	1.210 mA	2.975 mA	6.874 mA	14.14 mA	24.80 mA	37.27 mA
-2.270	2.270 nA	30.62 uA	80.78 uA	207.3 uA	529.4 uA	1.336 mA	3.272 mA	7.502 mA	15.23 mA	26.30 mA	39.03 mA
-2.260	2.260 nA	33.77 uA	89.15 uA	229.0 uA	584.6 uA	1.473 mA	3.597 mA	8.177 mA	16.37 mA	27.85 mA	40.82 mA
-2.250	2.250 nA	37.24 uA	98.40 uA	252.8 uA	645.6 uA	1.625 mA	3.952 mA	8.903 mA	17.57 mA	29.44 mA	42.65 mA
-2.240	2.240 nA	41.07 uA	108.6 uA	279.1 uA	712.8 uA	1.792 mA	4.338 mA	9.680 mA	18.83 mA	31.08 mA	44.51 mA
-2.230	2.230 nA	45.29 uA	119.8 uA	308.2 uA	786.8 uA	1.975 mA	4.759 mA	10.51 mA	20.14 mA	32.77 mA	46.41 mA
-2.220	2.220 nA	49.95 uA	132.2 uA	340.2 uA	868.5 uA	2.176 mA	5.216 mA	11.40 mA	21.52 mA	34.50 mA	48.34 mA
-2.210	2.210 nA	55.08 uA	145.9 uA	375.6 uA	958.4 uA	2.397 mA	5.711 mA	12.34 mA	22.94 mA	36.28 mA	50.30 mA
-2.200	2.200 nA	60.73 uA	161.0 uA	414.6 uA	1.057 mA	2.638 mA	6.249 mA	13.34 mA	24.43 mA	38.09 mA	52.30 mA
-2.190	2.190 nA	66.97 uA	177.7 uA	457.6 uA	1.167 mA	2.903 mA	6.830 mA	14.40 mA	25.97 mA	39.95 mA	54.32 mA
-2.180	2.180 nA	73.85 uA	196.1 uA	505.0 uA	1.287 mA	3.193 mA	7.457 mA	15.53 mA	27.56 mA	41.84 mA	56.37 mA
-2.170	2.170 nA	81.42 uA	216.3 uA	557.3 uA	1.419 mA	3.509 mA	8.133 mA	16.71 mA	29.21 mA	43.78 mA	58.46 mA
-2.160	2.160 nA	89.78 uA	238.7 uA	615.0 uA	1.564 mA	3.855 mA	8.861 mA	17.95 mA	30.90 mA	45.75 mA	60.57 mA
-2.150	2.150 nA	98.99 uA	263.3 uA	678.5 uA	1.724 mA	4.232 mA	9.641 mA	19.26 mA	32.65 mA	47.76 mA	62.71 mA
-2.140	2.140 nA	109.1 uA	290.5 uA	748.5 uA	1.899 mA	4.643 mA	10.48 mA	20.63 mA	34.45 mA	49.80 mA	64.88 mA
-2.130	2.130 nA	120.3 uA	320.5 uA	825.6 uA	2.091 mA	5.090 mA	11.37 mA	22.06 mA	36.30 mA	51.88 mA	67.08 mA
-2.120	2.120 nA	132.7 uA	353.5 uA	910.6 uA	2.303 mA	5.576 mA	12.32 mA	23.55 mA	38.19 mA	53.99 mA	69.30 mA
-2.110	2.110 nA	146.3 uA	390.0 uA	1.004 mA	2.534 mA	6.102 mA	13.34 mA	25.10 mA	40.13 mA	56.14 mA	71.55 mA
-2.100	2.100 nA	161.3 uA	430.1 uA	1.107 mA	2.788 mA	6.673 mA	14.42 mA	26.71 mA	42.11 mA	58.31 mA	73.82 mA
-2.090	2.090 nA	177.8 uA	474.4 uA	1.221 mA	3.066 mA	7.290 mA	15.56 mA	28.38 mA	44.13 mA	60.52 mA	76.12 mA
-2.080	2.080 nA	196.0 uA	523.2 uA	1.345 mA	3.370 mA	7.956 mA	16.76 mA	30.11 mA	46.19 mA	62.75 mA	78.44 mA

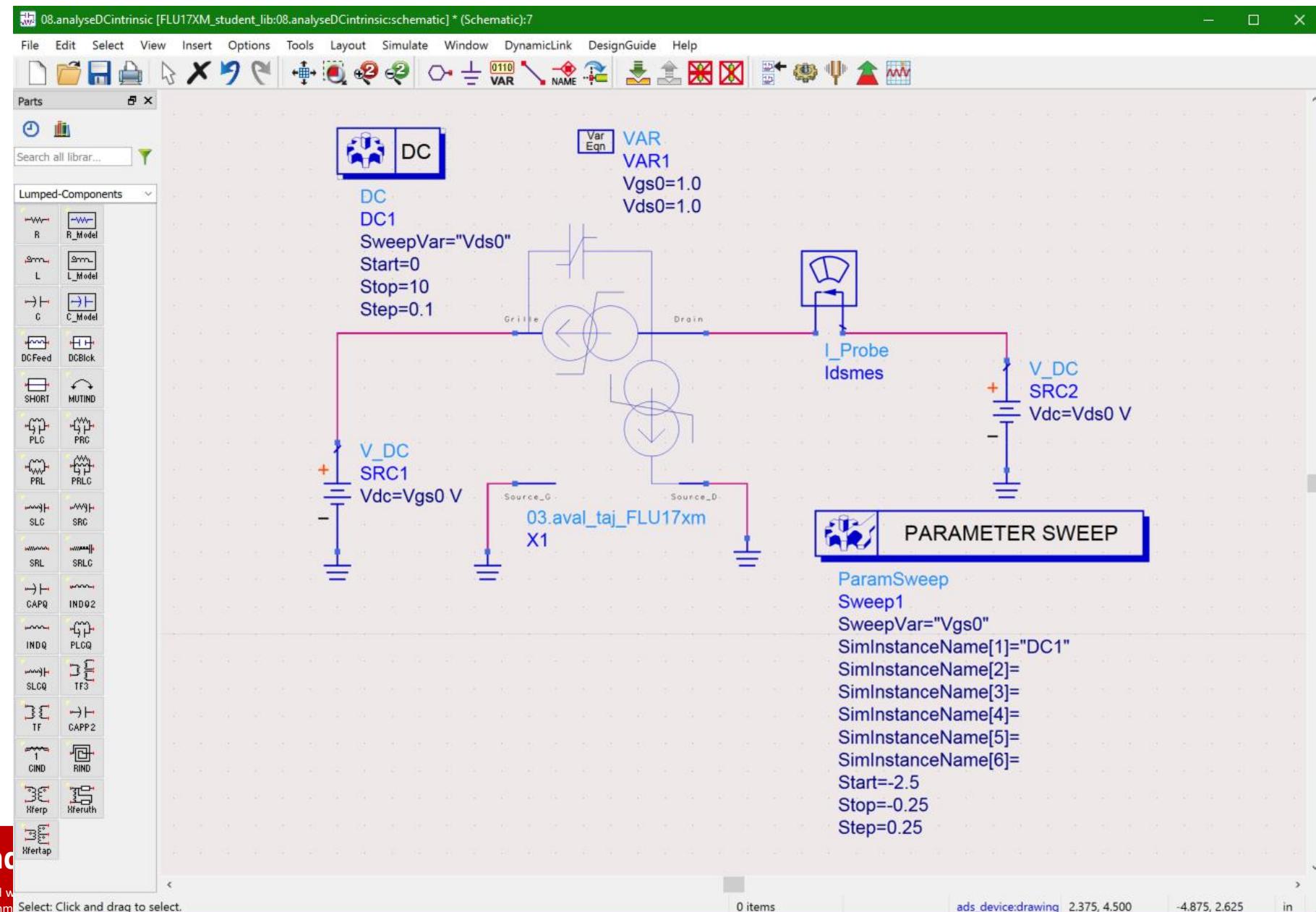Schematic to plot the
intrinsic I/V curves of the
Die transistor



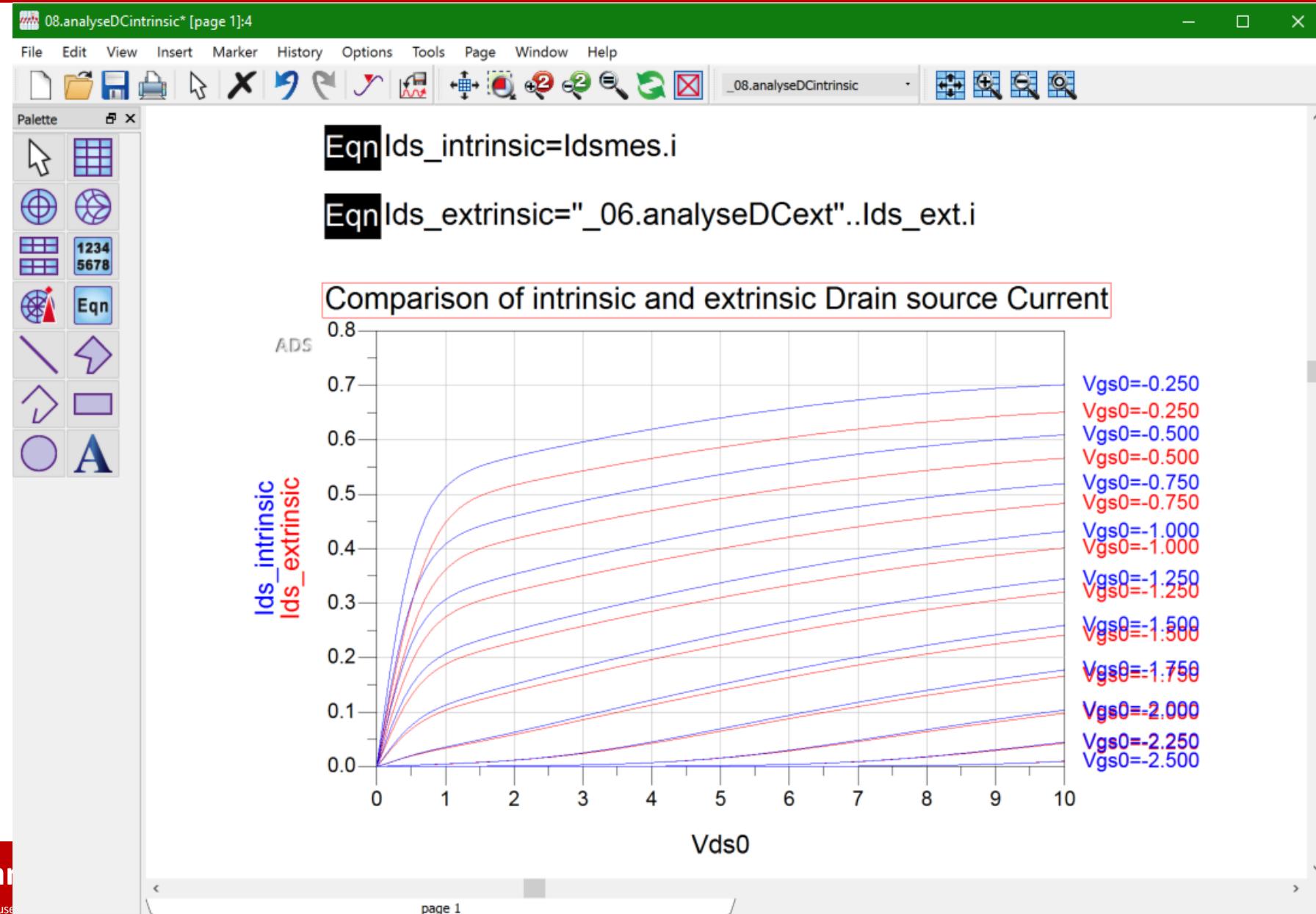




S Parameter Characteristics






UNIVERSITÀ
DEGLI STUDI
DI BRESCIA



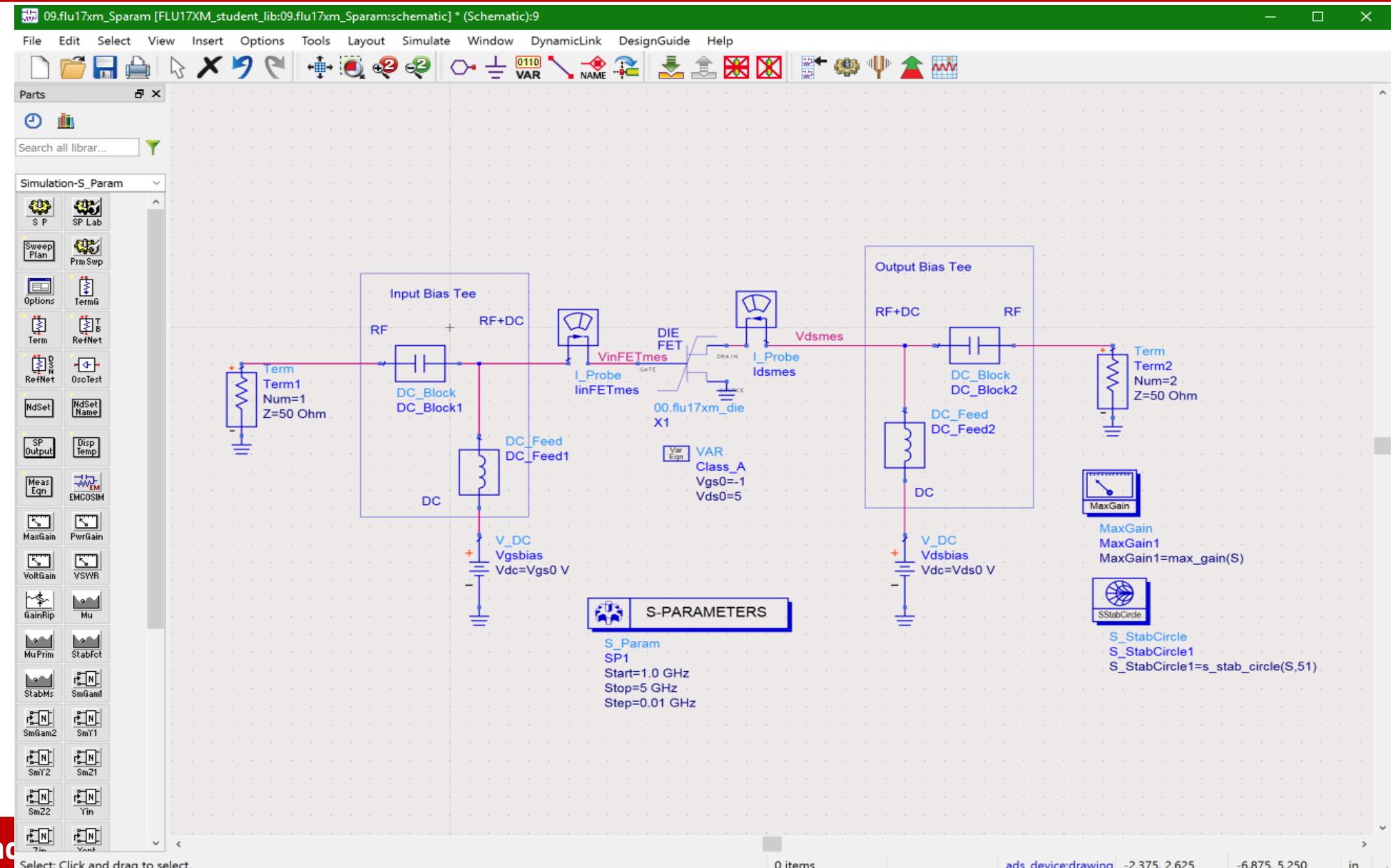
Schematic to plot the S parameter curves of the Die transistor



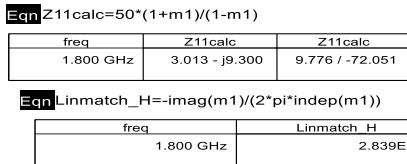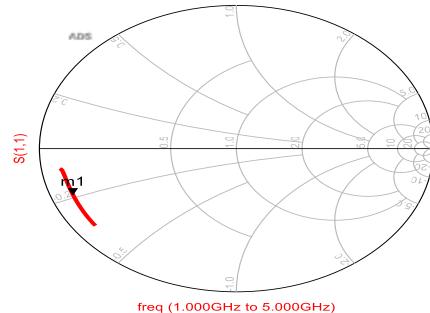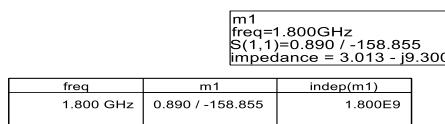

m3
freq=1.800GHz
 $\text{dB}(S(2,1))=8.528$


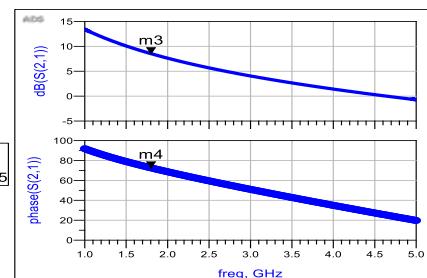
m4
freq=1.800GHz
 $\text{phase}(S(2,1))=72.605$



m5
freq=1.800GHz
MaxGain1=18.496


Eqn TPG=-1/(2*pi)*diff(S(2,1))

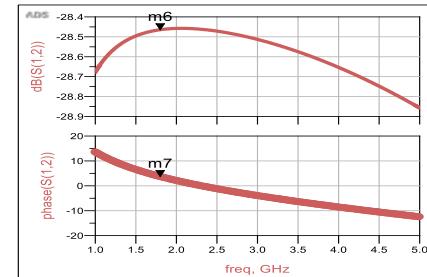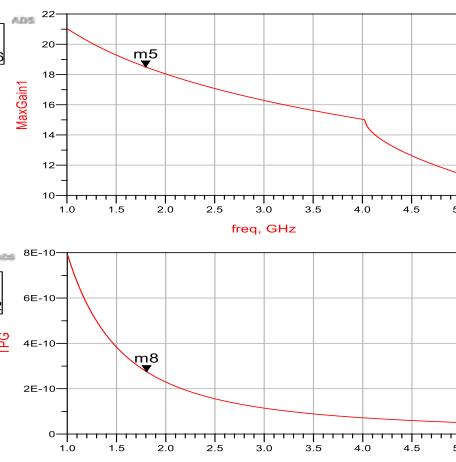m8
freq=1.805GHz
 $\text{TPG}=2.752E-10 / 105.182$



m6
freq=1.800GHz
 $\text{dB}(S(1,2))=-28.464$

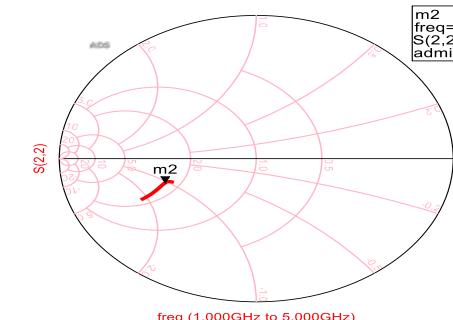m7
freq=1.800GHz
 $\text{phase}(S(1,2))=3.734$



m2
freq=1.800GHz
 $S(2,2)=0.492 / -159.975$
admittance = 0.048 + j0.021



freq	m2	indep(m2)
1.800 GHz	0.492 / -159.975	1.800E9

Eqn Z22calc=50*(1+m2)/(1-m2)


freq	Z22calc	Z22calc
1.800 GHz	17.511 - j7.774	19.159 / -23.938









Eqn Loutmatch_H=-imag(m2)/(2*pi*indep(m2))

freq	Loutmatch_H
1.800 GHz	1.488E-11

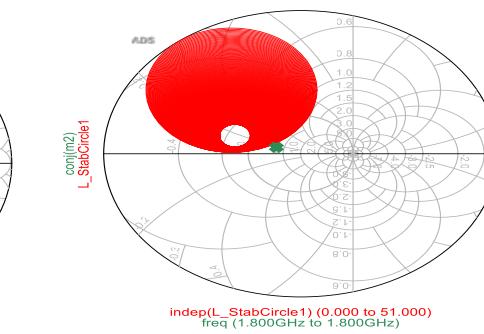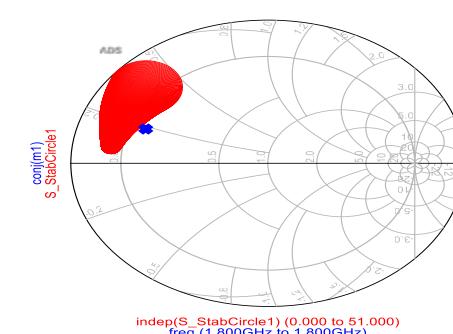

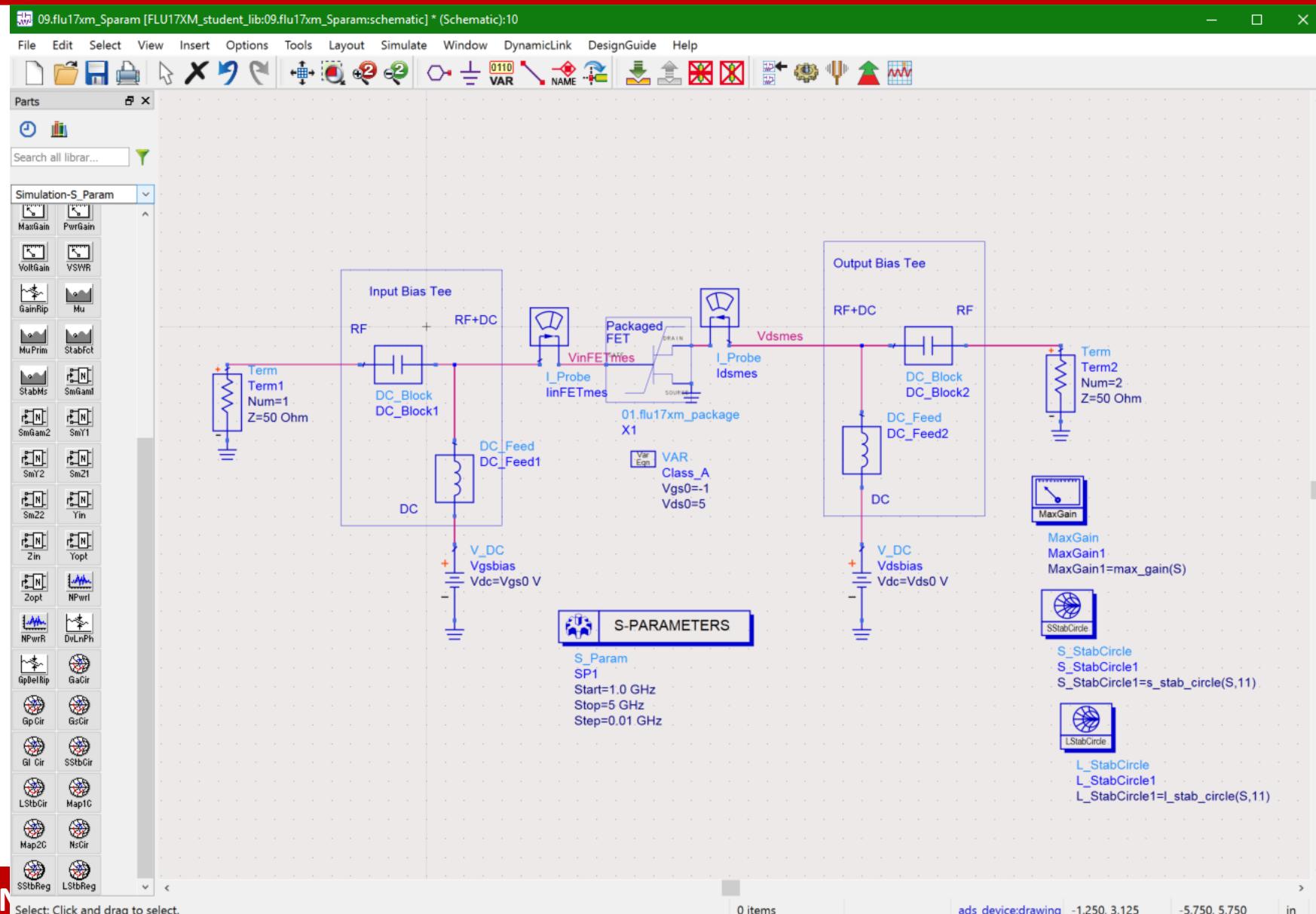Schematic to plot the S parameter curves of the Packaged transistor



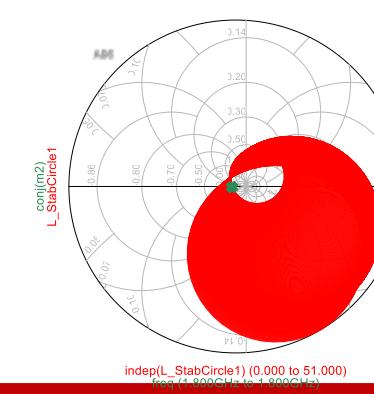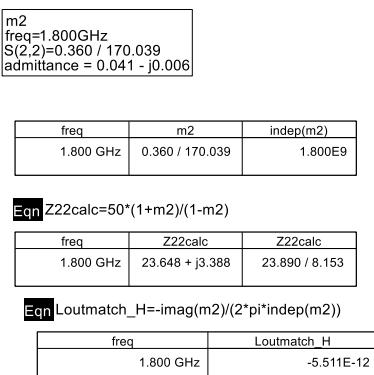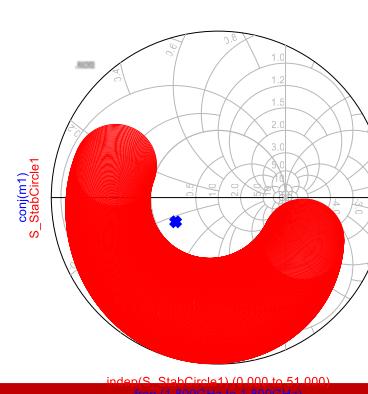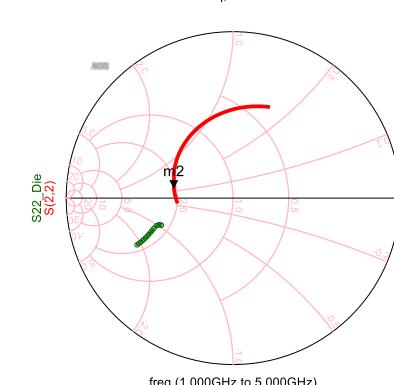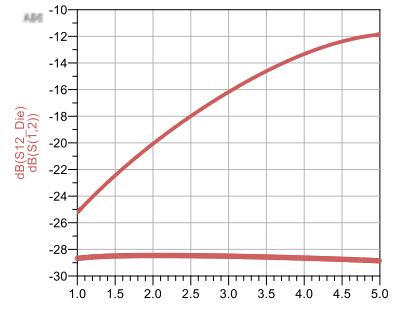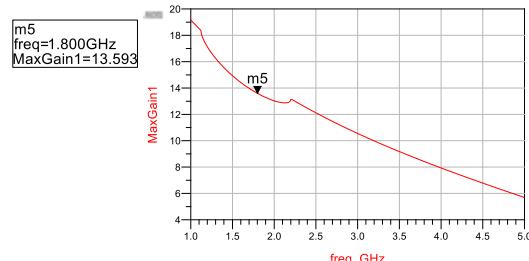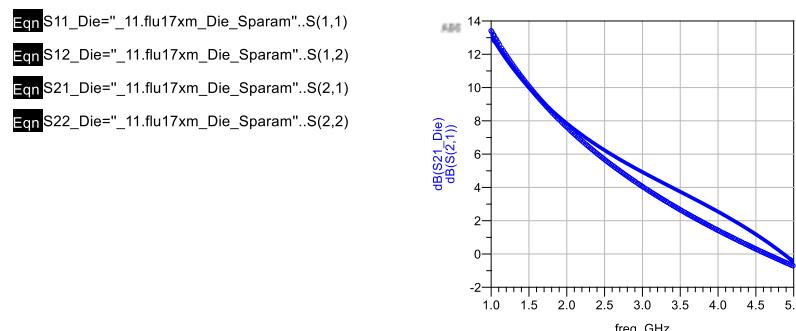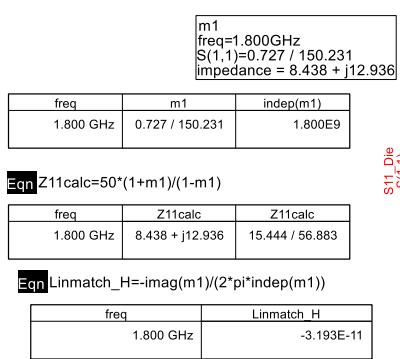





PA Design with Die transistor and Lumped components






UNIVERSITÀ
DEGLI STUDI
DI BRESCIA



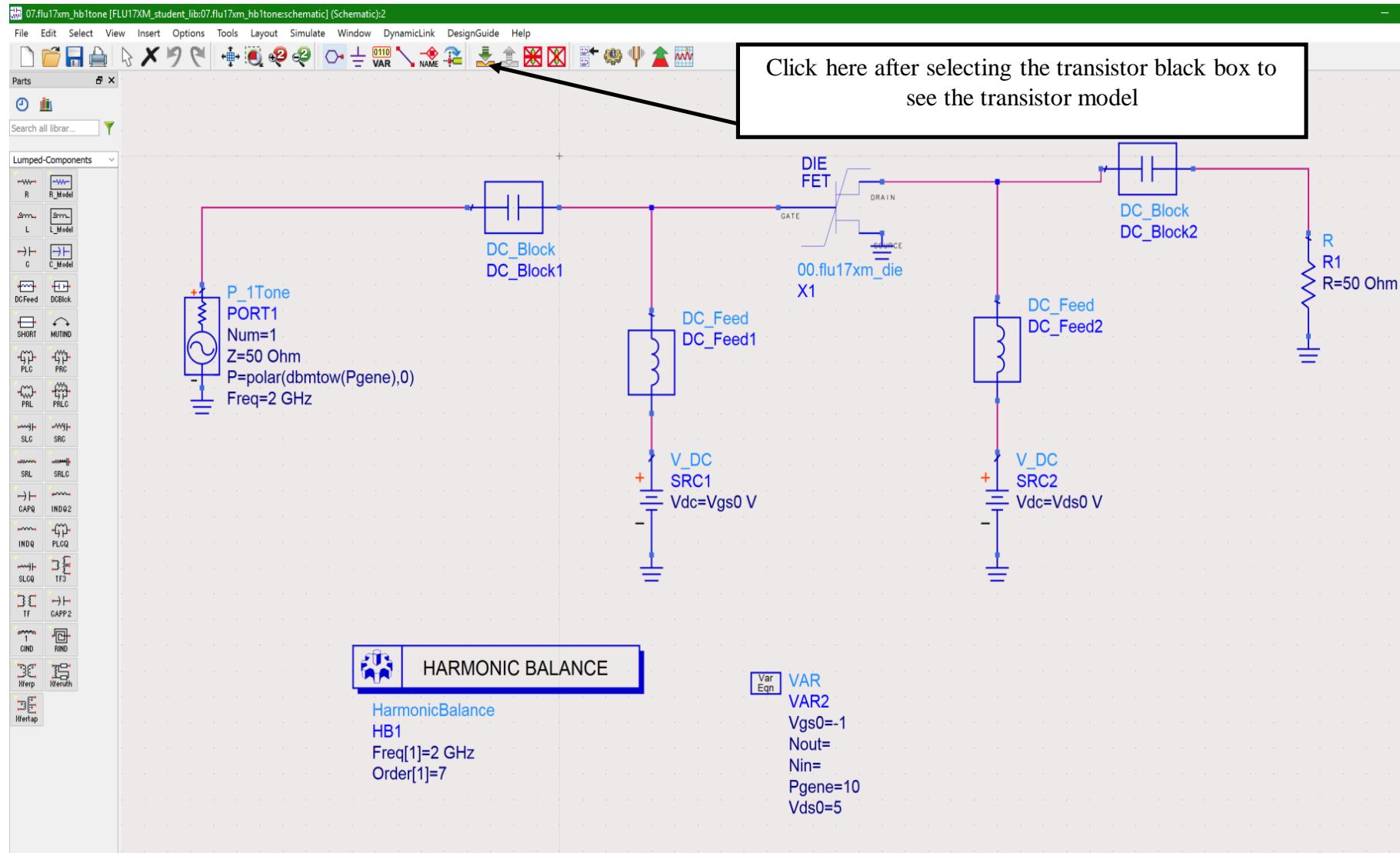

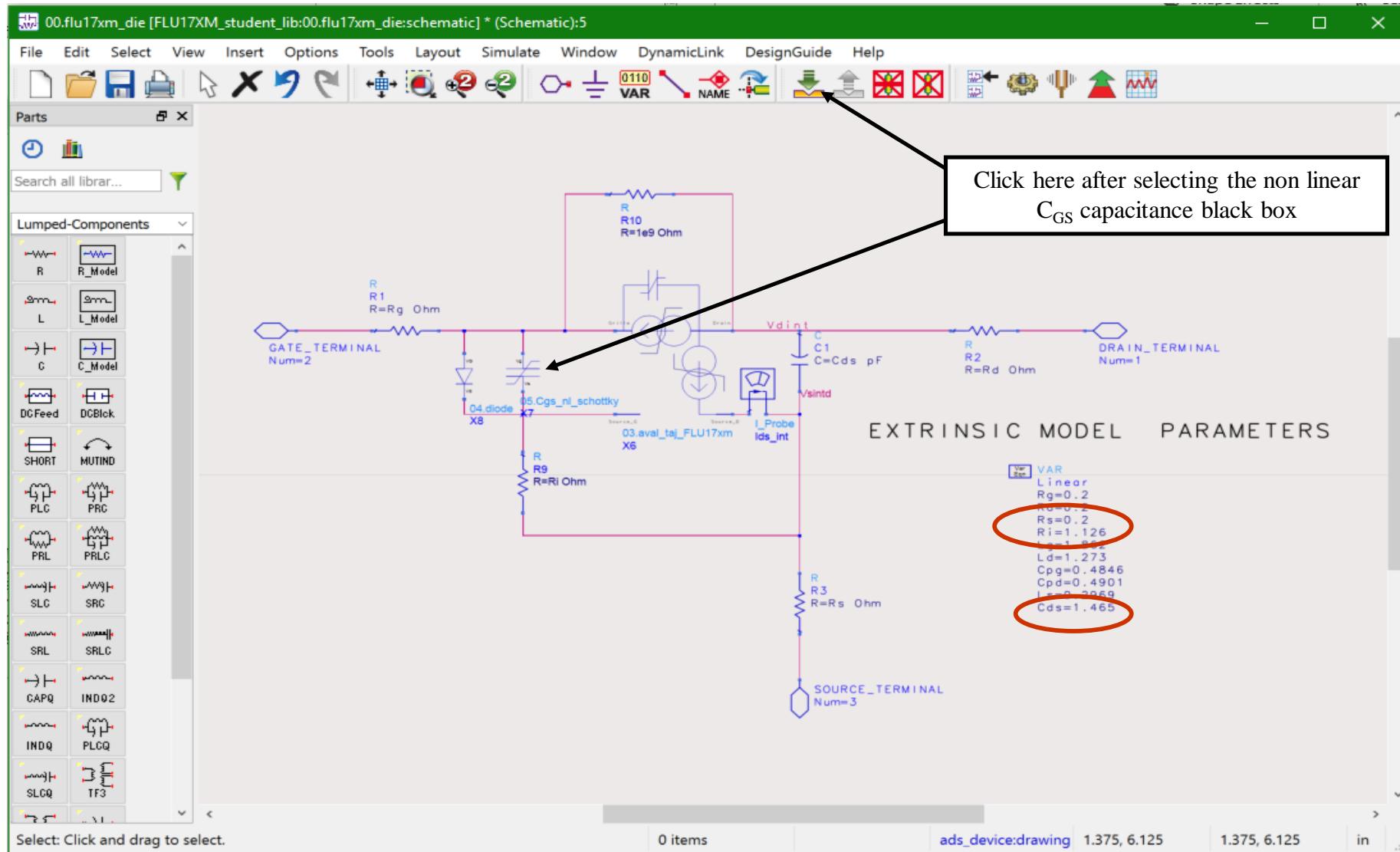

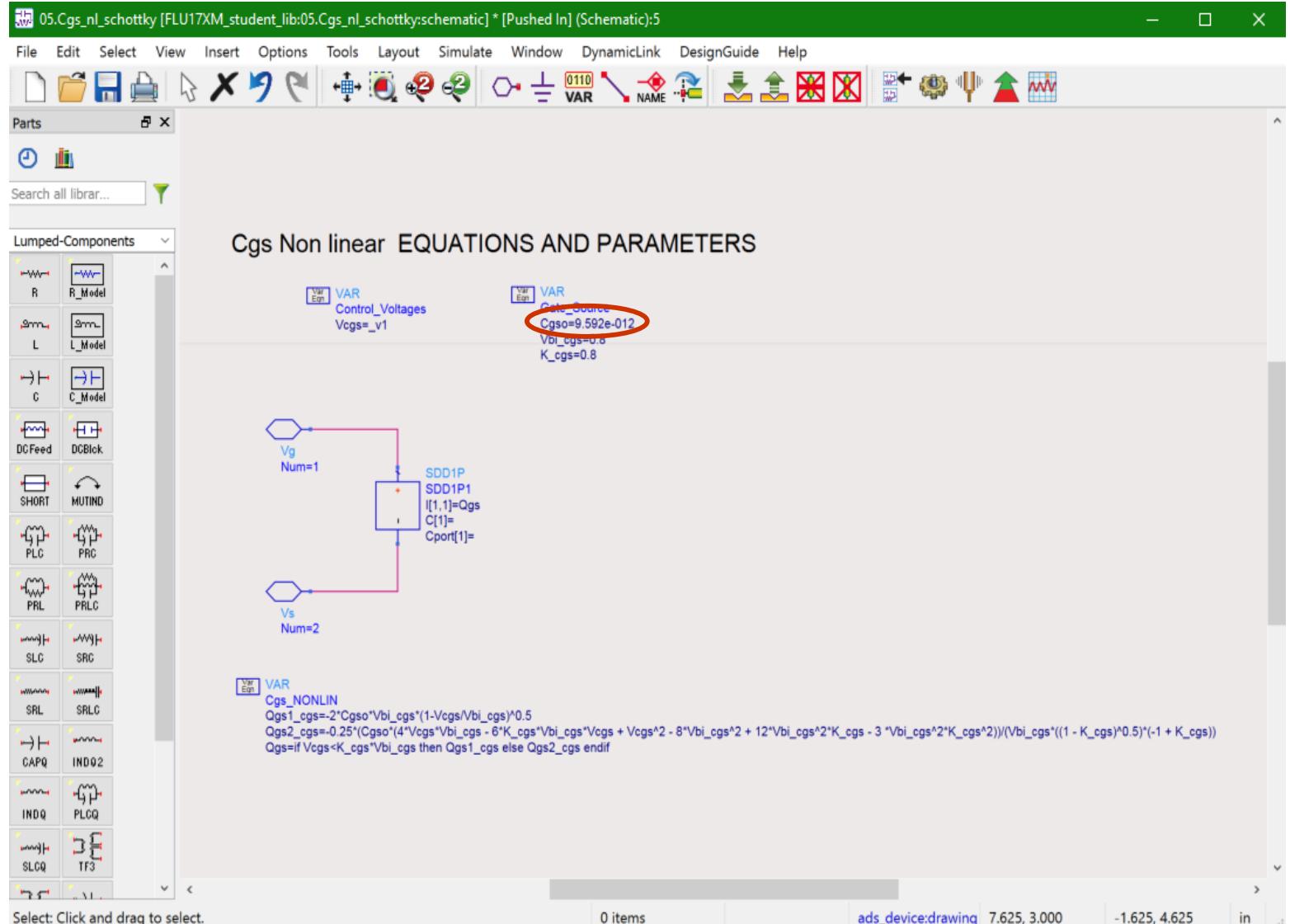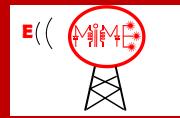

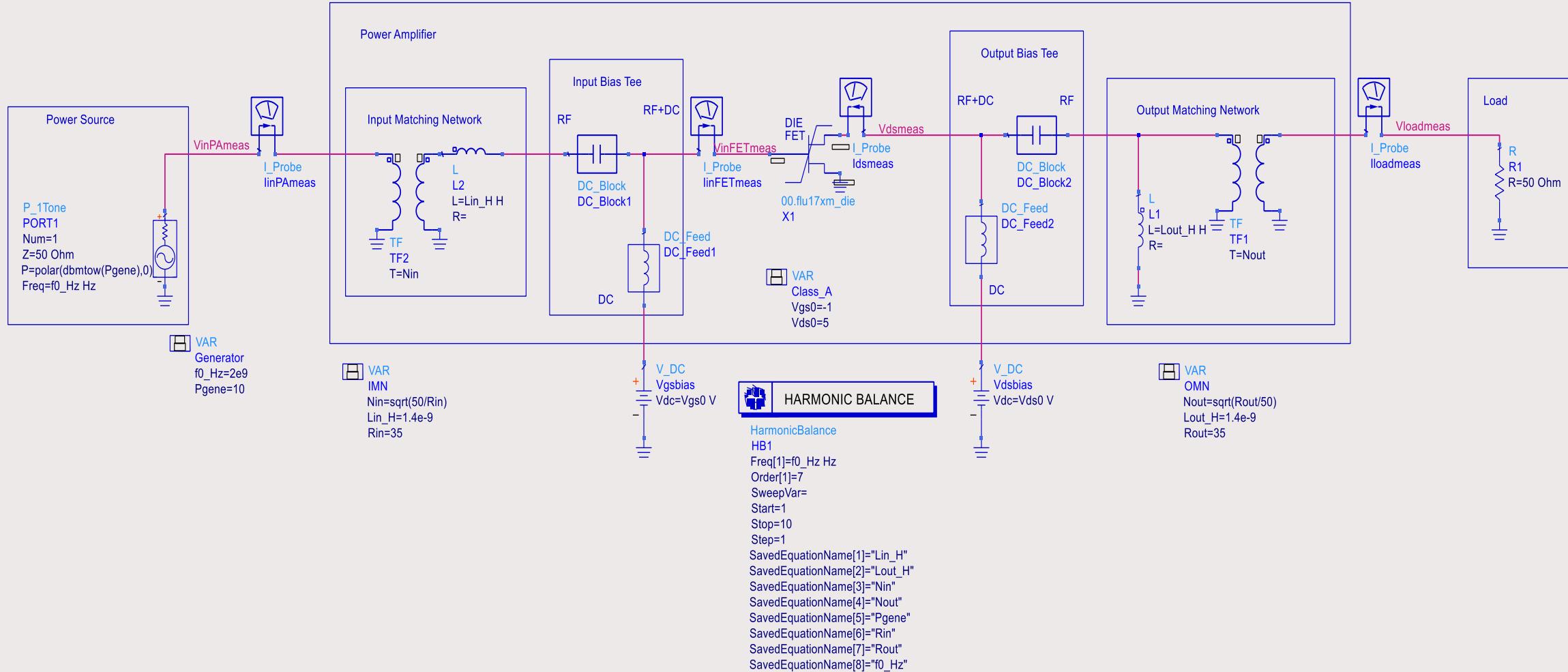

$$\text{Eqn} \quad \text{VinPA_f0} = \text{VinPAmeas}[1]$$

$$\text{Eqn} \quad \text{VoutPA_f0} = \text{Vloadmeas}[1]$$

$$\text{Eqn} \quad \text{linPA_f0} = \text{linPAmeas.i}[1]$$

$$\text{Eqn} \quad \text{outPA_f0} = \text{lloadmeas.i}[1]$$

$$\text{Eqn} \quad \text{PinPA_f0_mW} = 0.5 * 1000 * \text{real}(\text{VinPA_f0} * \text{conj}(\text{linPA_f0}))$$

$$\text{Eqn} \quad \text{PinPA_f0_dBm} = 10 * \log10(\text{PinPA_f0_mW})$$

$$\text{Eqn} \quad \text{GPA_f0} = \text{PoutPA_f0_mW} / \text{PinPA_f0_mW}$$

$$\text{Eqn} \quad \text{GPA_f0_dBm} = 10 * \log10(\text{GPA_f0})$$

$$\text{Eqn} \quad \text{VinPA_DC} = \text{mag}(\text{VinFETmeas}[0]) \quad \text{Eqn} \quad \text{linPA_DC} = \text{mag}(\text{linFETmeas.i}[0])$$

$$\text{Eqn} \quad \text{VoutPA_DC} = \text{mag}(\text{Vdsmeas}[0]) \quad \text{Eqn} \quad \text{outPA_DC} = \text{mag}(\text{Idsmeas.i}[0])$$

$$\text{Eqn} \quad \text{PoutPA_f0_mW} = 0.5 * 1000 * \text{real}(\text{VoutPA_f0} * \text{conj}(\text{outPA_f0}))$$

$$\text{Eqn} \quad \text{PoutPA_f0_dBm} = 10 * \log10(\text{PoutPA_f0_mW})$$

$$\text{Eqn} \quad \text{PaddPA_f0_mW} = \text{PoutPA_f0_mW} - \text{PinPA_f0_mW}$$

$$\text{Eqn} \quad \text{PaddPA_f0_dBm} = 10 * \log10(\text{PaddPA_f0_mW})$$

$$\text{Eqn} \quad \text{PDC_mW} = 1000 * (\text{VinPA_DC} * \text{linPA_DC} + \text{VoutPA_DC} * \text{outPA_DC})$$

$$\text{Eqn} \quad \text{Drain_Efficiency} = \text{PoutPA_f0_mW} / \text{PDC_mW} * 100$$


$$\text{Eqn} \quad \text{PAE} = \text{PaddPA_f0_mW} / \text{PDC_mW} * 100$$

$$\text{Eqn} \quad \text{ZinFET_f0} = \text{VinFETmeas}[1] / \text{linFETmeas.i}[1]$$

$$\text{Eqn} \quad \text{ZinPA_f0} = \text{VinPAmeas}[1] / \text{linPAmeas.i}[1]$$



$$\text{Eqn} \quad \text{GamainFET_f0} = (\text{ZinFET_f0} - 50) / (\text{ZinFET_f0} + 50)$$
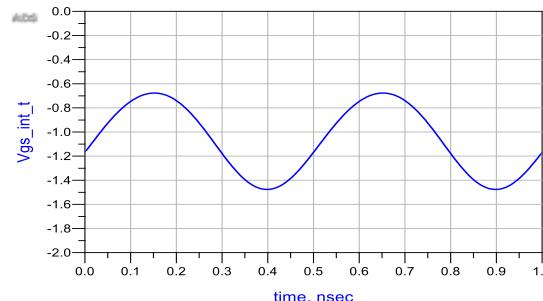
$$\text{Eqn} \quad \text{GamainPA_f0} = (\text{ZinPA_f0} - 50) / (\text{ZinPA_f0} + 50)$$



PinPA_f0_mW	PoutPA_f0_mW	GPA_f0	PDC_mW	Drain_Efficiency	PAE
0.045	82.285	1816.913	1554.143	5.295	5.292

PinPA_f0_dBm	PoutPA_f0_dBm	GPA_f0_dB	PDC_mW	Drain_Efficiency	PAE
-13.440	19.153	32.593	1554.143	5.295	5.292

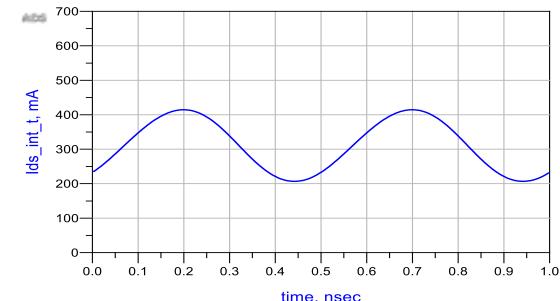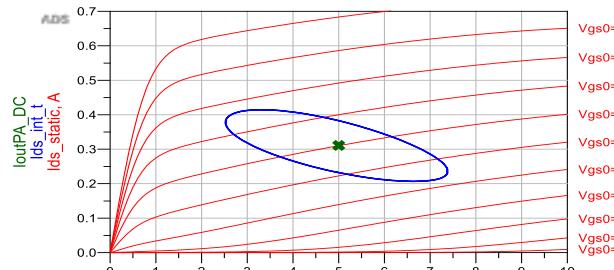

$$\text{Eqn} \quad \text{ds_static} = \text{"_06.analyseDCext".Ids_int.i}$$



$$\text{Eqn} \quad \text{time_s} = \text{ts(freq)}$$

$$\text{Eqn} \quad \text{Vds_int} = \text{Vdint} - \text{Vsintd}$$

$$\text{Eqn} \quad \text{Vds_int_t} = \text{ts(Vds_int)}$$

$$\text{Eqn} \quad \text{Vgs_int_t} = \text{ts(Vgint-Vsintg)}$$
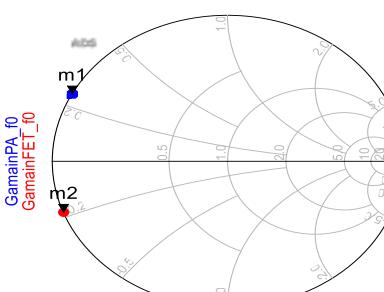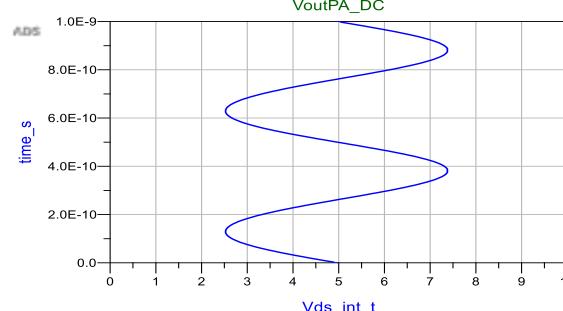
$$\text{Eqn} \quad \text{Ids_int_t} = \text{ts(Ids_int.i)}$$



$$\begin{aligned} m2 & \text{indep}(m2)=0 \\ \text{GamainFET_f0} &= 0.998 / -159.492 \\ \text{impedance} &= Z_0 * (8.417E-4 - j0.181) \end{aligned}$$

$$\begin{aligned} m1 & \text{indep}(m1)=0 \\ \text{GamainPA_f0} &= 0.998 / 152.552 \\ \text{impedance} &= Z_0 * (0.001 + j0.244) \end{aligned}$$

ZinFET_f0	GamainFET_f0
0.042 - j9.045	0.998 / -159.492
ZinPA_f0	GamainPA_f0
0.060 + j12.211	0.998 / 152.552

File Edit Select View Insert Options Tools Layout Simulate Window DynamicLink DesignGuide Help

Parts

Search all library...

Lumped-Components

- R
- L
- C
- DCFeed
- SHORT
- TUNE
- PLC
- PRL
- SLC
- SRL
- CAPO
- INDQ
- SLCQ
- TF
- CIND
- Kfrep
- Kfertap

Power Source

Power Amplifier

Input Matching Network

RF

Input Bias Tee

RF+DC

DIE FET

Vdsmeas

I_Probe

lntFETmeas

DC_Block

DC_Feed

DC_Feed1

DC

V_DC

Vgsbias

Vdc=Vgs0 V

HARMONIC BALANCE

HarmonicBalance

HB1

Freq[1]=0, Hz Hz

Order[1]=7

SaveEquationName[1]=Lin_H

SaveEquationName[2]=Lout_H

SaveEquationName[3]=Rin

SaveEquationName[4]=Rout

SaveEquationName[5]=Rin

SaveEquationName[6]=Rout

SaveEquationName[7]=Rout

SaveEquationName[8]=Rout

Output Bias Tee

RF+DC

DC_Block

DC_Feed2

DC_Feed

DC

V_DC

Vdsbias

Vdc=Vds0 V

Output Matching Network

RF

DC

DC_Feed

DC_Feed2

DC

V_Probe

lloadmeas

Load

R1

R=50 Ohm

1°) Click the « tuning » button

2°) Select the Parameters to tune : they appear in the « Tune Parameters » window

FLU17XM_student.lib:13.flu17xm_PA_lumped_imag_out:schematic

Rout	Lout_H	Lin_H	Rin	Pgene
Value Max Min Step Scale	17.511 26.2665 8.7555 1.7511 Lin	1.488e-1 2.232e-1 7.44e-12 1.488e-1 Lin	2.839e-1 4.2585e-1 1.4195e-1 2.839e-1 Lin	3.013 4.5195 1.5065 0.3013 Lin


Click a parameter to toggle tuning. Click an instance to open a tuning dialog.

VAR Generator

ads_device:drawing 0.125, -0.500 6.625, 3.125 in

- 28 -

After the tuning of the 5 parameters

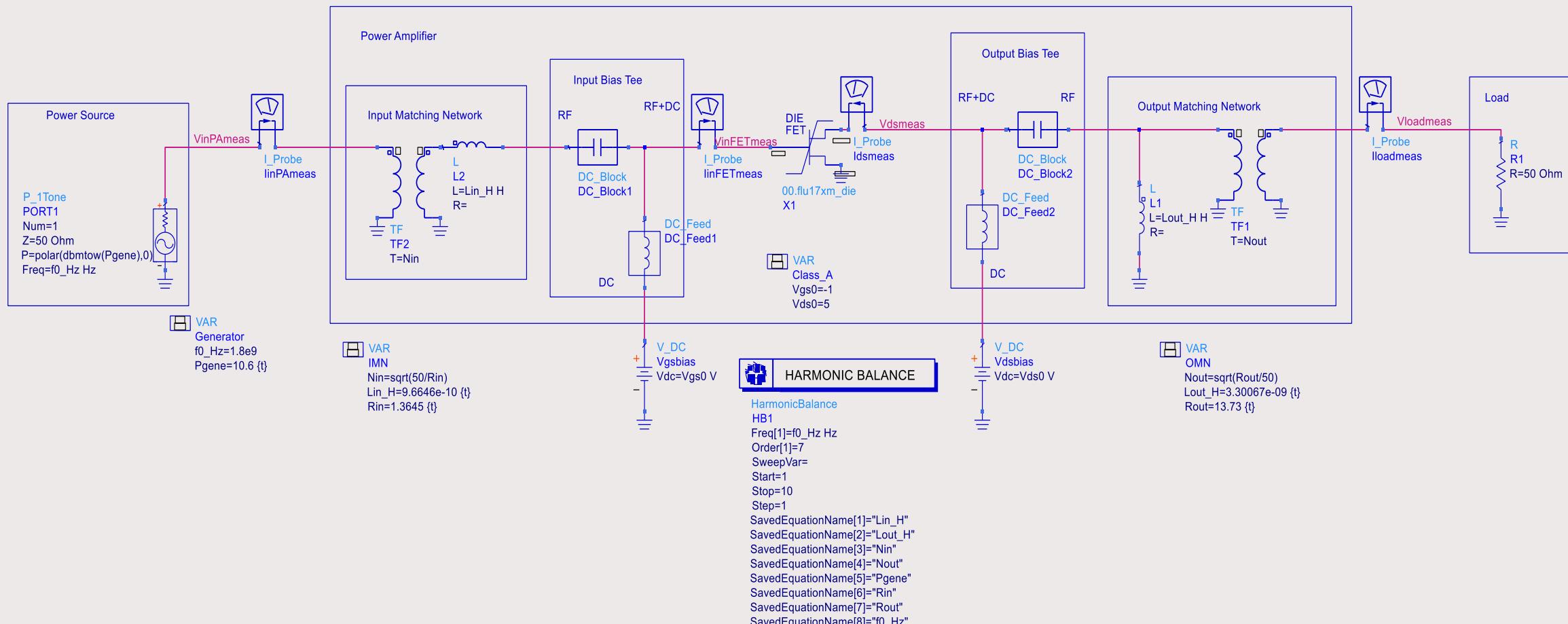

E(rasmus) Mundus on Innovative Microwave Electronics and Optics

Results after the tuning of the 5 parameters to maximise the output power of the PA.

Method to tune the parameters

- 1) Tune first Lout_H
- 2) Tune Secondly Rout
- 3) Modify Pgene if required
- 4) Tune again Lout_H
- 5) Tune again Rout
- 6) Tune then Lin_H to cancel Imag(ZinPA)
- 7) Tune Secondly Rin (To match ZinPA=50Ω)
- 8) Modify Pgene if required
- 9) Tune again Lout_H if required
- 10) Tune again Rout if required
- 11) Tune again Lin_H to cancel Imag(ZinPA)
- 12) Tune again Rin (To match ZinPA=50Ω)
- 13) Repeat again step 8 to 12 to maximise the Gain or the output power or the PAE

$$\text{Eqn} \quad \text{VinPA_f0} = \text{VinPAmeas}[1]$$

$$\text{Eqn} \quad \text{VoutPA_f0} = \text{Vloadmeas}[1]$$

$$\text{Eqn} \quad \text{VinPA_DC} = \text{mag}(\text{VinFETmeas}[0])$$


$$\text{Eqn} \quad \text{VoutPA_DC} = \text{mag}(\text{Vdsmeas}[0])$$

$$\text{Eqn} \quad \text{ZinFET_f0} = \text{VinFETmeas}[1]/\text{linFETmeas.i}[1]$$

$$\text{Eqn} \quad \text{ZinPA_f0} = \text{VinPAmeas}[1]/\text{linPAmeas.i}[1]$$

$$\text{Eqn} \quad \text{GamainFET_f0} = (\text{ZinFET_f0}-50)/(\text{ZinFET_f0}+50)$$
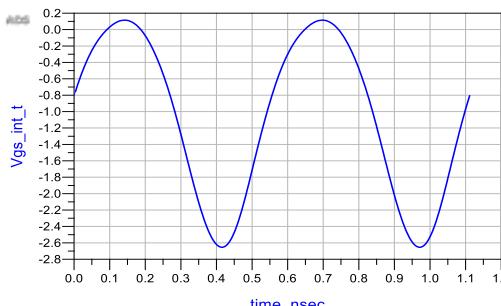
$$\text{Eqn} \quad \text{GamainPA_f0} = (\text{ZinPA_f0}-50)/(\text{ZinPA_f0}+50)$$



$$\text{Eqn} \quad \text{ids_static} = "_06.analyseDCext"\..ids_int.i$$

$$\text{Eqn} \quad \text{time_s} = \text{ts(freq)}$$

$$\text{Eqn} \quad \text{Vds_int} = \text{Vdint}\text{-Vsintd}$$

$$\text{Eqn} \quad \text{Vds_int_t} = \text{ts(Vds_int)}$$

$$\text{Eqn} \quad \text{Vgs_int_t} = \text{ts(Vgint-Vsintg)}$$

$$\text{Eqn} \quad \text{ids_int_t} = \text{ts(ids_int.i)}$$

$$\text{Eqn} \quad \text{linPA_f0} = \text{linPAmeas.i}[1]$$

$$\text{Eqn} \quad \text{loutPA_f0} = \text{lloadmeas.i}[1]$$

$$\text{Eqn} \quad \text{PinPA_f0_mW} = 0.5 * 1000 * \text{real}(\text{VinPA_f0} * \text{conj}(\text{linPA_f0}))$$

$$\text{Eqn} \quad \text{PinPA_f0_dBm} = 10 * \log10(\text{PinPA_f0_mW})$$

$$\text{Eqn} \quad \text{PoutPA_f0_mW} = 0.5 * 1000 * \text{real}(\text{VoutPA_f0} * \text{conj}(\text{loutPA_f0}))$$

$$\text{Eqn} \quad \text{PoutPA_f0_dBm} = 10 * \log10(\text{PoutPA_f0_mW})$$

$$\text{Eqn} \quad \text{PDC_mW} = 1000 * (\text{VinPA_DC} * \text{linPA_DC} + \text{VoutPA_DC} * \text{loutPA_DC})$$

$$\text{Eqn} \quad \text{GPA_f0} = \text{PoutPA_f0_mW}/\text{PinPA_f0_mW}$$

$$\text{Eqn} \quad \text{GPA_f0_dB} = 10 * \log10(\text{GPA_f0})$$

$$\text{Eqn} \quad \text{PaddPA_f0_mW} = \text{PoutPA_f0_mW} - \text{PinPA_f0_mW}$$



$$\text{Eqn} \quad \text{PaddPA_f0_dBm} = 10 * \log10(\text{PaddPA_f0_mW})$$

$$\text{Eqn} \quad \text{Drain_Efficiency} = \text{PoutPA_f0_mW}/\text{PDC_mW} * 100$$

$$\text{Eqn} \quad \text{PAE} = \text{PaddPA_f0_mW}/\text{PDC_mW} * 100$$

PinPA_f0_mW	PoutPA_f0_mW	GPA_f0	PDC_mW	Drain_Efficiency	PAE
11.482	790.611	68.859	1692.671	46.708	46.030


PinPA_f0_dBm	PoutPA_f0_dBm	GPA_f0_dB	PDC_mW	Drain_Efficiency	PAE
10.600	28.980	18.380	1692.671	46.708	46.030

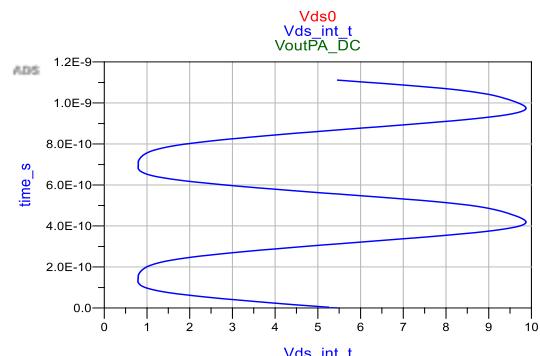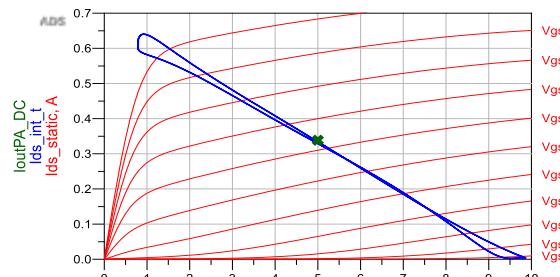

ZinFET_f0	GamainFET_f0
1.365 - j10.931	0.949 / -155.320

ZinPA_f0	GamainPA_f0
50.024 - j0.004	2.428E-4 / -8.749

m2 indep(m2)=0 GamainPA_f0=0.949 / -155.320 Impedance = Z0 * (0.027 - j0.219)	m1 indep(m1)=0 GamainPA_f0=2.428E-4 / -8.749 Impedance = Z0 * (1.000 - j7.390E-5)
--	--



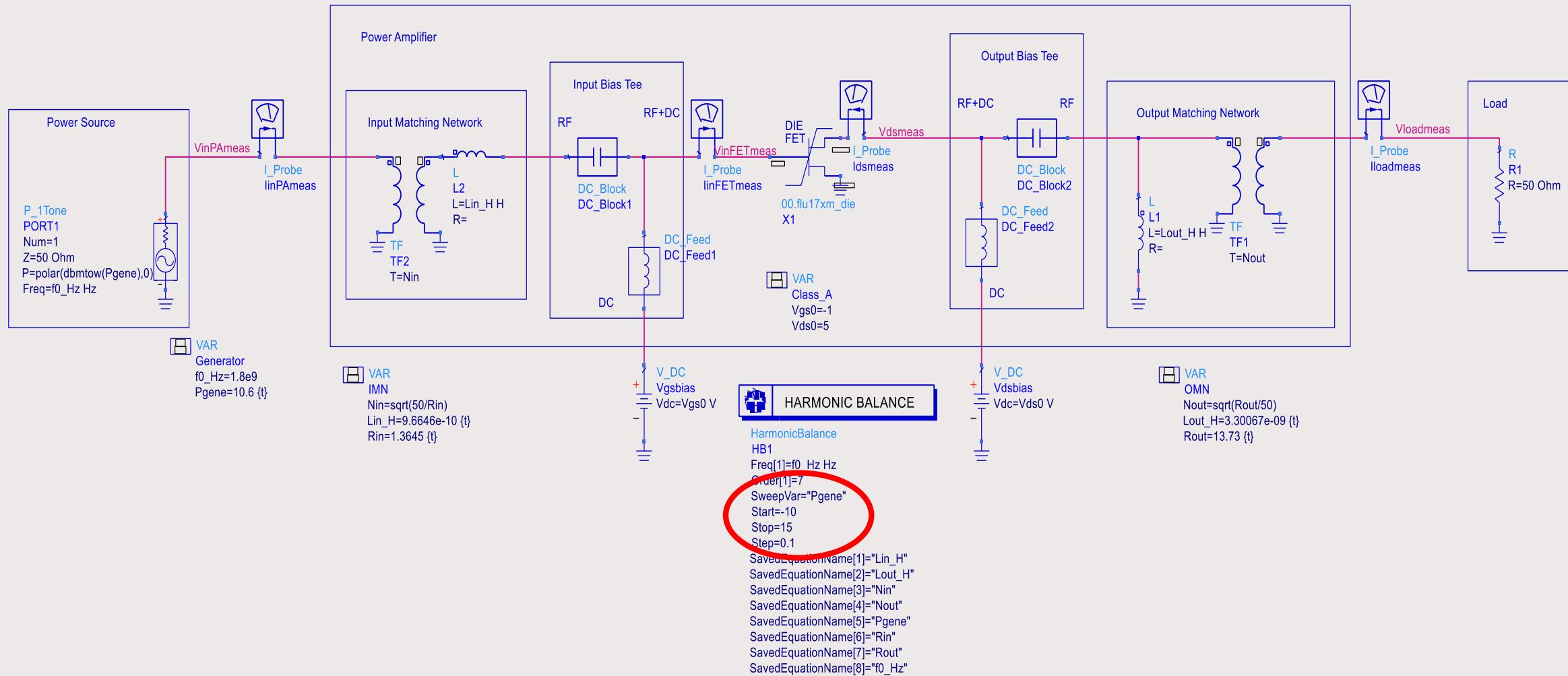


Eqn VinPA_f0=VinPAmeas[1]	Eqn linPA_f0=linPAmeas.i[1]	Eqn PinPA_f0_mW=0.5*1000*real(VinPA_f0*conj(linPA_f0))	Eqn GPA_f0=PoutPA_f0_mW/PinPA_f0_mW
Eqn VoutPA_f0=Vloadmeas[1]	Eqn loutPA_f0=lloadmeas.i[1]	Eqn PinPA_f0_dBm=10*log10(PinPA_f0_mW)	Eqn GPA_f0_dB=10*log10(GPA_f0)
Eqn VinPA_DC=mag(VinFETmeas[0])	Eqn linPA_DC=mag(linFETmeas.i[0])	Eqn PoutPA_f0_mW=0.5*1000*real(VoutPA_f0*conj(loutPA_f0))	Eqn PaddPA_f0_mW=PoutPA_f0_mW-PinPA_f0_mW
Eqn VoutPA_DC=mag(Vdsmeas[0])	Eqn loutPA_DC=mag(ldsmeas.i[0])	Eqn PoutPA_f0_dBm=10*log10(PoutPA_f0_mW)	Eqn PaddPA_f0_dBm=10*log10(PaddPA_f0_mW)
		Eqn PDC_mW=1000*(VinPA_DC*linPA_DC+VoutPA_DC*loutPA_DC)	Eqn Drain_Efficiency=PoutPA_f0_mW/PDC_mW*100
			Eqn PAE=PaddPA_f0_mW/PDC_mW*100



Eqn ZinFET_f0=VinFETmeas[1]/linFETmeas.i[1]	Pgene	PinPA_f0_mW	...lPA_f0_mW	GPA_f0	PDC_mW	...in_Efficiency	PAE
Eqn ZinPA_f0=VinPAmeas[1]/linPAmeas.i[1]	-10.000	0.099	9.234	92.811	1551.479	0.595	0.589
Eqn GamainFET_f0=(ZinFET_f0-50)/(ZinFET_f0+50)							
Eqn GamainPA_f0=(ZinPA_f0-50)/(ZinPA_f0+50)							

Pgene	PinPA_f0_mW	...lPA_f0_mW	GPA_f0	PDC_mW	...in_Efficiency	PAE
-10.000	0.099	9.234	92.811	1551.479	0.595	0.589









Pgene	...lPA_f0_dBm	...lPA_f0_dBm	GPA_f0_dB	PDC_mW	...in_Efficiency	PAE
-10.000	-10.022	9.654	19.676	1551.479	0.595	0.589

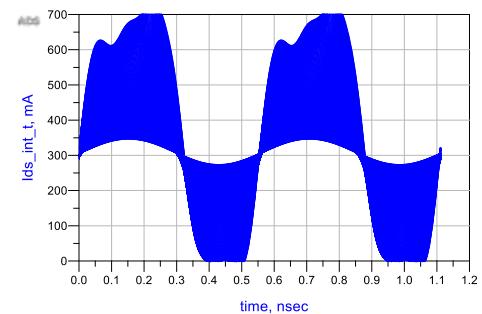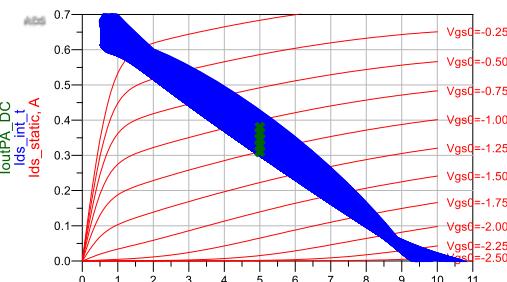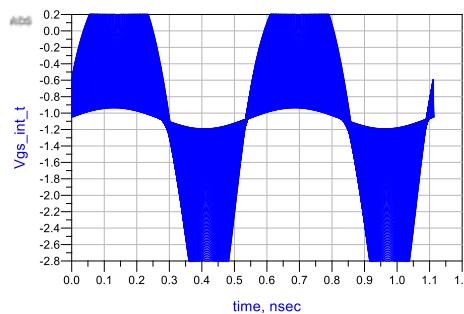


Eqn Ids_static="_06.analyseDCext"..Ids_int.i	Pgene	ZinFET_f0	...ainFET_f0
Eqn time_s=ts(freq)	-10.000	$1.332 + j11\ldots$	$0.951 / -154\ldots$
Eqn Vds_int=Vdint-Vsintd	-9.900	$1.332 - j11\ldots$	$0.951 / -154\ldots$
Eqn Vds_int_t=ts(Vds_int)			
Eqn Vgs_int_t=ts(Vgint-Vsintg)			
Eqn Ids_int_t=ts(Ids_int.i)			

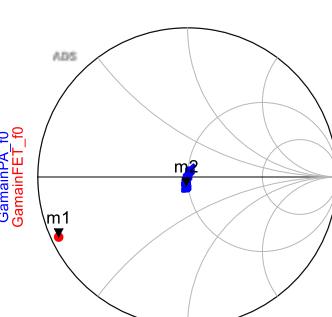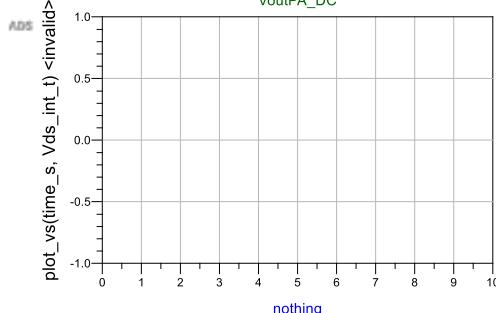

m1	Pgene = 1.879E-14	m2	Pgene = 1.879E-14
	GamainFET_f0 = 0.950 / -154.969		GamainPA_f0 = 0.061 / -97.558
	impedance = $Z_0 * (0.027 + j0.222)$		impedance = $Z_0 * (0.977 + j0.118)$

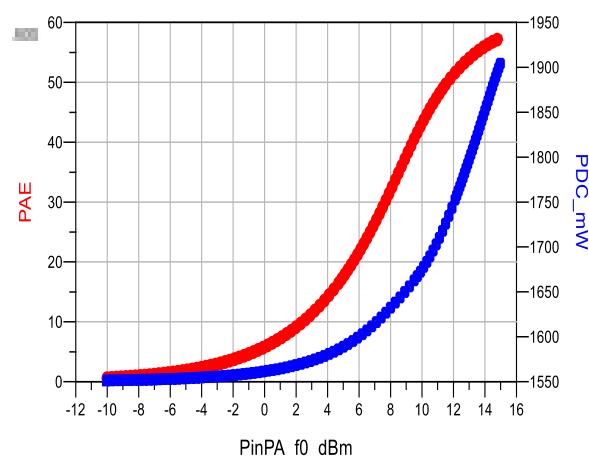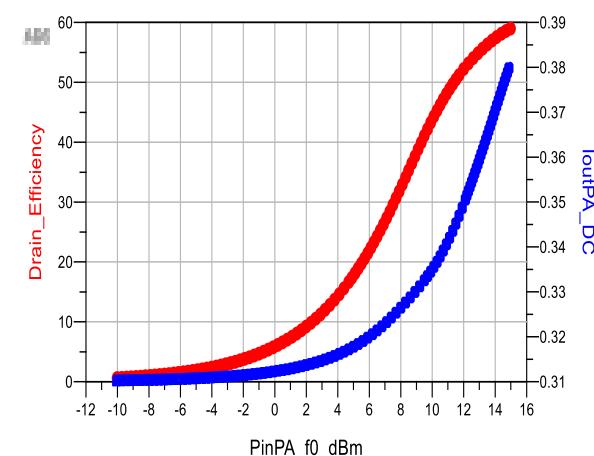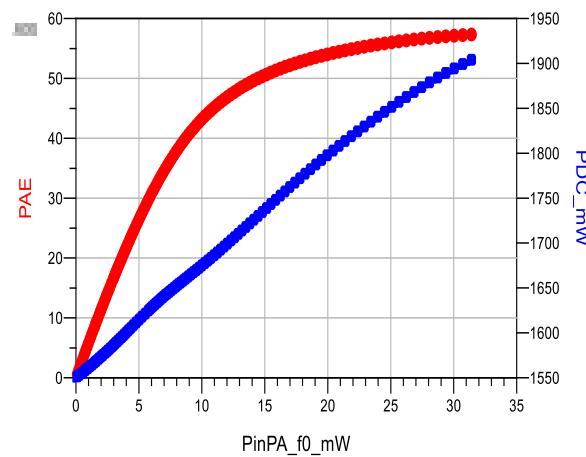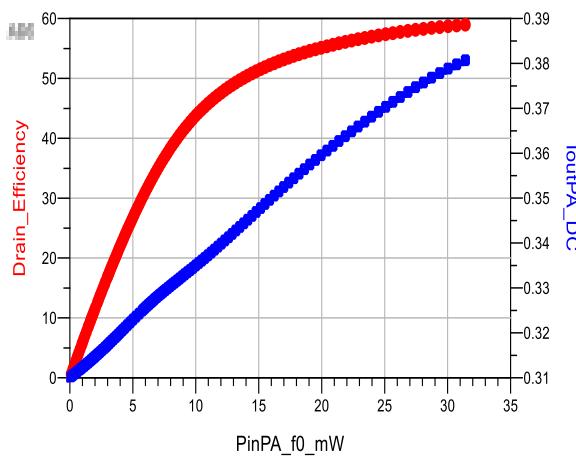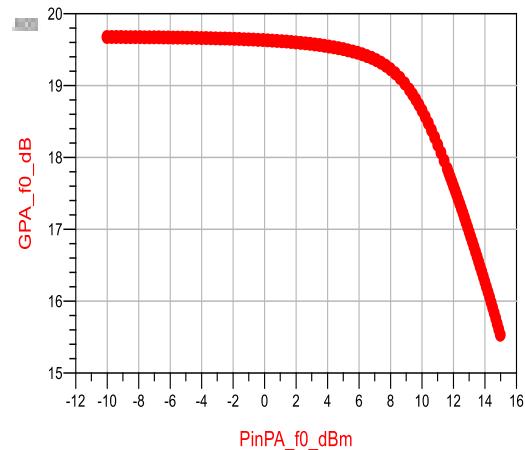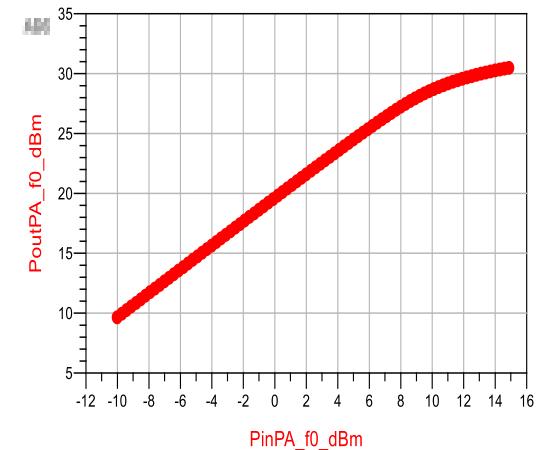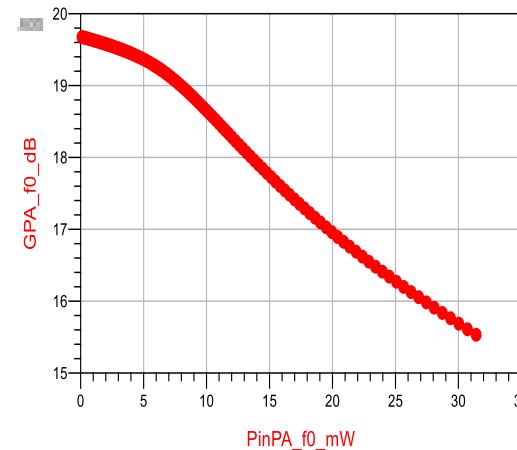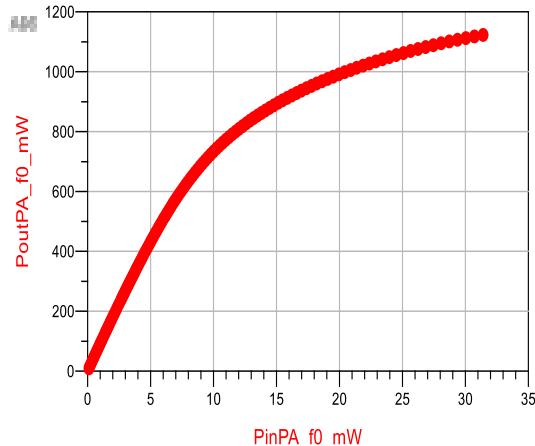

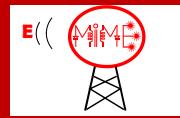

PA Design with the packaged transistor and transmission Lines

LineCalc/untitled

File Simulation Options Help

Lumpers

Component

Type MLIN ID MLIN: MLIN_DEFAULT

Substrate Parameters

ID MSUB_DEFAULT

Er	4.700	N/A
Mur	1.000	N/A
H	1.590	mm
Hu	3.9e+34	mil
T	25.000	um
Cond	1e50	N/A

Physical

W 2.876950 mm
L 22.219500 mm

Synthesize **Analyze**

Calculated Results

K_Eff = 3.511
A_DB = 0.125
SkinDepth = 0.000

Component Parameters

Freq 1.800 GHz
Wall1 mil
Wall2 mil

Values are consistent

MSUB

MSUB
MSub1
H=1.59 mm
Er=4.7
Mur=1
Cond=1.0E+50
Hu=3.9e+034 mil
T=35 um
TanD=0.02
Rough=0 mil



Circuit Diagram



```


    graph LR
        VDC1[V_DC SRC1] --> C1[C1 1.0 uF]
        C1 --> MLIN[MLIN TL1]
        MLIN --> C2[C2 1.0 uF]
        C2 --> VDC2[V_DC SRC2]
        MLIN --> SParam[S-PARAMETERS]
        SParam --> VAR1[VAR1 Vds0=5]
    
```

S-PARAMETERS

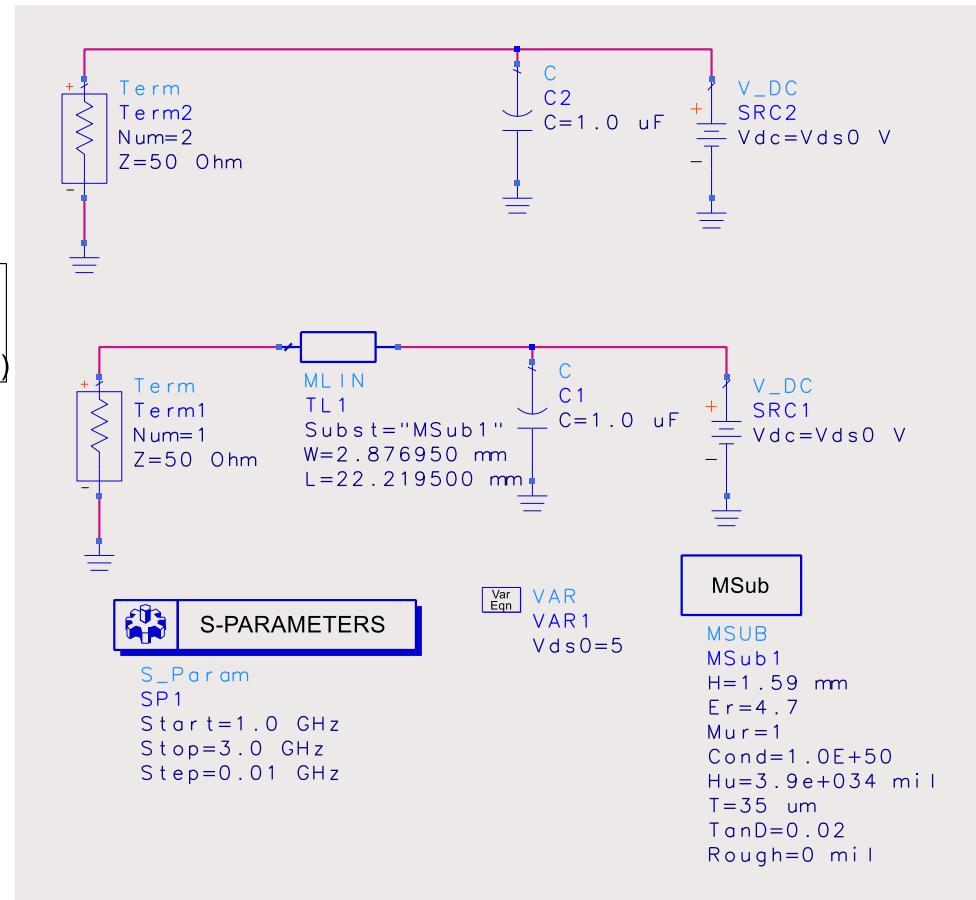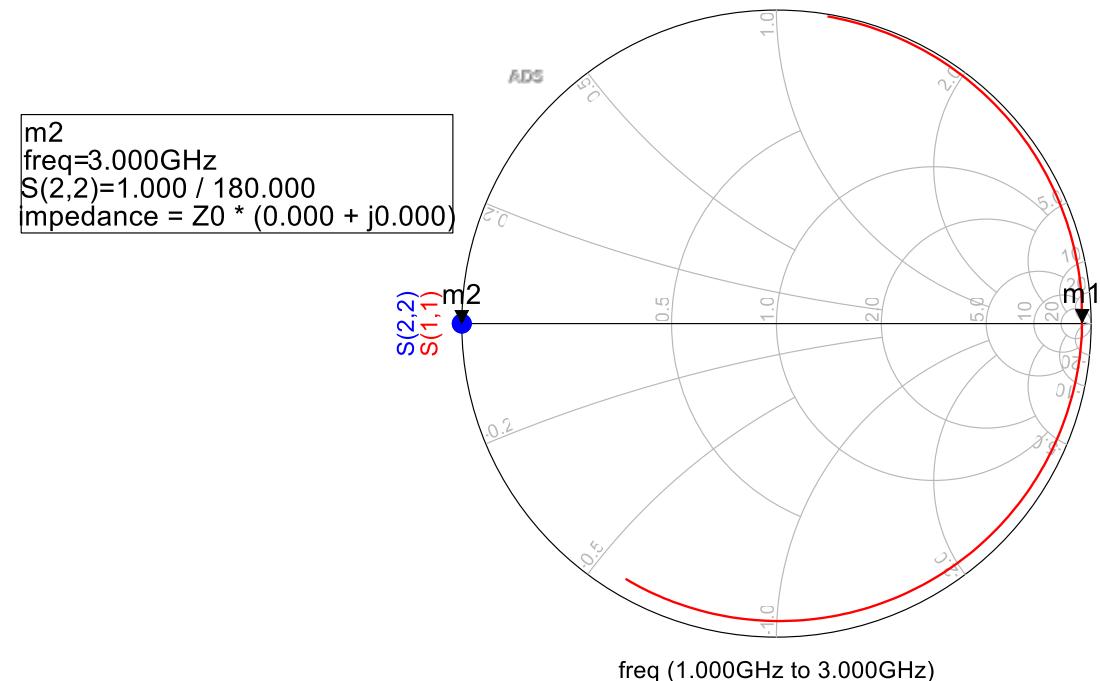
S_Param
SP1
Start=1.0 GHZ
Stop=3.0 GHZ
Step=0.01 GHZ



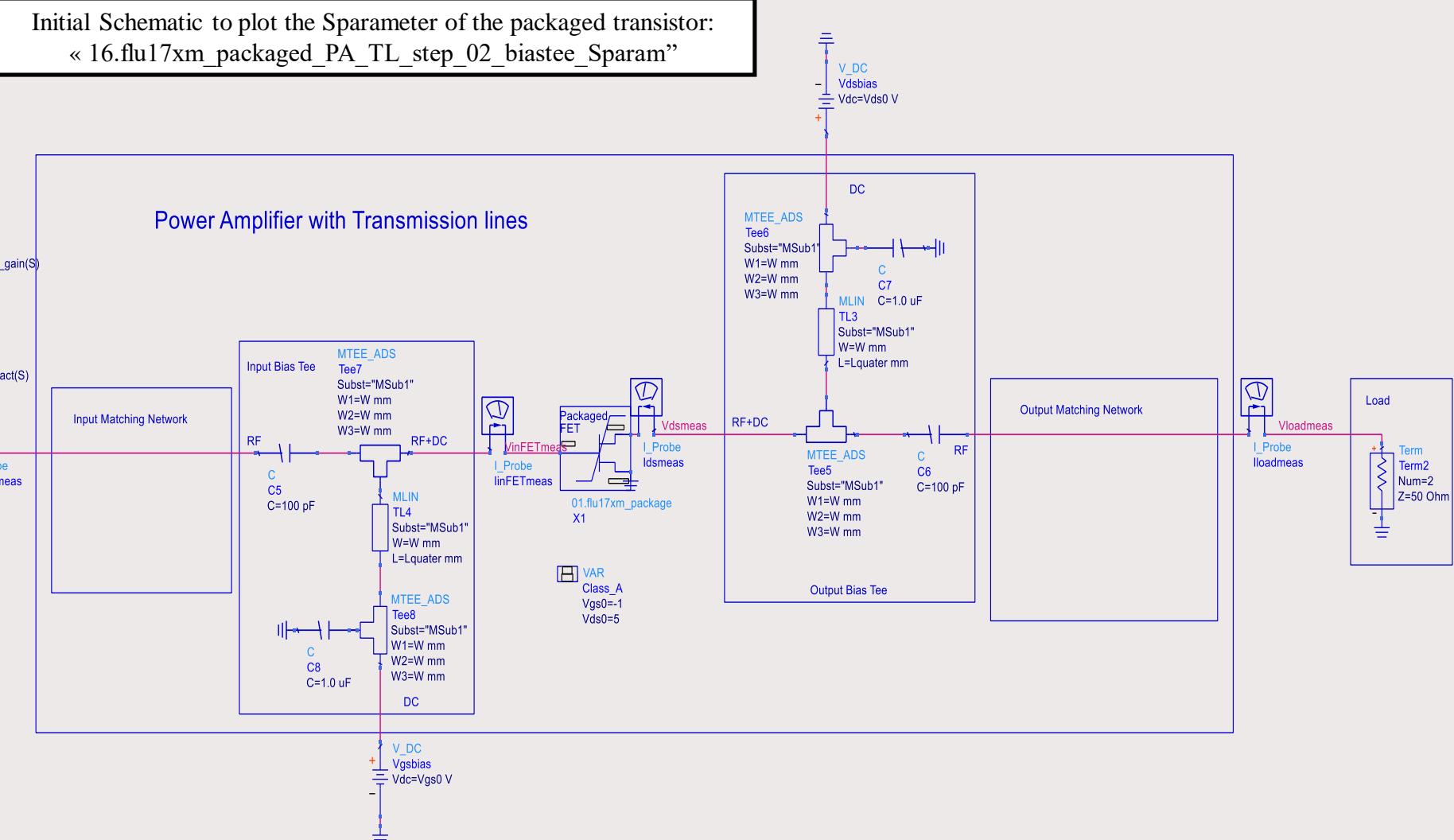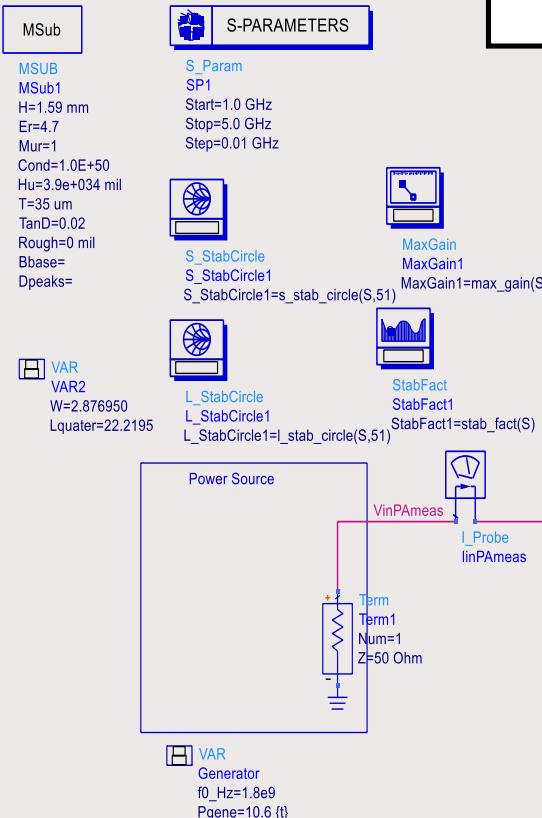

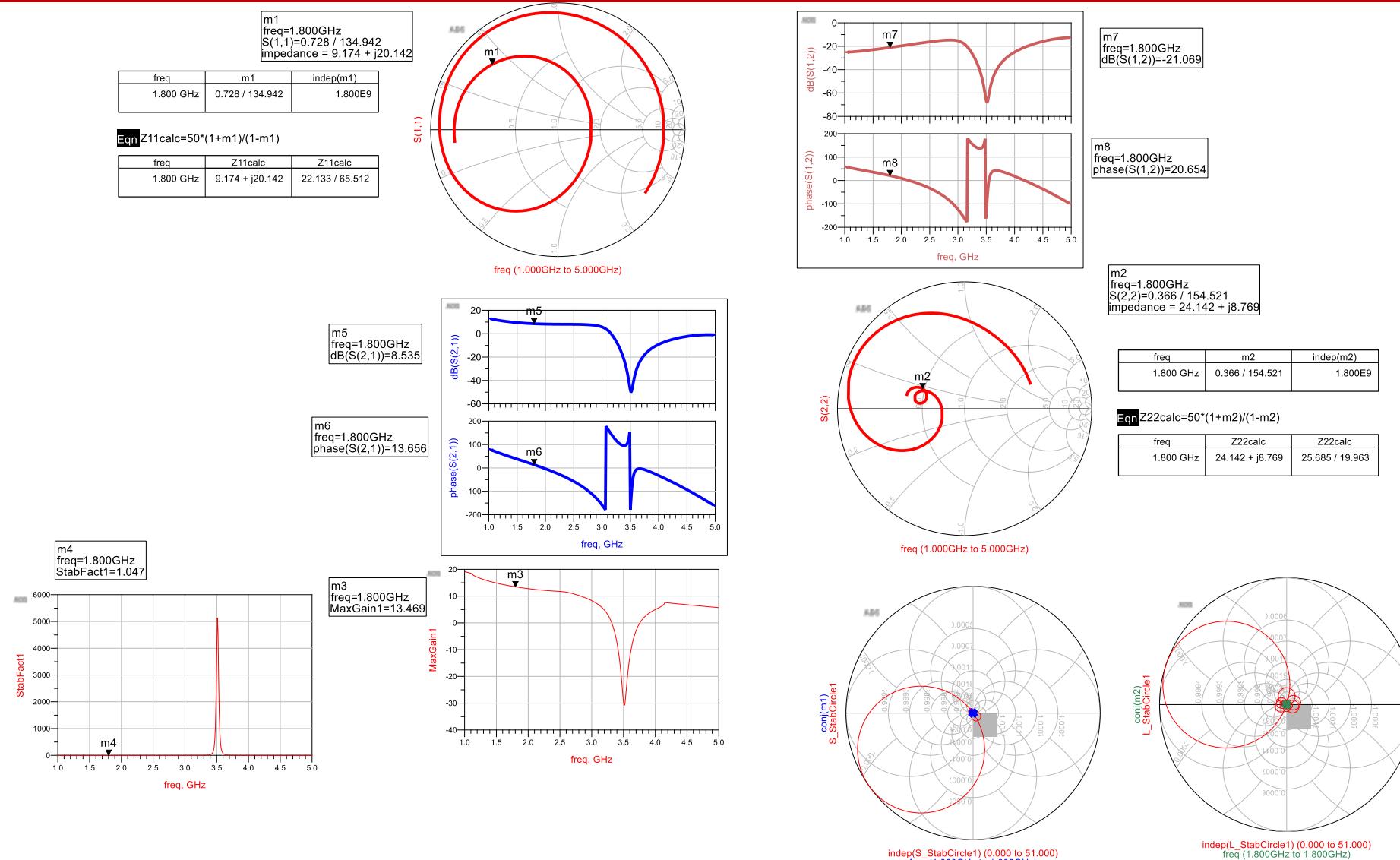

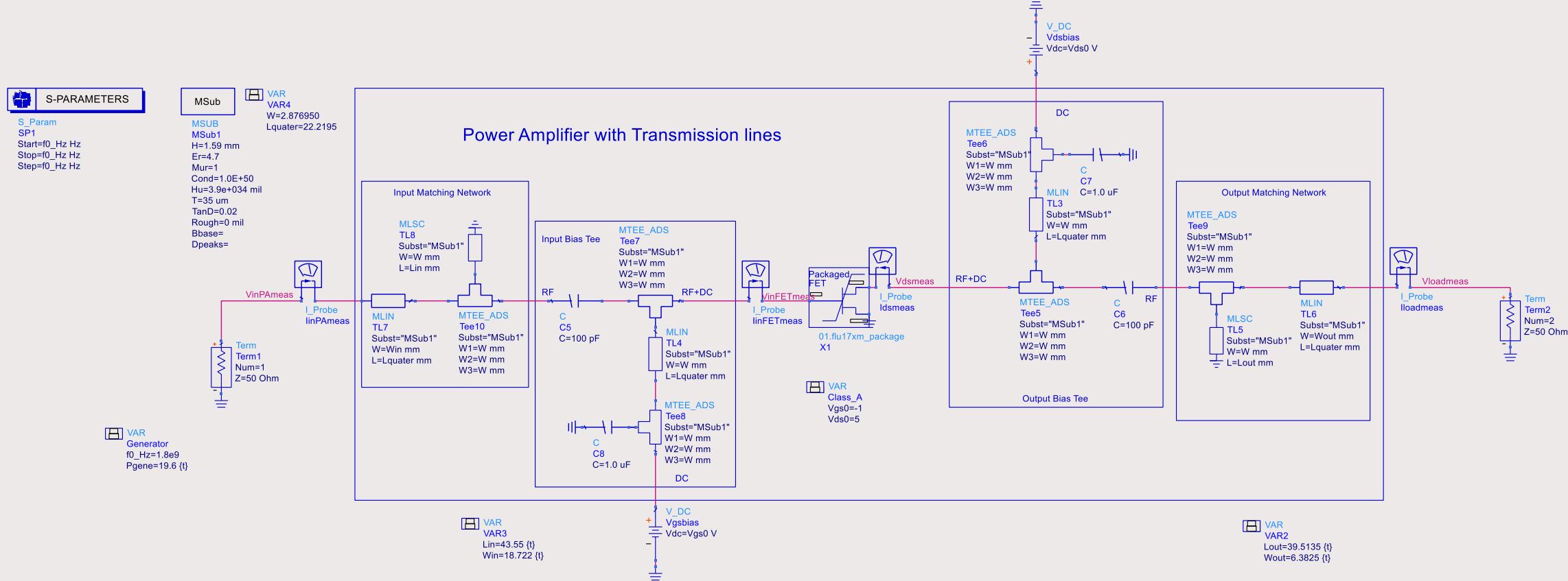
Final Schematic to design a linear PA : « 17.flu17xm_packaged_linear_PA_TL_final »



Results after the tuning
of the 4 parameters to
match the PA.

Method to tune the
parameters

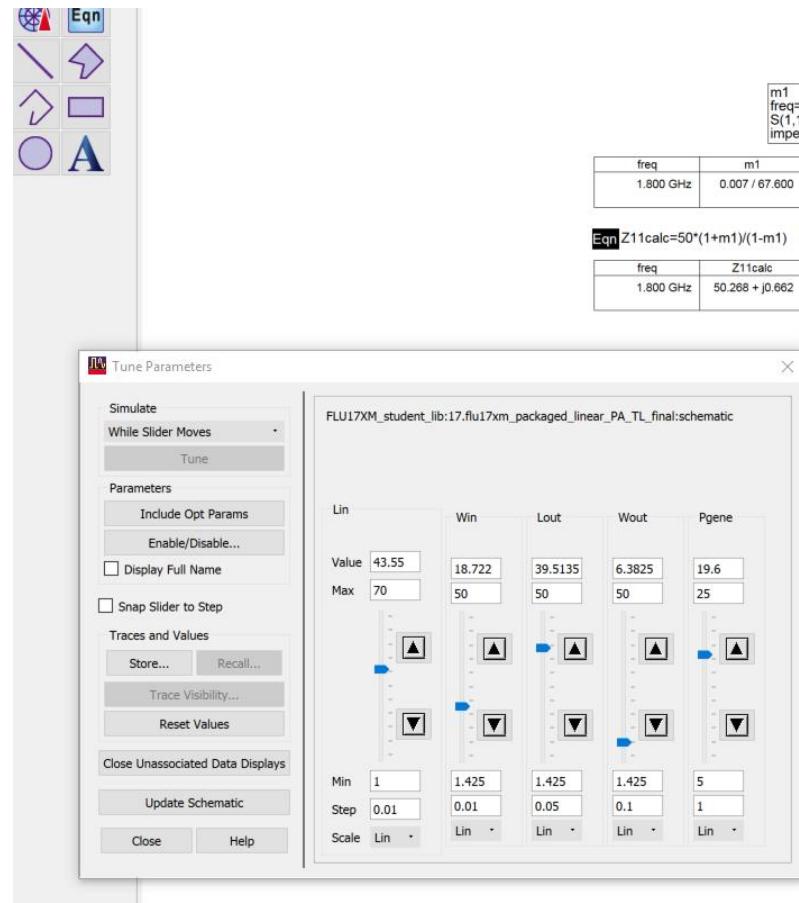
- 1) Tune first Lout
- 2) Tune Secondly Wout
- 3) Tune then Lin to cancel Imag(ZinPA)
- 4) Tune Secondly Win (To match ZinPA=50Ω)
- 5) Tune again Lout_H if required
- 6) Tune again Rout if required
- 7) Tune again Lin_H to cancel Imag(ZinPA)
- 8) Tune again Rin (To match ZinPA=50Ω)
- 9) Repeat again step 5 to 8 to better match the PA




m1
freq=1.800GHz
S(1,1)=0.007 / 67.600
impedance = 50.268 + j0.662

Eqn Z11calc=50*(1+m1)/(1-m1)

freq	Z11calc	Z11calc
1.800 GHz	50.268 + j0.662	50.272 / 0.754

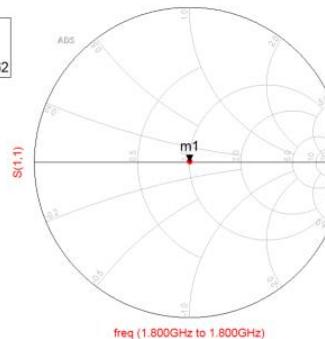


freq (1.800GHz to 1.800GHz)

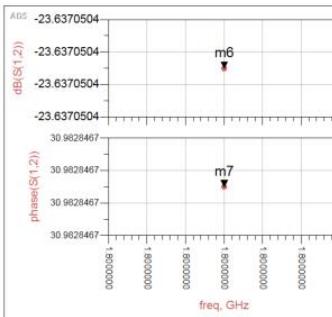

m6
freq=1.800GHz
dB(S(1,2))=-23.6370504


m7
freq=1.800GHz
phase(S(1,2))=30.983

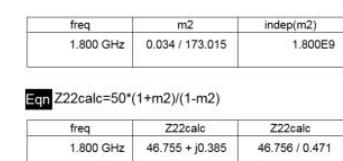m2
freq=1.800GHz
S(2,2)=0.034 / 173.015
impedance = 46.755 + j0.385




Eqn Z22calc=50*(1+m2)/(1-m2)


freq	Z22calc	Z22calc
1.800 GHz	46.755 + j0.385	46.756 / 0.471

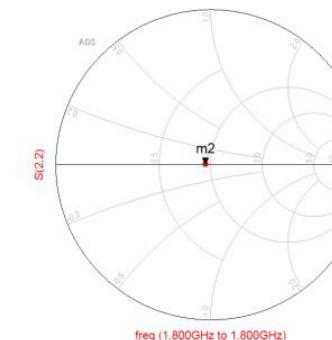

freq (1.800GHz to 1.800GHz)

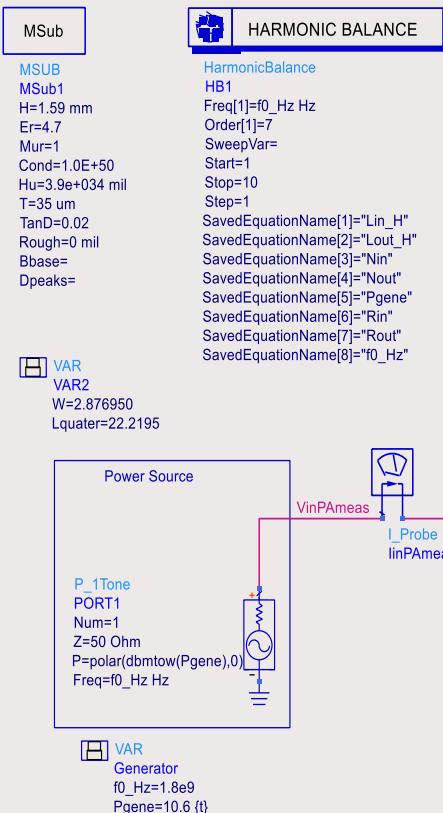

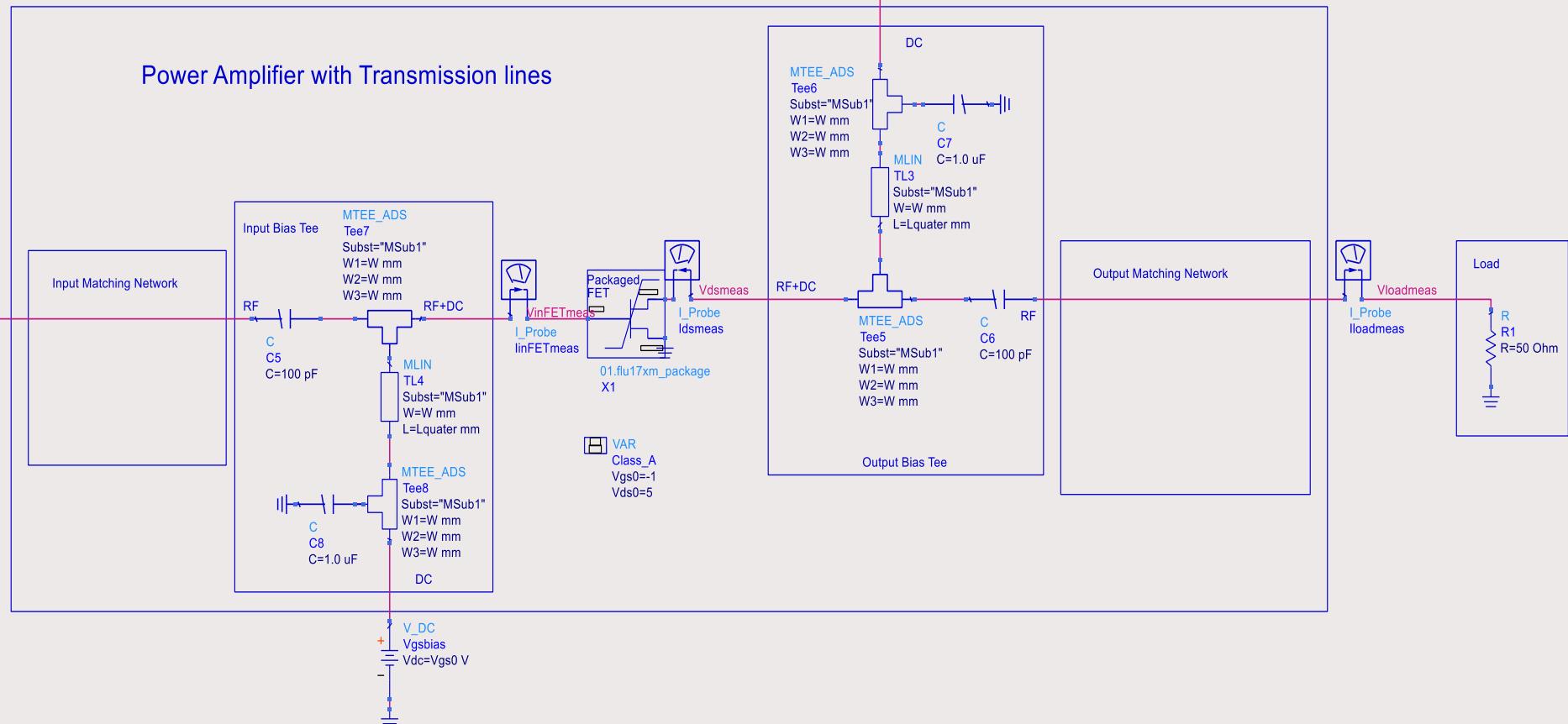Initial Schematic to design a Power PA :
 « 18.flu17xm_packaged_Power_PA_TL_final »



$$\text{Eqn } \text{VinPA_f0} = \text{VinPAmeas[1]}$$

$$\text{Eqn } \text{VoutPA_f0} = \text{Vloadmeas[1]}$$

$$\text{Eqn } \text{linPA_f0} = \text{linPAmeas.i[1]}$$

$$\text{Eqn } \text{loutPA_f0} = \text{lloadmeas.i[1]}$$

$$\text{Eqn } \text{PinPA_f0_mW} = 0.5 * 1000 * \text{real}(\text{VinPA_f0} * \text{conj}(\text{linPA_f0}))$$

$$\text{Eqn } \text{PinPA_f0_dBm} = 10 * \log10(\text{PinPA_f0_mW})$$

$$\text{Eqn } \text{GPA_f0} = \text{PoutPA_f0_mW} / \text{PinPA_f0_mW}$$

$$\text{Eqn } \text{GPA_f0_dB} = 10 * \log10(\text{GPA_f0})$$

$$\text{Eqn } \text{VinPA_DC} = \text{mag}(\text{VinFETmeas[0]}) \quad \text{Eqn } \text{linPA_DC} = \text{mag}(\text{linFETmeas.i[0]})$$

$$\text{Eqn } \text{VoutPA_DC} = \text{mag}(\text{Vdsmeas[0]}) \quad \text{Eqn } \text{loutPA_DC} = \text{mag}(\text{ldsmeas.i[0]})$$

$$\text{Eqn } \text{PoutPA_f0_mW} = 0.5 * 1000 * \text{real}(\text{VoutPA_f0} * \text{conj}(\text{loutPA_f0}))$$

$$\text{Eqn } \text{PoutPA_f0_dBm} = 10 * \log10(\text{PoutPA_f0_mW})$$

$$\text{Eqn } \text{PaddPA_f0_mW} = \text{PoutPA_f0_mW} - \text{PinPA_f0_mW}$$

$$\text{Eqn } \text{PaddPA_f0_dBm} = 10 * \log10(\text{PaddPA_f0_mW})$$

$$\text{Eqn } \text{ZinFET_f0} = \text{VinFETmeas[1]} / \text{linFETmeas.i[1]}$$




$$\text{Eqn } \text{ZinPA_f0} = \text{VinPAmeas[1]} / \text{linPAmeas.i[1]}$$

$$\text{Eqn } \text{GamainFET_f0} = (\text{ZinFET_f0} - 50) / (\text{ZinFET_f0} + 50)$$

$$\text{Eqn } \text{GamainPA_f0} = (\text{ZinPA_f0} - 50) / (\text{ZinPA_f0} + 50)$$

PinPA_f0_mW	PoutPA_f0_mW	GPA_f0	PDC_mW	Drain_Efficiency	PAE
5.381	81.252	15.099	1548.953	5.246	4.898

PinPA_f0_dBm	PoutPA_f0_dBm	GPA_f0_dB	PDC_mW	Drain_Efficiency	PAE
7.309	19.098	11.790	1548.953	5.246	4.898

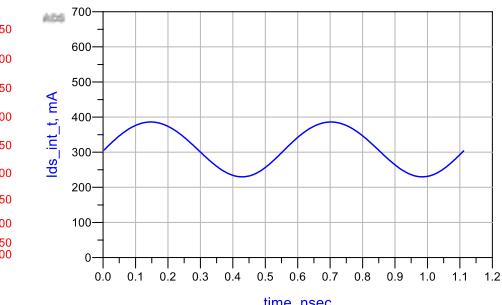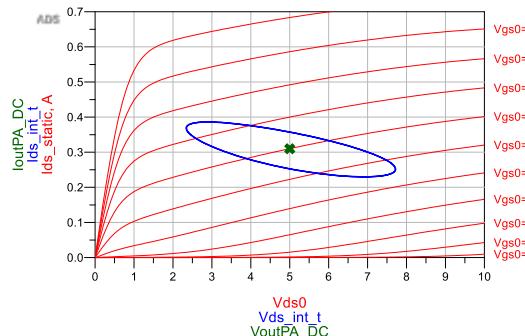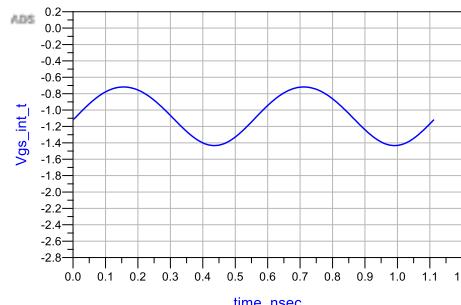

$$\text{Eqn } \text{ids_static} = \text{"_06.analyseDCext".Ids_int.i}$$



$$\text{Eqn } \text{time_s} = \text{ts(freq)}$$

$$\text{Eqn } \text{Vds_int} = \text{Vdint-Vsintd}$$

$$\text{Eqn } \text{Vds_int_t} = \text{ts(Vds_int)}$$

$$\text{Eqn } \text{Vgs_int_t} = \text{ts(Vgint-Vsintg)}$$

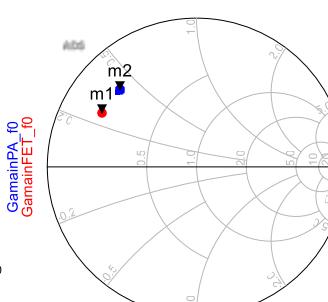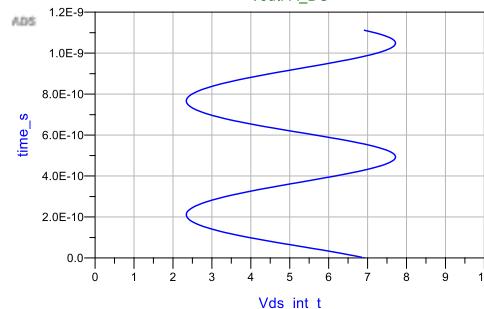
$$\text{Eqn } \text{Ids_int_t} = \text{ts(Ids_int.i)}$$



m1
indep(m1)=0
GamainFET_f0=0.729 / 150.212
impedance = $Z_0 * (0.167 + j0.259)$

m2
indep(m2)=0
GamainPA_f0=0.729 / 134.772
impedance = $Z_0 * (0.183 + j0.405)$

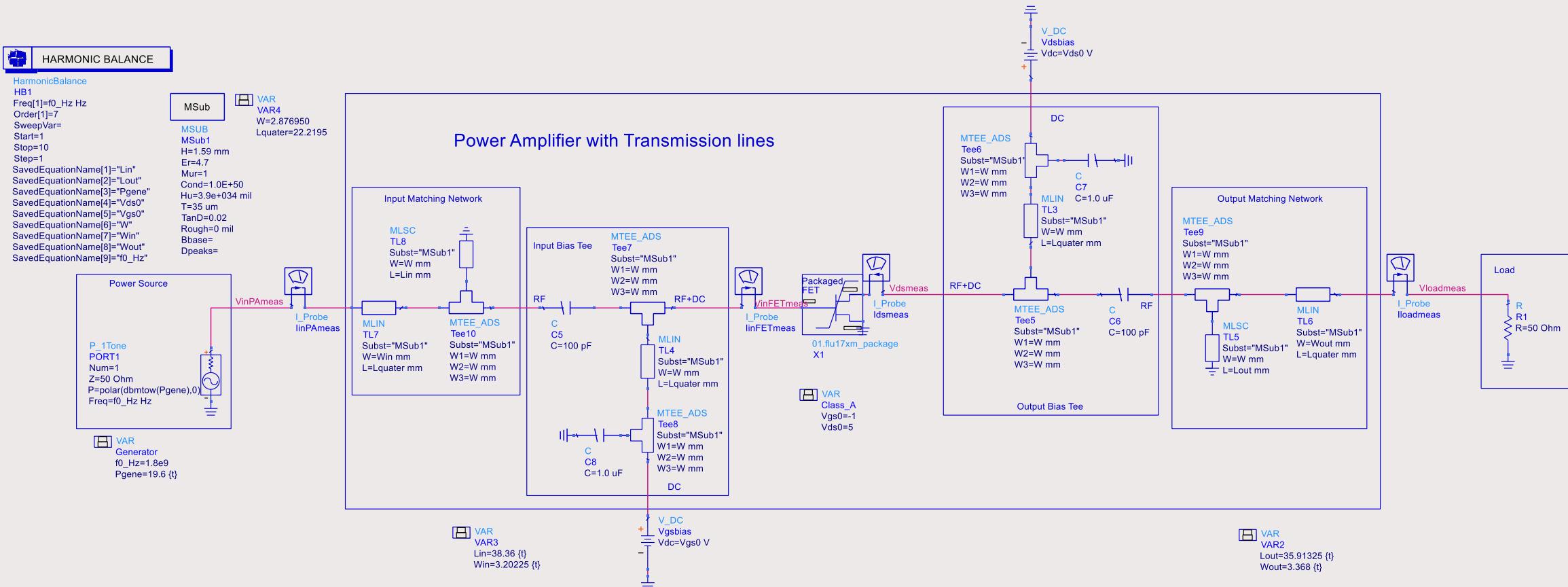Final Schematic to design a Power PA : « 18.flu17xm_packaged_Power_PA_TL_final »



E(rasmus) Mundus on Innovative Microwave Electronics and Optics


Results after the tuning of the 5 parameters to maximise the output power of the PA.

Method to tune the parameters

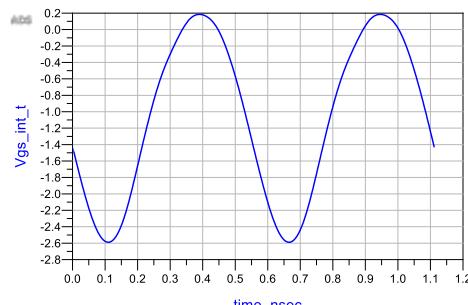- 1) Tune first Lout
- 2) Tune Secondly Wout
- 3) Modify Pgene if required
- 4) Tune again Lout
- 5) Tune again Wout
- 6) Tune then Lin to cancel Imag(ZinPA)
- 7) Tune Secondly Win (To match ZinPA=50Ω)
- 8) Modify Pgene if required
- 9) Tune again Lout_H if required
- 10) Tune again Rout if required
- 11) Tune again Lin_H to cancel Imag(ZinPA)
- 12) Tune again Rin (To match ZinPA=50Ω)
- 13) Repeat again step 8 to 12 to maximise the Gain or the output power or the PAE

$$\begin{aligned}
 & \text{Eqn } \text{VinPA_f0} = \text{VinPAmeas[1]} \\
 & \text{Eqn } \text{loutPA_f0} = \text{loutPAmeas.i[1]} \\
 & \text{Eqn } \text{VoutPA_f0} = \text{Vloadmeas[1]} \\
 & \text{Eqn } \text{loutPA_DC} = \text{mag(loutPAmeas.i[0])} \\
 & \text{Eqn } \text{VoutPA_DC} = \text{mag(Vdsmeas[0])} \\
 & \text{Eqn } \text{PinPA_f0_mW} = 0.5 * 1000 * \text{real}(\text{VinPA_f0} * \text{conj}(\text{loutPA_f0})) \\
 & \text{Eqn } \text{PinPA_f0_dBm} = 10 * \log_{10}(\text{PinPA_f0_mW}) \\
 & \text{Eqn } \text{PoutPA_f0_mW} = 0.5 * 1000 * \text{real}(\text{VoutPA_f0} * \text{conj}(\text{loutPA_f0})) \\
 & \text{Eqn } \text{PoutPA_f0_dBm} = 10 * \log_{10}(\text{PoutPA_f0_mW}) \\
 & \text{Eqn } \text{PDC_mW} = 1000 * (\text{VinPA_DC} * \text{loutPA_DC} + \text{VoutPA_DC} * \text{loutPA_DC}) \\
 & \text{Eqn } \text{GPA_f0} = \text{PoutPA_f0_mW} / \text{PinPA_f0_mW} \\
 & \text{Eqn } \text{GPA_f0_dB} = 10 * \log_{10}(\text{GPA_f0}) \\
 & \text{Eqn } \text{PaddPA_f0_mW} = \text{PoutPA_f0_mW} - \text{PinPA_f0_mW} \\
 & \text{Eqn } \text{PaddPA_f0_dBm} = 10 * \log_{10}(\text{PaddPA_f0_mW}) \\
 & \text{Eqn } \text{Drain_Efficiency} = \text{PoutPA_f0_mW} / \text{PDC_mW} * 100 \\
 & \text{Eqn } \text{PAE} = \text{PaddPA_f0_mW} / \text{PDC_mW} * 100
 \end{aligned}$$




$$\begin{aligned}
 & \text{Eqn } \text{ZinFET_f0} = \text{VinFETmeas[1]} / \text{linFETmeas.i[1]} \\
 & \text{Eqn } \text{ZinPA_f0} = \text{VinPAmeas[1]} / \text{linPAmeas.i[1]} \\
 & \text{Eqn } \text{GamainFET_f0} = (\text{ZinFET_f0} - 50) / (\text{ZinFET_f0} + 50) \\
 & \text{Eqn } \text{GamainPA_f0} = (\text{ZinPA_f0} - 50) / (\text{ZinPA_f0} + 50)
 \end{aligned}$$



$$\begin{aligned}
 & \text{Eqn } \text{ds_static} = \text{"_06.analyseDCext".Ids_int.i} \\
 & \text{Eqn } \text{time_s} = \text{ts(freq)} \\
 & \text{Eqn } \text{Vds_int} = \text{Vdint} - \text{Vsintd} \\
 & \text{Eqn } \text{Vds_int_t} = \text{ts(Vds_int)} \\
 & \text{Eqn } \text{Vgs_int_t} = \text{ts(Vgint} - \text{Vsintg)} \\
 & \text{Eqn } \text{Ids_int_t} = \text{ts(Ids_int.i)}
 \end{aligned}$$


PinPA_f0_mW	PoutPA_f0_mW	GPA_f0	PDC_mW	Drain_Efficiency	PAE
91.201	851.197	9.333	1580.144	53.868	48.097

PinPA_f0_dBm	PoutPA_f0_dBm	GPA_f0_dB	PDC_mW	Drain_Efficiency	PAE
19.600	29.300	9.700	1580.144	53.868	48.097

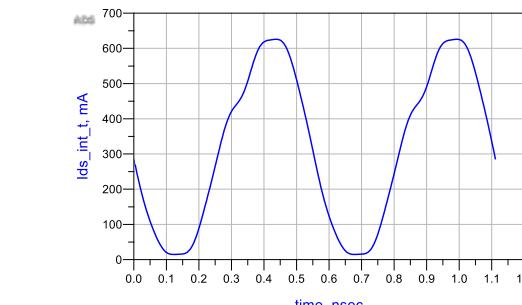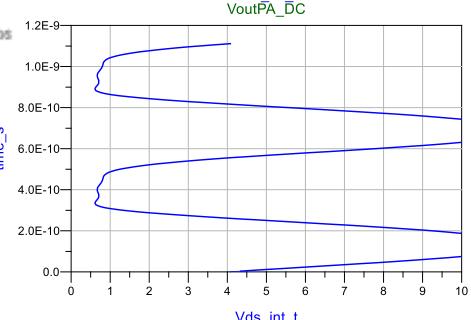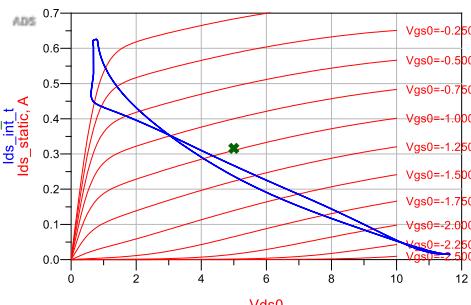

$$\begin{aligned}
 & \text{ZinFET_f0} & \text{GamainFET_f0} \\
 & 9.197 + j9.053 & 0.698 / 158.795
 \end{aligned}$$

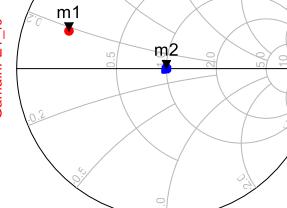
$$\begin{aligned}
 & \text{ZinPA_f0} & \text{GamainPA_f0} \\
 & 50.017 - j0.011 & 2.058E-4 / -32.816
 \end{aligned}$$



$$\begin{aligned}
 & m1 \\
 & \text{indep}(m1)=0 \\
 & \text{GamainFET_f0}=0.698 / 158.795 \\
 & \text{Impedance} = Z_0 * (0.184 + j0.181)
 \end{aligned}$$


$$\begin{aligned}
 & m2 \\
 & \text{indep}(m2)=0 \\
 & \text{GamainPA_f0}=2.058E-4 / -32.816 \\
 & \text{Impedance} = Z_0 * (1.000 - j2.231E-4)
 \end{aligned}$$

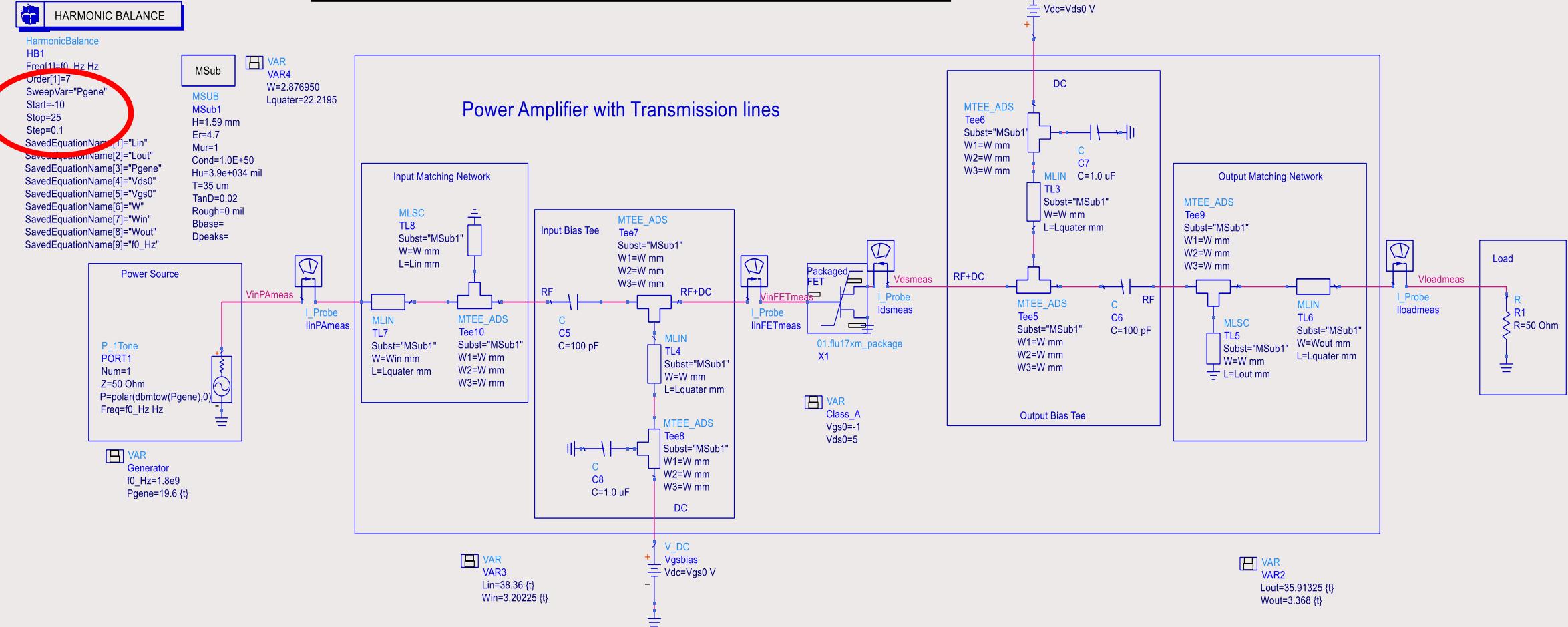Schematic to plot the power characteristics of the designed Power PA :
 « 18.flu17xm_packaged_Power_PA_TL_final »





Eqn VinPA_f0=VinPAmeas[1]	Eqn linPA_f0=linPAmeas.i[1]	Eqn PinPA_f0_mW=0.5*1000*real(VinPA_f0*conj(linPA_f0))	Eqn GPA_f0=PoutPA_f0_mW/PinPA_f0_mW
Eqn VoutPA_f0=Vloadmeas[1]	Eqn loutPA_f0=lloadmeas.i[1]	Eqn PinPA_f0_dBm=10*log10(PinPA_f0_mW)	Eqn GPA_f0_dB=10*log10(GPA_f0)
Eqn VinPA_DC=mag(VinFETmeas[0])	Eqn linPA_DC=mag(linFETmeas.i[0])	Eqn PoutPA_f0_mW=0.5*1000*real(VoutPA_f0*conj(loutPA_f0))	Eqn PaddPA_f0_mW=PoutPA_f0_mW-PinPA_f0_mW
Eqn VoutPA_DC=mag(Vdsmeas[0])	Eqn loutPA_DC=mag(ldsmeas.i[0])	Eqn PoutPA_f0_dBm=10*log10(PoutPA_f0_mW)	Eqn PaddPA_f0_dBm=10*log10(PaddPA_f0_mW)
		Eqn PDC_mW=1000*(VinPA_DC*linPA_DC+VoutPA_DC*loutPA_DC)	Eqn Drain_Efficiency=PoutPA_f0_mW/PDC_mW*100
			Eqn PAE=PaddPA_f0_mW/PDC_mW*100

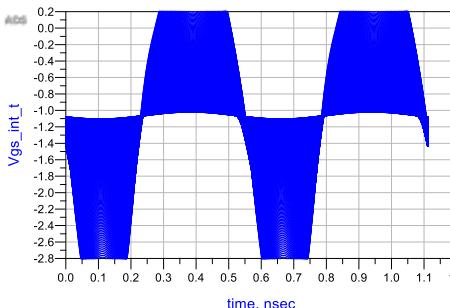Eqn ZinFET_f0=VinFETmeas[1]/linFETmeas.i[1]
Eqn ZinPA_f0=VinPAmeas[1]/linPAmeas.i[1]
Eqn GamainFET_f0=(ZinFET_f0-50)/(ZinFET_f0+50)
Eqn GamainPA_f0=(ZinPA_f0-50)/(ZinPA_f0+50)





Pgene	PinPA_f0_mW	...tPA_f0_mW	GPA_f0	PDC_mW	...in_Efficiency	PAE
-10.000	0.100	1.112	11.174	1550.420	0.072	0.065

Pgene	...PA_f0_dBm	...tPA_f0_dBm	GPA_f0_dB	PDC_mW	...in_Efficiency	PAE
-10.000	-10.021	0.461	10.482	1550.420	0.072	0.065

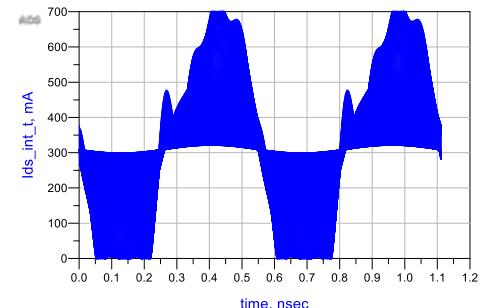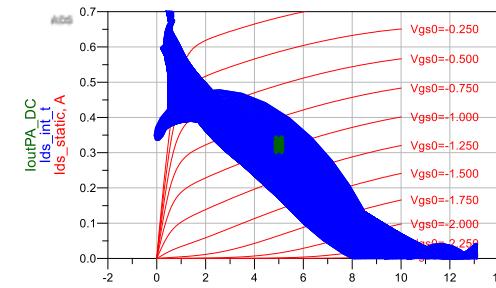







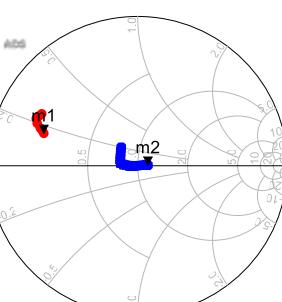
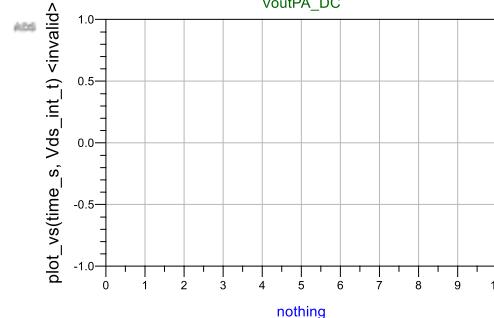
Eqn Ids_static="_06.analyseDCext"..Ids_int.i
Eqn time_s=ts(freq)
Eqn Vds_int=Vdint-Vsintd
Eqn Vds_int_t=ts(Vds_int)
Eqn Vgs_int_t=ts(Vgint-Vsintg)
Eqn Ids_int_t=ts(Ids_int.i)




m1 Pgene=-1.879E-14 GamainFET_f0=0.663 / 160.907 impedance = Z0 * (0.208 + j0.161)	m2 Pgene=1.879E-14 GamainPA_f0=0.068 / 2.946 impedance = Z0 * (1.147 + j0.008)
---	---


Pgene	ZinFET_f0	...ainFET_f0
-10.000	10.409 + j8...	0.663 / 160...
-9.900	10.409 + j8...	0.663 / 160...


Pgene	ZinPA_f0	...mainPA_f0
-10.000	57.370 + j0...	0.069 / 2.855
-9.900	57.370 + j0...	0.069 / 2.855

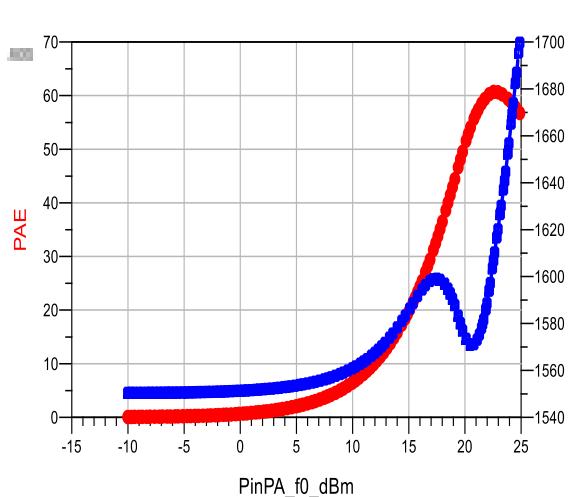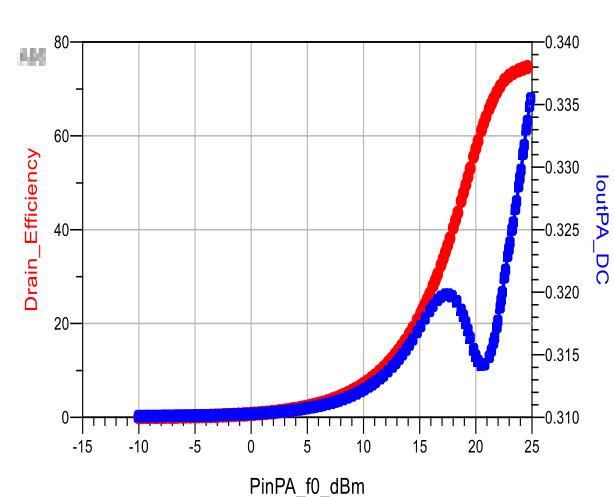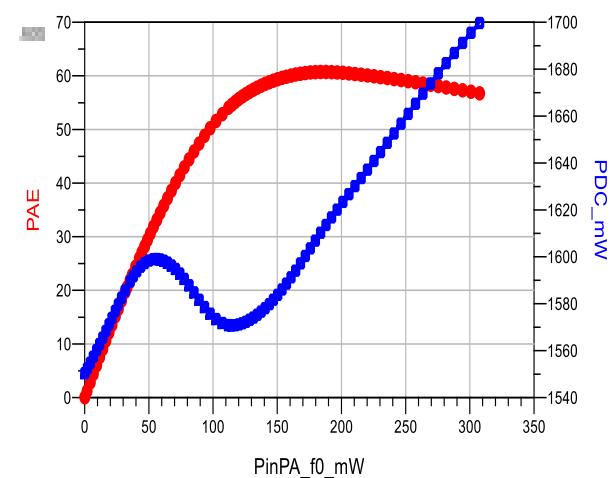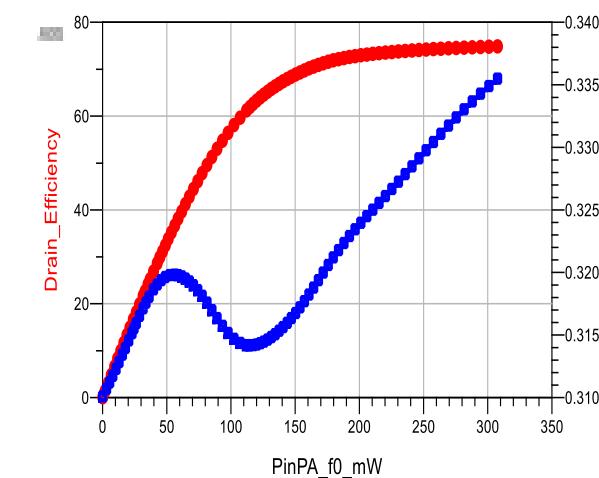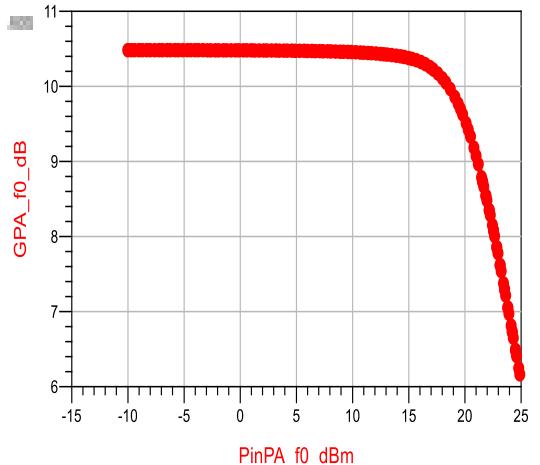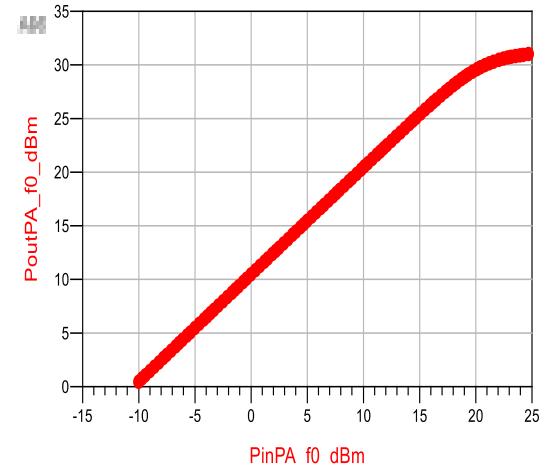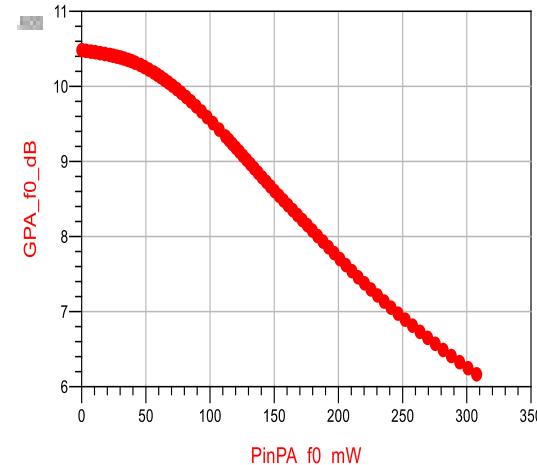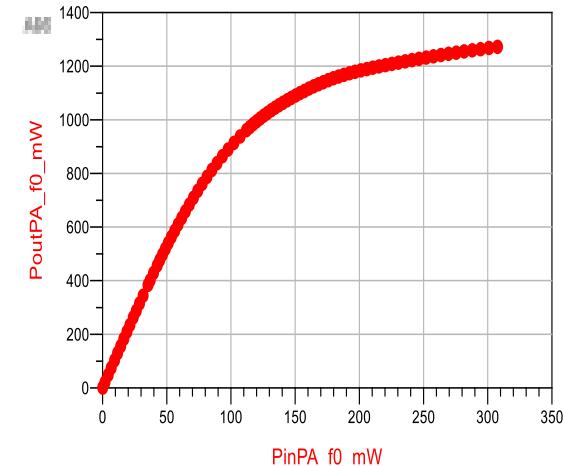


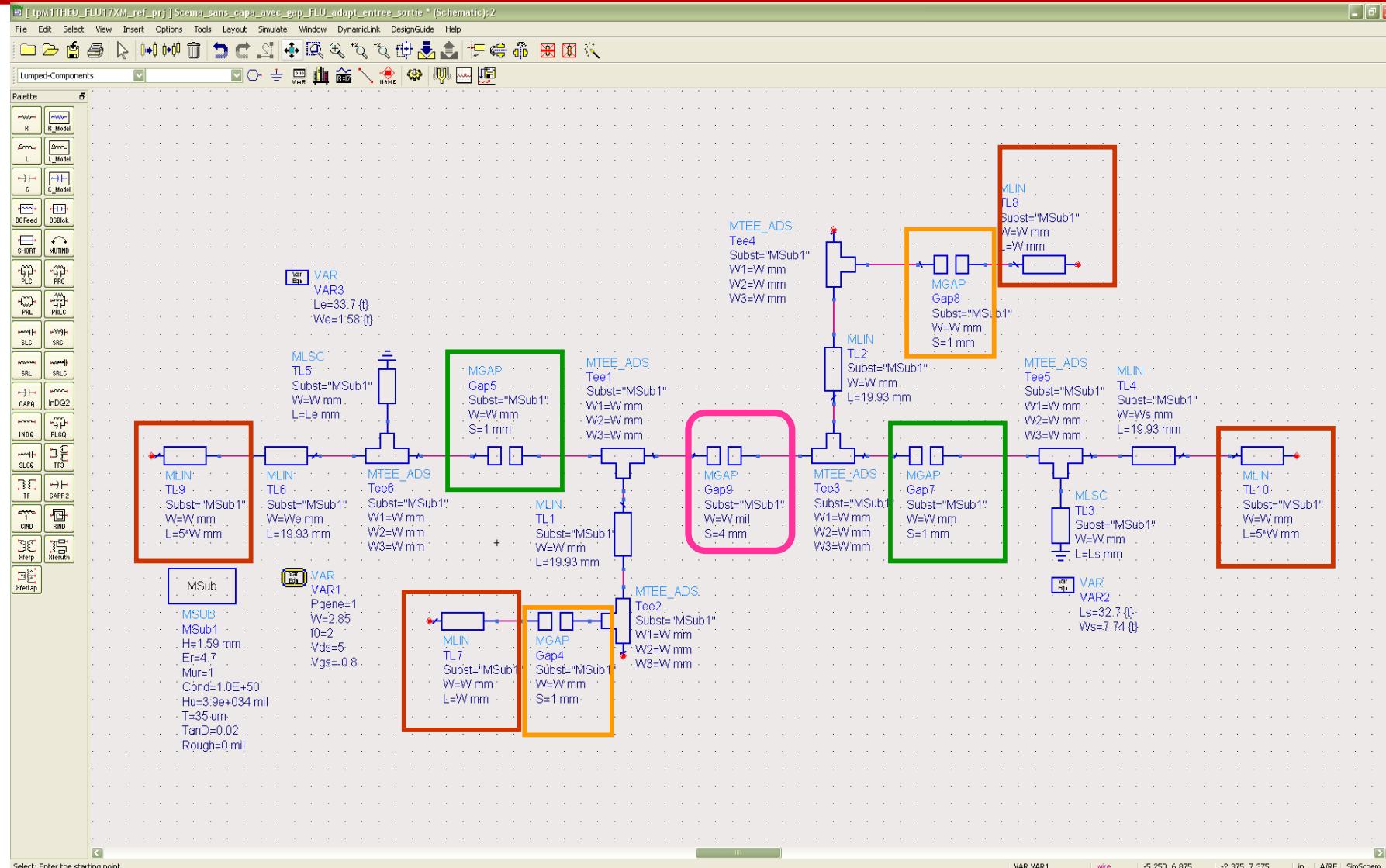Layout of the PA Design with the packaged transistor and transmission Lines



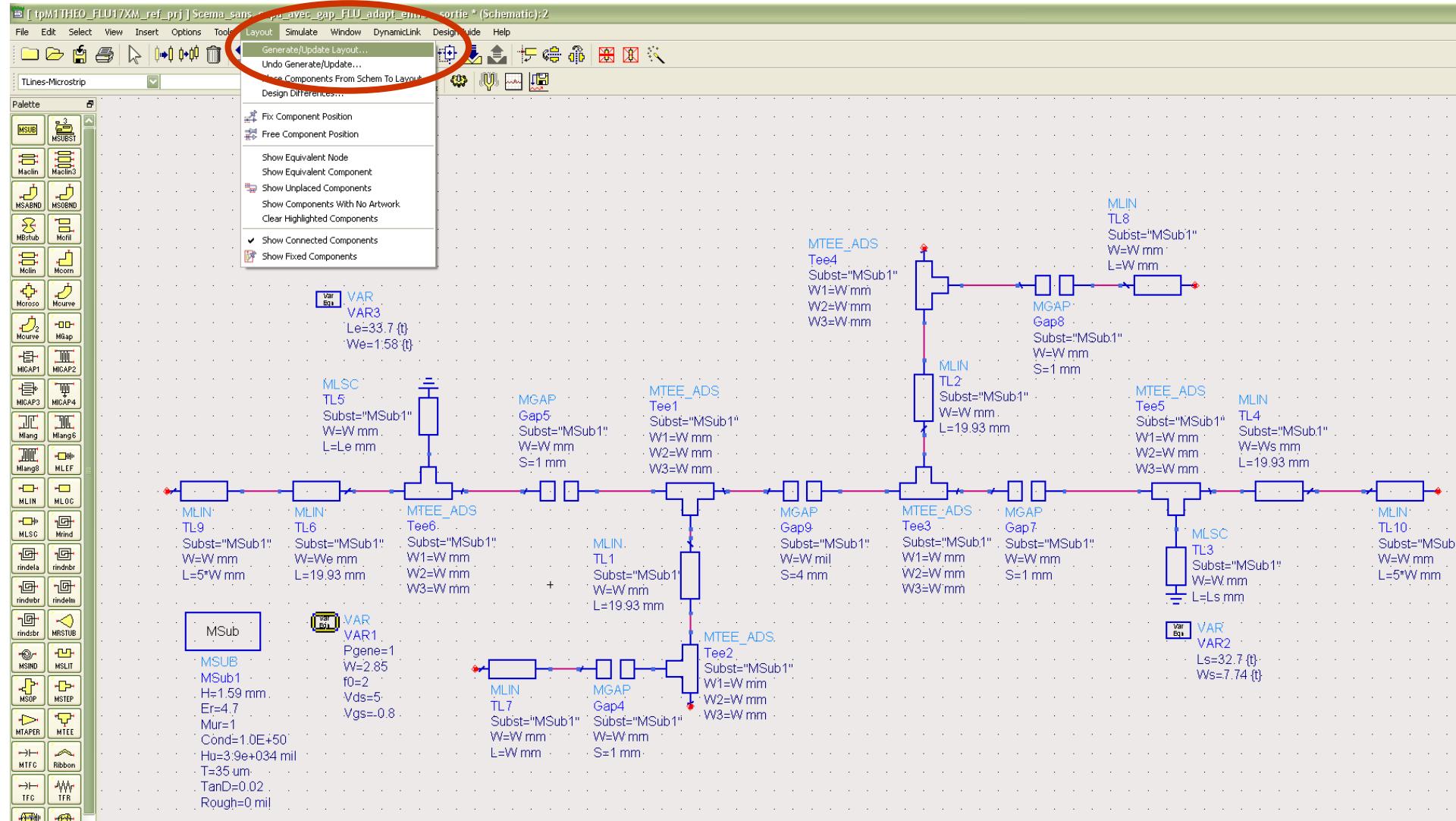

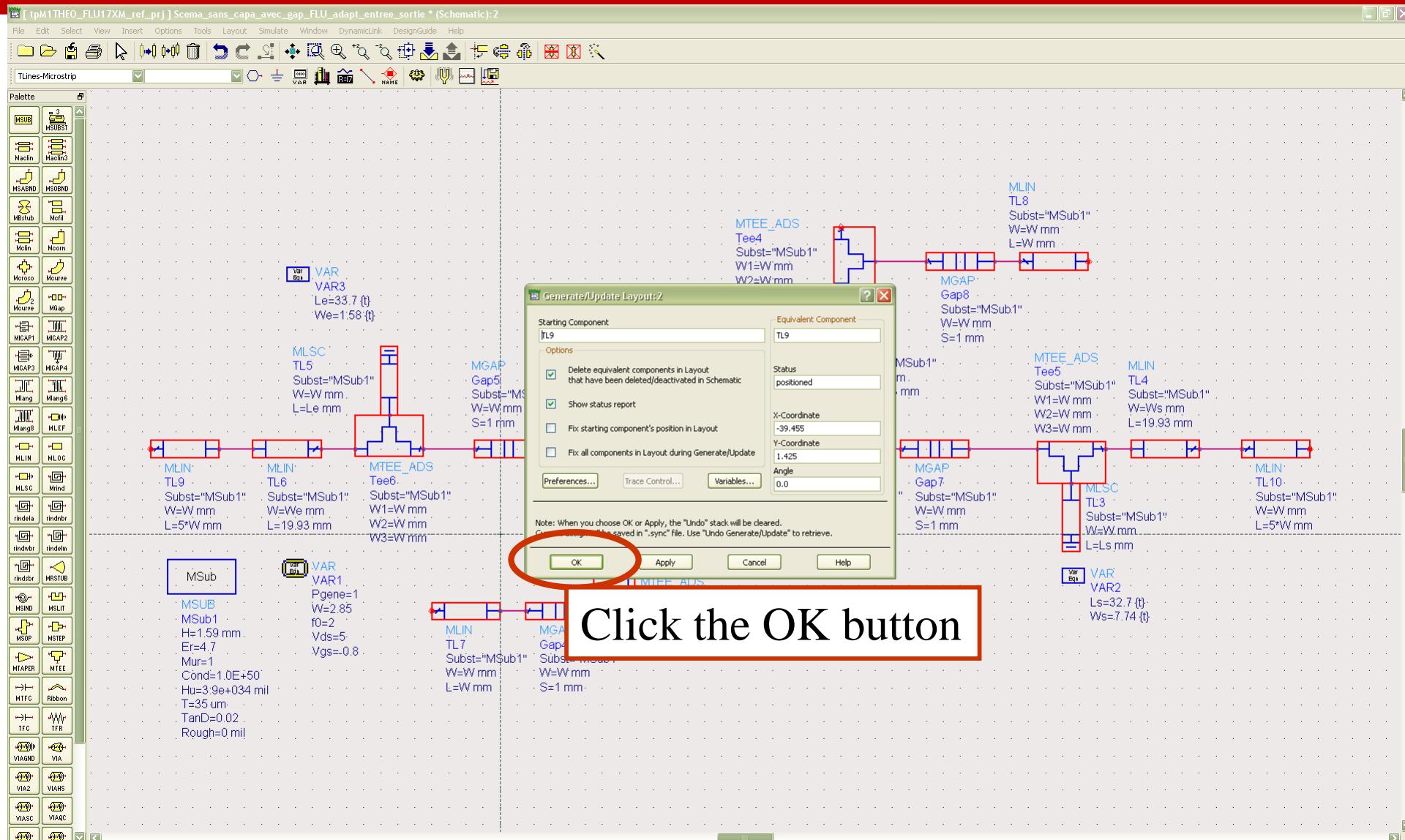


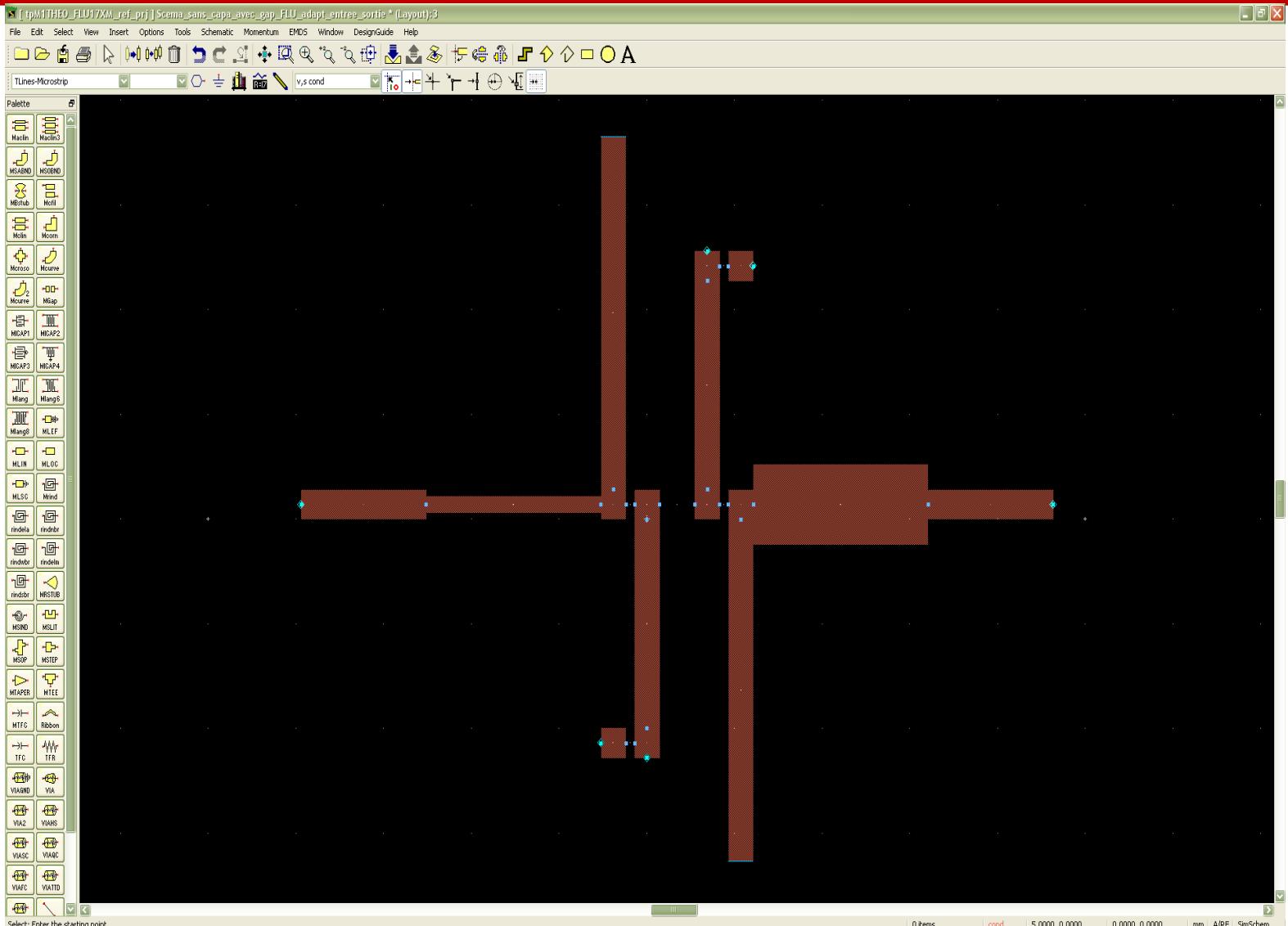



Basics of Active and Non-Linear Electronics : PW


Date _____


- 52 -

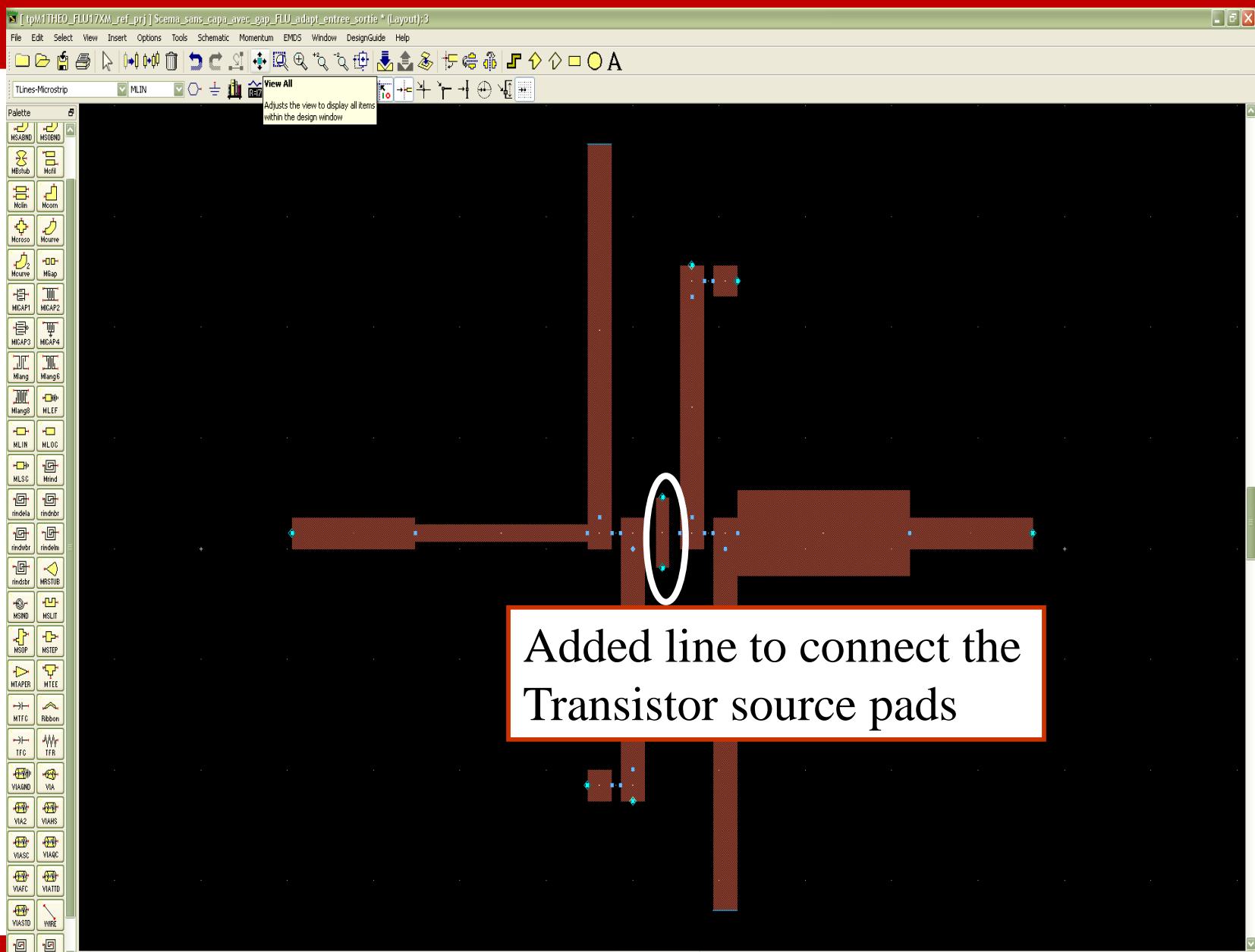



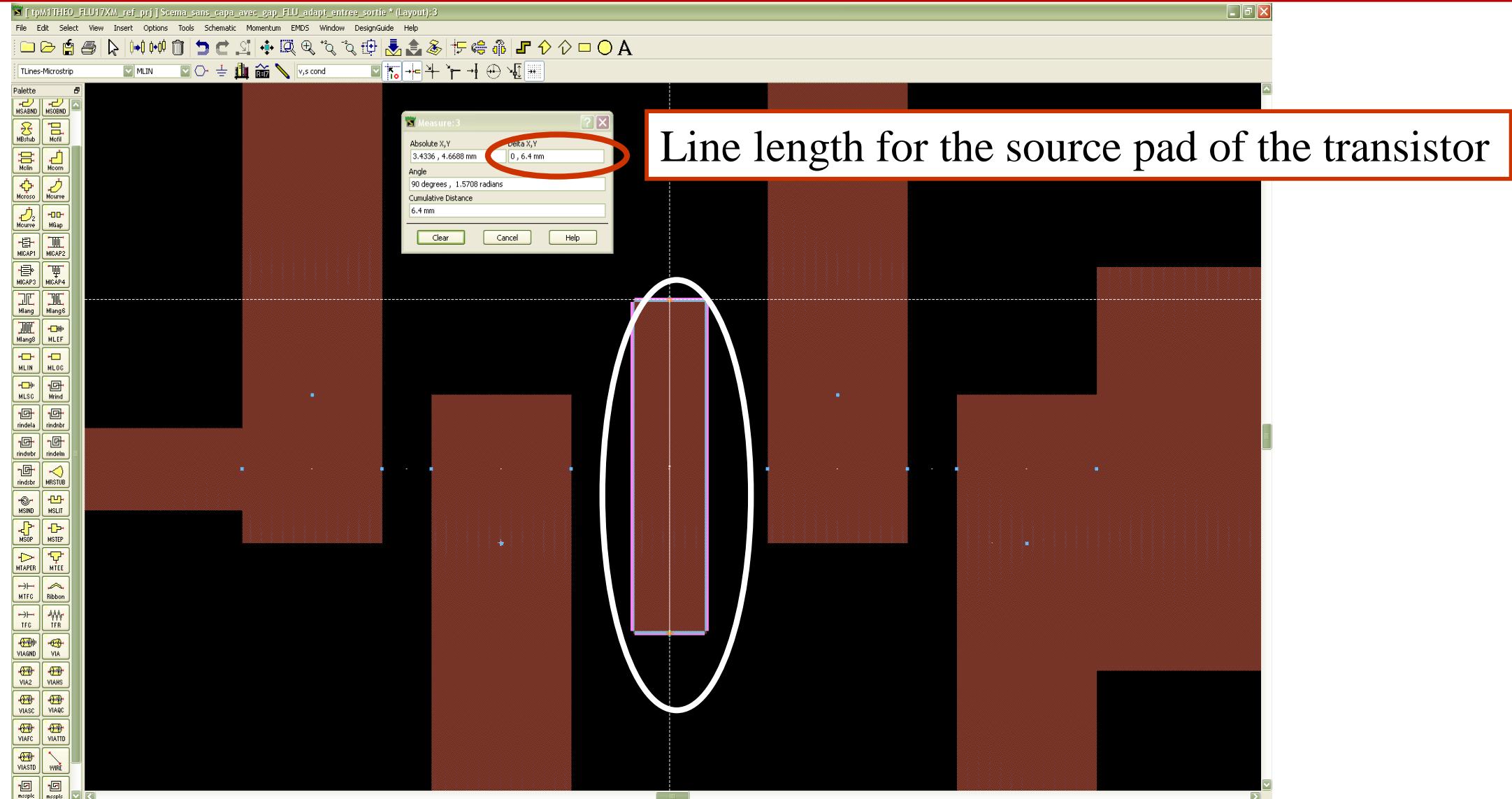


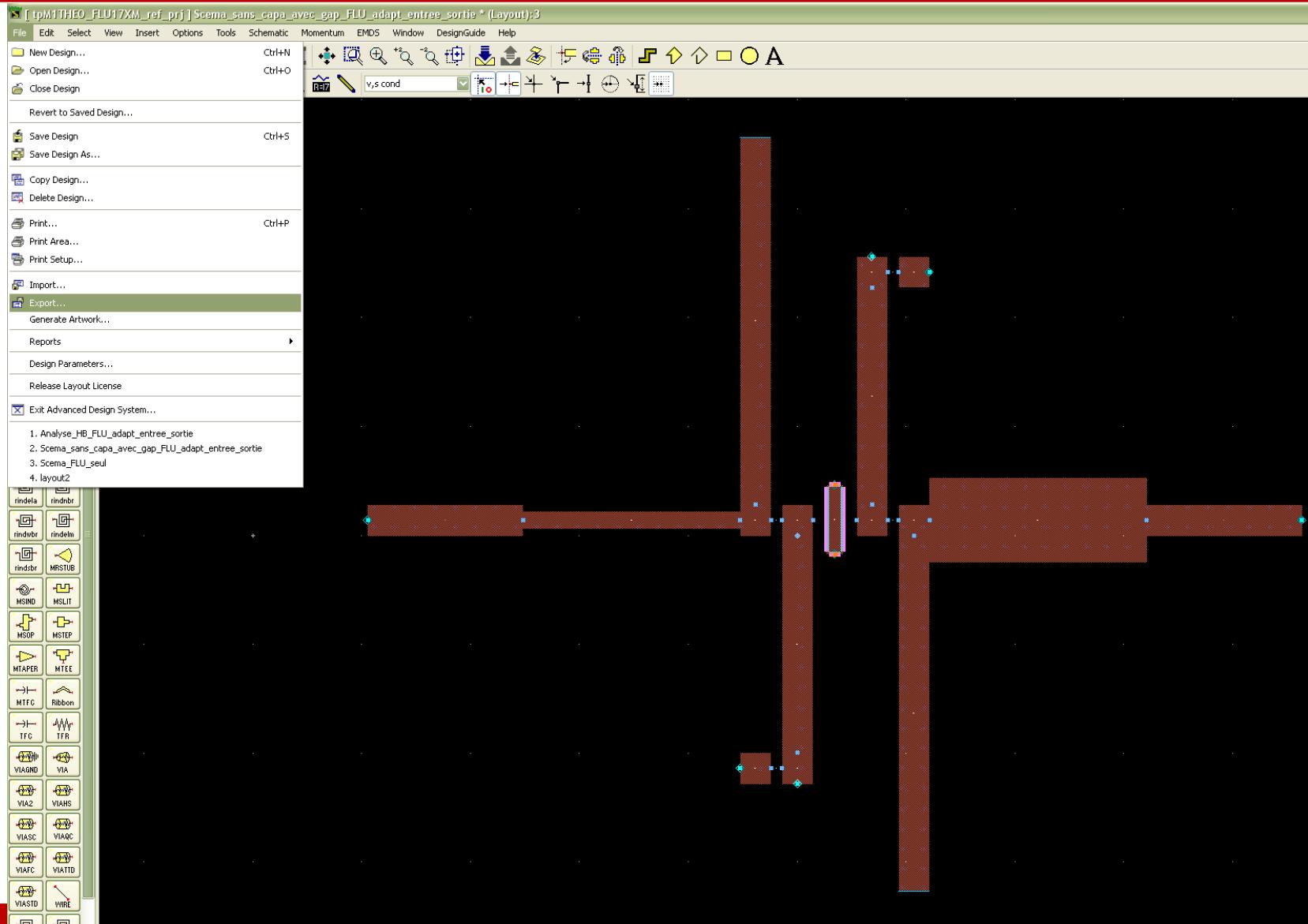


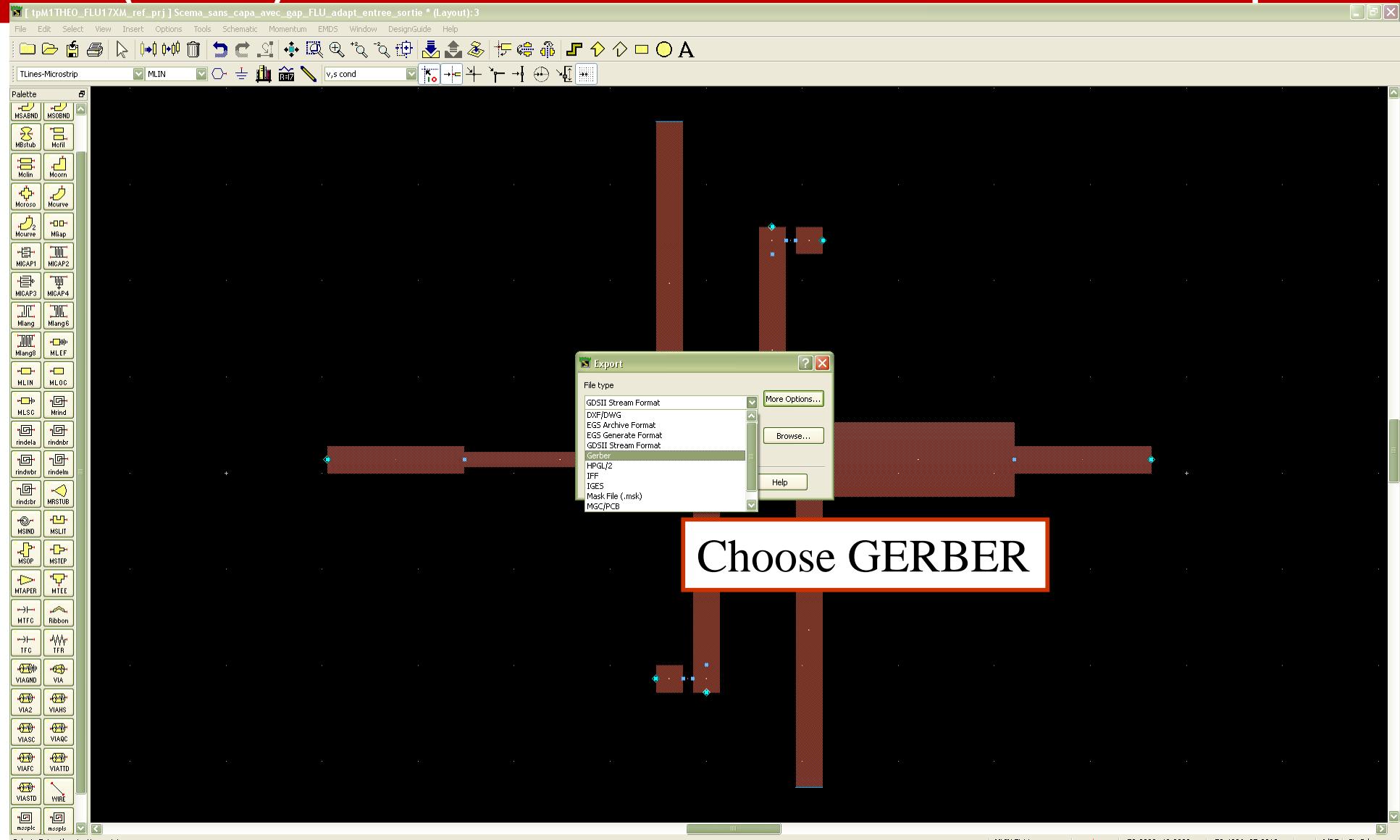

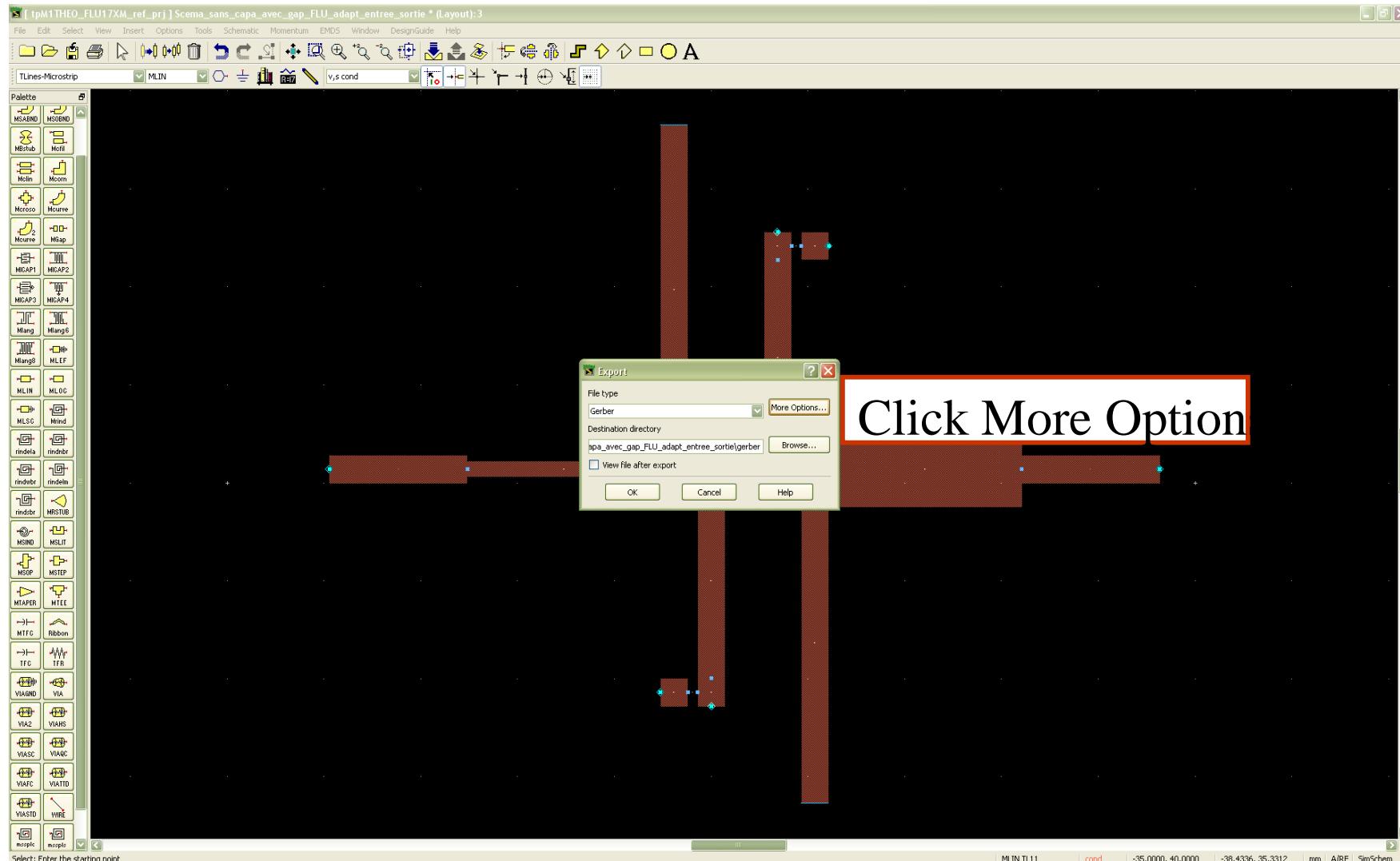

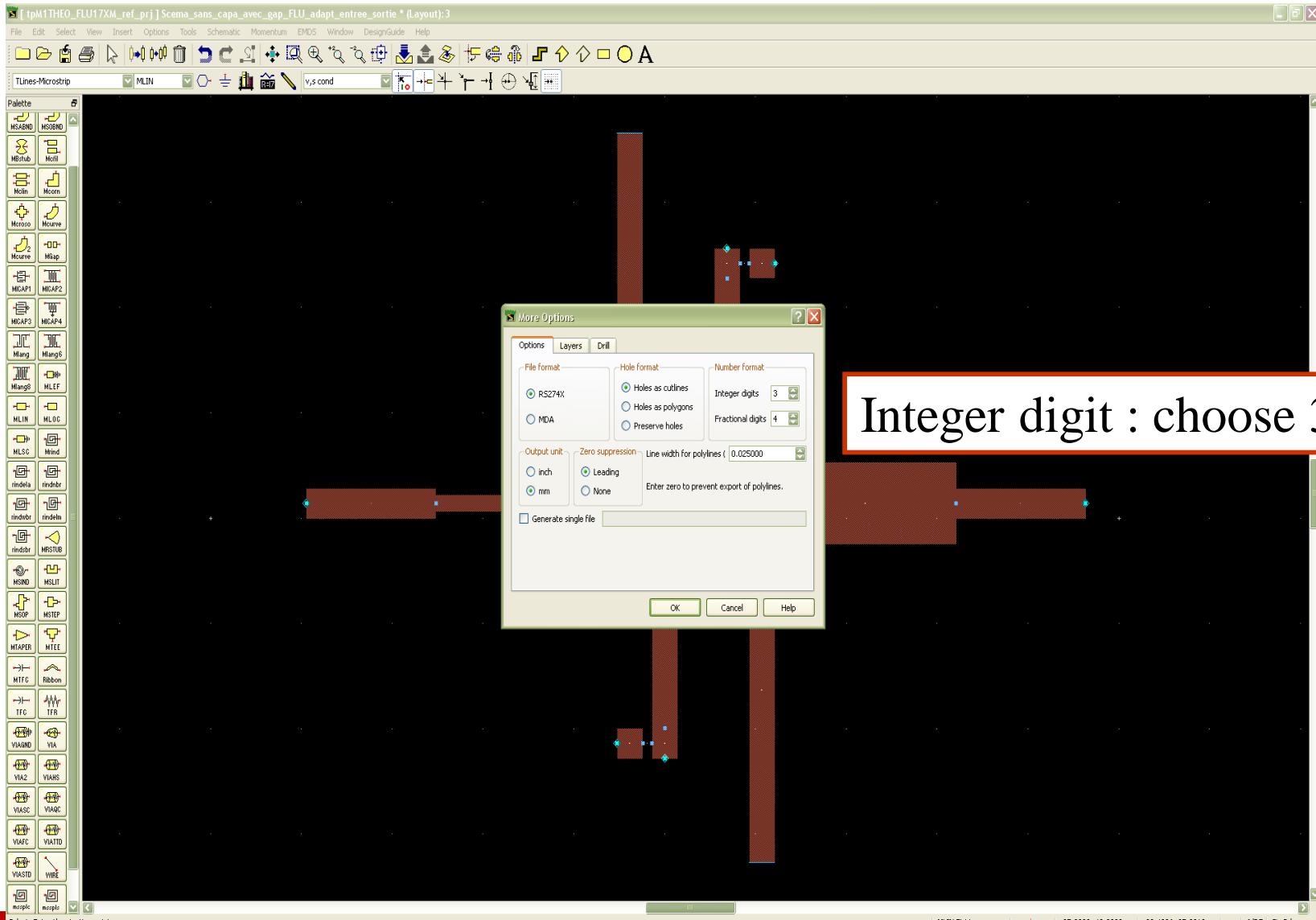

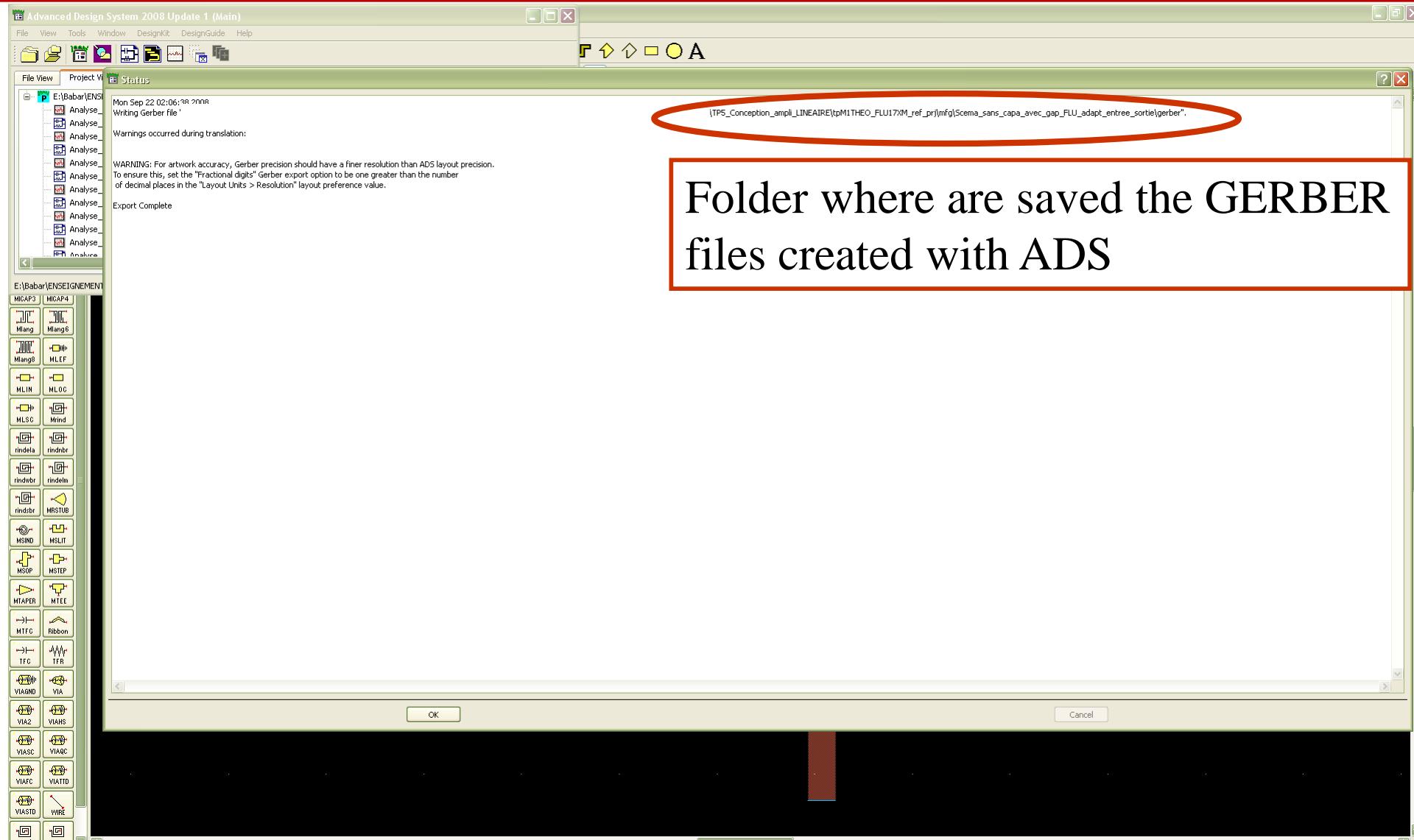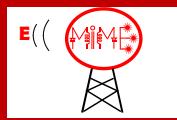


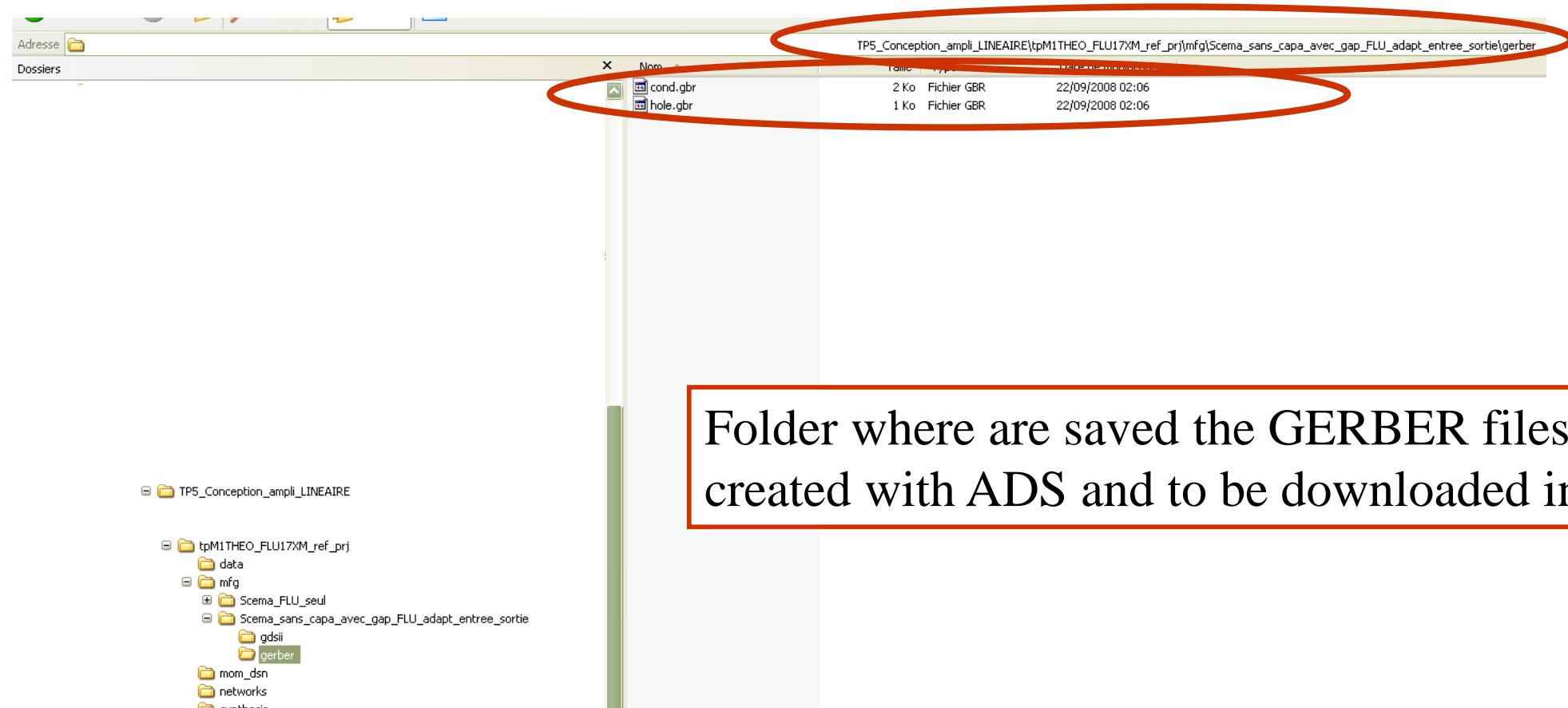


Folder where are saved the GERBER files
created with ADS and to be downloaded in ISOPRO



Front view

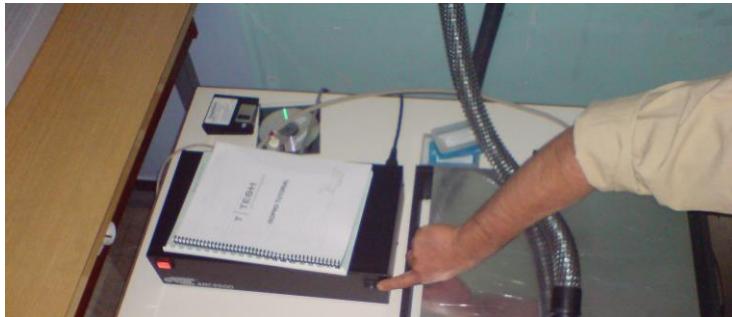

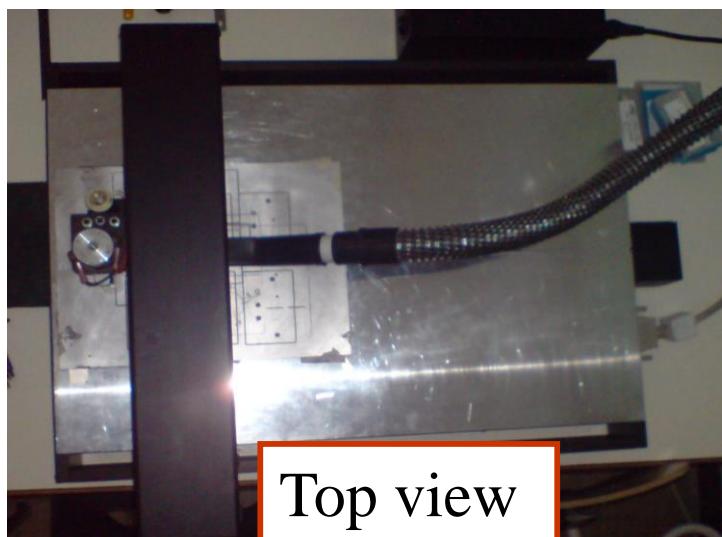
1°) Switch « ON »
The general power supply





Top view





2°) Press "ON"
Solenoid rear face

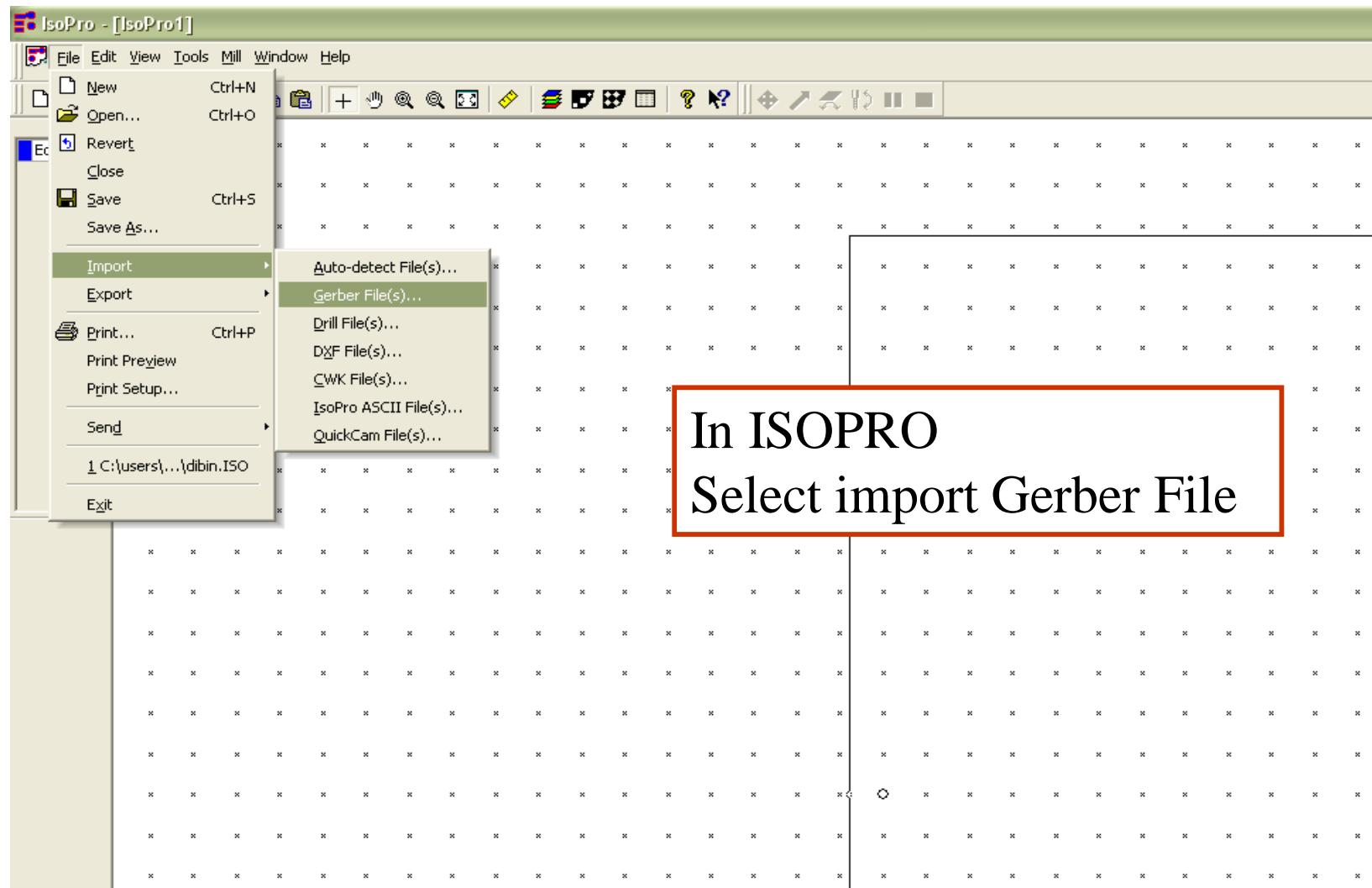


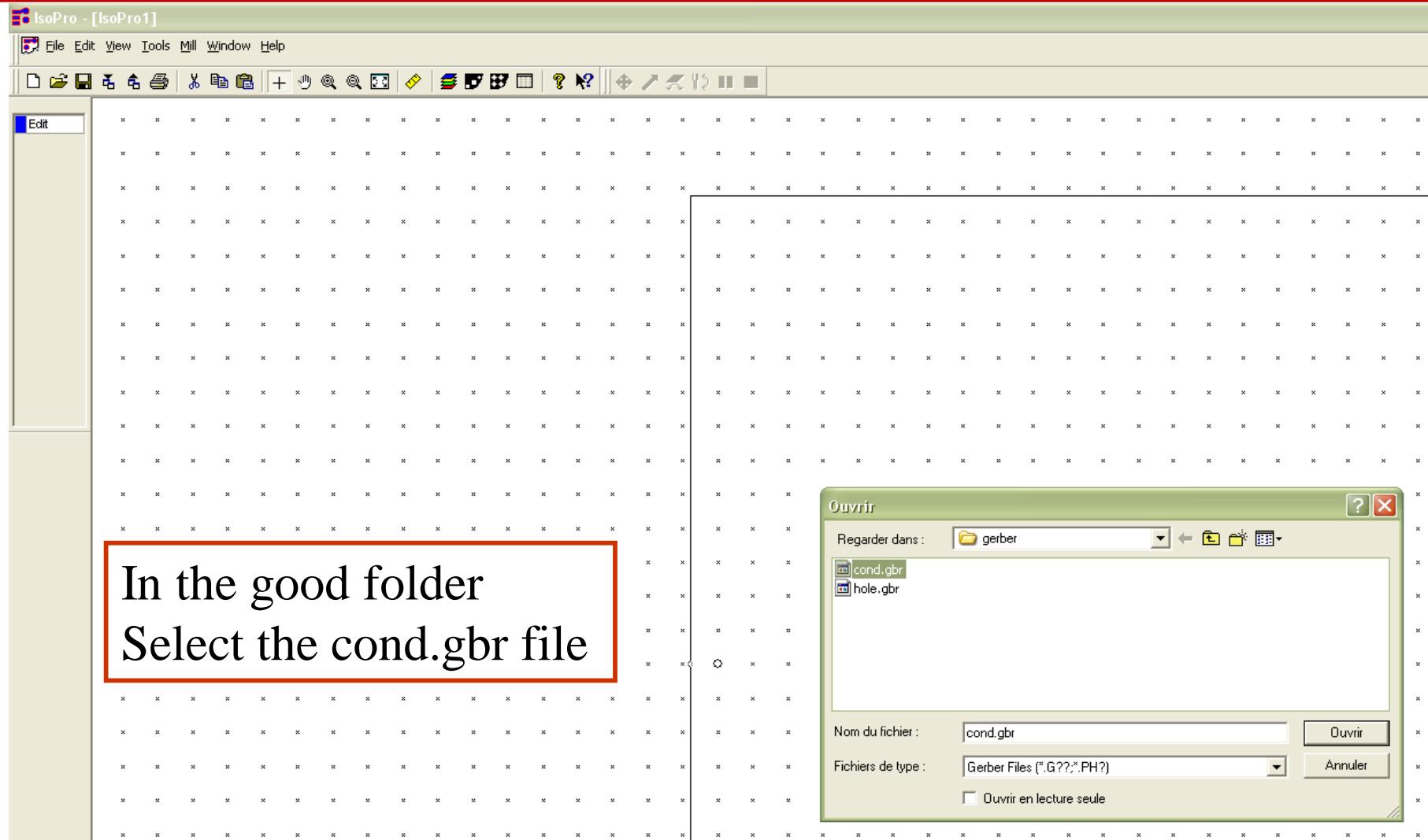


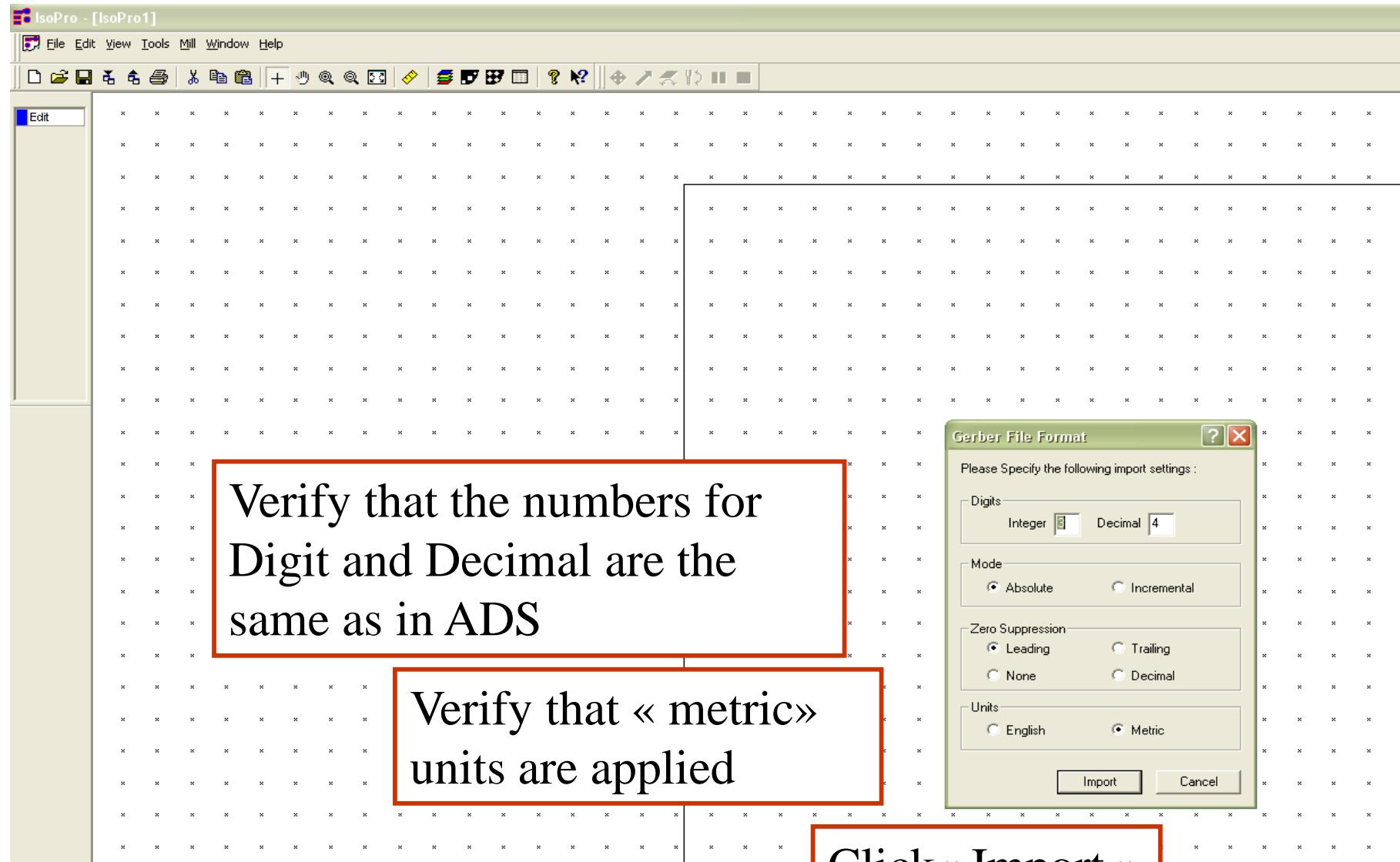


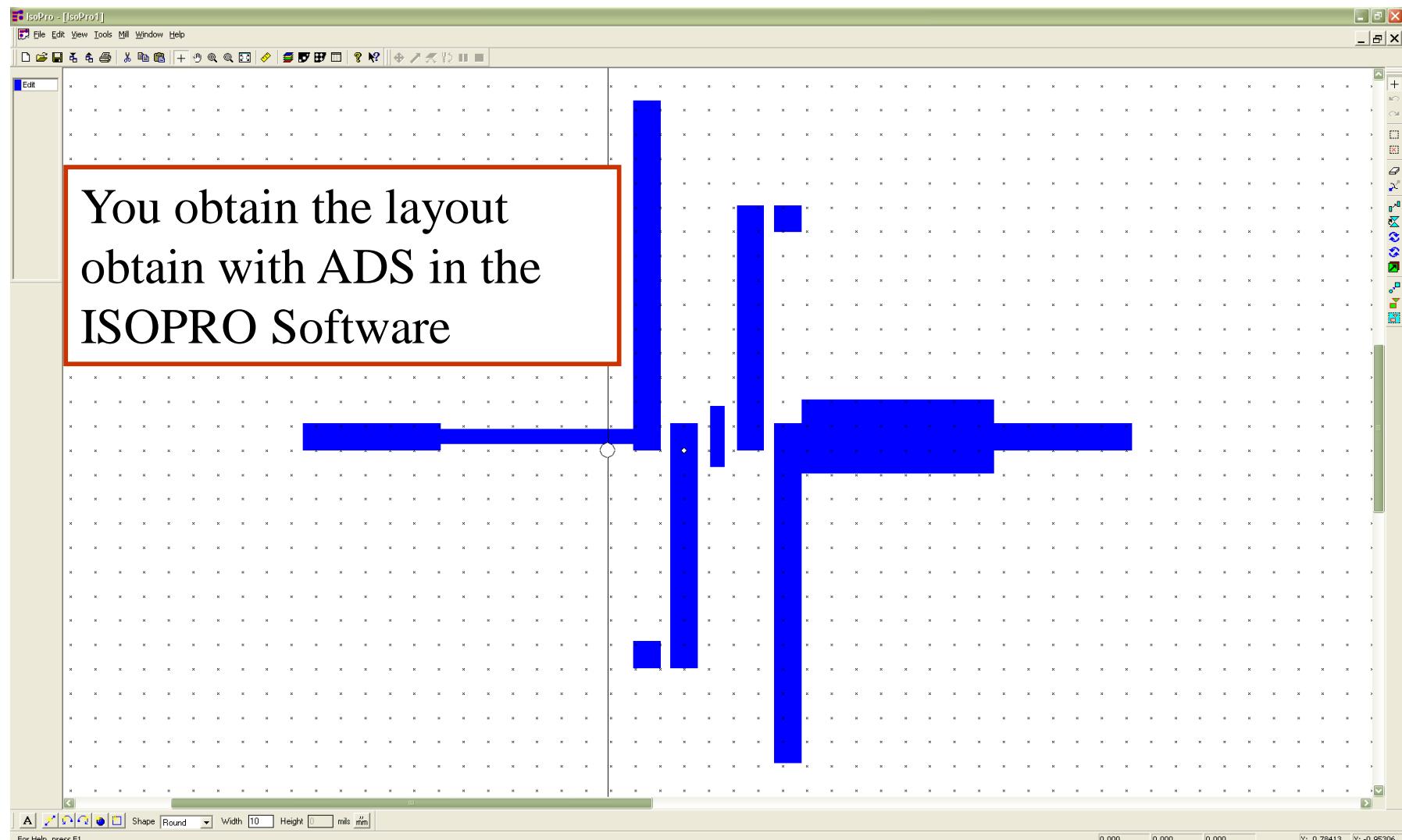


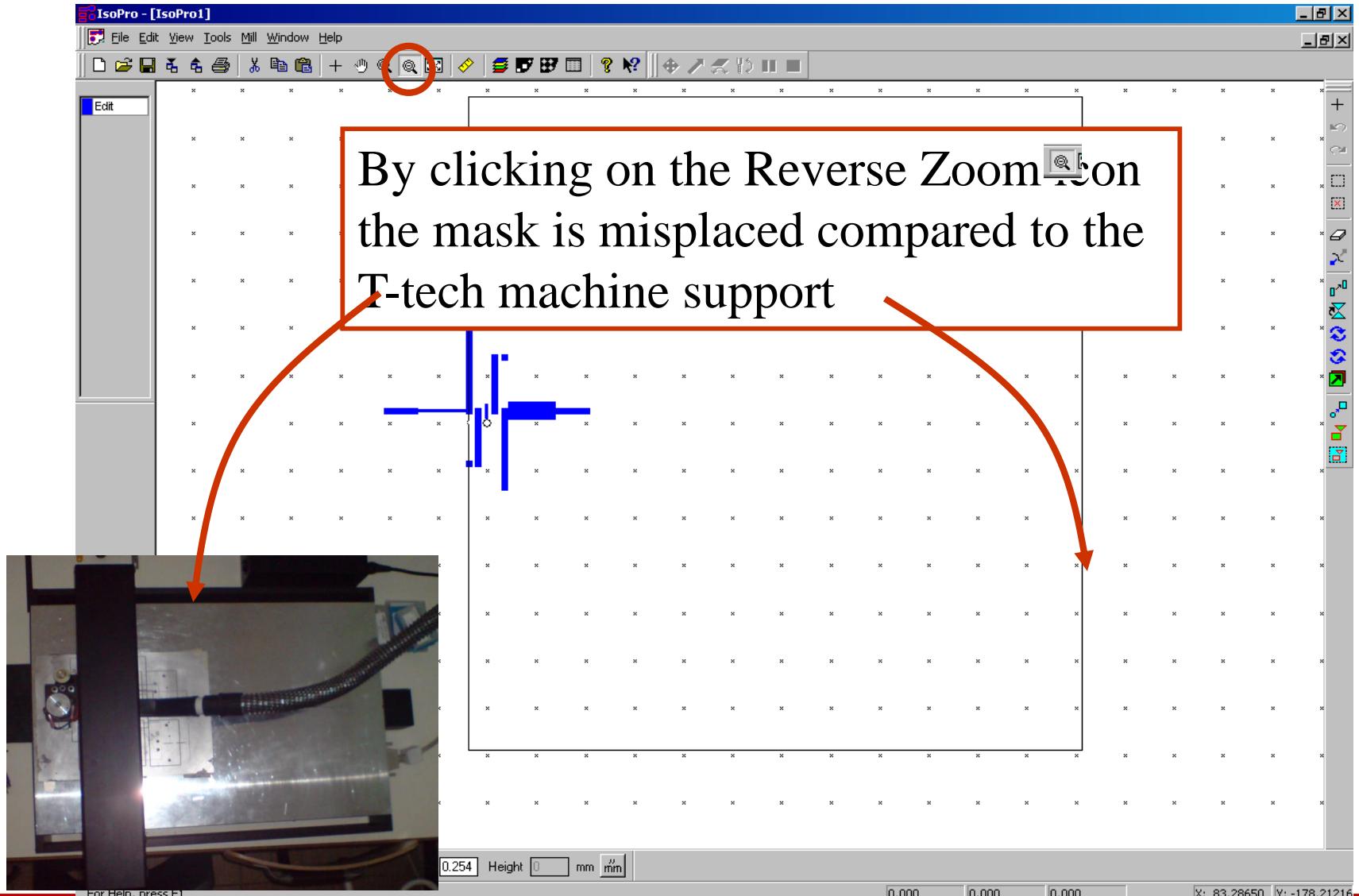


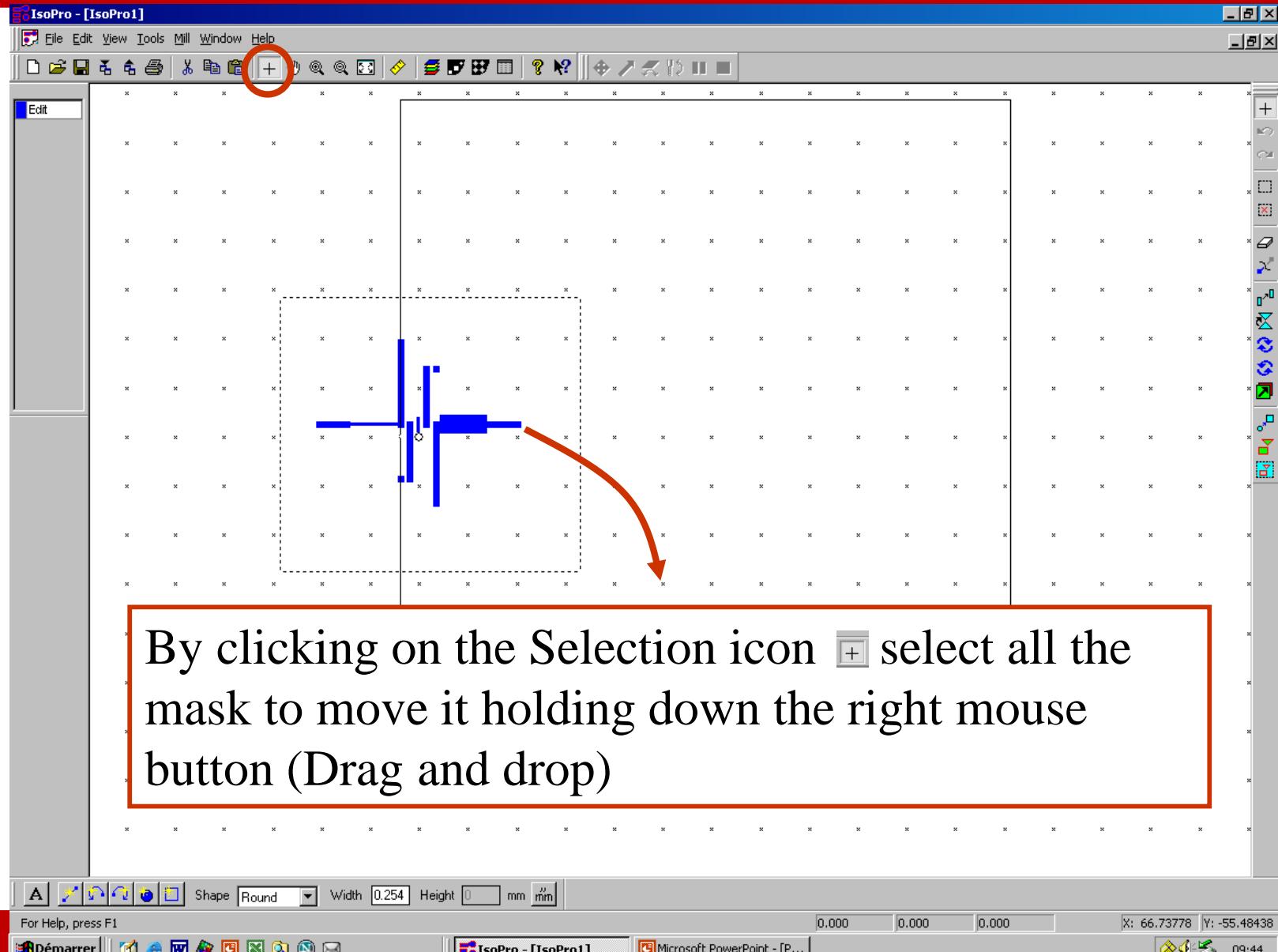


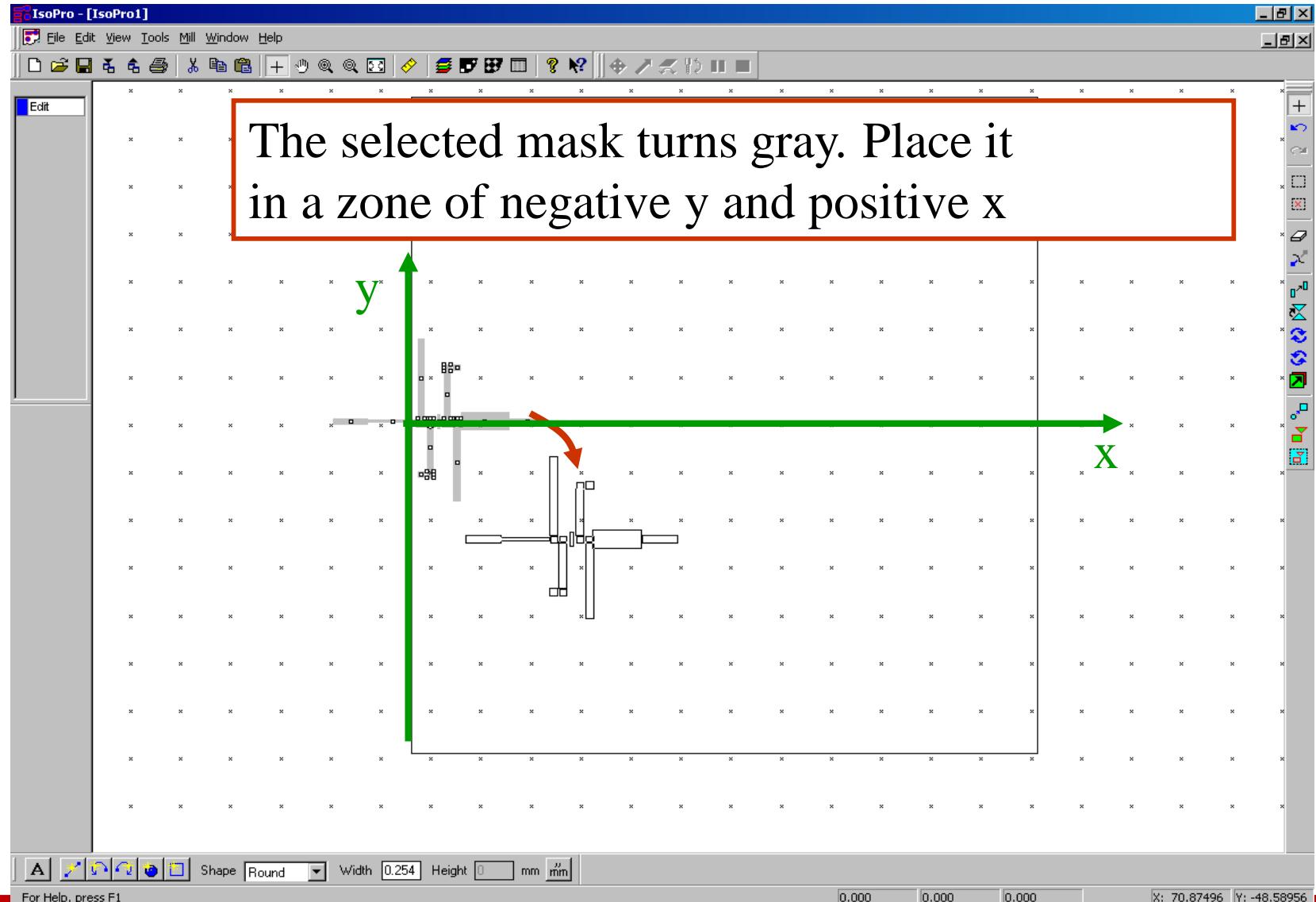


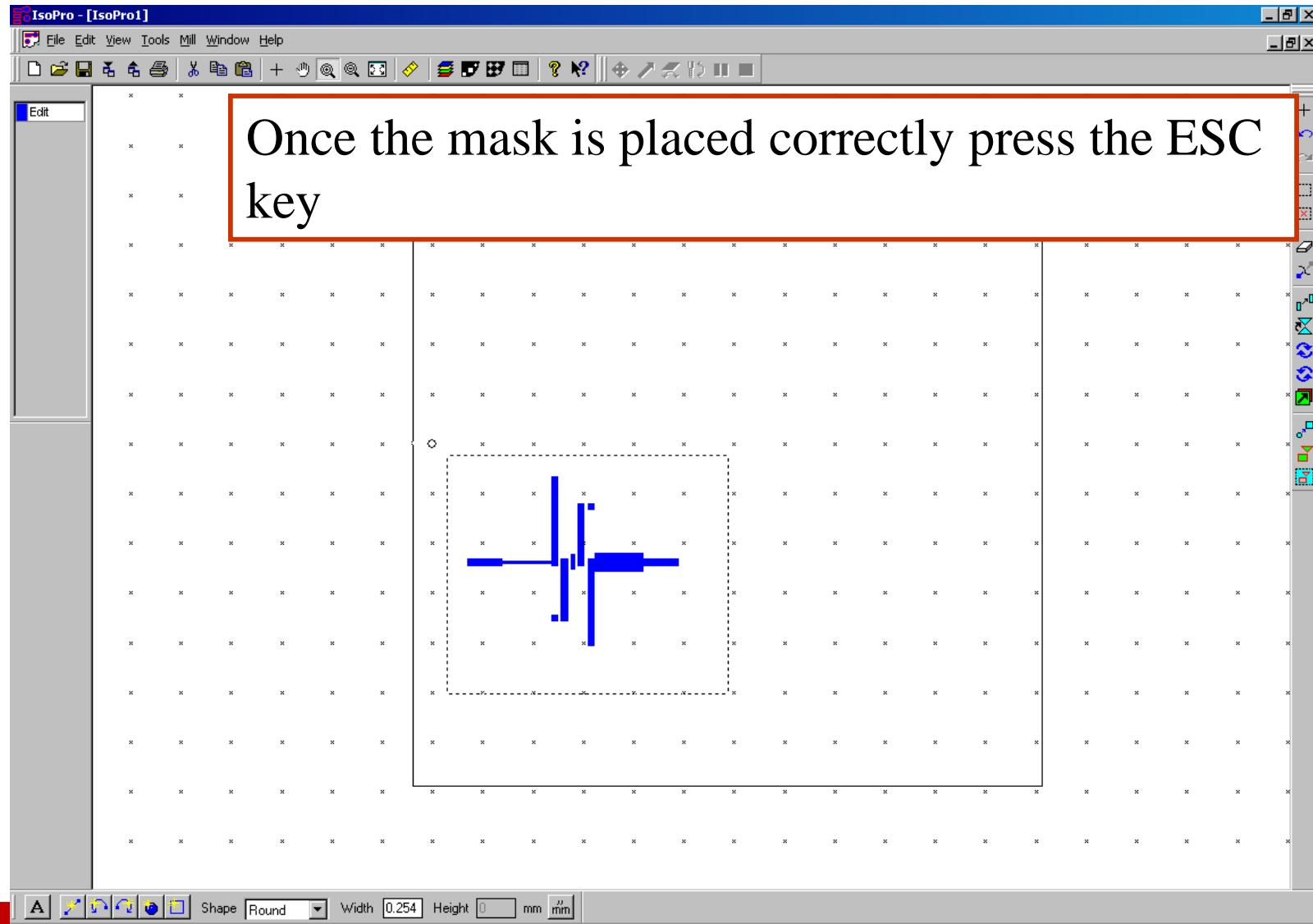


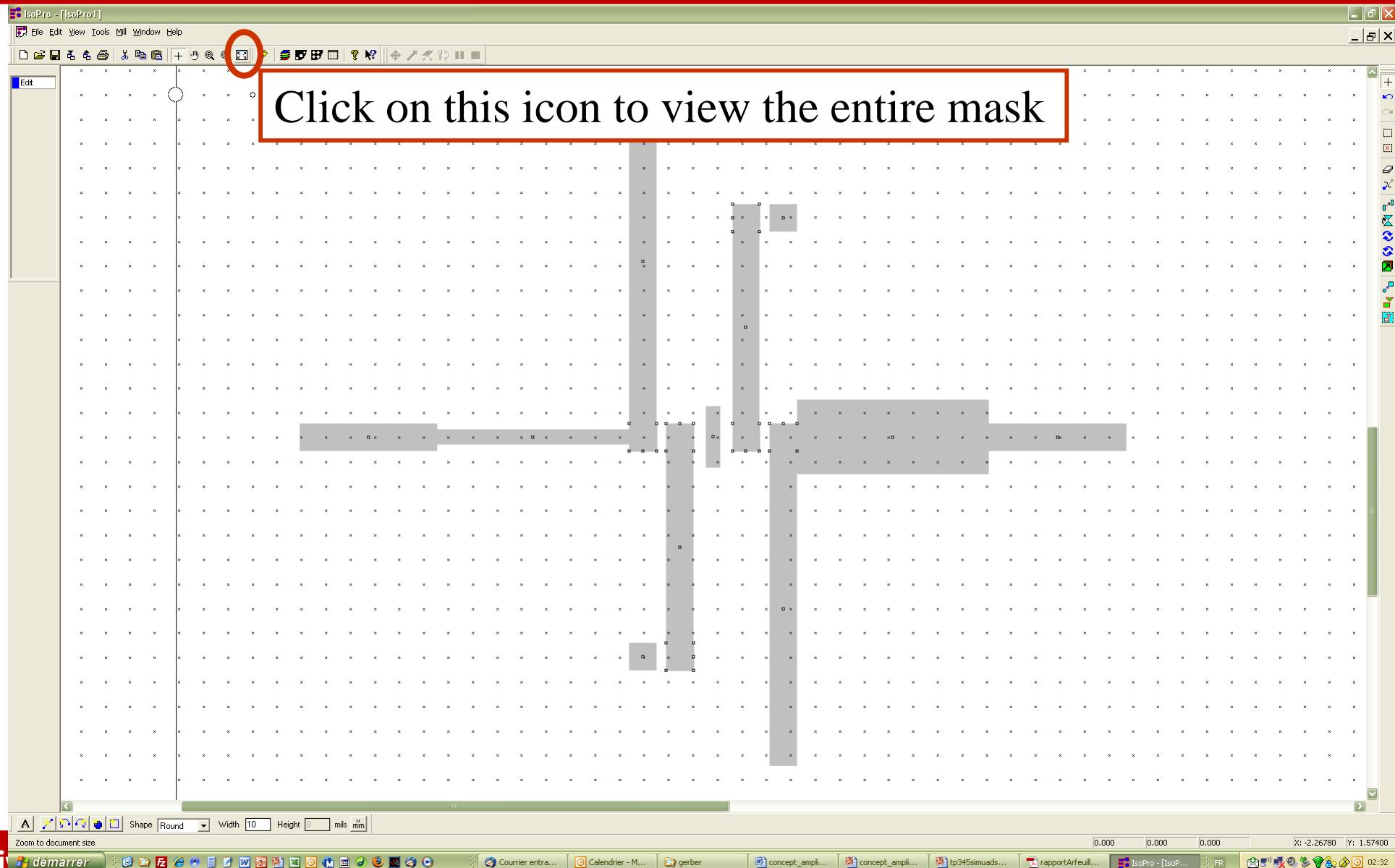


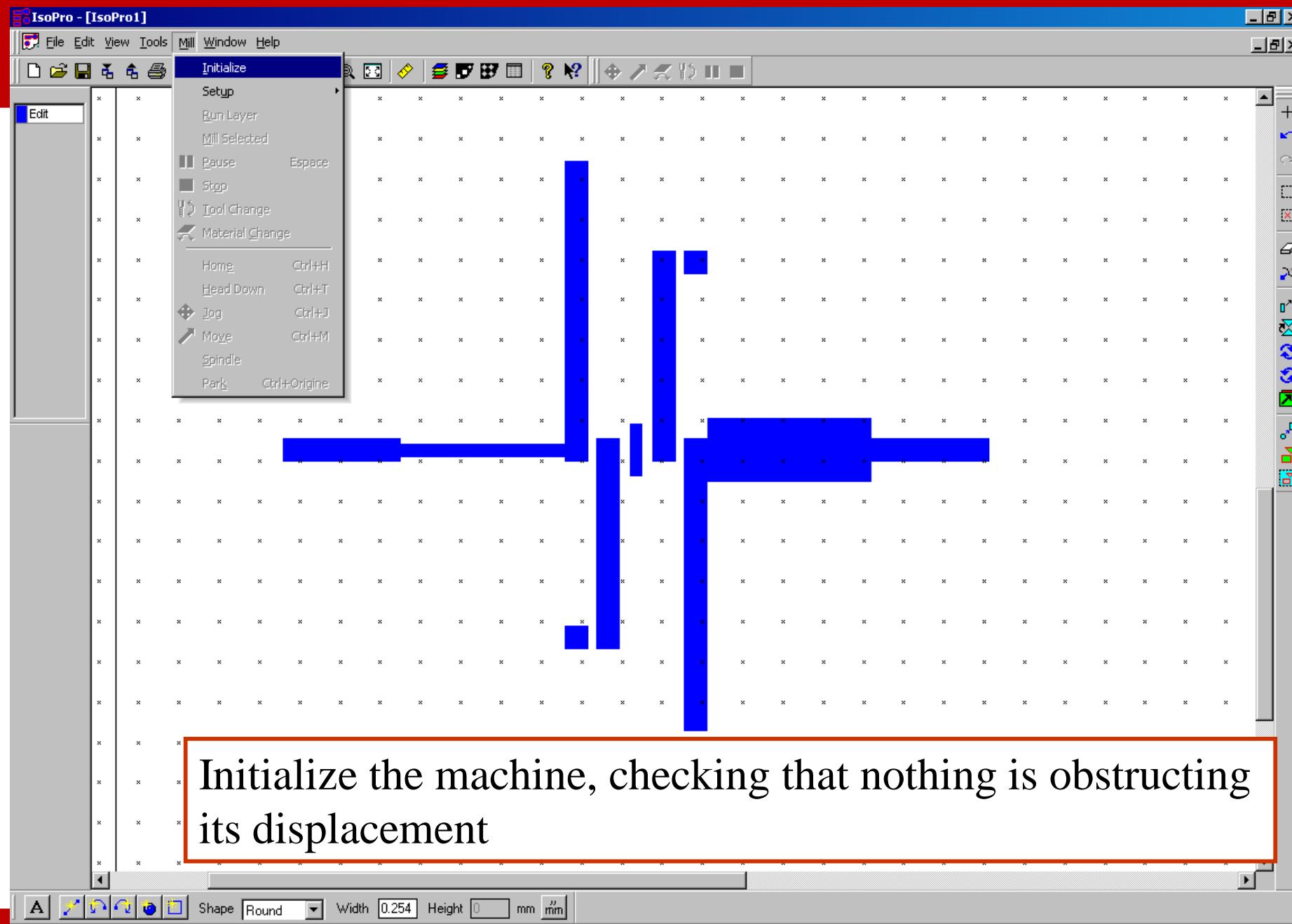


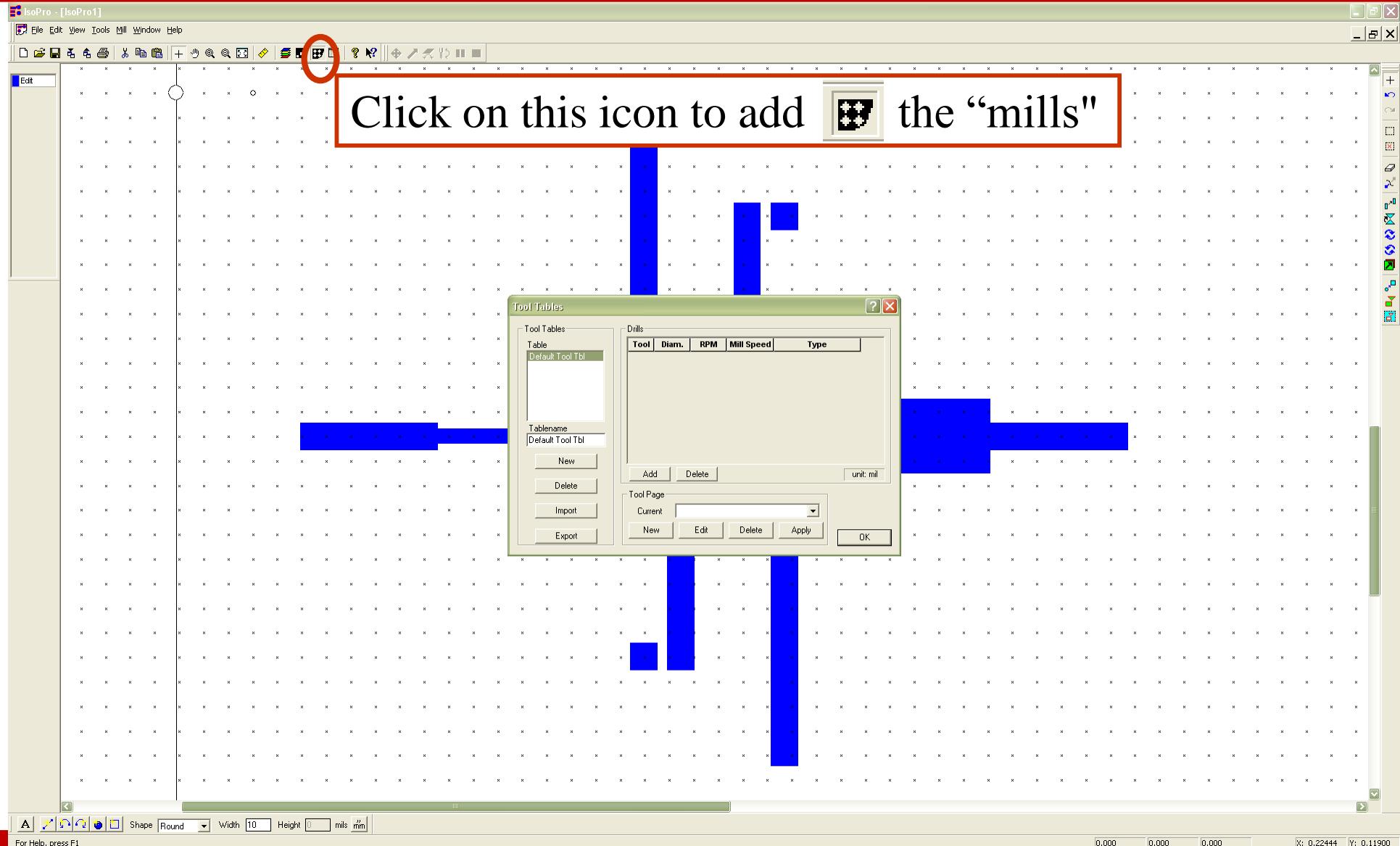

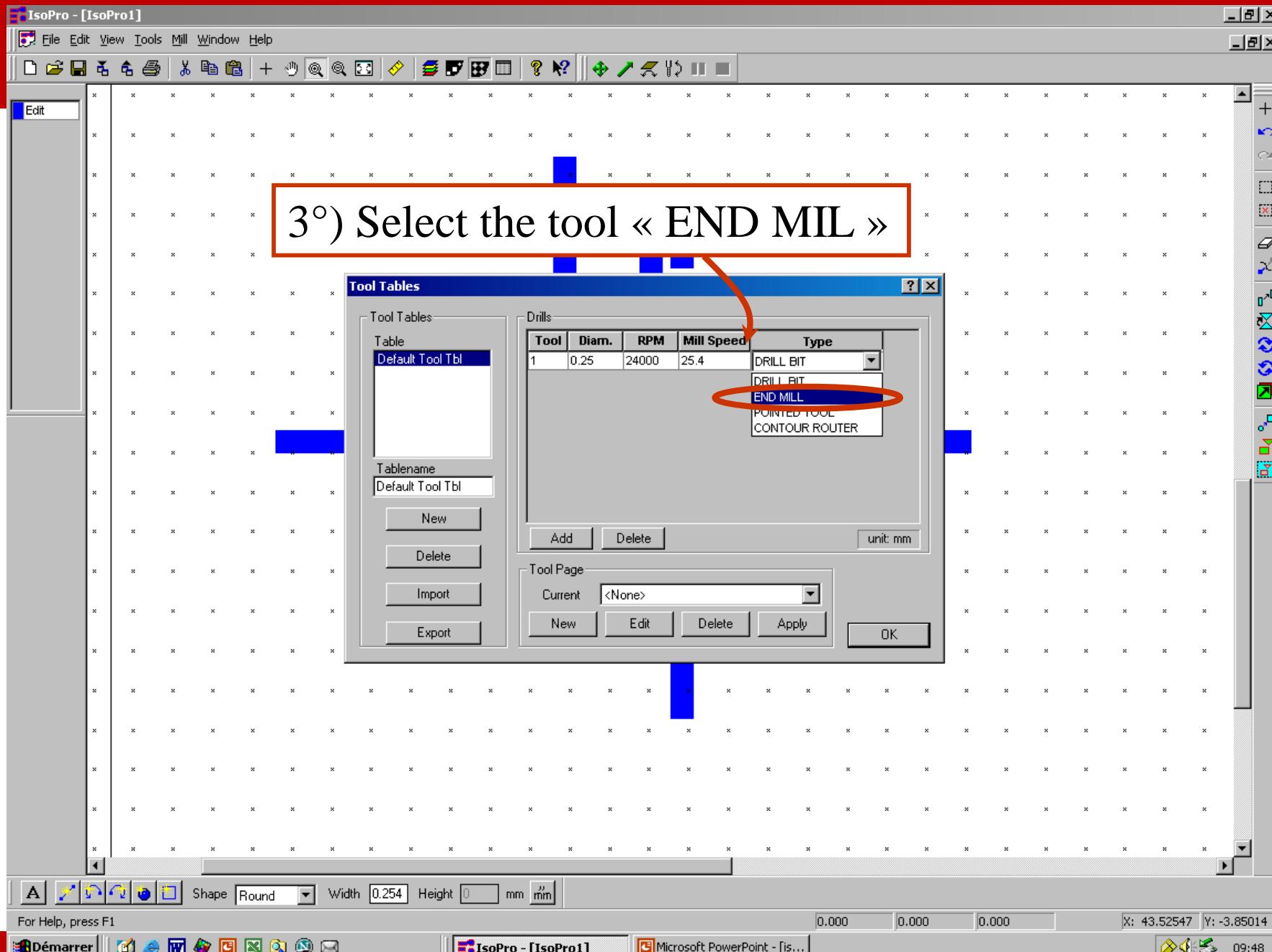


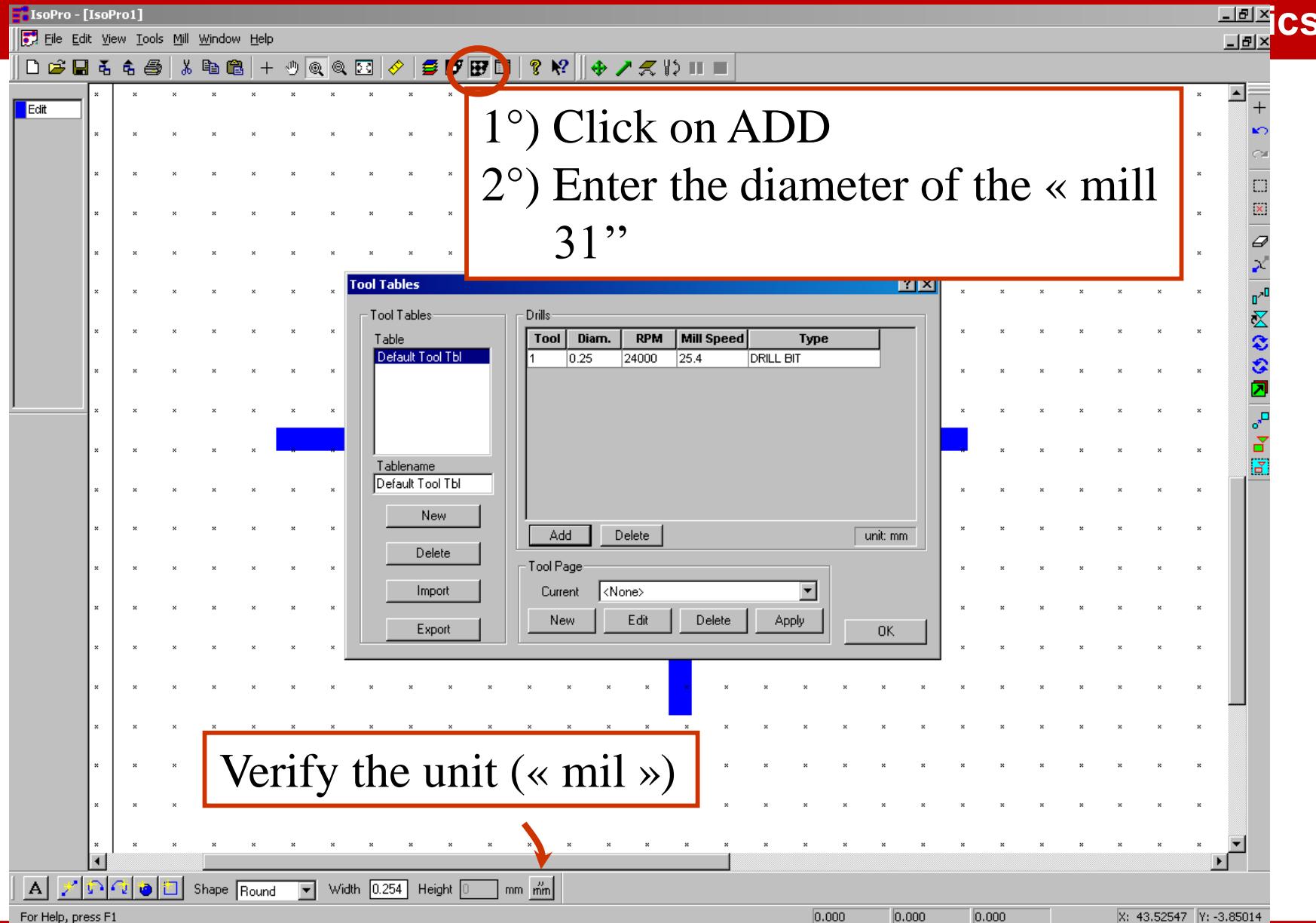

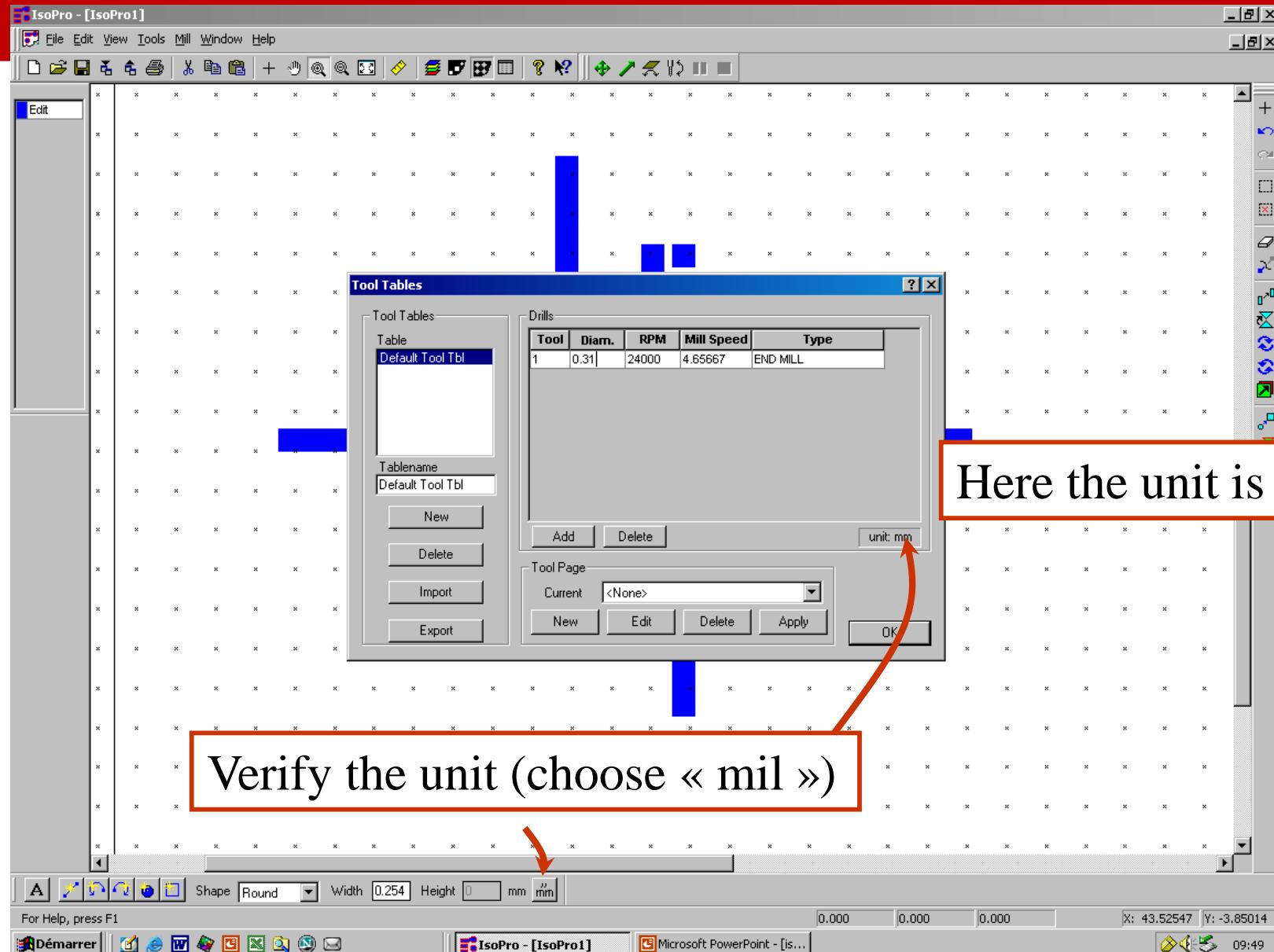

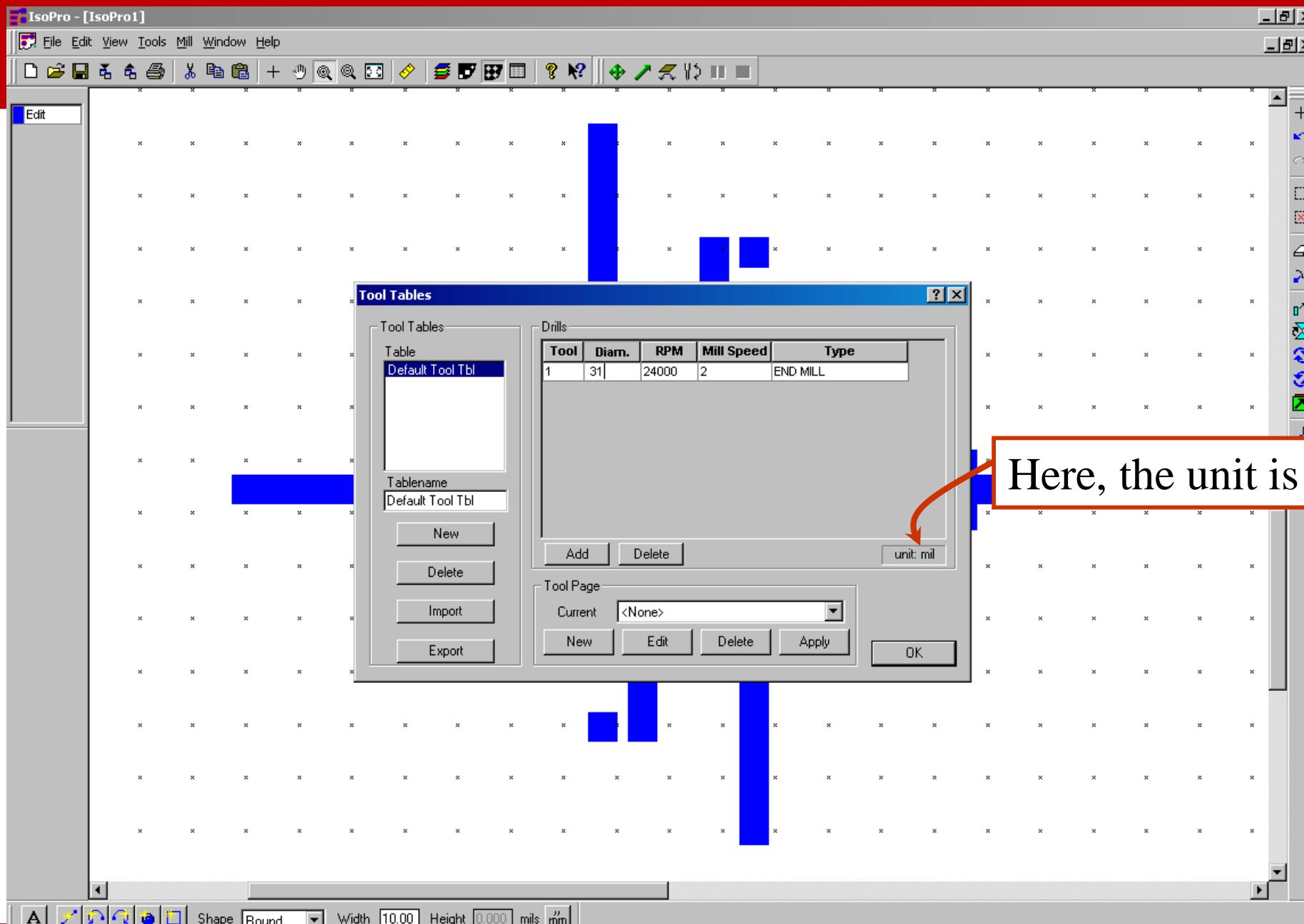

Edit

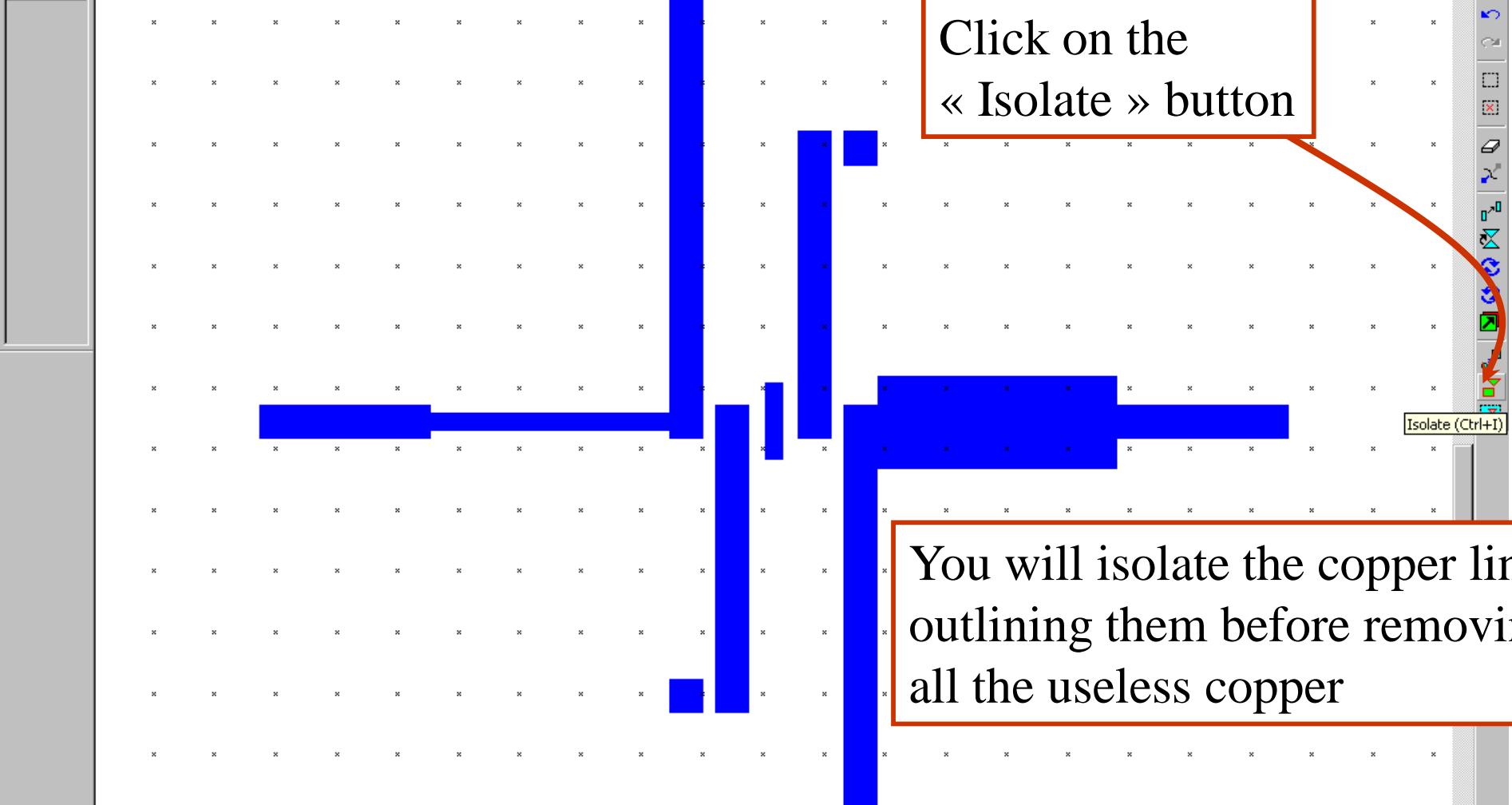

You will isolate the copper lines by outlining them before removing all the useless copper

A

Y

N

D

C

S

R

L

F

E

T

P

M

H

V

W

G

B

J

K

L

O

P

Q

R

S

T

U

V


W

X


Y


Z


_

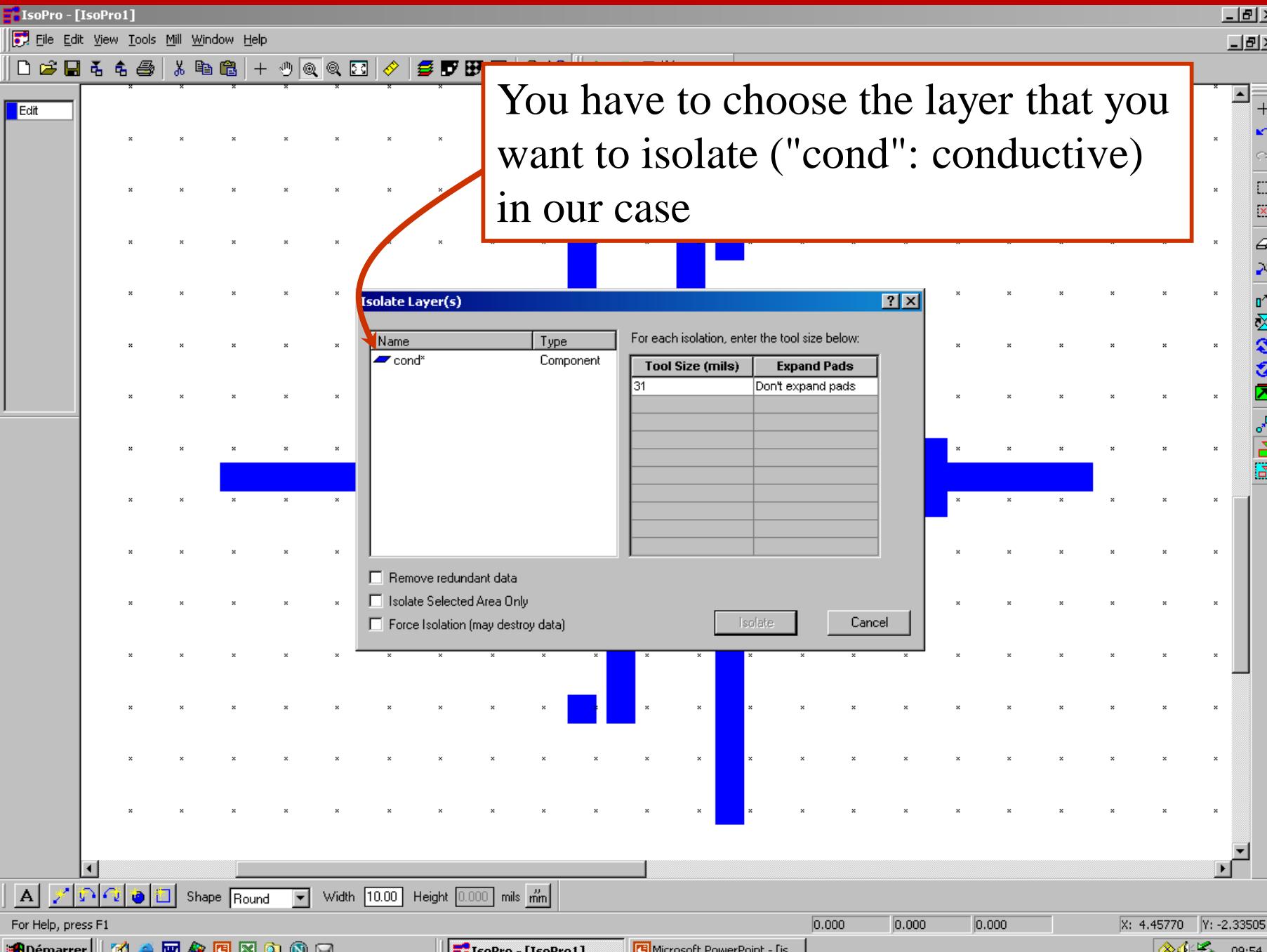

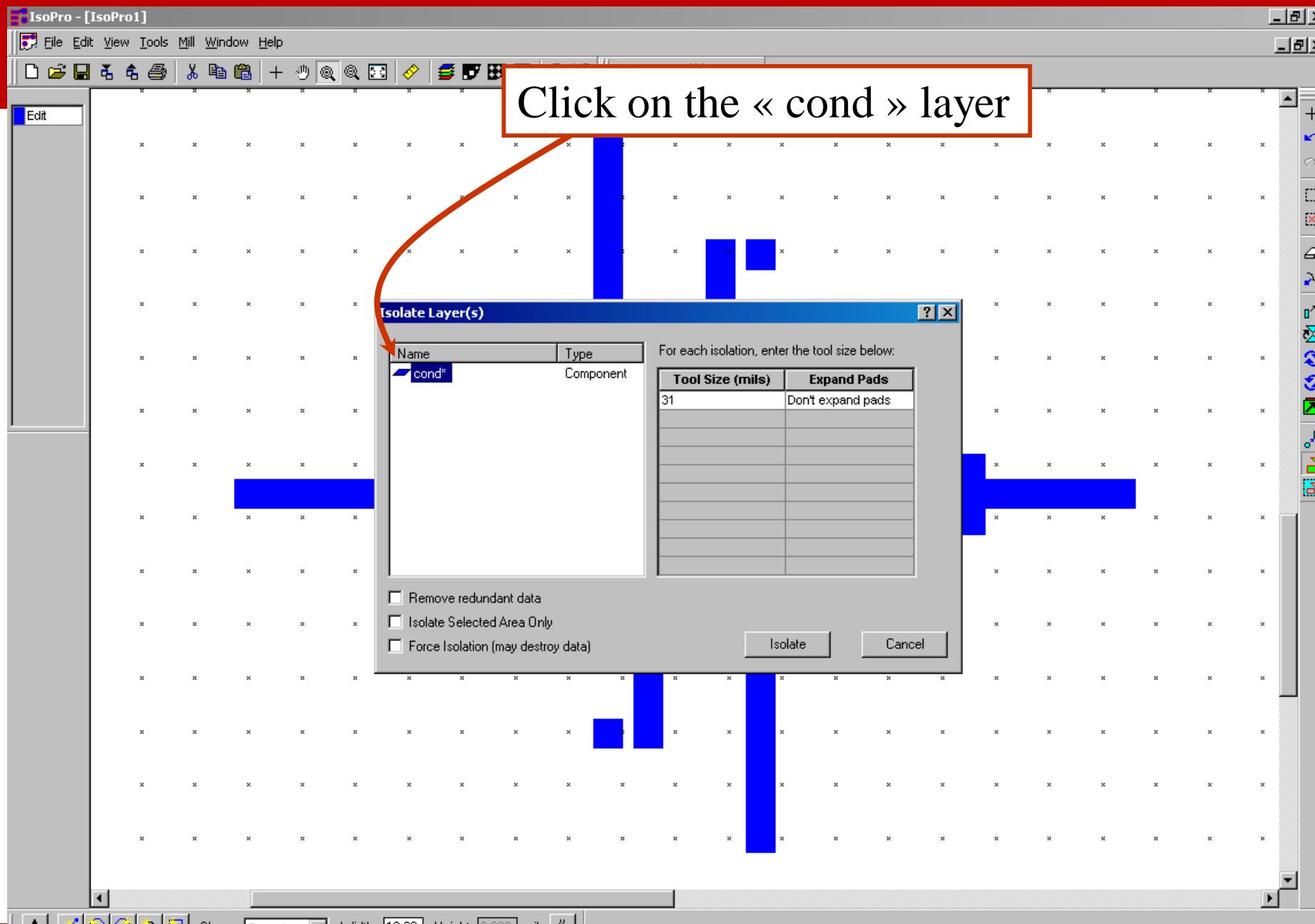You have to choose the layer that you want to isolate ("cond": conductive) in our case



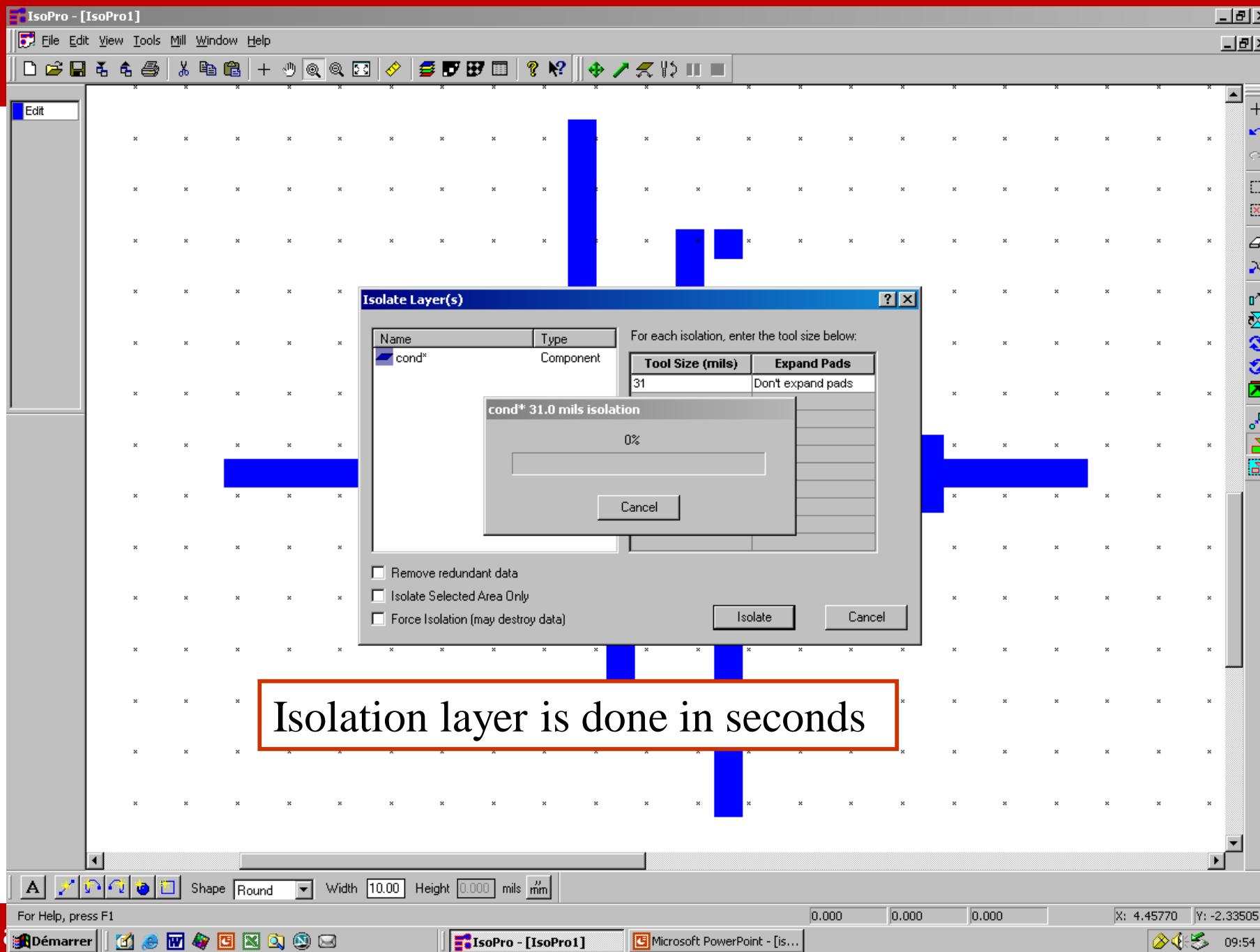


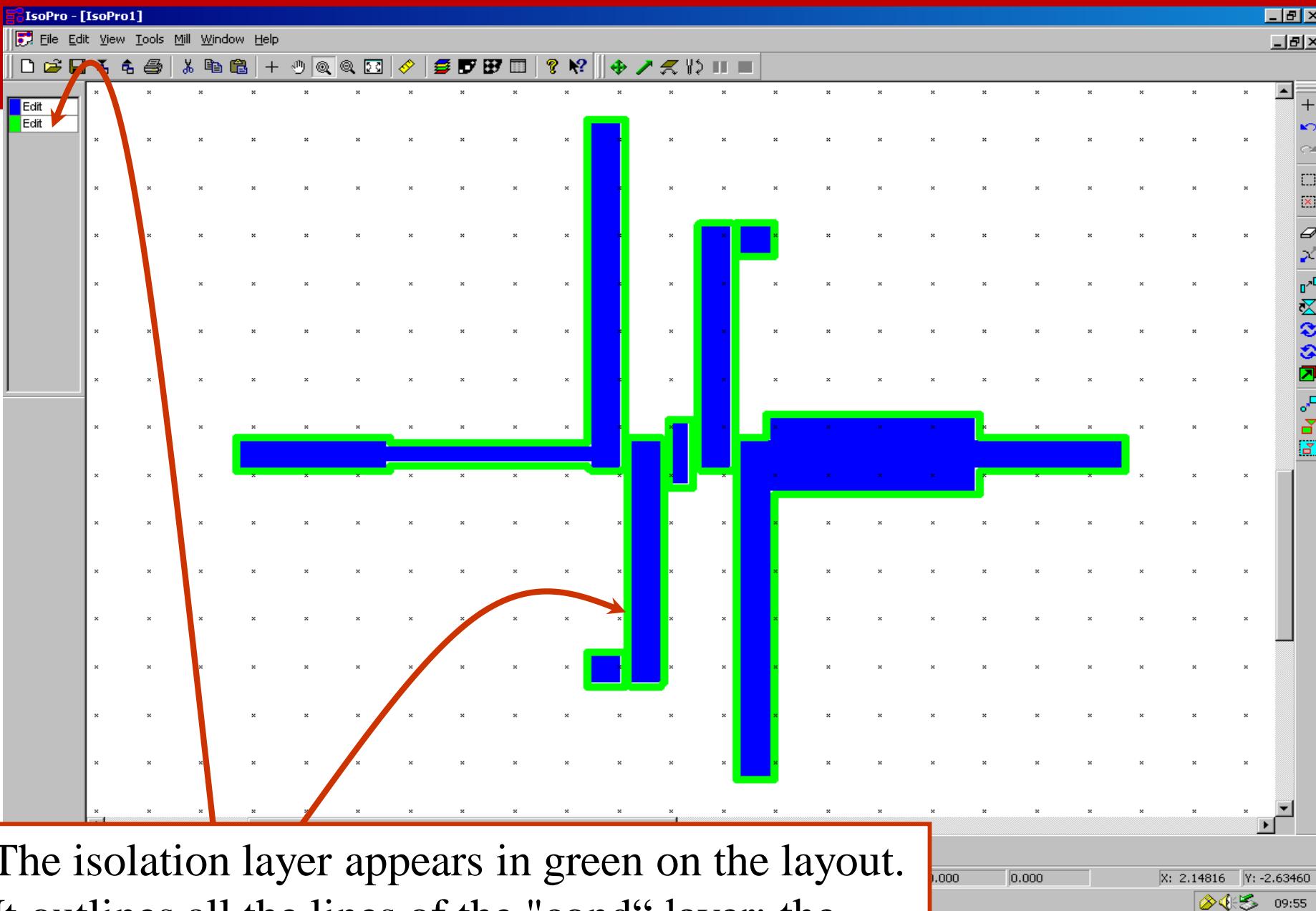


The isolation layer appears in green on the layout.
It outlines all the lines of the "cond" layer: the
copper will be removed by the selected "Edit"

Date


- 81 -

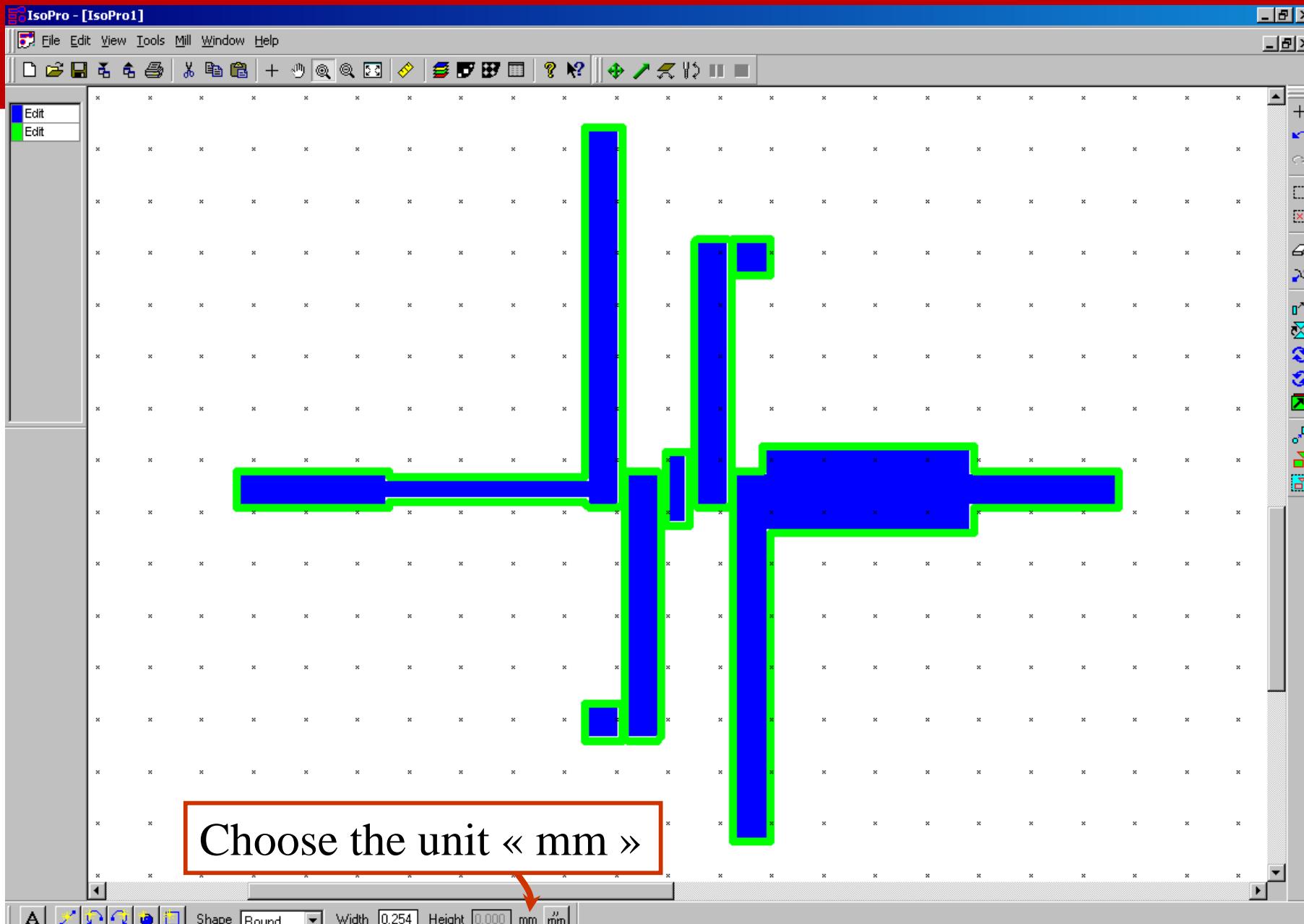

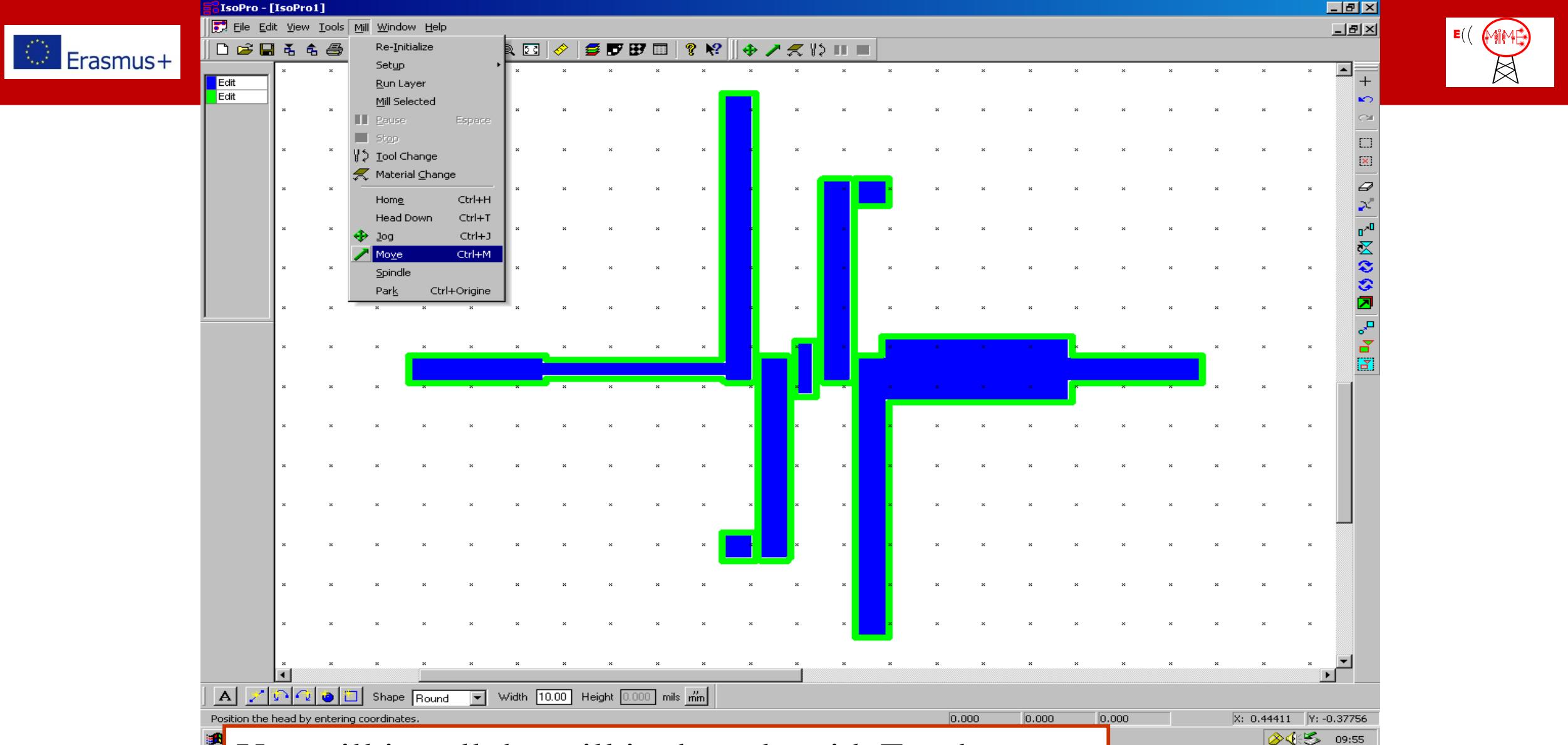

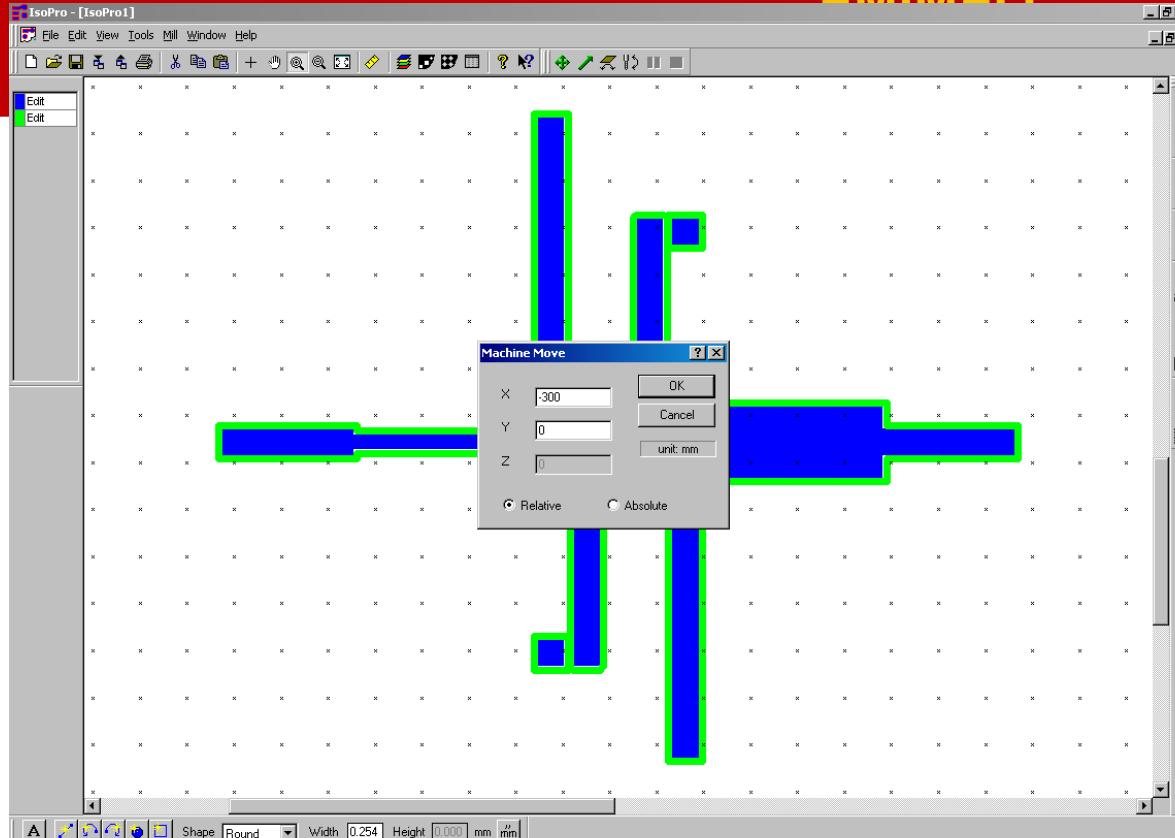
You will install the mill in the solenoid. For that, move the solenoid out of the table. Select the menu Mill / Move






Move the solenoid on the bench : -300 on the x

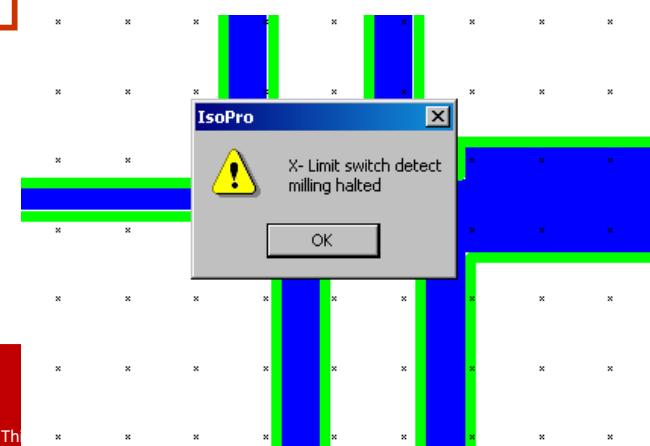The following normal message appears
meaning you want to go too far away
=> go to the next step.




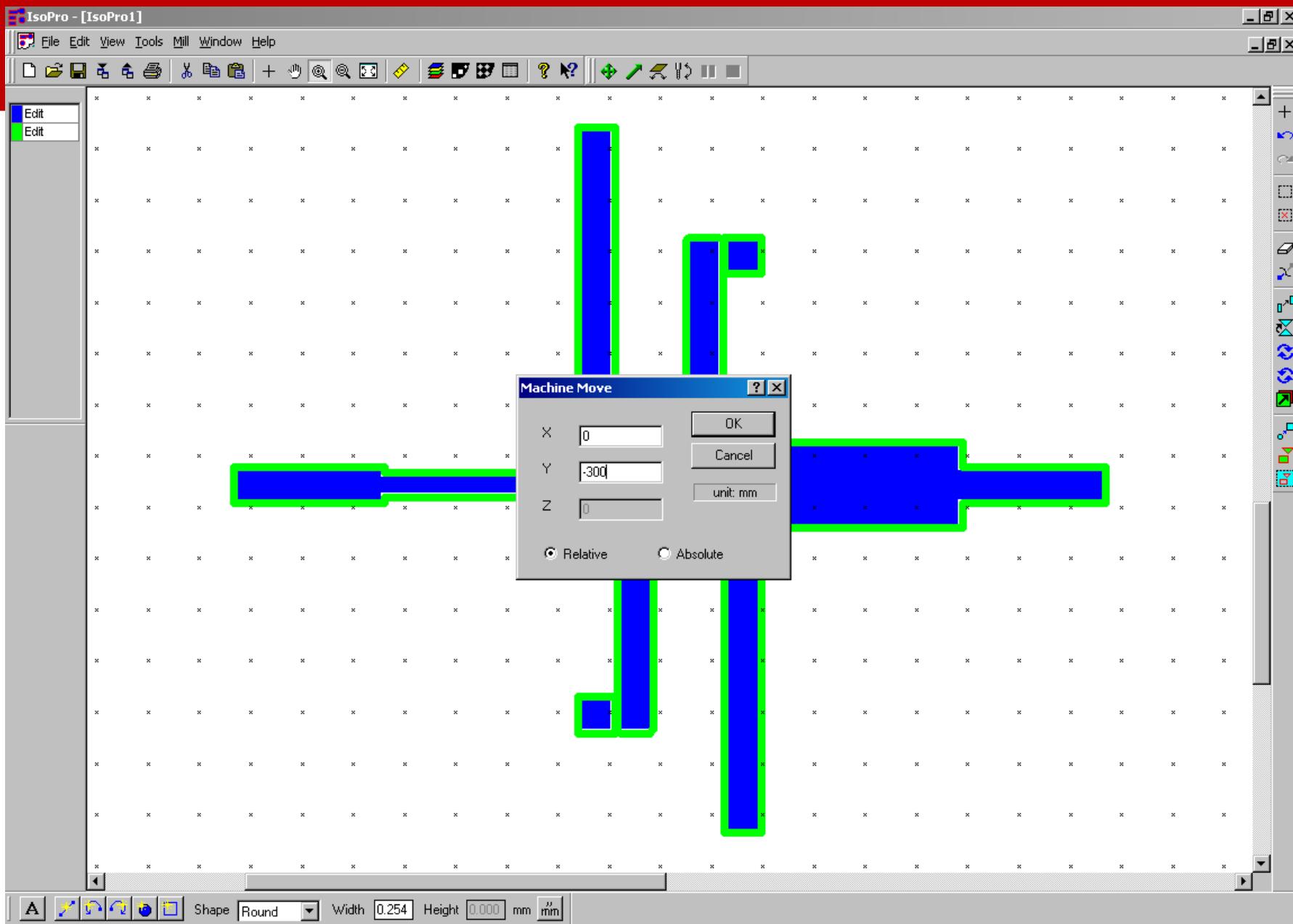

Move the solenoid on the bench : -300 on y

Date


- 85 -

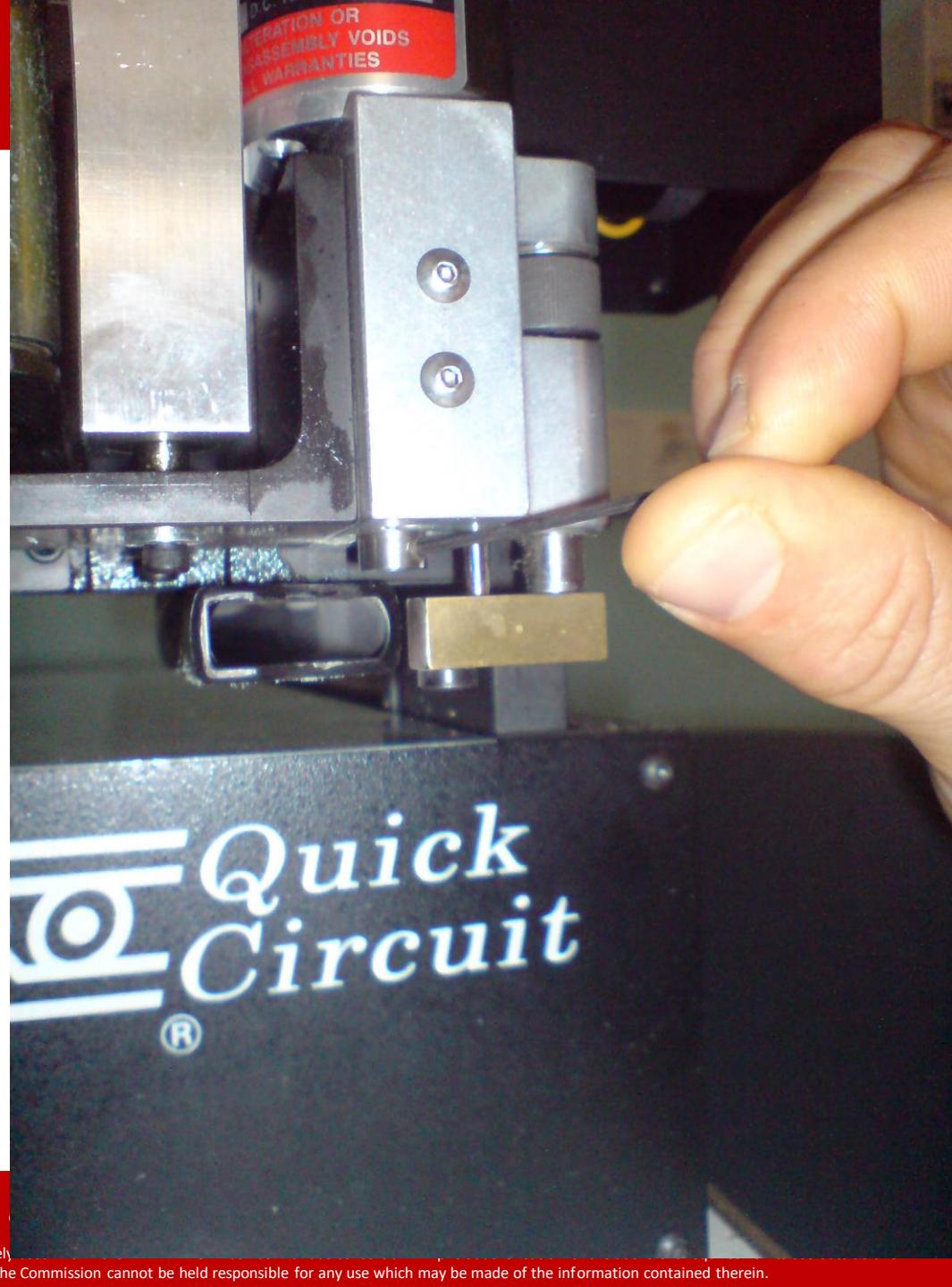


owa

The solenoid and
chuck are outside the
machine.

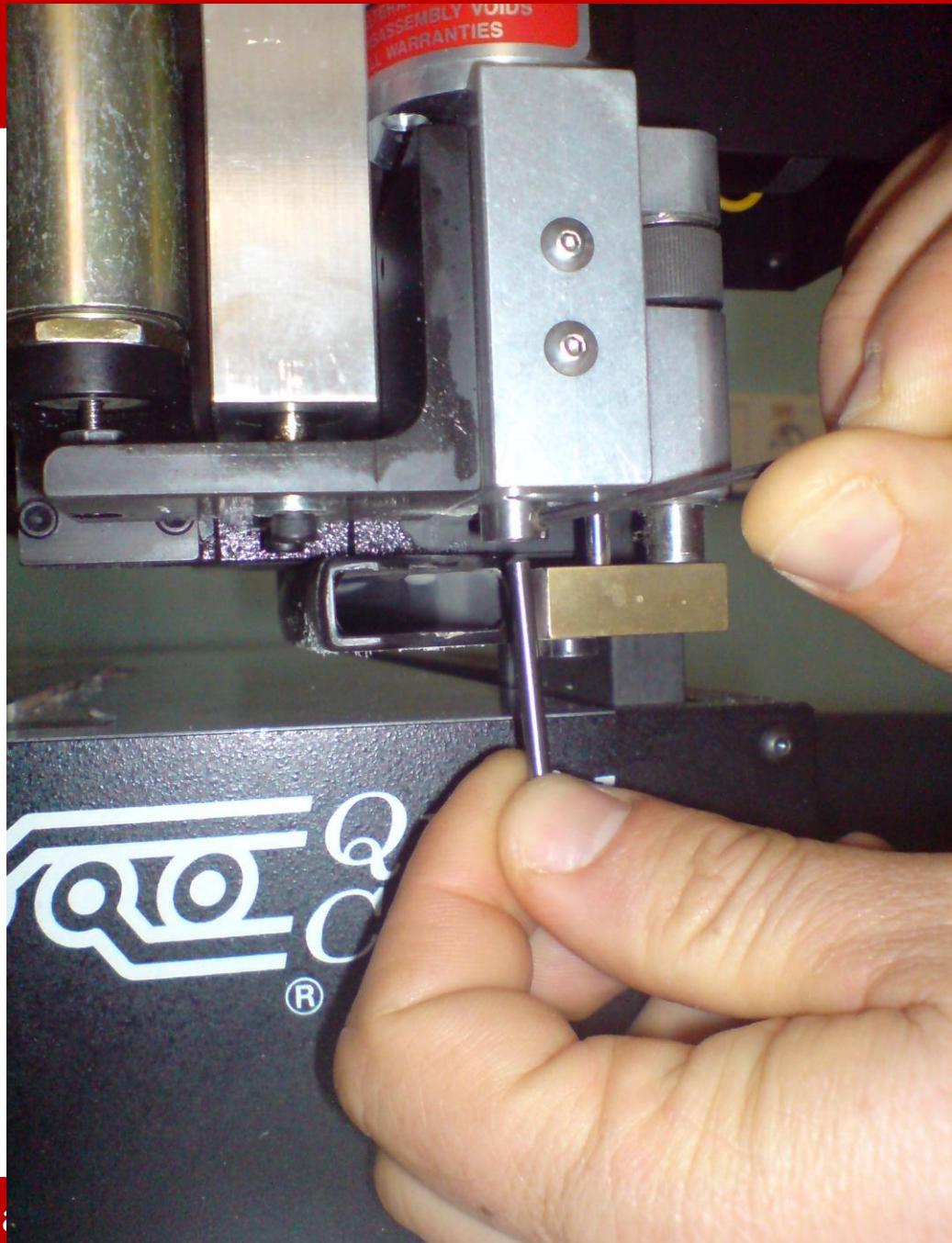
Unscrew the
clamping screw with
a wrench.



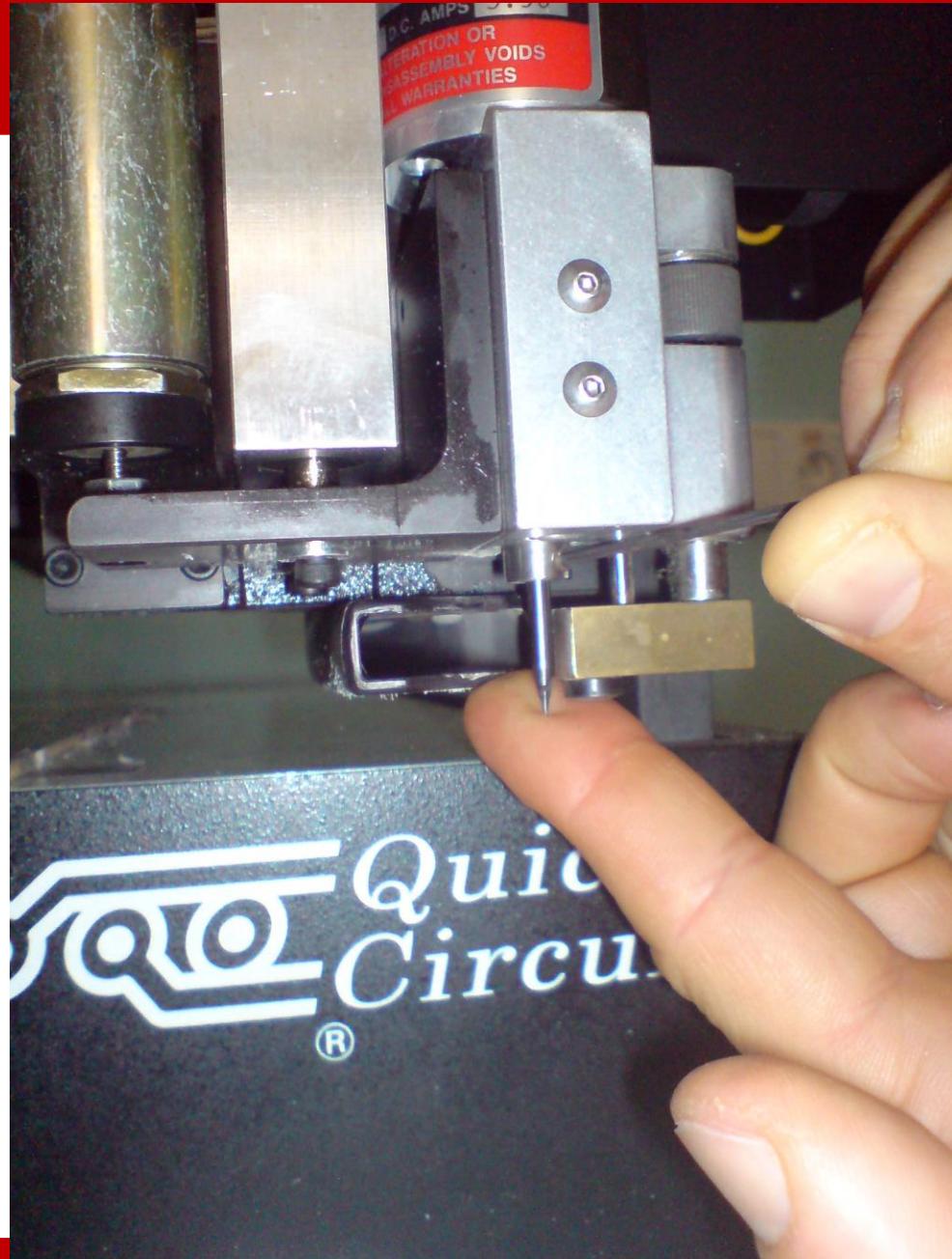rowa Insert the selected mill into the chuck




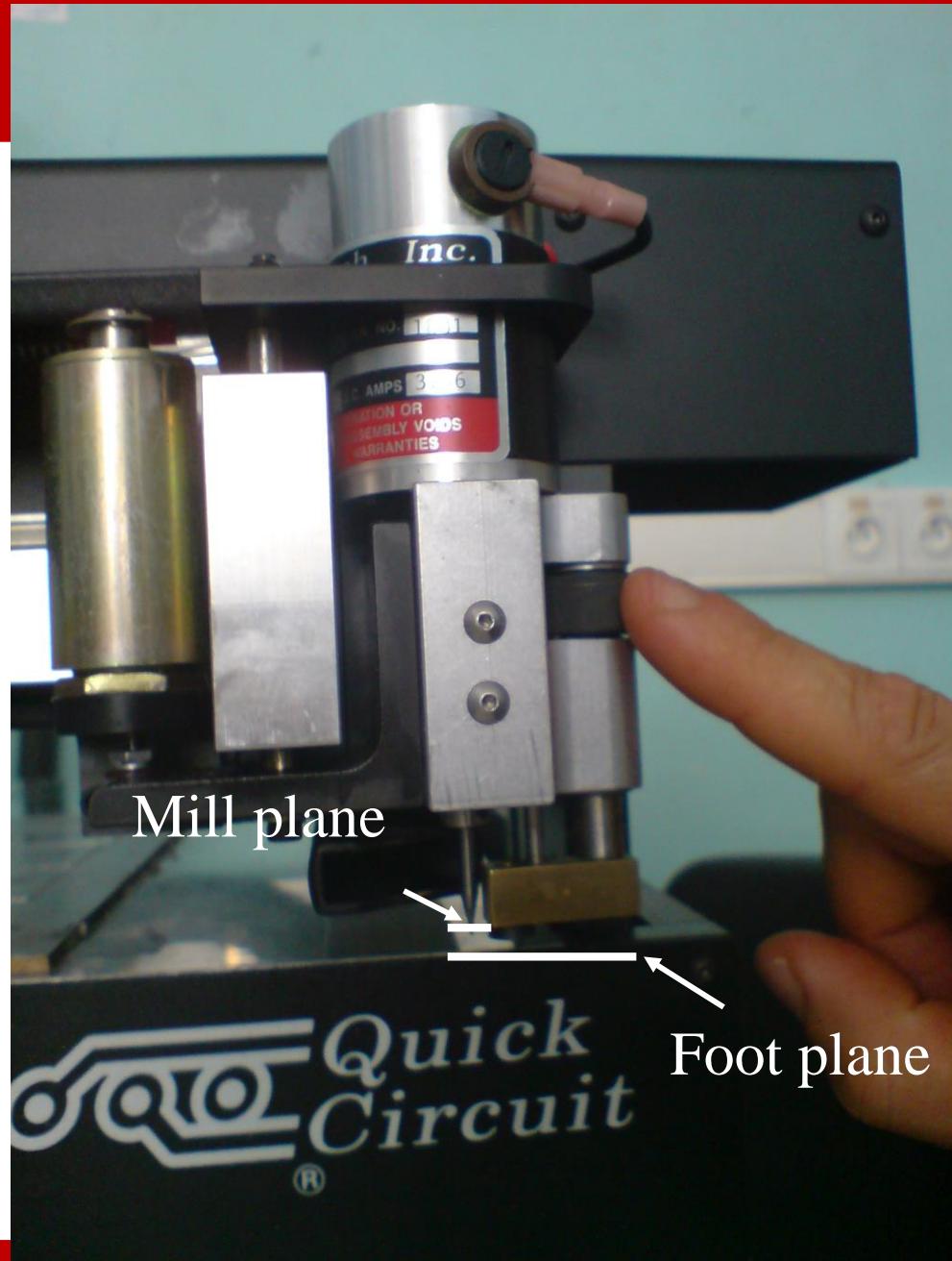Hold the mill in the chuck and tighten the clamping screw with the wrench.





Microwave Electronics and Optics

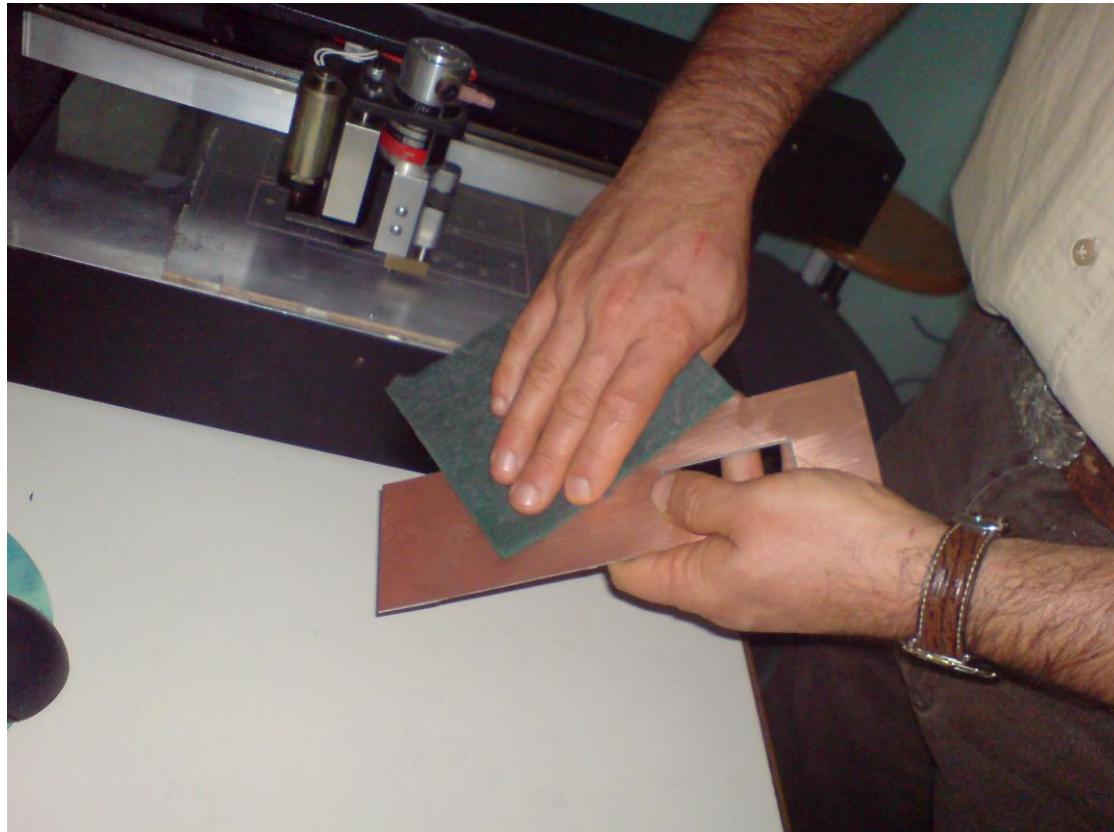Use the screw on the side of the solenoid so that the foot is placed under the mill.




Take a piece of FR4
plate and clean it

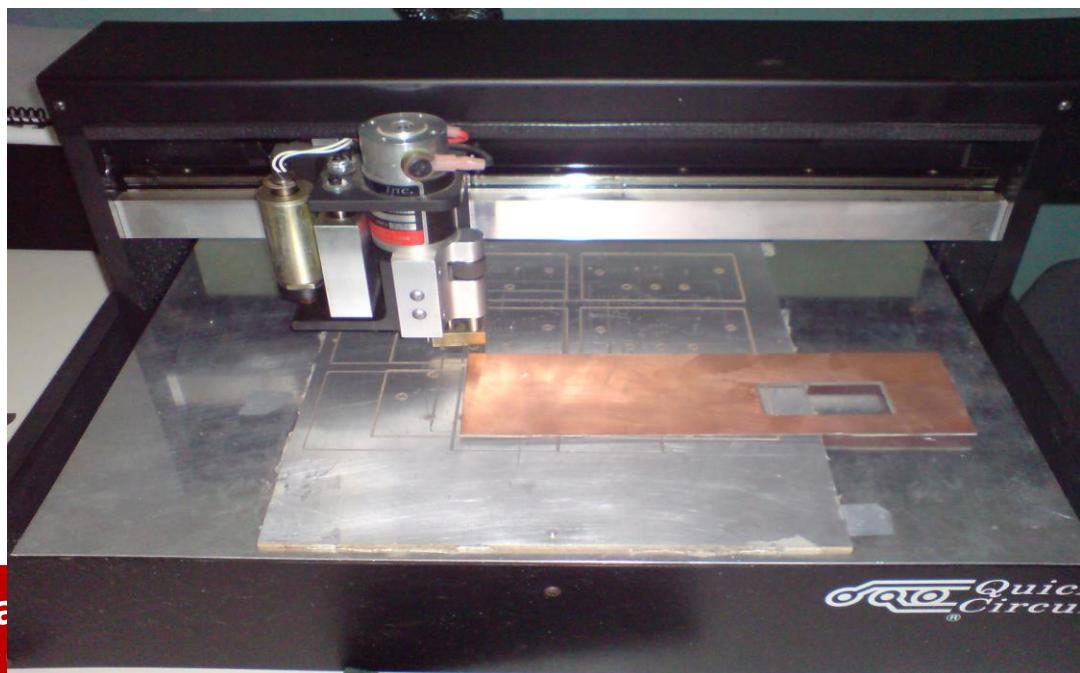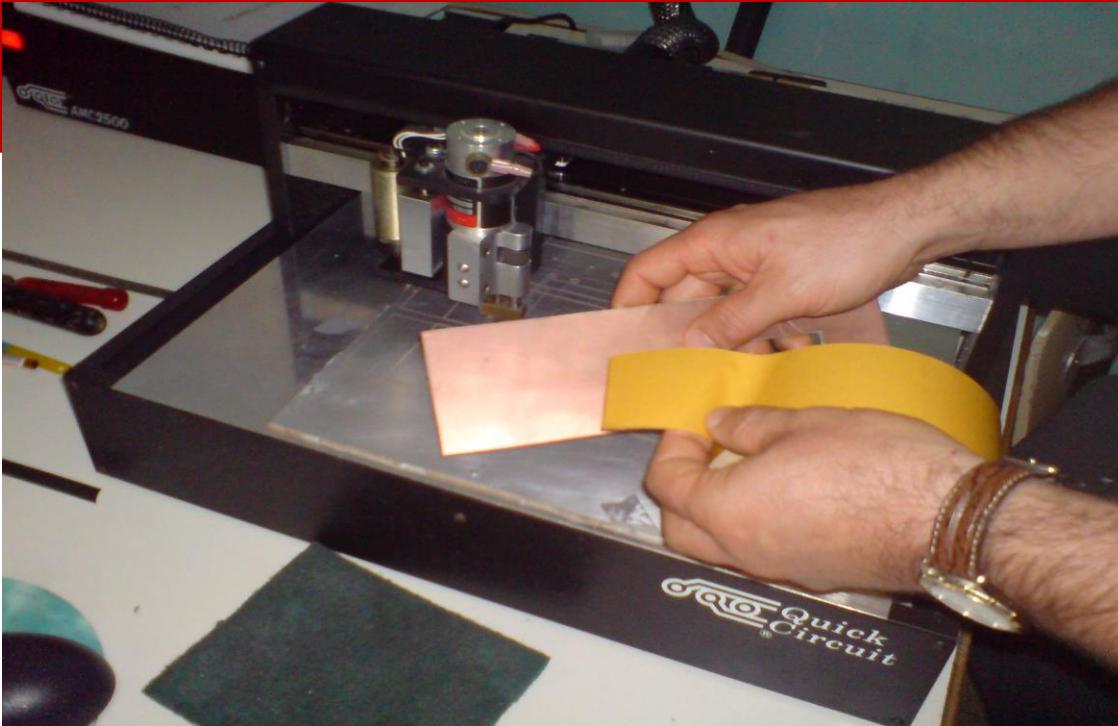


va After moving the
solenoid : +600 in y,

Use double-sided
tape to glue your FR4
layer to the engraving
table.

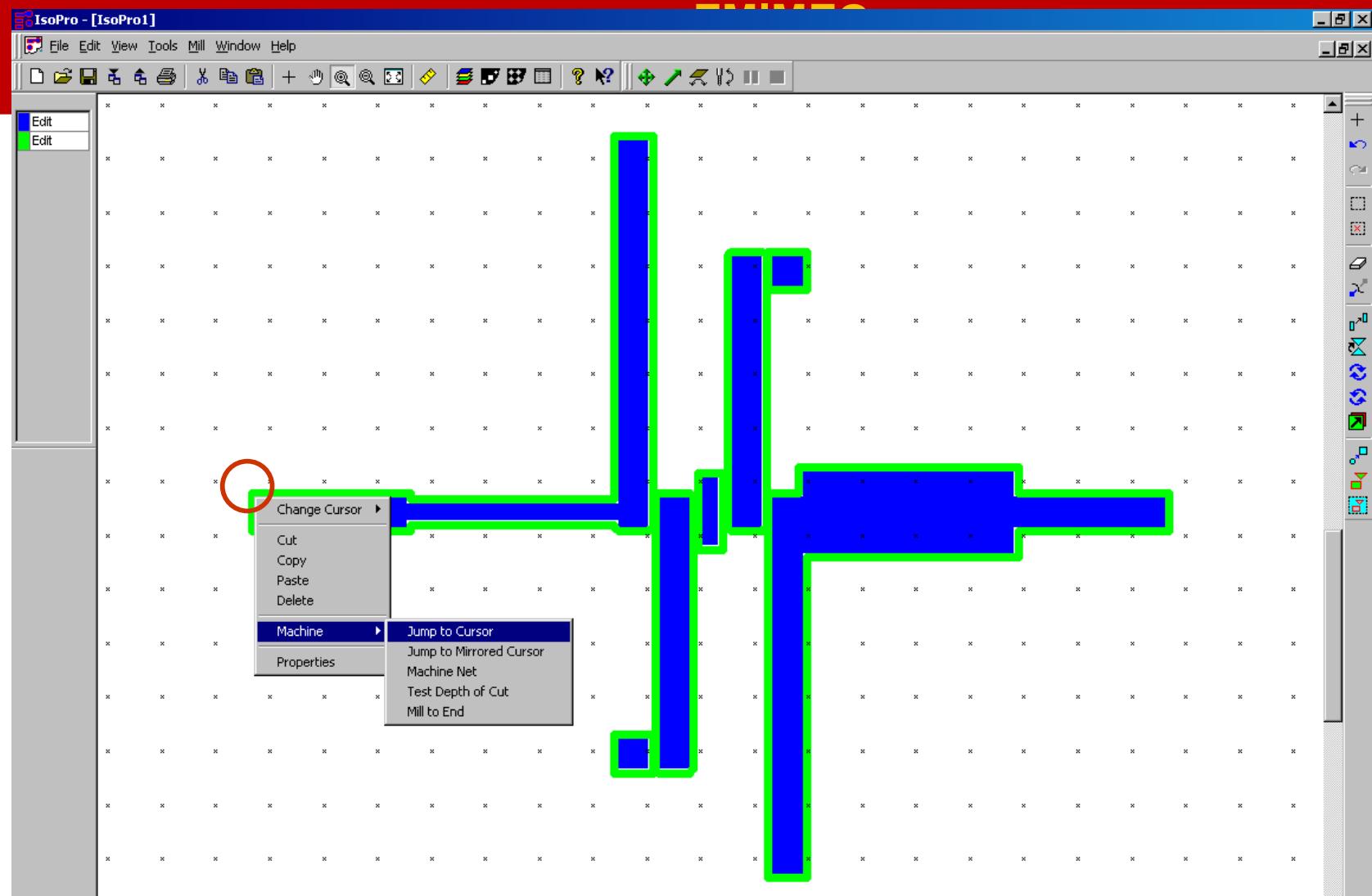
Make sure the
location of the plate
coincides with the
location of the mask
on ISOPRO



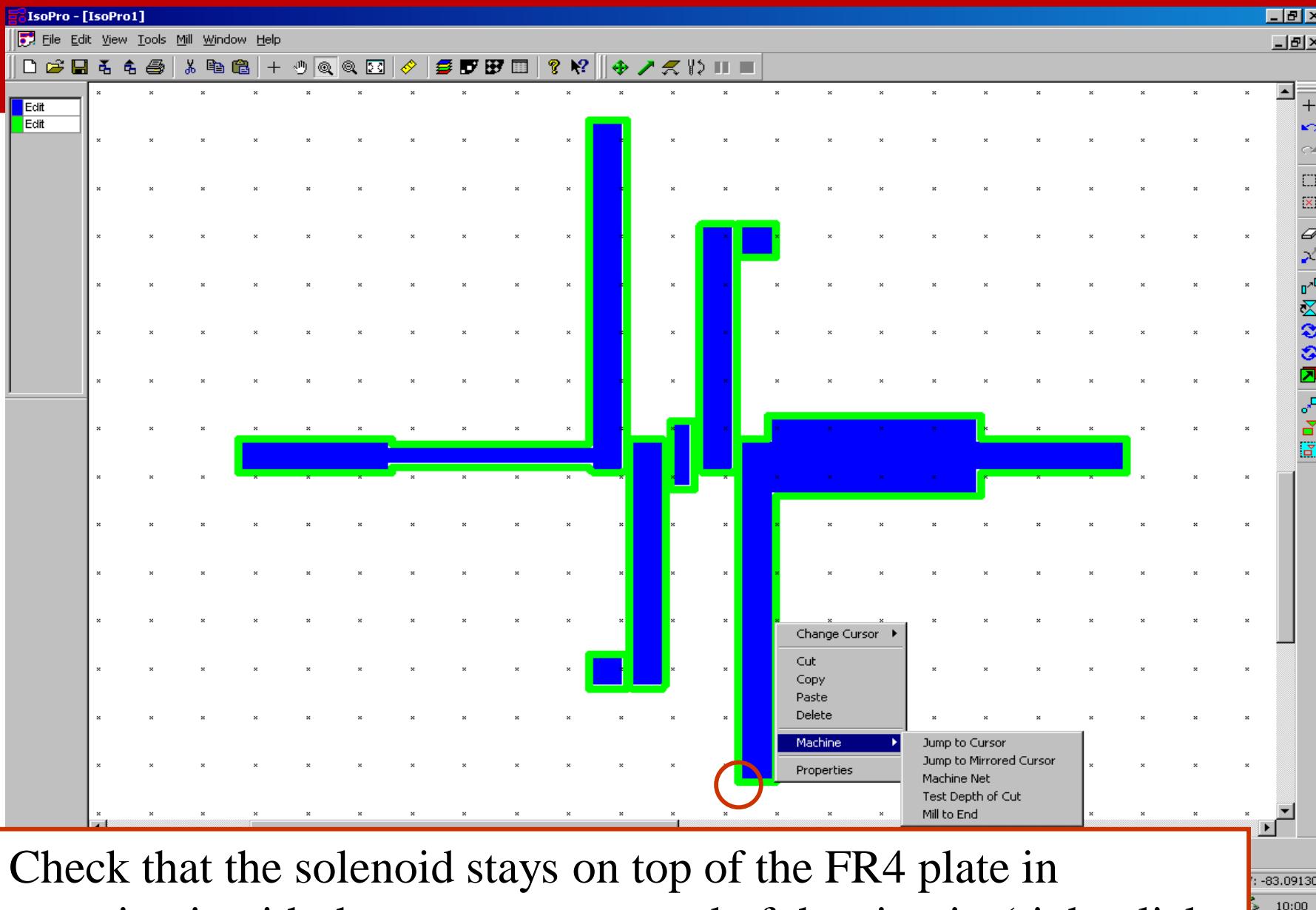
Check that the solenoid stays on top of the FR4 plate by moving it with the mouse at one end of the circuit: (right click: Jump to cursor)



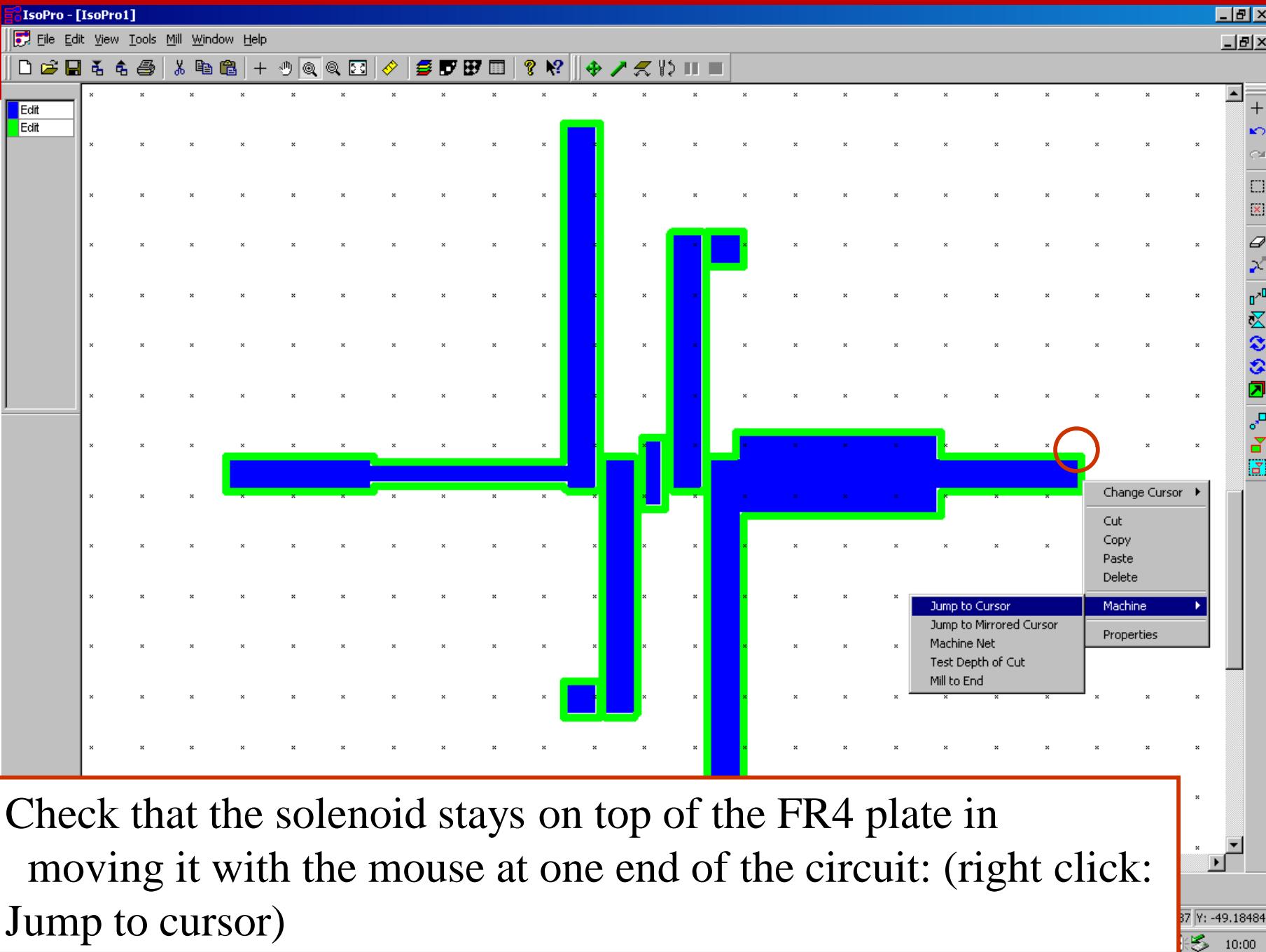
Check that the solenoid stays on top of the FR4 plate in moving it with the mouse at one end of the circuit: (right click: Jump to cursor)



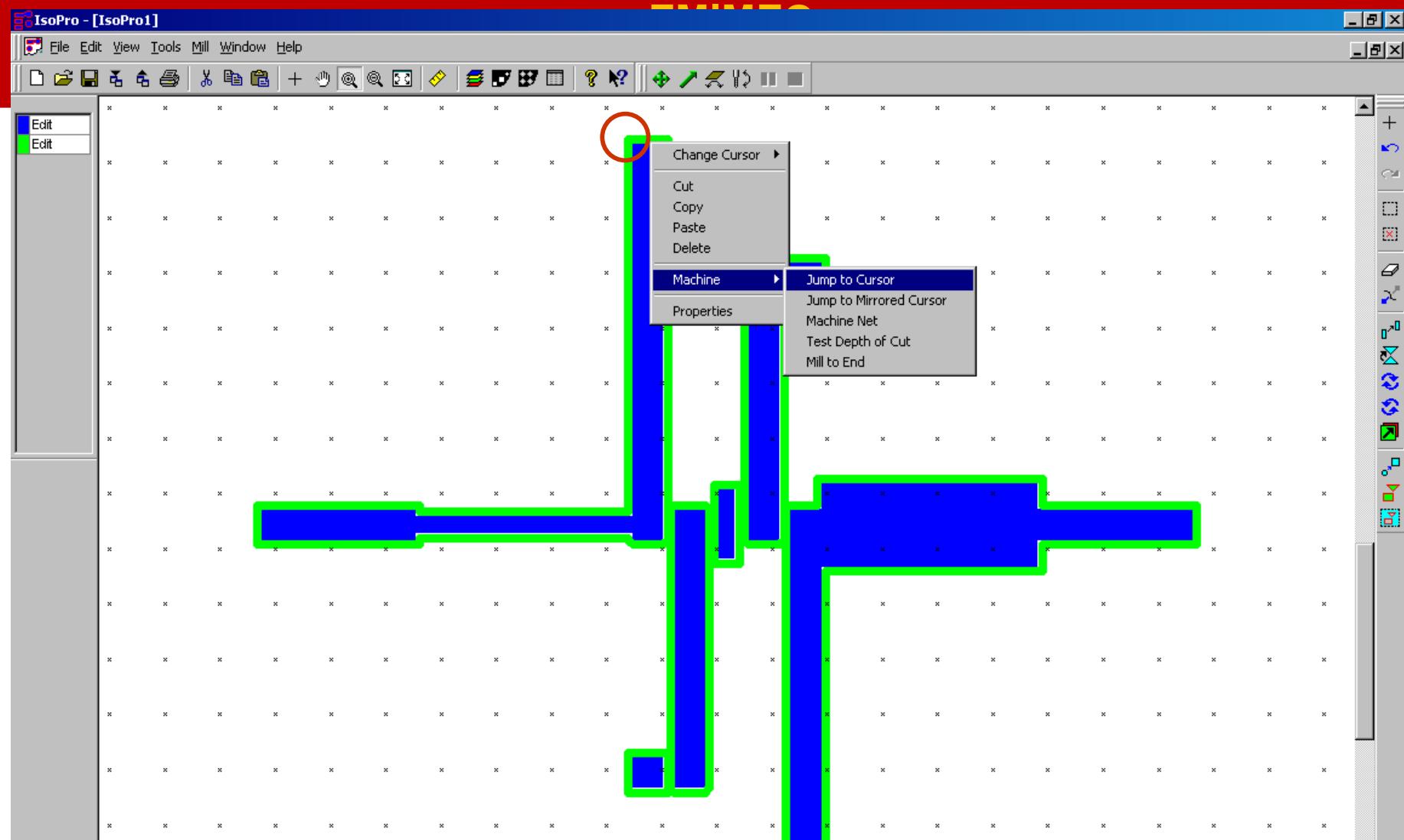
Check that the solenoid stays on top of the FR4 plate in moving it with the mouse at one end of the circuit: (right click: Jump to cursor)



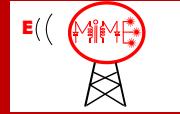
Check that the solenoid stays on top of the FR4 plate in moving it with the mouse at one end of the circuit: (right click: Jump to cursor)




E

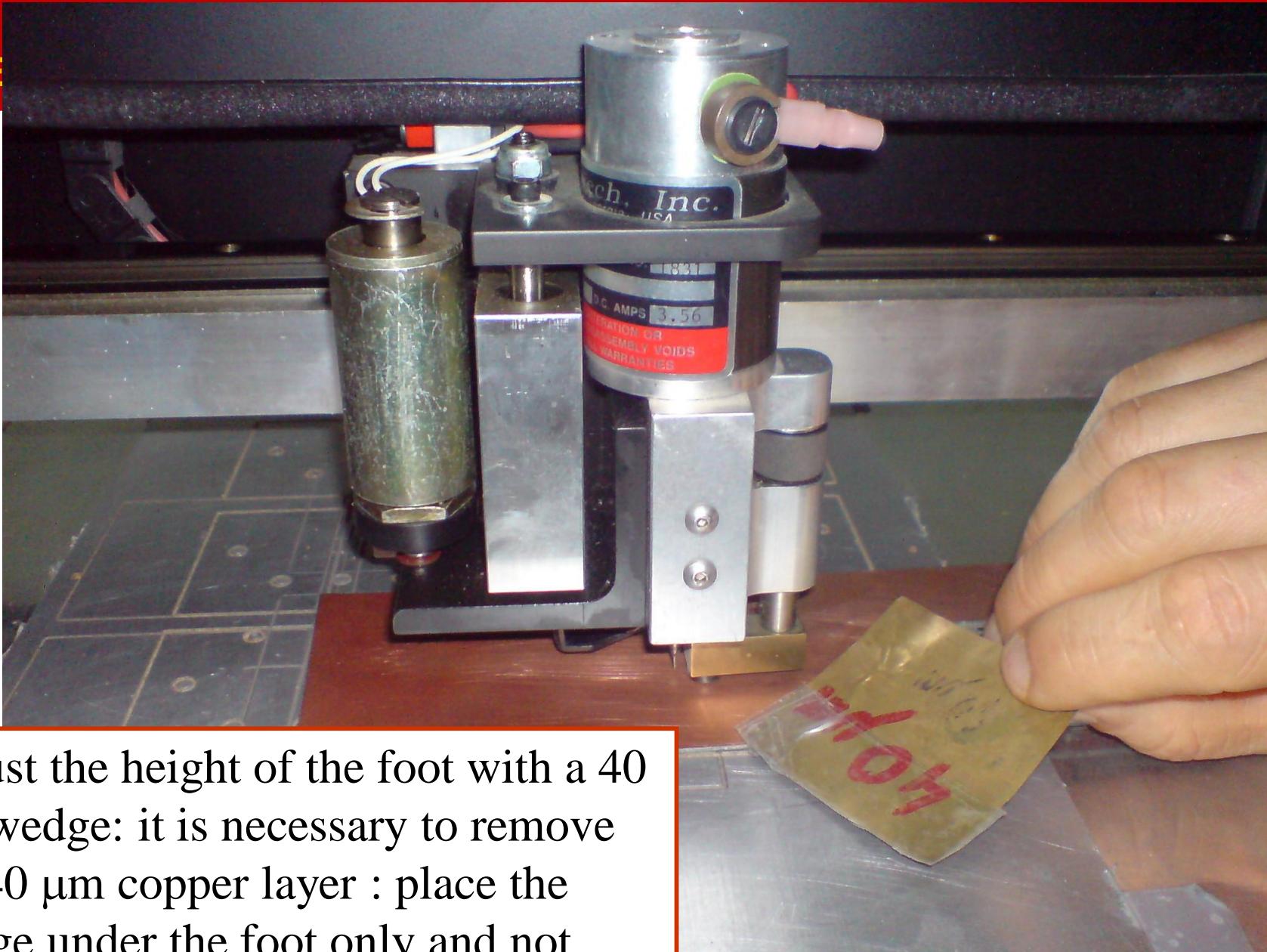


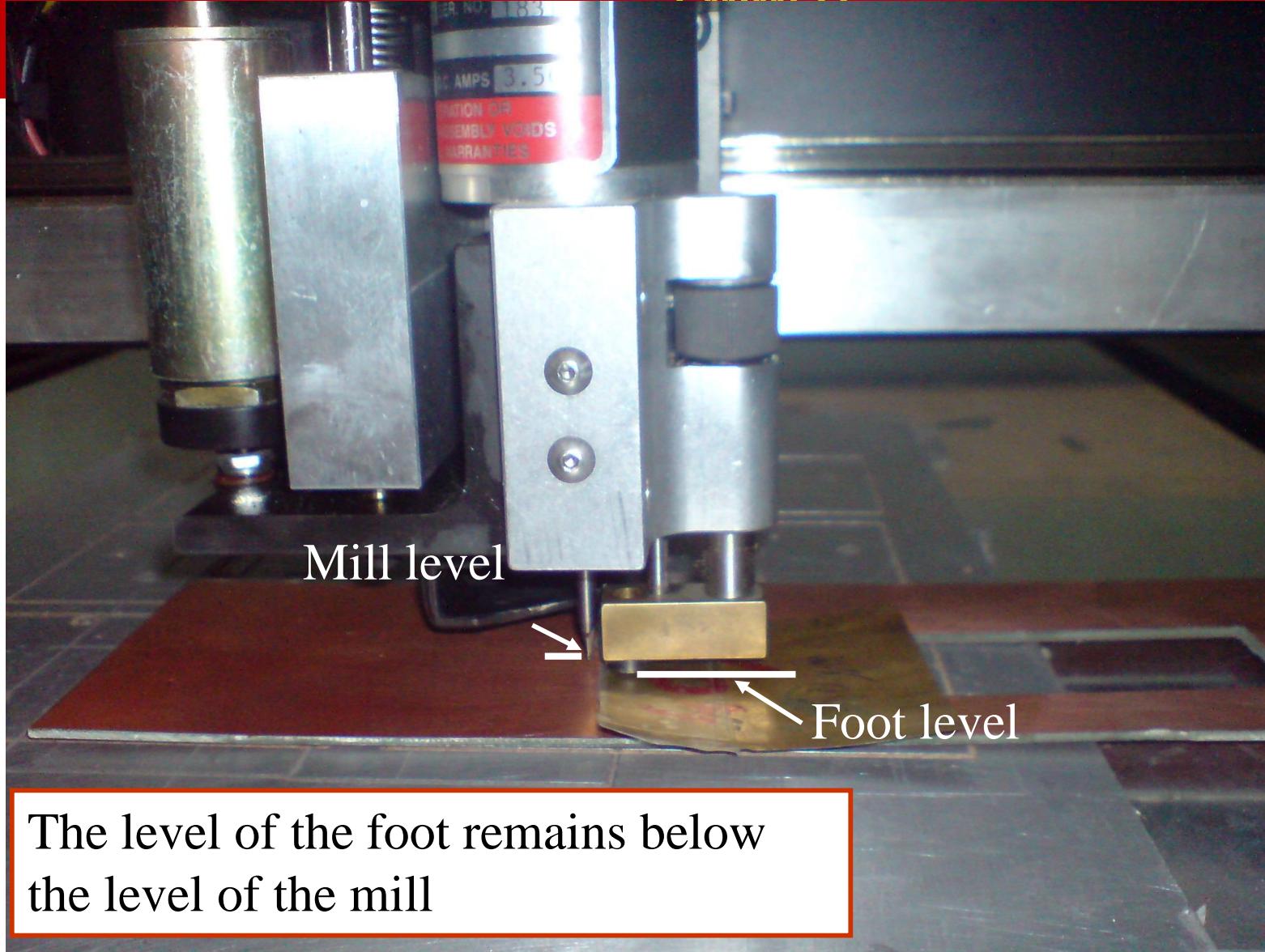Adjust the height of the foot with a 40 µm wedge: it is necessary to remove the 40 µm copper layer : place the wedge under the foot only and not under the mill



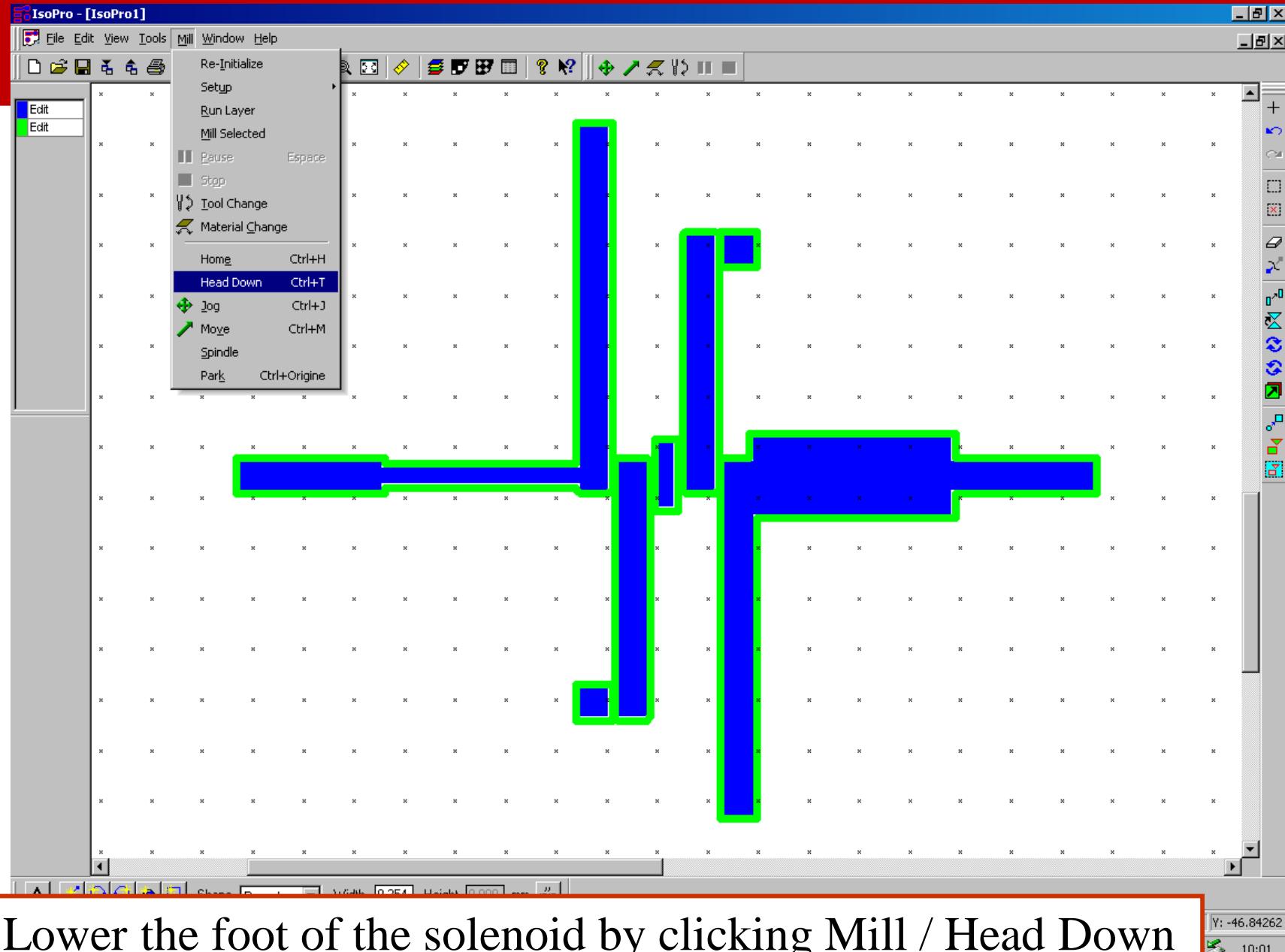


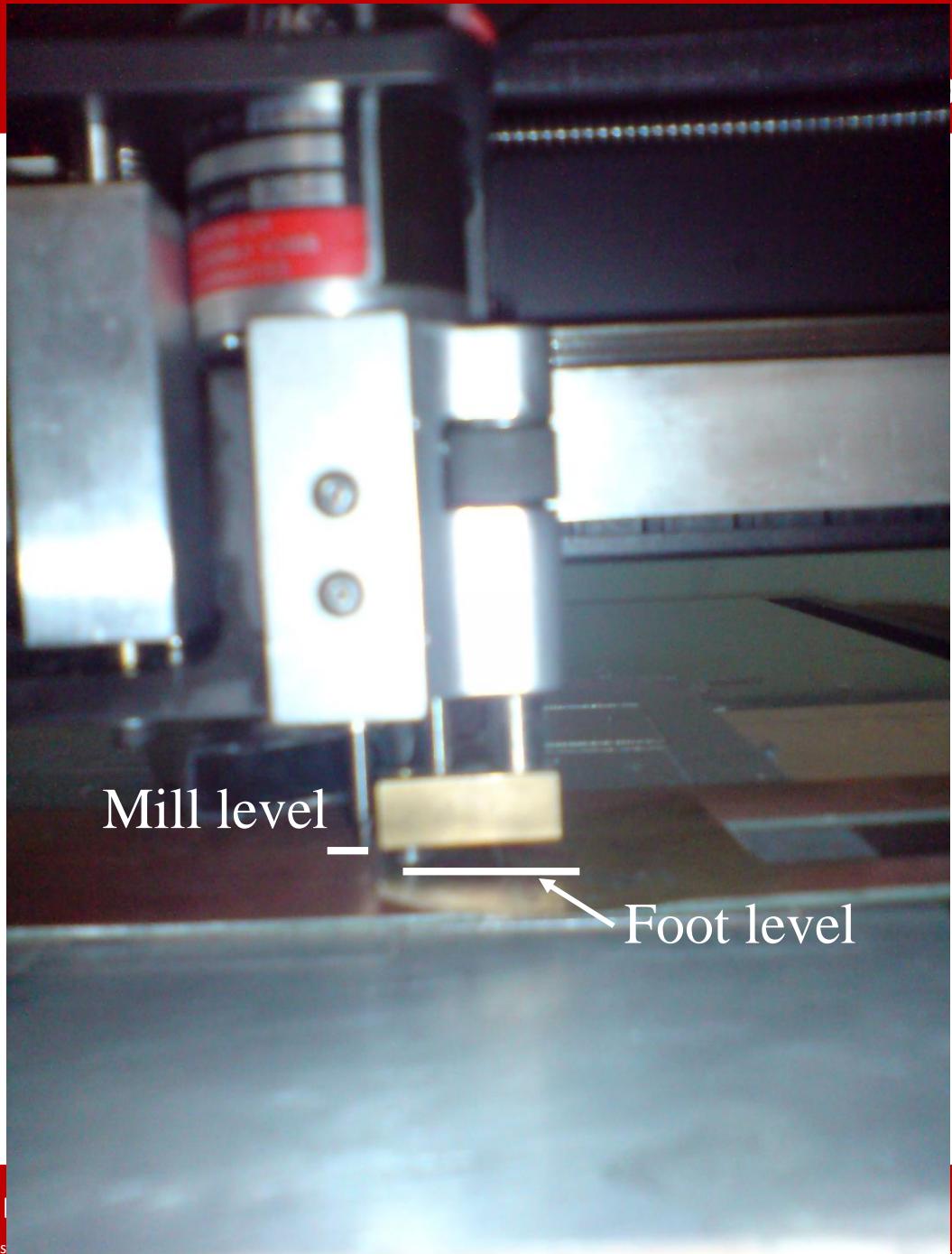Lower the foot of the solenoid by clicking Mill / Head Down



The foot blocks the hold.

The mill is always above the foot.

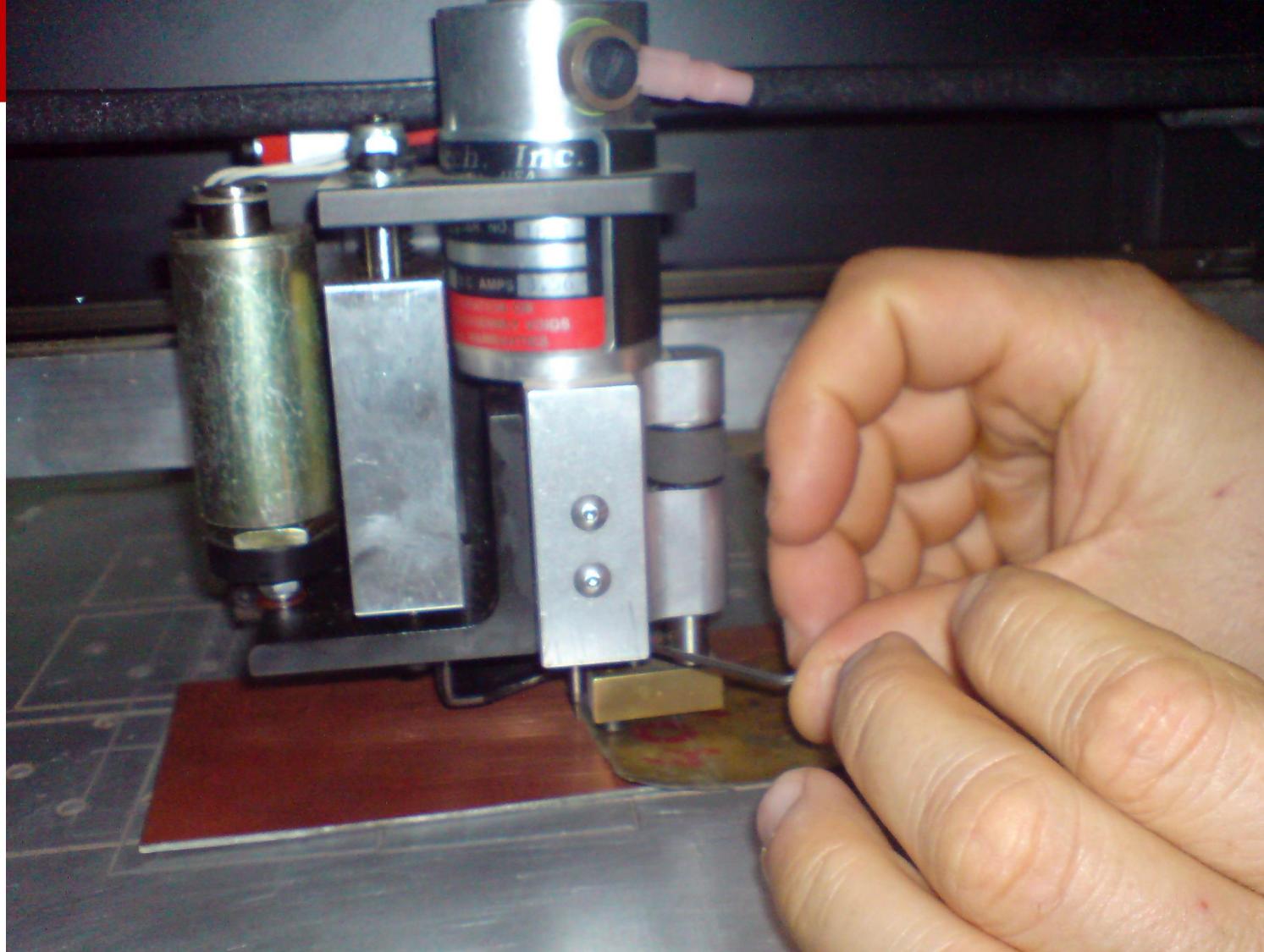


Lower the mill by unscrewing the clamping screw and tapping the solenoid

Basics of Active


Date

- 100 -

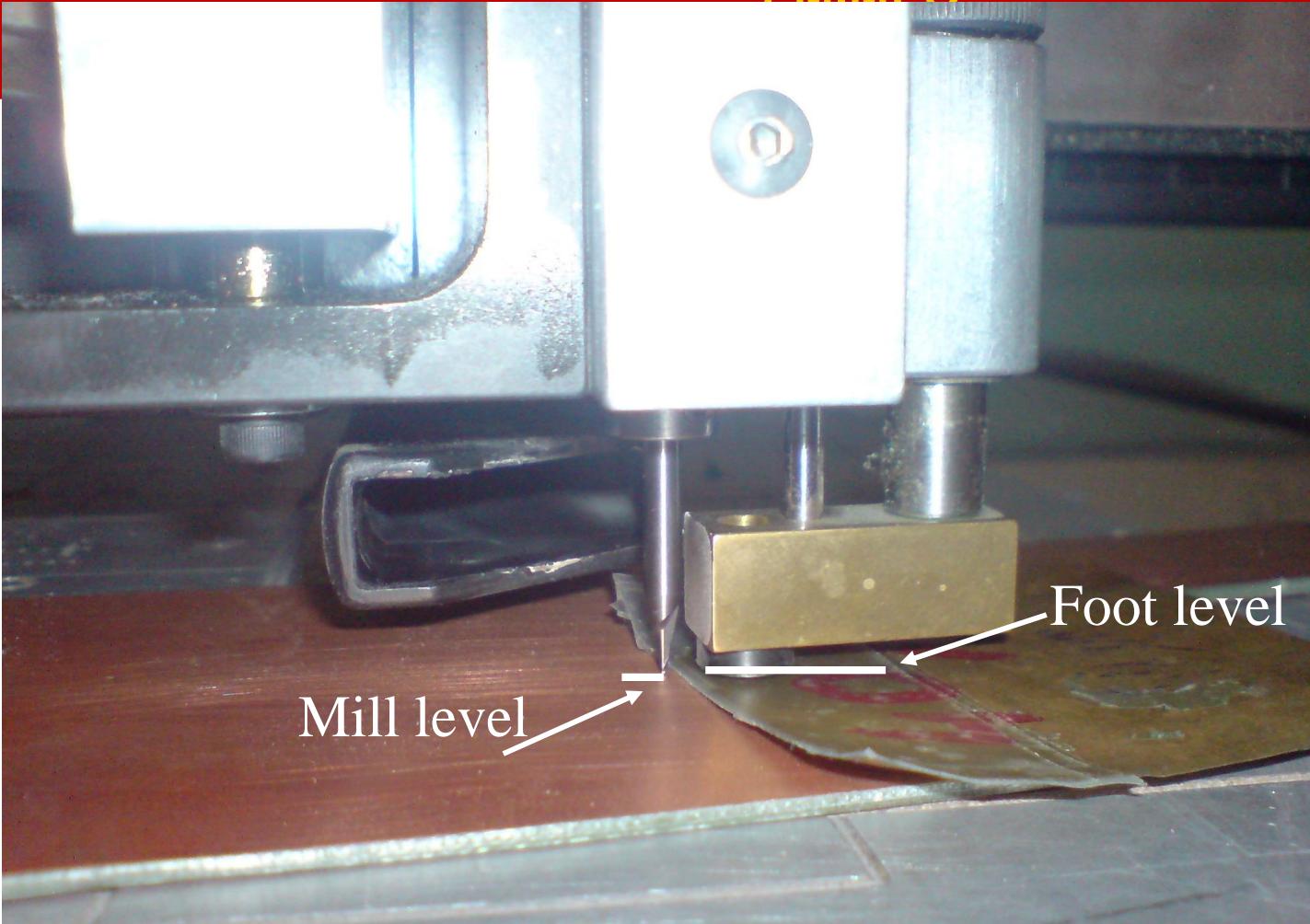


The foot blocks the hold.

The mill is now below the foot level.

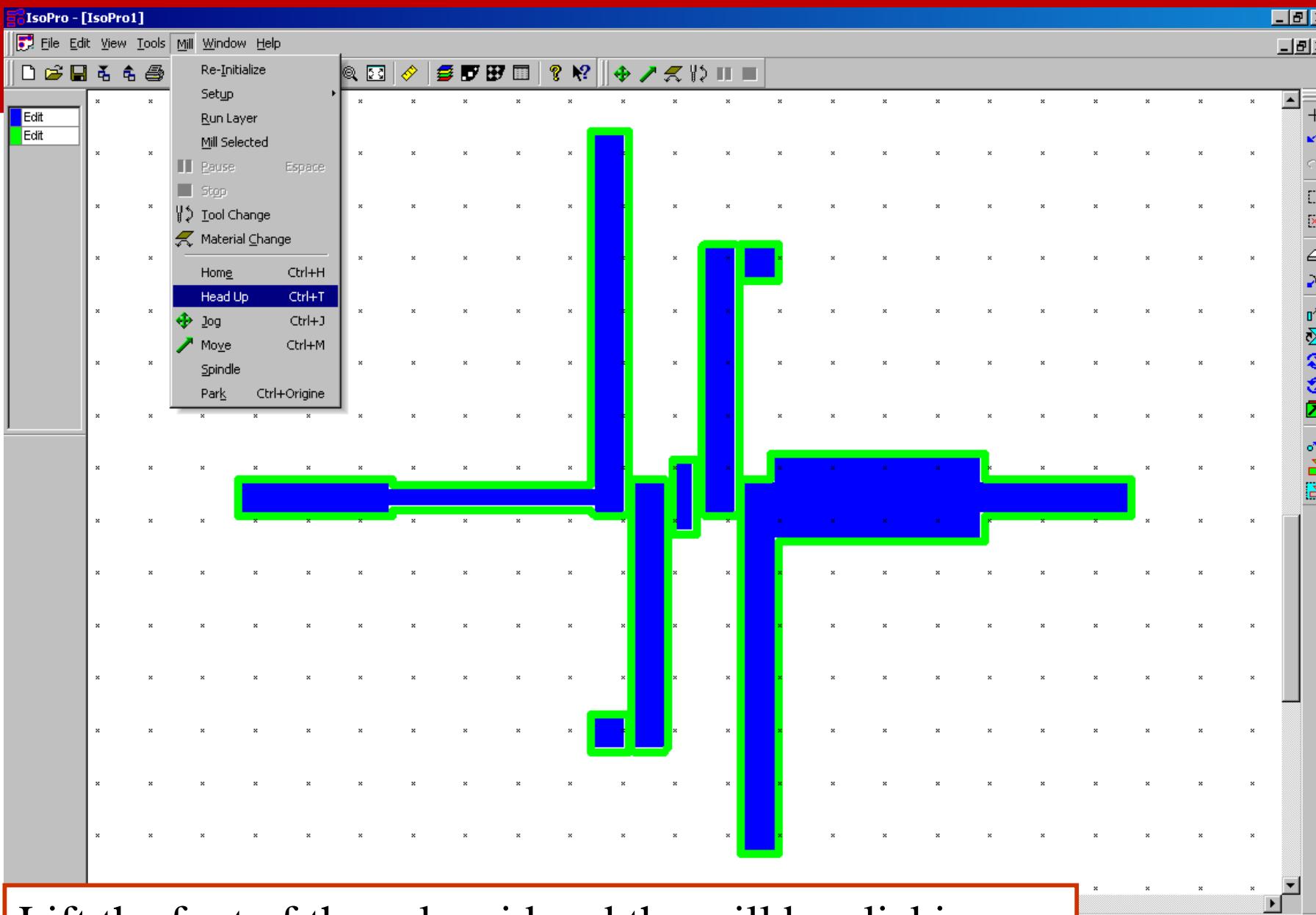


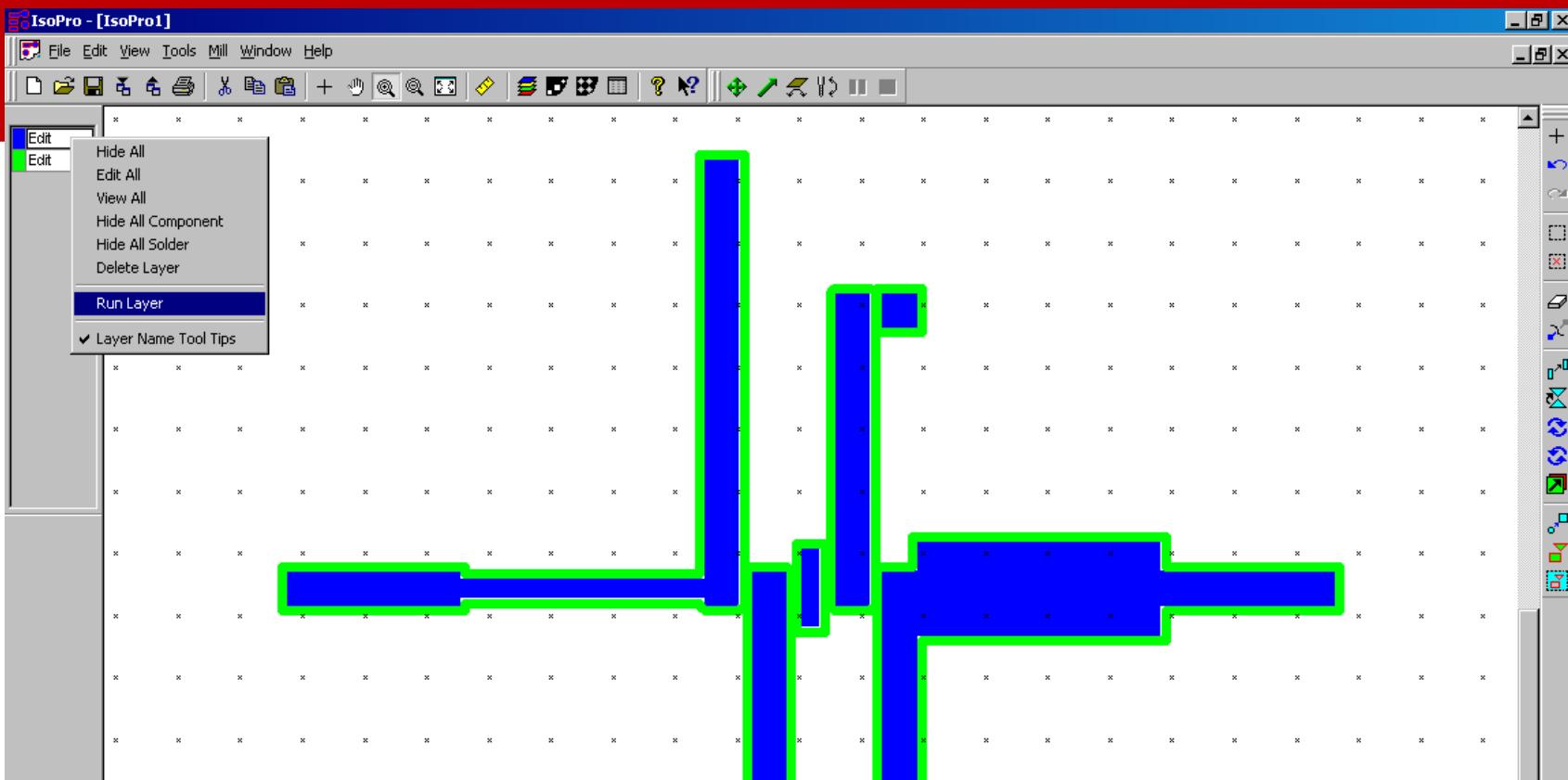Lift the foot of the solenoid and the mill by clicking on
Mill / Head up



Bring the mouse to the left menu and the green layer: click button right and select RUN LAYER: the vacuum starts, the mill rotates and the machine will outline the lines.

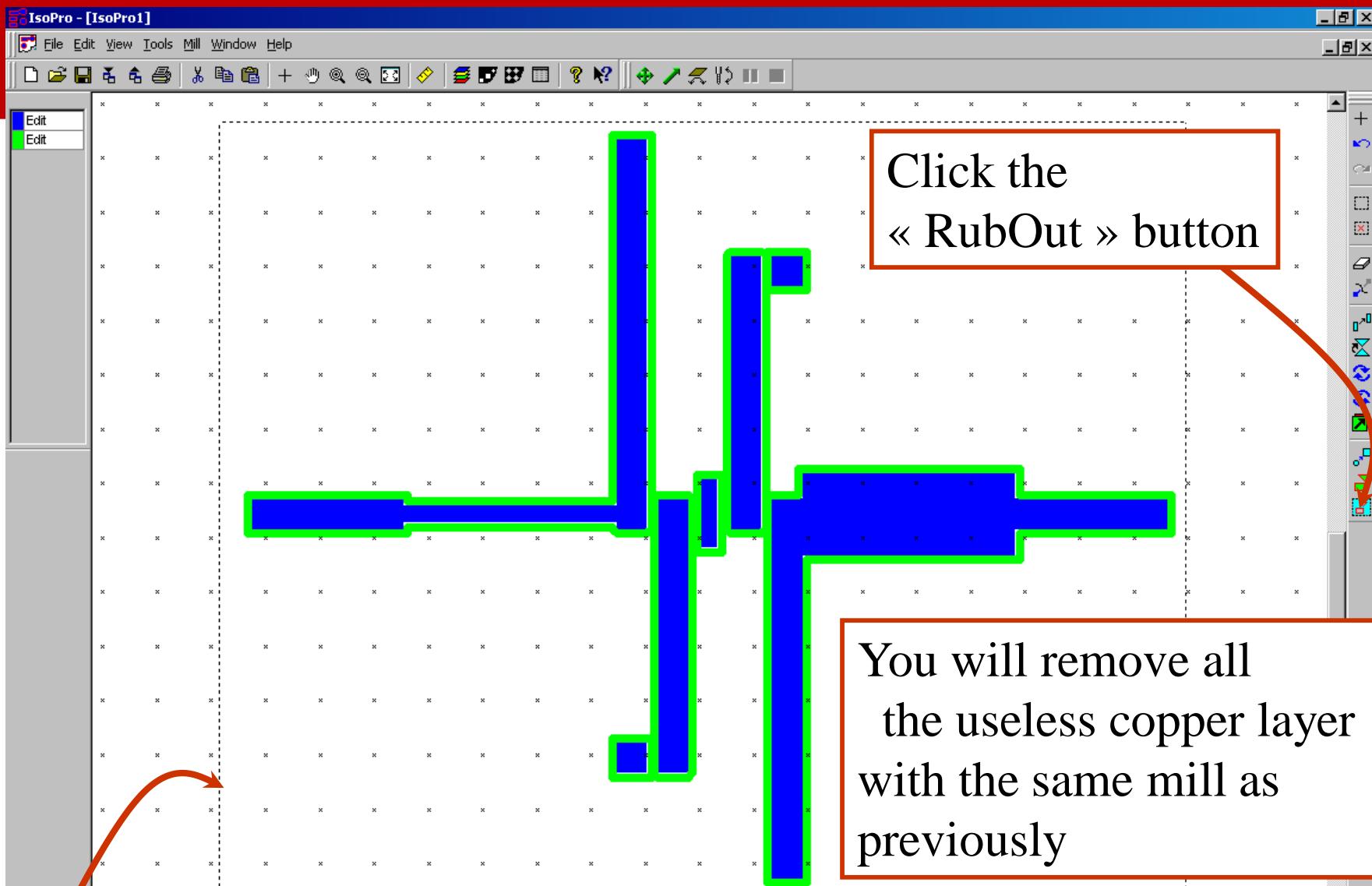
If it does not work the first time, select RUN LAYER a second time.




Click the
« RubOut » button

You will remove all
the useless copper layer
with the same mill as
previously

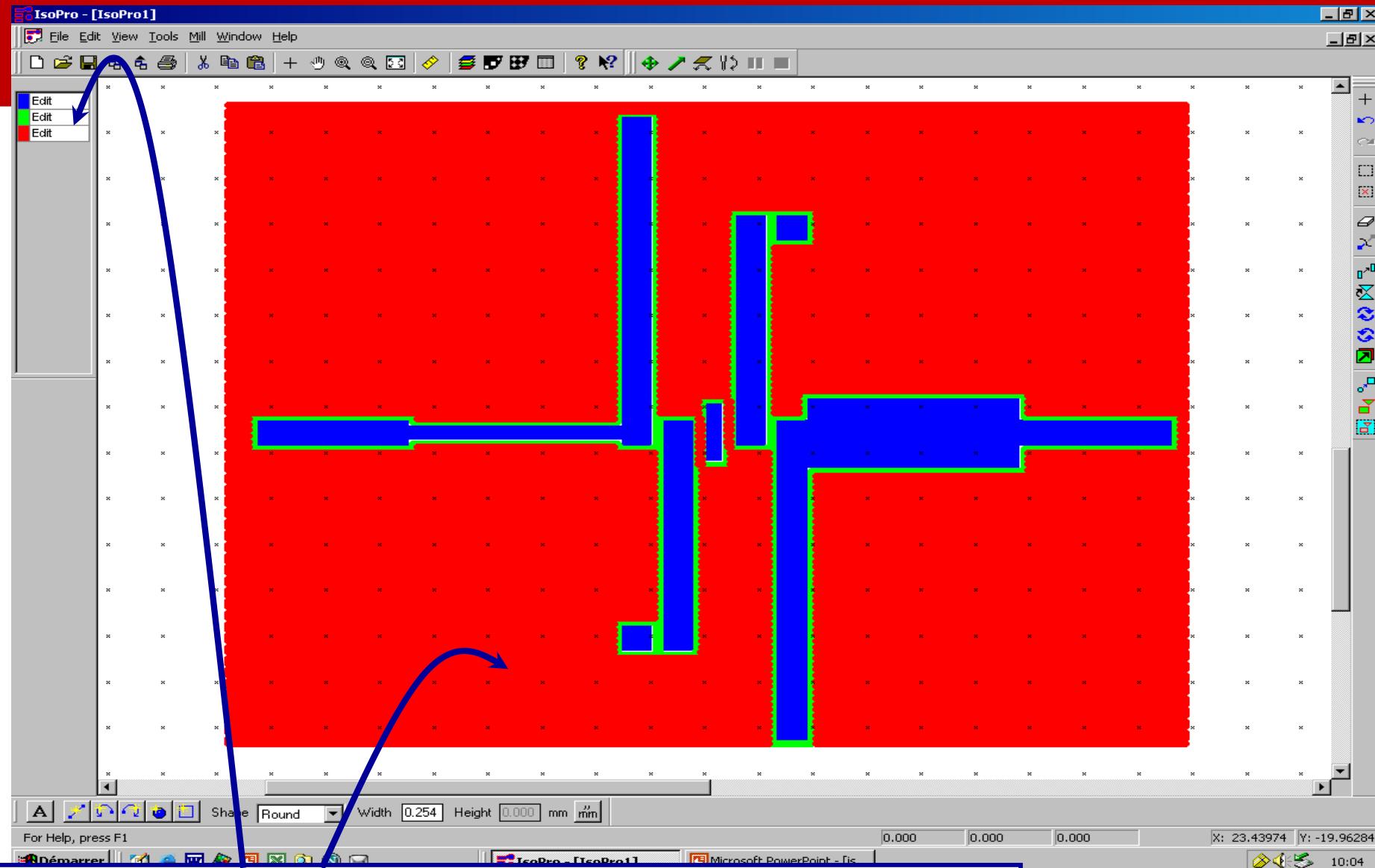Draw with the mouse the area of copper you wish to remove:
Left and right boundaries near lines. Leave some margin up and
down



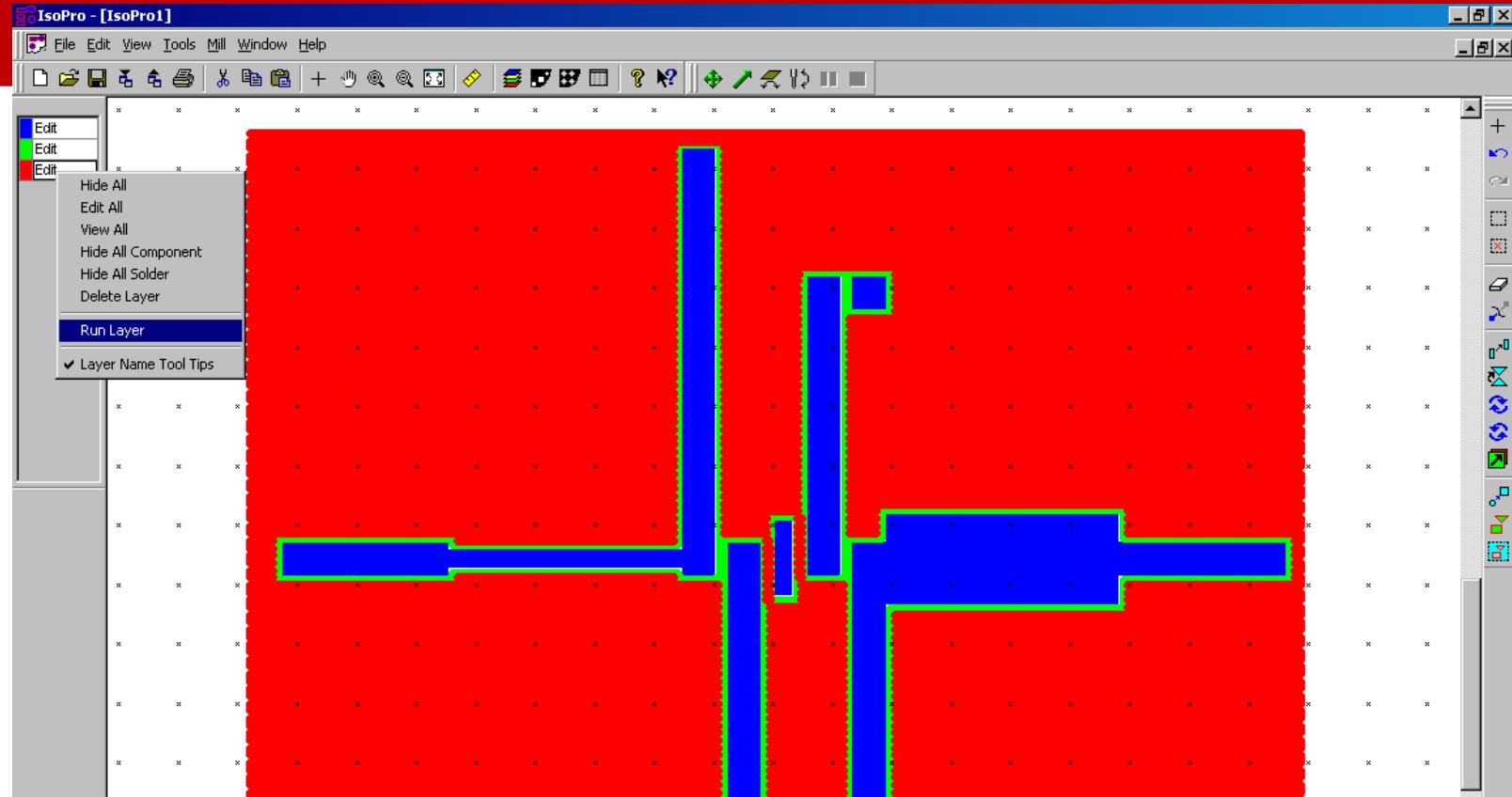The layer of "Rub Out" appears in red on the layout
and in the menu at the top left



Bring the mouse to the left menu and the red layer: click button right and select RUN LAYER: the vacuum starts, the mill rotates and the machine will remove unnecessary copper.

If it does not work the first time, select RUN LAYER a second time.


Date


Copyright notice : This material can be used freely but the European Commission. This publication reflects the views only of the author, and the Commission cannot be held responsible for any use which may be made of the information contained therein.


Once the copper layer is removed:

- 1°) move the bench and the solenoid as previously in
 $x = -300$ then $y = -300$
- 2°) when the chuck is out of the table, unscrew the clamping screw and remove the mill. Replace it immediately in its box.
- 3°) Replace the mill with a drill bit (Drill bit) which will allow to make the holes for the ground and screw the tightening screw.
- 4°) adjust the depth of the drill using a plate of FR4 + 2 wedges (20 and 40 μ m). Proceed as explained previously for adjusting the depth of the mill.

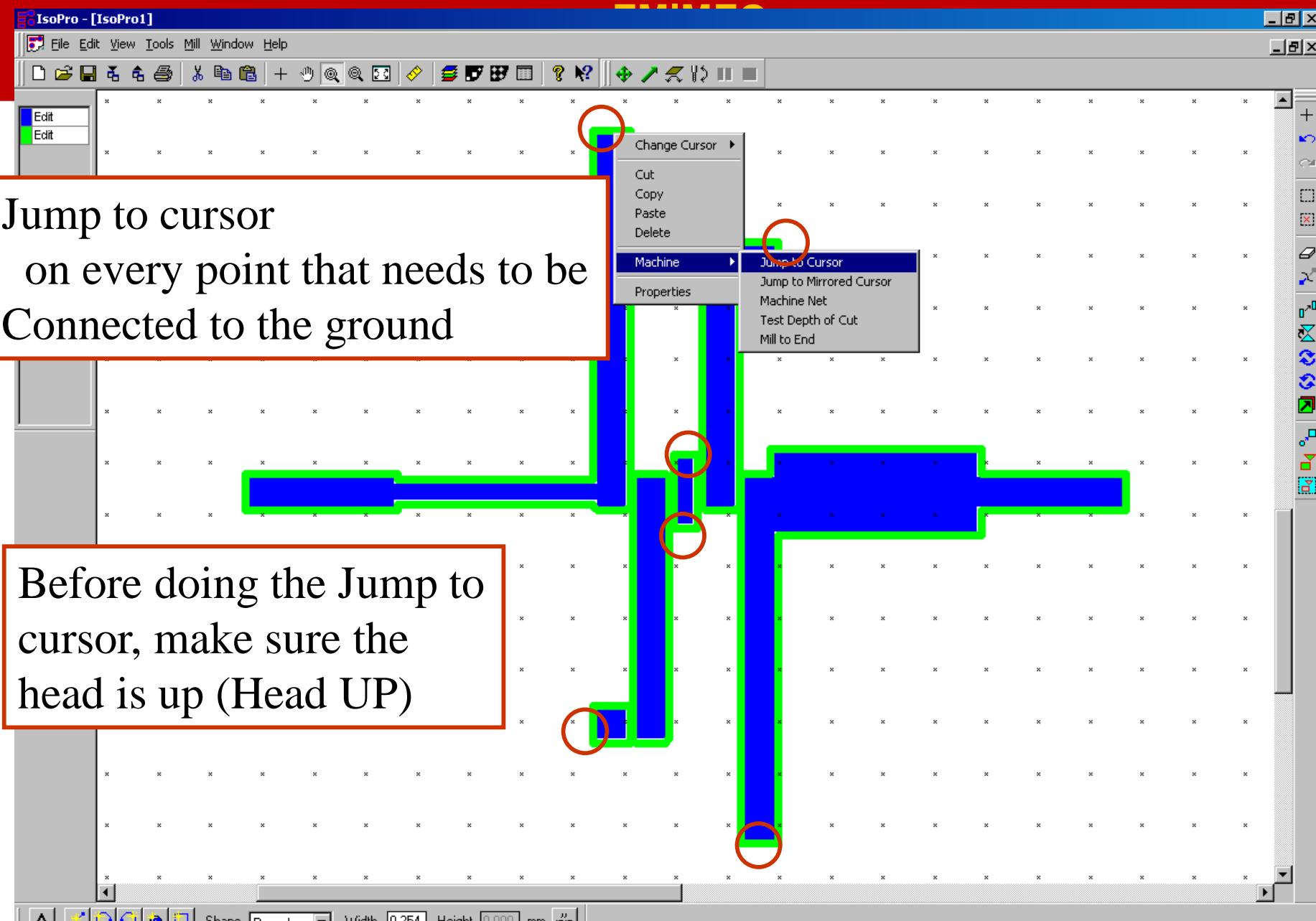
Another solution: you can also use the small drill in the room. In this case, in step 2 simply remove the mill and screw back the clamping screw then go to step 4 of the "Once copper layer removed" slide below



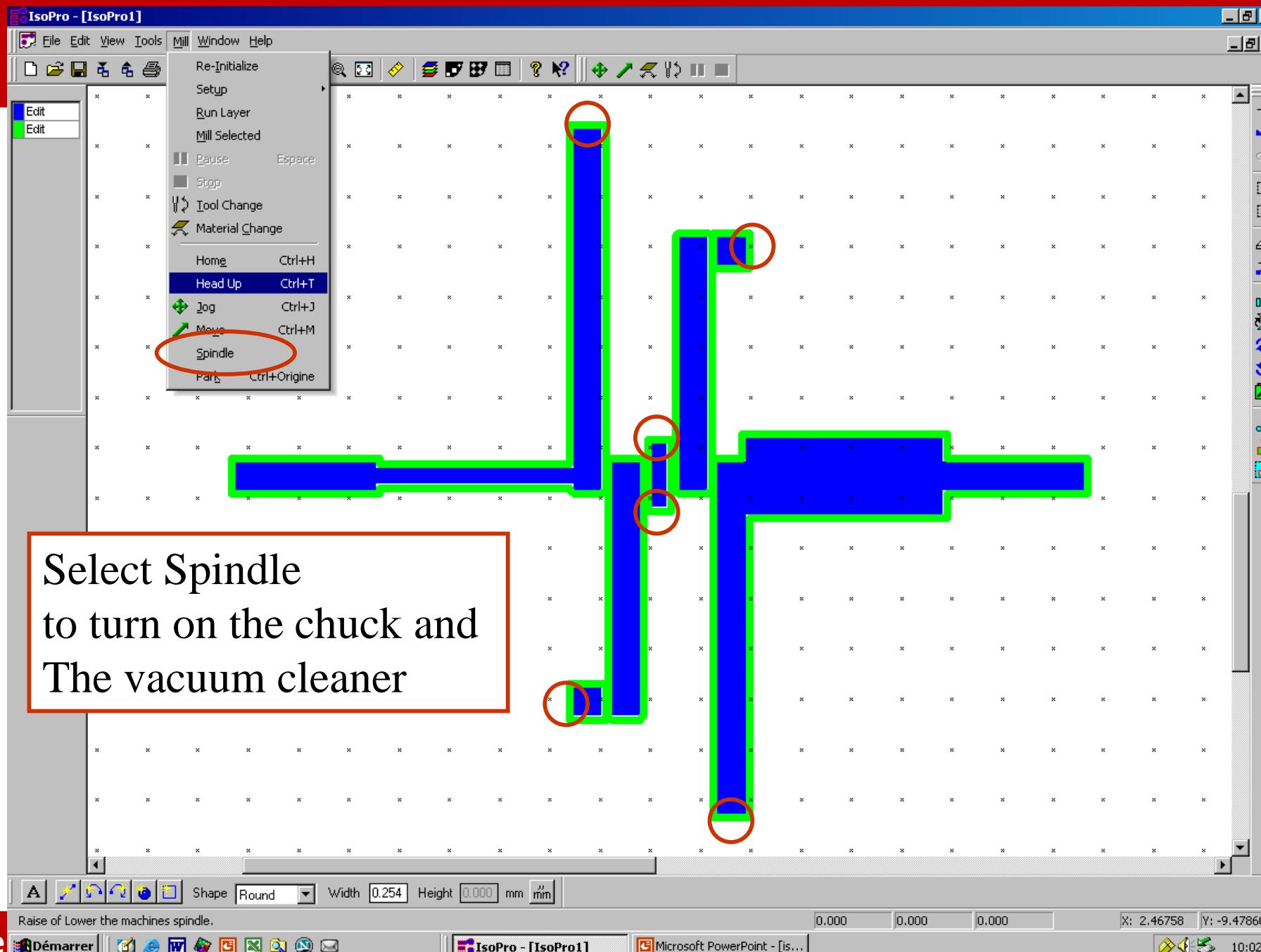


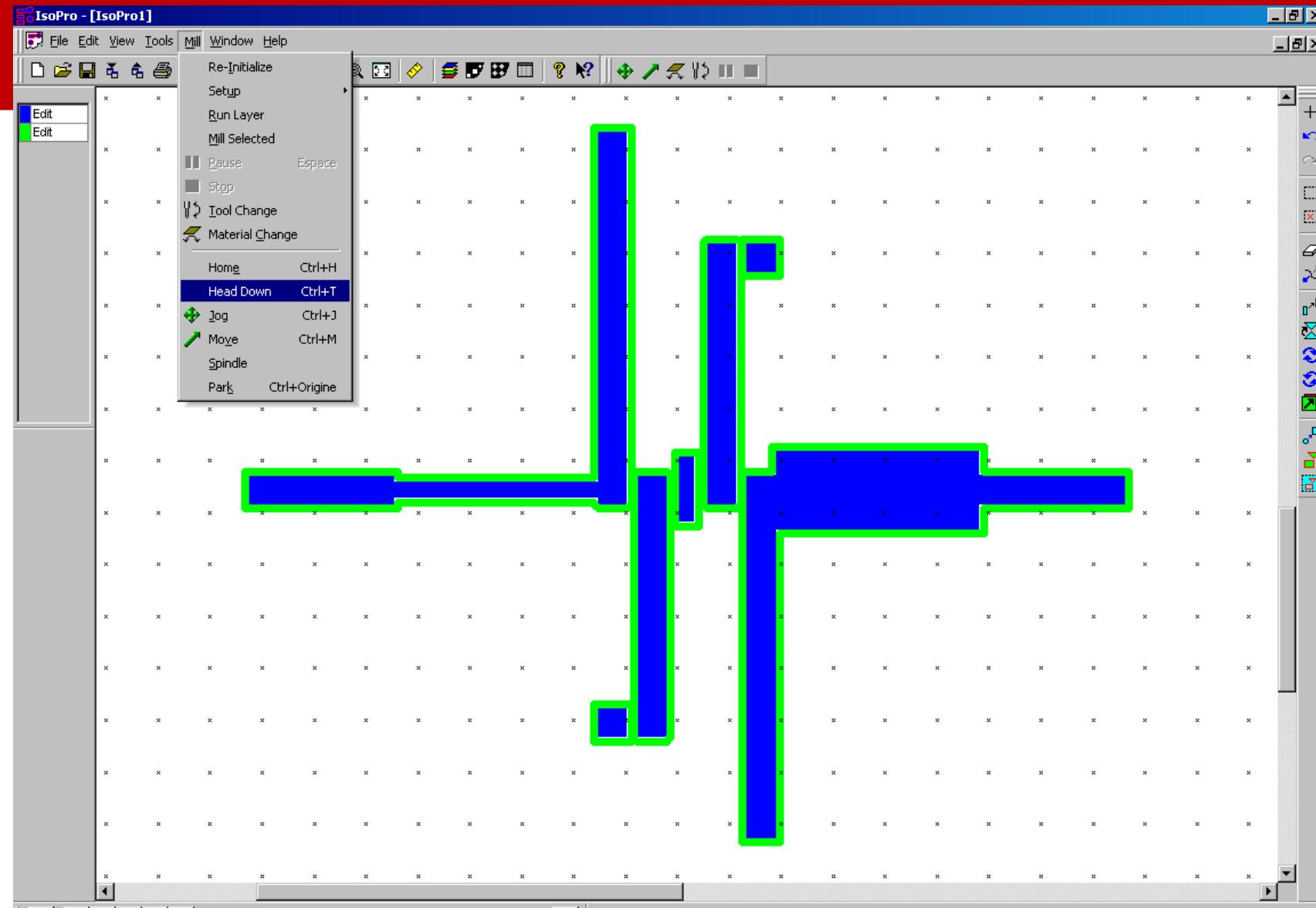

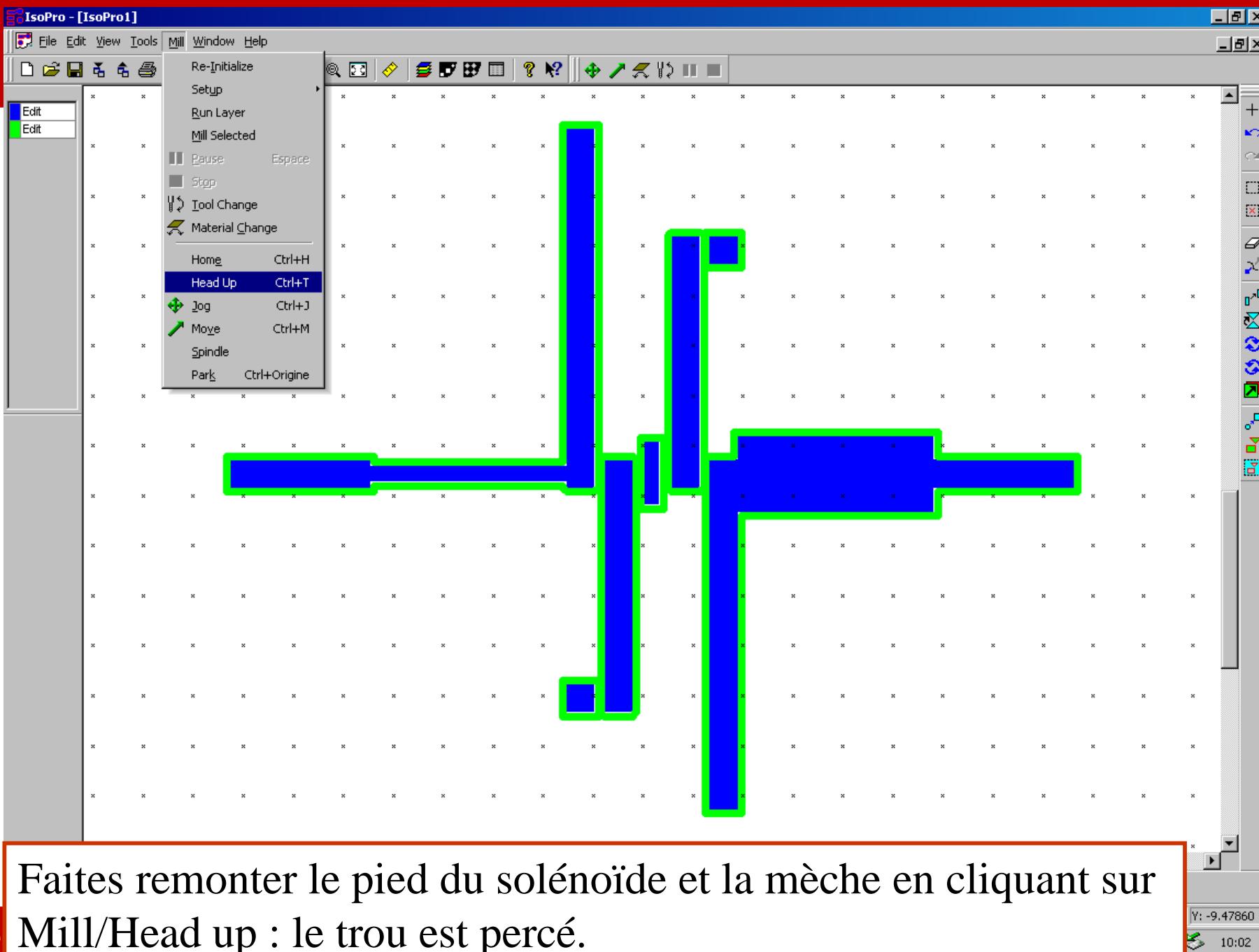Faites descendre le pied du solénoïde en cliquant sur Mill/Head Down



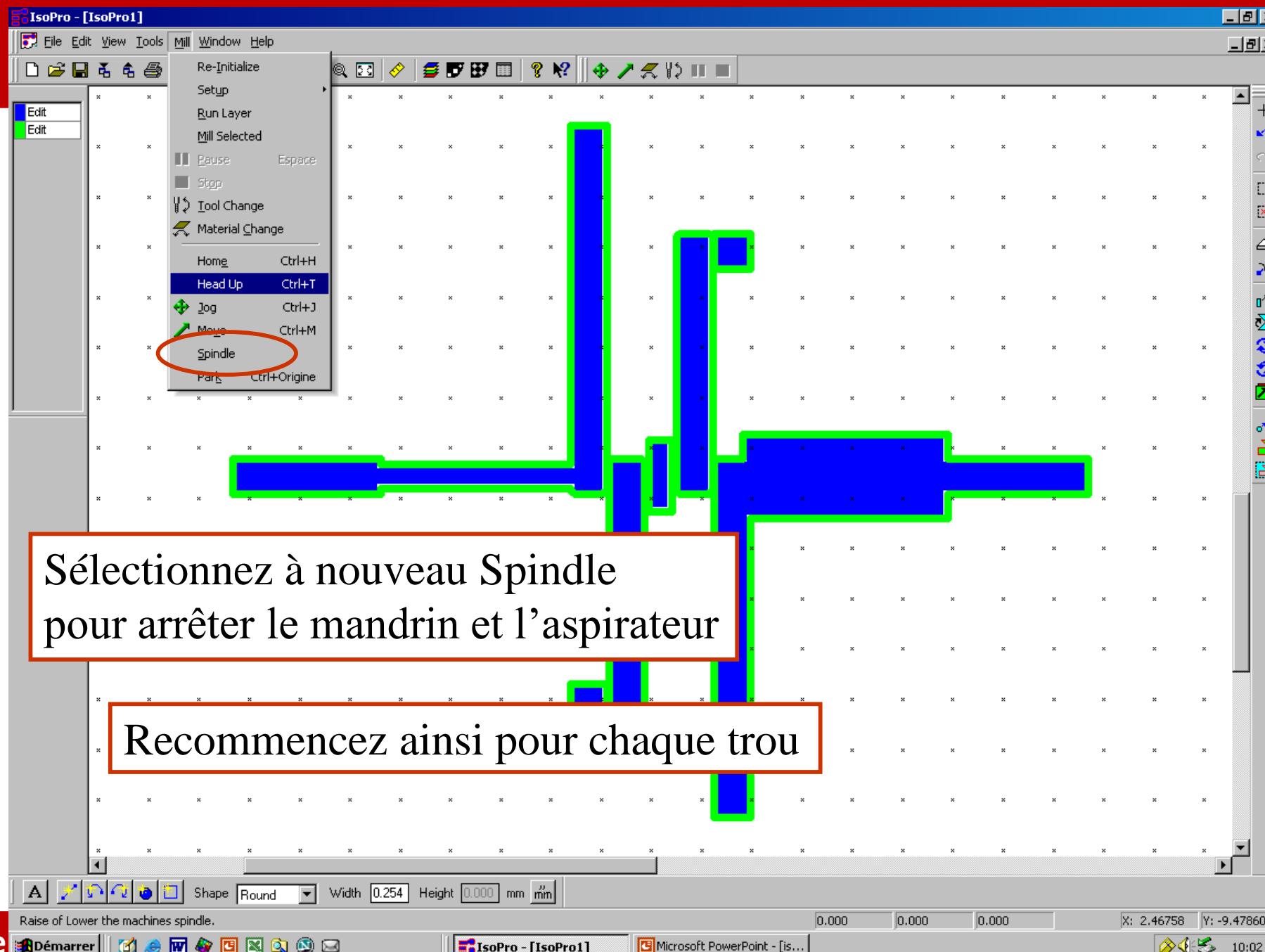Faites remonter le pied du solénoïde et la mèche en cliquant sur Mill/Head up : le trou est percé.





Once the copper layer is removed:

- 1°) move the bench and the solenoid as previously in
 $x = -300$ then $y = -300$
- 2°) when the chuck is out of the table, unscrew the clamping screw and remove the drill. Replace it immediately in its box.
- 3°) screw back the clamping screw
- 4°) move the bench and the solenoid as previously in
 $x = +600$.
- 5°) Unplug the vacuum at the back of the bench
- 6°) select Spindle and vacuum the chips on your plate
- 7°) Select Spindle again to stop vacuuming
- 8°) Clean your plate with the "scotch brite"
- 9°) peel off your FR4 plate from the table with a screwdriver
- 10°) Peel off the double-sided tape on the back of the plate and clean it with the "scotch brite"

11°) Look for soldering components: capacitors, transistors, ground wire, power supply wires, connectors

12°) Pass the wires in the ground holes and weld.

13°) Solder the other components.

The PA is complete: you must get:

