

# Problem 1

Firstly, we have the generator matched with the first transmission line because  $Z_g = 50 \Omega = Z_0$ , so there is not reflection and all the power is transmitted

$$P_{\text{generator}} = \frac{1}{2} |V_g|^2 \frac{1}{4 R_g} = \frac{1}{2} \cdot 20^2 \frac{1}{4 \cdot 50} = 1 \text{ W} \Rightarrow \boxed{P_g = 1 \text{ W}}$$

And because all the power is transmitted

$$\boxed{P_{\text{inc}} = P_g = 1 \text{ W}}$$

Secondly, in the junction between two transmission lines we know that:

$$T = 1 - \Gamma = \frac{2Z_1}{Z_1 + Z_0} \Rightarrow \Gamma = \frac{2Z_1}{Z_1 + Z_0} - 1 = \frac{2 \cdot 60}{60 + 50} - 1 \Rightarrow \boxed{\Gamma = 0,0909}$$

And the power transmitted is calculated,

$$P_{\text{trans}} = \frac{1}{2} |V_g|^2 \cdot \frac{R_{\text{in}}}{(R_{\text{in}} + R_g)^2 + (X_{\text{in}} + X_g)^2}$$

In this case  $R_{\text{in}} = 60 \Omega$   
because  $\lambda/2$  TL  $\Rightarrow$

$$\Rightarrow Z_{\text{in}} = Z_L = Z_1 = 60 \Omega$$


$$\text{And } X_{\text{in}} = X_g = 0$$

The reflected power:

$$P_{\text{ref}} = |\Gamma|^2 P_{\text{inc}} = 0,0909^2 \cdot 1 \Rightarrow \underline{P_{\text{ref}} = 0,0083 \text{ W}}$$

## Problem 2

The schematic will be:

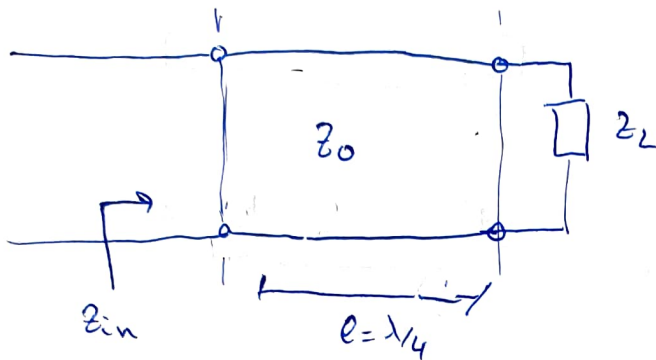

$$Z_{in} = 50 \Omega$$

$$Z_L = 10 \Omega$$

So we have:

$$Z_{in} = \frac{Z_0^2}{Z_L} \Rightarrow Z_0 = \sqrt{Z_{in} Z_L} = \sqrt{50 \cdot 10} \Rightarrow \boxed{Z_0 = 22,36 \Omega}$$

$$l = \frac{\lambda_0}{4} = \frac{\lambda_0}{\sqrt{\epsilon_r} \cdot 4} = \frac{c}{4 \cdot f \cdot \sqrt{\epsilon_r}} = \frac{3 \cdot 10^8}{4 \cdot 2 \cdot 10^9 \cdot \sqrt{2,25}} \Rightarrow \boxed{l = 2,25 \text{ cm}}$$

Using the given equation:

$$Z_0 = \frac{1}{2\pi} \sqrt{\frac{\mu}{\epsilon}} \ln\left(\frac{b}{a}\right) \Rightarrow \ln\left(\frac{b}{a}\right) = 2\pi Z_0 \sqrt{\frac{\epsilon_0 \epsilon_r}{\mu_0 \mu_r}} \overset{\mu_r=1}{=} 2\pi Z_0 \sqrt{\frac{\epsilon_0}{\mu_0}} \sqrt{\epsilon_r} \overset{\gamma_0 = \sqrt{\frac{\mu_0}{\epsilon_0}}}{=} \\ = \frac{2\pi Z_0}{\gamma_0} \sqrt{\epsilon_r} \overset{\gamma_0 = 120\pi}{=} \frac{2\pi Z_0}{120\pi} \sqrt{\epsilon_r} = \frac{Z_0}{60} \sqrt{\epsilon_r}$$

$$\Rightarrow \frac{b}{a} = e^{\frac{Z_0}{60} \sqrt{\epsilon_r}} = e^{\frac{22,36}{60} \sqrt{2,25}} = 1,74895$$

$$\boxed{\frac{b}{a} = 1,74895} \rightarrow \boxed{a = 1 \text{ cm}, b = 1,74895 \text{ cm}}$$

### Problem 3

The general formula for cut-off frequency:

$$f_{c_{nm}} = \frac{1}{2n} \cdot \frac{c}{\sqrt{\epsilon_r}} \sqrt{\left(\frac{np}{a}\right)^2 + \left(\frac{mp}{b}\right)^2}$$

Working in W-band the dimensions are:

$$a = 2,850 \text{ cm}$$

$$b = 1,262 \text{ cm}$$

① 4 first modes

medium: air  $\Rightarrow \epsilon_r = 1$

$$f_{c_{10}} = 5,26 \text{ GHz} \quad f_{c_{01}} = 11,89 \text{ GHz}$$

$$f_{c_{20}} = 10,53 \text{ GHz} \quad f_{c_{11}} = 13 \text{ GHz}$$

② 4 first modes

medium: teflon  $\Rightarrow \epsilon_r = 2,08$

$$f_{c_{10}} = \frac{5,26}{\sqrt{\epsilon_r}} = 3,65 \text{ GHz} \quad f_{c_{01}} = \frac{11,89}{\sqrt{\epsilon_r}} = 8,24 \text{ GHz}$$

$$f_{c_{20}} = \frac{10,53}{\sqrt{\epsilon_r}} = 7,3 \text{ GHz} \quad f_{c_{11}} = \frac{13}{\sqrt{\epsilon_r}} = 9,01 \text{ GHz}$$

If we operate at  $f = 9 \text{ GHz}$ :

$$\rightarrow V_{\text{teflon}} = \frac{c}{\sqrt{\epsilon_r}} = 2,08 \cdot 10^8 \text{ m/s}$$

→ Phase velocity:

$$V_{\phi} = \frac{\omega}{\beta_{nm}}$$

with

$$\beta_{nm} = \sqrt{\left(\frac{\omega}{c/\epsilon_r}\right)^2 - \left(\frac{n\pi}{a}\right)^2 - \left(\frac{m\pi}{b}\right)^2}$$

$$V_{\phi_{TE_{10}}} = 2,276 \cdot 10^8 \text{ m/s}$$

$$V_{\phi_{TE_{20}}} = 2,557 \cdot 10^8 \text{ m/s}$$

$$V_{\phi_{TE_{01}}} = 5,178 \cdot 10^8 \text{ m/s}$$

→ Group velocity

$$V_g = \frac{\beta_{nm}}{2\pi f} \frac{c^2}{\epsilon_r}$$

$$V_{g_{TE_{10}}} = 1,901 \cdot 10^8 \text{ m/s}$$

$$V_{g_{TE_{20}}} = 1,216 \cdot 10^8 \text{ m/s}$$

$$V_{g_{TE_{01}}} = 0,836 \cdot 10^8 \text{ m/s}$$