

Microwave Engineering


Homework 3

Solution


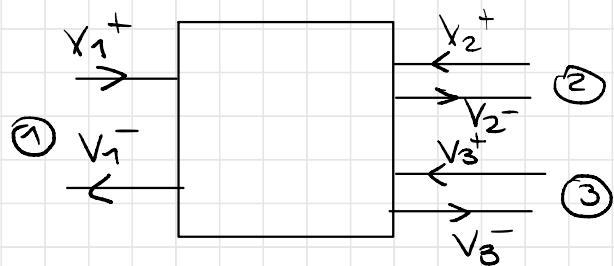
#1

$$[S] = \frac{1}{2} \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix}$$



a) The device is RECIPROCAL since $S_{ij} = S_{ji}$

b) The device is LOSSY since

$$|S_{11}|^2 + |S_{12}|^2 + |S_{13}|^2 \neq 1$$

c) The device IS MATCHED at all ports since $S_{ii} = 0$
 $(S_{11} = S_{22} = S_{33} = 0)$

d) Output ports 2 and 3 are NOT ISOLATED since
 $S_{23} = S_{32} \neq 0$

Let's consider $V_1^+ = 10V$ and output ports terminated with matched loads.

e) Calculate voltage at ports ② and ③ :

$$S_{21} = S_{12} = \frac{V_2^+}{V_1^+}$$

$$V_2^- = S_{21} V_1^+ = \frac{1}{2} V_1^+ = 5V$$

$$V_3^- = S_{31} V_1^+ = \frac{1}{2} V_1^+ = 5V$$

$V_2 = V_2^-$ and $V_3 = V_3^-$ since ports 2 and 3 are matched

④ Power available at ports ② and ③ is :

$$P_2 = \frac{1}{2} \frac{|V_2|^2}{Z_0} = \frac{1}{2} \frac{25}{50} = 0.25W$$

$$P_3 = P_2 = 0.25W \text{ since } V_2 = V_3$$

⑤ Dissipated power

$$P_1 = \frac{1}{2} \frac{|V_1|^2}{Z_0} = \frac{1}{2} \frac{100}{50} = 1W$$

$$P_{\text{loss}} = P_1 - P_2 - P_3 = 0.5 \text{ W}$$

□

0


#2

First mode is associated with the fundamental mode TE_{10} .

$$f_{c101} = \frac{c}{2\pi} \sqrt{\left(\frac{\pi}{a}\right)^2 + \left(\frac{\pi}{d}\right)^2} = 5 \text{ GHz}$$

\downarrow
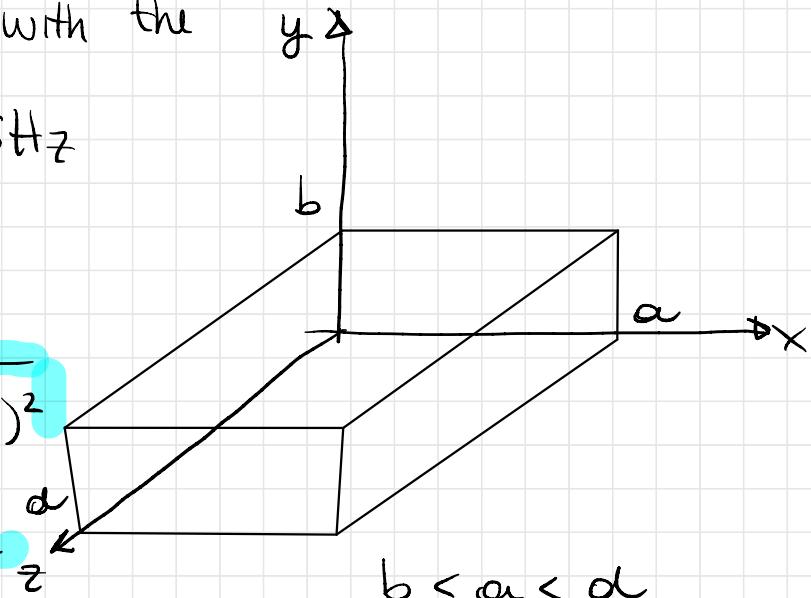
$$\boxed{\frac{1}{a^2} + \frac{1}{d^2} = \left(\frac{2.5 \cdot 10^9}{3 \cdot 10^8}\right)^2 = (83.3)^2}$$



The modes that follow are either TM_{110} , TE_{102} or TE_{011} with associated frequencies:

$$f_{110} = \frac{c}{2} \sqrt{\frac{1}{a^2} + \frac{1}{b^2}}$$

$$f_{102} = \frac{c}{2} \sqrt{\frac{1}{a^2} + \frac{4}{d^2}}$$

Since $d > a$
 $f_{011} < f_{110}$

$$f_{011} = \frac{c}{2} \sqrt{\frac{1}{b^2} + \frac{1}{d^2}}$$

From geometrical considerations it follows that the second and third mode are f_{102} and f_{011} .
 So we can write:

$$f_{102} = \frac{c}{2} \sqrt{\frac{1}{a^2} + \frac{4}{d^2}} = 6.5 \text{ GHz} \Rightarrow \boxed{\frac{1}{a^2} + \frac{4}{d^2} = (43.3)^2}$$

$$f_{011} = \frac{c}{2} \sqrt{\frac{1}{b^2} + \frac{1}{d^2}} = 7.2 \text{ GHz} \Rightarrow \frac{1}{b^2} + \frac{1}{d^2} = (48)^2$$

Solving for a , b and d we get

$d = 6.25 \text{ cm}$
$a = 3.42 \text{ cm}$
$b = 2.2 \text{ cm}$

$$d > a > b$$

We can verify that


$$f_{110} = \frac{c}{2} \sqrt{\frac{1}{a^2} + \frac{1}{b^2}} = 8.1 \text{ GHz}$$

> 7.2 GHz
(third mode)

#3

T network

Port 1

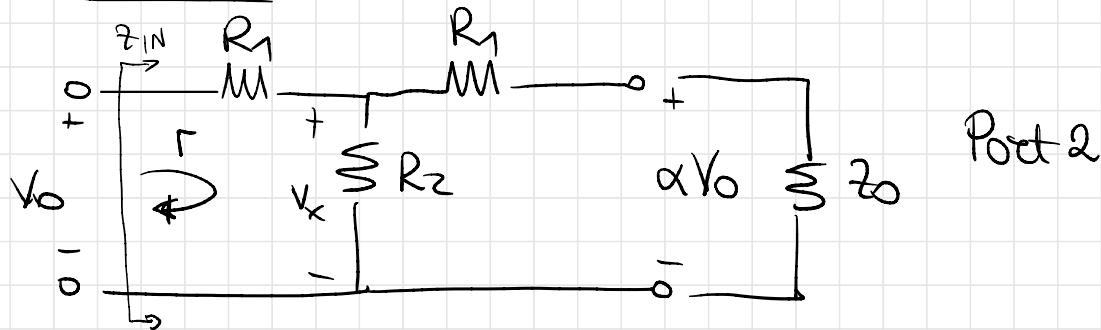

$$S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{V_2^+ = 0} = \Gamma = 0$$

$$\Gamma = \left. \frac{Z_{IN} - Z_0}{Z_{IN} + Z_0} \right|_{V_2^+ = 0} = \frac{\left[R_1 + R_2 / (R_1 + Z_0) \right] - Z_0}{\left[R_1 + R_2 / (R_1 + Z_0) \right] + Z_0} = 0$$

$$R_1 + \frac{R_2 (R_1 + Z_0)}{R_2 + R_1 + Z_0} - Z_0 = 0$$

$$R_1 R_2 + R_1^2 + \cancel{Z_0 R_1} + R_1 R_2 + \cancel{R_2 Z_0} - \cancel{R_2 Z_0} - \cancel{R_1 Z_0} - Z_0^2 = 0$$

$$R_1^2 + 2 R_1 R_2 - Z_0^2 = 0$$

$$R_2 = \frac{Z_0^2 - R_1^2}{2 R_1}$$

$$S_{12} = \left. \frac{V_2^-}{V_1^+} \right|_{V_2^+ = 0} = \alpha$$

Ports are matched so $V_2^- = V_2 = \alpha V_0$

$$V_2 = \frac{Z_0}{R_1 + Z_0} V_x$$

$$V_x = \frac{(R_1 + Z_0) // R_2}{[(R_1 + Z_0) // R_2] + R_1} V_1$$

$$S_{12} = \frac{V_2^-}{V_1^+} = \frac{V_2}{V_1} = \frac{Z_0}{R_1 + Z_0}$$
$$\frac{\frac{(R_1 + Z_0) R_2}{R_1 + Z_0 + R_2}}{\frac{(R_1 + Z_0) R_2}{R_1 + Z_0 + R_2} + R_1} = \alpha$$

$$S_{12} = \frac{Z_0 R_2}{(R_1 + Z_0) R_2 + R_1^2 + Z_0 R_1 + R_1 R_2} = \alpha$$

$$\frac{Z_0 R_2}{R_1 R_2 + Z_0 R_2 + R_1^2 + Z_0 R_1 + R_1 R_2} = \alpha$$

\equiv $=$ \equiv

Z_0^2

$$\frac{Z_0 R_2}{Z_0^2 + Z_0 R_2 + Z_0 R_1} = \alpha$$

$$\frac{R_2}{Z_0 + R_2 + R_1} = \alpha$$

$$R_2 = \alpha z_0 + \alpha R_2 + \alpha R_1$$

$$R_2 (1 - \alpha) = \alpha (z_0 + R_1)$$

since $R_2 = \frac{z_0^2 - R_1^2}{2R_1}$

$$\frac{(z_0 + R_1)(z_0 - R_1)}{2R_1} (1 - \alpha) = \alpha (z_0 + R_1)$$

$$R_1 = \frac{1 - \alpha}{1 + \alpha} z_0$$

If $z_0 = 50 \Omega$


$$\alpha_{dB} = 20 \log(\alpha_{lin}) \quad \alpha_{lin} = 10^{-\frac{\alpha_{dB}}{20}}$$

$$\alpha_{dB} = -3 dB \Rightarrow \alpha_{lin} = 0.708 \Rightarrow \begin{cases} R_1 = 8.65 \Omega \\ R_2 = 162 \Omega \end{cases}$$

$$\alpha_{dB} = -10 dB \Rightarrow \alpha_{lin} = 0.316 \Rightarrow \begin{cases} R_1 = 26 \Omega \\ R_2 = 35.1 \Omega \end{cases}$$

$$\alpha_{dB} = -20 dB \Rightarrow \alpha_{lin} = 0.1 \Rightarrow \begin{cases} R_1 = 40.9 \Omega \\ R_2 = 10.1 \Omega \end{cases}$$

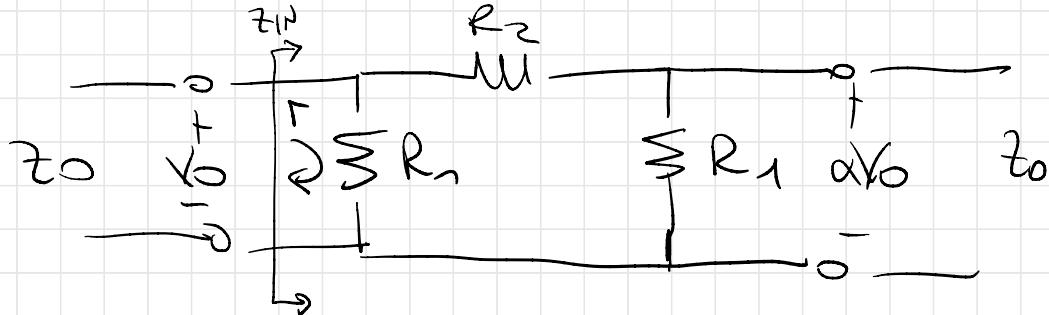For the π -network we repeat the same procedure



$$S_{11} = \frac{V_1^-}{V_1^+} \quad \left| \begin{array}{l} = \Gamma = 0 \\ V_2^+ = 0 \end{array} \right.$$

$$\Gamma = \frac{Z_{IN} - Z_0}{Z_{IN} + Z_0}$$

$$Z_{IN} = (R_1 // R_0 + R_2) // R_1$$

$$Z_{IN} = \frac{(R_1 Z_0 + R_1 R_2 + Z_0 R_2) R_1}{R_1 Z_0 + R_1 R_2 + Z_0 R_2 + R_1^2 + Z_0 R_1}$$

$$S_{11} = \frac{Z_{IN} - Z_0}{Z_{IN} + Z_0} = 0$$



$$R_2 = \frac{2R_1 Z_0}{R_1^2 - Z_0^2}$$

$$S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{V_2^+ = 0} = \frac{\alpha V_0}{V_0} = \alpha$$

$$V_2 = V_1 \cdot \frac{R_1 // Z_0}{R_1 // Z_0 + R_2} \rightarrow \frac{\frac{R_1 Z_0}{R_1 + Z_0}}{\frac{R_1 Z_0}{R_1 + Z_0} + R_2} V_1$$

$$\frac{V_2}{V_1} = \alpha \quad \Rightarrow \quad \frac{R_1 Z_0}{R_1 Z_0 + R_2 R_1 + Z_0 R_2} = \alpha$$

Replacing $R_2 = \frac{Z_0 R_1 \alpha^2}{R_1^2 - Z_0^2}$ we get

$$\cancel{R_1 Z_0} (1 - \alpha) = \alpha \frac{\cancel{Z_0 R_1} \alpha^2}{(R_1 + Z_0)(R_1 - Z_0)} (R_1 + Z_0)$$

$$(1 - \alpha)(R_1 - Z_0) = 2\alpha Z_0$$

$$R_1 = \frac{1 + \alpha}{1 - \alpha} Z_0$$

$$50 \text{ if } z_0 = 50 \Omega$$

$$\alpha_{dB} = -3 \text{ dB} \Rightarrow \alpha_{lin} = 0.708 \Rightarrow$$

$$\begin{cases} R_1 = 292.5 \Omega \\ R_2 = 14.6 \Omega \end{cases}$$

$$\alpha_{dB} = -10 \text{ dB} \Rightarrow \alpha_{lin} = 0.316 \Rightarrow$$

$$\begin{cases} R_1 = 96.2 \Omega \\ R_2 = 71.2 \Omega \end{cases}$$


$$\alpha_{dB} = -20 \text{ dB} \Rightarrow \alpha_{lin} = 0.1 \Rightarrow$$

$$\begin{cases} R_1 = 61.1 \Omega \\ R_2 = 247.5 \Omega \end{cases}$$

□ _____ 0
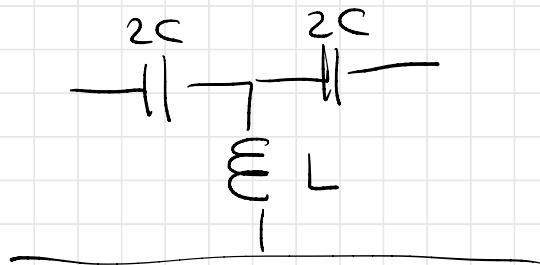
#4 $R_o = 75 \Omega$ $f_c = 50 \text{ MHz}$ $f_\infty = 68 \text{ MHz}$

First we calculate the parameters for constant-k section for high-pass filter



$$L = \frac{R_o}{2\omega_c} = \frac{R_o}{2 \cdot 2\pi f_c} = 119 \text{ nH}$$

$$C = \frac{1}{2R_o \omega_c} = \frac{1}{2 \cdot 75 \cdot 2\pi f_c} = 21.2 \text{ pF}$$

$$2C = 42.4 \text{ pF}$$

We add the m-derived section for sharp cut-off.



$$\frac{1}{\frac{1}{L/m}} = \frac{4m}{1-m^2} C$$


$$m = \sqrt{1 - \left(\frac{f_{\text{as}}}{f_c}\right)^2} = 0.28$$

$$\frac{2C}{m} = 151 \text{ pF}$$

$$\frac{L}{m} = 425 \text{ nH}$$

$$\frac{4mC}{1-m^2} = 25.8 \text{ pF}$$

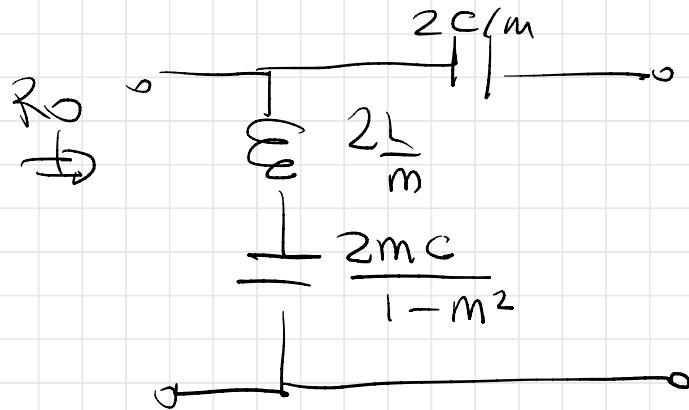Finally we add the matching section ($m=0.6$)



$$\frac{2C}{m} = 70.7 \text{ pF}$$

$$\frac{2L}{m} = 397 \text{ nH}$$

$$\frac{2mc}{1-m^2} = 39.8 \text{ pF}$$

The filter is then:

