

Semester S1 –Basics of active and non linear electronics

RF Power amplifiers (JM Nebus)

TUTORIAL N° 3

1.1.1.1 Operating classes of a Fiel Effet Transistor

Let us consider the schematic of Figure 1. The drain bias voltage V_{DD} is equal to 25V

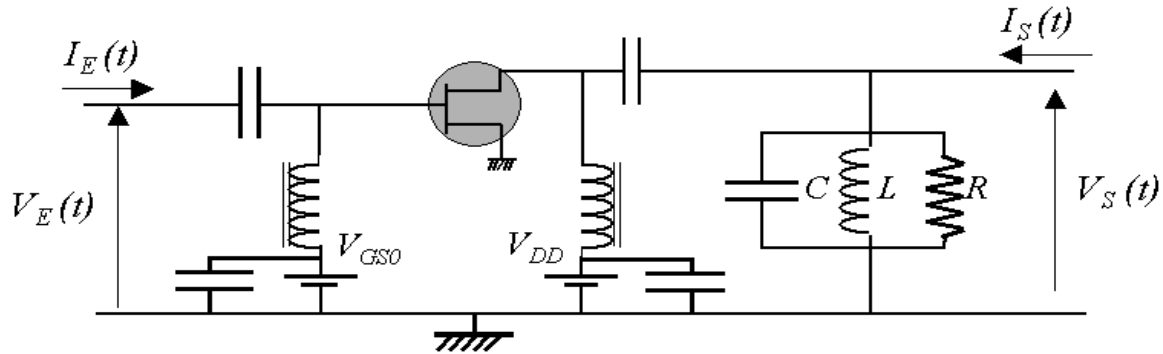


Figure 1

The static I/V characteristics of the transistor are plotted in figure 2 . The pinch off voltage $V_p = -4V$ and the maximum drain current $I_{dss} = 1A$.

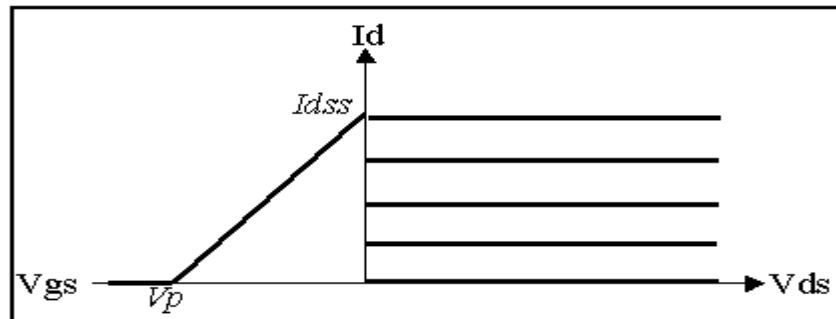


Figure 2

The input gate source voltage $V_{gs}(t)$ will be set to have a maximum value of 0V at $t=0$ in order to get the maximum acceptable swing of the gate source voltage and consequently the maximum swing of the output drain current $I_d(t)$

$$V_{gs}(t) = V_{gs0} + V_E(t) = V_{gs0} + V_{gs1} \cdot \cos(\omega t)$$

$$V_{gs}(0) = 0$$

1) We will study three different conditions corresponding to three different operating classes

Case N° 1 Class AB ($\varphi = 120^\circ = 2\pi/3$)

Case N° 2- Class B ($\varphi = 90^\circ = \pi/2$)

Case N° 3 Class C ($\varphi = 60^\circ = \pi/3$)

Answer to the following questions for the three cases :

- 1) Calculate the value of the corresponding bias voltage V_{GS0} and the magnitude of the RF voltage V_{GS1}
- 2) Plot the time domain waveform of $V_{GS}(t)$ below figure 2 and $I_d(t)$ on the right side of figure 2
- 3) Calculate the values of the drain current components I_{d0} at DC and I_{d1} at the fundamental frequency using the following equations

$$I_{d0} = \frac{I_p \cdot (\sin(\varphi) - \varphi \cos(\varphi))}{\pi(1 - \cos(\varphi))}$$
$$I_{d1} = \frac{I_p \cdot (\varphi - \sin(\varphi) \cdot \cos(\varphi))}{\pi(1 - \cos(\varphi))}$$

- 4) We want to have the maximum drain voltage swing in order to have the maximum output RF power. What is the corresponding value of V_{DS1}
- 5) What is the value of the load resistance R that is required to get the maximum output RF power .
- 6) Calculate the values of the RF output power P_{out} , the DC consumption P_{DC} and the drain efficiency $\eta_d = P_{out} / P_{DC}$

- 7) Plot the load lines on the I/V characteristic graph
- 8) The fundamental operating frequency is $F_0 = 2 \text{ GHz}$, and the value of the capacitance C of the parallel resonating circuit is 0.5 pF . Calculate the value of the inductance L
- 9) We consider now that the input resistance and capacitance of the transistor are respectively $R_g = 5 \Omega$ and $C_{gs} = 6 \text{ pF}$.
- Calculate the power added efficiency PAE and the power gain