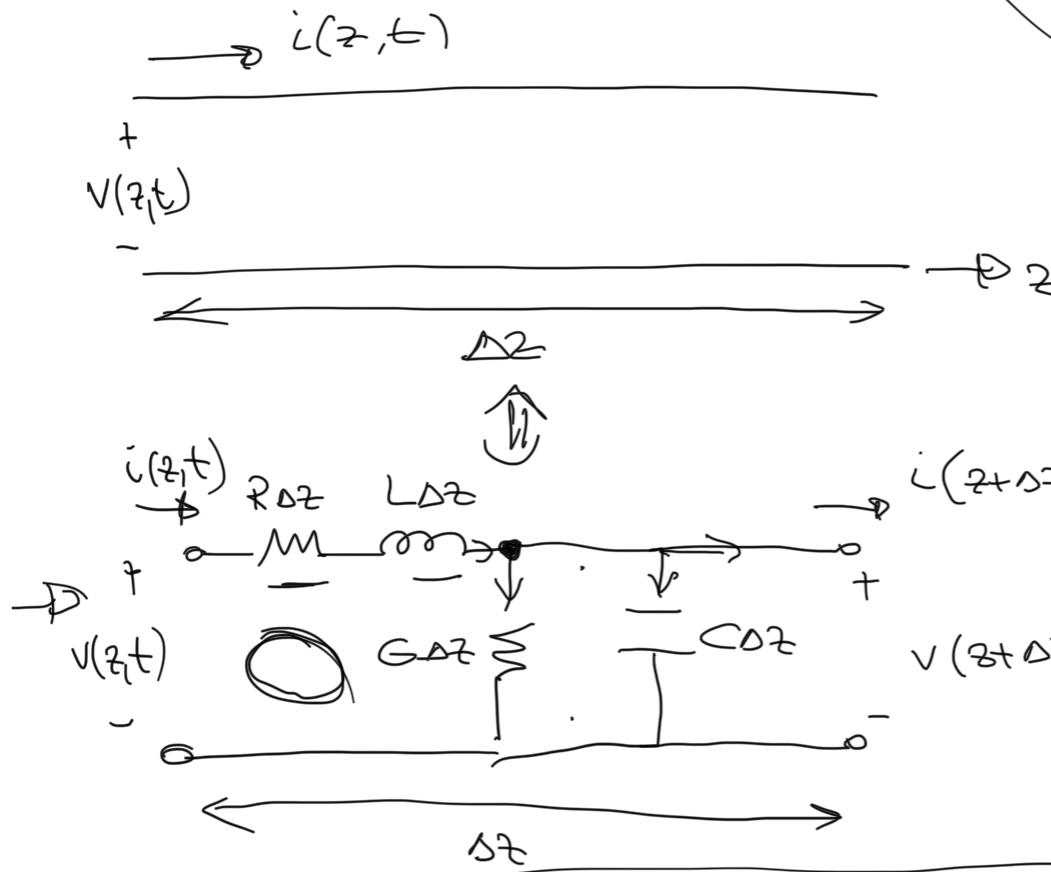


TRANSMISSION LINE THEORY

CIRCUIT MODEL

FIELD ANALYSIS

SIZES FRACTION OF WAVELENGTH



$$R = \frac{\Omega}{m}$$

$$L = \frac{H}{m}$$

$$G = \frac{S}{m}$$

$$C = \frac{F}{m}$$

$$\left\{ \begin{array}{l} \frac{\partial v(z, t)}{\partial z} - R \frac{\partial i(z, t)}{\partial t} - L \frac{\partial i(z, t)}{\partial z} - \frac{\partial v(z + \Delta z, t)}{\partial z} = 0 \\ G \frac{\partial v(z + \Delta z, t)}{\partial z} - C \frac{\partial v(z + \Delta z, t)}{\partial t} - \frac{\partial i(z + \Delta z, t)}{\partial z} = 0 \end{array} \right.$$

$$\left\{ \begin{array}{l} \frac{\partial v(z, t)}{\partial z} = -R i(z, t) - L \frac{\partial i(z, t)}{\partial t} \\ \frac{\partial i(z, t)}{\partial z} = -G v(z, t) - C \frac{\partial v(z, t)}{\partial t} \end{array} \right. \quad \text{TELEGRAPHER EQUATION}$$

$$\frac{d}{dt} = j\omega$$

↓

$$\begin{cases} \frac{dV(z)}{dz} = -(R + j\omega L) I(z) \\ \frac{dI(z)}{dz} = -(G + j\omega C) V(z) \end{cases}$$

PHASOR
FORM

WAVE PROPAGATION :

APPY DERIVATIVES OVER Z

$$\frac{d^2 V(z)}{dz^2} = -(R + j\omega L) \left(\frac{dI(z)}{dz} \right) \Rightarrow$$

$$\frac{d^2 V(z)}{dz^2} = (R + j\omega L)(G + j\omega C) V(z)$$

$$\frac{d^2 I(z)}{dz^2} = \underbrace{(R + j\omega L)(G + j\omega C) I(z)}$$

PROPAGATION CONSTANT

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\frac{d^2 V(z)}{dz^2} - \gamma^2 V(z) = 0$$

$$\frac{d^2 I(z)}{dz^2} - \gamma^2 I(z) = 0$$

$$\begin{cases} V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \\ I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z} \end{cases}$$

1*

L \leftarrow

$$\frac{dV(z)}{dz} = -(R+j\omega L) I(z)$$

$$\frac{d}{dz} \left(V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \right) = -(R+j\omega L) I(z)$$

$$- \gamma V_0^+ e^{-\gamma z} + \gamma V_0^- e^{\gamma z} = -(R+j\omega L) I(z)$$

$$I(z) = \frac{\gamma}{R+j\omega L} (V_0^+ e^{-\gamma z} - V_0^- e^{\gamma z}) \quad (1)$$

$$Z_0 = \frac{V}{I} = \frac{V_0^+}{I_0^+} = - \frac{V_0^-}{I_0^-} = \frac{R+j\omega L}{\gamma} = \sqrt{\frac{R+j\omega L}{G+j\omega C}}$$

$$\Rightarrow I(z) = \frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{\gamma z}$$

$$\gamma = \alpha + j\beta \Rightarrow \text{WAVELENGTH : } \lambda = \frac{2\pi}{\beta}$$

$$\text{PHASE VELOCITY : } V_p = \frac{\omega}{\beta}$$

LOSSLESS LINE

$$G=R=0$$

$$\gamma = \sqrt{(R+j\omega L)(G+j\omega C)} = j\omega \sqrt{LC}$$

$$\alpha = 0 \quad \beta = \omega \sqrt{LC}$$


$$\sqrt{R+j\omega L} = \sqrt{\frac{L}{C}} \quad \text{REAL NUMBER}$$

$$Z_0 = \sqrt{\frac{1}{\mu + j\omega C}}$$

WAVELENGTH $\Rightarrow \lambda = \frac{2\pi}{\beta} = \frac{2\pi}{\omega\sqrt{\mu C}}$

PHASE VELOCITY $\Rightarrow V_p = \frac{\omega}{\beta} = \frac{\omega}{\omega\sqrt{\mu C}} = \sqrt{\frac{1}{\mu C}}$

FIELD ANALYSIS

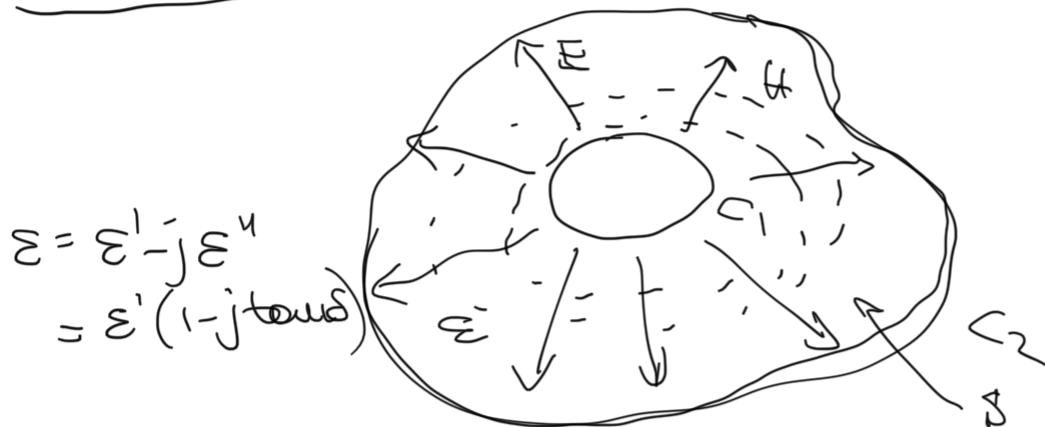

STORED MAGNETIC ENERGY

$$W_m = \frac{\mu}{4} \int_S \mathbf{H} \cdot \mathbf{H}^* dS = W_m = \frac{|I_o|^2}{4}$$

$$L = \frac{\mu}{|I_o|^2} \int_S \mathbf{H} \cdot \mathbf{H}^* dS \quad [\frac{H}{m}]$$

STORED ELECTRIC ENERGY

$$W_e = \frac{\epsilon}{4} \int_S \mathbf{E} \cdot \mathbf{E}^* dS$$

$$W_e = \frac{C|V_o|^2}{4}$$

$$C = \frac{\epsilon}{|V_0|^2} \int_S \vec{E} \cdot \vec{E}^* dS \quad \left[\frac{F}{m} \right]$$

POWER LOSS

$$P_C = \frac{R_s}{2} \int_{C_1+C_2} H \cdot H^* dl$$

$$P_C = R \frac{|V_0|^2}{2}$$

$$R = \frac{R_s}{\frac{|V_0|^2}{2}} \int_{C_1+C_2} H \cdot H^* dl \quad \left[\frac{\Omega}{m} \right]$$

$$R_s = \frac{1}{6 \sigma s} \quad \text{SURFACE RESISTANCE}$$

POWER DISSIPATED IN DIELECTRIC FILLING THE LINE

$$P_d = \frac{\omega \epsilon'}{2} \int_S E \cdot E^* dS$$

$$P_d = G \frac{|V_0|^2}{2}$$

||

$$G = \frac{\omega \epsilon'}{|V_0|^2} \int_S \vec{E} \cdot \vec{E}^* dS \quad \left[\frac{S}{m} \right]$$


COAXIAL LINE

$$\parallel E_z = H_z = 0$$

$$\parallel C_\phi = 0$$

$$\left\{ \begin{array}{l} \nabla_x E = -j\omega \mu H \\ \nabla_x H = j\omega \epsilon E \end{array} \right.$$

$$\epsilon = \epsilon' - j\epsilon''$$

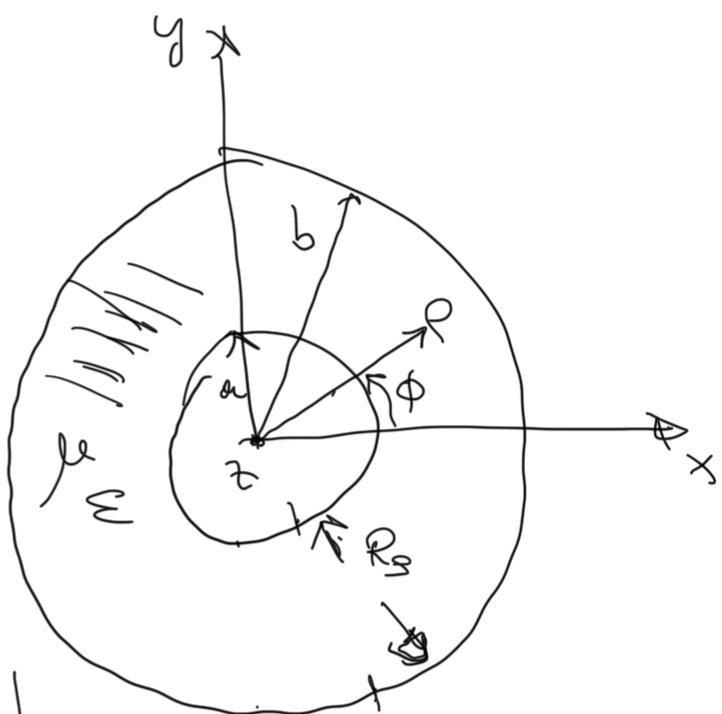

$$\begin{matrix} \nabla_x \bar{E} = & \hat{\rho} & \hat{\phi} & \hat{z} \\ \nabla_x H = & \frac{\partial}{\partial \rho} E_\rho & \frac{\partial}{\partial \phi} E_\phi & \frac{\partial}{\partial z} E_z \end{matrix}$$

$$- \hat{\rho} \frac{\partial E_\phi}{\partial z} + \hat{\phi} \frac{\partial E_\rho}{\partial z} + \hat{z} \frac{\partial}{\partial \rho} (E_\phi) = -j\omega \mu \left(\hat{\rho} H_\rho + \hat{\phi} H_\phi \right)$$

$$- \hat{\rho} \frac{\partial H_\phi}{\partial z} + \hat{\phi} \frac{\partial H_\rho}{\partial z} + \hat{z} \frac{\partial}{\partial \rho} (E_\phi) = j\omega \epsilon \left(\hat{\rho} E_\rho + \hat{\phi} E_\phi \right)$$

$$\rho = a, b \Rightarrow \cancel{E_\phi} = 0$$

$$H_\rho = 0$$

$$\left\{ \begin{array}{l} \frac{\partial E_p}{\partial z} = -j\omega \mu H_\phi \\ \frac{\partial H_\phi}{\partial z} = -j\omega \epsilon E_p \end{array} \right.$$

$$\begin{aligned} E_p &= \frac{n(z)}{e} \\ H_\phi &= g(z) \end{aligned}$$

$$\Rightarrow \left\{ \begin{array}{l} \frac{\partial h(z)}{\partial z} = -j\omega \mu g(z) \\ \frac{\partial g(z)}{\partial z} = -j\omega \epsilon h(z) \end{array} \right.$$

VOLTAGE

$$V(z) = \int_{p=a}^b E_p(p, z) dp = h(z) \int_{p=a}^b \frac{dp}{p} = \underline{h(z) \ln \frac{b}{a}}$$

CURRENT

$$I(z) = \int_{\phi=0}^{2\pi} H_\phi(a, z) a d\phi = \int_{\phi=0}^{2\pi} \underline{g(z)} \cdot \underline{a} d\phi = \underline{g(z) 2\pi a}$$

Teleg. eq. for coaxial line

$$\left\{ \begin{array}{l} \frac{\partial V(z)}{\partial z} = -j \frac{\omega \mu \ln \frac{b}{a}}{2\pi} I(z) \\ \frac{\partial I(z)}{\partial z} = -j\omega (\underbrace{\epsilon' - j\epsilon''}_{\epsilon}) \frac{2\pi V(z)}{\ln b} \end{array} \right.$$

ℓ ε a
 $\gamma^2 = \omega^2 \mu \varepsilon$

Feld Analys

$$\left\{ \begin{array}{l} E = \frac{\nu \hat{p}}{\rho \ln \frac{b}{a}} e^{-\gamma z} \\ H = \frac{I_0 \hat{\phi}}{2\pi \rho} e^{-\gamma z} \end{array} \right.$$

$$\textcircled{1} L = \frac{\mu}{|I_0|^2} \int_S H \cdot H^* = \frac{\mu}{(2\pi)^2} \int_{\phi=0}^{2\pi} \int_{\rho=a}^b \frac{1}{\hat{p}^2} \hat{p} d\rho d\phi =$$

$$= \frac{\mu}{2\pi} \ln \frac{b}{a} \left[\frac{1}{m} \right]$$

$$\textcircled{2} C = \frac{\varepsilon}{|\nu \ell|^2} \int_S E \cdot E^* dS = \frac{\varepsilon'}{\ln \left(\frac{b}{a} \right)^2} \int_{\phi=0}^{2\pi} \int_{\rho=a}^b \frac{1}{\hat{p}^2} \hat{p} d\rho d\phi =$$

$$= \frac{2\pi \varepsilon'}{\ln \frac{b}{a}} \left[\frac{E}{m} \right]$$

$$\textcircled{3} R = \frac{R_S}{|I_0|^2} \int_{C_1 + C_2} H \cdot H^* d\ell = \frac{R_S}{(2\pi)^2} \left\{ \int_{\phi=0}^{2\pi} \frac{1}{\hat{p}^2} \hat{p} d\phi + \int_{\phi=0}^{2\pi} \frac{\frac{1}{b^2} b d\phi}{C_2} \right\}$$

$$= \frac{R_s}{2\pi} \left(\frac{1}{a} + \frac{1}{b} \right) \left[\frac{\Omega}{m} \right]$$

$$\textcircled{4} \quad G = \frac{\omega \epsilon''}{4\pi l^2} \int_S E \cdot E^* dS = \frac{\omega \epsilon''}{4\pi \left(\frac{b}{a}\right)^2} \int_{\phi=0}^{2\pi} \int_{r=a}^b \frac{1}{r^2} r dr d\phi =$$

$$= \frac{2\pi \omega \epsilon''}{4\pi \frac{b}{a}} \left[\frac{\epsilon}{m} \right]$$

$$\left\{ \begin{array}{l} \frac{\partial E_p}{\partial z} = -j\omega \mu H \phi \\ \frac{\partial H \phi}{\partial z} = -j\omega \epsilon E_p \end{array} \right.$$

$$\frac{\partial^2 E_p}{\partial z^2} = -\omega^2 \mu \epsilon E_p$$

$\hookrightarrow \gamma^2 = -\tilde{\omega} \mu \epsilon$

\bullet

$$\gamma = \alpha + j\beta$$

LOSSLESS MEDIA

$$\beta = \omega \sqrt{\mu \epsilon} = \omega \sqrt{LC}$$

TEM TRANSMISSION
LINES

WAVE IMPEDANCE

$$Z = E_p / H \phi = \omega \mu \sqrt{\mu/\epsilon} = \gamma$$

MEDIUM
IMPEDANCE

$$Z_w = \frac{1}{H\phi} - \beta$$

LINE IMPEDANCE

$$Z_0 = \frac{V_0}{I_0} = \frac{E_p \ln \frac{b}{a}}{2\pi H\phi} = \frac{\eta \ln \frac{b}{a}}{2\pi} = \sqrt{\frac{\mu}{\epsilon}} \frac{\ln \frac{b}{a}}{2\pi}$$

geometry dependent


POWER FLOW

$$P = \frac{1}{2} \int_S E \times H^* dS =$$


$$= \frac{1}{2} \int_{\phi=0}^{2\pi} \int_{\rho=a}^b \frac{V_0 I_0^*}{2\pi \rho^2 \ln \frac{b}{a}} \rho d\rho d\phi =$$

$$= \frac{1}{2} V_0 I_0^* \frac{1}{2\pi \ln \frac{b}{a}} \cdot 2\pi \cdot \ln \frac{b}{a} = \frac{1}{2} V_0 I_0^*$$

TERMINATED LOSSLESS TRANSMISSION LINE

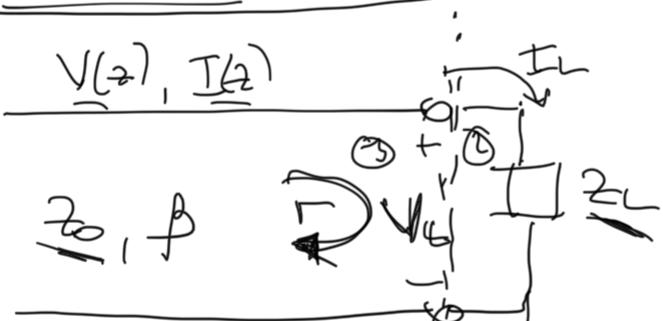
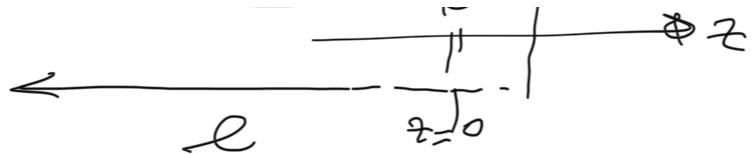
$$\left\{ \begin{array}{l} E_p = \frac{V_0}{\rho \ln \frac{b}{a}} \hat{\rho} e^{-j\phi} \\ H\phi = \frac{I_0}{2\pi \rho} \hat{\phi} e^{-j\phi} \end{array} \right.$$



$$Z_L \neq Z_0$$

$$\left\{ \begin{array}{l} V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z} \\ I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{j\beta z} \end{array} \right.$$

At the load ($z=0$) : $\frac{V(0)}{I(0)} = Z_L$

$$Z_L = \frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} Z_0 \Rightarrow$$

$$V_0^- = \frac{Z_L - Z_0}{Z_L + Z_0} \underline{\underline{V_0^+}}$$

Voltage reflection coefficient

$$\Gamma = \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Rightarrow \left\{ \begin{array}{l} V(z) = V_0^+ [e^{-j\beta z} + \Gamma e^{j\beta z}] \\ I(z) = \frac{V_0^+}{Z_0} [e^{-j\beta z} - \Gamma e^{j\beta z}] \end{array} \right.$$

$$P_{av} = \frac{1}{2} \operatorname{Re} [V(z) I(z)^*] =$$

$$= \frac{1}{2} \frac{|V_0^+|^2}{Z_0} \operatorname{Re} \left\{ 1 - \Gamma e^{-2j\beta z} + \Gamma e^{2j\beta z} - |\Gamma|^2 \right\}$$

Purely imaginary

$$P_{av} = \frac{1}{2} \frac{|V_0^+|^2}{Z_0} [1 - |\Gamma|^2]$$

P_{av} does not depend on z!

Maximum power transfer occurs $\Gamma = 0$

$$\text{RETURN LOSS (RL)} = -20 \log |\Gamma| \text{ dB}$$

$$\underline{\Gamma = 0} \Rightarrow R_L = \infty$$

$$\underline{\Gamma = 1} \Rightarrow RL = 0$$

If $\Gamma = 0$ $\Rightarrow |V(z)| = V_0^+ \Rightarrow$ CONSTANT ALONG THE LINE

If $\Gamma \neq 0 \Rightarrow$ STANDING WAVE

$$|V(z)| = |V_0^+| |1 + \Gamma e^{2j\beta z}| = \ell = -z$$

$$= |V_0^+| |1 + \Gamma e^{-2j\beta z}| =$$

$$= |V_0^+| |1 + \Gamma| e^{j(\theta - 2\beta z)} =$$

$$\Gamma = |\Gamma| e^{j\phi} =$$

$$\left\{ \begin{array}{l} V_{\max} = |V_0^+| (1 + |\Gamma|) \\ V_{\min} = |V_0^+| (1 - |\Gamma|) \end{array} \right.$$

Phase of
the reflection
coefficient

$$\text{STANDING WAVE RATIO} = \frac{V_{\max}}{V_{\min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

$$\frac{1 < \text{SWR} < \infty}{\text{matched} \quad \text{mismatched}}$$

DISTANCE BETWEEN TWO VOLTAGE MAXIMA

$$2\beta l = 2\pi \Rightarrow l = \frac{\pi}{2\beta} = \frac{\pi \lambda}{2\pi} = \frac{\lambda}{2}$$

DISTANCE BETWEEN MAX and MIN.

$$2\beta l = \pi \Rightarrow l = \frac{\lambda}{4}$$

$$\Gamma(-l) = \frac{V_0^- e^{-j\beta l}}{V_0^+ e^{j\beta l}} = \frac{\Gamma(0) e^{-2j\beta l}}{\Gamma(0) = \frac{Z_L - Z_0}{Z_L + Z_0}}$$

$$Z_{IN} = \frac{V(-l)}{\Gamma(-l)} = \frac{V_0^+ [e^{j\beta l} + \Gamma e^{-j\beta l}]}{V_0^+ [e^{j\beta l} - \Gamma e^{-j\beta l}]} Z_0 = Z_0 \frac{1 + \Gamma e^{-2j\beta l}}{1 - \Gamma e^{-2j\beta l}}$$

$$\Gamma = \frac{z_L - z_0}{z_L + z_0}$$

$$1 - \Gamma e^{-j\beta z}$$

$$z_{in} = z_0 \frac{z_0 + j z_0 \tan \beta L}{z_0 + j z_L \tan \beta L}$$

TRANSMISSION
LINE
IMPEDANCE


SPECIAL CASES

①

$$|z_L = 0|$$

SHORT CIRCUIT TERMINATION

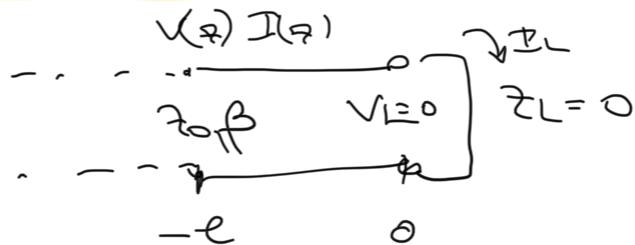
$$\Gamma = \frac{z_L - z_0}{z_L + z_0} = -1$$



$$SWR = \frac{1+|\Gamma|}{1-|\Gamma|} = \infty$$


$$V(z) = V_0^+ [e^{-j\beta z} - e^{j\beta z}] = -2jV_0^+ \sin \beta z$$
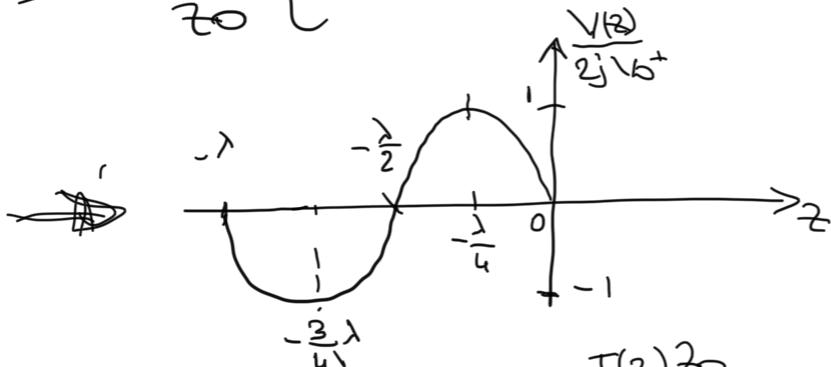
$$I(z) = \frac{V_0^+}{z_0} [e^{-j\beta z} + e^{j\beta z}] = 2 \frac{V_0^+}{z_0} \cos \beta z$$




$$\propto \frac{I(z) z_0}{2V_0^+}$$



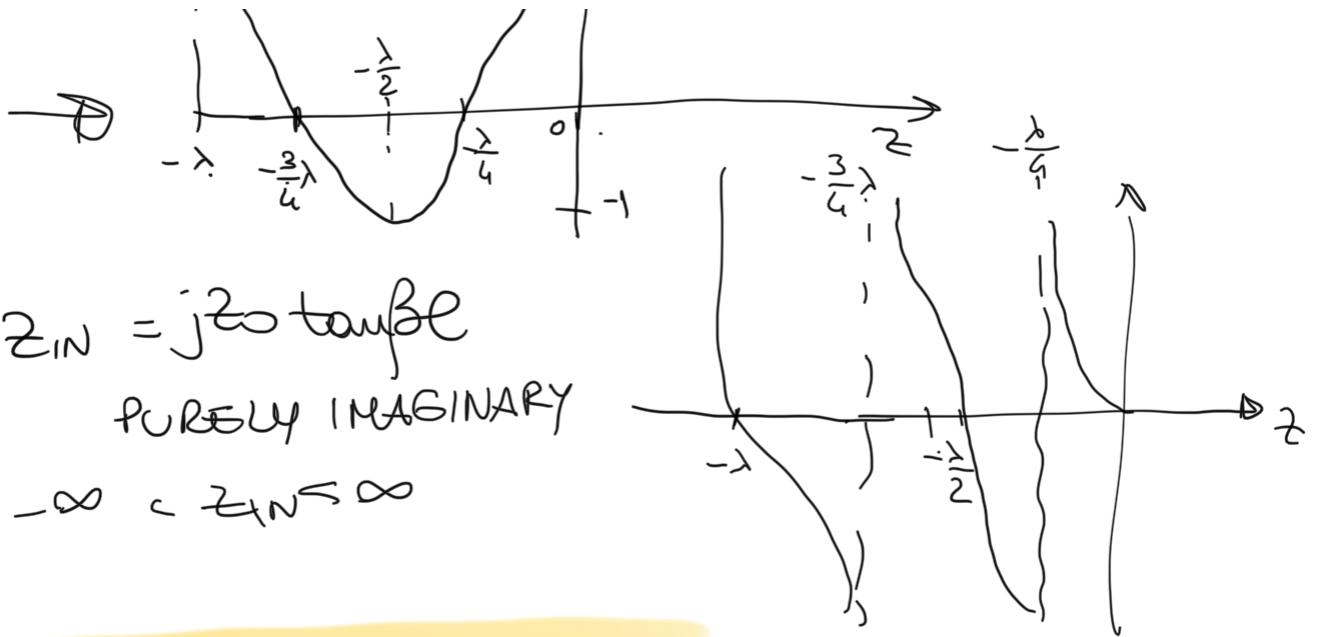

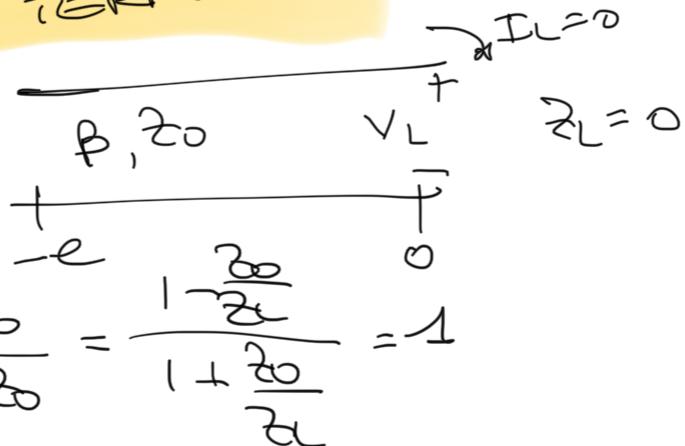② $Z_L = \infty$ OPEN CIRCUIT TERMINATION



$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{1 - \frac{Z_0}{Z_L}}{1 + \frac{Z_0}{Z_L}} = 1$$

$$SWR = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \infty$$

$$V(z) = 2V_0^+ \cos \beta z$$

$$I(z) = -\frac{2jV_0^+}{Z_0} \sin \beta z$$

$$Z_{1N} = -jZ_0 \cot \beta L \quad \text{purely imaginary}$$

③ $L = \lambda$

1)

- 2

$$\beta L = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{2} = \pi$$

$\tan \beta L = 0$

$$Z_{IN} = Z_L$$

④

$$l = \frac{\lambda}{4} + m \frac{\lambda}{2}$$


$$\beta L = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} = \frac{\pi}{2} \quad \tan \beta L = \infty$$

$$Z_{IN} = \frac{Z_0^2}{Z_L}$$

QUARTER
WAVE TRANSFORMER

⑤

JUNCTION BETWEEN TWO LINES

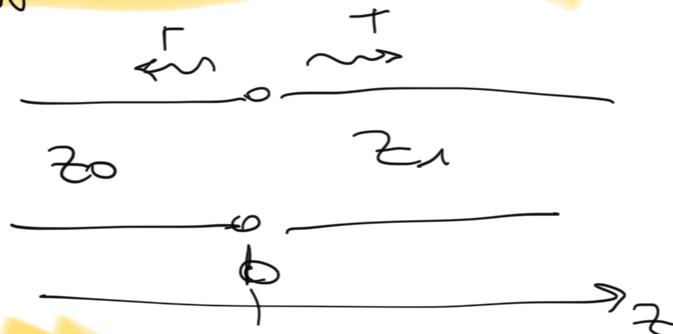

$$T = \frac{Z_1 - Z_0}{Z_1 + Z_0}$$

$$T = 1 + \rho = 1 + \frac{Z_1 - Z_0}{Z_1 + Z_0} = \frac{2Z_1}{Z_1 + Z_0}$$

INSERTION LOSS

$$IL = -20 \log |T| \quad \text{dB}$$