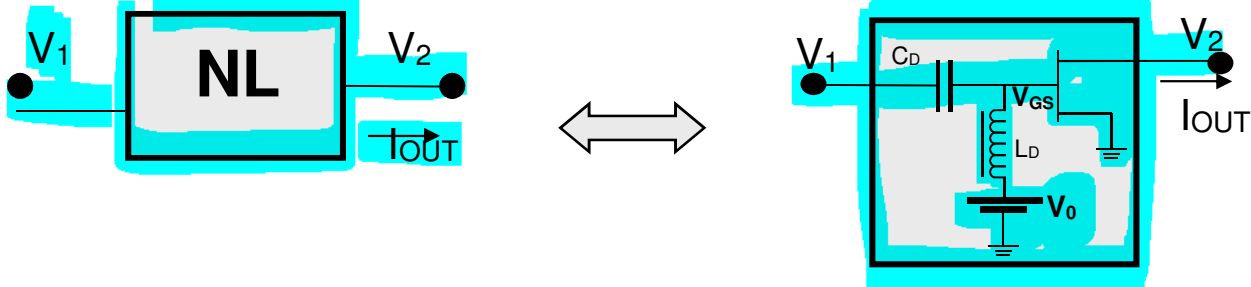


Tutorial (SEM cold-FET Mixer)

The following cold-FET mixer (biased @ $V_{DS0}=0$ V) is used to design a SEM up-converter where the LO signal V_1 is applied to the gate, which is biased @ ($V_{GS0}=V_0$) while the IF input signal is applied to the drain using a low-pass filter and the output signal is extracted at the drain port using a high-pass filter.



The nonlinear operation of the cold-FET (NL) is expressed by the 2 following equations that give the output current I_{OUT} as a function of input and output control voltages V_1 and V_2 :

$$V_{GS} = V_0 + V_1 \quad (\text{eq1})$$

where V_0 is a constant (gate bias voltage)

$$I_{OUT} = p V_2 - q V_2 V_{GS}^2 + r V_1 \quad (\text{eq2})$$

where p, q and r are constants


The SEM cold-FET mixer is shown below and the main frequencies are :

$$f_{LO} = 9 \text{ GHz}, f_{IF} = 0.5 \text{ GHz et } f_{RF} = f_{LO} + f_{IF} = 9.5 \text{ GHz} \quad (\omega_{RF} = \omega_{LO} + \omega_{IF}).$$


The two control voltages V_1 and V_2 of the FET mixer are :

$$\text{LO voltage at gate port : } V_1 = V_{LO} \cos(\omega_{LO} t) \quad (\text{eq3})$$
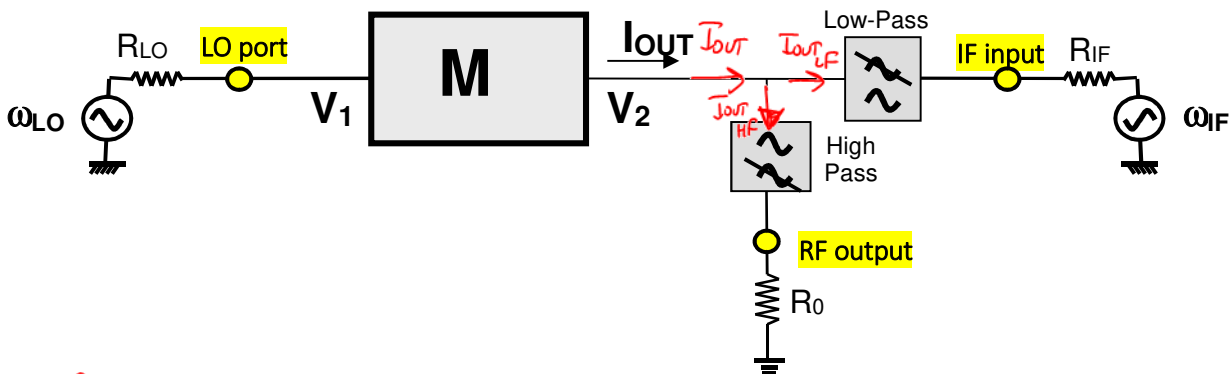
$$\text{IF voltage at drain port : } V_2 = V_{IF} \cos(\omega_{IF} t) \quad (\text{eq4})$$



- Using equations 1 to 4, express the output current I_{OUT} as a function of signal magnitudes (V_{LO}, V_{IF}), nonlinearity constants (p, q, r), gate bias V_0 and the mixing frequencies. The following notations can be used for mixing frequencies: $\omega_{IM} = (\omega_{LO} - \omega_{IF})$; $\omega_1 = (2\omega_{LO} - \omega_{IF})$; $\omega_2 = (2\omega_{LO} + \omega_{IF})$
- The high-pass filter is designed to reject frequencies lower than 5GHz while the low-pass frequency is designed to cut frequencies greater than 5GHz. Therefore, what are the mixing frequencies at the RF output port?
- Determine the expression of the voltage conversion gain G_{CV} .
- If the LO port is assumed to be matched to R_{LO} ,
 - express the LO power applied at the LO port
 - express the LO power at the RF output port
 - express in dB the LO-to-RF isolation
 - what is the LO-to-IF isolation ?
 - express the equivalent impedance Z_{IN} seen by the IF generator @ ω_{IF} at the IF input port

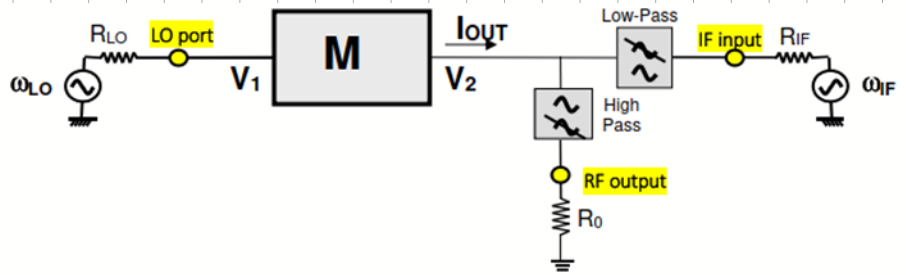

- 1) Using equations 1 to 4, express the output current I_{OUT} as a function of signal magnitudes (V_{LO} , V_{IF}), nonlinearity constants (p , q , r), gate bias V_0 and the mixing frequencies. The following notations can be used for mixing frequencies: $\omega_{IM} = (\omega_{LO} - \omega_{IF})$; $\omega_1 = (2\omega_{LO} - \omega_{IF})$; $\omega_2 = (2\omega_{LO} + \omega_{IF})$

$$\cos^2(x) = \frac{1}{2} + \frac{1}{2} \cos(2x)$$

$$V_{GS} = V_0 + V_1 \quad (eq1)$$

$$I_{OUT} = p V_2 - q V_2 V_{GS}^2 + r V_1 \quad (eq2)$$

$$V_2 \times V_{GS}^2 = V_2 (V_0 + V_1)^2 = V_2 (V_0^2 + V_1^2 + 2V_0 V_1)$$

$$= V_{IF} \cos(\omega_{IF} t) \left[\underbrace{V_0^2}_{\text{X}} + \underbrace{\frac{1}{2} V_{LO}^2}_{\text{X}} + \underbrace{\frac{1}{2} V_{LO}^2 \cos(2\omega_{LO} t)}_{\text{X}} + \underbrace{2V_0 V_{LO} \cos(\omega_{LO} t)}_{\text{X}} \right]$$

$$= \left(V_0^2 + \frac{V_{LO}^2}{2} \right) V_{IF} \cos(\omega_{IF} t) + \underbrace{V_0 V_{LO} V_{IF} [\cos(\omega_{RF} t) + \cos(\omega_{IM} t)]}_{\text{X}} + \underbrace{\frac{1}{4} V_{LO}^2 V_{IF} [\cos(\omega_1 t) + \cos(\omega_2 t)]}_{\text{X}}$$

$$I_{OUT} = \underbrace{\left[p - q \left(V_0^2 + \frac{V_{LO}^2}{2} \right) \right] V_{IF} \cos(\omega_{IF} t)}_{I_{OUT, LF}} - \underbrace{q V_0 V_{LO} V_{IF} [\cos(\omega_{RF} t) + \cos(\omega_{IM} t)] - \frac{q}{4} V_{LO}^2 V_{IF} [\cos(\omega_1 t) + \cos(\omega_2 t)] + r V_{LO} \cos(\omega_{LO} t)}_{I_{OUT, HF}}$$

