

Problem 1

$$[S] = \frac{1}{2} \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix}$$

A 3 port network cannot be reciprocal, lossless and be matched at the same time.

$[S]$ is symmetrical because $S = S^t$

$[S]$ is matched because the reflexion coefficients are zero

$$S_{ii} = 0 \rightarrow S_{11} = S_{22} = S_{33} = 0$$

So it has to be lossy

To be lossless: $[S]^t \cdot [S^*] = [U]$

$$\frac{1}{2} \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix} \cdot \frac{1}{2} \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix} = \frac{1}{4} \begin{bmatrix} 2 & 1 & 1 \\ 1 & 2 & 1 \\ 1 & 1 & 2 \end{bmatrix} \neq \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

a) Yes

b) No

c) Yes

d) To be isolated the two outputs (2 and):

The transmission coefficients S_{23} and S_{32} have to be zero and we see that:

$$S_{23} = S_{32} = 1$$

So it is not isolated.

e) We can calculate $[Z]$ matrix:

$$[U] + [S] = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} + \frac{1}{2} \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix} = \begin{bmatrix} 1 & 1/2 & 1/2 \\ 1/2 & 1 & 1/2 \\ 1/2 & 1/2 & 1 \end{bmatrix}$$

$$[U] - [S] = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} - \frac{1}{2} \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix} = \begin{bmatrix} 1 & -1/2 & -1/2 \\ -1/2 & 1 & -1/2 \\ -1/2 & -1/2 & 1 \end{bmatrix}$$

$$([U] - [S])^{-1} = \frac{2}{9} \begin{pmatrix} 2 & -1 & -1 \\ -1 & 2 & -1 \\ -1 & -1 & 2 \end{pmatrix}$$


using wolfram alpha

and $([U] - [S])^{-1}$ is pseudoinverse

since $([U] - [S])$ is singular

$$[Z] = (U + S)(U - S)^{-1} = \frac{1}{9} \begin{pmatrix} 2 & -1 & -1 \\ -1 & 2 & -1 \\ -1 & -1 & 2 \end{pmatrix} \rightarrow [V] = [Z][I]$$

(2)

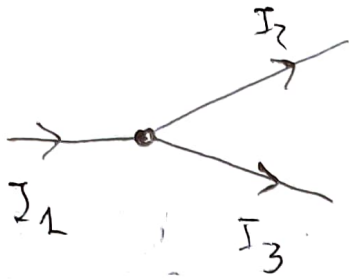

$$I_1 = I_2 + I_3$$

$$I_2 = I_3$$

$$I_1 = 2I_2$$

$$I_3 = I_2$$

$$V_1 = \frac{1}{9} (2I_1 - I_2 - I_3) = \frac{2}{9} I_2$$

$$V_2 = \frac{1}{9} (-I_1 + 2I_2 - I_3) = -\frac{1}{9} I_2$$

$$V_3 = \frac{1}{9} (-2I_2 - I_2 + 2I_2) = -\frac{1}{9} I_2$$


$$V_2 = V_3 = -\frac{1}{9} I_2$$

Disclaimer: As I_2 is defined like

$$V_1^+ = 10 \rightarrow I_2 = \frac{9}{2} V_1^+$$

$$V_2 = V_3 = -\frac{1}{9} (-1) I_2 = \frac{1}{9} \cdot \frac{9}{2} V_1^+ = \frac{10}{2}$$

$$\boxed{V_2 = V_3 = 5V}$$

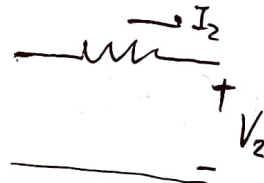

is in the opposite direction, so we have to add a minus sign

f)

$$P_1 = \frac{1}{2} |a_1|^2 (1 - |\Gamma_1|^2)$$

$$a_1 = \frac{V_1^+}{\sqrt{Z_0}}, \quad \Gamma_1 = \frac{b_1}{a_1} = S_{11} = 0$$

$$P_1 = \frac{1}{2} \frac{|V_1^+|^2}{Z_0} = \frac{1}{2} \frac{10^2}{50} = 1 \rightarrow \boxed{P_1 = 1W}$$

$$a) P_2 = \frac{1}{2} |a_2|^2 (1 - |\Gamma_2|^2)$$

$$P_3 = \frac{1}{2} |a_3|^2 (1 - |\Gamma_3|^2)$$

$$P_2 = P_3 = \frac{1}{2} |a_2|^2 = \frac{1}{2} \frac{|V_2^+|^2}{Z_0} = \frac{5^2}{2 \cdot 50}$$

$$\boxed{P_2 = P_3 = \frac{1}{4} W}$$

$$a_2 = \frac{V_2^+}{\sqrt{Z_0}}$$

$$a_3 = \frac{V_3^+}{\sqrt{Z_0}}$$

$$a_2 = a_3$$

$$V_2^+ = V_3^+$$

$$\Gamma_2 = \frac{b_2}{a_2} = S_{22} = 0$$

$$\Gamma_3 = \frac{b_3}{a_3} = S_{33} = 0$$

g)

$$P_1 = P_{\text{loss}} + P_2 + P_3 \rightarrow P_{\text{loss}} = P_1 - P_2 - P_3 = 1 - \frac{1}{4} - \frac{1}{4}$$

$$\boxed{P_{\text{loss}} = \frac{1}{2} W}$$

Problem 2

We have the next conditions

$$5 \text{ GHz} = f_{101} = \frac{c}{2} \sqrt{\left(\frac{1}{a}\right)^2 + \left(\frac{1}{d}\right)^2}$$

$$6.5 \text{ GHz} = f_{102} = \frac{c}{2} \sqrt{\left(\frac{1}{a}\right)^2 + \left(\frac{2}{d}\right)^2}$$

$$7.2 \text{ GHz} = f_{011} = \frac{c}{2} \sqrt{\left(\frac{1}{b}\right)^2 + \left(\frac{1}{d}\right)^2}$$

$$a) \quad \frac{4}{c^2} f_{101}^2 = \frac{1}{a^2} + \frac{1}{d^2} \rightarrow \frac{1}{a^2} = \frac{4}{c^2} f_{101}^2 - \frac{1}{d^2}$$

$$a) \quad \frac{4}{c^2} f_{102}^2 = \frac{1}{a^2} + \frac{4}{d^2} \Rightarrow \frac{1}{a^2} = \frac{4}{c^2} f_{102}^2 - \frac{4}{d^2}$$

$$\frac{4}{c^2} f_{101}^2 - \frac{1}{d^2} = \frac{4}{c^2} f_{102}^2 - \frac{4}{d^2}$$

$$\frac{4}{c^2} f_{101}^2 - \frac{4}{c^2} f_{102}^2 = \frac{1}{d^2} - \frac{4}{d^2}$$

$$\frac{1}{d^2} = \frac{4}{c^2} (f_{102}^2 - f_{101}^2) \rightarrow \boxed{d = 0,0361 \text{ m}}$$

$$a) \quad \boxed{a = 0,0539 \text{ m}}$$

$$\bullet) \frac{1}{b^2} = \frac{4}{c^2} \cdot f_{011}^2 - \frac{1}{d^2}$$

$$b = 0,0255 \text{ m}$$


Problem 3

(4)

Attenuator [S] matrix

$$[S] = \begin{bmatrix} 0 & \alpha \\ \alpha & 0 \end{bmatrix}$$

For T configuration

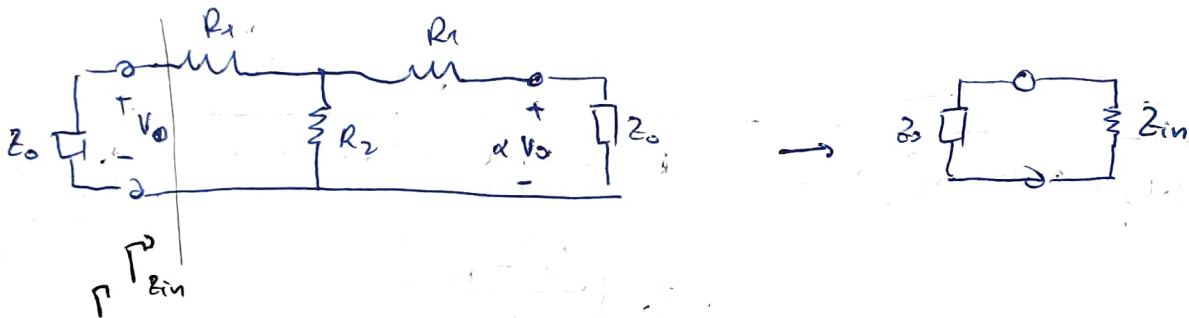

$$Z_{in} = R_1 + R_2 \parallel R_1 + Z_0 = R_1 + \frac{R_2 (R_1 + Z_0)}{Z_0 + R_1 + R_2}$$

$$\Gamma = S_{11} = 0 = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} \Rightarrow 0 \quad Z_{in} - Z_0 = 0$$

$$R_1 (Z_0 + R_1 + R_2) + R_2 (R_1 + Z_0) - Z_0 (Z_0 + R_1 + R_2) = 0$$

$$R_1^2 + R_1 R_2 + \cancel{R_1 Z_0} + R_1 R_2 + \cancel{R_2 Z_0} - Z_0^2 - \cancel{R_1 Z_0} - \cancel{R_2 Z_0} = 0$$

$$2 R_1 R_2 = Z_0^2 - R_1^2 \rightarrow$$

$$R_2 = \frac{Z_0^2 - R_1^2}{2 R_1}$$

$$S_{2,1} = \alpha = \frac{Z_0}{Z_0 + R_1} \cdot \frac{R_2 \parallel (R_1 + Z_0)}{R_2 \parallel (R_1 + Z_0) + R_1} =$$

$$= \frac{Z_0}{Z_0 + R_1} \cdot \frac{R_2 (R_1 + Z_0)}{Z_0 + R_1 + R_2} \cdot \frac{1}{\frac{R_2 (R_1 + Z_0)}{Z_0 + R_1 + R_2} + R_1} =$$

$$= \frac{Z_0}{(\cancel{Z_0 + R_1})} \cdot \frac{R_2 (\cancel{R_1 + Z_0})}{(\cancel{Z_0 + R_1 + R_2})} \cdot \frac{(\cancel{Z_0 + R_1 + R_2})}{R_2 (R_1 + Z_0) + R_1 (Z_0 + R_1 + R_2)} =$$

$$= \frac{Z_0 R_2}{R_1 R_2 + Z_0 R_2 + Z_0 R_1 + R_1^2 + R_1 R_2} = \frac{Z_0 R_2}{R_1^2 + 2 R_1 R_2 + Z_0 R_1 + Z_0 R_2} =$$

↳ previous cond

$$= \frac{Z_0 R_2}{Z_0^2 + Z_0 (R_1 + R_2)} = \frac{R_2}{Z_0 + R_1 + R_2}$$

$$\alpha (Z_0 + R_1 + R_2) = R_2$$

$$\alpha (Z_0 + R_1) = R_2 (1 - \alpha)$$

$$R_1 = \frac{R_2}{\alpha} (1 - \alpha) - Z_0 = \frac{Z_0^2 - R_1^2}{2 R_1 \alpha} (1 - \alpha) - Z_0$$

$$R_1^2 = \frac{(Z_0^2 - R_1^2)(1 - \alpha)}{2\alpha} - R_1 Z_0 = \frac{1}{2\alpha} [Z_0^2 - Z_0^2 \alpha - R_1^2 + R_1^2 \alpha]$$

$$2\alpha R_1^2 = Z_0^2 (1 - \alpha) + R_1^2 (\alpha - 1) \rightarrow R_1^2 (2\alpha - \alpha + 1) = Z_0^2 (1 - \alpha)$$

~~Ans~~

→

$$R_1^2 = Z_0^2 \frac{1-\alpha}{1+\alpha}$$

$$R_1 = Z_0 \sqrt{\frac{1-\alpha}{1+\alpha}}$$

So we get:

$$\left[R_1 = Z_0 \sqrt{\frac{1-\alpha}{1+\alpha}} \quad R_2 = \frac{Z_0^2 - R_1^2}{2R_1} \right]$$

$$Z_0 = 50 \Omega$$

$$\alpha = -3 \text{ dB} \rightarrow \alpha = 0,708$$

$$R_1 = 20,67 \Omega$$

$$R_2 = 50,14 \Omega$$

$$\bullet) \alpha = -10 \text{ dB} \rightarrow \alpha = 0,316$$

$$R_1 = 36,05 \Omega$$

$$R_2 = 16,66 \Omega$$

$$\bullet) \alpha = -20 \text{ dB} \rightarrow \alpha = 0,1$$

$$R_1 = 45,23 \Omega$$

$$R_2 = 5,022 \Omega$$

For π configuration

⑥

$$\Gamma = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = 0 \Rightarrow R_1^2 R_2 - 2 R_1 Z_0^2 - R_2 Z_0^2 = 0$$

$$R_2 = \frac{2 R_1 Z_0^2}{R_1^2 - Z_0^2}$$

$$\begin{aligned} S_{21} &= \alpha \frac{\frac{R_1 Z_0}{R_1 + Z_0}}{\frac{R_1 Z_0}{R_1 + Z_0} + R_2} = \frac{\frac{Z_0 R_1}{Z_0 + R_1}}{\frac{Z_0 R_1 + R_1 R_2 + Z_0 R_2}{Z_0 + R_1}} = \frac{-Z_0 R_1}{Z_0 R_1 + R_1 R_2 + Z_0 R_2} \\ &= \frac{Z_0 R_1}{Z_0 R_1 + R_2 (R_1 + Z_0)} \end{aligned}$$

$$\alpha Z_0 R_1 + \alpha R_2 (R_1 + Z_0) = Z_0 R_1$$

$$R_2 \alpha (Z_0 + R_1) = Z_0 R_1 (1 - \alpha)$$

$$R_2 = \frac{Z_0 R_1 (1 - \alpha)}{\alpha (Z_0 + R_1)}$$

$$\Rightarrow \frac{2 R_1 Z_0^2}{(Z_0 + R_1)(R_1 - Z_0)} = \frac{Z_0 R_1 (1 - \alpha)}{\alpha (Z_0 + R_1)} \Rightarrow \frac{2\alpha}{1 - \alpha} + Z_0 = R_1$$

So:

$$R_1 = Z_0 + \frac{2\alpha}{1-\alpha}$$

$$R_2 = \frac{2R_1 Z_0}{R_1^2 - Z_0^2}$$

a) $\alpha = -3 \text{ dB} = 0,708$

$$R_1 = 54,85 \Omega$$

$$R_2 = 16,37 \text{ k}\Omega$$

b) $\alpha = -10 \text{ dB} = 0,316$

$$R_1 = 50,92 \Omega$$

$$R_2 = 78,3 \text{ k}\Omega$$

c) $\alpha = -20 \text{ dB} = 0,1$

$$R_1 = 50,22 \Omega$$

$$R_2 = 320 \text{ k}\Omega$$

Problem 4

a) First: Constant-K T section

$$L = \frac{R_0}{2\omega_c} = \frac{R_0}{4\pi f_c} = \frac{75}{4\pi \cdot 50 \cdot 10^6} = 119,4 \text{ nH}$$

$$C = \frac{1}{2\omega_c R_0} = \frac{1}{4\pi \cdot 50 \cdot 10^6 \cdot 75} = 21,22 \text{ pF}$$

a) Second: m-derived T section

$$m = \sqrt{1 - \left(\frac{\omega_p}{\omega_c}\right)^2} = 0,28$$

$$\frac{2C}{m} = 151,6 \text{ pF}$$

$$\frac{4mC}{1-m^2} = 25,8 \text{ pF}$$

$$\frac{L}{m} = 426,4 \text{ nH}$$

a) Third: Bisected- π matching section

$$m = 0,6$$

$$\frac{2L}{m} = 398 \text{ nH}$$

$$\frac{2mC}{1-m^2} = 39,8 \text{ pF}$$

$$\frac{2C}{m} = 70,73 \text{ pF}$$