


# MICROWAVE ENGINEERING

Lecture 21:

Microwave Networks  
Problems



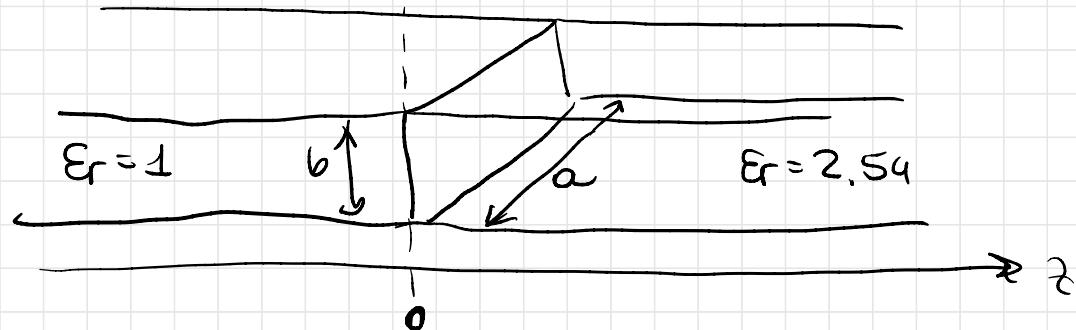① Consider a rectangular waveguide in the x-band ( $a = 2.286 \text{ cm}$  and  $b = 1.016 \text{ mm}$ ) filled with air for  $z < 0$  and Rexolite ( $\epsilon_r = 2.54$ ) for  $z > 0$ . If the operating frequency is  $f = 10 \text{ GHz}$  calculate, using an equivalent TL model, the reflection coefficient of a TE<sub>10</sub> wave at the interface.





Calculate the propagation constant in the two regions for TE<sub>10</sub> wave:

$$f_{air} = \sqrt{k_0^2 - \left(\frac{\pi}{a}\right)^2} = \sqrt{\left(\frac{2\pi f}{c}\right)^2 - \left(\frac{\pi}{a}\right)^2} = 158 \text{ m}^{-1}$$

$$k_0 = \frac{2\pi f}{c} = \frac{2\pi \cdot 10 \cdot 10^9}{3 \cdot 10^8} = 209.4 \text{ m}^{-1}$$

$$f_d = \sqrt{\epsilon_r k_0^2 - \left(\frac{\pi}{a}\right)^2} = 304.1 \text{ m}^{-1}$$

2.54

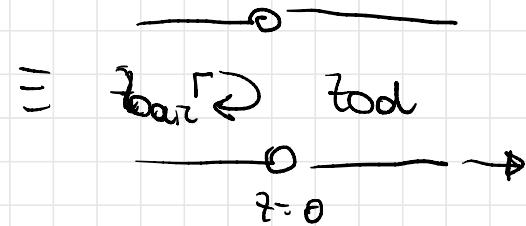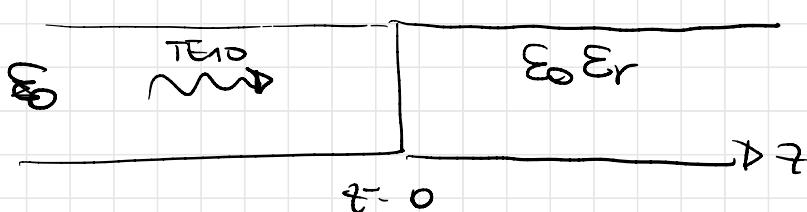

For a rectangular waveguide  $Z_{TE} = \frac{k\eta}{\beta}$


$$Z_{0\text{air}} = \frac{k_0\eta_0}{\beta_{\text{air}}} = \frac{(209.4)(377)}{158} = 500 \Omega$$

$$Z_{0d} = \frac{k_0\eta_0}{\beta_d} = \frac{(209.4)(377)}{304.1} = 259.6 \Omega$$

The reflection coefficient:

$$\Gamma = \frac{Z_{0d} - Z_{0\text{air}}}{Z_{0d} + Z_{0\text{air}}} = -0.316$$


② Where the TL analogy fails!

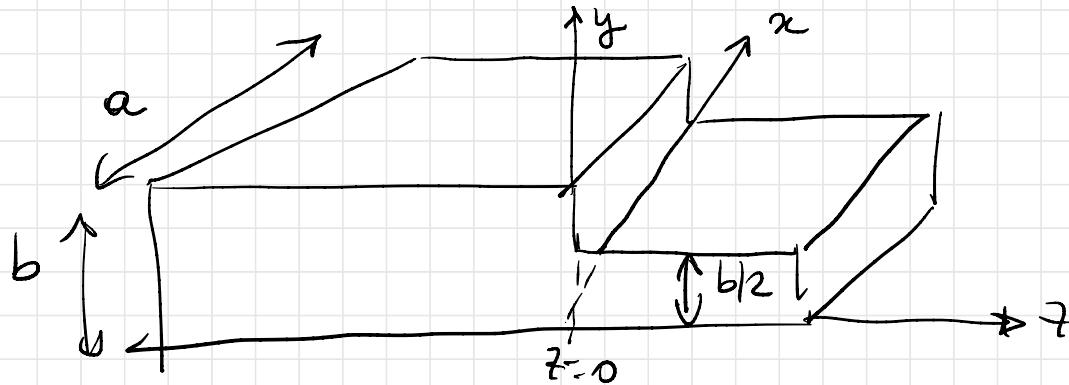

Consider the reflection of a  $T_{010}$  mode incident from  $z < 0$  at a step change in height of a rectangular waveguide.

What  $\Gamma$  do we get by using the TL approach? Is that correct?

Using the TL analogy

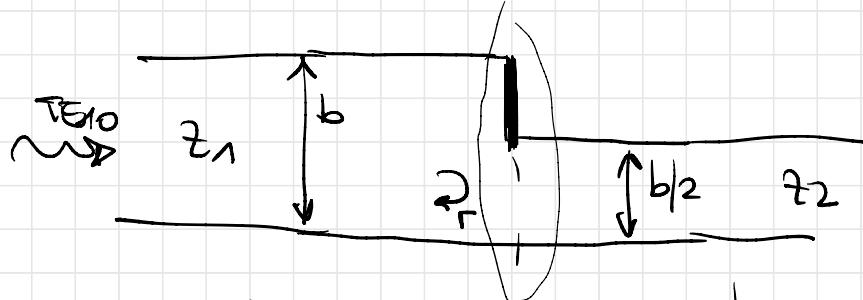

$$z_1 = \frac{k_0 m_0}{\beta_1}$$

$$z_2 = \frac{k_0 m_0}{\beta_2}$$

$$\Gamma = \frac{z_2 - z_1}{z_2 + z_1}$$

$$\beta_1 = \beta_2 = \sqrt{k_0^2 - \left(\frac{\pi}{a}\right)^2}$$


for  $T_{10}$

It's easy to conclude that  $\Gamma = 0$ .

That's not correct!

We must consider that at the interface only  $T_{10}$  is reflected!

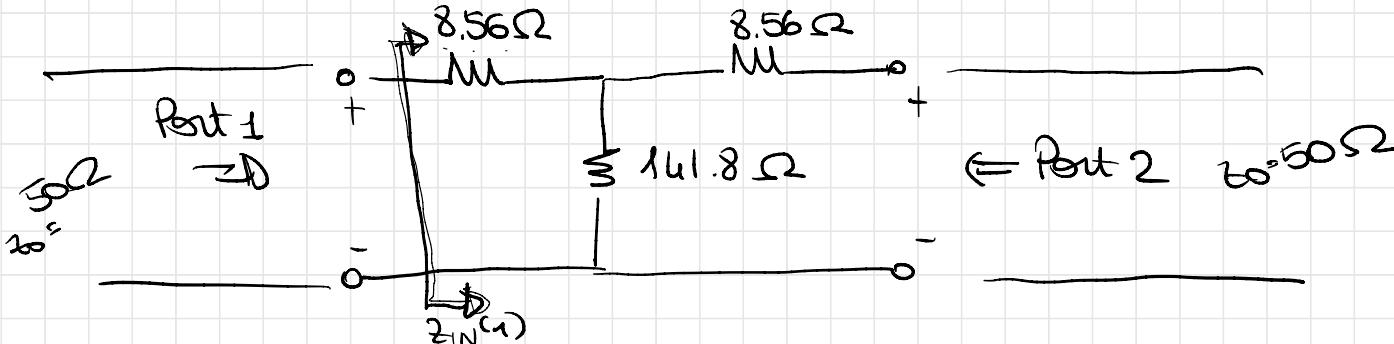③ Find the S parameters of the 3dB Attenuator:



The S matrix for a 2 port system is:

$$\begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix}$$

$$S_{ij} = \left. \frac{V_i^-}{V_j^+} \right|_{\substack{V_K^+ = 0 \\ K \neq j}}$$

$$S_{11} = \frac{V_1^-}{V_1^+} \Big|_{V_2^+ = 0} = \Gamma^{(1)} \Big|_{V_2^+ = 0} = \frac{z_{IN}^{(1)} - z_0}{z_{IN}^{(1)} + z_0}$$


$$z_{IN}^{(1)} = 8.56 + \frac{141.8 (8.56 + 50)}{141.8 + 8.56 + 50} = 50 \Omega$$

$$S_{11} = \Gamma^{(1)} = 0$$

$$S_{22} = \Gamma^{(2)} = 0 \quad \text{for symmetry}$$

$$S_{21} = S_{12} = \frac{V_2^-}{V_1^+} \Big|_{V_2^+ = 0}$$

$$z_0 = 50 \Omega$$

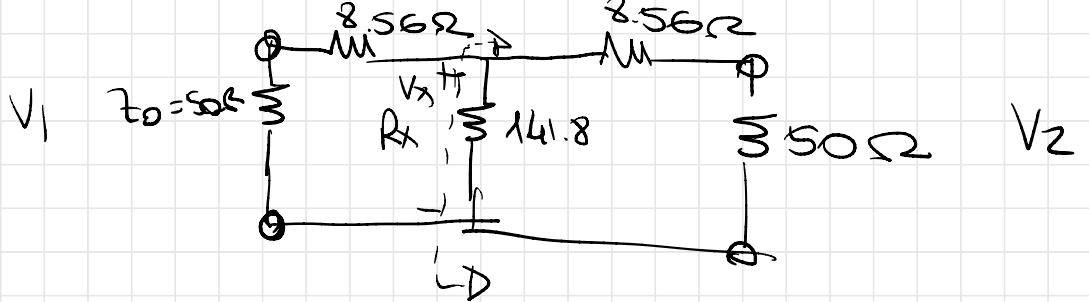

$$V_2 = \frac{50}{50 + 8.56} V_x$$

$$V_x = \frac{R_x}{R_x + 8.56} V_1$$

$$R_x = \frac{141.8 (8.56 + 50)}{141.8 + 8.56 + 50} = 41.44 \Omega$$

$$V_2 = \frac{50}{50 + 8.56} \cdot \frac{41.44}{41.44 + 8.56} V_1 \Rightarrow$$

$$S_{21} = \frac{V_2}{V_{1+}} = 0.707 = S_{12}$$


We can verify this is a 3dB attenuator:

If my input power is  $\frac{|V_1+R|^2}{270}$  then the output power is:

$$\frac{|V_2^-|^2}{270} = \frac{|S_{21}|^2 |V_1+R|^2}{270} = \frac{|S_{21}|^2}{270} |V_1+R|^2 = \frac{|V_1+R|^2}{420}$$

↓  
Is  $\frac{1}{2}$  of the  
input power?  
(-3dB)

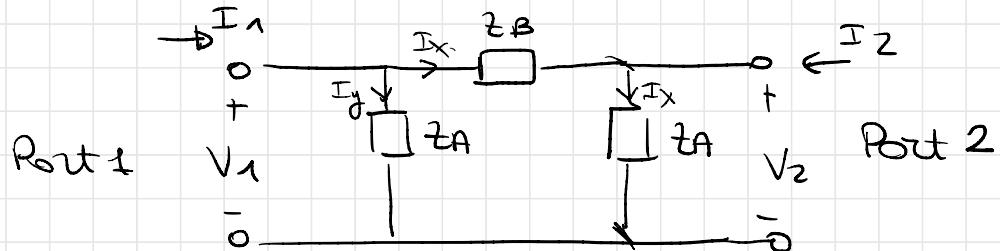4) Derive the impedance matrix for the following 2-port network



The impedance Matrix

$$[V] = [Z][I]$$

$$z_{ij} = \frac{V_i}{I_j} \quad \left| \begin{array}{l} I_k = 0 \\ k \neq i, j \end{array} \right.$$

$$\underline{\underline{z}}_{11} = \frac{V_1}{I_1} \quad \left| \begin{array}{l} I_2 = 0 \end{array} \right. = \frac{V_1}{\frac{V_1}{\frac{Z_A (Z_A + Z_B)}{2Z_A + Z_B}}} = \boxed{\frac{Z_A (Z_A + Z_B)}{2Z_A + Z_B}} = \underline{\underline{z}}_{22}$$

for symmetry

$$z_{21} = \left| \begin{array}{l} V_2 \\ I_1 \end{array} \right| \Big|_{I_2=0}$$

$$V_2 = z_A I_x$$

$$V_1 = I_x (z_B + z_A) = I_y z_A$$

$$I_x = \frac{z_A}{z_A + z_B} I_y$$

$$\underbrace{I_x + I_y = I_1}_{\boxed{I_x + I_y = I_1}}$$

$$I_1 = I_y \left( 1 + \frac{z_A}{z_B + z_A} \right)$$

$$z_{21} = \frac{V_2}{I_1} = \frac{z_A \left[ \frac{z_A}{z_A + z_B} \right] I_y}{I_y \left( 1 + \frac{z_A}{z_A + z_B} \right)} = \boxed{\frac{z_A^2}{2z_A + z_B}} = z_{12}$$

⑤ A four-port network has the following S matrix :

$$[S] = \begin{bmatrix} 0.1 \angle 90^\circ & 0.8 \angle -45^\circ & 0.3 \angle -45^\circ & 0 \\ 0.8 \angle 45^\circ & 0 & 0 & 0.4 \angle 45^\circ \\ 0.3 \angle -45^\circ & 0 & 0 & 0.6 \angle -45^\circ \\ 0 & 0.4 \angle 45^\circ & 0.6 \angle -45^\circ & 0 \end{bmatrix}$$

a) Is this network lossless?

$$|S_{11}|^2 + |S_{12}|^2 + |S_{13}|^2 + |S_{14}|^2 = 1 ?$$

$$|0.1|^2 + |0.8|^2 + |0.3|^2 = 0.74 \neq 1$$

No Network is LOSSY!

- b) Is the network reciprocal? Yes, S matrix is symmetric
- c) What is the return loss at port 1 if all other ports are matched?
- $$\Gamma = S_{11} \Rightarrow RL = -20 \log |\Gamma| = -20 \log (0.1) = 20 \text{ dB}$$
- d) What is the insertion loss between ports 2 and 4 when all other ports are terminated with matched loads?
- $$IL = -20 \log |S_{42}| = -20 \log (0.4) = 8 \text{ dB}$$
- e) What is the reflection coeff. at port 1 if a short circuit is placed at the terminal plane of port 3 and all other ports are matched.

If we place a SC at port 3 and match other ports

$$V_2^+ = V_4^+ = 0 \quad V_3^+ = -V_3^-$$



$$[S] = \begin{bmatrix} 0.1 \angle 90^\circ & 0 & 0.3 \angle -45^\circ & 0 \\ 0 & 0 & 0 & 0 \\ 0.3 \angle -45^\circ & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix}$$

$$\Gamma^{(1)} = \frac{V_1^-}{V_1^+}$$


$$\begin{aligned} V_1^- &= S_{11} V_1^+ + S_{13} V_3^+ = \\ &= S_{11} V_1^+ - \underline{S_{13} V_3^-} \end{aligned}$$

$$V_3^- = S_{31} V_1^+$$

$$V_1^- = S_{11} V_1^+ - S_{13} S_{31} V_1^+$$

$$\Gamma^{(1)} = \frac{(S_{11} - S_{13} S_{31}) V_1^+}{V_1^+}$$

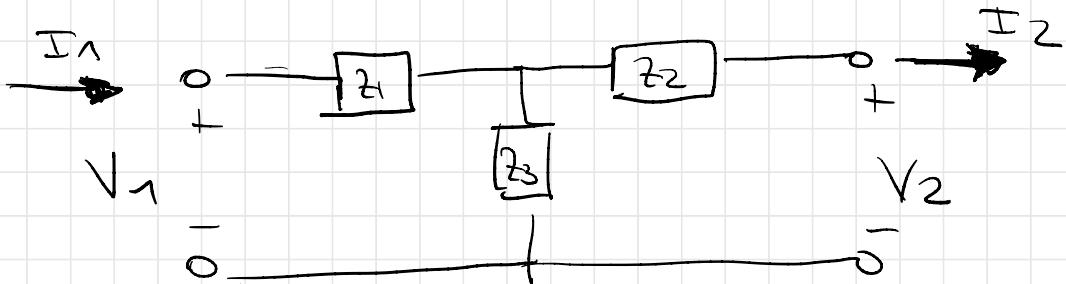⑦ Calculate the ABCD entries for the following circuit:



$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

$$A = \frac{V_1}{V_2} \Big|_{I_2=0} = \frac{\cancel{J_1}(Z_1 + Z_3)}{\cancel{J_1} Z_3} = 1 + \frac{Z_1}{Z_3}$$


$$B = \left. \frac{V_1}{I_2} \right|_{V_2=0} = \frac{I_1 \left( z_1 + \frac{z_2 z_3}{z_2 + z_3} \right)}{I_1 - \frac{z_3}{z_2 + z_3}} =$$

$$= \frac{z_2 z_1 + z_3 z_1 + z_2 z_3}{z_3} = z_1 + z_2 + \frac{z_1 z_2}{z_3}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{\cancel{\frac{V_1}{z_1 + z_3}}}{\cancel{\frac{V_1}{z_1 + z_3}}} = \frac{1}{z_3}$$

$$D = \left. \frac{I_1}{I_2} \right|_{V_2=0} = \frac{\cancel{I_1}}{I_1 \frac{\cancel{z_3}}{z_2 + z_3}} = \frac{z_2 + z_3}{z_3} = 1 + \frac{z_2}{z_3}$$

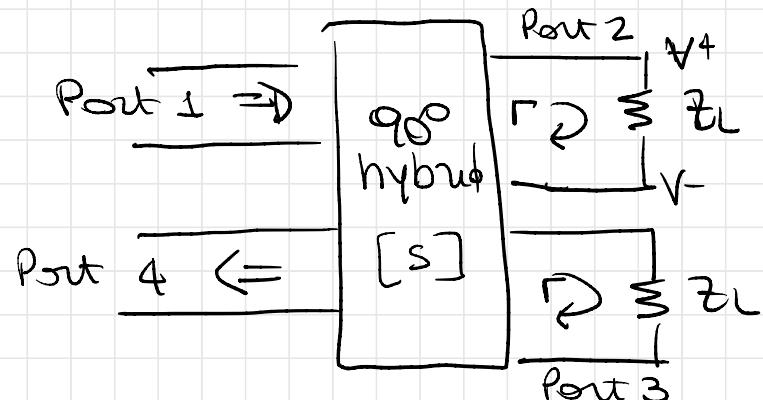8) A variable attenuator can be implemented with equal but adjustable loads. Using the S matrix for the coupler, show that the transmission coeff. even between port 1 and port 4 is  $j\Gamma$ , with  $\Gamma$  reflection coefficient of the mismatch at ports 2 and 3.



$$[S] = -\frac{1}{\sqrt{2}} \begin{bmatrix} 0 & j & 1 & 0 \\ j & 0 & 0 & 1 \\ 1 & 0 & 0 & j \\ 0 & j & -j & 0 \end{bmatrix}$$

Transmission from port 1 to port 4 is  $T = \frac{V_4}{V_1}$

$$T = \frac{V_4^-}{V_1^+} = \frac{1}{V_1^+} \left( -\frac{1}{\sqrt{2}} \right) (V_2^+ + j V_3^+)$$

$$V_2^+ = \Gamma V_2^-$$

$$V_3^+ = \Gamma V_3^-$$

$$\Rightarrow T = \frac{1}{V_1^+} \left( -\frac{1}{\sqrt{2}} \right) [ \Gamma V_2^- + j \Gamma V_3^- ]$$

$$V_2^- = -\frac{1}{\sqrt{2}} j V_1^+ ]$$

$$V_3^- = -\frac{1}{\sqrt{2}} V_1^+ ]$$

$$(T) = \frac{1}{V_1^+} \left( -\frac{1}{\sqrt{2}} \right) \left( -\frac{1}{\sqrt{2}} \right) [ \Gamma j V_1^+ + j \Gamma V_1^+ ] = \frac{1}{2} 2j \Gamma = j \Gamma$$

