

Exam: Basics of active and nonlinear electronics (SEM Mixer)

January 8, 2020


The following nonlinear device NL is used to design a SEM up-converter where the LO voltage signal V_1 is applied to the input while the IF voltage signal V_2 is applied to the output so that the output current I_{OUT} is generated with all its frequency components.



The nonlinear operation of this device (NL) is expressed by the following equation that gives the output current I_{OUT} as a function of input and output control voltages V_1 and V_2 :

$$I_{OUT} = p V_1^3 - q V_2 + r V_1 V_2 \quad (\text{eq1}) \quad \text{where } p, q \text{ and } r \text{ are constants}$$

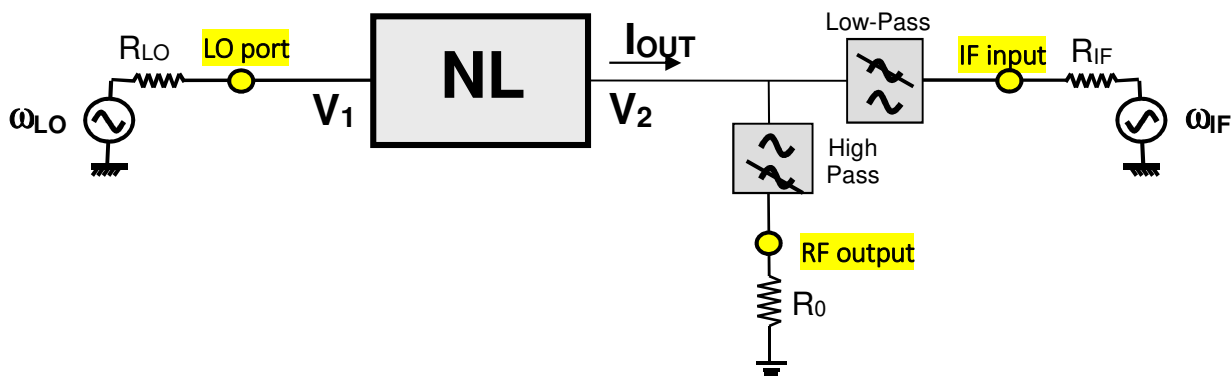The SEM cold-FET mixer is shown below and the main frequencies are $f_{LO} = 9 \text{ GHz}$ and $f_{IF} = 0.5 \text{ GHz}$



The two control voltages V_1 and V_2 are:

○ LO voltage: $V_1 = V_{LO} \cos(\omega_{LO} t)$ (eq2)

○ IF voltage: $V_2 = V_{IF} \cos(\omega_{IF} t)$ (eq3)

- Using equations 1 to 3, express the output current I_{OUT} as a function of signal magnitudes (V_{LO} , V_{IF}), nonlinearity constants (p , q , r) and mixing frequencies. The following notations can be used for mixing frequencies: $\omega_{RF} = (\omega_{LO} + \omega_{IF})$; $\omega_{IM} = (\omega_{LO} - \omega_{IF})$
- The high-pass filter is designed to reject frequencies lower than 5GHz while the low-pass frequency is designed to cut frequencies greater than 5GHz. Therefore, what are the mixing frequencies at the RF output port?
- Determine the expression of the voltage conversion gain G_{CV} .
- If the LO port is assumed to be matched to R_{LO} ,
 - express the LO-to-RF isolation in dB
 - what is the LO-to-IF isolation ?
 - express the equivalent impedance Z_{IN} seen by the IF generator @ ω_{IF} at the IF input port
 - express the required value of R_{IF} to match the IF input port?