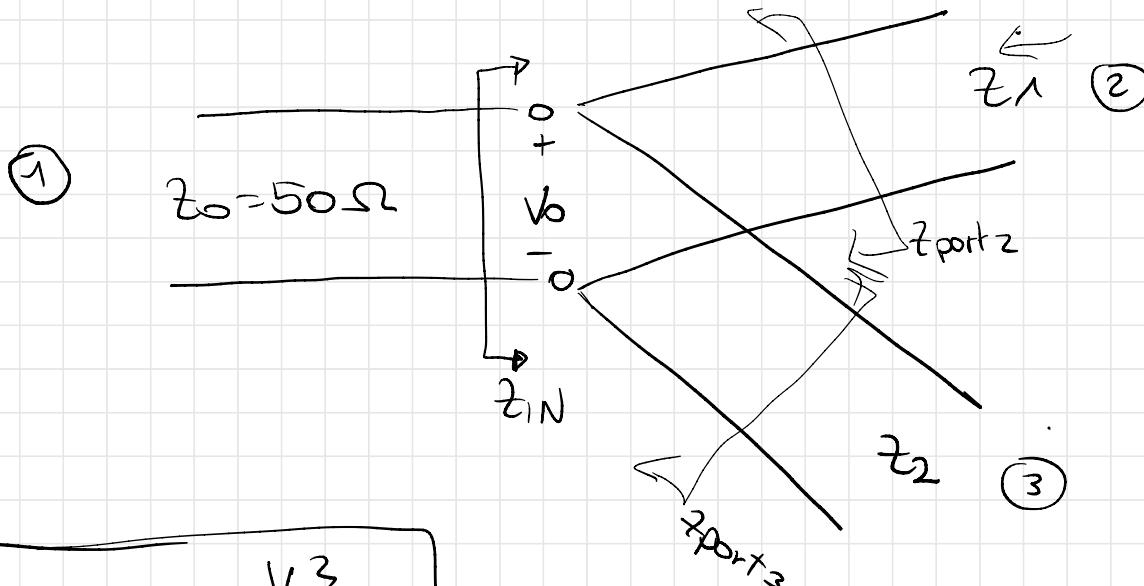


# MICROWAVE ENGINEERING

Lecture 26:  
Problems on power  
dividers and  
combiners

Problem 1 A lossless T-Junction power divider has a source impedance of  $50\Omega$ . Find the output impedances so that  $P_{IN}$  is divided in a 2:1 ratio. Calculate the reflection coefficients at the output ports.



$$P_{IN} = \frac{1}{2} \frac{V_0^2}{z_0}$$

If we want a 2:1 ratio

$$P_1 = \frac{1}{2} \frac{V_0^2}{Z_1}$$

$$\Rightarrow P_2 = 2P_1 = \frac{V_0^2}{Z_1}$$

$$P_2 = \frac{1}{2} \frac{V_0^2}{Z_1}$$

$$P_{IN} = P_1 + P_2 = \frac{1}{2} \frac{V_0^2}{Z_1} + \frac{V_0^2}{Z_1} = \frac{3}{2} \frac{V_0^2}{Z_1}$$

but

$$P_{IN} = \frac{1}{2} \frac{V_0^2}{Z_0}$$

$$\frac{1}{2} \frac{V_0^2}{Z_0} = \frac{3}{2} \frac{V_0^2}{Z_1}$$

$$\Rightarrow Z_1 = 3Z_0 = 150\Omega$$

$$P_2 = \frac{1}{2} \frac{V_o^2}{Z_2} = 2P_1 = \frac{V_o^2}{Z_1} \Rightarrow Z_1 = 2Z_2 \Rightarrow \boxed{Z_2 = 75\Omega}$$

$$Z_{IN} = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{75 \cdot 150}{75 + 150} = 50 \Omega \quad \text{Matched with the input line}$$

looking into port ② our  $Z_{Port\ 2} = \frac{50 \cdot 75}{50 + 75} = 30 \Omega$

looking into port ③  $Z_{Port\ 3} = \frac{50 \cdot 150}{50 + 150} = 37.5 \Omega$


The reflection coefficients at ports 2 and 3 are:

$$\Gamma_{\text{port}2} = \frac{30 - 150}{30 + 150} = -0.67$$

$$\Gamma_{\text{port}3} = \frac{37.5 - 75}{37.5 + 75} = -0.33$$

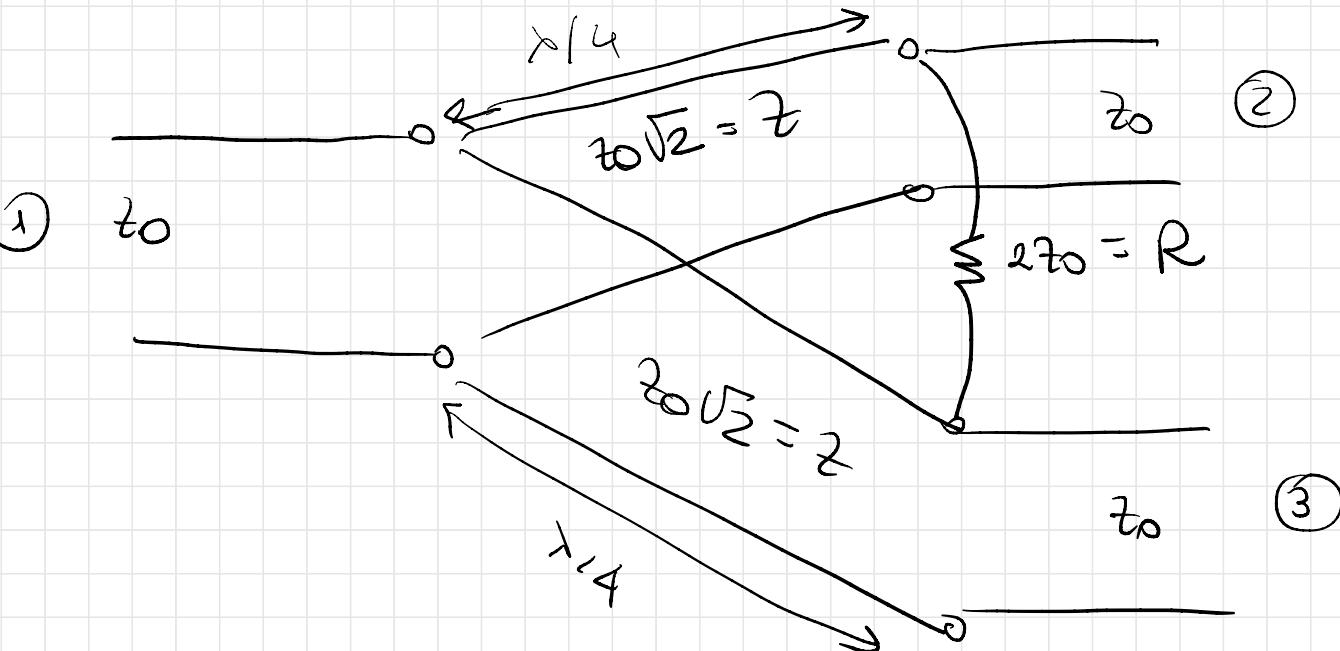Problem 2

Design an equal split Wilkinson power divider for  
50 Ω system impedance at  $f_0 = 5 \text{ GHz}$ .



$$Z = z_0\sqrt{2} = 50\sqrt{2} = 70.7 \Omega$$

$$R = 2z_0 = 100 \Omega$$

$$f = \frac{c}{\lambda} \quad \rightarrow \quad \lambda = \frac{c}{f}$$
$$l = \frac{\lambda}{4} = \frac{c}{4f} = \frac{3 \cdot 10^8}{4 \cdot 5 \cdot 10^9} =$$


$$= 0.015 \text{ m} =$$

$$\underline{1.5 \text{ cm}}$$
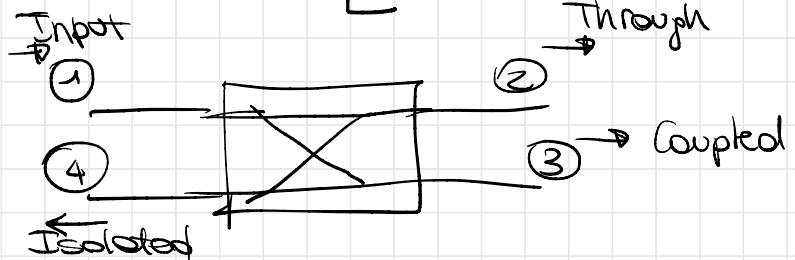
### Problem 3

A directional coupler has the following scattering matrix. Find Directivity, Coupling, Isolation and Return loss at the input port when other ports are terminated with matched loads.

$$[S] = \begin{bmatrix} 0.05 \angle 30^\circ & 0.96 \angle 0^\circ & 0.1 \angle 90^\circ & 0.05 \angle 90^\circ \\ 0.96 \angle 0^\circ & 0.05 \angle 30^\circ & 0.05 \angle 90^\circ & 0.1 \angle 90^\circ \\ 0.1 \angle 90^\circ & 0.05 \angle 90^\circ & 0.04 \angle 30^\circ & 0.96 \angle 0^\circ \\ 0.05 \angle 90^\circ & 0.1 \angle 90^\circ & 0.96 \angle 0^\circ & 0.05 \angle 30^\circ \end{bmatrix}$$



The Directivity is

$$D = 10 \log \frac{P_3}{P_4} = 20 \log \frac{\beta}{|S_{14}|} =$$

$$\beta^2 = |S_{13}|^2$$

coupling factor

$$= 20 \log \left| \frac{S_{13}}{S_{14}} \right| = 20 \log \frac{|0.1|}{|0.05|} = 6 \text{dB}$$

Coupling is:

$$C = 10 \log \frac{P_1}{P_3} = -20 \log \beta = -20 \log |S_{13}| =$$

$$= -20 \log |0.1| = 20 \text{dB}$$

Isolation is:


$$I = 10 \log \frac{P_1}{P_u} = -20 \log |S_{14}| = -20 \log 0.05 \\ = 26 \text{ dB}$$

The return loss:

$$RL = -20 \log |\Gamma| = -20 \log |S_{11}| = -20 \log 0.05 \\ = 26 \text{ dB}$$

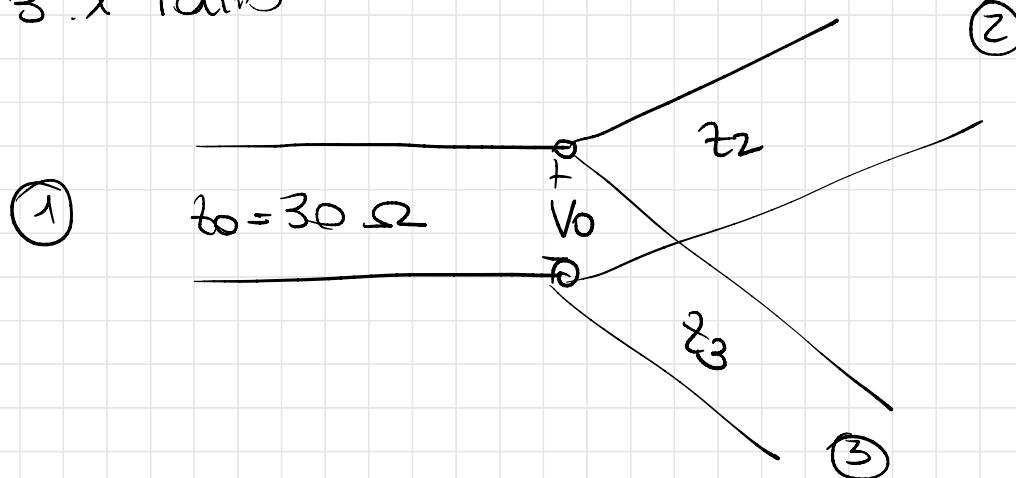Problem 4 Design a lossless T-junction divider with a  $30\ \Omega$  source impedance to give a 3:1 power split. Design quarter-wave matching transformers to convert the impedances of the output lines to  $30\ \Omega$ .

First step we find port 2 and 3 impedances to realize 3:1 ratio



⑤  $z$

$$\frac{P_2}{P_3} = 3$$

$$\begin{cases} P_1 = P_2 + P_3 \\ P_2 = \frac{3}{4} P_1 \quad P_3 = \frac{1}{4} P_1 \end{cases}$$


$$P_1 = \frac{1}{2} \frac{V_0^2}{Z_0}$$

$$P_2 = \frac{1}{2} \frac{V_0^2}{Z_2} = \frac{3}{4} P_1 = \frac{3}{4} \left( \frac{1}{2} \frac{V_0^2}{Z_0} \right) \Rightarrow \frac{1}{Z_2} = \frac{3}{4} \frac{1}{Z_0} \Rightarrow$$

$$\Rightarrow Z_2 = \frac{4}{3} Z_0 = 40\Omega$$

$$P_3 = \frac{1}{2} \frac{V_0^2}{Z_3} = \frac{1}{4} P_1 = \frac{1}{4} \left( \frac{1}{2} \frac{V_0^2}{Z_0} \right) \Rightarrow \frac{1}{Z_3} = \frac{1}{4} \frac{1}{Z_0} \Rightarrow Z_3 = 4Z_0 = 120\Omega$$

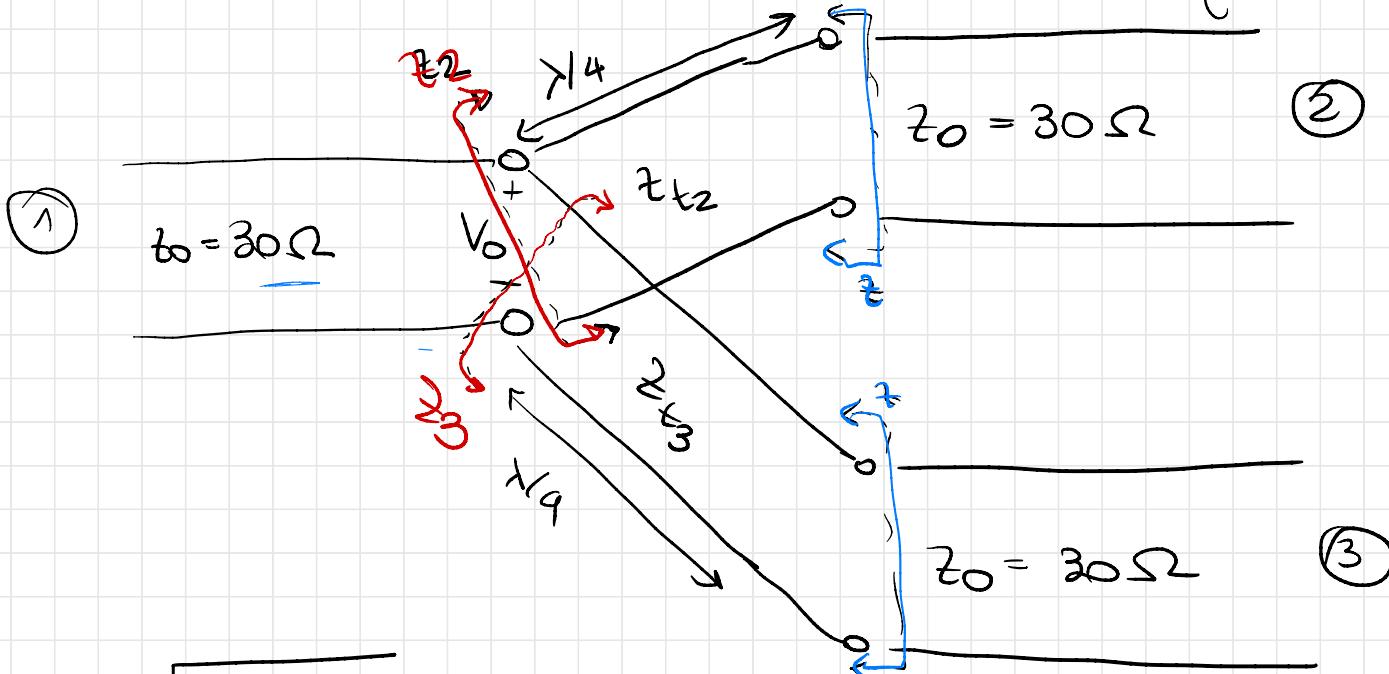If we now want our output port 2 and 3 to be on output lines  $30\Omega$  our circuit need to be changed:




$$z_{t2} = \sqrt{30 \cdot 40} = 34.64 \Omega$$

$$z_{t3} = \sqrt{30 \cdot 120} = 60 \Omega$$

Determine the S parameters magnitude for the circuit.

If we analyze the original network

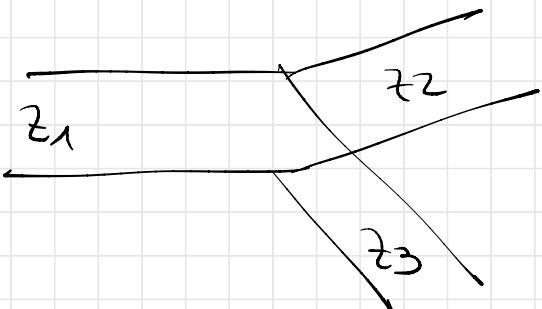

$$Z_1 = 30 \Omega$$

$$Z_2 = 40 \Omega$$

$$Z_3 = 120 \Omega$$

$$|S_{11}| = \begin{vmatrix} Z_2 // Z_3 - Z_1 \\ Z_2 // Z_3 + Z_1 \end{vmatrix} = \begin{vmatrix} 30 - 30 \\ 30 + 30 \end{vmatrix} = 0$$

$$|S_{22}| = \begin{vmatrix} Z_1 // Z_3 - Z_2 \\ Z_1 // Z_3 + Z_2 \end{vmatrix} = \begin{vmatrix} 30 // 120 - 40 \\ 30 // 120 + 40 \end{vmatrix} =$$

$$|S_{33}| = \begin{vmatrix} Z_1 // Z_2 - Z_3 \\ Z_1 // Z_2 + Z_3 \end{vmatrix} = \begin{vmatrix} 40 // 30 - 120 \\ 40 // 30 + 120 \end{vmatrix} = 0.75 \quad 0.25$$

If we analyze the modified network :

$$|S_{11}| = \left| \frac{z_2/z_3 - z_1}{z_2/z_3 + z_1} \right| = \phi$$

$$|S_{22}| = \left| \frac{z - 30}{z + 30} \right| = \left| \frac{50 - 30}{50 + 30} \right| = 0.25$$

$$z = \frac{z_{t_2}}{z_1/z_3} = \frac{\frac{30 \cdot 160}{30 \cdot 120}}{\frac{30 + 120}{3}} = \frac{150}{3} = 50$$

$$|S_{33}| = \left| \frac{z - 30}{z + 30} \right| = \left| \frac{210 - 30}{210 + 30} \right| = \left| \frac{180}{240} \right| = 0.75$$

$$z = \frac{z_1 z_2}{z_1 + z_2} = \frac{30 \cdot 120}{30 + 40} = 210$$

$$|S_{21}| = |S_{12}| = \left| \sqrt{\frac{P_2}{P_1}} \right| = \sqrt{\frac{3}{4}} = 0.866$$

$$|S_{31}| = |S_{13}| = \left| \sqrt{\frac{P_3}{P_1}} \right| = \sqrt{\frac{1}{4}} = 0.5$$

$S$  matrix is unitary since the network is lossless

$$|S_{21}|^2 + |S_{22}|^2 + |S_{23}|^2 = 1$$

$$\begin{aligned} |S_{23}| &= |S_{32}| = \sqrt{1 - |S_{21}|^2 - |S_{22}|^2} = \\ &= \sqrt{1 - (0.25)^2 - (0.866)^2} = 0.433 \end{aligned}$$

$$|S| = \begin{bmatrix} 0 & 0.866 & 0.5 \\ 0.866 & 0.25 & 0.433 \\ 0.5 & 0.433 & 0.75 \end{bmatrix}$$